



Literature Number: SNAP002

# PLL Fundamentals

Part 2: PLL Behavior

**Dean Banerjee**


# Overview

- General PLL Performance Concepts
  - PLL Loop Theory
  - Lock Time
  - Spurs
  - Phase Noise
- Fractional PLL Performance Concepts
  - Generation of Fractional N Value
  - Fractional N Phase Noise
  - Fractional N Spurs



 
# Derivation of Noise Transfer Functions


- **$G = K\phi \cdot (Kvco/s) \cdot Z(s)$** 
  - $K\phi$  = Charge Pump Gain
  - $Kvco$  = VCO Gain
  - $Z(s)$  = Transfer function of the loop filter
  - Note that  $G$  is a DECREASING function in  $s = j\omega$
- **$H = 1/N$** 
  - Note that  $H$  is a CONSTANT with respect to  $s = j\omega$
- **Transfer functions apply to both phase and frequency**



# Analysis of Transfer Functions

 

# Closed Loop Gain

 


- **Spur Gain Applies more to Integer PLL Phase Noise and Spurs**
- **Roll-Off Applies more to fractional PLL Phase Noise and Spurs**

# Overview

- General PLL Performance Concepts
  - PLL Loop Theory
  - Lock Time
  - Spurs
  - Phase Noise
- Fractional PLL Performance Concepts
  - Generation of Fractional N Value
  - Fractional N Phase Noise
  - Fractional N Spurs

 
# Lock Time

- Indicates the time it takes from an initial to within a tolerance of a final frequency.
  - Depends mainly on Loop Bandwidth
  - Depends on size of frequency switch






# The Impact of Cycle Slipping

 




# The Anatomy of a Cycle Slip

 


- Cycle slip is caused when the phase detector is off by 1 cycle
- Voltage is produced across loop filter resistor R2, which causes the glitch
 
# Impact of $f_{PD}/BW$ Ratio on Cycle Slipping



- Discrete sampling action of phase detector impacts lock time
- $f_{PD}/BW$ 
  - Ratio of phase detector frequency to loop bandwidth
  - As the ratio gets smaller, instability increases
  - As the ratio gets larger, cycle slipping increases

# LMX2485 Cycle Slip Reduction Technique

 

## No Cycle Slip Reduction

- Peak Time = 561  $\mu$ S
- Lock Time = 834  $\mu$ S

## With Cycle Slip Reduction

- Peak Time = 151  $\mu$ S
- Lock Time = 486  $\mu$ S




# Overview

- General PLL Performance Concepts
  - PLL Loop Theory
  - Lock Time
  - **Spurs**
  - Phase Noise
- Fractional PLL Performance Concepts
  - Generation of Fractional N Value
  - Fractional N Phase Noise
  - Fractional N Spurs

# Reference Spurs

- **Undesired Spurious outputs that appear at a spacing of  $F_{PD}$  from the carrier**
- **VCO Tuning Voltage has small AC component**
  - Caused by leakage of the charge pump
  - Caused by mismatched currents of the charge pump
  - Smaller for narrower loop bandwidths
  - Smaller for larger comparison frequencies due to more filtering
- **This AC Voltage causes frequency spurs**
- **By making the Comparison Frequency Larger, thus making  $N$  smaller, these spurs are filtered out more**

# Reference Spur Example

 


# Overview

- General PLL Performance Concepts
  - PLL Loop Theory
  - Lock Time
  - Spurs
  - Phase Noise
- Fractional PLL Performance Concepts
  - Generation of Fractional N Value
  - Fractional N Phase Noise
  - Fractional N Spurs
 
# PLL Noise Sources

- VCO Noise is high pass filtered
- All other noise sources are multiplied by N and low pass filtered
- Charge Pump Noise and VCO Noise tend to dominate







# Noise Transfer Functions

| Source               | Transfer Function   | Low Freq. Approx.             | High Freq. Approx.    | Response Shape |
|----------------------|---|-------------------------------|-----------------------|----------------|
| VCO                  | $\frac{1}{1 + \left[ G(s) \cdot \frac{1}{N} \right]}$                           | $1/G(s),$<br>$ 1/G(s) ^2$     | 1                     | Highpass       |
| Reference Oscillator | $\frac{1}{R} \cdot \frac{G(s)}{1 + \left[ G(s) \cdot \frac{1}{N} \right]}$      | $N/R,$<br>$(N/R)^2$           | $G(s),$<br>$ G(s) ^2$ | Lowpass        |
| R counter            | $\frac{G(s)}{1 + \left[ G(s) \cdot \frac{1}{N} \right]}$                        | $N,$<br>$N^2$                 | $G(s),$<br>$ G(s) ^2$ | Lowpass        |
| N counter            | $\frac{G(s)}{1 + \left[ G(s) \cdot \frac{1}{N} \right]}$                        | $N,$<br>$N^2$                 | $G(s),$<br>$ G(s) ^2$ | Lowpass        |
| Phase Detector       | $\frac{1}{K_\phi} \cdot \frac{G(s)}{1 + \left[ G(s) \cdot \frac{1}{N} \right]}$ | $N/K_\phi,$<br>$(N/K_\phi)^2$ | $G(s),$<br>$ G(s) ^2$ | Lowpass        |



# Noise Transfer Functions

    



# 1 Hz Normalized Phase Noise

- **Good way to characterize the phase noise of a PLL**
- **Assumes Charge Pump Noise is Dominant**
- **Number is deceptive for fractional N parts because it does not take into account the phase noise advantage of having a lower N counter.**
- **$PN_{1Hz} = PN - 20 \cdot \log(N) - 10 \cdot \log(f_{PD})$** 
  - **N = N Counter Value**
  - **$f_{PD}$  = Phase Detector frequency in Hz**
  - **PN = Phase Noise**
- **This number is part specific.**
  - **LMK03001C = -224 dBc/Hz**
  - **LMX2485 = -212 dBc/Hz**
  - **LMX2470/LMX2531 = -212 dBc/Hz**
  - **LMX2541 = -225.4 dBc/Hz**




# Normalized 1/f Noise

- This models the close-in phase noise of the PLL
- Normalized to a 1 GHz Output Frequency
- Normalized to a 10 kHz offset
- Important to consider if the comparison frequency is high
- Number is deceptive for fractional N parts because it does not take into account the phase noise advantage of having a lower N counter.
- $PN_{10kHz} = PN(10kHz) - 20 \bullet \log(F_{out}/1GHz) - 10 \bullet \log(10kHz/Offset)$
- This number is part specific.
  - LMK03001C = -122 dBc/Hz
  - LMX2485 = -104 dBc/Hz
  - LMX2531/LMX2470 = -104 dBc/Hz
  - LMX2541 = -124.5 dBc/Hz


 
# LMX2541 Phase Noise


- VCO Frequency = 3700 MHz
- Phase Detector Frequency = 100 MHz



# Overview

- General PLL Performance Concepts
  - PLL Loop Theory
  - Lock Time
  - Spurs
  - Phase Noise
- Fractional PLL Performance Concepts
  - **Generation of Fractional N Value**
  - Fractional N Phase Noise
  - Fractional N Spurs

# Fractional N Counter

 

- **Allowing N to be fractional allows it to be lower, which results in finer tuning resolution and better noise performance. For more narrow channel spacing, it also can result in lower spurs and faster switching speed.**
- **The denominator of the fractional part of the N counter is called the fractional modulus (5 in this case)**

# Fractional N Implementation



- **Uses Fractional N Averaging**

|            |                   |
|------------|-------------------|
| 900        | First Time        |
| 900        | Second Time       |
| 900        | Third Time        |
| 900        | Fourth Time       |
| <u>901</u> | <u>Fifth time</u> |
| 900.2      | Average Value     |


- **Although the Average Value is correct, compensation is necessary to correct for the instantaneous phase error. This phase error gives rise to fractional spurs. They would be at offsets that are increments of 200 kHz in this example.**
  
# The Need for Compensation

$$\varepsilon = \frac{900.2 - 900}{900.2 \text{ MHz}}$$




# Fractional Compensation Techniques

 

- Current Correction Technique cancels current with another current, but this can be unpredictable, especially over temperature
- Phase Delay Technique corrects with a phase delay at the phase detector, but can add phase noise

# Delta Sigma N Counter

 

Traditional Fractional N: 0, +1


2<sup>nd</sup> Order Delta Sigma Fractional N: -1, 0, 1, 2

3<sup>rd</sup> Order Delta Sigma Fractional N: -7, -6, ... + 8

4<sup>th</sup> Order Delta Sigma Fractional N: -15, -14, ... + 16


- **N counter value is modulated such that the average value is equal to the desired fraction**

# First Order Modulator

 

- $Z^{-1}$  is a one clock cycle delay
- $1 / (1-z^{-1})$  is a summation


# 3<sup>rd</sup> Order Modulator Example

 

# Overview

- General PLL Performance Concepts
  - PLL Loop Theory
  - Lock Time
  - Spurs
  - Phase Noise
- Fractional PLL Performance Concepts
  - Generation of Fractional N Value
  - **Fractional N Phase Noise**
  - Fractional N Spurs

# Delta Sigma Noise Shaping

 

$$Y = X + (1-z^{-1}) * Q = Y = X + N(z) * Q$$

- $N(z) = 1 - z^{-1} = 1 - e^{-j\omega} = 1 - \cos(\omega) + j\sin(\omega)$ ,  $\omega = 2\pi f / f_{PD}$ .
- $|N(z)|^2 = (1 - \cos(\omega))^2 + \sin^2(\omega) = 4 * \sin^2(\pi f / f_{PD})$
- $|N(z)|^2 = |Q(z)|^2 = 4 * \sin^2(\pi f / f_{PD})$

# $\Sigma$ - $\Delta$ Phase Noise


- **The full expression for quantization noise at the synthesizer output:**

$$S_{\phi}(f) = \frac{1}{12} \frac{1}{T_{PD}} \cdot |T_{PD} \cdot G(f)|^2 (2\pi)^2 \left( 2 \cdot \sin\left(\frac{\pi f}{f_{PD}}\right) \right)^{2(n-1)}$$

- **G(f) is PLL lowpass response, so excluding this gives the shaped PSD of the quantization noise alone**


$$S_Q(f) = \frac{1}{12 \cdot f_{PD}} (2\pi)^2 \left( 2 \cdot \sin\left(\frac{\pi f}{f_{PD}}\right) \right)^{2(n-1)}$$

# Delta Sigma Noise

 

- **Excellent agreement with theory at far offsets**
- **Charge Pump causes higher frequency noise to mix down to lower offsets**
- **This close-in noise is relatively consistent for the LMX2485, LMX2531, and LMX2541 families**
  - **2<sup>nd</sup> Order Modulator -105 dBc**
  - **3<sup>rd</sup> Order Modulator -95 dBc**
  - **4<sup>th</sup> Order Modulator -90 dBc**

# Notion of Well-Randomized

 


# Overview

- General PLL Performance Concepts
  - PLL Loop Theory
  - Lock Time
  - Spurs
  - Phase Noise
- Fractional PLL Performance Concepts
  - Generation of Fractional N Value
  - Fractional N Phase Noise
  - Fractional N Spurs




# Primary Fractional Spurs

 

- **Highly Dependent on Fraction**
- **Theory and Measured Data Agree Well for Analog Compensation**
  - Theory involves calculating Fourier series
  - Subtract out a Constant Factor
  - Tracks Roll-off
  - Sort of works the same for Delta-Sigma PLLs



# Sub-Fractional Spurs

 

- Occur at a fraction of the channel spacing



# Sub-Fractional Spurs

- Occur at a sub-multiple of where the fractional spur would be
- Typically less than primary fractional spur
- Impacted a lot by dithering and also the way the fraction is expressed (i.e. 1000/1000000 vs. 1/10)
- Occurrence based on chart below

| ORDER               | Fractional Denominator Factors |                       |                       |                   |
|---------------------|--------------------------------|-----------------------|-----------------------|-------------------|
|                     | No Factor of 2 or 3            | Factor of 2 but not 3 | Factor of 3 but not 2 | Factor of 2 and 3 |
| Integer Mode        | None                           | None                  | None                  | None              |
| 1st Order Modulator | None                           | None                  | None                  | None              |
| 2nd Order Modulator | None                           | Fch/2                 | None                  | Fch/2             |
| 3rd Order Modulator | None                           | Fch/2                 | Fch/3                 | Fch/6             |
| 4th Order Modulator | None                           | Fch/4                 | Fch/3                 | Fch/12            |

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

|                        |  |
|------------------------|--|
| Audio                  | <a href="http://www.ti.com/audio">www.ti.com/audio</a>                               |
| Amplifiers             | <a href="http://amplifier.ti.com">amplifier.ti.com</a>                               |
| Data Converters        | <a href="http://dataconverter.ti.com">dataconverter.ti.com</a>                       |
| DLP® Products          | <a href="http://www.dlp.com">www.dlp.com</a>   |
| DSP                    | <a href="http://dsp.ti.com">dsp.ti.com</a>   |
| Clocks and Timers      | <a href="http://www.ti.com/clocks">www.ti.com/clocks</a>                             |
| Interface              | <a href="http://interface.ti.com">interface.ti.com</a>                               |
| Logic                  | <a href="http://logic.ti.com">logic.ti.com</a>                                       |
| Power Mgmt             | <a href="http://power.ti.com">power.ti.com</a>                                       |
| Microcontrollers       | <a href="http://microcontroller.ti.com">microcontroller.ti.com</a>                   |
| RFID                   | <a href="http://www.ti-rfid.com">www.ti-rfid.com</a>                                 |
| OMAP Mobile Processors | <a href="http://www.ti.com/omap">www.ti.com/omap</a>                                 |
| Wireless Connectivity  | <a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a> |

### Applications

|                               |  |
|-------------------------------|--|
| Communications and Telecom    | <a href="http://www.ti.com/communications">www.ti.com/communications</a>                 |
| Computers and Peripherals     | <a href="http://www.ti.com/computers">www.ti.com/computers</a>                           |
| Consumer Electronics          | <a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>                   |
| Energy and Lighting           | <a href="http://www.ti.com/energy">www.ti.com/energy</a>                                 |
| Industrial                    | <a href="http://www.ti.com/industrial">www.ti.com/industrial</a>                         |
| Medical                       | <a href="http://www.ti.com/medical">www.ti.com/medical</a>                               |
| Security                      | <a href="http://www.ti.com/security">www.ti.com/security</a>                             |
| Space, Avionics and Defense   | <a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a> |
| Transportation and Automotive | <a href="http://www.ti.com/automotive">www.ti.com/automotive</a>                         |
| Video and Imaging             | <a href="http://www.ti.com/video">www.ti.com/video</a>                                   |

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated