

AN-466 Improving the Performance of a High Speed PBX Backplane



Literature Number: SNLA149

Improving The Performance Of A High Speed PBX Backplane

National Semiconductor
 Application Note 466
 Ramiro Calvo
 August 1982



ABSTRACT

This article will provide solutions to performance problems associated with PBX backplanes. Some of these problems are: long settling time, excessive propagation delay, low impedance bus lines, crosstalk, and electromagnetic radiation (EMR). These problems are caused by high output capacitance drivers that use TTL signal levels. National's solution to these problems is the Backplane Transceiver Logic (BTL) family of devices.

INTRODUCTION

To be able to meet the bandwidth and high system reliability requirements of the next generation PBXs, the industry must use parallel, high speed Pulse Code Modulation (PCM) highways. This article will deal with the following problems encountered by these high speed PCM highways.

- Crosstalk
- Power Consumption
- Noise Margin
- Bus Impedance
- Signal Settling Time
- Propagation Delays
- Propagation Delay Skew
- Live Insertion
- Extending A Bus Beyond The Rack
- Bus Termination
- Pin Layout

I. REDUCING CROSSTALK

Crosstalk can reduce the data integrity of the system or even cause a total shutdown. Crosstalk amplitude is proportional to the slew rate, signal swing, and physical layout of the board. To reduce crosstalk, the DS3890/92/98: shrink the standard TTL three volt swing to the Backplane Transceiver Logic (BTL) one volt swing; slow down the rise and fall time to 6 ns; use low pass filters and precision thresholds on the receivers.

II. REDUCING POWER CONSUMPTION

Because of excessive heat dissipation and a mandatory battery backup, power consumption must be kept to a minimum. Low impedance, open collector busses that use TTL signal levels need drivers capable of sinking approximately 300 mA. By using the BTL one volt signal swing, the drivers need only sink 50 mA. Refer to the section **Signal Settling Time** for more details. The reduction in power consumption will enable PBXs to coexist with other office equipment in "normal" office environments.

III. NOISE MARGIN

Noise margins protect the system from crosstalk, ground noise, and external EMR. The magnitude of the absolute noise margin is a good measure of how well protected the system is against external electro magnetic interference (EMI) and ground noise. The relative noise margin is a good measure as to how well protected the system is against crosstalk, assuming most signals within the system have the

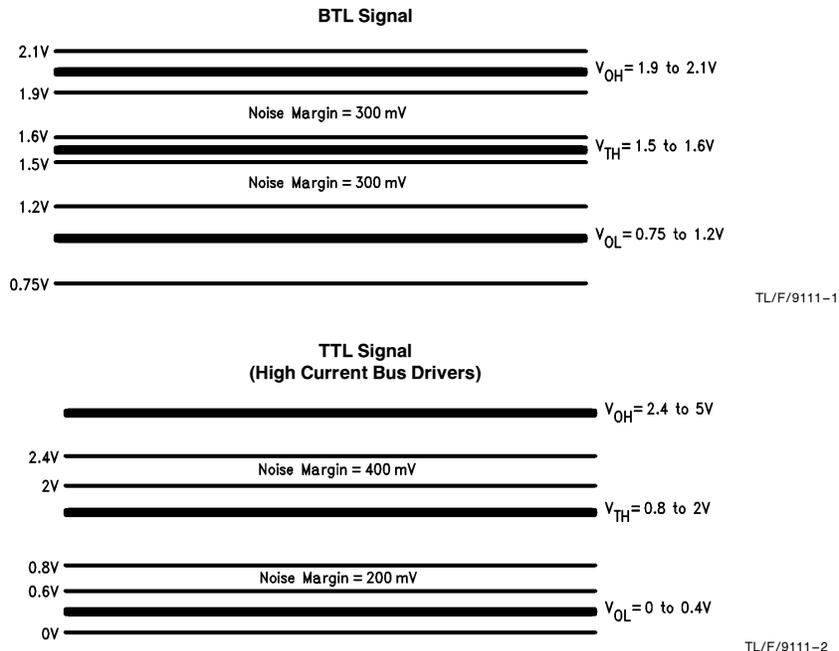


FIGURE 1

same voltage swing. As shown below, BTL signals improve both the absolute and relative noise margins

- Absolute Noise Margin

Despite the smaller signal swing, BTL signals have a 300 mV noise margin, as compared to the 200 or 400 mV guaranteed noise margin in TTL signals (see *Figure 1*). The absolute noise margin is usually not very critical since PBXs are usually well protected from external EMR by the metallic racks.

- Relative Noise Margin

Based on the data sheet guaranteed limits, BTL signals have a 30% [(300 mV absolute noise margin)/(1V signal swing)] relative noise margin, as compared to 7% [(200 mV absolute noise margin)/(3V swing)] in standard TTL signals.

IV. IMPROVING BUS IMPEDANCE

Standard TTL drivers do not have sufficient drive current to drive a heavily loaded backplane. A larger output transistor is needed to increase the drive current. The large TTL output transistor, however, increases the capacitance loading, which decreases the bus impedance, which in turn requires more drive current. The BTL drivers have a Schottky diode in series with the driver transistor's collector. When the driver transistor is off, the diode is reverse biased, which reduces the output capacitance to only 1–2 pF. As shown below, the reduced output capacitance greatly improves the overall bus impedance.

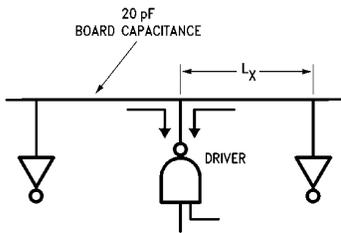


FIGURE 2

TL/F/9111-3

- L_x = Board Spacing = 0.6 in
- L_{foot} = 20 loads per foot
- $C_{x\text{-TTL}}$ = Capacitance per TTL Driver
= Transceiver Capacitance + PC Trace and Connector Capacitance
= 15 pF + 5 pF
= 20 pF per load
- $C_{x\text{-BTL}}$ = Capacitance per BTL Driver
= Driver Capacitance + Receiver Capacitance + PC Trace and Connector Capacitance
= 2 pF + 2 pF + 1 pF + 5 pF
= 10 pF per load
- $C_{L\text{-TTL}}$ = (20 load per foot) \times (20 pF per load)
= 400 pF per Foot
- $C_{L\text{-BTL}}$ = (20 load per foot) \times (10 pF per load)
= 200 pF per Foot
- Unloaded Bus Impedance
- L = Standard PC Board Inductance Per Foot
= 0.2 μ H per foot
- C = Standard PC Board Capacitance Per Foot
= 20 pF per foot

$$Z_O = (L/C)^{1/2}$$

$$= (0.2 \mu\text{H}/20 \text{ pF})^{1/2} = 100\Omega$$

- Loaded Bus Impedance (for a uniform capacitive loading C_x spaced at equal intervals)

$$Z_L = Z_O/(1 + C_L/C)^{1/2}$$

$$Z_{L\text{-TTL}} = 100/(1 + 400/20)^{1/2} = 22\Omega$$

$$Z_{L\text{-BTL}} = 100/(1 + 200/20)^{1/2} = 30\Omega$$

Note that each driver sees TWO loaded line impedances in parallel (see *Figure 2*). This reduces the bus impedance by half.

V. PROPAGATION DELAYS (related to excessive capacitance loading)

Since the DS3890 reduces the backplane capacitance loading, the propagation delay through the bus lines is improved by 28%, as shown below.

- Unloaded Bus Propagation Delay (data based on a single strip line PC board)

$$T_P = (LC)^{1/2} = [(0.2 \mu\text{H}/\text{ft}) \times (20 \text{ pF}/\text{ft})]^{1/2}$$

$$= 2 \text{ ns per foot}$$

- Loaded Bus Propagation Delay (data based on a single strip line PC board)

$$T_{PL} = (T_P) \times (1 + C_L/C)^{1/2}$$

$$T_{PL\text{-TTL}} = (2 \text{ ns}) \times [1 + (400 \text{ pF per Foot})/(20 \text{ pF})]^{1/2}$$

$$= 9.2 \text{ ns/ft}$$

$$T_{PL\text{-BTL}} = T_P \times (1 + C_L/C)^{1/2} = (2 \text{ ns}) \times [1 + (200 \text{ pF per Foot})/(20 \text{ pF})]^{1/2} = 6.6 \text{ ns/ft}$$

$$\text{Improvement} = (6.6 \text{ ns per foot})/(9.2 \text{ ns per foot}) \times (100)$$

$$= 28\%$$

VI. SIGNAL SETTLING TIME

The signal settling time refers to the amount of time the signal takes to cross the threshold. In low impedance buses, the signaling settling time depends NOT ONLY on the slew rate, but more importantly, on the current driving capability of the driver, bus impedance, reflections, and bus length.

For example, in a fully loaded open collector TTL bus ($Z_{O\text{-TTL}} = 22\Omega$) with 50 mA drivers, the first output transition is $[V_1 = (I_L) \times (Z_O \parallel Z_O) = (50 \text{ mA}) \times (11\Omega)]$ 0.55V. This means that the signal does NOT cross the threshold region ($V_{TH} = 0.8$ to 2V) on the first signal transition (see *Figure 3*). The second transition appears after a round trip prop delay [R.T.D. = $(2) \times (T_{L\text{-TTL}})$]. In a one foot fully loaded bus, the delay can be 18.4 ns [R.T.D. = $(2) \times (9.2 \text{ ns per foot})$]. If it takes several signal transitions to cross the threshold, the ACTUAL signal settling time consists of several round trip prop delays. Also note that the signal crosses the threshold in a staircase fashion, which may cause false triggering.

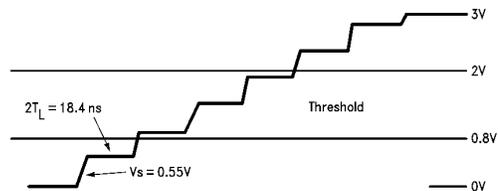


FIGURE 3

TL/F/9111-4

$$V_{I-TTL} = (50 \text{ mA}) \times (11\Omega) = 0.55\text{V}$$

$$\text{Round Trip Prop Delay of the Bus} = (2) \times (T_{L-TTL})$$

$$= (2) \times (2 \text{ ns per foot})$$

$$= 4 \text{ ns/ft (unloaded bus)}$$

$$= (2) \times (9.2 \text{ ns per foot})$$

$$= 18.4 \text{ ns/ft (loaded bus)}$$

In a fully loaded BTL bus ($Z_{O-BTL} = 30\Omega$), the first output transition is 0.75V [$V_1 = (50 \text{ mA}) \times (15\Omega)$]. Since V_{TH} is between 1.5V and 1.6V , the FIRST output transition crosses the threshold (see Figure 4). The actual settling time consists of ONLY the slew rate. The danger of false triggering is eliminated because the reflections are not seen as the signal crosses the threshold.

$$V_{I-BTL} = (50 \text{ mA})^* (15\Omega) = 0.75\text{V}$$

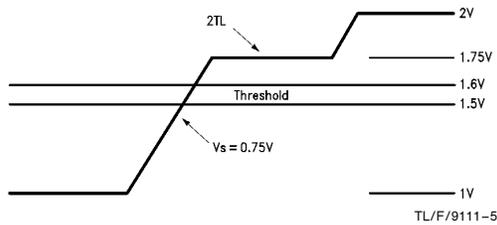


FIGURE 4

Therefore, despite the slower slew rate, the BTL devices have a much shorter settling time due to the lower output

capacitance, one volt signal swing, and precision threshold. This improves the data integrity and speed of the bus.

VII. PROPAGATION DELAY SKEW

The propagation delay consists of the delays through the driver, receiver, and transmission medium (PC strip). These delays can vary if the ICs have differences in their process, temperature, V_{CC} , or PC board layout. In parallel address/data lines, propagation delay skews are very critical. If the signals arrive at their destination at different times, the system must delay all signals to assume for a worst case delay. Therefore, if the propagation delay skew is small, the worst case delay is also small. It is safe to assume that ICs on a single board or system have the same temperature, same V_{CC} , and similar PC board layout configurations. This reduces the propagation delay skew to only the variations in the process.

VIII. LIVE INSERTION GUIDELINES

Live insertion of line cards is a must for PBX maintenance without interrupting customer service. The DS3890/92/98 support live insertion by guaranteeing glitch-free power up/down. However, uncharged by-pass capacitors and board static can bring the system down when plugging in a line card. One way of avoiding these problems is to use an umbilical cord (temporary power line) to discharge static and slowly charge by-pass capacitors. This method will set the line card V_{CC} and GND equal to the levels of the system before it is plugged in.

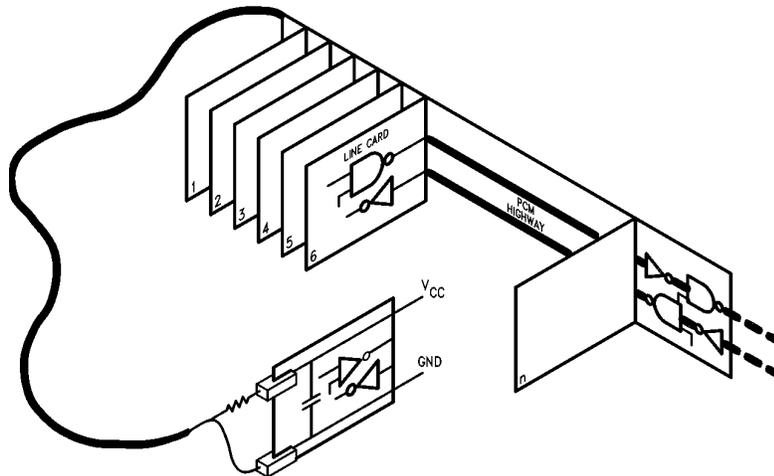



FIGURE 5. Temporary Power Cord

TL/F/9111-6

IX. EXTENDING A BUS BEYOND THE RACK

The DS3898 (BTL repeater) is ideal for cases where the system bus must be extended. If the bus is of considerable length, the repeaters regenerate the signal levels. The repeaters also isolate, or separate, different electrical environments. For example, if a ribbon cable is used to connect one rack to another, the repeaters will isolate the different impedance and noise levels present in a ribbon cable from the bus on the rack.

X. USING THE PROPER BUS TERMININATION

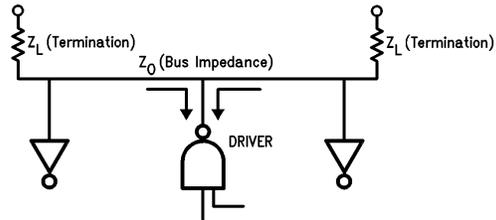

TL/F/9111-7

FIGURE 6

An ideal termination (Z_L) should match the bus impedance (Z_0) in order to eliminate reflections. If the termination matches the impedance of a fully loaded bus, then $Z_L = Z_0 = 30\Omega$. With the 30Ω terminations, the driver is required to drive a ($Z_L \parallel Z_L = 30 \parallel 30$) 15Ω load. However, the lowest load that a standard TTL driver will guarantee is (5V/50 mA) 100Ω . If the designer uses the ($Z_L \parallel Z_L = 200 \parallel 200 = 100\Omega$ load) 200Ω terminations on the 30Ω bus, the reflections will be very large. On the other hand, BTL drivers can guarantee a (1V/50 mA) 20Ω load. In this case, the ($Z_L \parallel Z_L = 40 \parallel 40 = 20\Omega$ load) 40Ω terminations will have small reflections. Note that the improvement of the guaranteed load (from 100Ω to 20Ω) was achieved by reducing the voltage swing and driver output capacitance, NOT by increasing the current capabilities of the drivers.


XI. TWO VOLT RAIL

There are many ways of supplying the two volt rail needed for the 90/92/98. Four possibilities are: a separate two volt

power supply; a voltage divider; a voltage regulator; and a high current voltage follower. The two volt power supply is very expensive to implement and does not track the five volt supply voltage, thereby reducing the effectiveness of the precision threshold. However, it is very efficient in terms of power consumption, making it appropriate for very large systems. The voltage divider is inexpensive, tracks the five volt supply voltage, but consumes too much current when the line is high. The voltage regulator is moderately efficient with current consumption, but does not track the five volt supply voltage. Finally, the high current voltage follower does not waste current when the line is high; is inexpensive to implement; and tracks the five volt supply voltage. Therefore, the high current voltage follower seems to be the best choice for small systems where cost is a major consideration.

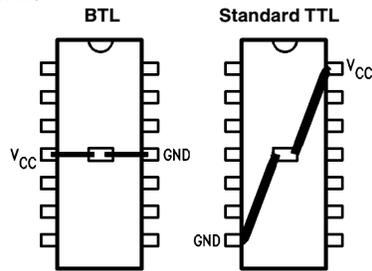XII. NOISE REDUCTION THROUGH IMPROVED PIN LAYOUT

In order to reduce ground noise caused by long lead inductance, one must make V_{CC} and GND lead lengths as short as possible. The packaging of National's BTL circuits contributes to shorter V_{CC} and GND lead inductance by placing the power pins in the center of the IC package, instead of the corners.



TL/F/9111-8

Top View

FIGURE 7

XIII. OVERVIEW OF THE BTL TRAPEZOIDAL PRODUCT LINE

The BTL Trapezoidal products have low output capacitance (5 pF max), one volt signal swing, and noise immunity features which make them ideal for driving parallel, low impedance bus lines with minimum power dissipation.

- DS3890

The DS3890 is an octal BTL driver. It is designed specifically to overcome problems associated with driving densely populated backplanes. The trapezoidal wave forms and the one volt swing reduces noise coupling to adjacent lines. The open collector driver output allows for wired-OR connections.

- DS3892

The DS3892 is an octal receiver. The receivers have precision thresholds to increase the noise margins, and low pass filters to filter out crosstalk.

- DS3898

The DS3898 is an octal repeater. It combines the BTL characteristics of the DS3890 and DS3892. The part is ideal for extending backplanes.

- DS3896

The DS3896 is an octal high speed schottky bus transceiver with common control signals. It provides high package density for data/address lines.

- DS3897

The DS3897 is a quad transceiver with independent driver input and receiver output pins. It has a separate driver disable for each driver.

- DS3893

The DS3893 is the newest member of the family. It is designed to drive and receive signals at data rates of up to 100 MBaud. The trapezoidal feature has been removed to reduce the propagation delay down to 15 ns for the driver and receiver combination.

National's BTL drivers, receivers, and transceivers offer the most complete approach for operating high speed parallel backplanes.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor Corporation
 1111 West Bardin Road
 Arlington, TX 76017
 Tel: 1(800) 272-9959
 Fax: 1(800) 737-7018

National Semiconductor Europe
 Fax: (+49) 0-180-530 85 86
 Email: onjwge@tevm2.nsc.com
 Deutsch Tel: (+49) 0-180-530 85 85
 English Tel: (+49) 0-180-532 78 32
 Français Tel: (+49) 0-180-532 93 58
 Italiano Tel: (+49) 0-180-534 16 80

National Semiconductor Hong Kong Ltd.
 19th Floor, Straight Block,
 Ocean Centre, 5 Canton Rd.
 Tsimshatsui, Kowloon
 Hong Kong
 Tel: (852) 2737-1600
 Fax: (852) 2736-9960

National Semiconductor Japan Ltd.
 Tel: 81-043-299-2309
 Fax: 81-043-299-2408

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated