

CB-6

CB-6 RAM Keep-Alive



Literature Number: SNOA634

RAM Keep-Alive

National Semiconductor
COP Brief 6
May 1980



RAM Keep-Alive

A COPSTM application is a small scale computer system and the design of a power shut-down is not trivial. During the time that power is available, but out of the designed operating range, the system must be prevented from doing anything to harm protected data. This will typically involve some type of external protection of timing circuit.

There is an option on the COP420, 420L, and 410L parts called "RAM Keep-Alive" that provides a separate power supply to the RAM area of the chip via the CKO pin. The application of power to the RAM while the remainder of the chip has been powered down via VCC will keep the RAM "alive".

However, the integrity of data in the RAM is not only a function of power but is also influenced by transient conditions as power is removed and reapplied. During power-on, the Power On Reset (POR) circuit will keep transients from causing changes in the RAM states. The condition of power loss will have some probability of data change if external control is not used.

At some point below the minimum operating voltage certain gates will no longer respond properly while others may still be functional until a much lower voltage. During this transition time any false signal could cause a false write to one or more cells. Another effect could be to turn on multiple address select lines causing data destruction.

Testing the rate of data change is very difficult because it must be done on a statistical basis with many turn/on-turn/off cycles. Two factors have a major bearing on the numbers derived by testing. One is to call any change in a related data block a failure, even though more than one bit in that block may have changed (this latter case may well be due to the "address select mode"). The second factor is that without massive instrumentation it is impossible to examine the data after each power cycle. Indeed, to do so might have caused errors!

By running the power cycle for a period of time and then looking for changes, one could overlook multiple changes thus reducing the error rate. This has been minimized by more frequent checking which indicates that the errors are spread out randomly over time.

With a power supply that drops from 4.5 to 2V in approximately 100 ms, the drop-out rate is 1 in 5k to 6k power cycles. Reducing the voltage fall time will cause an improvement in the number of cycles per drop-out. This will reach a limit condition of a very high number (1 per 1 million?) when the power falls within one instruction cycle (4-10 μs for the 420, 15-40 μs for the "L" parts). Attaining very rapid fall time may cause problems due to the lack of decoupling/bypass capacitance. By inserting an electronic switch between the regulator and VCC of the COP chip one might be able to meet this type of fall time. By implication some type of sensing is required to cause the switching.

The desirable approach is to force the COP reset input to zero before the voltage falls below 4.5V. This provides a drop out rate of approximately 1 in 50k for the "L" parts and 1 in 100k for the 420. By also stopping the clock of the "L" parts they can achieve a drop-out rate similar to the 420. While not perfect, the number of cycles between data error should be considered with respect to the needs of the application.

The external circuitry to control the chip during the power transition has several implementations each one being a function of the application. The simplest hardware is found in a battery powered (automotive) application. The circuit must sense that the switched 12V is falling (e.g., at some value much below 12V and still greater than 5V). This can be done by using the unswitched 12V as a reference for a divider to a nominal voltage of 8V. As the switched 12V drops below the reference a detector will turn on a clamp transistor to a series switch, the POR, and/or the clock circuit (Figure 1). It should be noted that this draws current during the absence of the switched 12V circuit.

In non-automotive usage a similar circuit can be used where there is a stable reference voltage available to use with the comparator/clamp. Thus a 3.6V rechargeable Ni-Cad battery could be used as the reference voltage and V_{RAM} if the appropriate divider is used to level shift to this operating range.

In AC line-powered applications, a similar method could be used with the raw DC being sensed for drop. Another method would be to sense that the line had missed 2-3 cycles either by means of a charge pump or peak detection technique. This will provide the signal to turn on the clamp. One must make this faster than the time to discharge the output capacitance of the power supply, thus assuring that the clamp has performed its function before the supply falls below spec value.

In conclusion, to protect the data stored in RAM during power-off cycle, the POR should go low before the V_{CC} power drops below spec and come up after V_{CC} is within spec. The first item must be handled with an external circuit like Figure 1 and the latter by an RC per the data sheet.

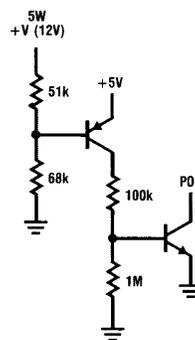


FIGURE 1

TL/DD/6946-1

COPSTM is a trademark of National Semiconductor Corp.

CB-6

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- 1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- 2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor Corporation
 1111 West Bardin Road
 Arlington, TX 76017
 Tel: 1(800) 272-9959
 Fax: 1(800) 737-7018

National Semiconductor Europe
 Fax: (+49) 0-180-530 85 86
 Email: onjwge@tevm2.nsc.com
 Deutsch Tel: (+49) 0-180-530 85 85
 English Tel: (+49) 0-180-532 78 32
 Français Tel: (+49) 0-180-532 93 58
 Italiano Tel: (+49) 0-180-534 16 80

National Semiconductor Hong Kong Ltd.
 19th Floor, Straight Block,
 Ocean Centre, 5 Canton Rd.
 Tsimshatsui, Kowloon
 Hong Kong
 Tel: (852) 2737-1600
 Fax: (852) 2736-9960

National Semiconductor Japan Ltd.
 Tel: 81-043-299-2309
 Fax: 81-043-299-2408

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated