

PurePath® Digital Audio Power Amplifiers

Application Overview

Fred Shipley, MGTS
snag@ti.com



Topics

- Target Markets
- Signal Path/Device Examples
- DSP Interface Example
- Power Supply Considerations
- Thermal Overview
- PCB Layout
- Key Components – Critical Parameters
- Putting it all together

Minds in Motion

Target Markets

EE	DVDR/HTIB	Mini/Micro Component	AVR
			
Price	\$200 to \$1000 (w/ speakers)	\$50 to \$300 (w/ speakers)	\$200 to \$500 (stand-alone)
# of ch's	5.1 to 7.1	2.0 to 2.1	5.1 to 7.1
Power per ch	50W-200W/3-6Ω/10%THD	10W-300W/3-6Ω/10%THD	70W-150W/8Ω/<0.09%THD
Sources	DVDR, Tuner, (VCR)	CD, Tape, (DVD), (HDD)	FM Tuner, (XM)
Appearance	"Sleek and stylish"	"Reincarnation of the '80's rack systems"	"Big/heavy, bells and whistles"
Other	Power often rated as PMPO; SMPS is default;	Power often rated as PMPO; Typically SMPS; (sometimes linear)	Typically FTC power and THD rating; Advanced audio proc. features (DSP);
Care-about: Primary...	Cost; development time; Form factor/weight Efficiency (small heat sink)	Cost; development time; robustness	Audio performance; features; Lots of I/O's
Secondary...	Audio performance; features	(Form factor); audio performance	(cost); efficiency;

Minds in Motion

Conventional Signal Path


DAC needed

Analog processing
Complex & long analog signal path:

Sound degradation!!!

High Analog Gain:

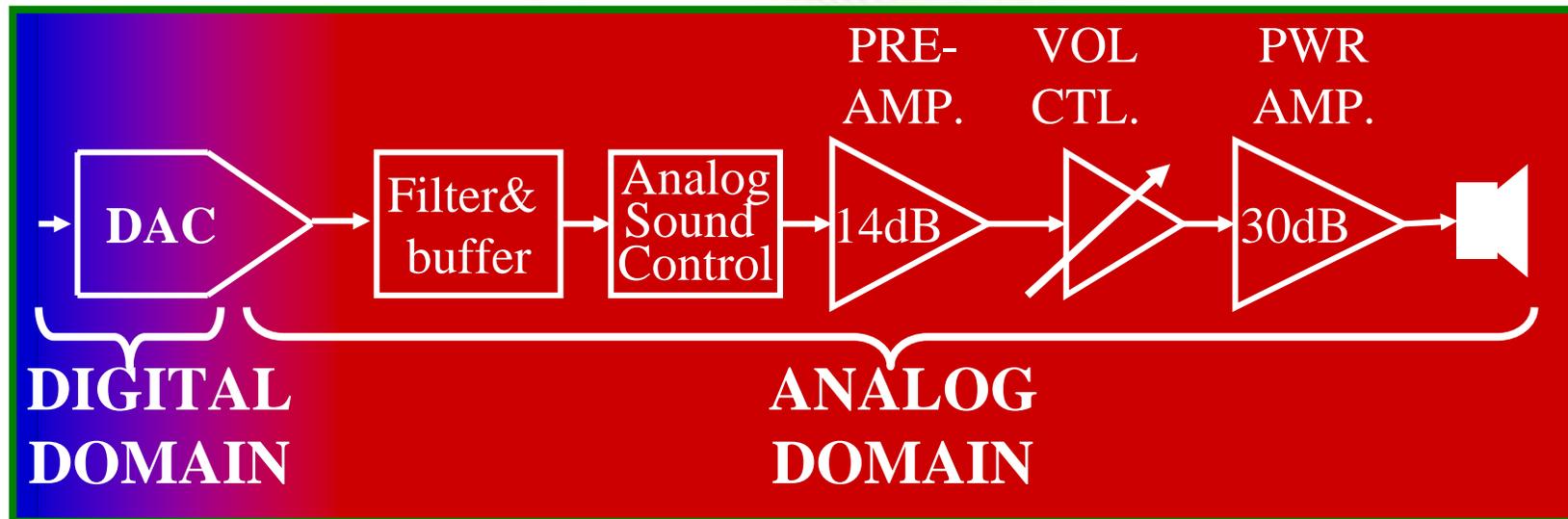
Sensitive to noise & Hum pick up
SNR at speakers is much lower
than theoretical DAC spec



Minds in Motion

PurePath[®] Modulator Signal Path

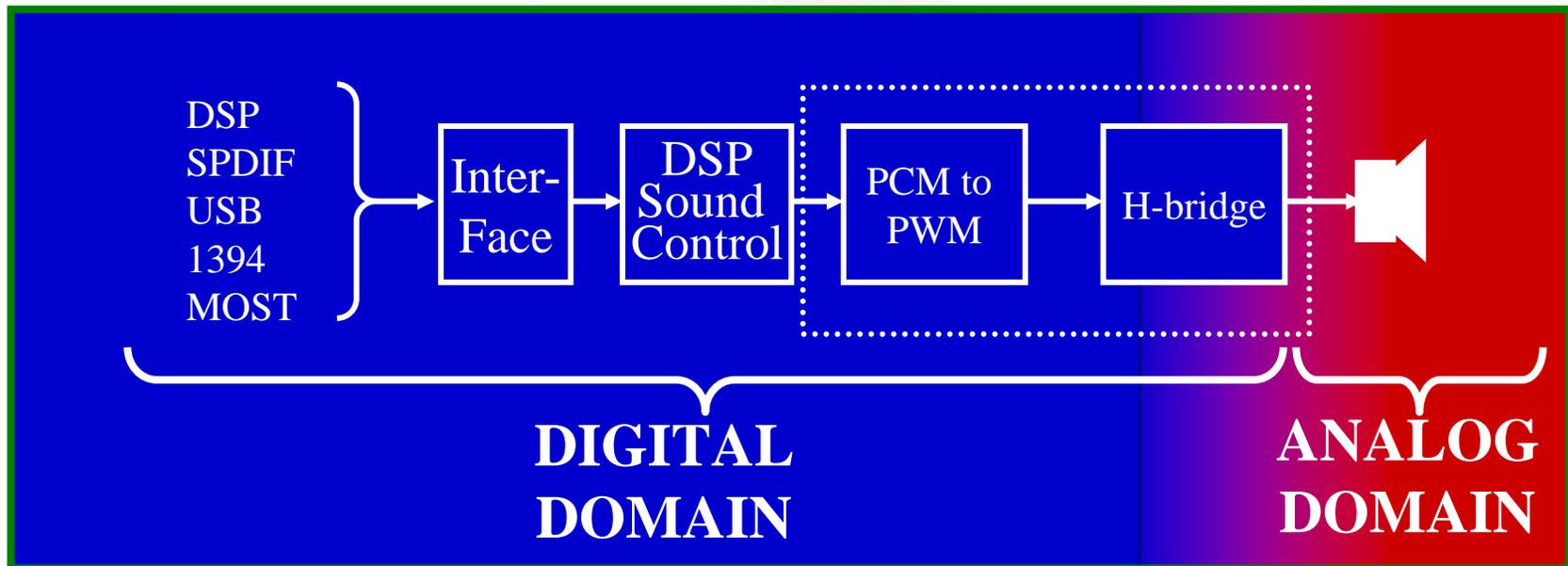
- True digital path
- Only digital processing
- No analog processing
- No D/A converter used
- No-loss DSP sound control
- No gain or amplification
- Digital is immune to noise/
hum pick-up



Minds in Motion

PurePath[®] Modulator

(Basic Principle)

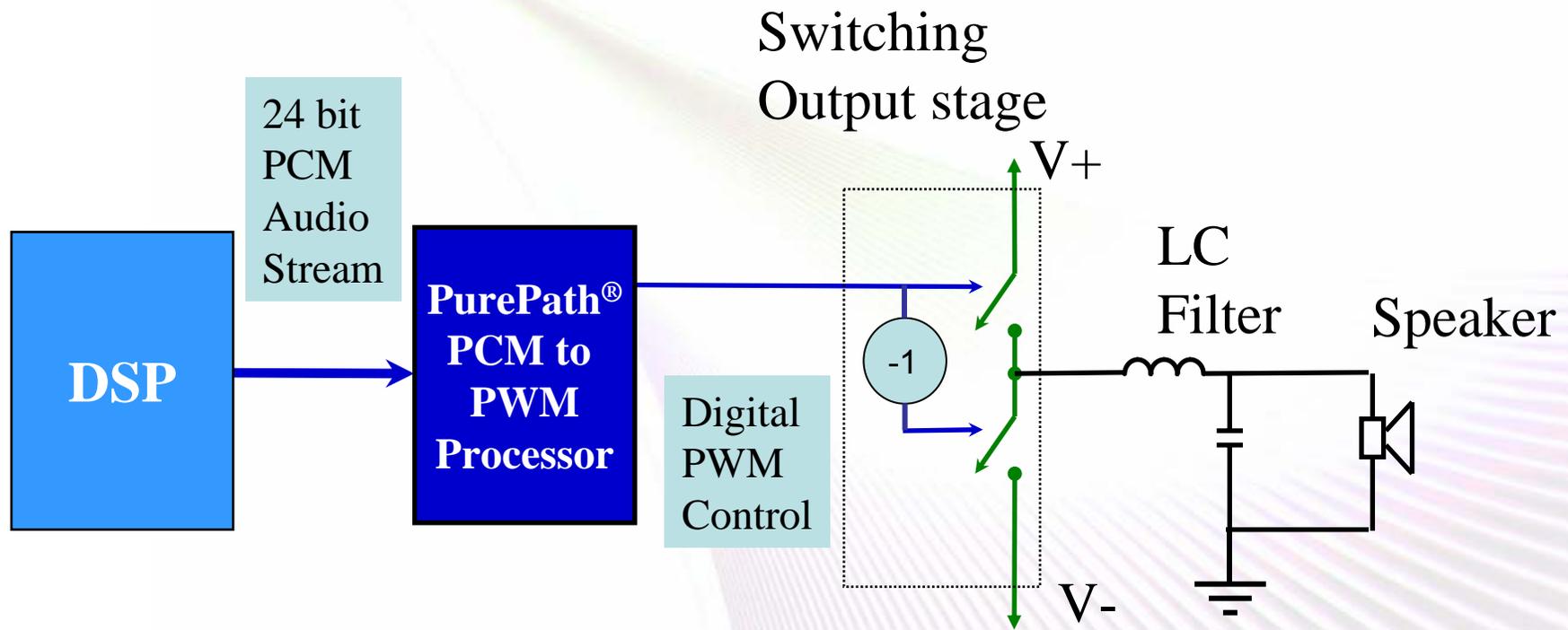


Minds in Motion

DSP Interface Example



DSP/Amplifier Interconnect


Interface Port to Amplifiers

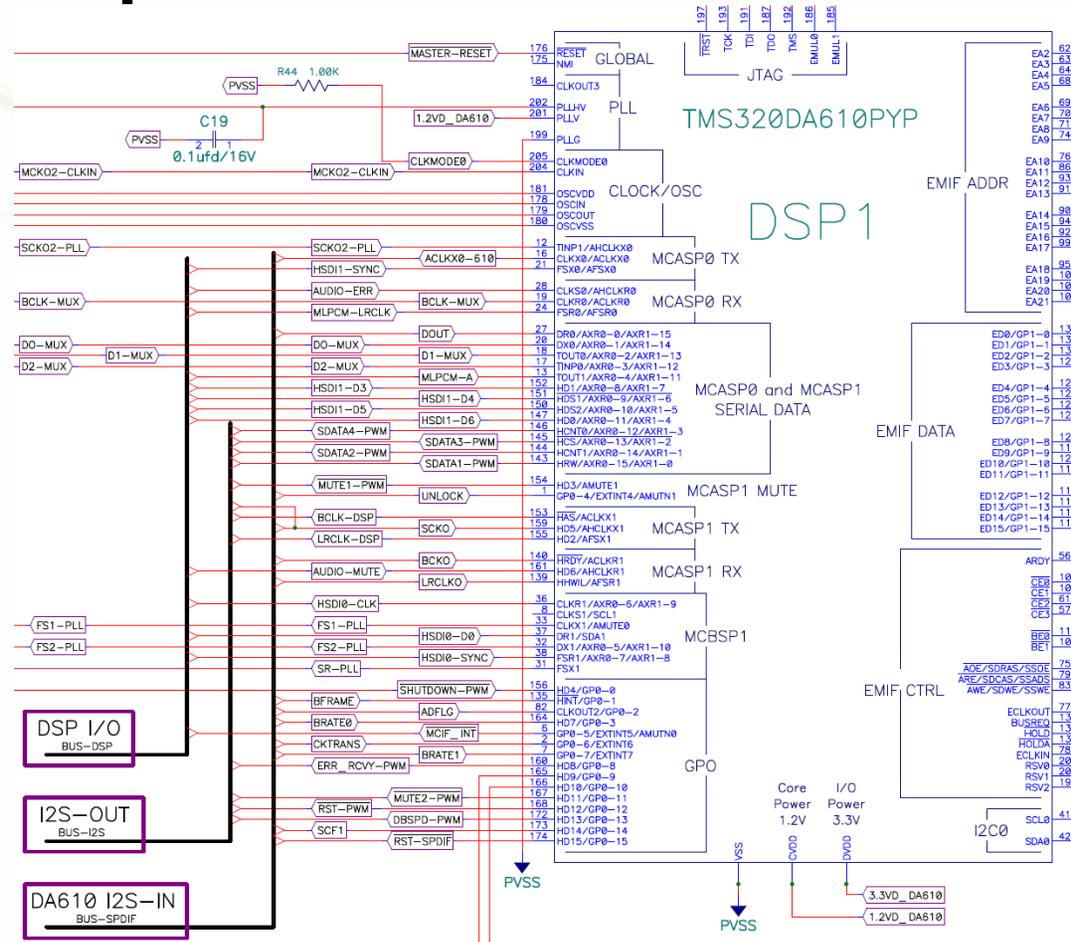

Minds in Motion


DSP Connection to Modulator

PWM MODULATORS

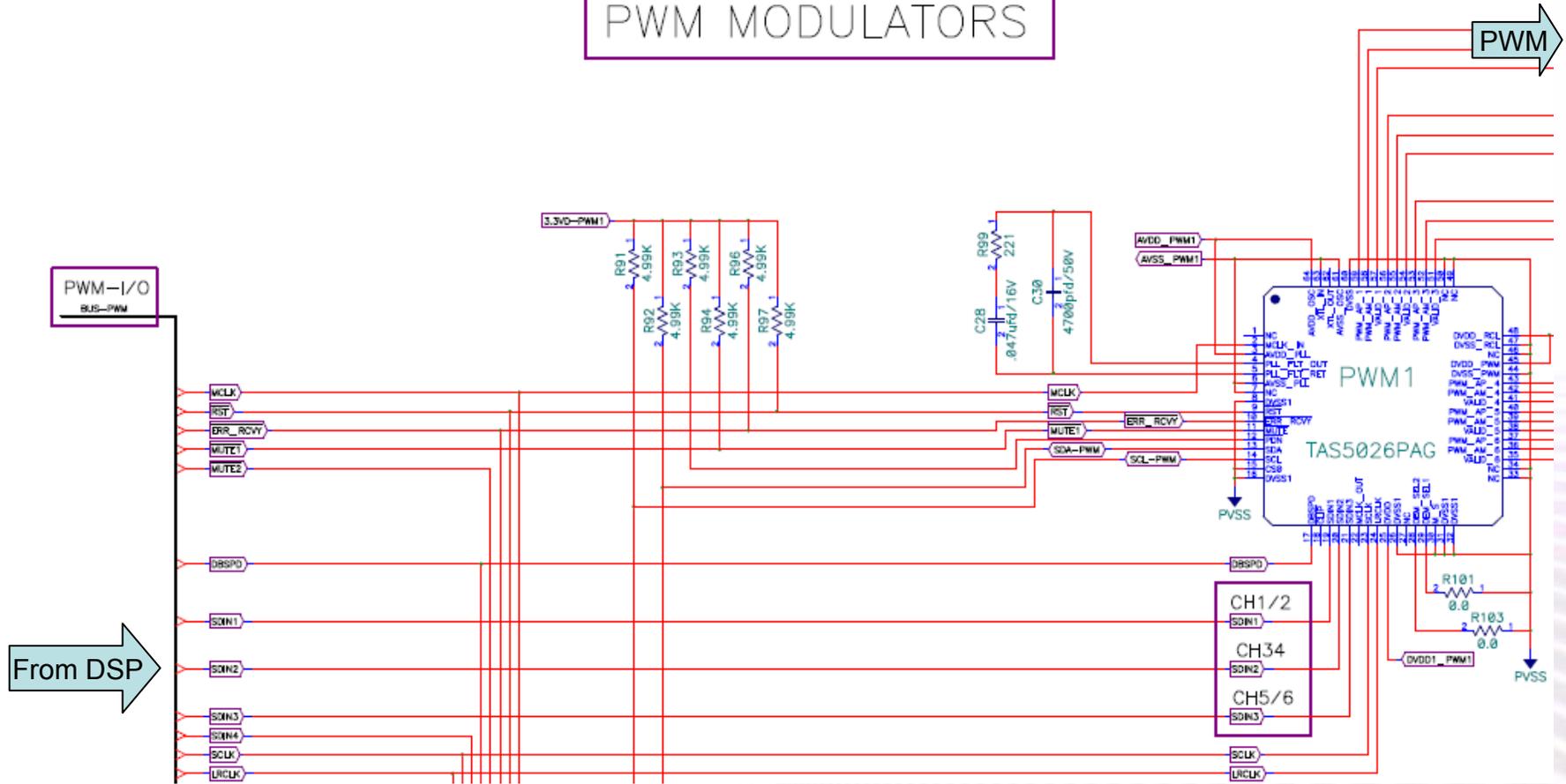


Minds in Motion

Modulator to Power Stage

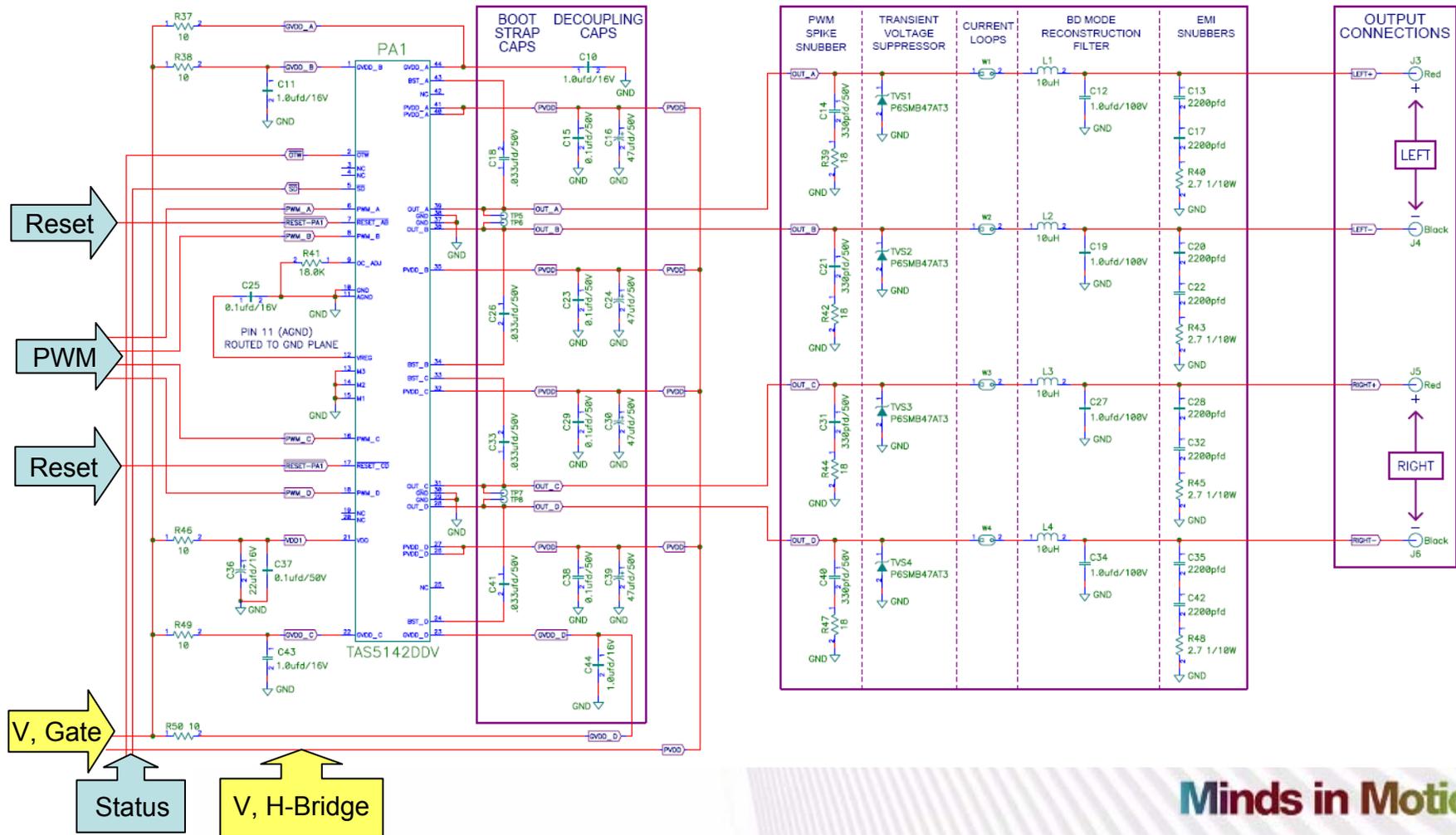

Minds in Motion

DSP to DAC and Headphone Amp

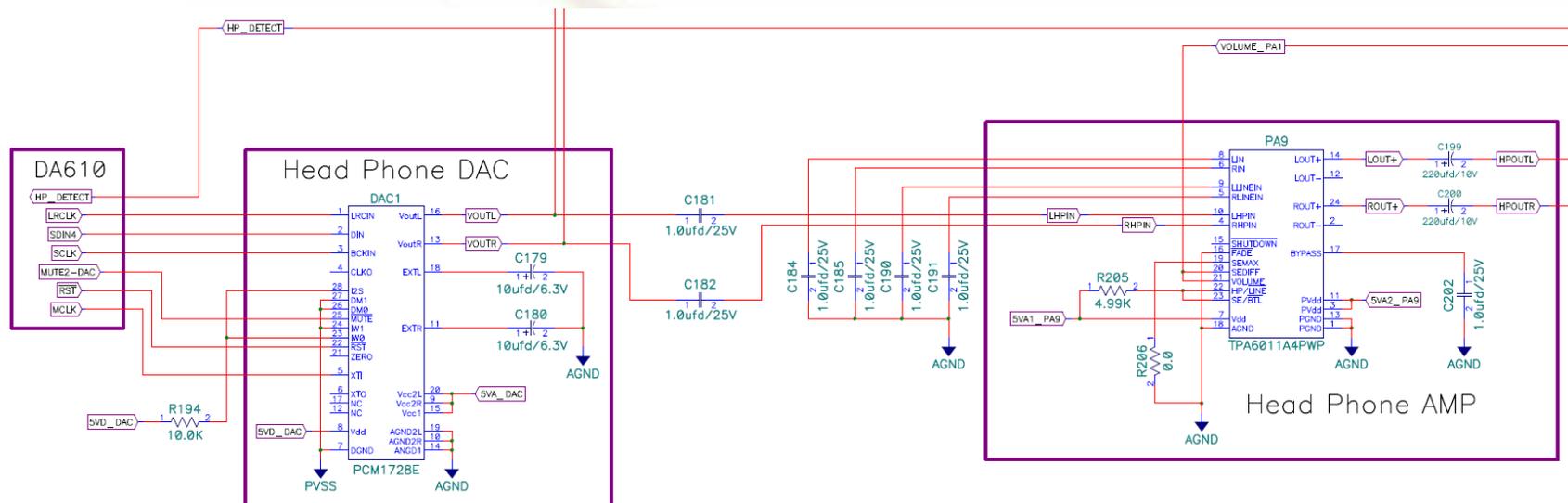

Minds in Motion

Power Supply Considerations



Voltage Requirement



- Using following equation:
 - Voltage needed for an application can be calculated as:

$$V_{PSU} = \frac{(R_{LOAD} + 2 \cdot (R_{DSon} + R_{INDUCTOR})) \cdot \sqrt{\left(\frac{2 \cdot P_{MAX}}{R_{LOAD}} \right)}}{M}$$

Minds in Motion

Voltage Requirement

- Graphs from TAS5142 datasheet:

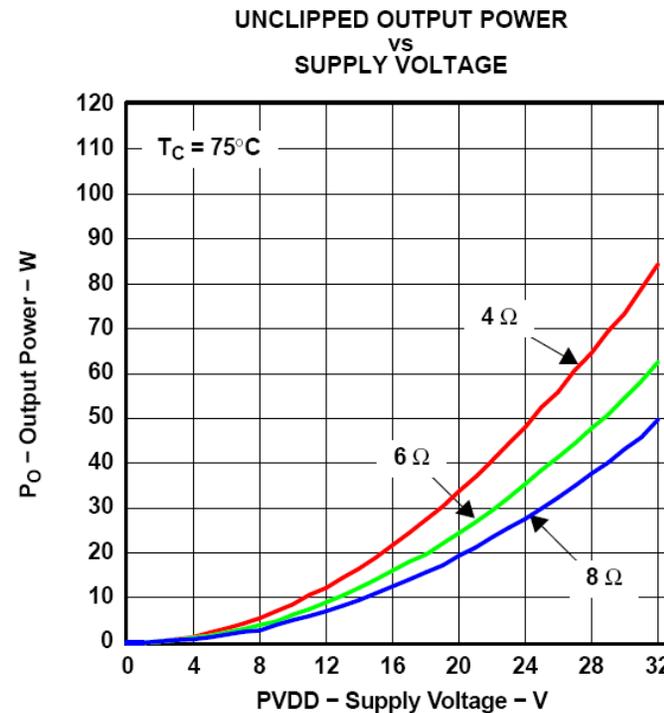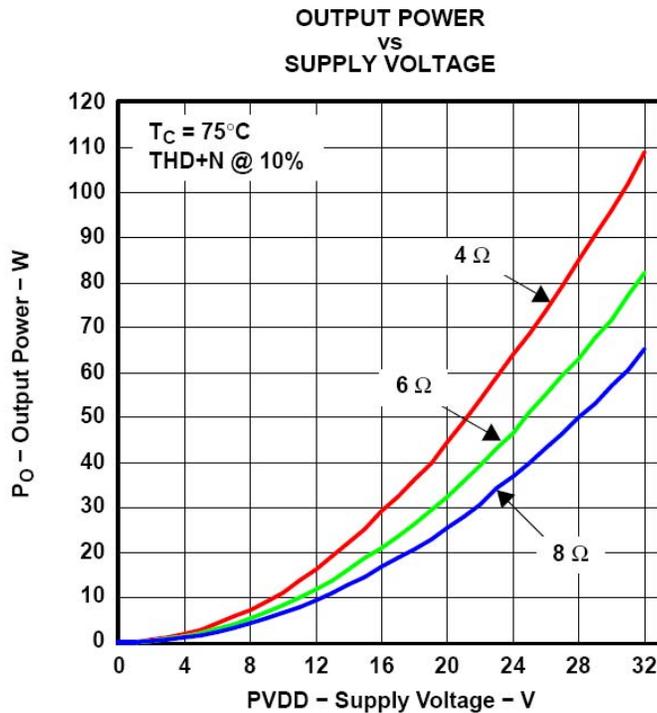

Minds in Motion

Power Requirement

- Typical music and movies have 12-15dB headroom from average power to peak power.
- This corresponds well with normal requirement of testing all channels at 1/8 power for 1 hour.
- Different government regulations and company preferences require higher power for shorter periods of time.

Specification	Preconditioning (Warm-Up)	Time at Continuous Rated Power
DIN EN 61305-3	None	600 seconds
EIA/CEA-490-A	1/8 power for ½ hour	5 minutes ⁽¹⁾
FTC 16 CFR Part 432	1/8 power for 1 hour	5 minutes ⁽²⁾

(1) Each channel is tested individually with the other channels at 1/8 power.
 (2) Channels in same frequency range test at full power. The subwoofer test is separately.

Minds in Motion



Power Supply Rejection Ratio

- PSRR is well known for class AB amplifiers.
- Normal definitions of PSRR also apply for Class D amplifiers using feedback.
- PurePath® digital amplifiers do not use feedback; PSRR term is slightly different:
 - $V_{out}(t) = V_{psu}(t) \times d(t)$
- Conventional mains transformer supply will have 100Hz/120Hz ripple.
- Common Switch Mode Power Supplies (SMPS) switch in the 100KHz to 200KHz range; therefore, their ripple is out of the audio band *and* they are regulated.

Minds in Motion

Power Supply Rejection Ratio

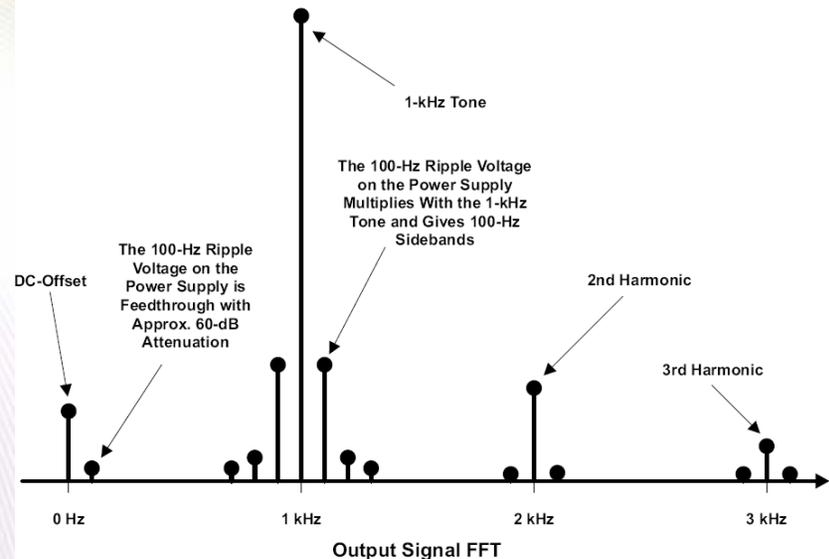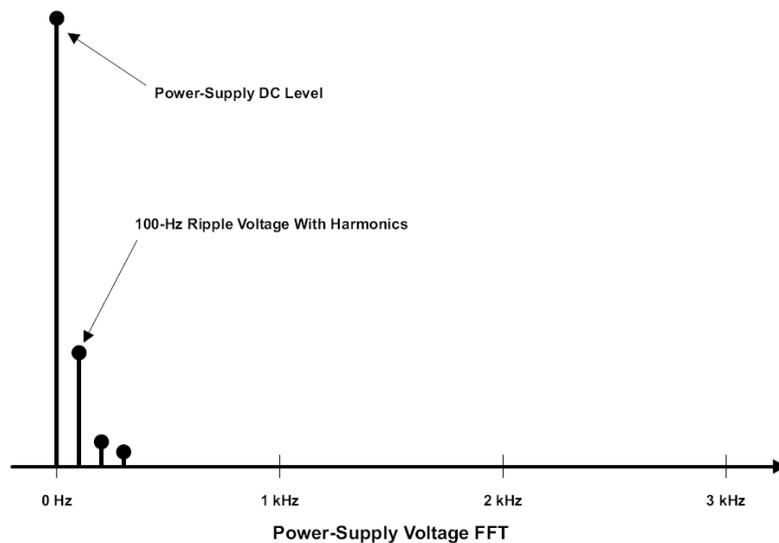
- Conventional mains transformer supply will have 100Hz/120Hz ripple.



Minds in Motion

Power Supply Rejection Ratio

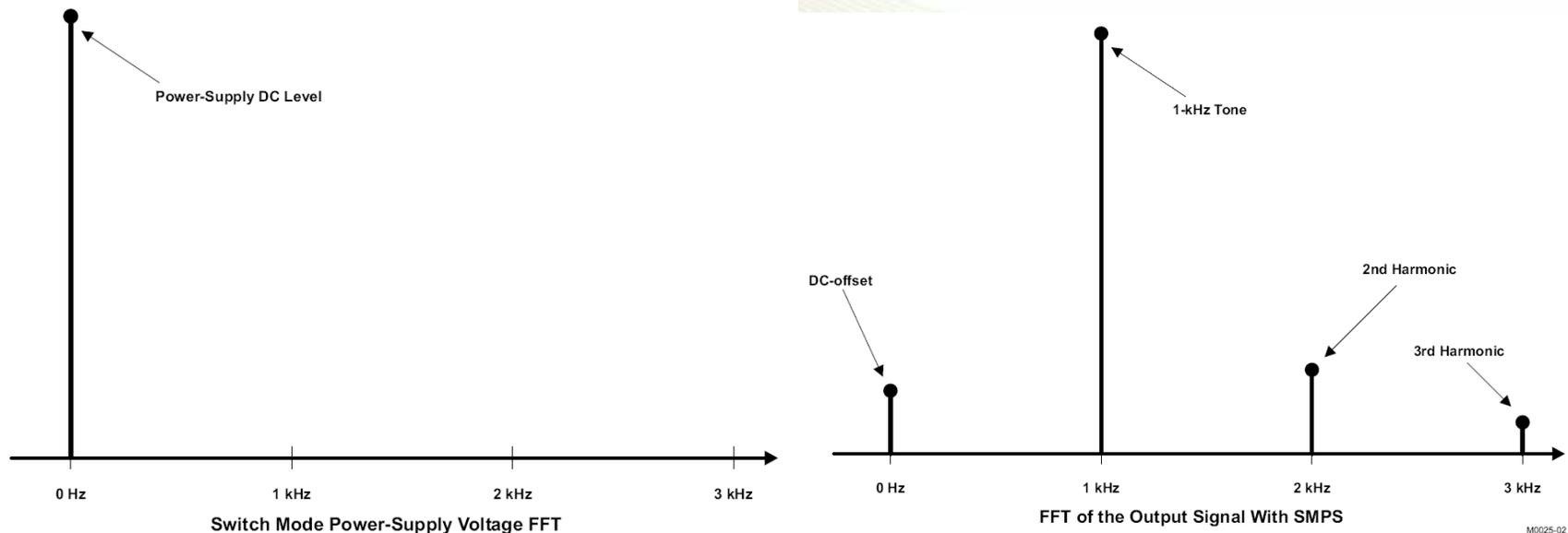
- A switch mode power supply will not have ripple within the audio band.



Minds in Motion

Power Supply Rejection Ratio


- How to measure PSRR

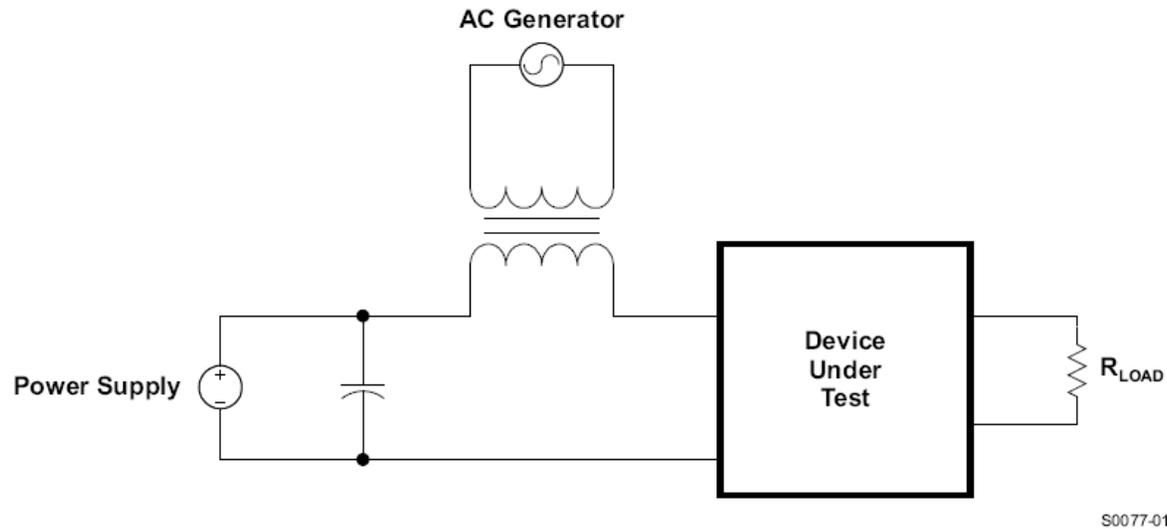

$$PSRR(f) = 20 \cdot \log \frac{V_{OUT}(f)}{V_{INJECT}(f)}$$

Minds in Motion

Power Supply Rejection Ratio

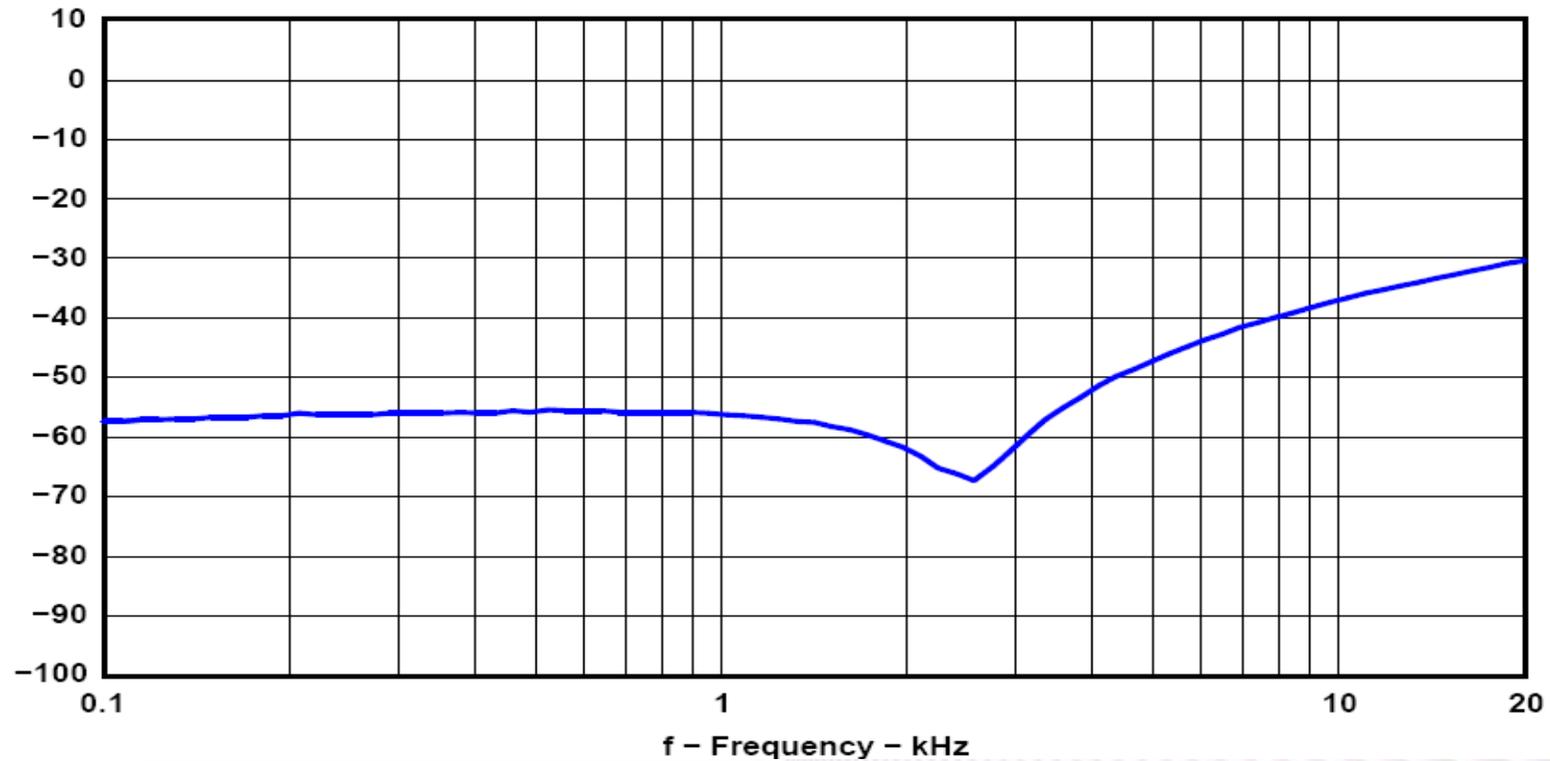


PSRR measurement for TAS5086-5142V6EVM

Minds in Motion


Power Supply Output Impedance

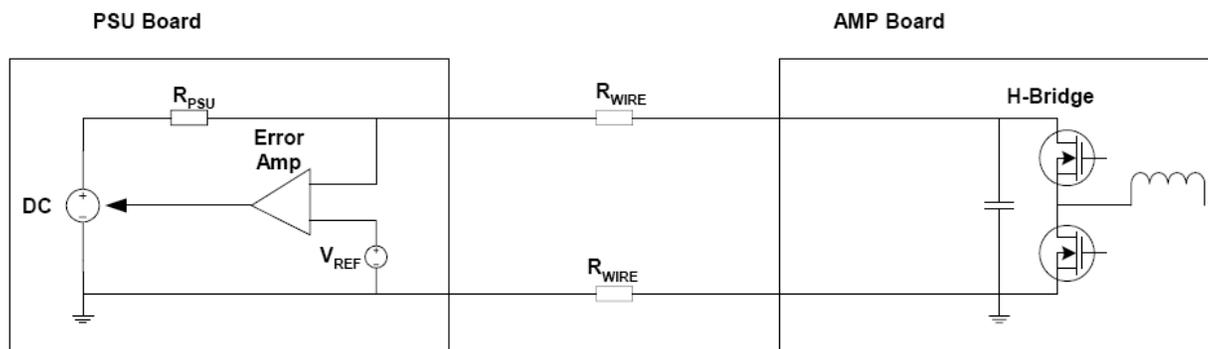- The Power supply output impedance and the wire resistance to and from the amplifier will affect THD performance of the amplifier.
- If designed poorly, THD will increase at low frequencies up to around 1kHz, depending on application.
- This is due to the fact that the current to the amplifier is twice the frequency of the audio current.



Minds in Motion

Power Supply Output Impedance

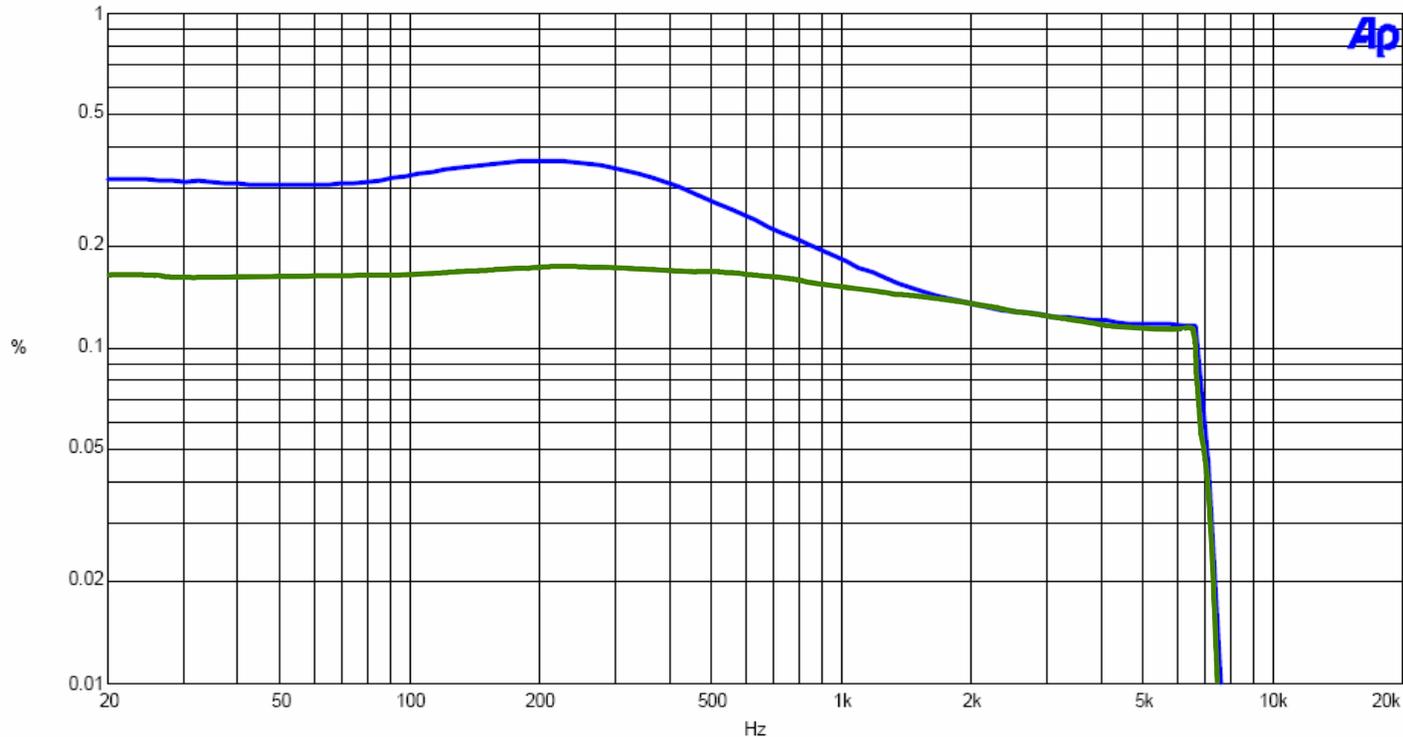

Blue Line – High power supply Output Impedance
Green Line – Correct power supply Output Impedance


Minds in Motion

More Info

- Power Supply Recommendations for DVD Receivers, TI Literature No. SLEA027
- Power Supply Recommendations for A/V Receivers, TI Literature SLEA028
- PSRR for PurePath Digital Audio Amplifiers, TI Literature SLEA049

Minds in Motion

Thermal Overview

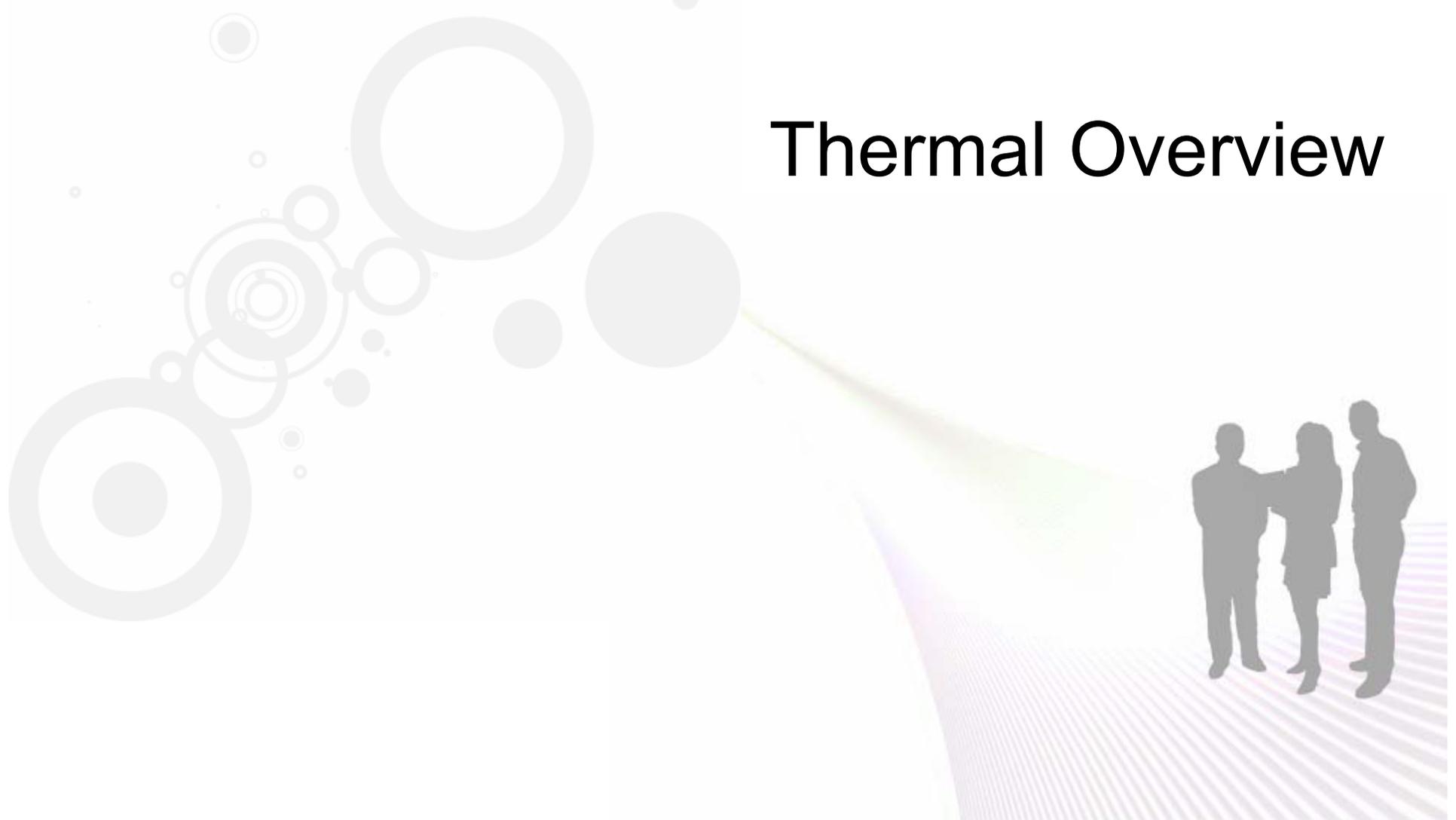

Device Thermal Parameters

- The thermal parameters for each device are available in its datasheet.
- As in the case of the power supply, the size of the heatsink is dependant on the system thermal requirement and its power specification.
- The thermal solution is generally not designed to accommodate all channels (if there are >2) at full power, simultaneously.

Specification	Preconditioning (Warm-Up)	Time at Continuous Rated Power
DIN EN 61305-3	None	600 seconds
EIA/CEA-490-A	1/8 power for ½ hour	5 minutes ⁽¹⁾
FTC 16 CFR Part 432	1/8 power for 1 hour	5 minutes ⁽²⁾

(1) Each channel is tested individually with the other channels at 1/8 power.

(2) Channels in same frequency range test at full power. The subwoofer test is separately.

Minds in Motion

Heatsink Size

- In many cases a heatsink of $2.5^{\circ}/W$ to $4.5^{\circ}C$ is appropriate.
 - There are many variables such as airflow and test temperature to be considered.
- TI EVMs are delivered with a good thermal solution.
 - It may be necessary to change the size or geometry to meet space constraints or other system factors.

Minds in Motion

TI | **Developer Conference**
March 7-9, 2007 • Dallas, TX

Minds in Motion

PCB Layout

- Do's and Don'ts



Technology for Innovators™

 **TEXAS INSTRUMENTS**

PCB Layout and EMI

- PCB layout, Audio Performance and EMI are linked closely together.
- Generally EMI is concerned with reducing EMI sources and removing antennas.
- Circuit contains high currents at high frequencies.
- Care must be taken to prevent unwanted ringing and spikes.
- Current loops with high currents and high frequencies act as EMI sources and must be kept as small as possible.
- Small signal level CMOS inputs can pick up noise and must therefore be kept away from EMI sources.

Minds in Motion

Ground Plane



Ground Plane The forgotten return path

- Every signal has a return current.
- Routing of the return path is just as important as signal current.
- The best/only solution is the use of a ground plane.
- Ground plane is an unbroken Cu-PCB layer only used for ground signal.
- Optimum path for return currents then becomes embedded in the design.
- Note that optimum return path is not necessarily the shortest path for high frequency currents.


Minds in Motion

Routing of Sensitive Tracks

- Decoupling capacitors must be placed close to the device. Goal - .050" of PCB track length in decoupling path.
- All Power tracks must be designed with care to get good audio and EMI performance.
- PWM tracks must go as directly as possible from TAS5086/TAS5508 to TAS5142 and other power stages. The tracks must not interleave the PCB.
- MCLK track must be as short as possible and must always be accompanied by ground.

Minds in Motion

Implementation of TAS5142

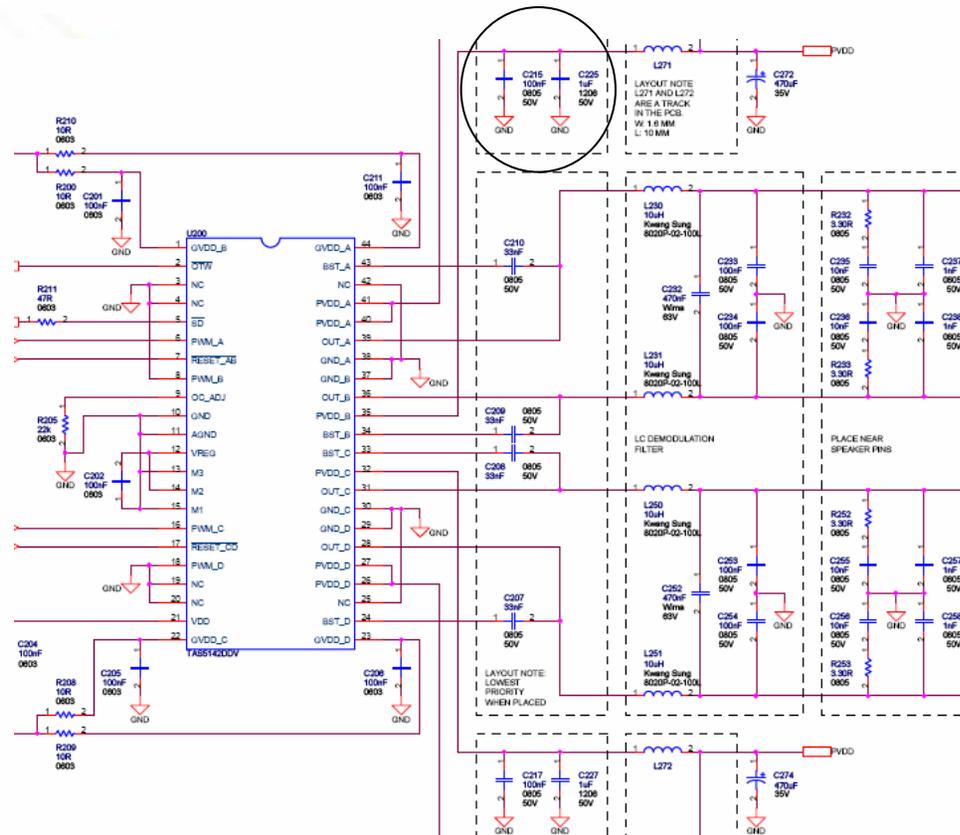


- PWM output voltage goes from 0V to 32V within 5ns.
- Ripple current in inductors is 2A at 384kHz in idle.

Minds in Motion

Implementation of TAS5142

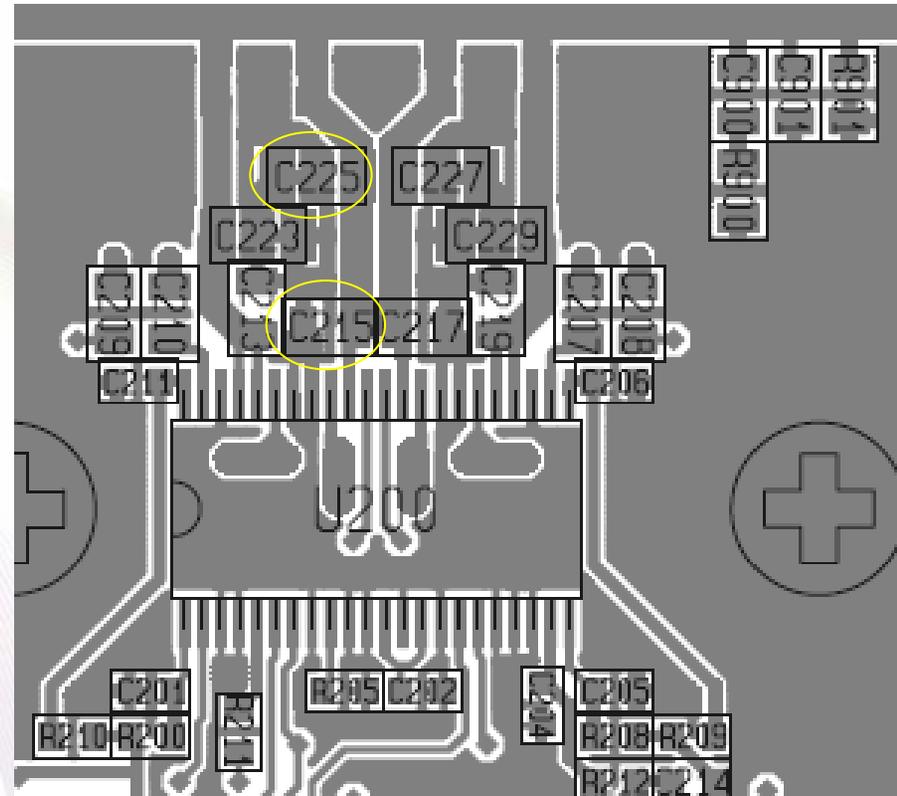
- Decoupling capacitors must be placed close to the device.
 - Return path should be on the top PCB layer (with the device)
- High power and high frequency paths must be routed with as few vias as possible.
- A via has 5nH to 7nH of inductance.



Minds in Motion

PCB Ground Domains

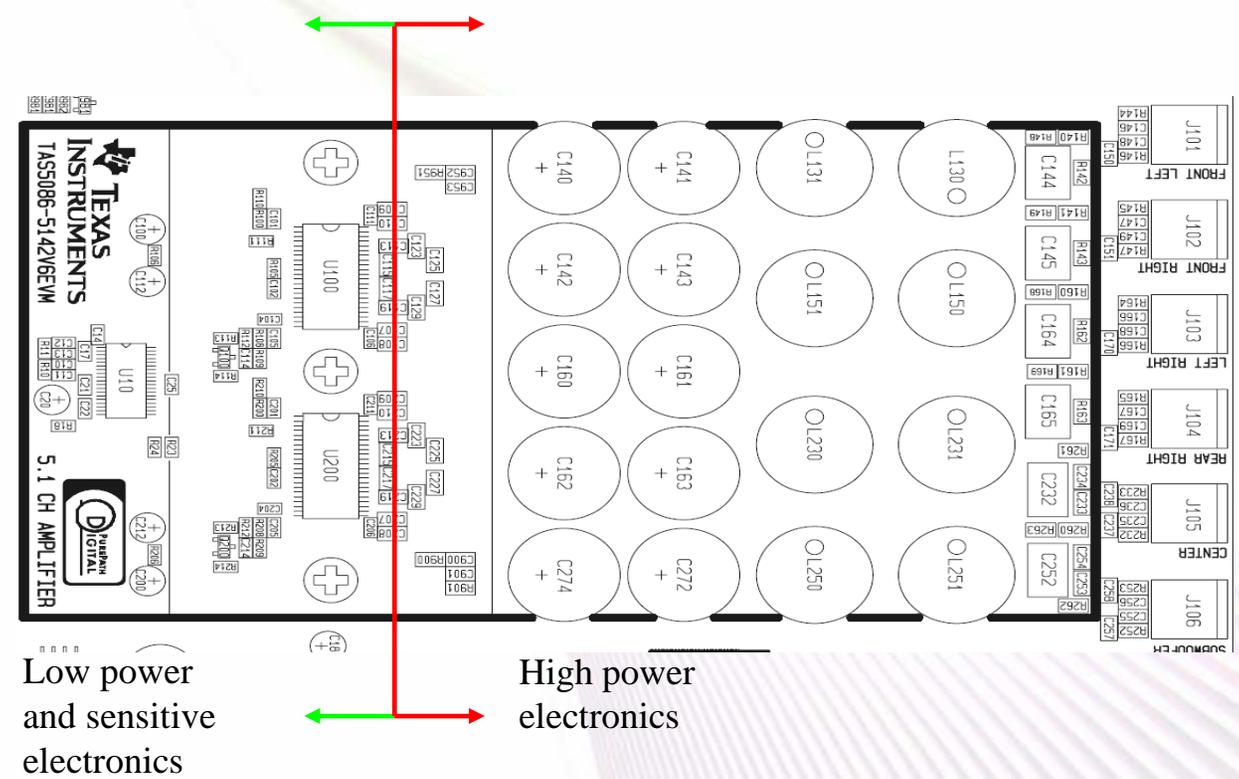- PCB must be divided into a high power zone and a low power zone.




This does not mean split the plane! (or you may develop a "Contentious Plane")

Minds in Motion

Spike Voltage

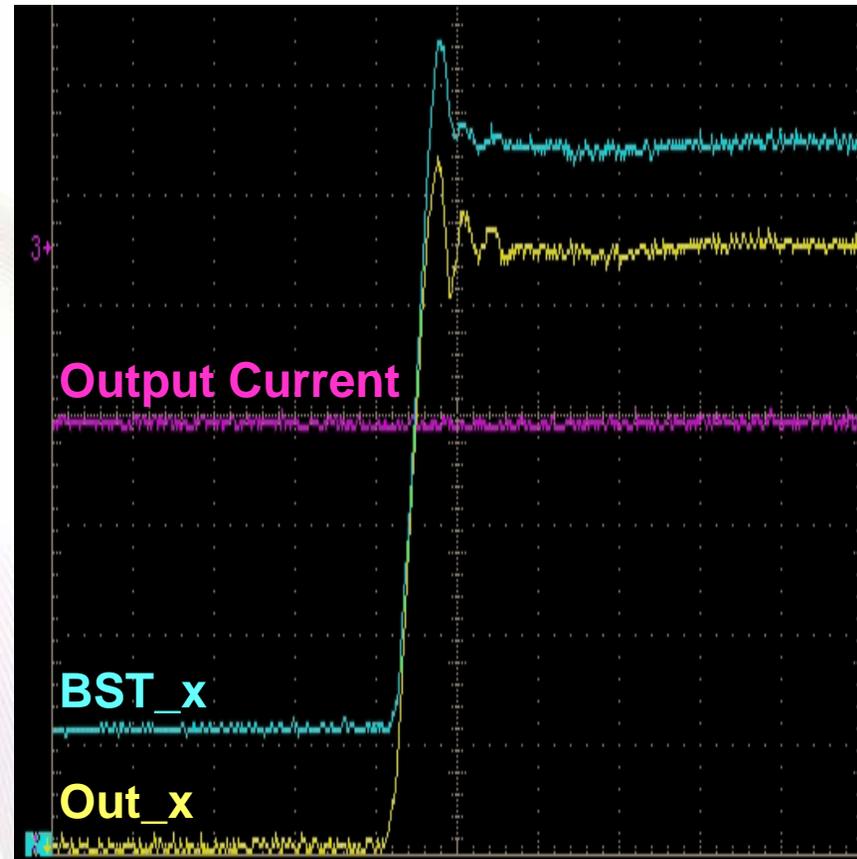- Spike voltage is the voltage overshoot on the output pins.
- Its amplitude is a function of current and is maximum during an error event (short circuit).
- The Absolute Maximum Voltage specified for the device includes the spike voltage.



Minds in Motion

Voltage Spike Reduction

- Good PCB layout
 - Careful placement of close decoupling caps
 - PVDD bulk cap close to power stage
 - Good ground plane
- Use Transient Voltage Suppressors (TVS)
 - Bi-Directional TVS should be used
 - 1SMAxxx series for all designs except TAS5261 and the TAS5162
 - 1SMBxxx for the TAS5261 and the TAS5162
 - TVS's will also decrease system issues with ESD
- Spike Voltage will adversely impact device reliability and cause EMI problems.


Minds in Motion

Key Components – and their Critical Parameters



Simplified Amplifier Diagram

Power Stage is S1 and S2

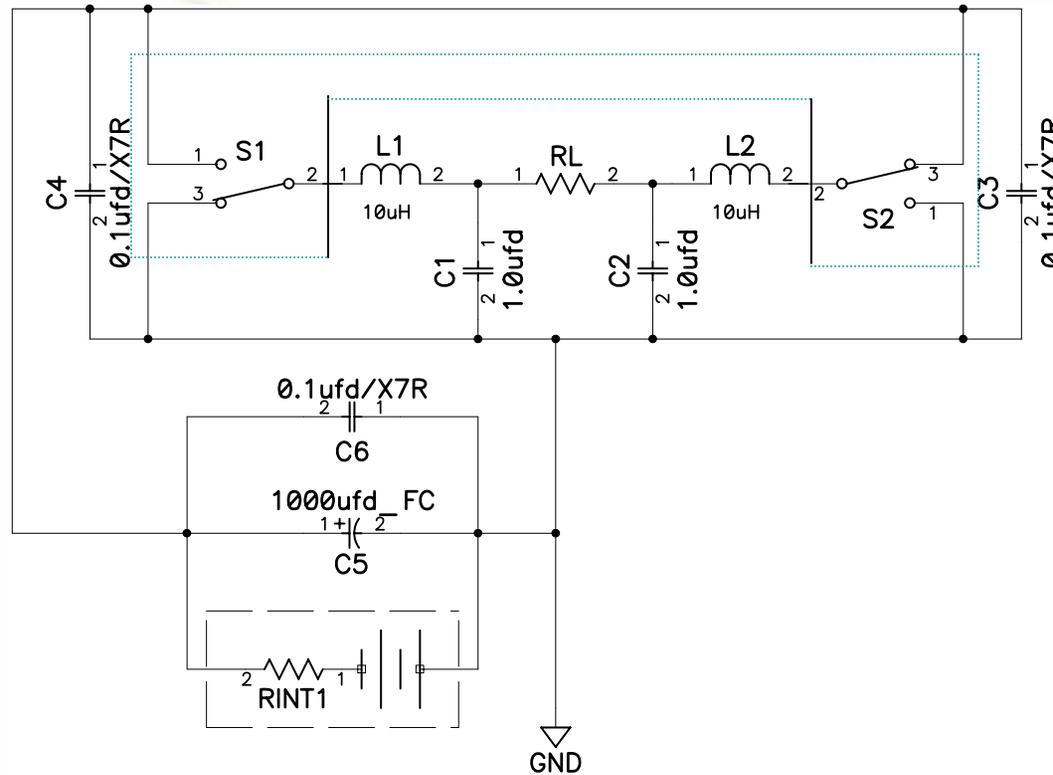

Minds in Motion


Amplifier Component Considerations

- Choice of components sets the audio performance.
- MOSFET Switches (taken care of by the power stage)
- PWM Filter Capacitor (use a film capacitor)
 - Stability with voltage
 - Ripple Current
- Inductor (use TI recommended)
 - Series resistance (dc), skin effect (ac)
 - Parallel resistance (hysteresis loss)
 - Parallel capacitance
 - Saturation in core material
- Decoupling capacitor (use X7R)
 - Series resistance
 - Series inductance
- Bulk Capacitor (Use low ESR)
 - ESR
 - ESL
 - Ripple Current
- PSU
 - Output impedance
 - Current limitation
 - Current Slew-rate
 - Surge Capability

Minds in Motion

Inductors: Inductance vs Current

- Inductance versus current diagrams are typically shown in the datasheet for an inductor.
- In order to have a proper working current limitation there must be $> 5\mu\text{H}$ inductance at 2x the programmed current limit. Worst case test condition is short at the output.
- Note that the saturation current decreases with temperature.
- Any variation in inductance within the operating area will result in increased THD. This is normally seen above 1kHz.

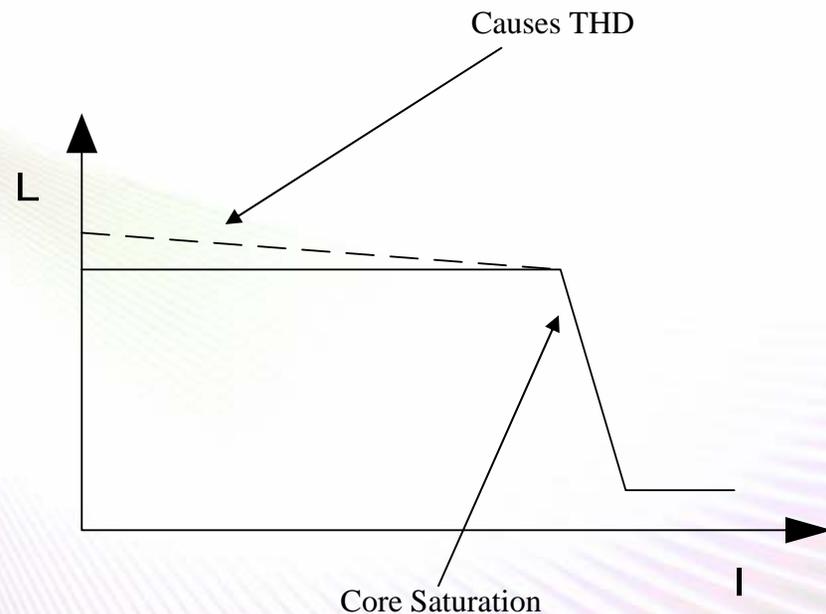


Minds in Motion

Inductor Losses

Parallel Impedance Model

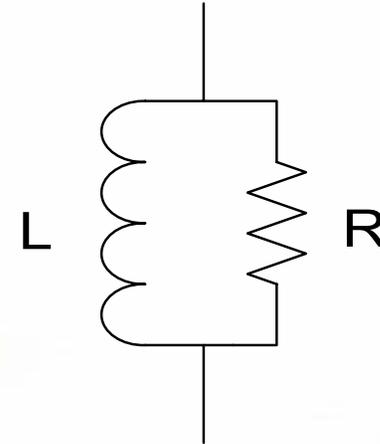- When measuring an inductor a Parallel Impedance model can be used.
- The model assumes an ideal inductor in parallel with an ideal resistor.
- Applying this model when measuring at 100kHz gives an indication of idle power losses.



100kHz Measurements	Measured Inductance	Measured Parallel Resistance
Bad Inductor	9.8 μ H	53.4 Ω
Medium Inductor	11.5 μ H	125 Ω
Good Inductor	10.2 μ H	220 Ω

Minds in Motion

More Info

- Magnetics Design Handbook, MAG100A, (Texas Instruments)
 - Available from TI Website

Minds in Motion

PWM Filter Capacitor Considerations

- Capacitor Types
 - Metal Film Capacitors, linear over applied voltage
 - Ceramic X7R, change value over applied voltage resulting in increase THD
- SMD – Leaded
 - SMD capacitors, especially ceramic capacitors, change physical size over applied voltage.
 - This will result in audible noise and mechanical stress of the part and its soldering.

Minds in Motion

TI | **Developer Conference**
March 7-9, 2007 • Dallas, TX

Minds in Motion

Putting It All Together



Technology for Innovators™

 **TEXAS INSTRUMENTS**

Components

- Choice of components sets the audio performance
- MOSFET Switches S1 & S2 (Power Stage)
 - TAS5132, 0W to 25W, 2 Channels
 - TAS5142, 0W to 100W, 2 Channels
 - TAS5152, 0W to 125W, 2 Channels
 - TAS5162, 0W to 210W, 2 Channels
 - TAS5261, 0W to 315W, 1 Channel
 - TAS5186, 210W Total Power, 6 Channel
- Modulators
 - TAS5086, Low cost, 6 Channel
 - TAS5508B, 8 Channel, Feature Rich
 - TAS5518A, 8channel, Feature Rich, High Performance
- PWM Filter Capacitor (Use a film capacitor)
 - Generally .47 μ for AD Mode Filter
- PWM Filter Inductor (Use TI recommended)
 - Generally 10 μ H
- Decoupling capacitors (Use X7R)
 - 0.1 μ F is a good rule of thumb
 - Select voltage for PVDD + Overshoot + Temperature Derating
- Bulk Capacitors (Use low ESR)
 - 1000 μ F Good rule of thumb
 - Select voltage for PVDD + Overshoot + Temperature Derating
- PSU
 - Output impedance
 - Current limited
 - Current Slew-rate
 - Surge Capability

Minds in Motion

Getting Started

- TI has a complete library of EVMs and reference designs @ www.ti.com -- follow the design carefully .
- Contact your local TI FSE for assistance.

Minds in Motion