

Which Is Better? Discrete or Combined Controllers for an AC/DC Power Supply?



VA Viswanathan

If you have ever listened in on typical hallway conversations in a power-supply design company, it's likely you have heard a spirited debate on whether the right way to design a >75W power supply involves the architecture shown in [Figure 1](#) or [Figure 2](#). The power-supply components in both cases are exactly the same; the only difference is the controller.

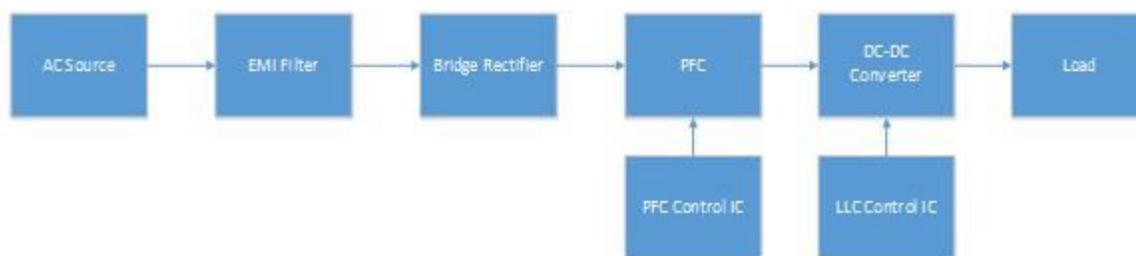


Figure 1. Discrete Controller IC-based AC/DC Design

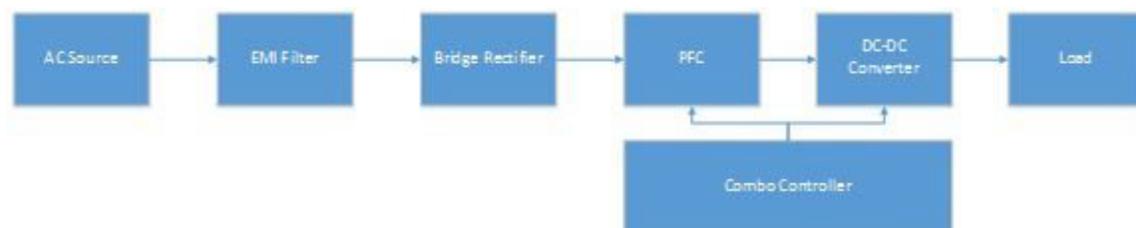


Figure 2. Combo Controller IC-based AC/DC Design

Texas Instruments has supporters on both sides of the debate, and a track record of products to back both solutions.

Notwithstanding the length and breadth of TI's product portfolio in the combination or "combo" controller space and the ability to get more features within the same solutions, I still subscribe to the argument that in the long run, a stand-alone power factor correction (PFC) controller followed by a stand-alone DC/DC converter offers an unparalleled set of advantages for engineers designing a wide range of applications, especially in the current cost-conscious consumer space.

Layout

Most power-supply designers will tell you that the technical aspect of the power-supply design that comes back to haunt them most is the printed circuit board (PCB) layout. A bad layout is a good recipe for a one-way ticket to Nowheresville. Power supplies come in all shapes and sizes, and require very different layout considerations depending on the form-factor requirements.

The following image shows the form-factor-compliant [Slim 150 Watt LED TV Power Reference Design](#). Note that there is a fair amount of space between components. Also, the "slim" requirements in a television force the layout to be ultra-low profile, making the large components on the board look like my son's kindergarten class during recess/naptime. The PFC stage and inductor-inductor-capacitor (LLC) stage are far away from each

other, making it extremely hard for a combo controller to have an optimal layout. Discrete solutions have no such problem, since the controllers reside right next to their respective power-stage components.

The following image displays the form-factor-compliant [High Efficiency 350W AC/DC Power Supply Reference Design](#) for industrial power supplies. Here is a space-constrained design that looks more like downtown Dallas than a low-cost two-layer PCB layout. Having a single combo controller to which signals are routed is no different than wanting a single massive parking lot catering to the whole of Manhattan fed by single-lane alleys ... good luck getting in and out.



Figure 3: TV power supply



Figure 4: Industrial power supply

The uniqueness of power-supply requirements and the one-size-fits-all nature of combo controllers fundamentally do not jive. Some power supplies are constant current, some are constant voltage, some require high total harmonic distortion (THD), some require low standby, some are meant to be fixed load – but almost none need all of these things. Using such a solution for your application can become a bit of overkill. **"Some power supplies are more equal than others"**

As long as the diversity of the power supplies continues to exist, there will always be logical reasons where a 2-IC solution may be a much better fit for your applications and the coffee pot in the hallway nearest to my desk will continue to get its broad patronage...

Discover the [controllers](#) that TI is currently offers to target these applications.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated