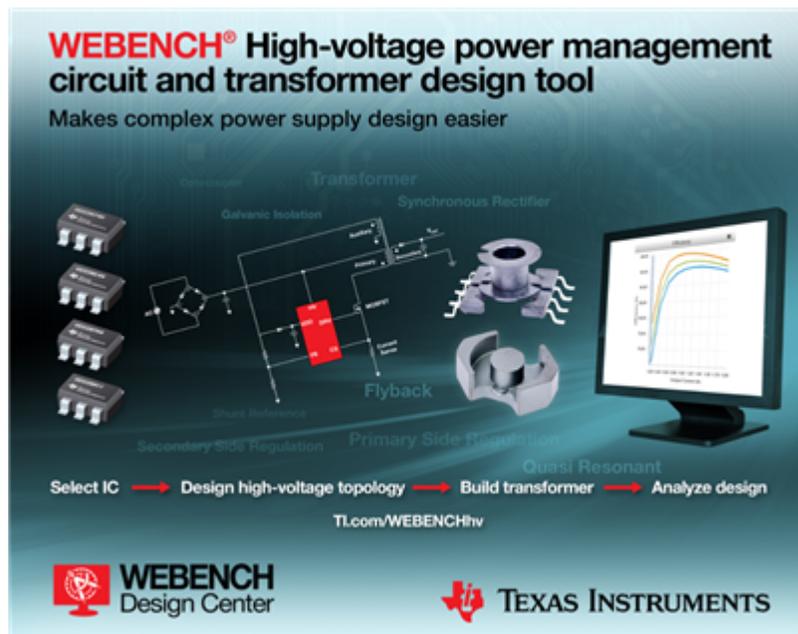


How to Simplify High-Voltage Power-Supply Design



Gerold Dhanabalan



High voltage power supplies are ubiquitous whether you are designing an AC/DC adapter or your high voltage on-board power supply for industrial applications. You find them commonly to step down your high voltage input voltage to a lower intermediate voltage before you power your point-of-load (POL) converters. The design of these front-end power supplies pose unique challenges from the requirements that they have. This post is intended to give you a basic understanding of high-voltage power-supply design, and how design tools can make it simple to design for these applications. There are three main things that you need while designing for your AC/DC or high-voltage DC/DC application.

1. Understand Your System Requirements.

Most of you know where your end equipment will be used and whether you will need a universal voltage range (85V to 265V) or region-specific voltages such as U.S. (120V), Japan (100V), U.K. (230V) or China (220V). Also, are you designing for a charger-type application or an on-board power supply? Are you designing for a supply that needs tight output-voltage regulation? What type of isolation requirements do you have?

The answers to each of these questions will help you make appropriate trade-offs while you design. Designing for universal voltage ranges ensures operability across different parts of the globe at the expense of higher voltage-/current-rated components, which come at a higher price and footprint. Charger-type supplies typically require a constant-voltage/constant-current (CV/CC) characteristic. So selecting a controller that meets this requirement is essential.

If your power supply requires tight regulation of the output, you need to consider secondary-side regulated controllers that tightly regulate the voltage on the secondary, versus primary-side controller regulators where the output could vary with changes in the transformer or secondary diode parameters. Certain applications require that your transformer provide a certain class of isolation for safer, robust end equipment.

TI's **WEBENCH® High-Voltage Power Designer** is an easy to use tool to design your AC/DC or HV-DC/DC applications. You simply enter your voltage and current requirements and find solutions that work for your application. With the optimizer dial, you can optimize your design for cost, footprint and efficiency based on your system needs. To get started, visit the **WEBENCH panel** on ti.com. **Figure 1** shows a view of the power solutions generated by WEBENCH Power Designer.



Figure 1. WEBENCH Power Designer with High Voltage Solutions

Figure 2 shows an AC/DC flyback using primary-side regulation that provides a low-cost, low-footprint solution, as well as loose regulation of the output on the secondary. **Figure 3** shows an AC/DC flyback in secondary-side regulation using optocoupler feedback, which is more expensive but provides tighter regulation on the secondary.

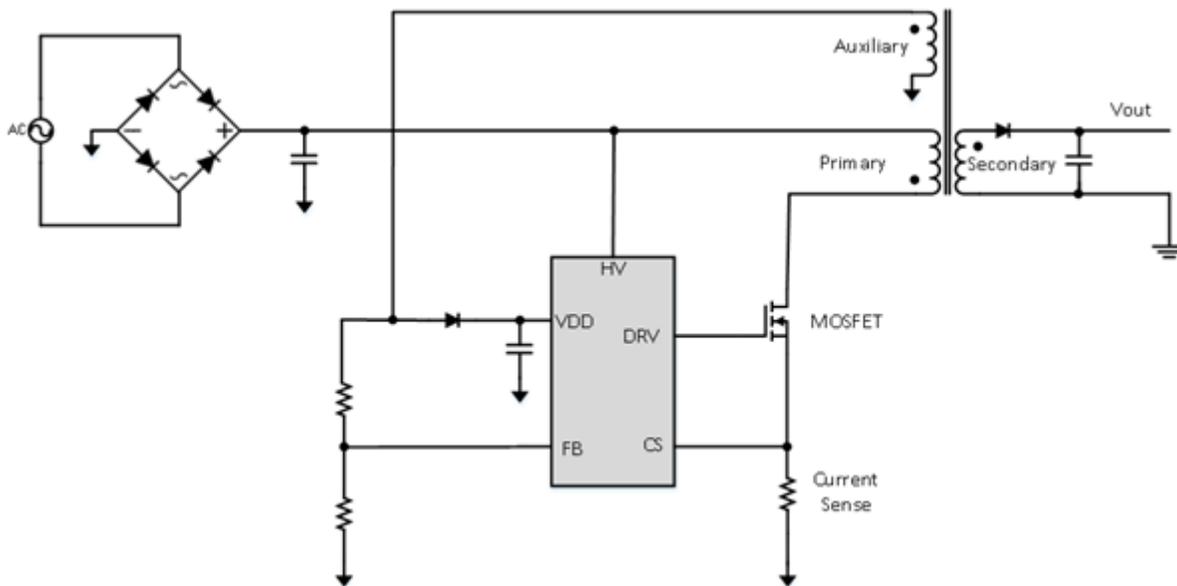


Figure 2. AC/DC Flyback with Primary-side Regulation

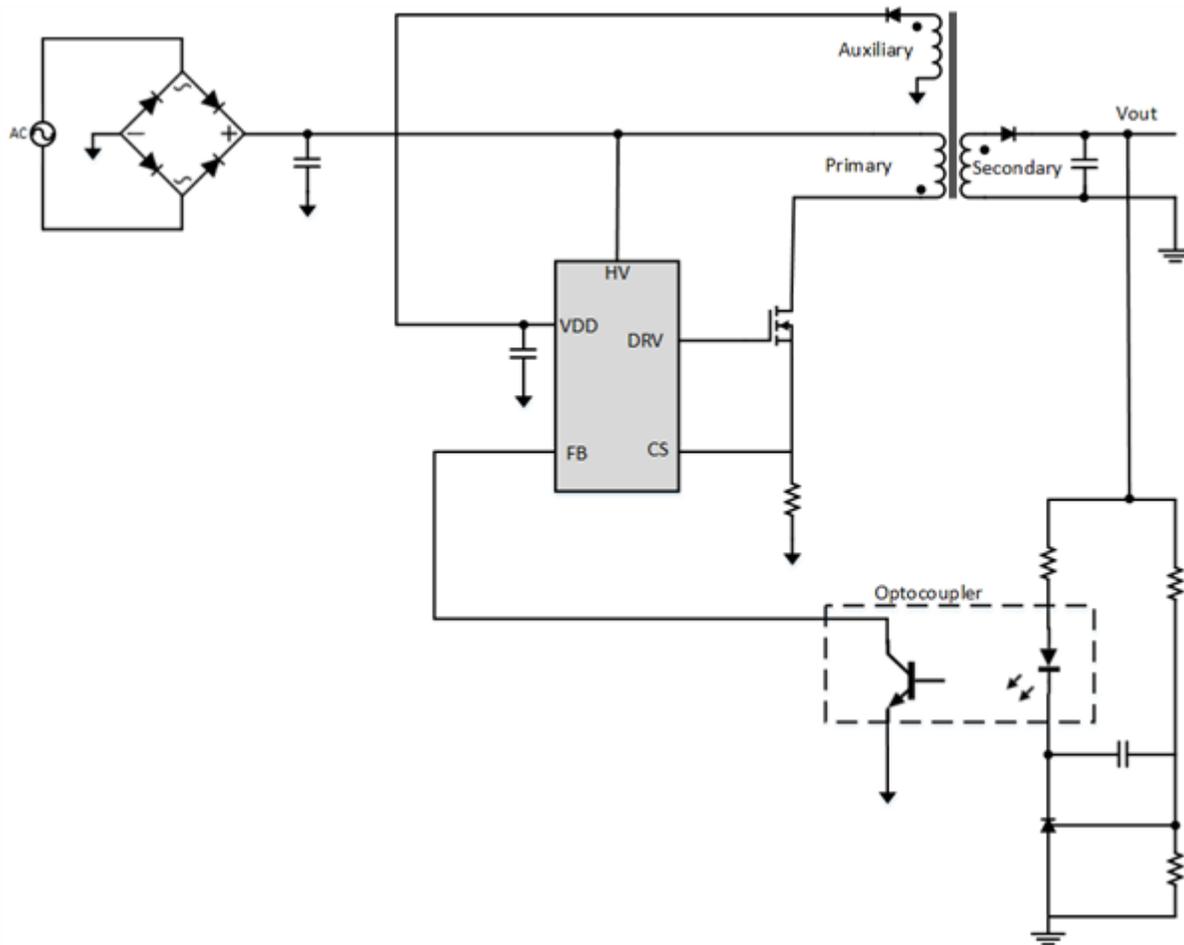


Figure 3. AC/DC Flyback with Secondary-side Regulation Using Optocoupler Feedback

2. Select the Right Topology/control Scheme.

At low power (greater than 10W and less than 100W), flyback is the most widely used topology. Forward and half-bridge topologies typically serve power levels from 100W to 500W, with full-bridge topologies serving >500W. Theoretically, you could build a flyback for high power levels too, but the voltage/current stress on the components makes this topology require higher voltage-/current-rated components, which are expensive and bulky. This paves the way for the natural adoption of other topologies at higher power levels.

You could design the controller to operate in continuous conduction mode (CCM) (the magnetizing current in the transformer does not reach zero), discontinuous conduction mode (DCM) (the magnetizing current reaches zero and stays zero till the next switching cycle), or transition mode (TM) (the magnetizing current reaches zero and the next switching cycle starts immediately). CCM is typical for higher power levels, while DCM and TM provide lower-loss solutions.

WEBENCH Power Designer saves you time and effort by creating the complete design for the topology using the necessary equations depending on the device and its operating mode. The tool also lets you evaluate efficiency and also other parameters such as output ripple, the RMS currents, losses etc. at various operating points within the design range.

3. Design Your Transformer.

One of the main things required in a good high-voltage power supply design is designing the transformer correctly for your applications. The transformer is generally the energy-conversion element in a high-voltage design, which also provides isolation between the primary and secondary.

By definition, transformers do not store energy, but transfer energy from the primary to the secondary. This is one of the main reasons why people refer to flyback transformers as coupled inductors, because components in the flyback topology store energy during the on-time of the switching cycle and then transfer that energy to the secondary during the off-time.

Transformers typically have a core (which is the magnetic element); the bobbin (or coil former), which is the plastic housing for the core (see Figure 4); and the wire that gets wound on the core-bobbin structure.



Figure 4. Core, Coil Former and Assembled Transformer

Assembled pre-built transformers are readily available from manufacturers with a fixed turns ratio (N_s/N_p) and primary inductance (the magnetizing inductance of the transformer that causes energy to build up). Depending on the operating frequency and output power levels, the requirements for the primary inductance and the turns ratio vary widely, and a pre-assembled off-the-shelf transformer might not be available. In such cases, selecting a transformer core and bobbin and winding the transformer will be necessary. This requires an in-depth knowledge of transformer magnetics.

WEBENCH design tools now give you the ability to design the transformer by selecting the core and bobbin that meet the requirements and also provides the winding structure details as well. You can click on the transformer symbol in the schematic to view and download the transformer details and also to change the transformer core/bobbin combination. Figure 5 shows a view of the transformer design window giving you the various core/bobbin combinations for a specific design requirement. You can also compare different transformers in terms of height, losses (core/copper losses), footprint and cost. If you have a preference for a specific core type or material, use the transformer listing to pick the one that is appropriate for your needs.

The transformer construction diagram gives you instructions on how to wind the transformer. This along with the transformer construction details table gives you information on the number of layers, strands, the AWG of the wire and more. You can also download the transformer design report as shown in Figure 6 to get this information. This will simplify your effort to build the transformer whether you are prototyping it yourself or having it wound by a transformer winding company.

TRANSFORMER DESIGNER

Recommended Transformer (See Details below): Core=B66317G000X127_CoilFormer=B66208W1010T001

Core 3D View

Bobbin 3D View

Transformer Electrical Diagram

Transformer Construction Diagram

Transformer Electrical Properties

Property	Value
Primary Inductance(mH)	780.0
Flux density(T)	0.25
Skin depth(mm)	0.27
Core Area(cm ²)	52.5
Frequency(kHz)	59.83
DMax	0.6
Primary Peak Current(A)	1.58
Primary RMS Current(A)	0.27
Secondary Peak Current(A)	14.8

Transformer Construction Details

Property	Value
Primary Turns	54
Primary AWG	27
Primary Insulation	Heavy Insulated Magnet Wire
Primary Layers	3
Primary Strands	1
Secondary Turns	10
Secondary AWG	26
Secondary Insulation	Triple Insulated
Secondary Layers	2

Search Found 4 Transformers

Select	Transformer	Apply	Top View	Manufacturer	Orientation	Core Type	Core Material	Transformer Cost(\$)	Transformer Footprint(mm ²)	Transformer Height(mm)	Transformer Losses(W)	Core Losses(W)	Copper Losses(W)
<input checked="" type="radio"/>	Core=B66317G000X127_CoilFormer=B66208W1010T001	Apply to Design Download Transformer PDF		Core-TDK, CoilFormer-TDK	V	E25137	N27	\$0.79	476	26	2.420	1.210	1.210
<input type="radio"/>	Core=B66317G000X187_CoilFormer=B66208W1010T001			Core-TDK, CoilFormer-TDK	V	E25137	N87	\$0.77	476	26	3.820	1.510	1.510
<input type="radio"/>	Core=B66317G000X127_CoilFormer=B66208W1010T001			Core-TDK, CoilFormer-TDK	H	E25137	N27	\$0.81	776	17.800	2.420	1.210	1.210
<input type="radio"/>	Core=B66317G000X187_CoilFormer=B66208W1010T001			Core-TDK, CoilFormer-TDK	H	E25137	N87	\$0.80	776	17.800	3.820	1.510	1.510

Figure 5. Transformer Design Capability in WEBENCH



WEBENCH® Transformer Report

Design: Z36228M5799 UCC28C42DR
 UCC28C42DR 85.0V-365.0V @ 12.00V @ 4.0A

#	Name	Value
1.	Core Part Number	B66317G0000K127
2.	Core Manufacturer	TDK
3.	Coil Former Part Number	B66208W1010T001
4.	Coil Former Manufacturer	TDK


Transformer Electrical Diagram

Primary

Turns	94
AWG	27
Layers	3
Strands	1
Insulation Type	Heavy Insulated Magnet Wire

Auxiliary


Turns	12
AWG	24
Layers	1
Strands	2
Insulation Type	Heavy Insulated Magnet Wire

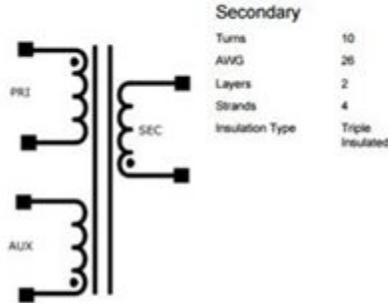

Secondary

Turns	10
AWG	26
Layers	2
Strands	4
Insulation Type	Triple Insulated

Transformer Construction Diagram

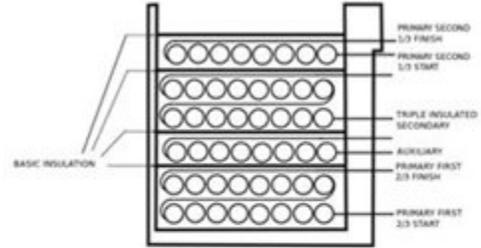

Winding Instruction

Winding	AWG	Turns	Winding Orientation
Primary First 2/3	27	65	Clockwise
Auxiliary	24	12	Counter Clockwise
Triple Insulated Secondary	26	10	Counter Clockwise
Primary Second 1/3	27	31	Clockwise

Transformer Parameters

#	Name	Value
1.	Len	7.864in
2.	Insulation Factor(s)	800V
3.	Npt	94
4.	Nsec	10
5.	Naux	12
6.	Core Type	E29x19T
7.	Core Material	N27
8.	Wire	0.207
9.	Switching Frequency	35.00kHz
10.	Drift	0.0
11.	spc(Primary)	1.564
12.	spc(Secondary)	0.774
13.	spc(Auxiliary)	14.84

Figure 6. Transformer Design Report

Additional Resources

- Start a [design](#) in WEBENCH high voltage designer with TI's [UCC28C42](#) high-performance, current-mode PWM controller.
- Access thousands of power supply reference designs from the [TI Designs library](#).
- Download "[Control Challenges for Low Power AC/DC Converters](#)" from the 2014 Power Supply Design Seminar (myTI login required).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated