

Predicting Output-capacitor Ripple in a CCM Boost PFC Circuit



Colin Gillmor

The output capacitor is the main energy storage element in a boost [power factor correction \(PFC\)](#) circuit ([Figure 3](#)); it is also one of the larger and more expensive components. Many factors govern its choice: the required capacitance, ambient temperature, expected service life and physical room available. In this post, I want to look at the ripple current that flows in the capacitor. The most accurate way to predict the ripple current is to do a numerical simulation, but there are some simple formulas that can give you a fairly accurate estimate of the currents, as well as some insight into how these currents vary with operating conditions.

Capacitance

As I said, the output capacitor is a relatively expensive component, so you will likely choose the minimum amount of capacitance that still will enable the design to meet its specification. All other things being equal, a smaller capacitor will have a lower cost than a larger one. Two main considerations determine how much capacitance you will need: the required holdup time and the allowable ripple voltage.

For the required holdup time, you can use Equation [Figure 1](#) to calculate the required capacitance:

$$C_{out} = \frac{2 P_{out} t_{hu}}{V_{initial}^2 - V_{final}^2} \quad (1)$$

Figure 1. (1)

where P_{out} is the power taken from the output capacitor, t_{hu} is the required holdup time, and $V_{initial}$ and V_{final} are the initial and final capacitor voltages, respectively.

If holdup time is not important, then you can size the capacitor according to the allowable voltage ripple. Equation [Figure 2](#) gives C_{out} as:

$$C_{out} = \frac{I_{out}}{2 * \pi * f_{line} * V_{ripple}} \quad (2)$$

Figure 1. (2)

where I_{out} is the load current and V_{ripple} is the peak-to-peak voltage ripple on the capacitor.

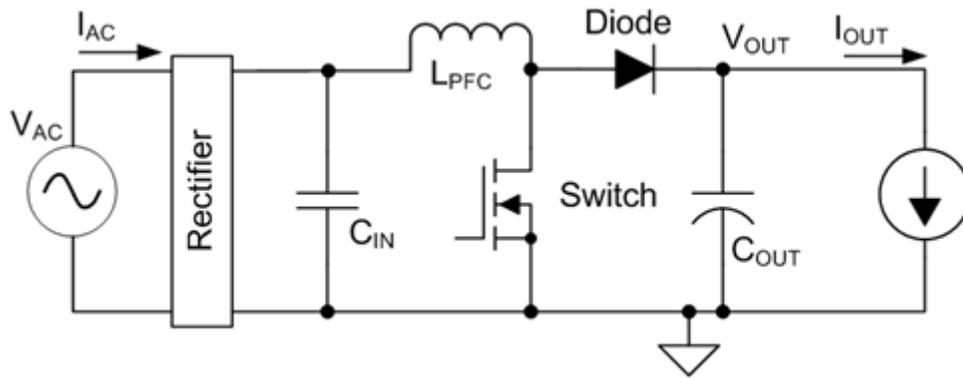


Figure 1. Typical Boost PFC Schematic

Capacitor Current

A rearranged Equation [Figure 2](#) can determine the low-frequency ripple voltage on the capacitor. This ripple is sinusoidal, provided that the line current drawn by the PFC stage is sinusoidal. It will be at twice the line frequency and you can calculate the ripple voltage's peak-to-peak amplitude with Equation [Figure 4](#):

$$V_{ripple} = \frac{I_{out}}{2 * \pi * f_{line} * C_{out}} \quad (3)$$

Figure 2. (3)

The low-frequency ripple current in the capacitor is very simply related to the output current. Equation [Figure 5](#) gives the RMS (Root Mean Square) value of the current because most capacitors are specified in terms of RMS ripple currents. The result here agrees closely with numerical simulation results:

$$I_{r_lf} = \frac{1}{\sqrt{2}} I_{out} = \frac{1}{\sqrt{2}} \frac{P_{out}}{V_{out}} \quad (4)$$

Figure 2. (4)

The ripple current also has a high-frequency component at the PFC switching frequency and its harmonics in addition to the component at twice the line frequency. You can use a slightly modified version of the formula in Erickson and Maksimovic's "Fundamentals of Power Electronics" to calculate the RMS total capacitor ripple current. This formula ignores the effect of inductor switching-frequency ripple current and thus underestimates the current when compared to a numerical simulation. This underestimation becomes proportionally greater at high line, but because ripple currents are greatest at low line, Equation [Figure 6](#) is accurate to better than about 10%:

$$I_{r_tot} = I_{out} \sqrt{\frac{16}{3\pi} \frac{V_{out}}{\sqrt{2} V_{ac}} - 1} \quad (5)$$

Figure 2. (5)

The high-frequency component of the capacitor current is then the total current minus the low-frequency current. The result that Equation [Figure 7](#) gives is an RMS value:

$$I_{r_hf} = \sqrt{I_{r_tot}^2 - I_{r_lf}^2} \quad (6)$$

Figure 2. (6)

Some Things to Note

I looked at a single-phase CCM (Continuous Conduction Mode) PFC stage in this post, but the low-frequency ripple calculation is also valid for interleaved, CrCM (Critical Conduction Mode) and DCM (Discontinuous Conduction Mode) designs. The high-frequency ripple calculation is valid for single-phase CCM designs only, however.

Both low- and high-frequency ripple currents are not functions of the amount of capacitance. Low-frequency current is a function of the output power; it is not a function of line voltage. High-frequency ripple is greatest at low line and is a function of line, boost inductance and output power.

Check out TI's portfolio of analog, digital and combination [PFC controllers](#) or learn the basics of power factor with the blog post, "[What does a beer and power factor have in common?](#)"

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated