

Power Tips: Calculate an R-C Snubber in Seven Steps



John Betten

Ringing in switching power supplies can generate radiated and conducted noise, create circuit jitter and excessive dissipation, and easily overstress components. Ringing is a major concern in applications such as audio, processor power and any design that requires electromagnetic interference (EMI) qualification.

Often, you can tame the circuit by adding a simple resistor-capacitor (R-C) snubber to “damp out the ringing.” In this post, I’ll outline a seven-step procedure that can help take the guesswork out of selecting your snubber values.

Ringing can occur in any switching converter where an inductance and a capacitance form an inductor-capacitor (L-C) tank. The inductance may be from component leads, printed circuit board traces and transformer leakage, while the capacitance may be due to nonlinear components such as rectifiers and interwinding transformer capacitance. The ring frequency and amplitude are generally unknown since most circuit parasitics are typically unknown. Two common locations where excessive ringing occurs (at least in converters such as a flyback) are across the rectifier diode and the switching FET. One simple solution to reduce this ringing is by damping or “snubbing” it with a series R-C circuit, typically placed directly across the rectifier or FET.

The seven-step procedure shown in Table 1 uses a common methodology that shifts the resonant frequency of the ringing to calculate the circuit’s parasitic capacitance (C_o) and inductance (L). Once you know those, you can calculate the snubber capacitor (C_{snub}) and resistor (R_{snub}). I took the example waveforms in [Figure 1](#) and [Figure 3](#) with an R-C snubber placed in parallel with the rectifier in the [9Vdc-57Vdc Input, 56V/20W Isolated Flyback Reference Design](#), but the procedure is the same if used across the FET.


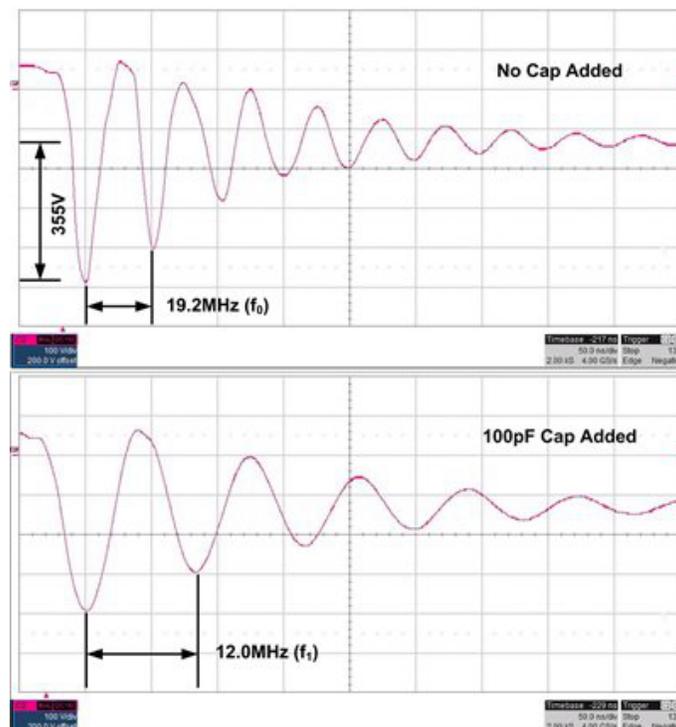


Figure 1. Unsnubbed Rectifier Ringing (Top) and Frequency-shifted Ringing (Bottom)

Seven steps to calculate an R-C snubber	
Step 1	Measure the circuit's oscillation frequency (f_0). See Figure 1 (top).
Step 2	Add a capacitor (C_1) in parallel with the rectifier or FET and measure the shifted oscillation frequency (f_1). Select a C_1 value that is several times larger than the rectifier's stated typical capacitance at full-reverse voltage in the data sheet. In this example, the rectifier's reverse capacitance is 22pF, so I chose a 100pF value for C_1 . A frequency shift of at least 50% is reasonable. See Figure 1 (bottom).
Step 3	Calculate the frequency shift ratio: $m = \frac{f_0}{f_1}$.
Step 4	Calculate the circuit's parasitic capacitance: $C_0 = \frac{C_1}{(m^2-1)}$.
Step 5	Calculate the circuit's parasitic inductance: $L = \frac{(m^2-1)}{(2\pi f_0)^2 C_1}$.
Step 6	Calculate the starting snubber capacitor value: $C_{snub} = 3 * C_0$.
Step 7	Calculate the starting snubber-resistor value: $R_{snub} = \sqrt{\frac{L}{C_0}}$.

Figure 3 shows the spike reduction and damping effect of the calculated values. You can adjust the ringing higher or lower by varying the C_{snub} value. Larger values for C_{snub} reduce the voltage-spike amplitude further, but increase power loss in R_{snub} .

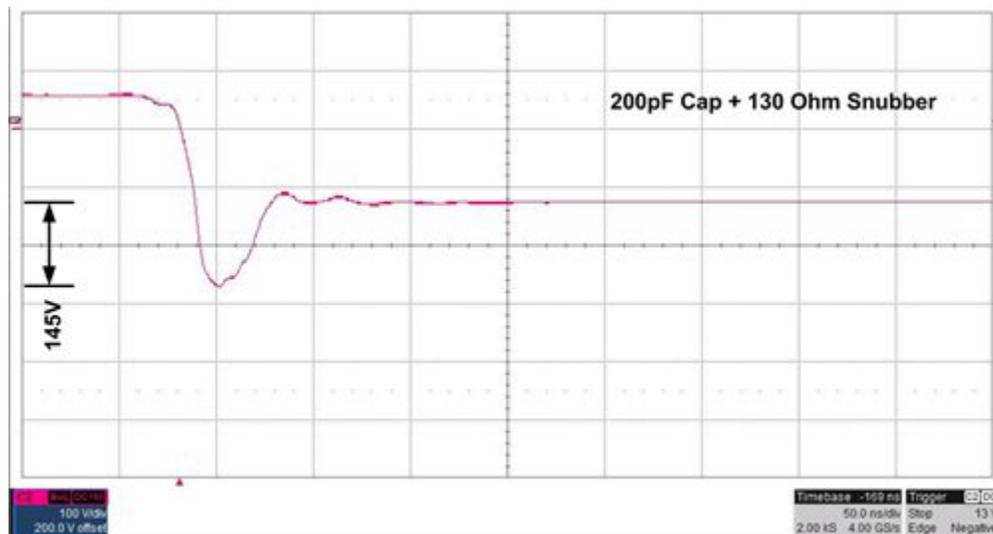Alternatively, you can decrease the power dissipation in R_{snub} by lowering C_{snub} , but ringing will increase. You must weigh the trade-off between acceptable voltage-ringing amplitude and R_{snub} losses.



Undamped ringing in switching converters can create excessive EMI and overstress components. A properly calculated R-C snubber can be instrumental in taming these issues. I hope you'll find my seven-step procedure simple to follow and a good starting point to help you damp out the ringing. For more about the topic covered here, see my EETimes Power Tips post [Calculating an R-C snubber](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated