

How to Get No-load Power Savings in AC to DC Supplies



James Lockridge

In the interest of reducing wasted power in consumer electronics, many government policy initiatives have been created to reduce no-load or standby power in AC to DC power supplies. Among these are the Environmental Protection Agency’s (EPA) ENERGY STAR and the European Union’s Standby Initiative. Last year, in an Analog Applications Journal article, TI’s Adnaan Lokhandwala discussed components commonly used in flyback supplies that dissipate a significant amount of standby power. In his article, Adnaan recommends using [flyback converter ICs](#) to reduce power by eliminating the optocoupler feedback circuit. However, this requires the power supply to be completely redesigned. Alternatively, by replacing the [TL431](#) with the [ATL431](#) standby power can be significantly reduced without significant redesign.

While the [TL431](#) is a popular device that has been used for years in flyback supplies, its minimum required cathode current of 1 mA dissipates significant standby power. TI’s new [ATL431](#) shunt regulator requires only 35 μ A for its cathode current. With its lower cathode current, the [ATL431](#) can be used to reduce the standby power dissipated by the feedback circuitry by a factor of 10 in designs that currently use the [TL431](#).

[Figure 1](#) shows the standard circuit of a flyback power supply. To ensure that the [TL431](#) remains biased, a resistor, R_{bias} , is placed in parallel with the optocoupler. Just to bias the [TL431](#), this circuit will dissipate 24 mW.

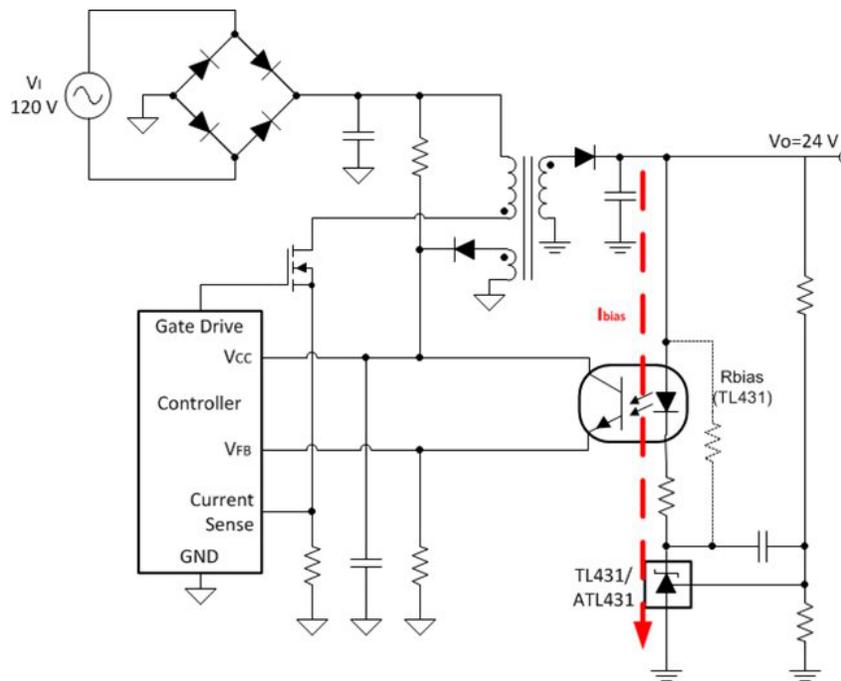


Figure 1. General Schematic of a Flyback Power Supply

Since the [ATL431](#) can operate well within the minimum current requirement for the optocoupler, the R_{bias} resistor is no longer needed. Using the [ATL431](#), the no-load power consumption drops by a factor of 20. [Table 1](#) illustrates the power savings of the [ATL431](#) in flyback supplies.

Table 1. Solution Comparison between the TL431 And ATL431

	Required minimum shunt regulator cathode current ($I_{KA(min)}$)	Required minimum current to bias the optocoupler	Power dissipated by components dissipating I_{bias}
TL431 solution	1 mA	50 μ A (R bias needed)	24 mW
ATL431 solution	35 μ A	50 μ A	1.2 mW

The [TL431](#) sets the required minimum bias current, I_{bias} , to 1 mA. This means that 1 mA will flow through the resistor, optocoupler, and shunt reference. In this case, the shunt reference sets the I_{bias} current.

When the design uses the [ATL431](#), the minimum cathode current is so low that the optocoupler is the component that sets I_{bias} . In this case, I_{bias} is 50 μ A. When less current is used for I_{bias} , the no-load power consumption of the design decreases.

The lower cathode current requirement of the [ATL431](#) shunt reference reduces no-load power consumption in any circuit that uses the [TL431](#). By substituting the [ATL431](#) for the [TL431](#), no-load power consumption and wasted energy can be reduced in any existing power design.

Additional Resources:

- Download the [ATL431 datasheet](#).
- Start your design in [WEBENCH Power Designer](#)
- Download the [ATL431 Pspice transient models](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated