Test Report: PMP23194

# Three-Output Reference Design for Automotive ADAS Including Power for Main Processor And Cameras



# **Description**

This reference design provides power for automotive advanced driver-assistance systems (ADAS) to power the cameras (8 V), controller area network CAN communications (5 V), and main processor (3.3 V). Operation is over the full automotive range including battery voltage surges to 34 V and dips to 6 V due to cold cranking. The design is low-noise to meet the stringent CISPR 25 Class 5 emissions requirements and includes an input filter. The board is designed for easy testing, providing jumpers to disable each output and an onboard dynamic load for the high-current 3.3-V output. The test report includes operational data on each output, and conducted emissions scans for the complete design against CISPR 25 Class 5.




**Board Photo (Top)** 

#### **Features**

- Three output automotive ADAS power supplies using one controller
- Operation over the full automotive battery range including cold cranking and surges
- Provides power for main processor, CAN communications, and cameras
- Designed for low emissions and includes input filter to meet stringent CISPR 25 Class 5 requirements
- Tested for both performance and emissions against CISPR 25
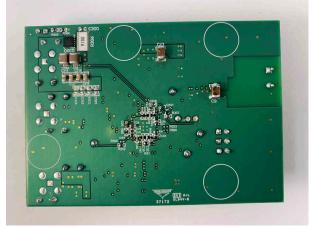
# **Applications**

- Driver monitoring
- Drive assist ECU
- Automotive thermal camera
- Camera module without processing



**Board Photo (Bottom)** 



# 1 Test Prerequisites

This section provides the testing guide used in the detailed testing of the three-output power supply.

## 1.1 Power and Load Connections and Test Points

Table 1-1 describes power and load connections. Table 1-2 lists the test point descriptions and devices.

**Table 1-1. Power and Load Connections** 

Connections	Description
J-BAT	V <sub>IN</sub> to LM5127-Q1 three-output power supply 9-V to 18-V steady state main power input 2 × 1 5.08-mm terminal block
J8 and J8R	8-V, 600-mA SEPIC output, 2 × Keystone 1212-ST (0.187 in [4.75 mm] Quick-connect male solder connector non-insulated)
J5 and J5R	5-V, 120-mA buck output, 2 × Keystone 1212-ST
J3 and J3R	3.3-V, 6.7-A buck output, 2 × Keystone 1212-ST

## **Table 1-2. Test Points**

Test Point	Description	Device
SP8	8-V output sense	MCX jack receptacle
TP801	Bode plot injection point for the 8-V loop	
TP1	Active low when any output active	
J55	Jumper to disable 5 V	TSW-102-07-G-S
J33	Jumper to disable 3.3 V	TSW-102-07-G-S
SP5	5-V output sense	MCX jack receptacle
TP501	Bode plot injection point for the 5-V loop	
SP3	3.3-V output sense	MCX jack receptacle
TP301	Bode plot injection point for the 3.3-V loop	
J300	Dynamic current monitor off the 3.3-V dynamic load	Receptacle, ultra miniature coaxial, male pin, 50- $\Omega$ , SMT
J301	Signal generator injection for the 3.3-V dynamic load	TSW-102-07-G-S
J302	Not used, was to change 3.3-V loop speed	

www.ti.com Test Prerequisites

Figure 1-1 shows the test setup.

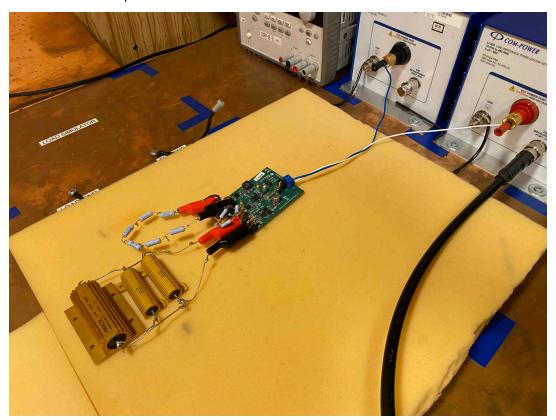


Figure 1-1. Test Setup for Conducted Emissions

# 1.2 Voltage and Current Requirements

Table 1-3. Requirements

Parameter	Specifications
Input Power	6-V to 18-V steady-state with surges to 42 V
8-V output	Load up to 600 mA
5-V output	Load up to 120 mA
3.3-V output	Load up to 6.7 A

## 1.3 Required Equipment

- V<sub>IN</sub> power supply 6 V to 18 V, at least 5 A
- · Resistive loads: Use actual resistors for conducted emissions testing
- Electronic load to step for efficiency graphs, and for dynamic load testing such as Kikusui PLZ334WL
- To connect onboard dynamic load for the 3.3-V output current sense, J300 to a BNC scope input: Taoglas CAB.011 (cable SMA jack) and Amphenol RF 095-850-250-024 [cable assembly coaxial BNC to SMA RG-316 DS 24.00 in (609.60 mm)]
- Signal generator with pulse mode such as Tektronix AFG3102
- Oscilloscope such as Tektronix MDO34 with TPP0500B 10 × voltage probes and 30-A TCP0030A current probe
- Digital multimeters such as Fluke 87iii or 87V
- For Bode plots: Vector Network Analyzer such as Bode 100 from OMICRON Lab
- Thermal camera such as FLIR E75
- Keysight 34970 data acquisition, switch unit along with calibrated 10-A and 1-A current shunts for efficiency measurements
- Automotive CISPR 25 conducted emissions setup with EMI receiver such as Rohde & Schwarz ESRP EMI test receiver



# 1.4 Considerations

When powering the board, the input voltage range must be 6 V to 18 V. All three outputs come up unless jumpers are placed on J88, J55, or J33 to disable the 8 V, 5 V, or 3.3 V, respectively. With each output loaded, switching frequency is approximately 440 kHz with dithering.

When testing for surges with input in the 18-V to 42-V range for more than a few seconds, use a fan blowing on the board.

## 1.5 Board Dimensions


3.4 in by 2.4 in

# 2 Testing and Results

## 2.1 Efficiency and Loss Graphs

Figure 2-1 through Figure 2-3 show the PMP23194 efficiency graphs for 3.3 V, 5 V and 8 V, respectively.

For the main 3.3 V with 22-W maximum output power, efficiency peaks at 95% at 10  $V_{IN}$ , just over 93% for 14  $V_{IN}$ , and about 91.5% for 18  $V_{IN}$ . For the lowest power 5 V with 0.6-W maximum output power, efficiency is in the 70%–80% range at 14  $V_{IN}$  and loading above 50% maximum load. For the 8 V with 4.8-W maximum output power, efficiency is in the 80%–86% range for loads at and above 2 W at all three input voltages tested.

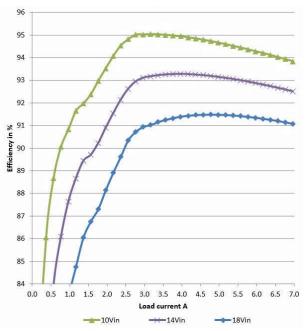

84 82 80 78 76 74 72 70 sucy 68 66 64 62 60 56 54 52  $0.00 \ 0.01 \ 0.02 \ 0.03 \ 0.04 \ 0.05 \ 0.06 \ 0.07 \ 0.08 \ 0.09 \ 0.10 \ 0.11 \ 0.12 \ 0.13$ Load current A **→**10Vin 

Figure 2-1. PMP23194 3.3-V DC/DC Converter Efficiency

Figure 2-2. PMP23194 5-V DC/DC Converter Efficiency


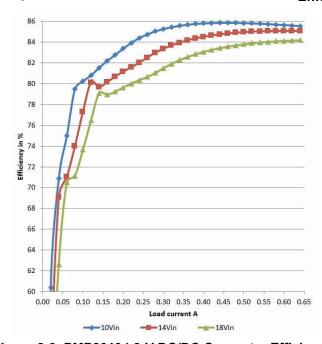


Figure 2-3. PMP23194 8-V DC/DC Converter Efficiency

Testing and Results www.ti.com

Figure 2-4 through Figure 2-6 show the loss graphs for 3.3 V, 5 V and 8 V, respectively. These loss graphs for all three outputs are shown from no load thru maximum load at the same input voltages. Losses in input EMI filters are not included here.

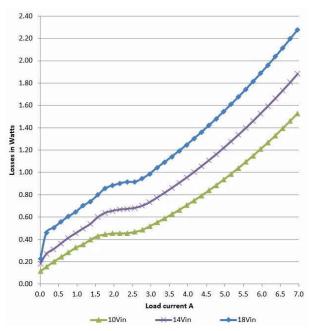

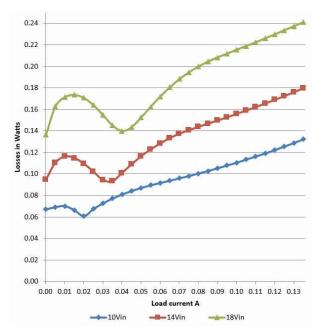


Figure 2-4. PMP23194 3.3-V DC/DC Converter Losses

Figure 2-5. PMP23194 5-V DC/DC Converter Losses

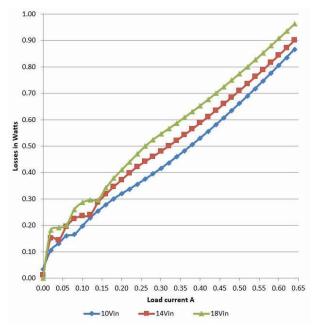


Figure 2-6. PMP23194 8-V DC/DC Converter Losses

## 2.2 Thermal Images

Figure 2-7 through Figure 2-10 show the worst-case thermal images. All outputs are loaded to their maximum; or 6.7 A off the 3.3 V, 120 mA off the 5 V, and 600 mA off the 8 V. Thermal images were taken at 10  $V_{IN}$ , 14  $V_{IN}$  and 18  $V_{IN}$ . Ambient is room temperature or about 22°C, and there are no fans blowing on the boards.

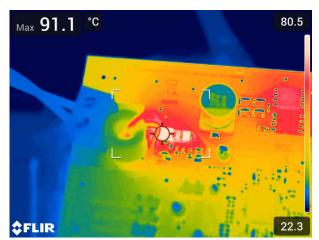


Figure 2-7. Input Reverse Protection Diode D1 Worst Case at 10 V<sub>IN</sub>, 91°C

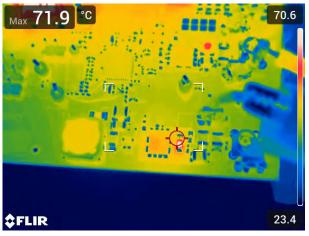


Figure 2-9. Output Rectifier of the 8-V SEPIC D2 Worst Case at 10  $V_{IN}$ , 72°C

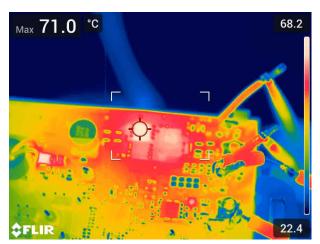


Figure 2-8. High-Side FET Q4 of the 3.3-V Buck Converter Worst Case at 18  $V_{IN}$ , 71°C

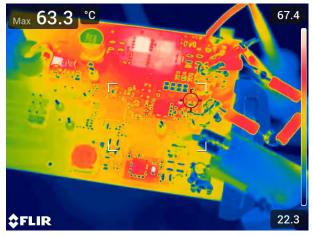


Figure 2-10. Main Inductor of the 5-V Buck L2 Worst Case at 18 V<sub>IN</sub>, 63°C

Testing and Results www.ti.com

#### 2.3 Bode Plots

Figure 2-11 through Figure 2-13 show the bode plots with 14 V<sub>IN</sub> for 3.3-V, 5-V, and 8-V outputs respectively.



Crossover at 32 kHz with 51 degrees of phase margin, -180 degrees shift at 86 kHz with 14-dB gain margin

Fixed Frequency 15.693 kHz -86.954 mdB 67.124° 1 kHz Start frequency 105.23 kHz -19.29 dB 119,222 m° Delta C2-C1 89.537 kHz 19,204 dB -67.004° m Stop frequency 300 kHz 180 60 Center 150.5 kHz 160 299 kHz 50 140 40 120 Sweep Linear Logarithmic 100 Number of points 201 Variable Constant (dB) 20 60 Reference level -20 dBm 🕏 1: Gain Magnitude 40 10 Shape level.. 20 0 Attenuator Receiver 1 Receiver 2 -20 20 dB ▼ 20 dB ▼ -10 -40 race Receiver bandwidth 30 Hz -20 -60 -80 -30 -100 -40 -120 -140 -50 -160 180 -60 1k Frequency (Hz)

Figure 2-11. 3.3-V, 3-A Bode Plot off 14 V<sub>IN</sub>

Crossover at 16 kHz with 67 degrees of phase margin, -180 degrees shift at 105 kHz with 19-dB gain margin

Figure 2-12. 5-V, 120-mA Bode Plot off 14 V<sub>IN</sub>




Crossover at 10 kHz with 49 degrees of phase margin, -180 degrees shift at 31 kHz with 14-dB gain margin

Figure 2-13. 8-V, 600-mA Bode Plot off 14 V<sub>IN</sub>

Testing and Results Www.ti.com

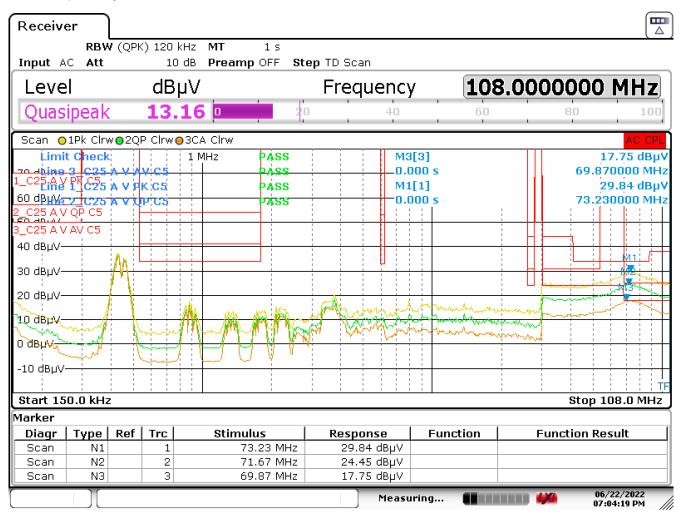
## 2.4 Conducted Emissions vs CISPR Class 5

See the test setup for conducted emissions in Figure 1-1. Conducted EMI scans over the full 150-kHz to 108-MHz range are shown in the following figures. All three PMP23194 models were tested with near maximum loading on all three outputs. Each scan shows the maximum peak detection trace, quasi-peak detection trace, and CISPR average detection trace. Limit lines shown are for CISPR 25 Class 5 peak, quasi-peak and average limits. Worst cases were around 70 MHz for both quasi-peak and average with less than 1-dB margin, and for maximum peak with 4- to 5-dB margin. All three models scanned show passing Class 5 and very similar results. The worst-case average and quasi-peak results varied less than 0.5 dB. The following scans are models t1, t2, and t3 respectively.



Date: 22.JUN.2022 19:04:19


Figure 2-14. Model t1 Conducted Emissions

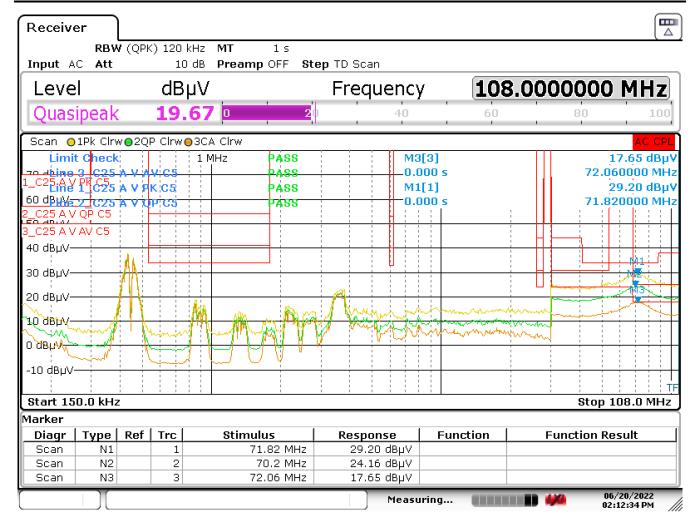

Date: 20.JUN.2022 14:12:34

Figure 2-15. Model t2 Conducted Emissions

Testing and Results www.ti.com

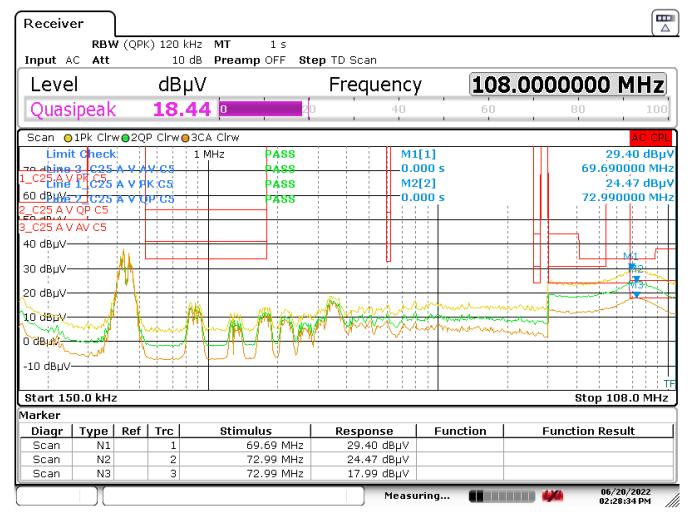

Date: 20.JUN.2022 14:28:34


Figure 2-16. Model t3 Conducted Emissions

www.ti.com Waveforms

## 3 Waveforms

# 3.1 Output Voltage Ripple


Figure 3-1 through Figure 3-3 show the output voltage ripple waveforms with switching frequency dithering turned on. Ripple is from the 11-kHz dithering of the main 440-kHz switching frequency dominated the overall output ripple for all three outputs.

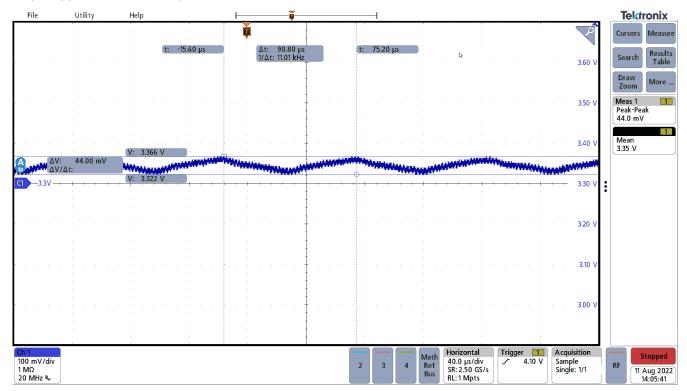

40 mV peak to peak


Figure 3-1. Output Voltage Ripple 3.3 V, 6.7 A off 14 V<sub>IN</sub>

Waveforms www.ti.com

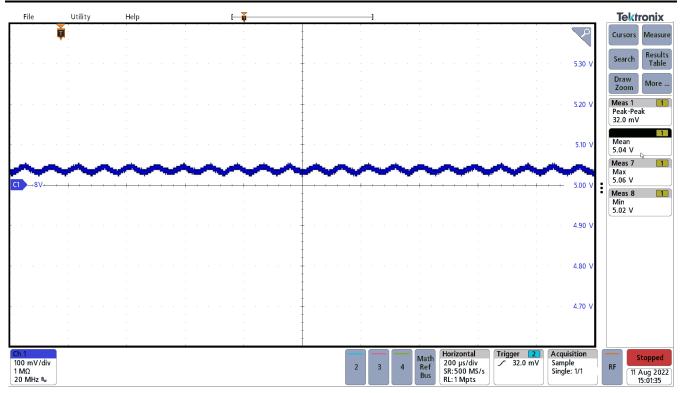

40 mV peak to peak

Figure 3-2. Output Voltage Ripple 5 V, 120 mA off 14  $V_{IN}$ 

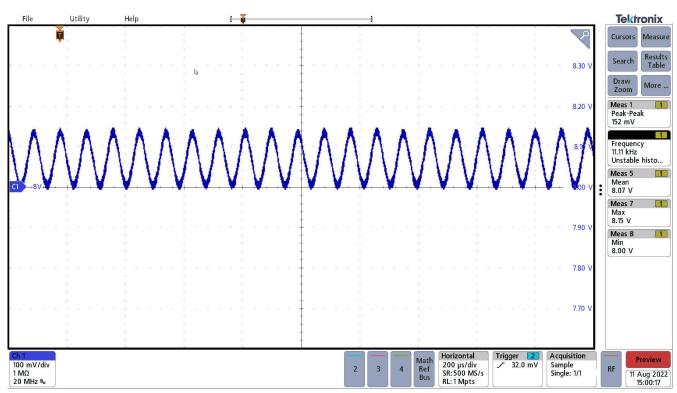


150 mV peak to peak

Figure 3-3. Output Voltage Ripple 8 V, 600 mA off 14 V<sub>IN</sub>

www.ti.com Waveforms

## 3.2 Load Transients


Figure 3-4 shows the load transient waveform at 8 V. The waveform was taken at 14  $V_{IN}$  with the load going from 3 A to 6.35 A and back to 3 A. The onboard dynamic load (J301 and Q300) was driven by Tektronix AFG3102.

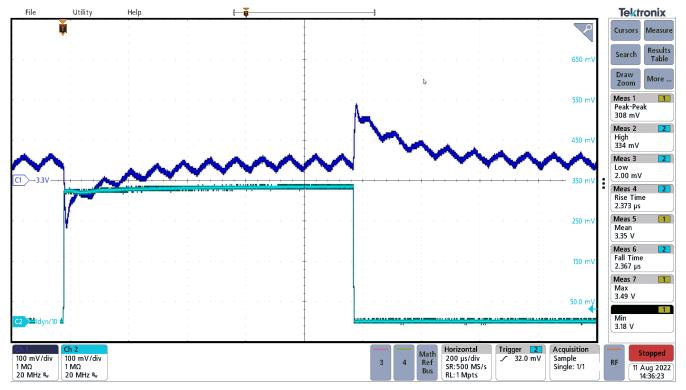

Output undershoot and overshoot each about 150 mV (purple trace). Dynamic current measured at J300 across a 100-m $\Omega$  shunt R306 on the PMP23194 board (blue trace).

Figure 3-4. Load Transient 3.3 V

Waveforms www.

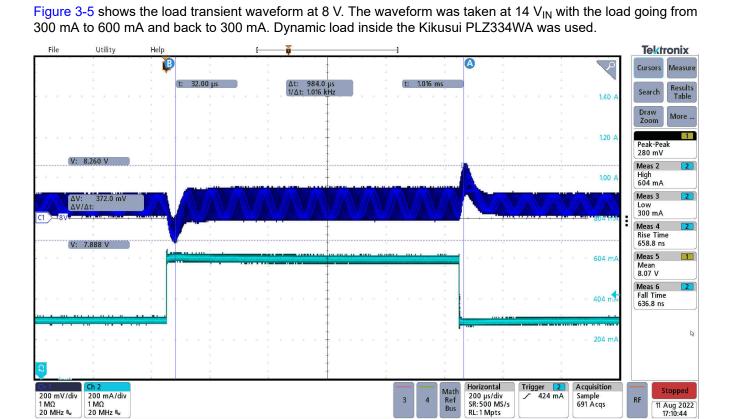


Undershoot and overshoot are each about 120 mV (dark blue trace). Dynamic current was measured with clip-on current probe (blue trace).

Figure 3-5. Load Transient 8 V

www.ti.com Waveforms
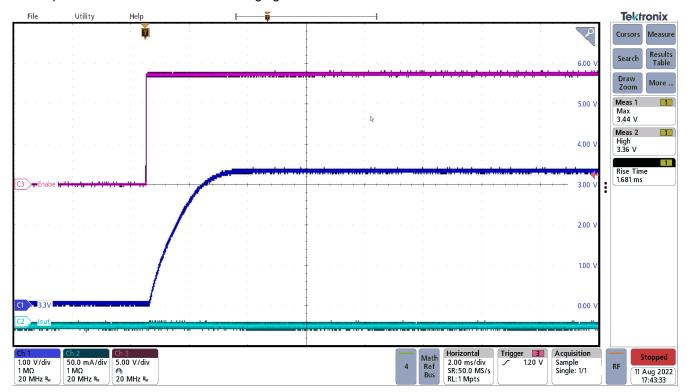
# 3.3 Start-Up of Each Independently-Controlled Output


Start-up behavior is shown in the following figures.



Enable going high: Red trace is the enable signal, the dark blue trace is  $V_{OUT}$ , and the light blue trace is the load current. Smooth  $V_{OUT}$  rise in under 2.5 ms with no overshoot seen.

Figure 3-6. Start-Up 3.3-V No-Load Off 14 V<sub>IN</sub> From 3.3 V

Waveforms www.ti.com

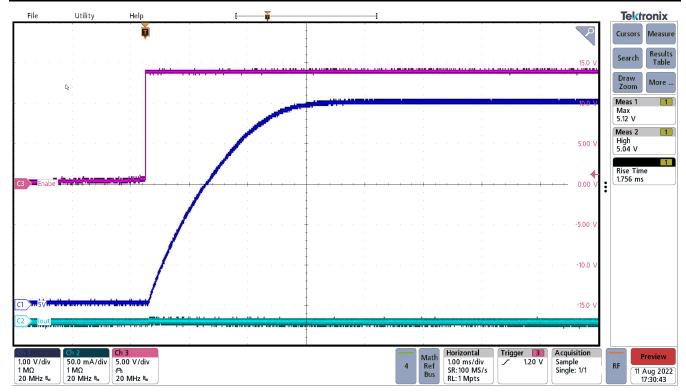

Enable going high: Enable going high: the red trace is the enable signal, the dark blue trace is V<sub>OUT</sub>, and the light blue trace is the load current. Smooth 5 V<sub>OUT</sub> rise in under 3 ms with no overshoot seen.

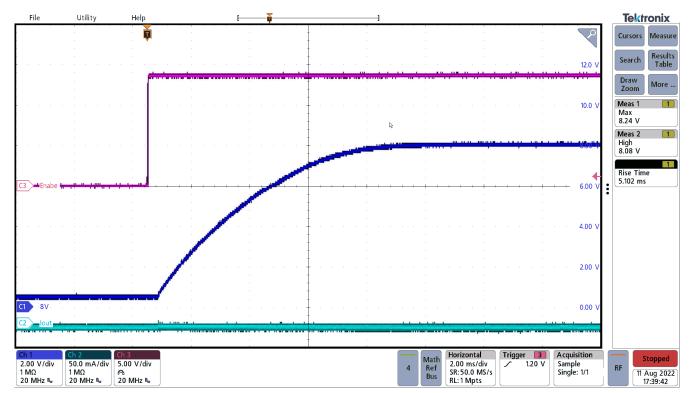


Figure 3-7. Start-Up 5-V No-Load off 14 V<sub>IN</sub> From 5 V

Enable going high: Enable going high: the red trace is the enable signal, the dark blue trace is  $V_{OUT}$ , and the light blue trace is the load current. Smooth 8  $V_{OUT}$  rise in under 10 ms with no overshoot seen.

Figure 3-8. Start-Up 8-V No-Load off 14 V<sub>IN</sub> From 8 V

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2022, Texas Instruments Incorporated