

1 Conversion and Total Efficiency

The efficiency comprises two values:

Eff1 is the Conversion Efficiency: Input power in U3 (pin1) divided by USB output power

Eff2 is the Total Efficiency: Output power divided by USB output power


Two measurements were taken:

The first measurement was performed with no distance between the two PCBs.

In the second measurement a 0.5mm spacer was inserted between the two PCBs.


Efficiency table and graph without any spacer inserted between the two PCBs.

Iusb	Pin	Iout	VinU3	VoutU3	Pout1	Pout2	Eff1	Eff2
mA	mW	mA	Volt	Volt	mW	mW	%	%
26.0	130	0	10.40	5.519	0.0	0.0	0.0	0.0
36.1	180.5	5	10.14	5.519	50.7	27.6	28.1	15.3
46.4	232	10	9.73	5.518	97.3	55.2	41.9	23.8
56.8	284	15	9.41	5.516	141.2	82.7	49.7	29.1
66.7	333.5	20	9.07	5.515	181.5	110.3	54.4	33.1
75.6	378	25	8.67	5.513	216.8	137.8	57.3	36.5

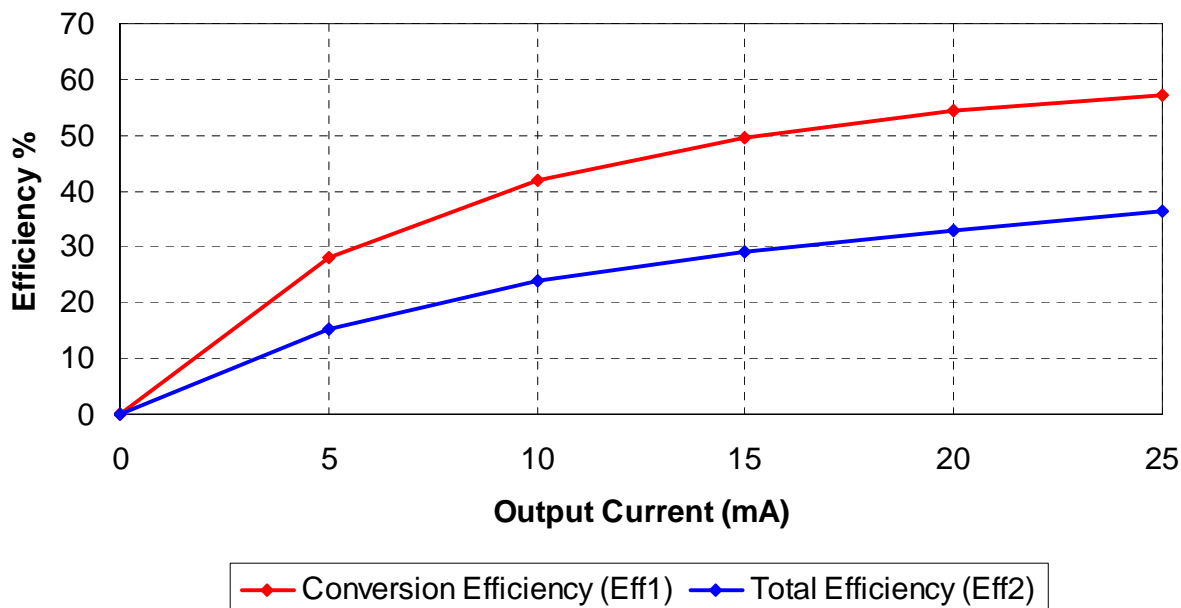

Efficiency table and graph with a 0.5mm spacer inserted between the two PCBs.


Iusb	Pin	Iout	VinU3	VoutU3	Pout1	Pout2	Eff1	Eff2
mA	mW	mA	Volt	Volt	mW	mW	%	%
25.2	126	0	10.47	5.519	0.0	0.0	0.0	0.0
34.1	170.5	5	8.89	5.519	44.5	27.6	26.1	16.2
43.4	217	10	8.72	5.517	87.2	55.2	40.2	25.4
52.7	263.5	15	8.51	5.516	127.7	82.7	48.4	31.4
61.3	306.5	20	8.14	5.514	162.8	110.3	53.1	36.0
63.2	316	25	6.53	5.513	163.3	137.8	51.7	43.6

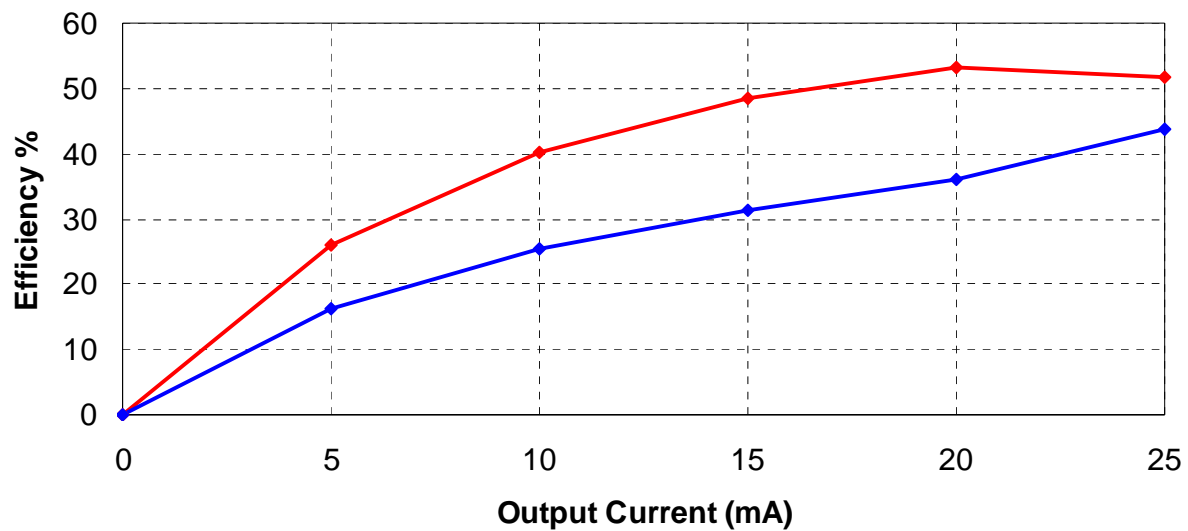

—●— Conversion Efficiency (Eff1) —●— Total Efficiency (Eff2)

2 Output Voltage Load Regulation

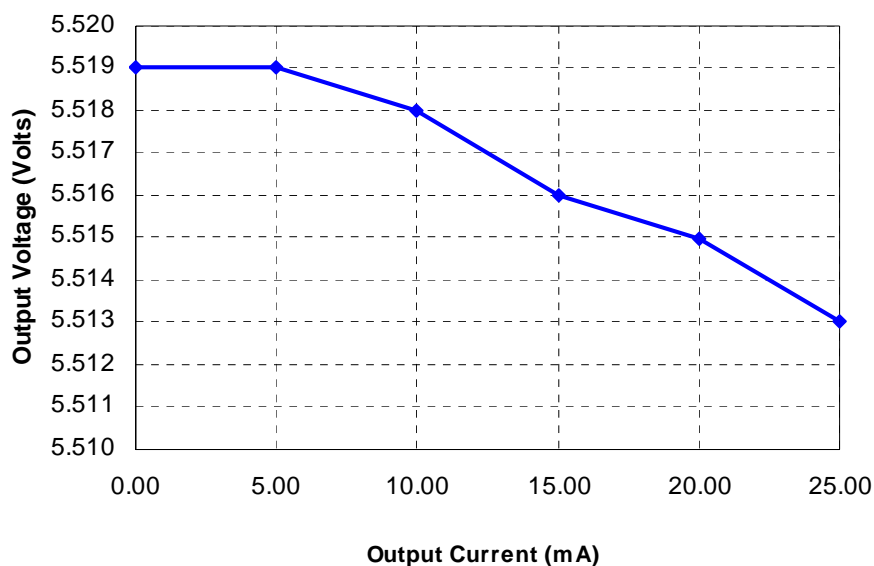The output voltage variation with load is plotted below.




3 Output Ripple Voltage


The U3 input voltage ripple is shown in the plot below.

Load was set to 25mA


Channel 2: VinU3 (ac coupled) 50mV/div

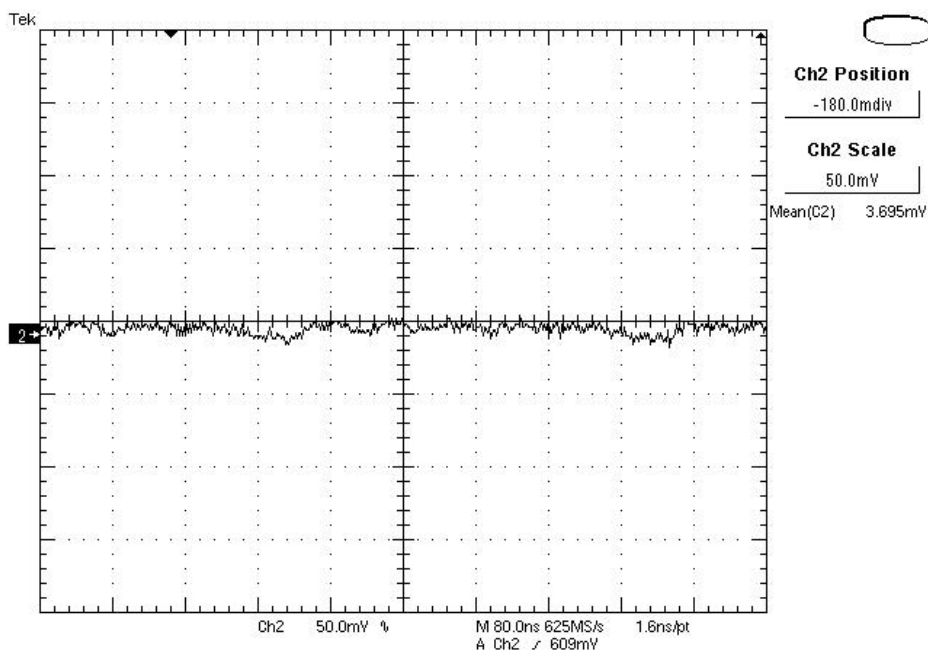

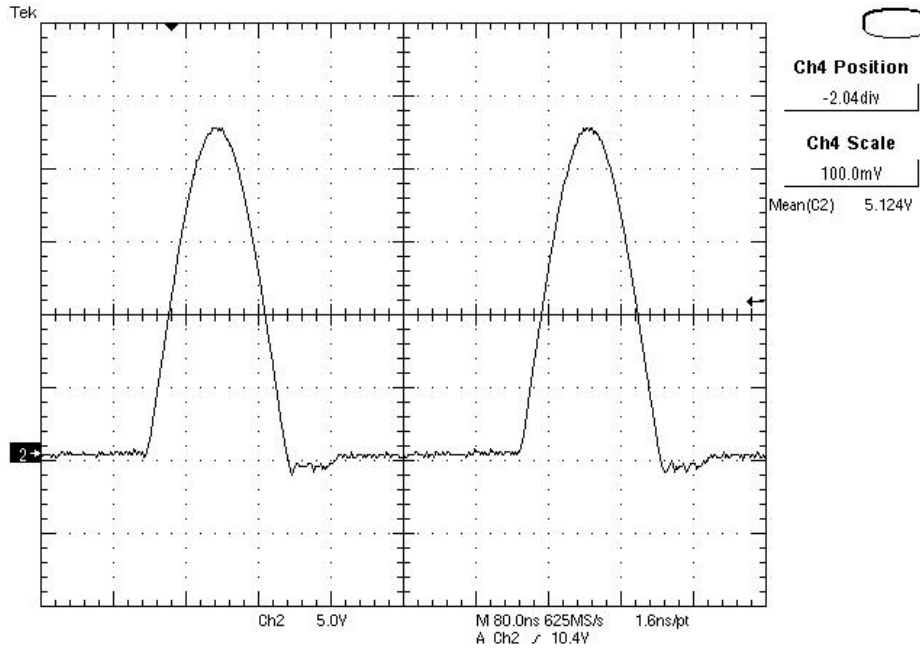4 Q1 Drain Switching Waveform with No Load



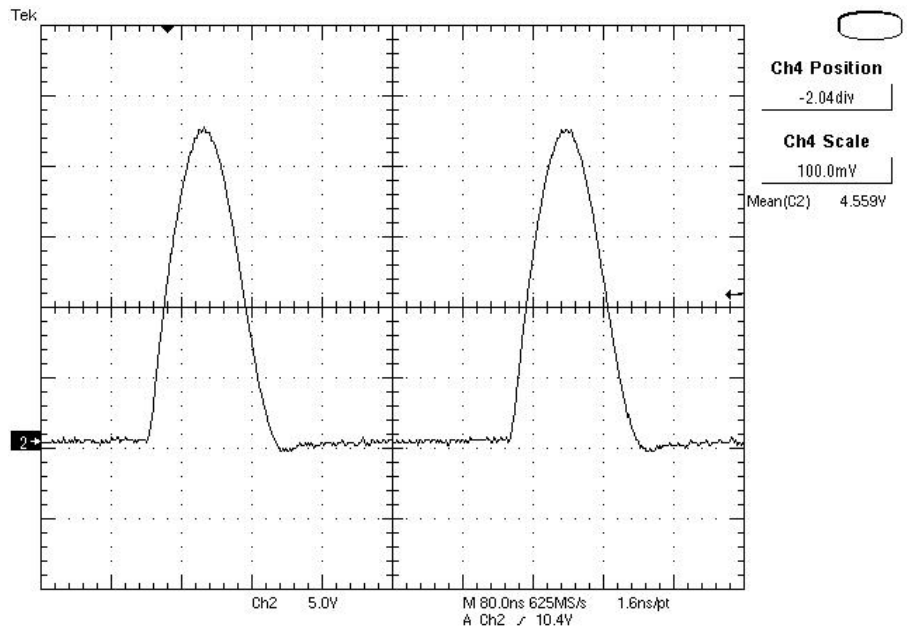5 Q1 Drain Switching Waveform with Full Load



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated