
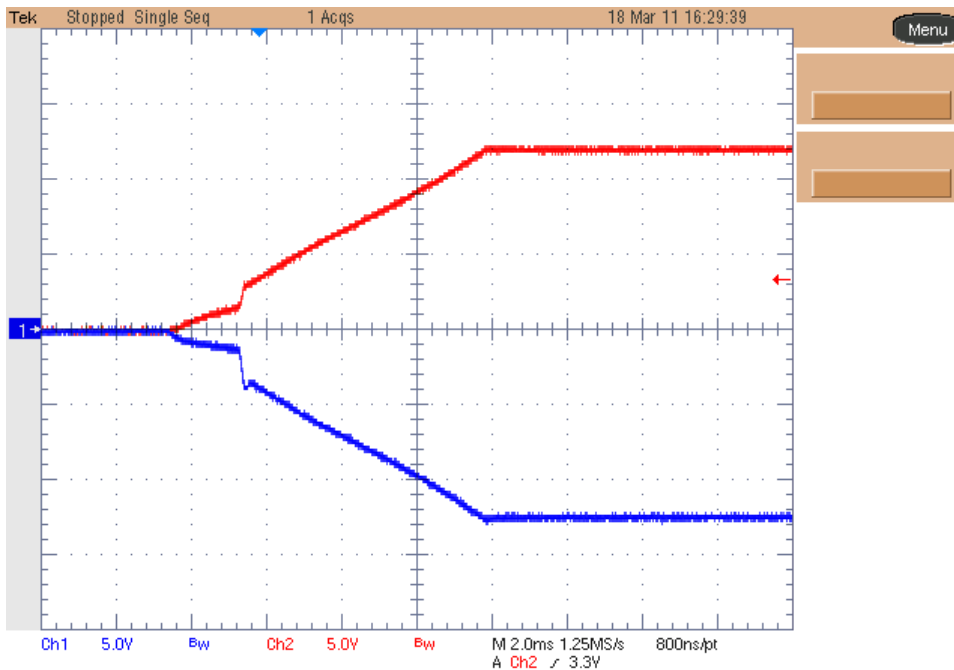


1 Startup

The +12Vout and the -12Vout startup behavior is shown in the pictures below. The input voltage has been set to 20V. Upper picture: no load, lower: full load on both outputs.

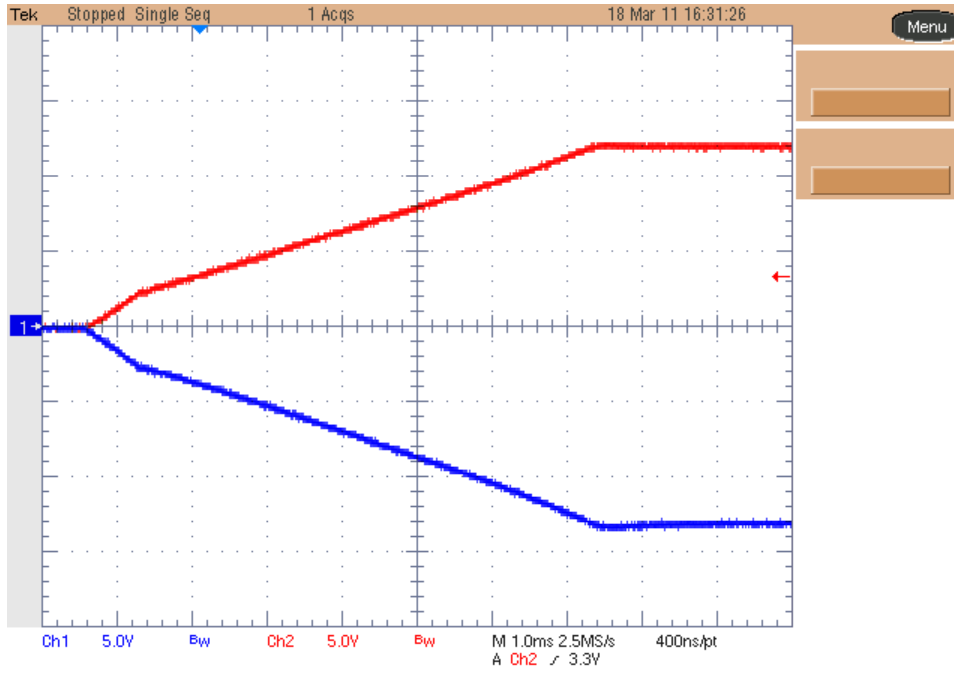
Channel 1 and 2: +12Vout and -12Vout (5V/div, 1ms/div, 20MHz BWL).



2 Shutdown


The +12Vout and the -12Vout behavior during shut down is shown in the picture below. The input voltage has been set to 20V and the load set to full load for both outputs.

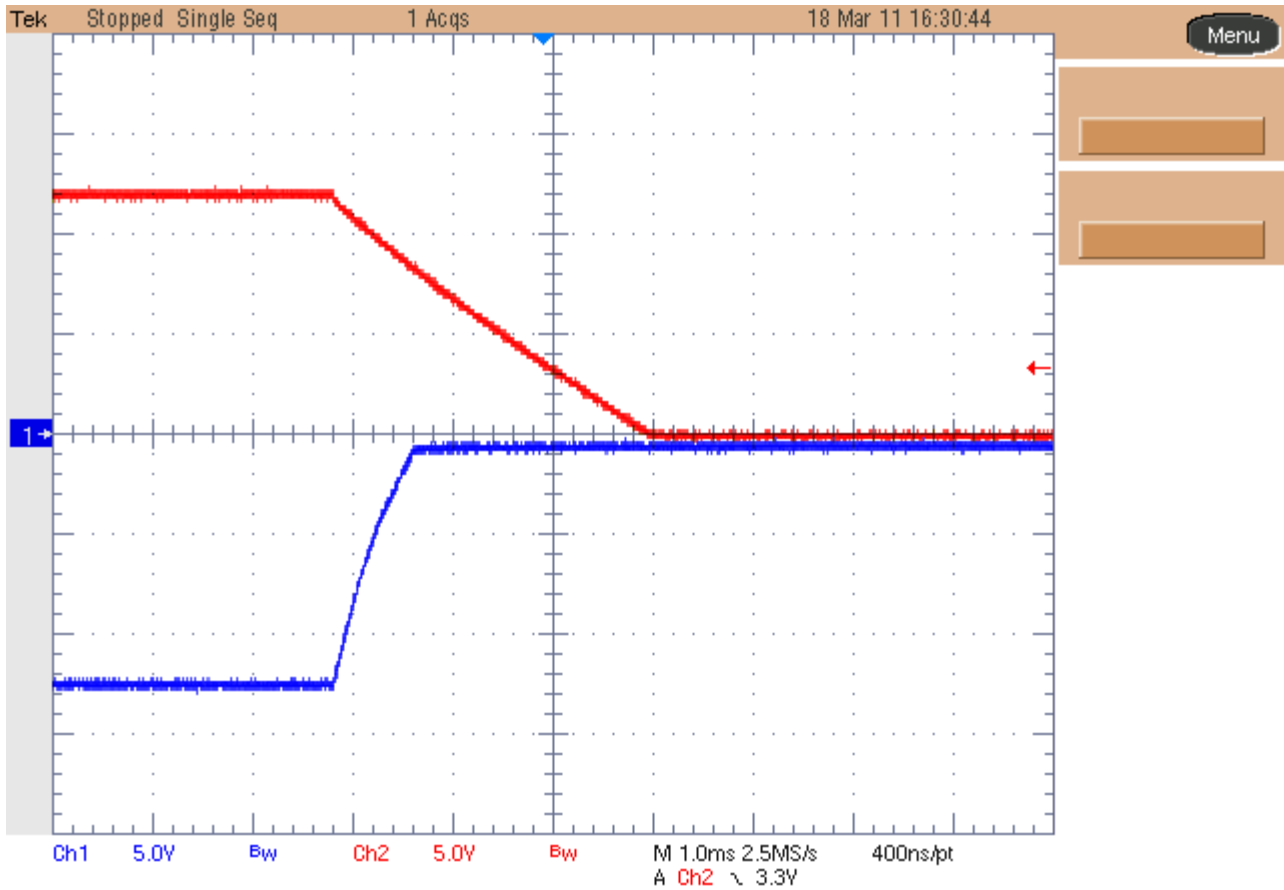Channel 1 and 2: +12Vout and -12Vout (5V/div, 1ms/div, 20MHz BWL).



3 Efficiency

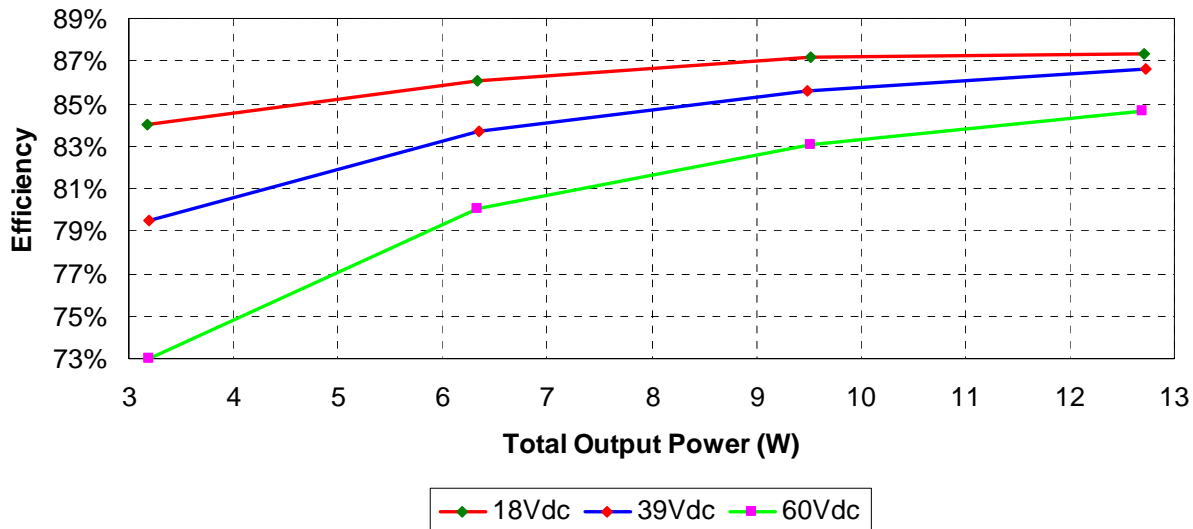The efficiency data is shown in the tables and graph below. The input voltage was set to 18V, 39V and 60V, while the load has been varied between 0, 25, 50, 75 and 100% of the nominal load at the same rate for both outputs.



Out 1: +12V		Out 2: -12V		Pout (W)	Iin (mA)	Vin (V)	Pin (W)	Ploss (W)	Eff
I (mA)	V (V)	I (-mA)	V (-V)						
0.0	11.99	0.0	12.61	0.00	15.7	17.99	0.282	0.28	0.00%
201.2	11.99	61.9	12.25	3.17	208.7	18.08	3.773	0.60	84.03%
400.7	11.99	124.5	12.27	6.33	409.0	17.99	7.358	1.03	86.06%
600.5	11.99	189.1	12.32	9.53	606.5	18.02	10.929	1.40	87.20%
800.2	11.99	250.9	12.39	12.70	807.8	18.01	14.548	1.85	87.32%

Out 1: +12V		Out 2: -12V		Pout (W)	Iin (mA)	Vin (V)	Pin (W)	Ploss (W)	Eff
I (mA)	V (V)	I (-mA)	V (-V)						
0.0	11.99	0.0	12.60	0.00	12.2	39.08	0.477	0.48	0.00%
201.5	11.99	63.8	12.25	3.20	103.0	39.04	4.021	0.82	79.52%
400.8	11.99	125.5	12.28	6.35	194.4	39.00	7.582	1.23	83.71%
600.5	11.99	186.6	12.31	9.50	284.5	39.00	11.096	1.60	85.59%
800.0	11.99	254.1	12.34	12.73	376.7	39.00	14.691	1.96	86.63%

Out 1: +12V		Out 2: -12V		Pout (W)	Iin (mA)	Vin (V)	Pin (W)	Ploss (W)	Eff
I (mA)	V (V)	I (-mA)	V (-V)						
0.0	11.99	0.0	12.68	0.00	10.3	60.1	0.619	0.62	0.00%
201.5	11.99	62.8	12.26	3.19	72.6	60.1	4.363	1.18	73.02%
400.9	11.99	124.8	12.28	6.34	131.8	60.1	7.921	1.58	80.03%
600.5	11.99	188.2	12.31	9.52	191.0	60.0	11.460	1.94	83.04%
800.0	11.99	250.9	12.34	12.69	249.9	60.0	14.994	2.31	84.62%

Output Voltage tracking between +12V and -12V:

The table below shows which minimum load must be present on the outputs to keep into regulation the -12Vout. Since the regulation is done on the +12Vout, it will always be stable.


Out 1: +12V		Out 2: -12V	
I (mA)	V (V)	I (-mA)	V (-V)
21.2	11.99	261.0	11.58
21.2	11.99	0.0	12.85
800.0	11.99	0.0	14.45
800.0	11.99	26.4	13.30

When the +12Vout is loaded between 21.2mA and 800mA, the -12Vout is always lower than 14.45V, even if unloaded (the D5 zener is clamping). If the +12Vout is lightly loaded (21.2mA) and the -12Vout fully loaded (261mA) then the voltage drops down to 11.58V, which is still acceptable.

If the converter has zero load on the +12V, the -12V is able to deliver only few mA (~ 10mA) before losing regulation.

4 Output voltage regulation

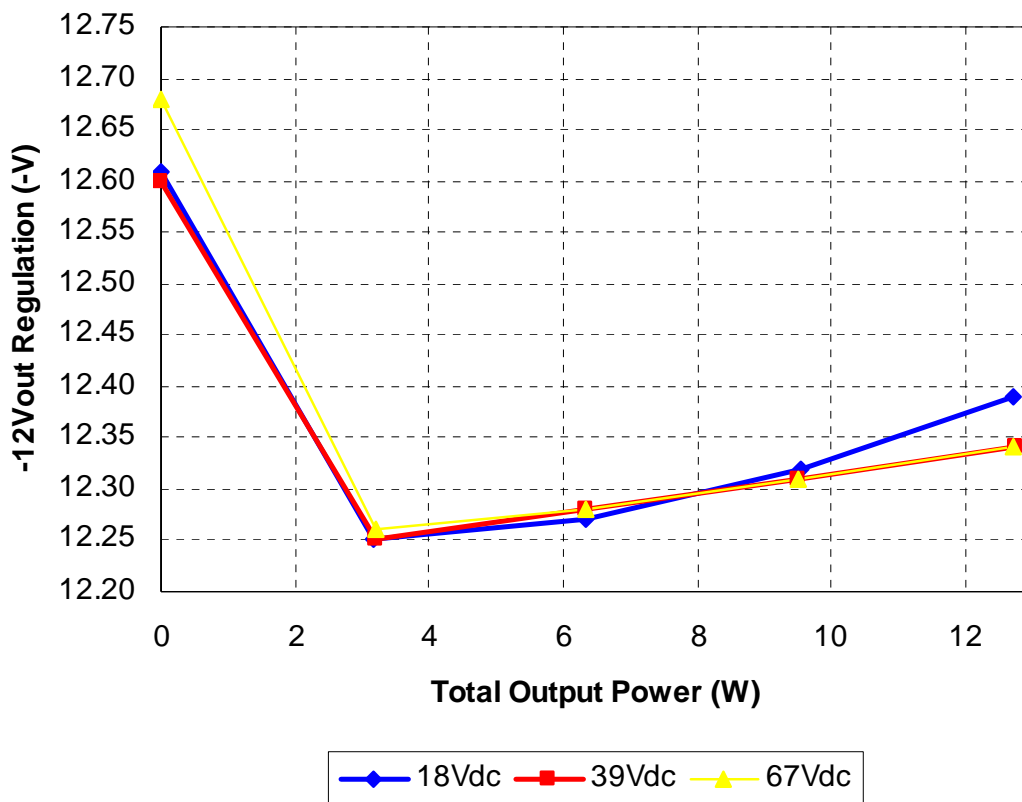The -12Vout output voltage versus total output power is plotted below. Since the regulation is done on the +12Vout, it will always be stable, so it hasn't been plotted. The input voltage was set to 18V, 39V and 60V, while the load has been varied between 0, 25, 50, 75 and 100% of the nominal load at the same rate for both outputs.




5 Output ripple voltage

The output ripple voltages for both outputs are shown in the plot below. The input was set to 18Vin and the outputs both fully loaded.

Channel 2: +12V Output voltage (20 mV/div, 2us/div, AC coupling, 20MHz BWL)

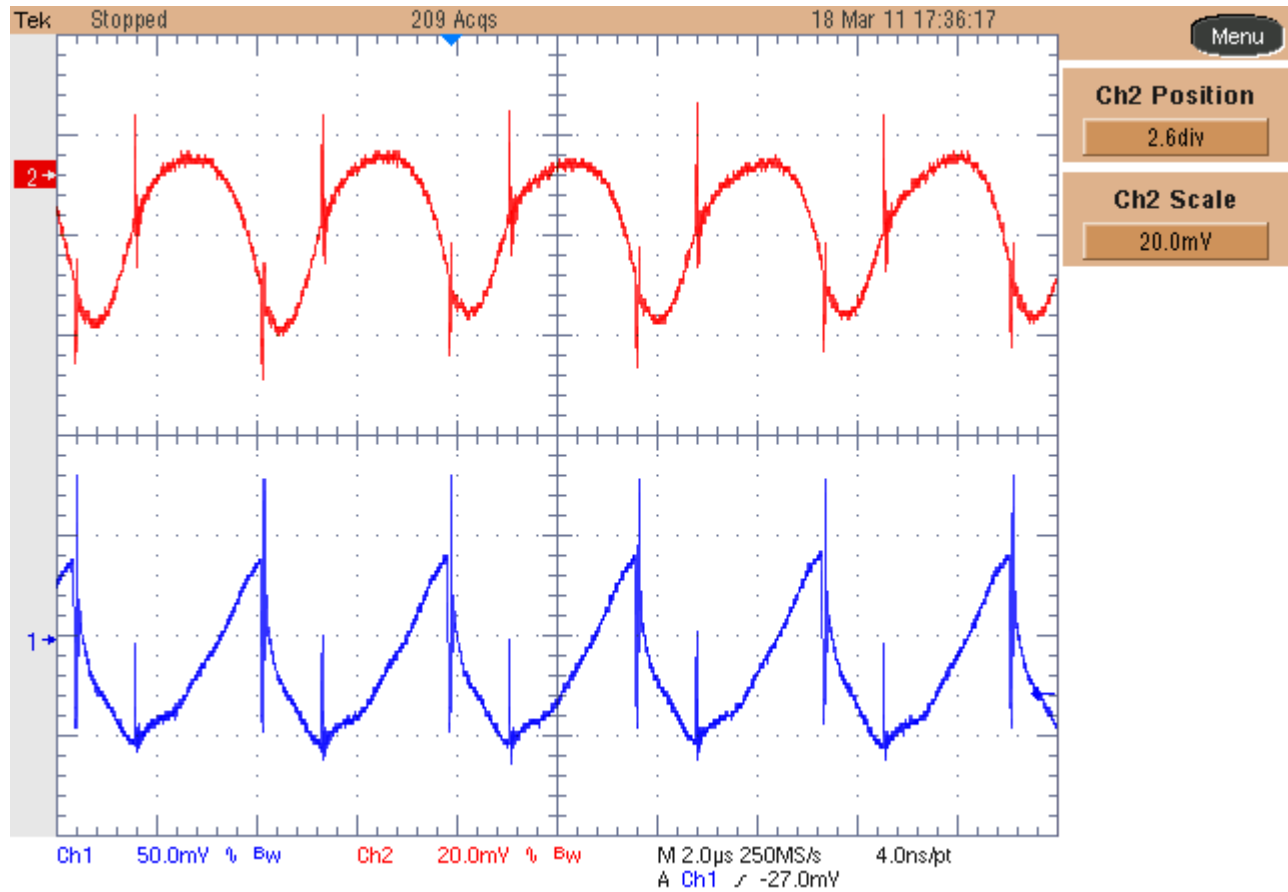Channel 1: -12V Output voltage (50 mV/div, AC coupling, 20MHz BWL).




6 Switch-node


The images below show the switch-node waveform (drain of Q1). The input voltage was set to 18Vin and 60Vin respectively. A full load condition (on both outputs) and no load condition show the variation of the duty cycle. It never reaches zero because of the small clamping load made by D5, R24.

Channel 1: Q1 Vds voltage (20 V/div, 1us/div, No BWL).


Full Load, 18Vin; Duty cycle: 68.5%

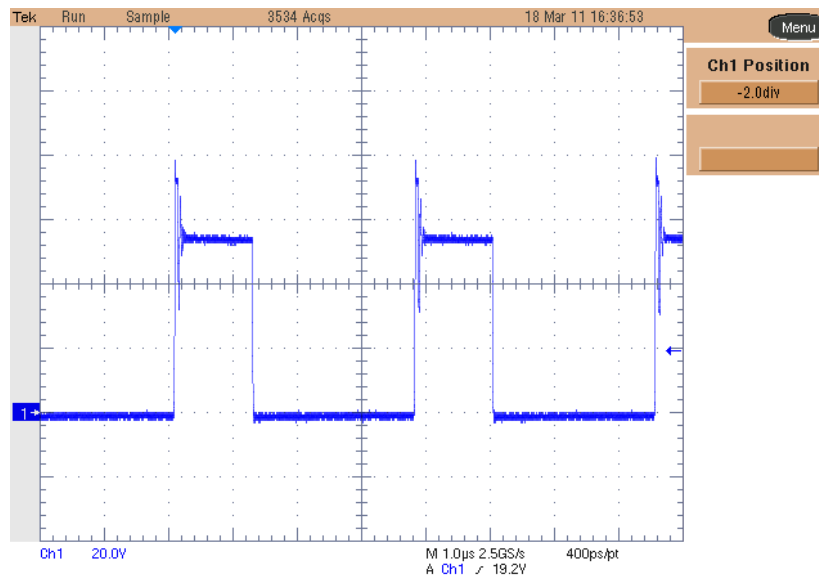


Full Load, 60Vin; Duty cycle: 28.23%

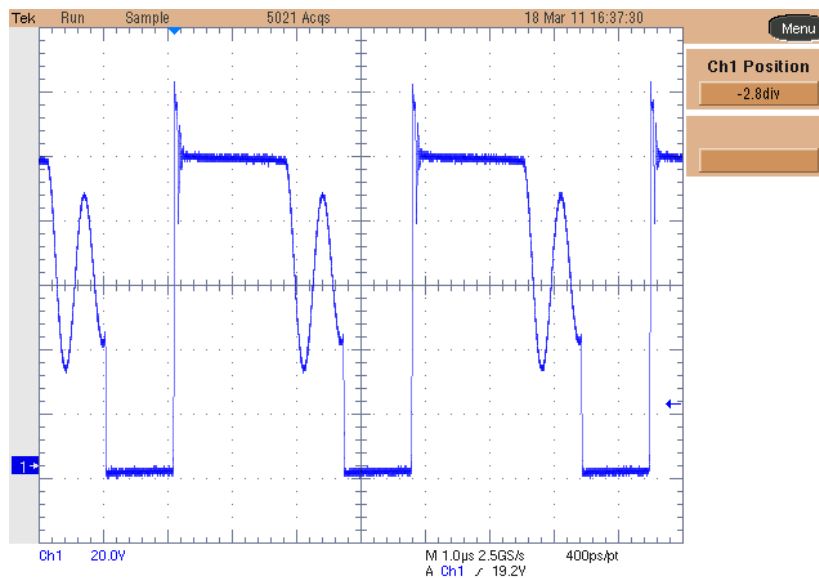

No Load, 18Vin; Ton = 320nsec

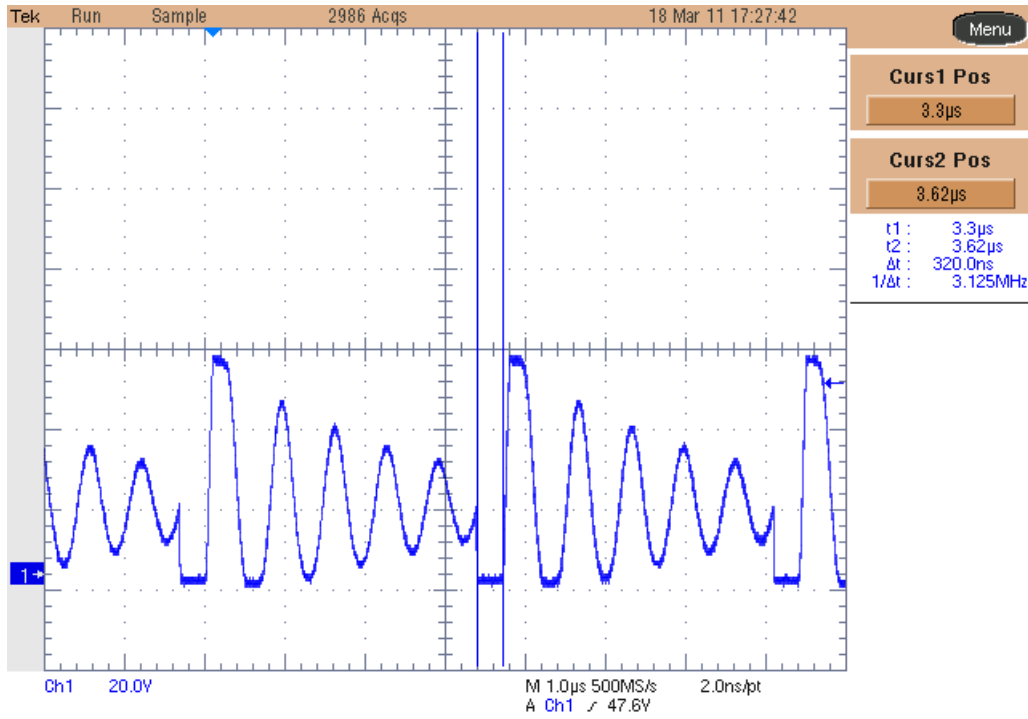

No Load, 60Vin; Ton = 88nsec

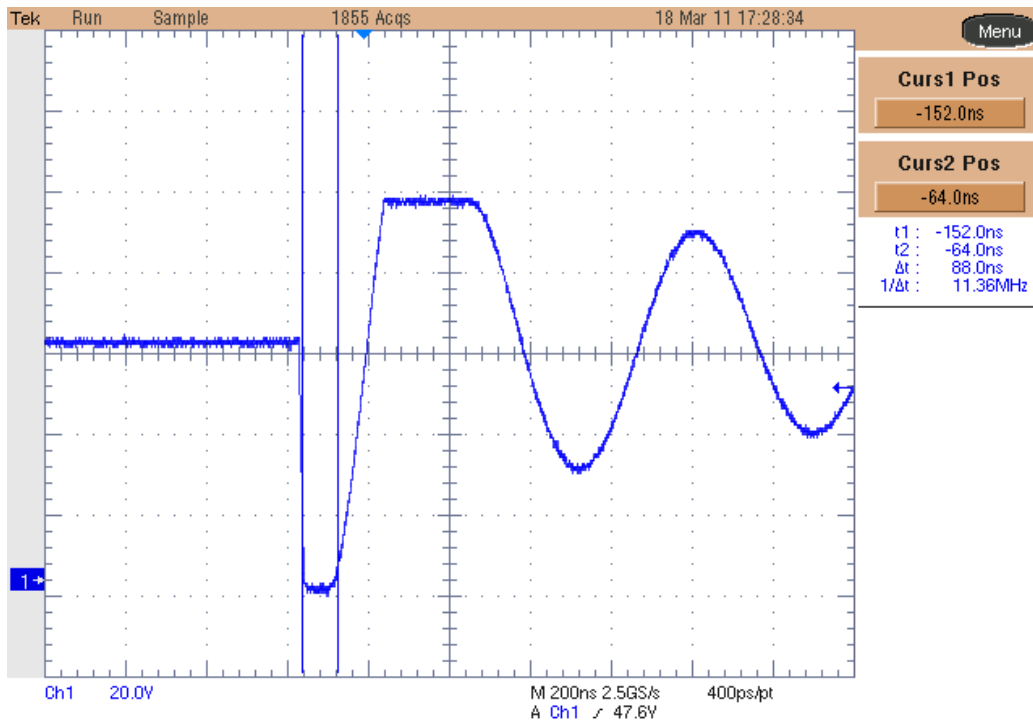


7 Transient response

The image below shows the transient response of the +12V_{out} when the load was switched between 250mA and 500mA, and the -12V was loaded continuously with 250mA constant current load. The input voltage was set to 20V.

Channel 1: +12V output voltage (100 mV/div, AC coupling, 20 MHz BWL, 400us/div).

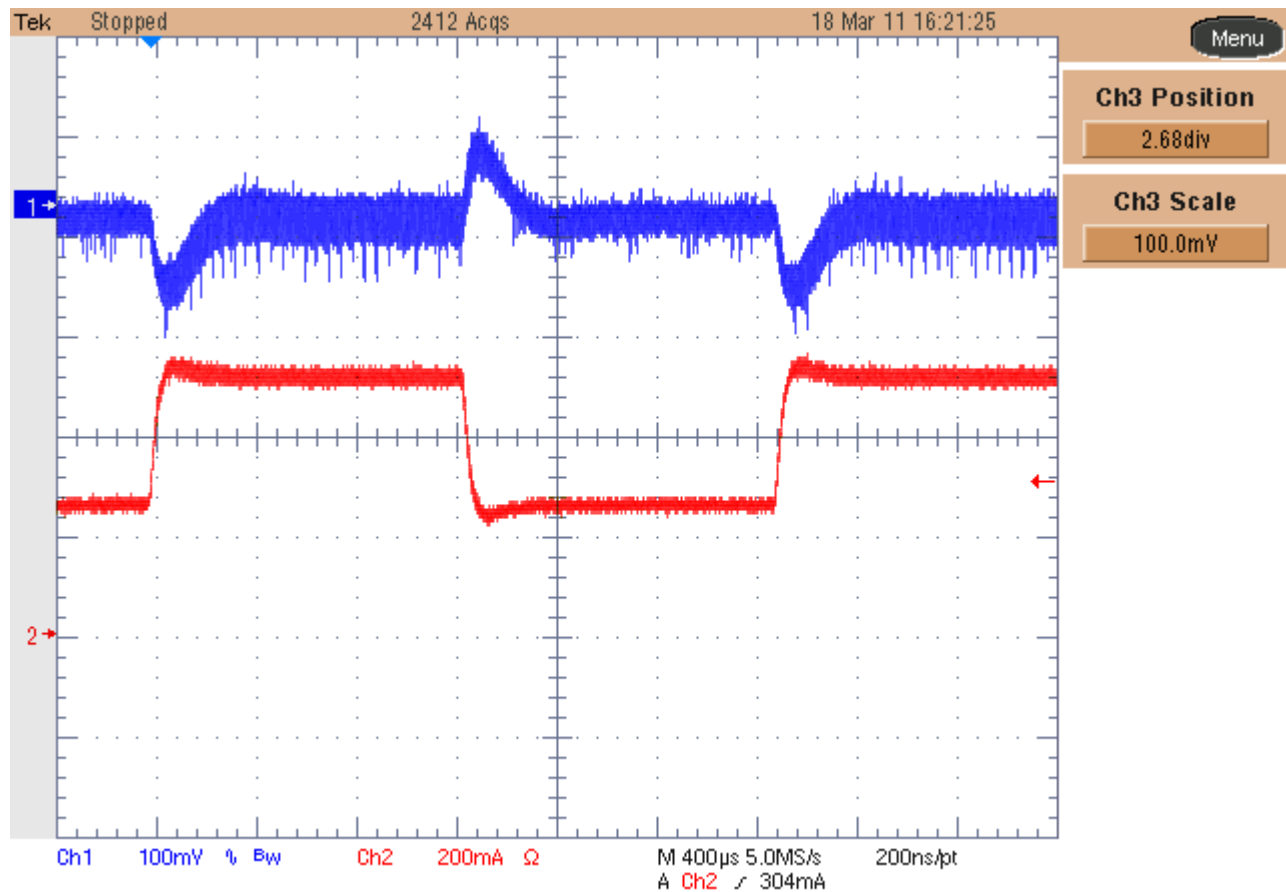
Channel 2: Output current (200 mA/div, DC coupling, No BWL).



8 Loop Response


The image below shows the loop response of the converter measured with a 18Vdc input, and full load on both outputs. This is the worst case since the converter works, at this input voltage, in continuous conduction mode, thus generating a right half plane zero; this is the reason why we must keep low the crossover frequency.

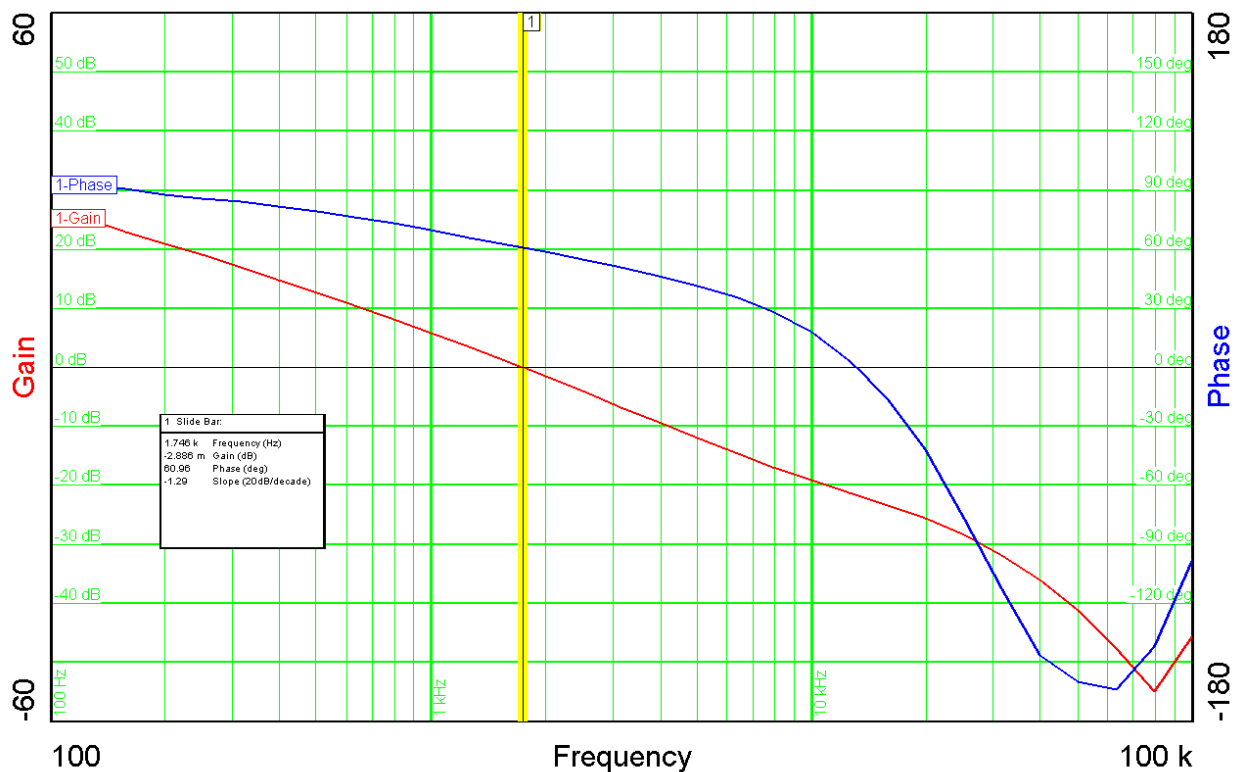The phase margin was 60.96 deg., the gain margin 21.62dB, and the crossover frequency was 1.746KHz.



9 Thermal Image

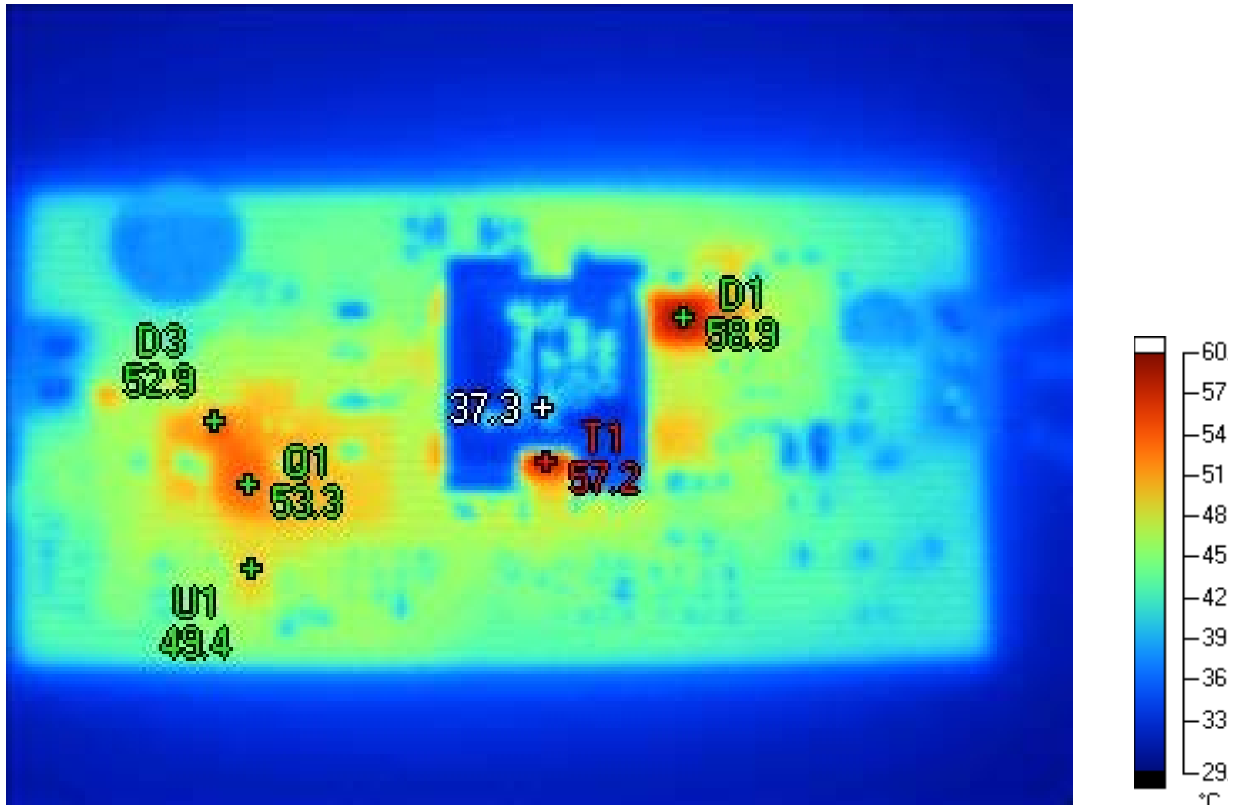The image below shows the thermal image taken from a **Fluke Ti40FT** Thermal camera. The input voltage was set to 39V and the power supply was fully loaded on both outputs; the ambient temperature was 23C and the measurement has been performed in still air conditions. The hottest spot was the diode D1 with 58.9C.



3/21/2011 12:44:30 PM

Image Info

Emissivity	0.95
Background	20.0 °C
Average Temperature	38.2 °C
Calibration Range	-20.0 °C to 100.0 °C
Camera Model	Ti40FT
Image Range	29.9 °C to 58.9 °C
Image Time	3/21/2011 12:44:30 PM
Lens Description	20mm/F0.8
Lens Serial #	40948-4409
Manufacturer	Fluke
Camera Serial Number	Ti40FT-070263

Markers

Label	Temperature	Emissivity	Background
Center Point	37.3 °C	0.95	20.0 °C
Q1	53.3 °C	0.95	20.0 °C
D3	52.9 °C	0.95	20.0 °C
U1	49.4 °C	0.95	20.0 °C
T1	57.2 °C	0.95	20.0 °C
D1	58.9 °C	0.95	20.0 °C

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated