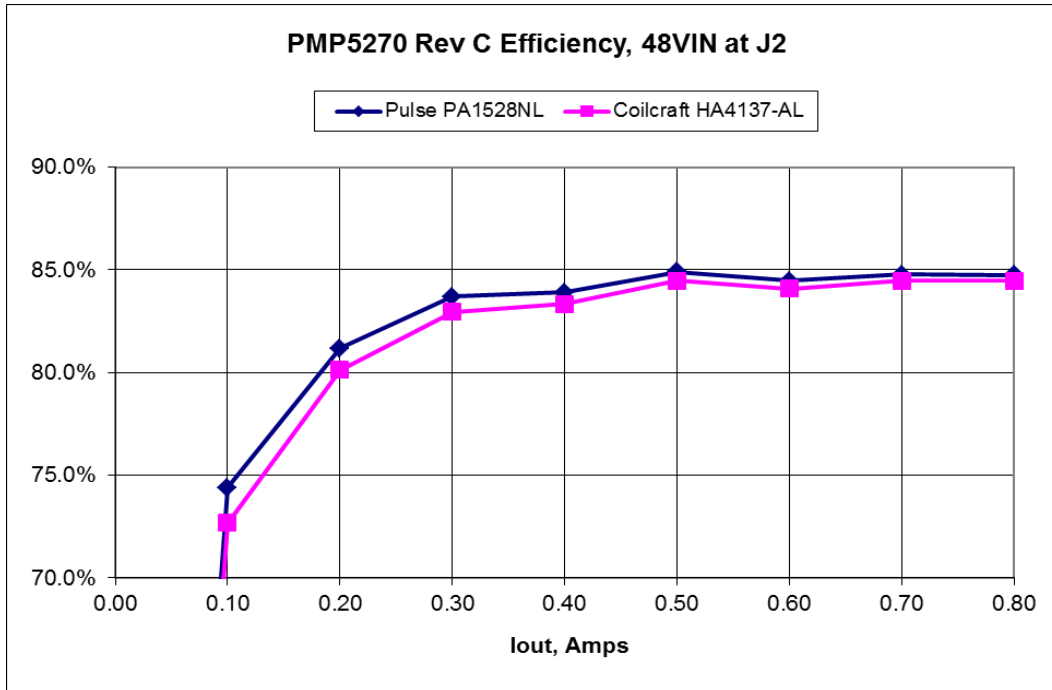


Efficiency


The efficiency of the converter is shown below:




Ripple and Noise

Ripple measurements taken with a 48V input and maximum load on all outputs. The test data is taken with the Coilcraft HA4137-AL transformer. The Pulse PA1528NL transformer test data is virtually identical.

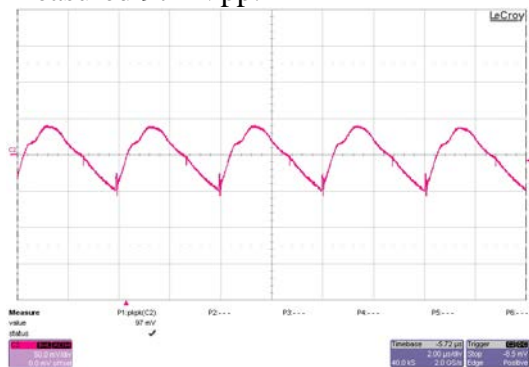15V ripple across C26, 50mV/div
 Measured 97mVpp:




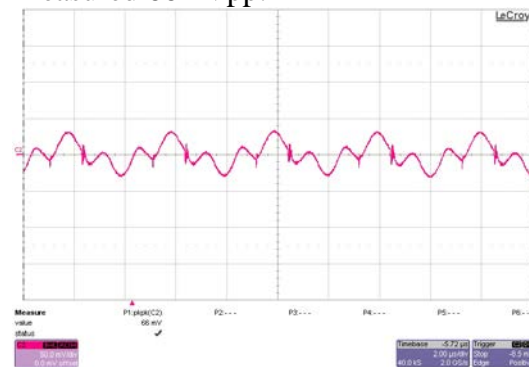Input ripple across C6, 50mV/div
 Measured 66mVpp:




Dynamic Loading

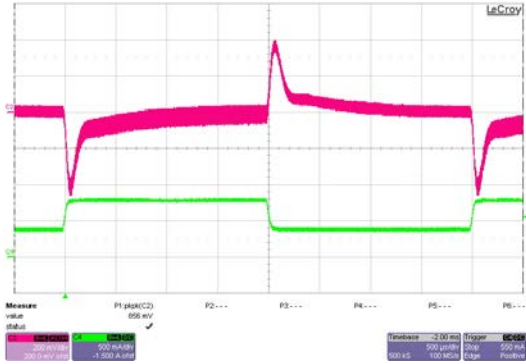Output load step, 400mA to 800mA, 500usec/div, slew rate 10mA/usec
200mV/div, 500mA/div; Measured 856mVpp:




Turn On Response

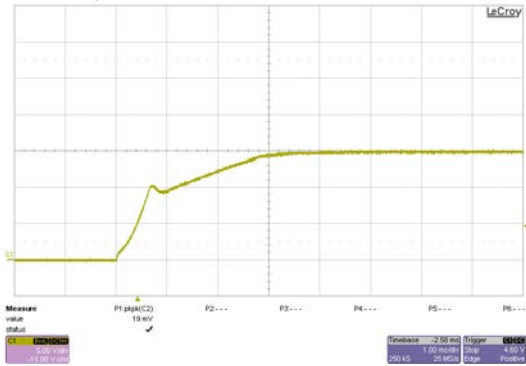Turn-on response: 48V_{in}, 800mA load
5V/div; 1msec/div:




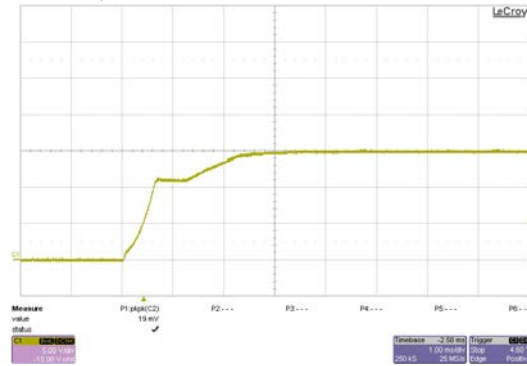Turn-on response: 48V_{in}, 0A load
5V/div, 1msec/div:



Stability Analysis (Loop Gain)

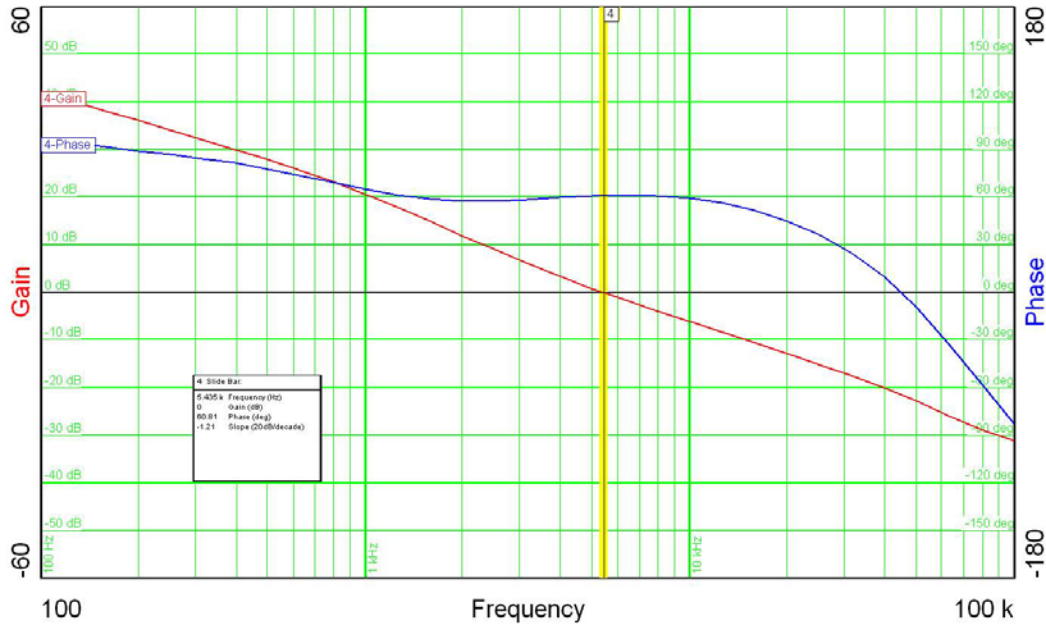The figure below is the loop gain of the converter with a 48V input and a 720mA load using the Coilcraft HA4137-AL transformer. The Bandwidth is 5.4 KHz, the Phase Margin is 60 degrees, and the Gain Margin is 23 dB.



Photo



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated