


AN-1446 LM3495 Evaluation Board

Specifications Of The Board

The evaluation board has been designed for testing of various circuits using the LM3495 buck regulator controller. A complete schematic for all the components is shown in [Circuit Schematic](#). The board is four layers, consisting of signal/power traces on top and bottom, one internal ground plane, and an internal split power plane. The top and bottom planes are 1oz. copper, internal planes are 1/2 oz., and the board is 62mil FR4 laminate.

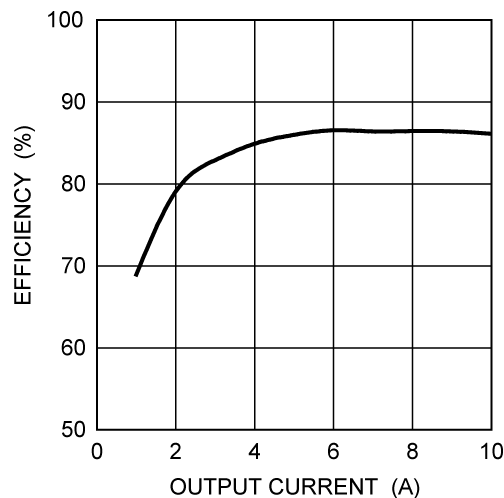Example Circuit

The example circuit that comes on the evaluation board steps input voltages of 12V \pm 10% down to 1.2V at currents up to 10A with a switching frequency of 500 kHz. The measured efficiency of the converter is 86% at an output current of 7A.



Efficiency for $V_{IN} = 12V$

Powering The Converter

The example circuit for the LM3495 evaluation board is optimized to run at inputs of 12V, however the circuit will operate with input voltages ranging from 2.9V to 18.0V connected between the 'Vin' and 'GND' terminals at the top of the board. Fixed loads, resistors, and variable electronic loads can be connected between the 'Vo' and 'GND' terminals. [Table 1](#) lists all the components used in the example circuit.

Enabling The Converter

The SPDT switch **ON/OFF** controls the state of the converter while power is applied to the input terminals. While in the OFF position the COMP/SD* pin of the LM3495 is grounded, the output is disabled, and the IC enters a low power state. While in the ON position the output voltage is regulated and is capable of delivering current to a load connected at the output terminals.

Testing The Converter

[Efficiency Measurement Setup](#) shows a block diagram of connections for making measurements of efficiency. The wires used for making connections at both the input and output should be rated to at least 10A of continuous current and should be no longer than is needed for convenient testing. A series ammeter capable of measuring 10A or more should be used for both the input and the output lines. Dedicated voltmeters should be connected with their positive and negative leads right at the four power terminals at the top of the evaluation board. This measurement technique minimizes the voltage loss in the wires that connect the evaluation board to the input power supply and the electronic load.

Output voltage ripple measurements should be taken directly across the 100 nF ceramic capacitor **Cox**, placed right between the output terminals. Care must be taken to minimize the loop area between the oscilloscope probe tip and the ground lead. One method to minimize this loop is to remove the probe's spring tip and 'pigtail' ground lead and then wind bare wire around the probe shaft. The bare wire should contact the ground of the probe, and the end of the wire can then contact the ground side of **Cox**. [Output Voltage Ripple Measurement Setup](#) shows a diagram of this method.


An oscilloscope probe modified as described above can also be used to measure the switch node voltage, LG pin voltage, and HG pin voltage (all three with respect to ground) using the 40mil diameter hole pairs labeled "+ SW -", "+ LG -", and "+ HG -", respectively.

SKIP/PWM

A second SPDT switch labeled SKIP/FPWM determines that control scheme the LM3495 uses at low output currents. When set to SKIP, the converter saves energy during light loads (approximately 100 mA or less) by using the body diode of the low side FET, as well as leaving the high side FET off if possible. When the switch is set to FPWM, the LM3495 forces both top and bottom FETs to switch during every cycle, regardless of the load current.

MOSFET Footprints

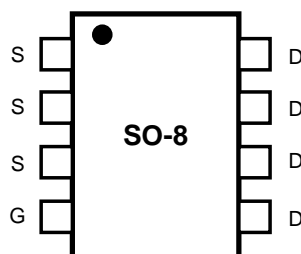The LM3495 evaluation board has footprints for single N-MOSFETs with SO-8 packages and standard pinouts. These footprints can also accept newer MOSFET packages that are compatible with SO-8 footprints. see [SO-8 MOSFET Pinout](#). **Q1** is the high side FET, and **Q2** low side FET.



SO-8 MOSFET Pinout

Permanent Components

The following components should remain the same for any new circuits evaluated on the LM3495 evaluation board:

Name	Value
Cb	0.1 μ F
Cf	1 μ F
Cdd	2.2 μ F

Additional Footprints

A 100 pF ceramic capacitor should be placed at position **Dsync** whenever the LM3495 runs without an external clock. When an external clock is used, **Dsync** should be removed and a 100 pF ceramic capacitor placed at **Csync**.

The 0Ω resistor **J1** connects the TRACK pin and VDD pins of the LM3495 together. It should be removed only when the tracking function is used.

The 0Ω resistor **J2** connects the VIN and VLIN5 terminals of the LM3495 together. This resistor should be used only when the input voltage is 5.5V or less, to provide maximum MOSFET gate drive.

The 0Ω resistor **J3** connects the 'Vin' terminal to the VIN pin of the LM3495. This resistor should be removed only for testing of the input current draw of the LM3495 IC.


The 0Ω resistor **Rbst** can be replaced with a higher value resistor to limit the current drawn by the BOOST pin. This slows the high-side FET gate drive rise time and may reduce ringing on the switch node. Care must be taken, as slowing the gate drive too much can cause shoot-through current.

Components **Rt1** and **Rt2** are used if the output of the converter is tracking another supply during startup. For this application the output of the external supply should be connected to the TRACK IN terminal. When the tracking feature is not used, the track pin should be connected to the VDD pin by placing a 0Ω resistor in position **J2**.

Components **Rsnb** and **Csnb** can be used to filter ringing on the switch node.


D2 provides a position for a diode to go in parallel with **Q2**. In circuits with output currents of approximately 5A or less, a Schottky diode at **D2** can improve the efficiency of the converter.

Complete Circuit Schematic

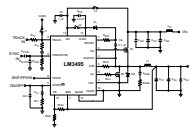

Circuit Schematic

Connection Diagrams

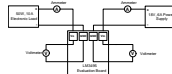


Efficiency Measurement Setup




Output Voltage Ripple Measurement Setup


Typical Performance Waveforms

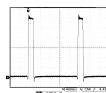

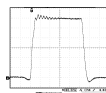
Switch Node Voltage ($V_{IN} = 12V$, $V_O = 1.2V$, $I_O = 5A$)



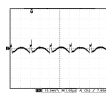
Switch Node Voltage ($V_{IN} = 12V$, $V_O = 1.2V$, $I_O = 5A$)



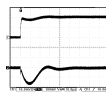Output Voltage Ripple, AC Coupled ($V_{IN} = 12V$, $V_O = 1.2V$, $I_O = 5A$)



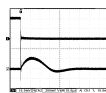Load Transient Response ($V_{IN} = 12V$, $V_O = 1.2V$, $I_O = 0A$ to $4A$)




Load Transient Response ($V_{IN} = 12V$, $V_O = 1.2V$, $I_O = 4A$ to $0A$)

Bill of Materials (BOM)


Table 1. Bill of Materials (BOM)

Qty	ID	Part Number	Type	Size	Parameters	Vendor
1	U1	LM3495	Synchronous Controller	TSSOP-16		TI
1	Q1	HAT2198R	N-MOSFET	SO-8	30V, 9.6mΩ 11nC	Renesas
1	Q2	HAT2165H	N-MOSFET	LFAK	30V 3.4mΩ, 33nC	Renesas
1	D1	MBR0530	Schottky Diode	SMA	30V, 0.5A	Vishay
1	L1	RLF12560T-1R0N140	Inductor	12.5x12.8 x6.0mm	1μH 14A 3mΩ	TDK
1	Cin	C3225X5R1E226M	Capacitor	1210	22μF, 25V	TDK
2	Co1, Co2	C3225X5R0J107M	Capacitor	1210	100μF 6.3V 1mΩ	TDK
1	Cf	C3216X7R1E105M	Capacitor	1206	1μF, 25V	TDK
1	Cdd	C3216X7R1E225M	Capacitor	1206	2.2μF 25V	TDK
2	Cb, Cinx	VJ1206Y104KXXAT	Capacitor	1206	100nF 10%	Vishay
1	Cc1	VJ1206Y103KXXAT	Capacitor	1206	10nF 10%	Vishay
3	Cc2, Csync, Dsync	VJ1206A101KXXAT	Capacitor	1206	100pF 10%	Vishay
1	Cox	VJ0805Y104KXXAT	Capacitor	805	100nF 10%	Vishay
3	Rbst, J1, J3	CRCW08050R00F	Resistor	805	0Ω	Vishay
1	Lin	CRCW25120R00F	Resistor	2512	0Ω	Vishay
1	Rc1	CRCW12061501F	Resistor	1206	1.5kΩ 1%	Vishay
2	Rfb1, Rfb2	CRCW12061002F	Resistor	1206	10kΩ 1%	Vishay
1	Rfrq	CRCW12065492F	Resistor	1206	54.9kΩ 1%	Vishay
1	Rlg	CRCW12061R00F	Resistor	1206	1Ω 1%	Vishay
1	Rlim	CRCW12063321F	Resistor	1206	3.32kΩ 1%	Vishay
2	SKIP/FPWM ON/OFF	NKK A12AB	SPST			NKK
5	Vo, GND1 GND2, GND3 Vin	Newark 40F6004	Terminal Silver	0.094"		Cambion
4	SYNC IN GND4, GND5 TRACK IN	Newark 94F1478	Terminal Silver	0.062"		Keystone


PCB Layout

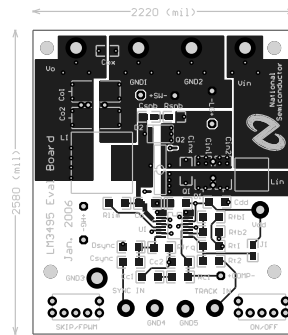


Top Layer and Top Overlay

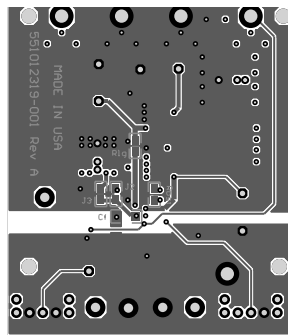

Bottom Layer

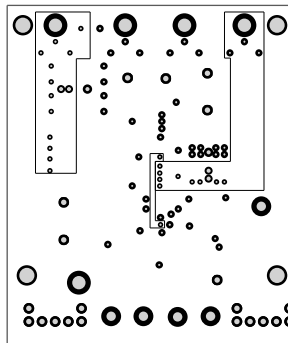

Internal Layer 1

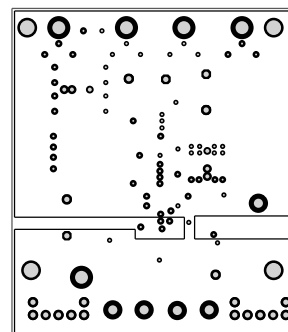

Internal Layer 2

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com