


## AN-2130 LM21215 Evaluation Board

### 1 Introduction

This evaluation board provides a solution to examine the high efficiency LM21215 buck switching regulator. The LM21215 is capable of driving up to 15A of continuous load current with excellent output voltage accuracy due to its  $\pm 1\%$  internal reference. The LM21215 is capable of down converting from an input voltage between 2.95V and 5.5V at a fixed switching frequency of 500 kHz. This device also features an adjustable current limit that allows the user to set the internal current limit protection value. Other fault protection features include output power good and output over-voltage protection. The dual function soft-start/tracking pin can be used to control the startup response of the LM21215, and the precision enable pin can be used to easily sequence the LM21215 in applications with sequencing requirements.

The LM21215 evaluation board has been optimized to work from 2.95V to 5.5V, achieving a balance between overall solution size and regulator efficiency. The evaluation board measures just over 2" x 2" on a four layer PCB, and exhibits a junction-to-ambient thermal impedance ( $\theta_{JA}$ ) of 24°C/W with no air flow. The power stage and compensation components of the LM21215 evaluation board have been optimized for an input voltage of 5V, but for testing purposes, the input can be varied across the entire operating range. The output voltage of the evaluation board is nominally 1.2V, but this voltage can be easily changed to any voltage between 0.6V and  $V_{IN}$  by modifying the feedback resistor network.

### 2 Evaluation Board Schematic

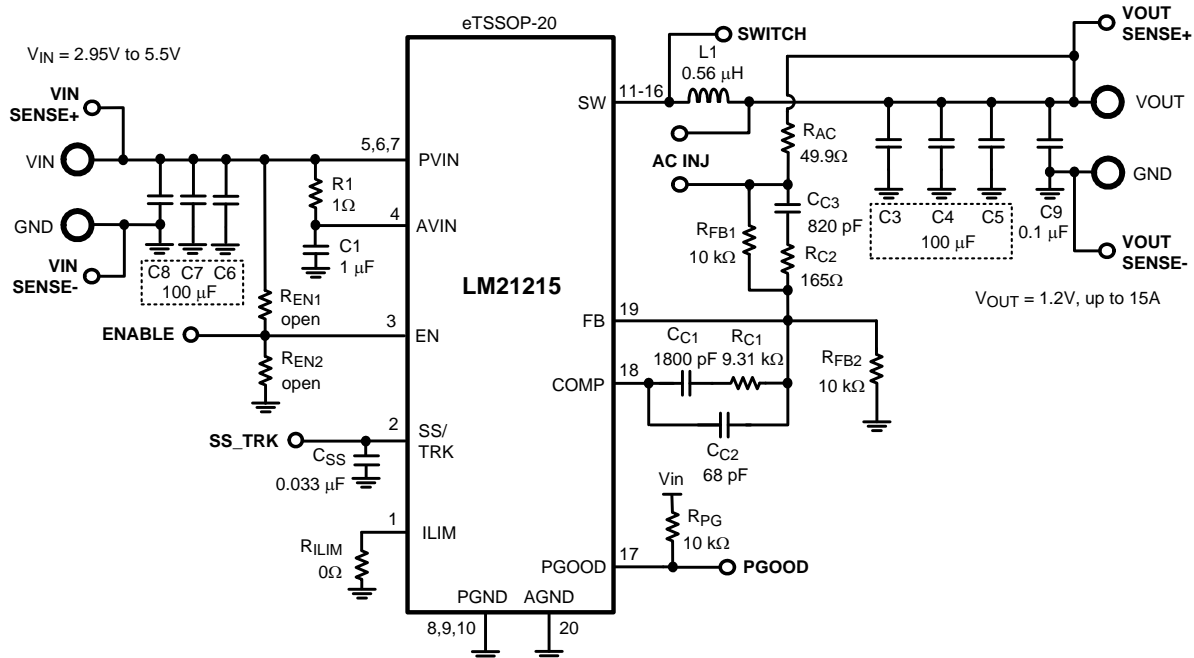

**Figure 1. Evaluation Board Schematic**

All trademarks are the property of their respective owners.

### 3 Powering and Loading Considerations

Read this entire section prior to attempting to power the evaluation board.

#### 3.1 Quick Setup Procedure

**Step 1:** Set the input source current limit to 10A. Turn off the input source. Connect the positive output of the input source to  $V_{IN}$  and the negative output to the corresponding GND.

**Step 2:** Connect the load (with 15A capability) to  $V_{OUT}$  for the positive connection and GND for the negative connection.

**Step 3:** The ENABLE pin should be left open for normal operation.

**Step 4:** Set the input source voltage to 5V. The load voltage should be in regulation with a nominal 1.2V output.

**Step 5:** Slowly increase the load while monitoring the load voltage at  $V_{OUT}$ . It should remain in regulation with a nominal 1.2V output as the load is increased up to 15A.

**Step 6:** Slowly sweep the input source voltage from 2.95V to 5.5V. The load voltage should remain in regulation with a nominal 1.2V output. If desired, the output of the device can be disabled by connecting the ENABLE pin to GND.

#### 3.2 Powering Up

It is suggested that the load power be kept low during the first power up. Once the device is powered up, immediately check for 1.2V at the output.

A quick efficiency check is the best way to confirm that everything is operating properly. If something is amiss you can be reasonably sure that it will affect the efficiency adversely. Few parameters can be incorrect in a switching power supply without creating losses and potentially damaging heat.

Some voltage supplies can exhibit severe voltage overshoot during high current transients. If a supply overshoots above 6.0V, damage to the LM21215 can occur. For these supplies, a large capacitor across the terminals of the supply (1000 $\mu$ F) can alleviate this problem.

#### 3.3 Over Current Protection

The LM21215 features a resistor-programmable current limit that allows the user to set the current limit to any desired value between 4A and 20A by changing the resistor  $R_{ILIM}$ . This evaluation board allows the maximum possible current limit for the LM21215 by populating  $R_{ILIM}$  with a 0 $\Omega$  resistor. If the user desires a lower current limit, the current limit should be set above the peak inductor current under maximum load and ripple conditions to avoid a current limit event in normal operation. See [Section 5.8](#) for details on how to determine the  $R_{ILIM}$  value.

### 4 Connection Descriptions

**Table 1. Connection Descriptions**

Terminal Silkscreen	Description
VIN	This terminal is the input voltage to the device. The evaluation board will operate over the input voltage range of 2.95V to 5.5V.
GND	These terminals are the ground connections to the device. The input power ground should be connected next to the input $V_{IN}$ connection, and the output power ground next to the $V_{OUT}$ connection.
VOOUT	This terminal connects to the output voltage of the power supply and should be connected to the load.
ENABLE	This terminal connects to the enable pin of the device. This terminal can be left floating or driven externally. If left floating, a 2 $\mu$ A current source will pull the pin high, thereby enabling the device. If driven externally, a voltage typically less than 1.2V will disable the device.
SS/TRK	This terminal provides access to the SS/TRK pin of the device. Connections to this terminal are not needed for most applications. The feedback pin of the device will track the voltage on the SS/TRK pin if it is driven with an external voltage source that is below the 0.6V reference.

**Table 1. Connection Descriptions (continued)**

Terminal Silkscreen	Description
PGOOD	This terminal connects to the power good output of the device. This pin is pulled up through a 10 kΩ pull-up resistor to $V_{IN}$ .
AC INJ	This terminal block allows the user to insert an AC injection signal across a 49.9Ω resistor for open-loop gain bode measurements. A jumper shorts out this resistor when it is not needed.
SWITCH	This terminal allows easy probing of the switch node. Do not apply any external voltage source to this pin.
VIN_SENSE+, VIN_SENSE- VOUT_SENSE+, VOUT_SENSE-	These terminals allow a sense connection on the board for accurate $V_{IN}$ and $V_{OUT}$ measurements, respectively.

## 5 Component Selection

This section provides a walk-through of the design process of the LM21215 evaluation board. Unless otherwise indicated, all equations assume units of amps (A) for current, farads (F) for capacitance, henries (H) for inductance, and volts (V) for voltages.

### 5.1 Input Capacitors: C1, C2, C3

The required RMS current rating of the input capacitor for a buck regulator can be estimated by the following equation:

$$I_{CIN(RMS)} = I_{OUT} \sqrt{D(1-D)} \quad (1)$$

The variable D refers to the duty cycle, and can be approximated by:

$$D = \frac{V_{OUT}}{V_{IN}} \quad (2)$$

From this equation, it follows that the maximum  $I_{CIN(RMS)}$  requirement will occur at a full 15A load current with the system operating at 50% duty cycle. Under this condition, the maximum  $I_{CIN(RMS)}$  is given by:

$$I_{CIN(RMS)} = 15A \sqrt{0.5 \times 0.5} = 7.5A \quad (3)$$

Ceramic capacitors feature a very large  $I_{RMS}$  rating in a small footprint, making a ceramic capacitor ideal for this application.

The input capacitors also keep the input stable during load transient conditions. If the input capacitance is too low, the input can drop below the UVLO threshold and cause the device to disable the output. This may result in repetitive dropout and re-enable oscillation, or "motorboating". To give the user the ability to operate with a low  $V_{IN}$  voltage, three 100 μF ceramic capacitors were used on the input.

### 5.2 Inductor: L1

The value of the inductor was selected to allow the device to achieve a 5V to 1.2V conversion at 500kHz to provide a peak to peak ripple current of 3.2A, which is about 21% of the maximum output current. To have an optimized design, generally the peak to peak inductor ripple current should be kept to within 20% to 40% of the rated output current for a given input voltage, output voltage and operating frequency. The peak to peak inductor ripple current can be calculated by the equation:

$$\Delta I_{P-P} = \frac{(V_{IN} - V_{OUT}) \times D}{L \times f_{SW}} \quad (4)$$

Once an inductance value is calculated, an actual inductor needs to be selected based on a trade-off between physical size, efficiency, and current carrying capability. For the LM21215 evaluation board, a Vishay IHLP4040DZERR56M01 inductor offers a good balance between efficiency (1.8 mΩ DCR) and size.

### 5.3 Output Capacitors: C3, C4, C5, C9

The value of the output capacitor in a buck regulator influences the voltage ripple that will be present on the output voltage as well as the large signal output voltage response to a load transient. Given the peak-to-peak inductor current ripple ( $\Delta I_{P-P}$ ) the output voltage ripple can be approximated by the equation:

$$\Delta V_{OUT} = \Delta I_{P-P} \times \left[ R_{ESR} + \frac{1}{8 \times f_{SW} \times C_{OUT}} \right] \quad (5)$$

The variable  $R_{ESR}$  above refers to the ESR of the output capacitor. As can be seen in Equation 5, the ripple voltage on the output can be divided into two parts, one of which is attributed to the AC ripple current flowing through the ESR of the output capacitor and another due to the AC ripple current actually charging and discharging the output capacitor. The output capacitor also has an effect on the amount of droop that is seen on the output voltage in response to a load transient event.

For the evaluation board, three 100 $\mu$ F ceramic capacitors were selected to provide good transient and DC performance. Ceramic capacitors give the lowest  $R_{ESR}$  of any standard capacitor chemistries, resulting in the lowest output ripple for the given ripple current. Ceramic capacitors (especially high capacitance, small package multi-layer types, or MLCC) lose their capacitance as the DC voltage is increased. For this configuration, the actual capacitance value was approximated to be 50  $\mu$ F per capacitor, or 150  $\mu$ F total. This is lower than measured capacitance values for 1.2V, but will allow the user to change the output voltage up to 3.3V and maintain stability.

### 5.4 Soft-Start Capacitor: C<sub>SS</sub>

A soft-start capacitor can be used to control the startup time of the LM21215 voltage regulator. The startup time of the regulator when using a soft-start capacitor can be estimated by the following equation:

$$t_{SS} = \frac{0.6V \times C_{SS}}{I_{SS}} \quad (6)$$

For the LM21215,  $I_{SS}$  is nominally 5  $\mu$ A. For the evaluation board, the soft-start time has been designed to be roughly 10 ms, resulting in a  $C_{SS}$  capacitor value of 33 nF.

### 5.5 Compensation Components: C<sub>C1</sub>, C<sub>C2</sub>, C<sub>C3</sub>, R<sub>C1</sub>, R<sub>C2</sub>

These components are used in conjunction with the error amplifier to create a type 3 voltage-mode compensation network. The analysis of type 3 compensation is outside the scope of this document, but an example of the step-by-step procedure to generate compensation component values is given. The parameters needed for the compensation values are given in the following table.

Parameter	Value
$V_{IN}$	5.0V
$V_{OUT}$	1.2V
$I_{OUT}$	15A
$f_{CROSSOVER}$	100 kHz
L	0.56 $\mu$ H
$R_{DCR}$	1.8 m $\Omega$
$C_O$	150 $\mu$ F
$R_{ESR}$	1.0 m $\Omega$
$\Delta V_{RAMP}$	0.8V
$f_{SW}$	500 kHz

where  $\Delta V_{RAMP}$  is the oscillator peak-to-peak ramp voltage (nominally 0.8 V),  $f_{CROSSOVER}$  is the frequency at which the open-loop gain is a magnitude of 1,  $R_{DCR}$  is the effective DC resistance of the inductor,  $R_{ESR}$  is the effective resistance of the output capacitor, and  $C_O$  is the effective output capacitance at the programmed output voltage. It is recommended that  $f_{CROSSOVER}$  not exceed one-fifth of the switching frequency. The output capacitance,  $C_O$ , depends on capacitor chemistry and bias voltage. For Multi-Layer

Ceramic Capacitors (MLCC), the total capacitance will degrade as the DC bias voltage is increased. Measuring the actual capacitance value for the output capacitors at the output voltage is recommended to accurately calculate the compensation network. Note that it is more conservative, from a stability standpoint, to err on the side of a smaller output capacitance value in the compensation calculations rather than a larger, as this will result in a lower bandwidth but increased phase margin.

First, the value of  $R_{FB1}$  should be chosen. A typical value is 10k $\Omega$ . From this, the value of  $R_{C1}$  can be calculated to set the mid-band gain so that the desired crossover frequency is achieved.

$$\begin{aligned} R_{C1} &= \frac{f_{\text{CROSSOVER}}}{f_{\text{LC}}} \cdot \frac{\Delta V_{\text{RAMP}}}{V_{\text{IN}}} \cdot R_{\text{FB1}} \\ &= \frac{100 \text{ kHz}}{17.4 \text{ kHz}} \cdot \frac{0.8 \text{ V}}{5.0 \text{ V}} \cdot 10 \text{ k}\Omega \\ &= 9.2 \text{ k}\Omega \end{aligned} \tag{7}$$

Next, the value of  $C_{C1}$  can be calculated by placing a zero at half of the LC double pole frequency.

$$\begin{aligned} C_{C1} &= \frac{1}{\pi f_{\text{LC}} R_{C1}} \\ &= 1.99 \text{ nF} \end{aligned} \tag{8}$$

Now the value of  $C_{C2}$  can be calculated to place a pole at half of the switching frequency.

$$\begin{aligned} C_{C2} &= \frac{C_{C1}}{\pi f_{\text{SW}} R_{C1}} \\ &= 71 \text{ pF} \end{aligned} \tag{9}$$

$R_{C2}$  can then be calculated to set the second zero at the LC double pole frequency.

$$\begin{aligned} R_{C2} &= \frac{R_{\text{FB1}} f_{\text{LC}}}{f_{\text{ESR}} - f_{\text{LC}}} \\ &= 166 \Omega \end{aligned} \tag{10}$$

Last,  $C_{C3}$  can be calculated to place a pole at the same frequency as the zero created by the output capacitor ESR.

$$\begin{aligned} C_{C3} &= \frac{1}{2\pi f_{\text{ESR}} R_{C2}} \\ &= 898 \text{ pF} \end{aligned} \tag{11}$$

The standard values used for the above calculations are given in the Bill of Materials ([Section 7](#)).

## 5.6 Feedback Resistors: $R_{\text{FB1}}$ , $R_{\text{FB2}}$ , and $R_{\text{AC}}$

The resistors labeled  $R_{\text{FB1}}$  and  $R_{\text{FB2}}$  create a voltage divider from  $V_{\text{OUT}}$  to the feedback pin that is used to set the output of the voltage regulator. Nominally, the output of the LM21215 evaluation board is set to 1.2V, giving resistor values of  $R_{\text{FB1}} = R_{\text{FB2}} = 10\text{k}\Omega$ . If a different output voltage is required, the value of  $R_{\text{FB2}}$  can be adjusted according to the equation:

$$R_{\text{FB1}} = \left( \frac{V_{\text{OUT}}}{0.6} - 1 \right) \times R_{\text{FB2}} \tag{12}$$

$R_{\text{FB1}}$  does not need to be changed from its value of 10k $\Omega$ . Resistor  $R_{\text{AC}}$  has a value of 49.9 $\Omega$  and is provided as an injection point for loop stability measurements, as well as, a way to further tweak the output voltage accuracy to account for resistor tolerance values differing from ideal calculated values. The jumper is used to short out  $R_{\text{AC}}$  when not needed.

### 5.7 Programmable UVLO: $R_{EN1}$ and $R_{EN2}$

The resistors labeled  $R_{EN1}$  and  $R_{EN2}$  create a voltage divider from  $V_{IN}$  to the enable pin that can be used to enable the device above a programmed  $V_{IN}$ , effectively creating a programmable UVLO voltage above the device's internal UVLO (nominally 2.7V). To allow evaluation of the device down to 2.95V, these components are not installed. To change the turn-on threshold of the device a 10 k $\Omega$  resistor is recommended for  $R_{EN1}$  and the value of  $R_{EN2}$  can be calculated using the equation:

$$R_{EN1} = \left( \frac{V_{TO}}{1.35} - 1 \right) \times R_{EN2} \quad (13)$$

where  $V_{TO}$  is the desired  $V_{IN}$  voltage at which the device will enable.

### 5.8 Programmable Current Limit: $R_{ILIM}$

The resistor  $R_{ILIM}$  will set the internal current limit on the LM21215. A 0 $\Omega$  resistor is used on this board, allowing the maximum current capability of the device. If a user desires a lower current limit, it should be programmed such that the peak inductor current ( $I_L$ ) does not trigger the current limit in normal operation. This requires setting the resistor  $R_{ILIM}$  to the appropriate value to allow the maximum ripple current plus the DC output current through the high-side FET during normal operation. The maximum ripple current can be described as:

$$\begin{aligned} &\text{FOR } D > 0.5 \\ \Delta I_{LMAX} &= \frac{(V_{INMAX} - V_{OUTMIN}) \cdot V_{OUTMIN}}{L_{MIN} \cdot f_{SWMIN} \cdot V_{INMAX}} \\ &\text{FOR } D < 0.5 \\ \Delta I_{LMAX} &= \frac{(V_{INMIN} - V_{OUTMAX}) \cdot V_{OUTMAX}}{L_{MIN} \cdot f_{SWMIN} \cdot V_{INMIN}} \end{aligned} \quad (14)$$

where  $V_{INMAX}$ ,  $V_{INMIN}$ ,  $V_{OUTMAX}$ ,  $V_{OUTMIN}$ ,  $L_{MIN}$  and  $F_{SWMIN}$  are the respective maximum and minimum conditions of the system as defined by the component tolerance and device variation. From this, the maximum allowable current through the high-side FET ( $I_{HSMAX}$ ) of device can be described as:

$$I_{HSMAX} = \frac{\Delta I_{LMAX}}{2} + I_{DCMAX} \quad (15)$$


where  $I_{OUTMAX}$  is the maximum defined DC output current, up to 15 A. Once the  $I_{HSMAX}$  value has been determined, a nominal value of the  $R_{ILIM}$  resistor can be calculated as follows:

$$R_{ILIM} \text{ (k}\Omega\text{)} = \frac{582.4}{I_{HSMAX}} - 14.2 \quad (16)$$

where the  $R_{ILIM}$  value is the nominal resistance necessary for the given  $I_{HSMAX}$  value. A conservative design should also take into account the device variation over  $V_{IN}$  and temperature, which can be seen in the Electrical Characteristics table for the  $I_{CLR}$  parameter and the typical performance characteristics in *15A High Efficiency Point of Load Synchronous Buck Regulator* ([SNVS625](#)). These variations can cause the  $I_{HSMAX}$  value to increase, depending on the range of the input voltage and junction temperature.


## 6 Performance Characteristics

Figure 2 shows the conversion efficiency versus output current for a 5V input voltage for output voltages of 1.2V and 3.3V. The default output voltage is 1.2V.

 

**Figure 2. Conversion Efficiency Versus Output Current**

A soft-start sequence occurs when applying power to the LM21215 evaluation board. Figure 3 shows the output voltage during a typical start-up sequence.

 

**Figure 3. Startup Waveform (2 ms/DIV)**

Figure 4 shows the output voltage ripple. This measurement was taken with the scope probe tip placed on the output capacitor C9 VOUT connection and the scope probe ground "barrel" wired to the GND connection of C9. The scope bandwidth is set to 20 MHz.

 


Figure 4. Output Ripple Waveform (2  $\mu$ s/DIV)

Figure 5 shows the typical SW pin voltage with the output current set to 10A.

 
 


Figure 5. Primary Switch Node Waveform (400 ns/DIV)

 


Figure 6 shows the  $V_{OUT}$  deviation for a 3A to 12A output current transient condition.




**Figure 6.  $V_{OUT}$  Transient Response (50  $\mu$ s/DIV)**

Figure 7 shows the  $V_{OUT}$  output response to an output current limit condition.



**Figure 7. Output Current Limit (10  $\mu$ s/DIV)**

Figure 8 shows the open loop bode response generated by inserting a stimulus signal across  $R_{AC}$  and using a network analyzer to plot the gain and phase.

 

**Figure 8. Open Loop Bode Response**


## 7 Bill of Materials

**Table 2. Bill of Materials**

Item	Description	Vendor	Part Number	Qty
AC INJ	Header, TH, 100mil, 2 x 1, Gold plated, 230 mil above insulator	Samtec Inc.	TSW-102-07-G-S	1
C1	CAP, CERM, 1 uF, 10V, +/-10%, X7R, 0603	MuRata	GRM188R71A105KA61D	1
C3, C4, C5, C6, C7, C8	CAP, CERM, 100 uF, 6.3V, +/-20%, X5R, 1206	MuRata	GRM31CR60J107ME39L	6
C9	CAP, CERM, 0.1 uF, 50V, +/-10%, X7R, 0603	TDK	C1608X7R1H104K	1
C <sub>C1</sub>	CAP, CERM, 1800 pF, 50V, +/-5%, COG/NPO, 0603	MuRata	C1608C0G1H182J	1
C <sub>C2</sub>	CAP, CERM, 68 pF, 50V, +/-5%, COG/NPO, 0603	MuRata	GRM1885C1H680JA01D	1
C <sub>C3</sub>	CAP, CERM, 820 pF, 50V, +/-5%, COG/NPO, 0603	MuRata	GRM1885C1H821JA01D	1
C <sub>SS</sub>	CAP, CERM, 0.033 uF, 16V, +/-10%, X7R, 0603	MuRata	GRM188R71C333KA01D	1
GND_FI, GND_FO, VIN_F, VOUT_F	Standard Banana Jack, Uninsulated, 15A	Johnson Components	108-0740-001	4
L1	Inductor, Shielded Drum Core, Powdered Iron, 560nH, 27.5A, 0.0018 ohm, SMD	Vishay-Dale	IHLP4040DZERR56M01	1
R1	RES, 1.0 ohm, 5%, 0.1W, 0603	Vishay-Dale	CRCW06031R00JNEA	1
R <sub>AC</sub>	RES, 49.9 ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW060349R9FKEA	1
R <sub>C1</sub>	RES, 9.31 kohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW06039K31FKEA	1
R <sub>C2</sub>	RES, 165 ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW0603165RFKEA	1
R <sub>FB1</sub> , R <sub>FB2</sub> , R <sub>PG</sub>	RES, 10 kohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW060310K0FKEA	3
R <sub>ILIM</sub>	RES, 0 ohm, 1%, 0.1W, 0603	Vishay-Dale	CRCW06030000Z0EA	1
SH-J1	Shunt, 100mil, Gold plated, Black	Samtec Inc.	SNT-100-BK-G	1
U1	15A Buck DC/DC Converter	Texas Instruments	LM21215	1

## 8 PCB Layout

The PCB was manufactured with 2oz. copper outer layers, and 1oz. copper inner layers. Twenty 8 mil. diameter vias placed underneath the device, along with additional vias placed throughout the ground plane around the device, help improve the thermal dissipation of the board.

 

**Figure 9. Top Layer (Copper planes outlined in grey)**

 


Figure 10. Mid Layer1


 


Figure 11. Mid Layer2

 

**Figure 12. Bottom Layer**

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)