



**LM5017
Isolated Supply**

TI reference design number: PMP9321 Rev B

**Input: 24V Nominal
Output: 5V @ 0.6A**

DC-DC Converter Test Results

Table of Contents

1. Circuit Description	3
2. Fabrication	3
3. Efficiency	4
3.1 LM5017 Isolated Flyback Efficiency Data	5
4. Thermal	6
Top View.....	6
5. Switch Node Voltage and Output Ripple Voltage	7
5.1 24V Input – 0.6A Load (Primary Switch)	7
5.2 24V Input – 0.6 Load (Secondary Switch)	7
6. Transient Response	8
6.1 24V Input – 0.3A to 0.6A, 100mA/μs, 100 Hz, 50% duty cycle, 5V out.....	8


PMP9321 Rev B Test Results

1. Circuit Description


PMP9321 uses a LM5017 which is a 100V 600mA synchronous step down regulator with integrated high and low side MOSFETs. The supply delivers an isolated 5V bias supply for various applications. The input voltage is 24V nominal and can deliver 5V out at 0.6A maximum. The input voltage range is 21.6V to 26.4V. The LM5017 uses constant-on-time control. Various configurations are available for the designer to use low ESR ceramics on the output and still provide enough ripple voltage for the feedback comparator in order to operate in a stable condition. Please note, the circuit is meant to provide an isolated output. Yet, if the user chooses to use both the isolated and non-isolated outputs, be sure to limit the total combined output current draw to 0.6A maximum.

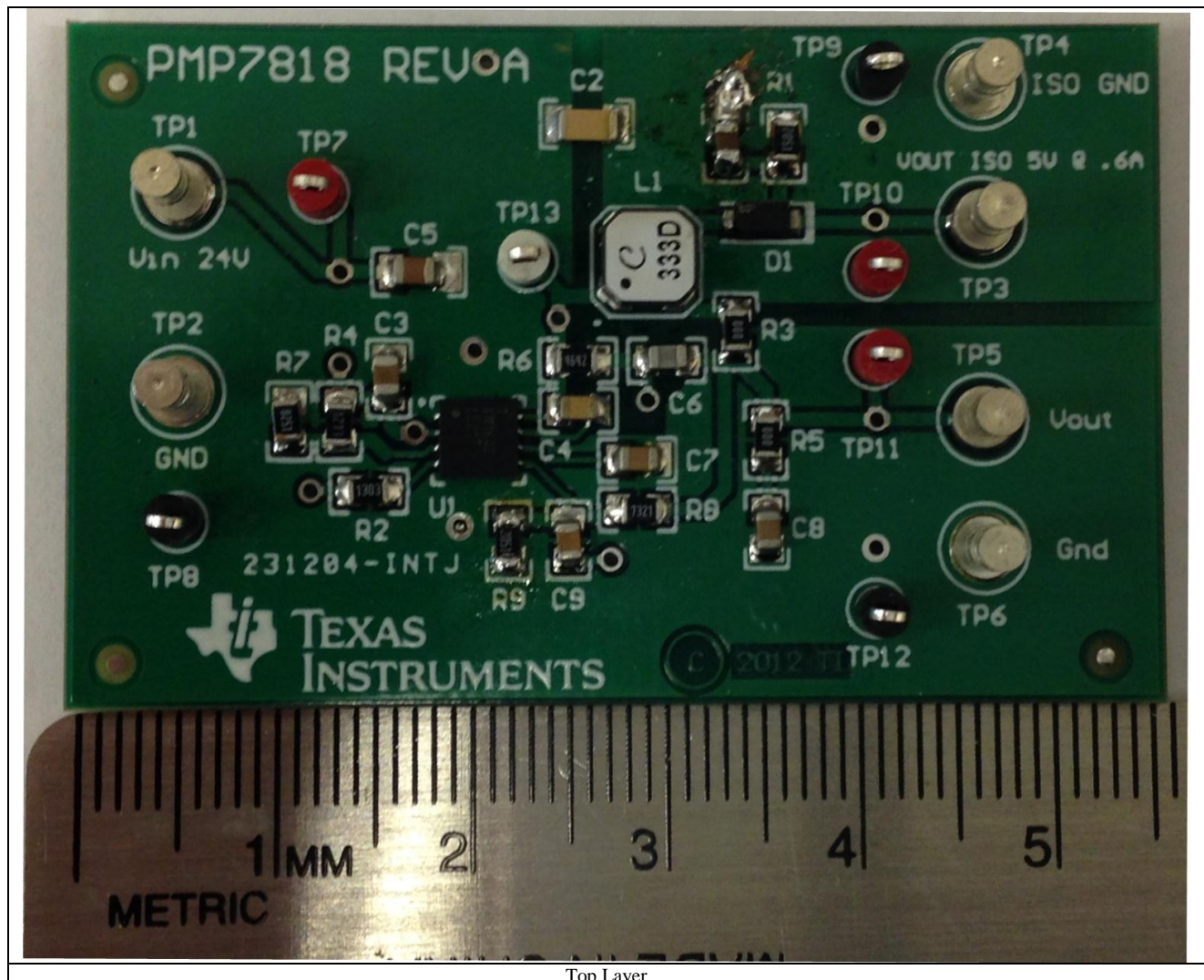2. Fabrication

The PMP9321 isolated supply was built on PMP7818 printed circuit board. This is a two layer board with overall dimensions of 2.2" (56mm) x 1.37" (35mm). The copper weight is 0.5oz on the outer layer.



3. Efficiency

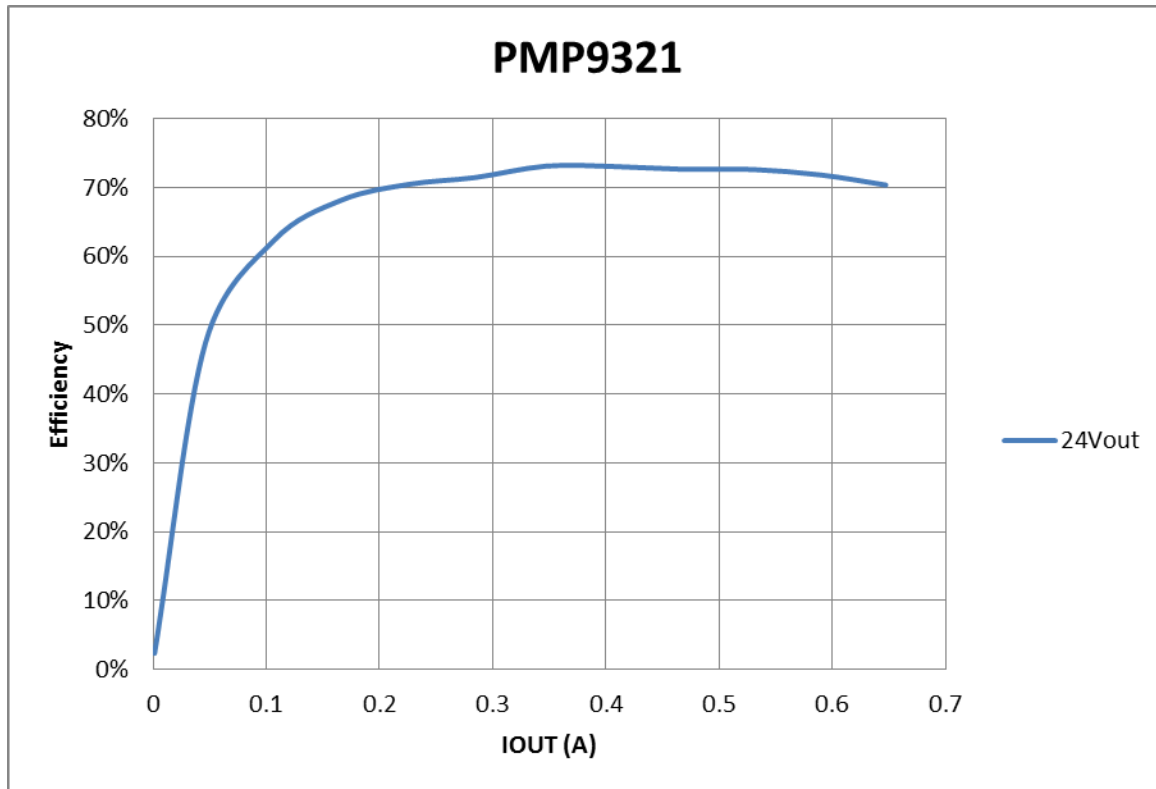


Peak efficiency of 73% was measured. Efficiency can be further improved with a lower forward voltage drop diode and also a larger coupled inductor with a lower DCR. Potential increase of around ~10%, providing a total efficiency of ~84% max, can be realized with these two adjustments in the design.

3.1 LM5017 Isolated Flyback Efficiency Data

Vin (V)	Iin (A)	Vout (V)	Iout (A)	Efficiency (%)	Pin (W)	Pout (W)	Losses (W)
24.002	0.022	5.323	0.046	47.49%	0.519	0.247	0.273
24.002	0.037	5.239	0.106	62.26%	0.895	0.558	0.338
24.002	0.053	5.193	0.167	68.19%	1.268	0.865	0.403
24.002	0.069	5.152	0.227	70.49%	1.657	1.168	0.489
24.002	0.085	5.119	0.284	71.45%	2.036	1.455	0.581
24.002	0.101	5.089	0.347	73.12%	2.414	1.765	0.649
24.002	0.117	5.063	0.407	73.06%	2.820	2.060	0.760
24.002	0.135	5.037	0.467	72.66%	3.238	2.353	0.885
24.001	0.152	5.011	0.530	72.63%	3.654	2.654	1.000
24.001	0.170	4.982	0.590	71.84%	4.089	2.938	1.152

4. Thermal

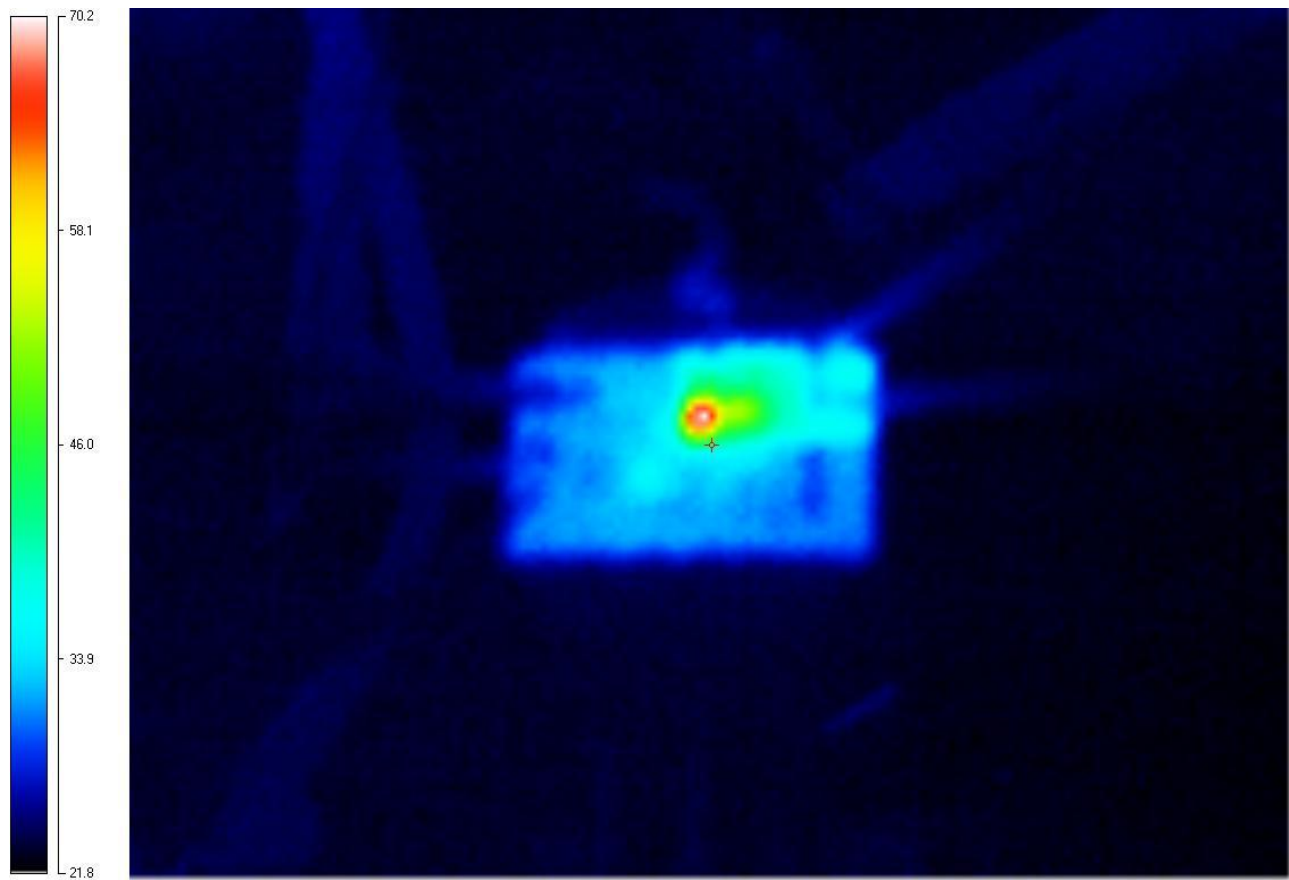4.1 Steady State Temperature - 24Vin, 5Vout with a load of 0.6A




Top View

The warmest area on the printed circuit card is the inductor.

5. Switch Node Voltage and Output Ripple Voltage

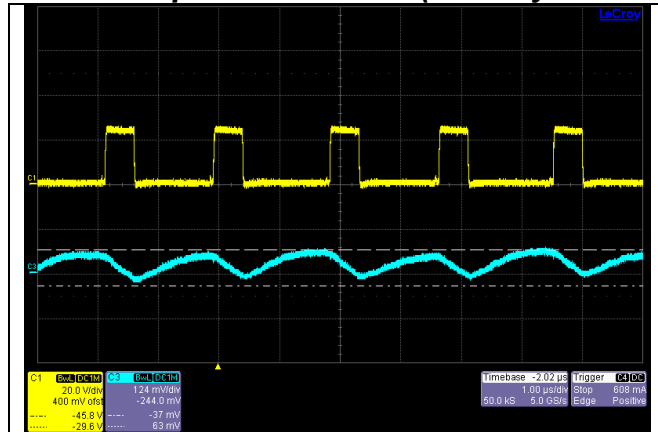5.1 24V Input – 0.6A Load (Primary Switch)




Less than 100mV p-p Ripple

Channel 1 VSW1

Channel 3 VOUT

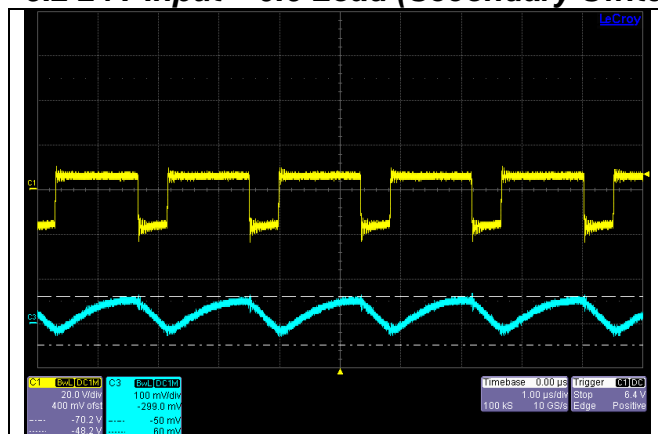5.2 24V Input – 0.6 Load (Secondary Switch)




Less than 100mV p-p Ripple

Channel 1 VSW2

Channel 3 VOUT

6. Transient Response

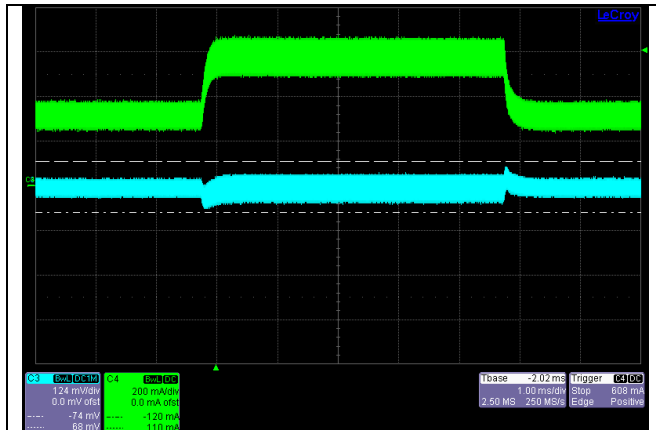6.1 24V Input – 0.3A to 0.6A, 100mA/ μ s, 100 Hz, 50% duty cycle, 5V out.



Cursors indicate ~100mV maximum deviation across output capacitor.

Channel 3 VOUT

Channel 4 IOUT

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated