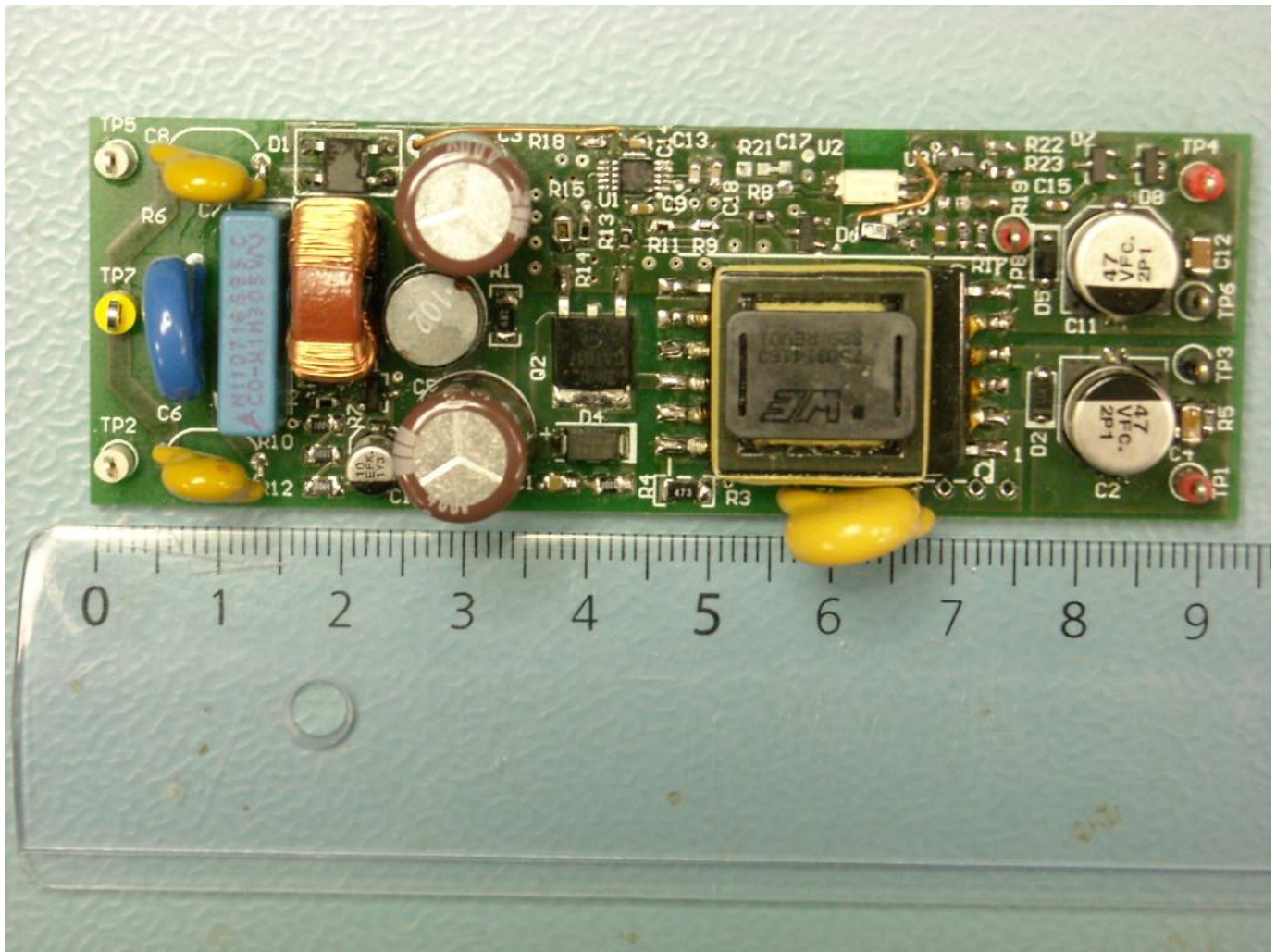



PICTURE OF THE BOARD:




1 Startup

The output voltage behavior at startup is shown in the images below. Four cases have been analyzed at 24Vdc, 320Vdc, full and no-load.

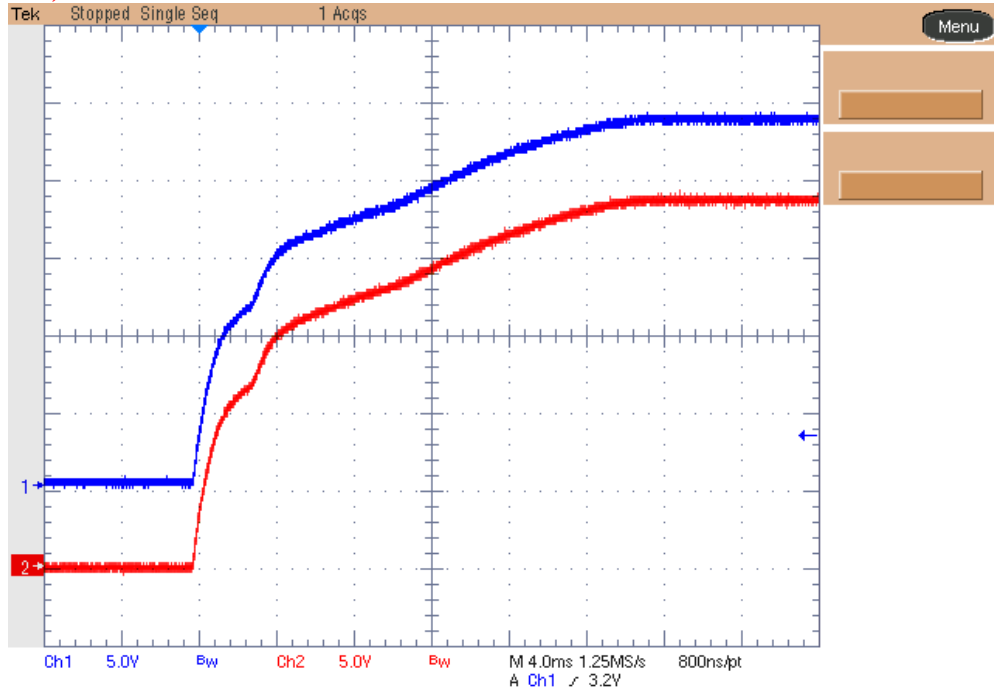
Ch.1: Vout-1 (5V/div, 4ms/div, DC coupling, 20MHz BWL), Ch.2: Vout-2 (5V/div)
Vin = 24Vdc, Full load.




Vin = 24Vdc, No load.

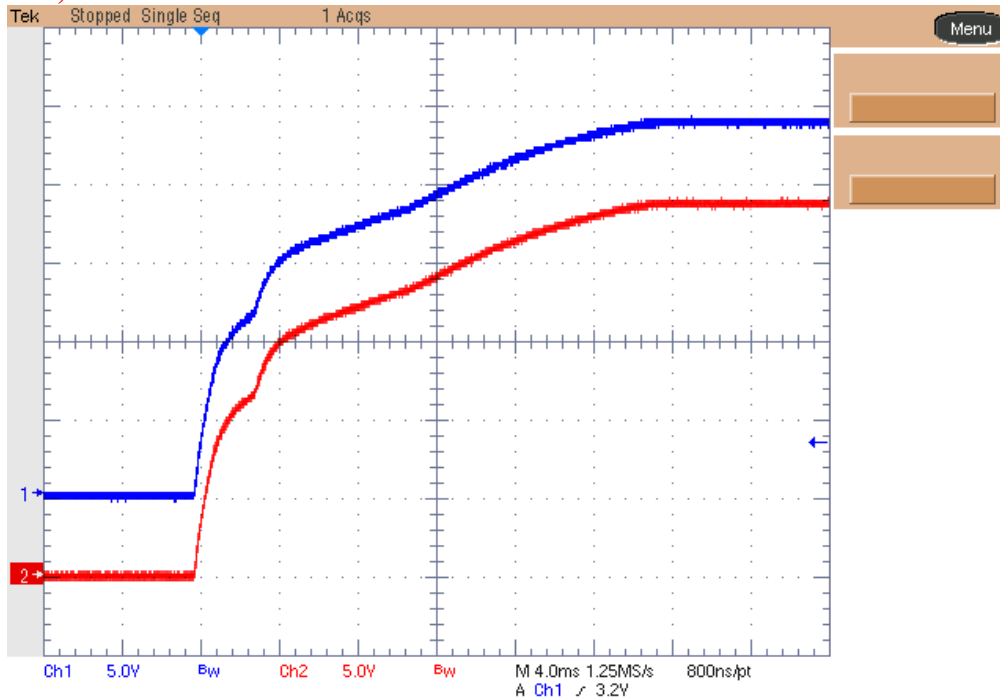

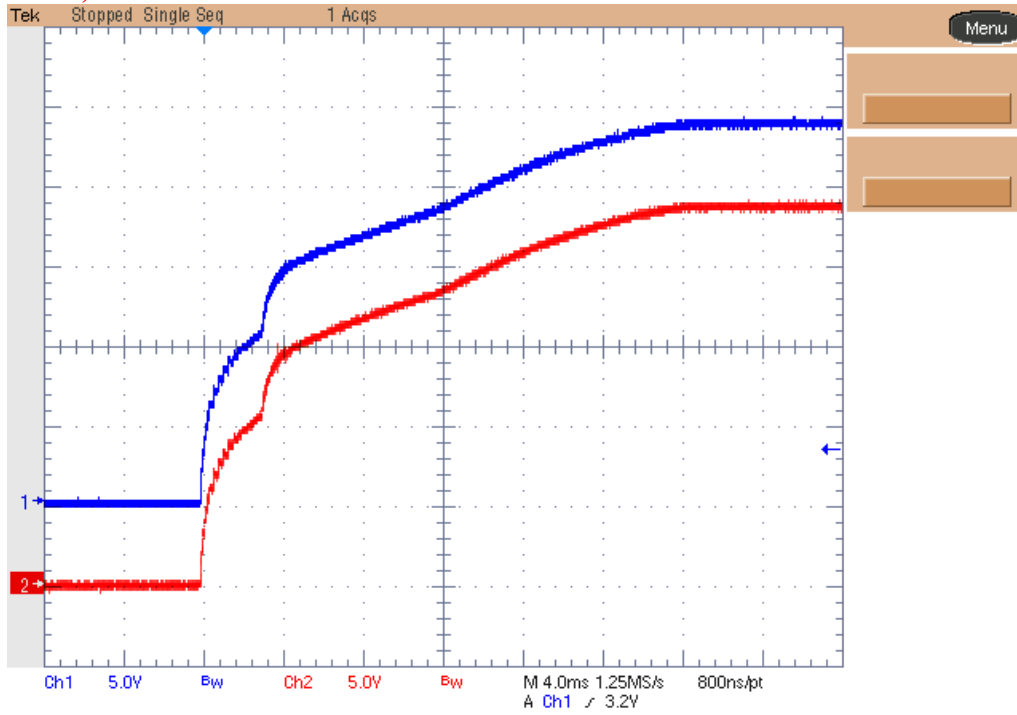Ch.1: Vout-1 (5V/div, 4ms/div, DC coupling, 20MHz BWL), Ch.2: Vout-2 (5V/div)
Vin = 320Vdc, Full load.




Vin = 320Vdc, No load.

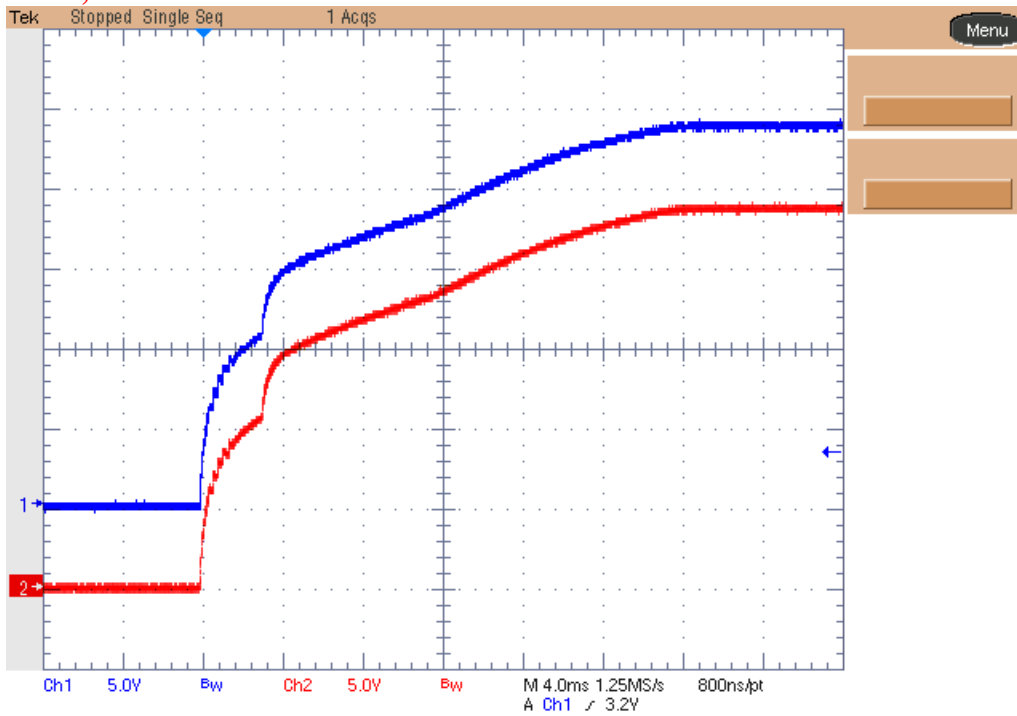

2 Shut down



The output voltage behavior during shut down is shown in the image below. The input voltage has been set to 320Vdc and the outputs loaded with resistors at full load.

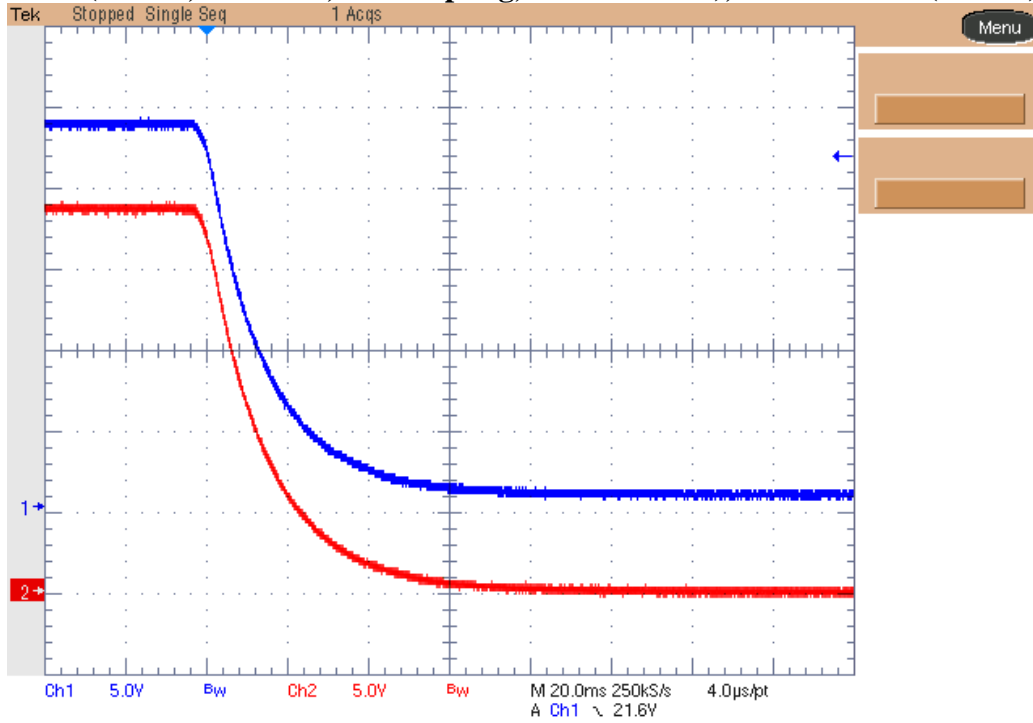Ch.1: Vout-1 (5V/div, 20ms/div, DC coupling, 20MHz BWL), Ch.2: Vout-2 (5V/div)



3 Efficiency

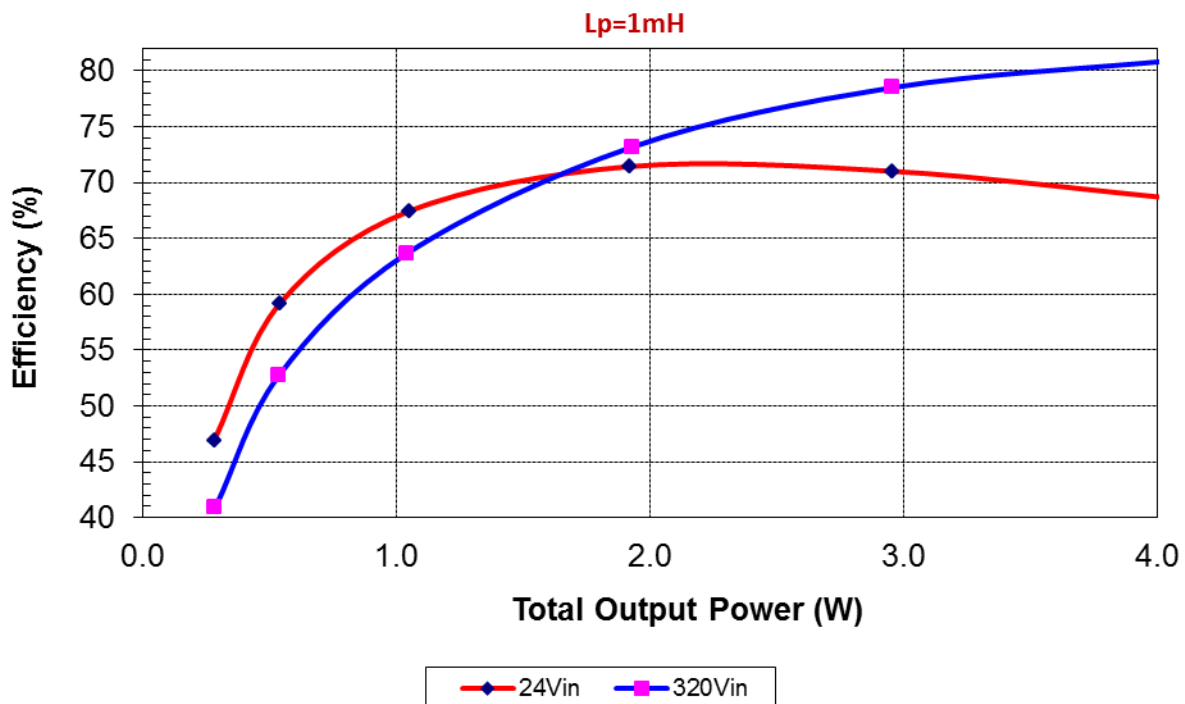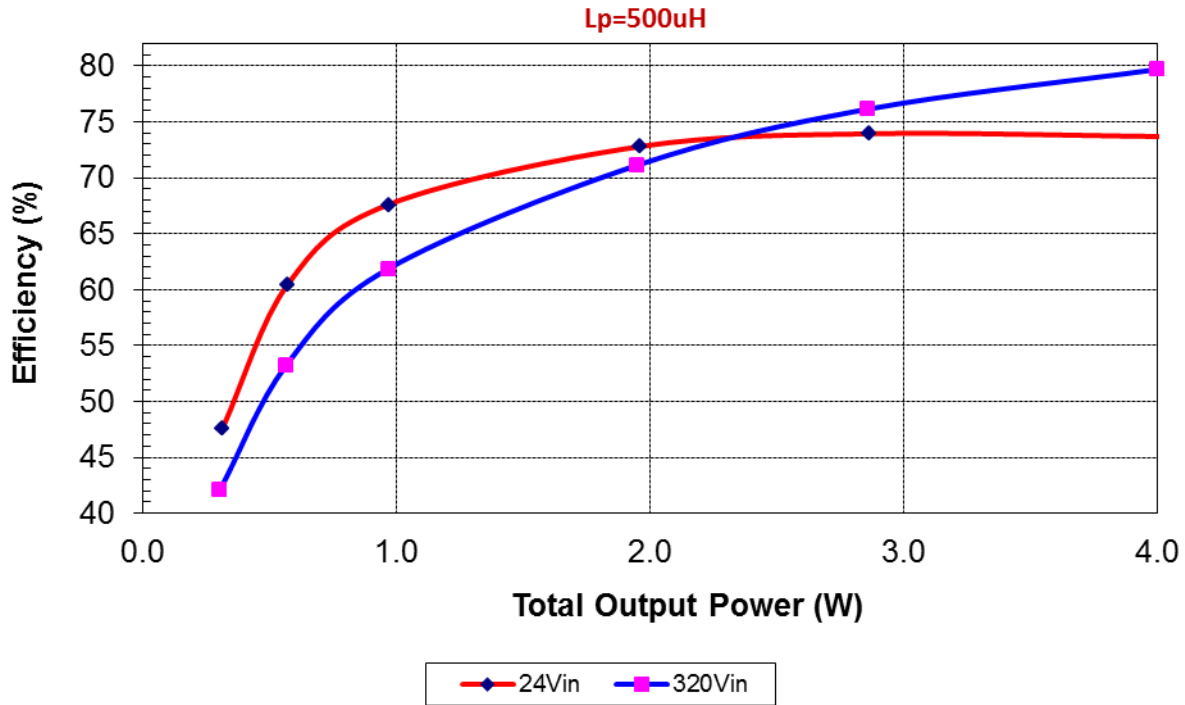The efficiency data are shown in the tables and graph below. A DC voltage source has been set to the maximum and minimum input voltage (24Vdc and 320Vdc). Two different transformers have been used: the first one with $L_p=500\mu\text{H}$ and the second one with 1mH. The turn ratios were the same for both transformers. The 500uH value has been chosen for the final design.



Lp=500uH, 24Vin									
Iout-1 (mA)	Vout-1 (V)	Iout-2 (mA)	Vout-2 (V)	Pout (W)	Iin (mA)	Vin (Vdc)	Pin (W)	Ploss (W)	Eff (%)
0	23.72	0	23.69	0.000	11.98	24.05	0.288	0.2881	0.00
6.5	23.71	6.7	23.69	0.313	27.35	24.04	0.657	0.3447	47.58
12.1	23.70	12.0	23.69	0.571	39.3	24.02	0.944	0.3729	60.49
20.7	23.69	20.1	23.69	0.967	59.6	23.99	1.430	0.4633	67.60
40.6	23.69	42.1	23.69	1.959	112.5	23.92	2.691	0.7318	72.80
60.3	23.68	60.7	23.68	2.865	162.4	23.86	3.875	1.0096	73.95
86.2	23.65	84.5	23.68	4.040	228.3	24.01	5.481	1.4419	73.70


Lp=500uH, 320Vin									
Iout-1 (mA)	Vout-1 (V)	Iout-2 (mA)	Vout-2 (V)	Pout (W)	Iin (mA)	Vin (Vdc)	Pin (W)	Ploss (W)	Eff (%)
0	23.73	0	23.69	0.000	1.025	320.2	0.328	0.3282	0.00
6.2	23.72	6.6	23.69	0.303	2.25	320.2	0.720	0.4170	42.12
11.8	23.71	12.0	23.69	0.564	3.31	320.2	1.060	0.4958	53.22
20.7	23.70	20.1	23.69	0.967	4.88	320.2	1.563	0.5958	61.87
40.7	23.70	41.6	23.69	1.950	8.56	320.2	2.741	0.7908	71.15
60.5	23.70	60.1	23.69	2.858	11.72	320.2	3.753	0.8951	76.15
84.5	23.69	84.3	23.69	3.999	15.67	320.2	5.018	1.0187	79.70

Lp=1mH, 24Vin									
Iout-1 (mA)	Vout-1 (V)	Iout-2 (mA)	Vout-2 (V)	Pout (W)	Iin (mA)	Vin (Vdc)	Pin (W)	Ploss (W)	Eff (%)
0	23.69	0	23.69	0.000	11.02	24.08	0.265	0.2654	0.00
6.1	23.68	5.7	23.69	0.279	24.77	24.07	0.596	0.3167	46.88
11.7	23.67	11.1	23.69	0.540	37.91	24.06	0.912	0.3722	59.19
22.5	23.67	21.9	23.68	1.051	64.9	24.01	1.558	0.5071	67.46
40.3	23.67	40.7	23.68	1.918	110.7	24.25	2.684	0.7668	71.44
62.8	23.65	62.1	23.68	2.956	172.2	24.17	4.162	1.2063	71.02
86.2	23.64	86.3	23.68	4.081	247.3	24.08	5.955	1.8736	68.54


Lp=1mH, 320Vin									
Iout-1 (mA)	Vout-1 (V)	Iout-2 (mA)	Vout-2 (V)	Pout (W)	Iin (mA)	Vin (Vdc)	Pin (W)	Ploss (W)	Eff (%)
0	23.71	0	23.69	0.000	1.026	320.3	0.329	0.3286	0.00
6.2	23.68	5.8	23.68	0.284	2.17	320.3	0.695	0.4109	40.88
11.5	23.68	11.1	23.68	0.535	3.17	320.3	1.015	0.4802	52.71
22.0	23.68	21.9	23.68	1.040	5.10	320.3	1.634	0.5940	63.64
40.8	23.67	40.7	23.68	1.930	8.23	320.3	2.636	0.7066	73.20
62.8	23.67	62.0	23.68	2.955	11.75	320.3	3.764	0.8089	78.51
86.1	23.67	86.1	23.68	4.077	15.72	320.3	5.035	0.9583	80.97


4 Output Voltage Regulation

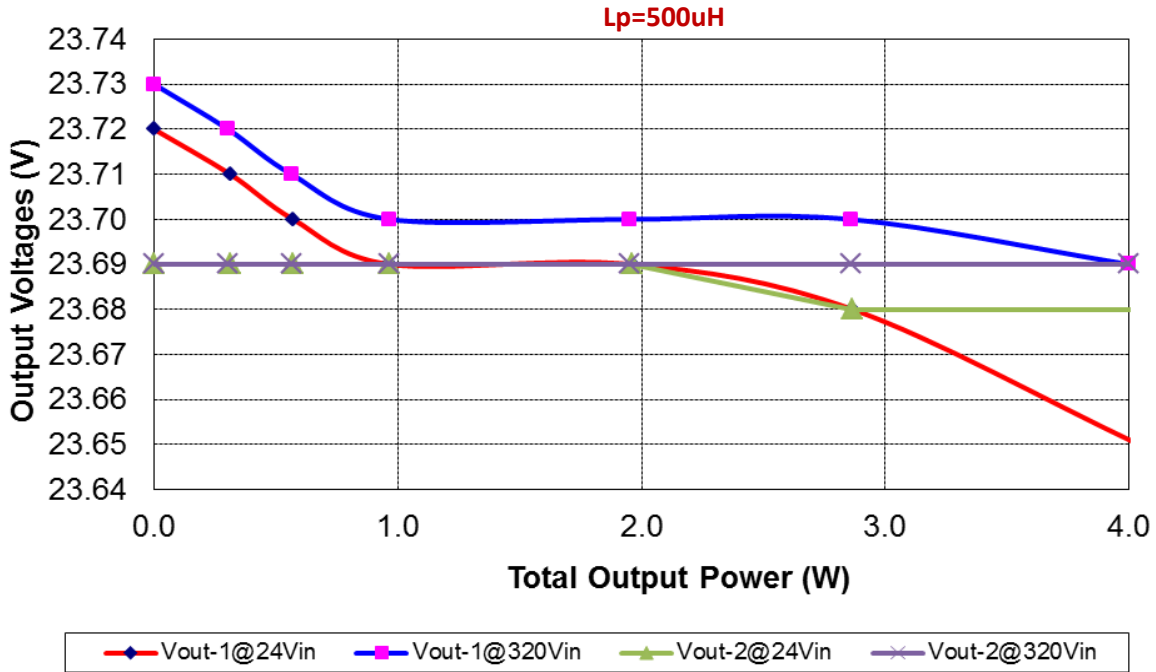The output voltage variation as function of load and input voltage is shown below. The two output loads have been varied proportionally. From now and beyond, the primary inductance of the transformer was 500uH.



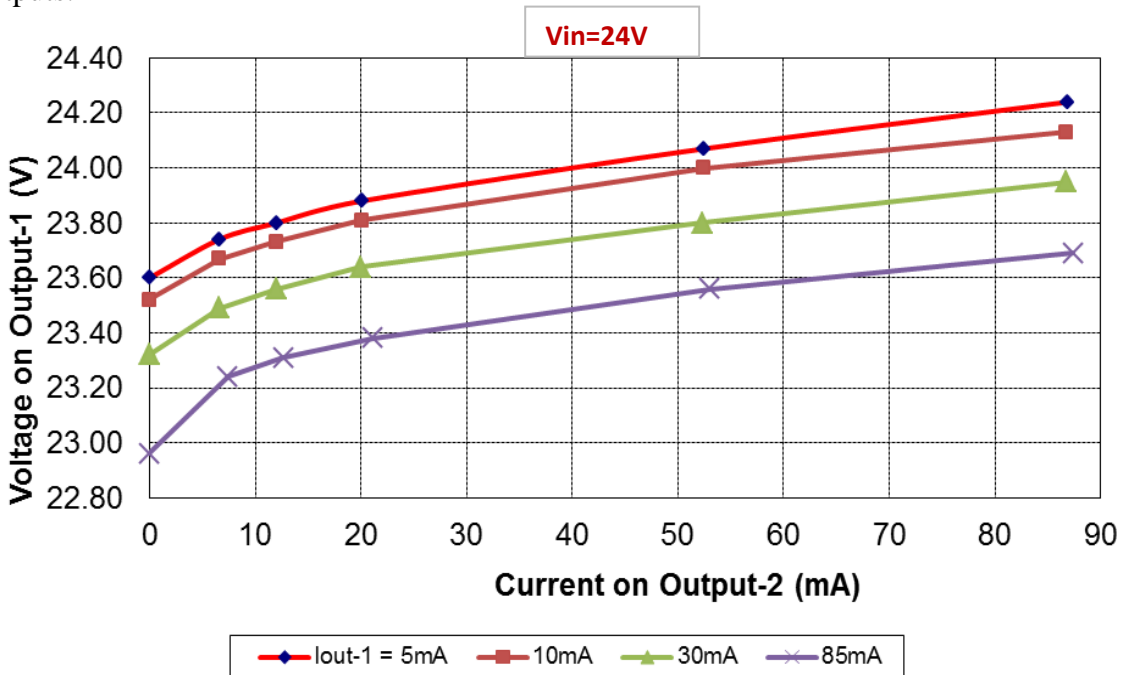A further measurement has been performed in order to measure the cross regulation between outputs.




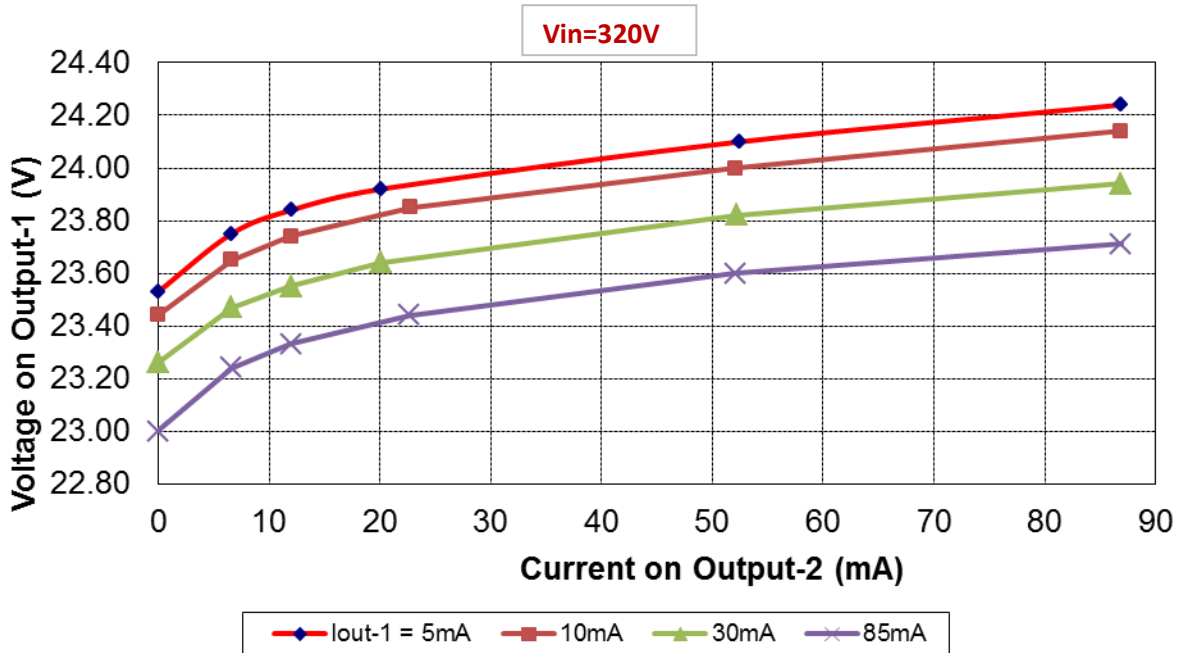


5 Output Ripple Voltage

The output ripple voltage (the same for both outputs) is shown in the plots below. The input was set to 24Vdc and 320Vdc while the output was fully loaded.

Ch.2: Vout-1 (50mV/div, 4us/div, AC coupling, 20MHz BWL), Vin = 24Vdc

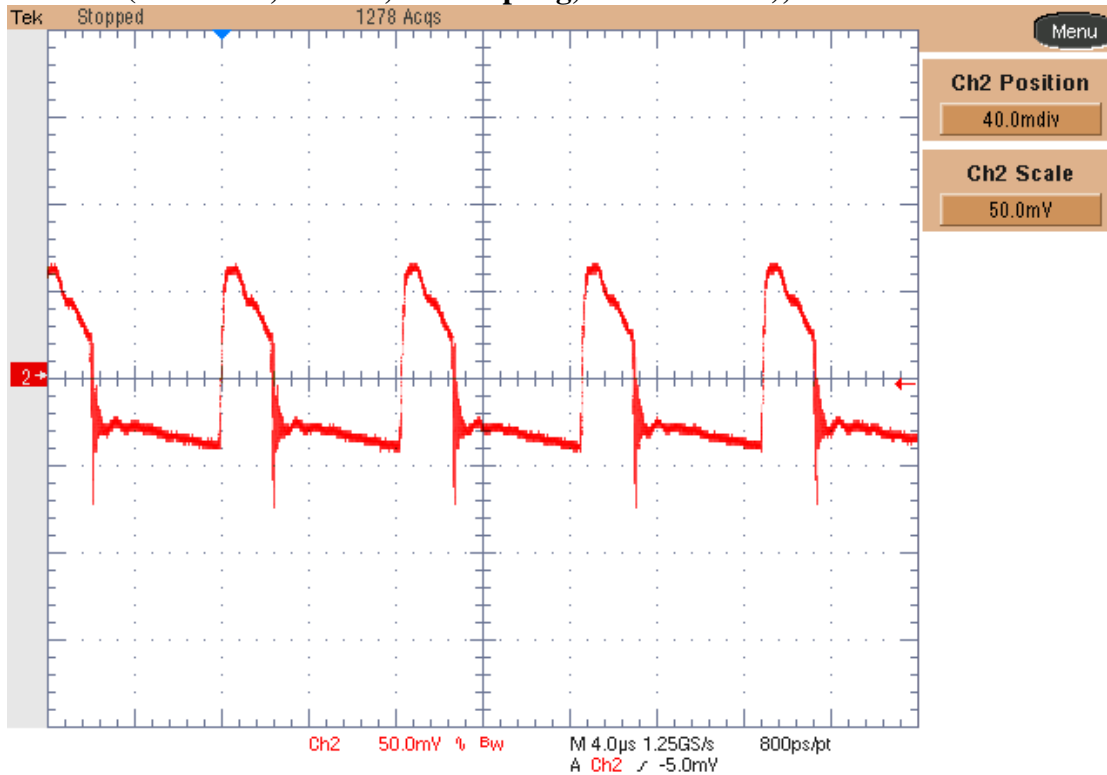

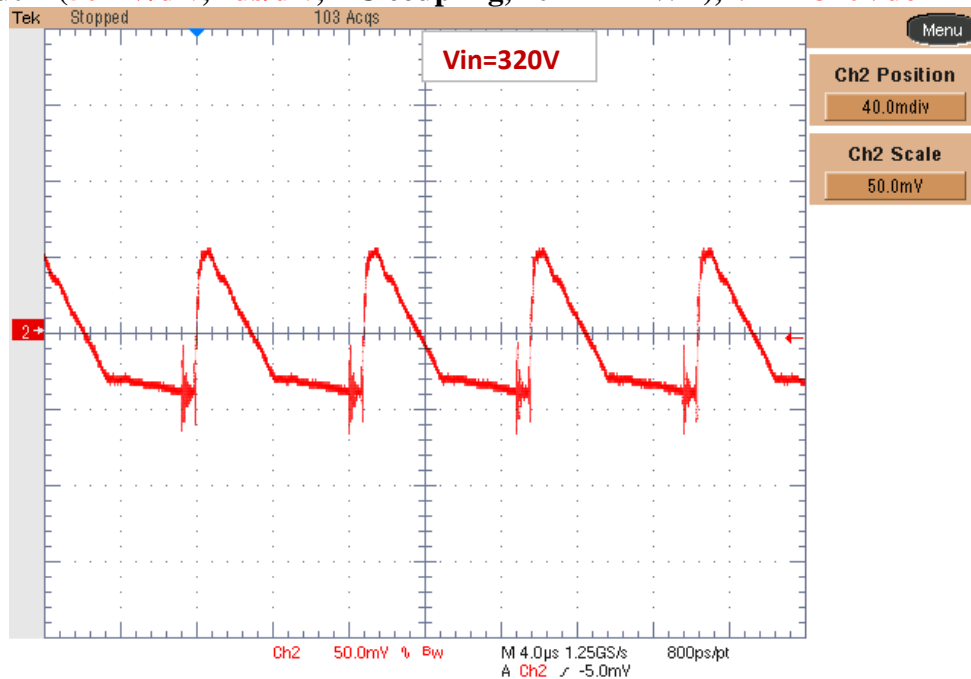Ch.2: Vout-1 (50mV/div, 4us/div, AC coupling, 20MHz BWL), Vin = 320Vdc



6 Transient response

The image below shows the transient response on the output-1 voltage when its load has been switched between 10mA and 100mA while the load on output-2 has been kept constant to 85mA. The input voltage was 24Vdc.


Ch2: Vout-1 (100mV/div, 1ms/div, AC coupled, 20MHz BWL), Ch4: Iout-1 (50mA/div)




7 Switching Node Waveform

The image below shows the peak voltage on drain of Q2 at 24Vdc and 320Vdc input voltage in full load conditions.

Ch3: Q2 drain Voltage (20V/div, 2us/div, No BWL), Vin=24Vdc.

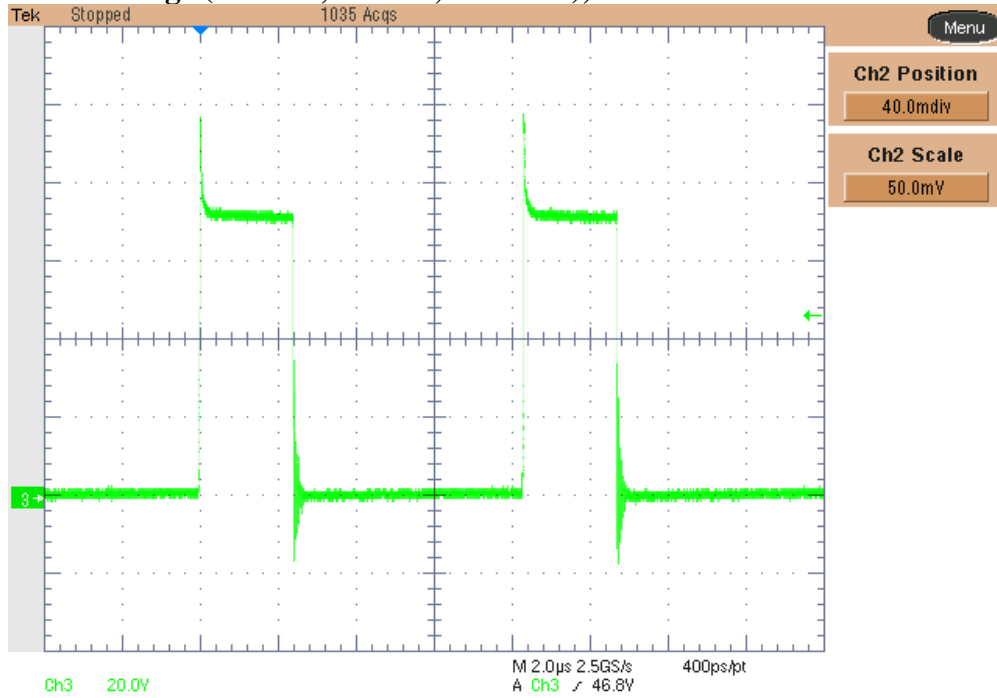


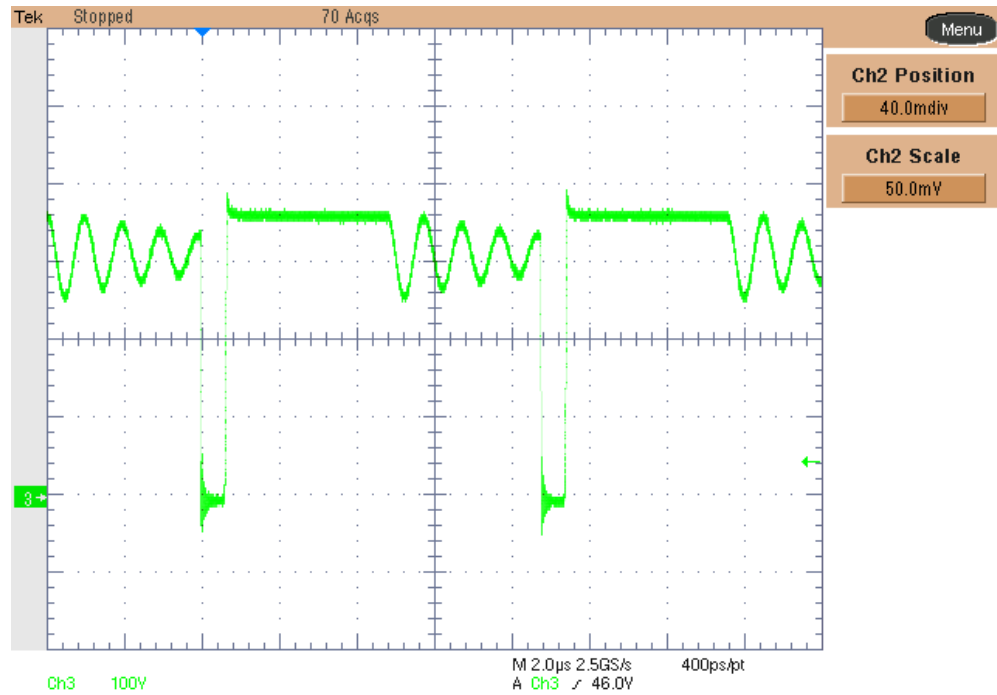Ch3: Q2 drain Voltage (100V/div, 2us/div, No BWL), Vin=24Vdc.



The load has been reduced down to 15mA for each output. The image below shows that the converter works in burst mode. The input voltage was 320Vdc.

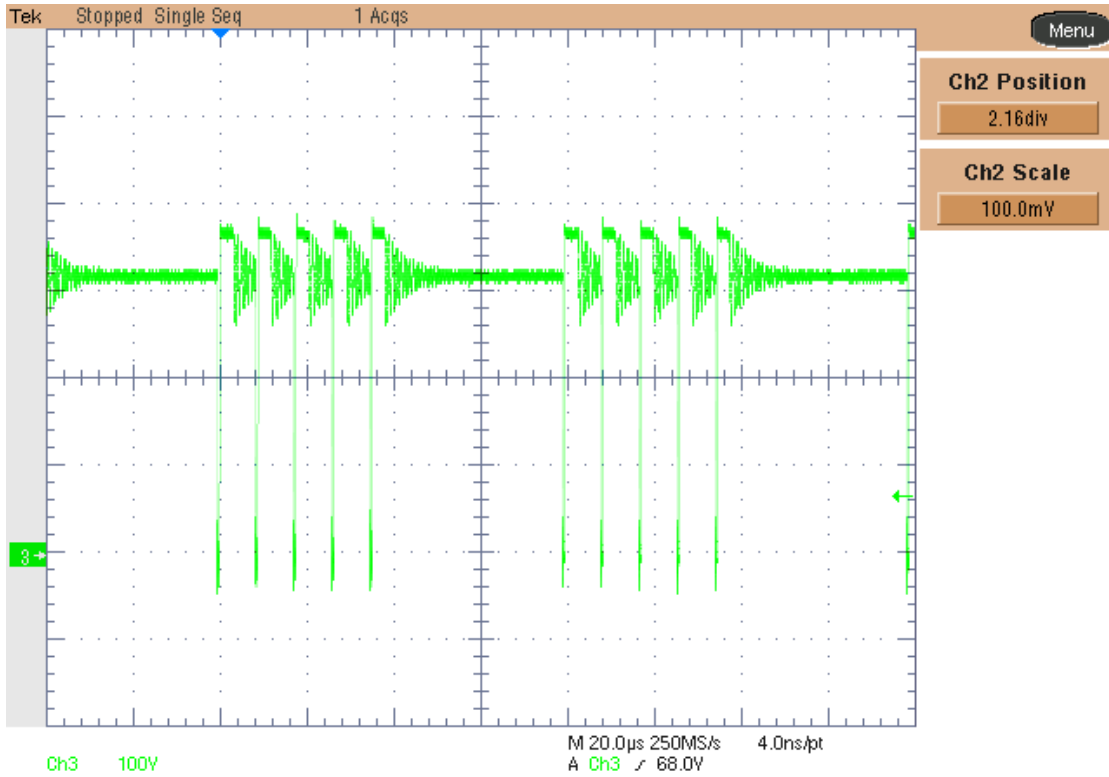Ch3: Q2 drain Voltage (100V/div, 20us/div, No BWL), Vin=320Vdc.



8 Thermal Analysis

The thermal analysis of the converter shows the temperatures for each component, in the graphs below. The converter has been placed horizontally on the bench without any forced convection. The input voltage was 24Vdc for the first scan and 320Vdc for the second one. Both outputs have been fully loaded. The ambient temperature was 25C.

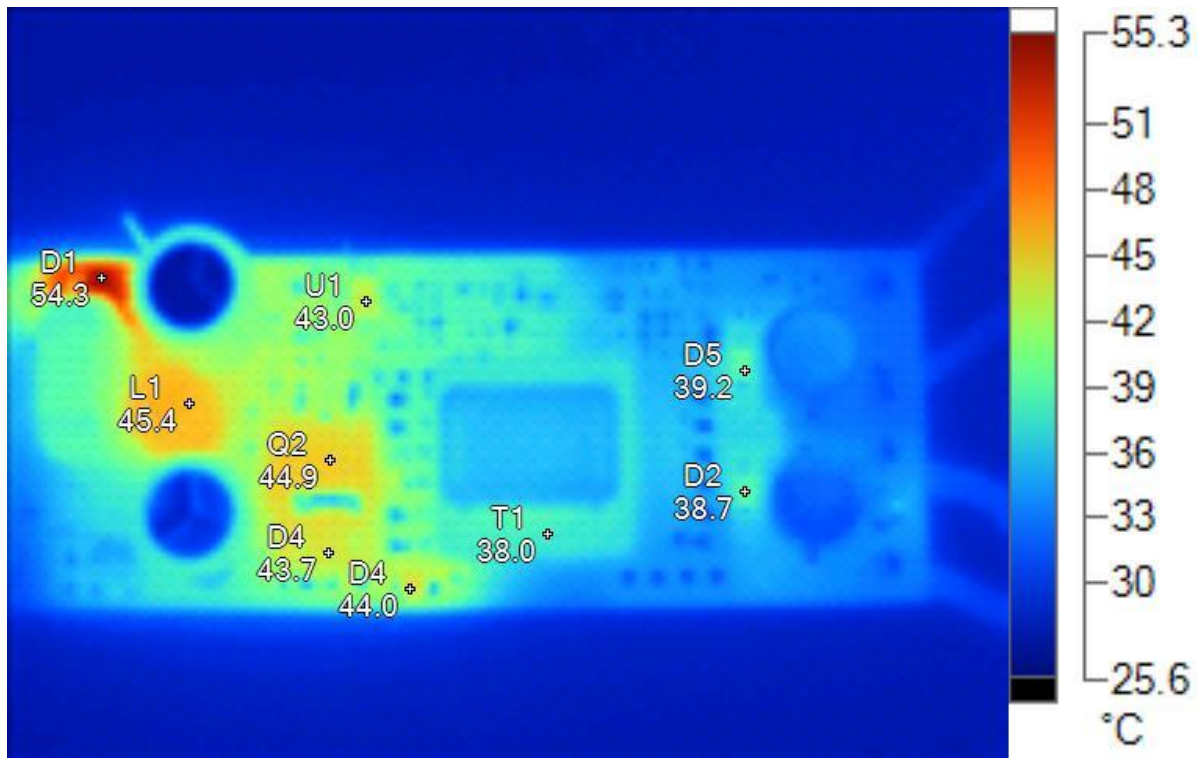


Image Info

Background temperature	25.0°C
Average Temperature	31.9°C
Image Range	26.8°C to 54.3°C
Camera Model	Ti40FT
Camera Manufacturer	Fluke
Image Time	7/29/2013 2:41:22 PM

Main Image Markers

Name	Temperature
D1	54.3°C
L1	45.4°C
Q2	44.9°C
D4	43.7°C
U1	43.0°C
T1	38.0°C
D5	39.2°C
D2	38.7°C
D4	44.0°C

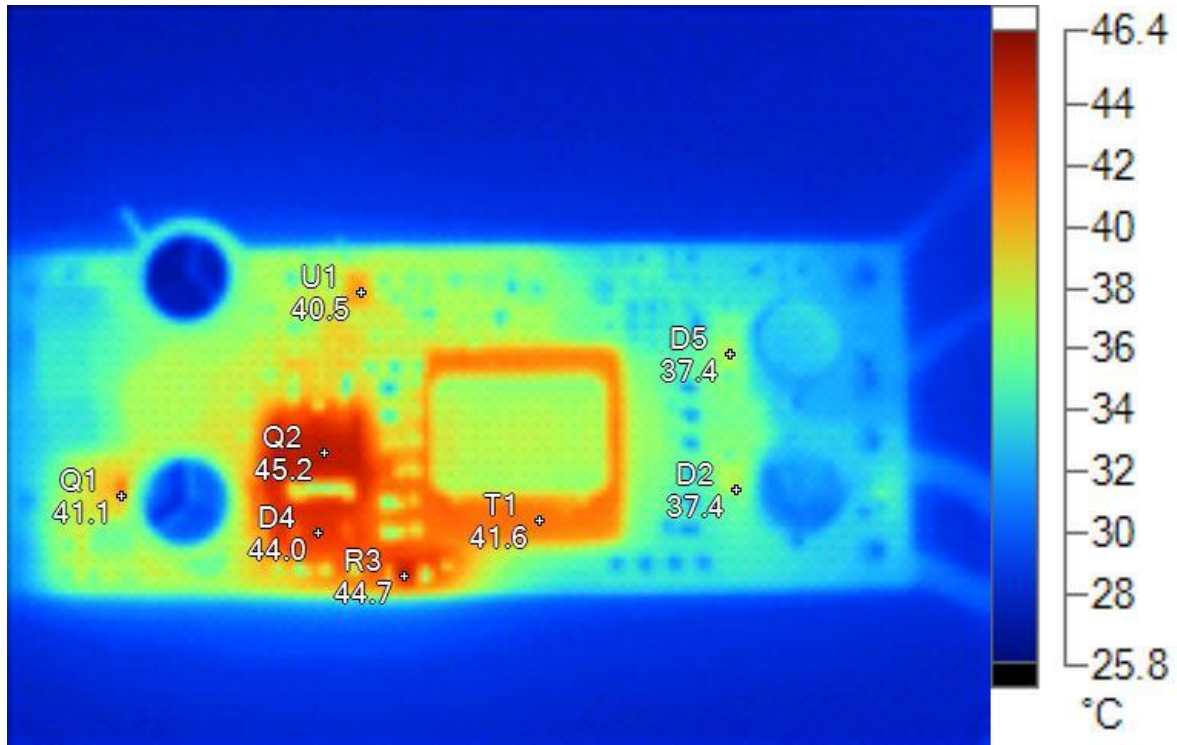


Image Info

Background temperature	25.0°C
Average Temperature	31.6°C
Image Range	26.8°C to 45.4°C
Camera Model	Ti40FT
Camera Manufacturer	Fluke
Image Time	7/29/2013 2:45:12 PM

Main Image Markers


Name	Temperature
Q1	41.1°C
Q2	45.2°C
R3	44.7°C
D4	44.0°C
U1	40.5°C
D5	37.4°C
D2	37.4°C
T1	41.6°C

9 Loop Analysis

The loop analysis on the converter shows results regarding phase margin and gain margin, as well as crossover frequency. The converter has been supplied @ 24Vdc and 320Vdc input voltage while fully loaded.

The graph below shows the worst case gain and phase margin, measured when the input voltage was 24Vdc and therefore the converter was running in CCM:

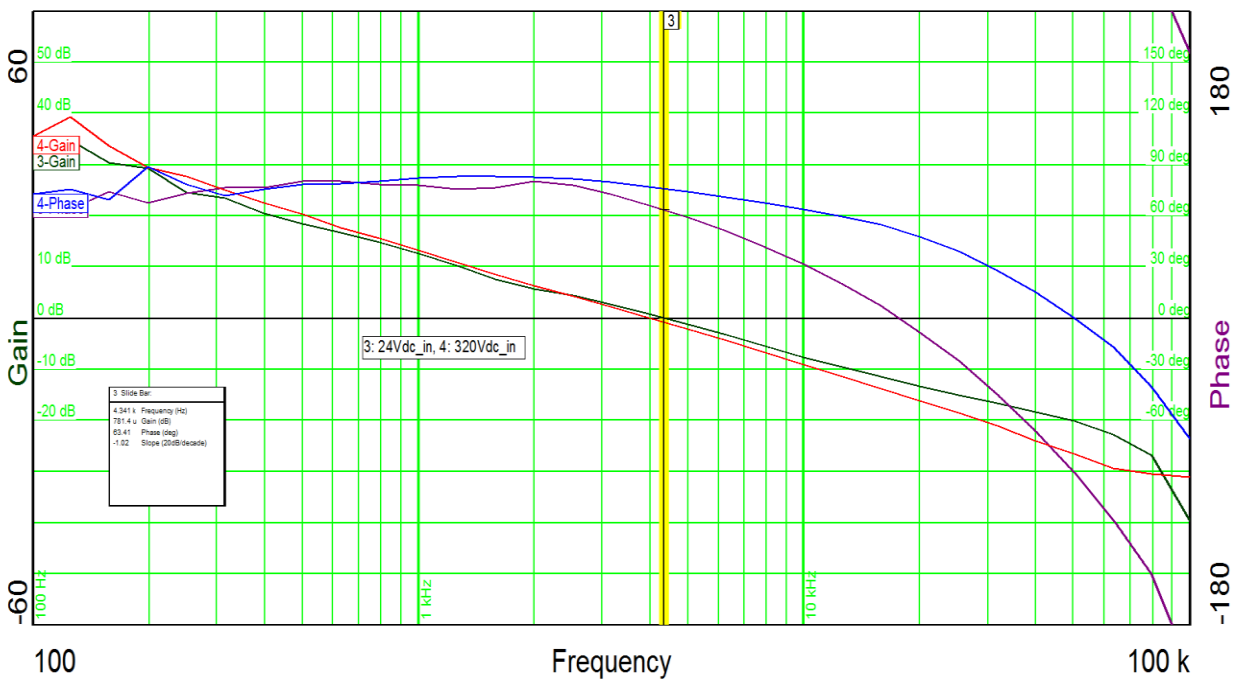- 1) Phase margin = 63.41 deg.
- 2) Gain margin = 12.34 dB
- 3) Crossover frequency = 4.341 KHz



EVALUATION BOARD/KIT/MODULE (EVM) WARNINGS, RESTRICTIONS AND DISCLAIMER

For Feasibility Evaluation Only, in Laboratory/Development Environments. The EVM is not a complete product. It is intended solely for use for preliminary feasibility evaluation in laboratory / development environments by technically qualified electronics experts who are familiar with the dangers and application risks associated with handling electrical / mechanical components, systems and subsystems. It should not be used as all or part of a production unit.

Your Sole Responsibility and Risk. You acknowledge, represent and agree that:

1. You have unique knowledge concerning Federal, State and local regulatory requirements (including but not limited to Food and Drug Administration regulations, if applicable) which relate to your products and which relate to your use (and/or that of your employees, affiliates, contractors or designees) of the EVM for evaluation, testing and other purposes.
2. You have full and exclusive responsibility to assure the safety and compliance of your products with all such laws and other applicable regulatory requirements, and also to assure the safety of any activities to be conducted by you and/or your employees, affiliates, contractors or designees, using the EVM. Further, you are responsible to assure that any interfaces (electronic and/or mechanical) between the EVM and any human body are designed with suitable isolation and means to safely limit accessible leakage currents to minimize the risk of electrical shock hazard.
3. Since the EVM is not a completed product, it may not meet all applicable regulatory and safety compliance standards (such as UL, CSA, VDE, CE, RoHS and WEEE) which may normally be associated with similar items. You assume full responsibility to determine and/or assure compliance with any such standards and related certifications as may be applicable. You will employ reasonable safeguards to ensure that your use of the EVM will not result in any property damage, injury or death, even if the EVM should fail to perform as described or expected.

Certain Instructions. Exceeding the specified EVM ratings (including but not limited to input and output voltage, current, power, and environmental ranges) may cause property damage, personal injury or death. If there are questions concerning these ratings please contact a TI field representative prior to connecting interface electronics including input power and intended loads. Any loads applied outside of the specified output range may result in unintended and/or inaccurate operation and/or possible permanent damage to the EVM and/or interface electronics. Please consult the EVM User's Guide prior to connecting any load to the EVM output. If there is uncertainty as to the load specification, please contact a TI field representative. During normal operation, some circuit components may have case temperatures greater than 60°C as long as the input and output ranges are maintained at nominal ambient operating temperature. These components include but are not limited to linear regulators, switching transistors, pass transistors, and current sense resistors which can be identified using the EVM schematic located in the EVM User's Guide. When placing measurement probes near these devices during normal operation, please be aware that these devices may be very warm to the touch.

Agreement to Defend, Indemnify and Hold Harmless. You agree to defend, indemnify and hold TI, its licensors and their representatives harmless from and against any and all claims, damages, losses, expenses, costs and liabilities (collectively, "Claims") arising out of or in connection with any use of the EVM that is not in accordance with the terms of this agreement. This obligation shall apply whether Claims arise under the law of tort or contract or any other legal theory, and even if the EVM fails to perform as described or expected.

Safety-Critical or Life-Critical Applications. If you intend to evaluate TI components for possible use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, such as devices which are classified as FDA Class III or similar classification, then you must specifically notify TI of such intent and enter into a separate Assurance and Indemnity Agreement.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated