

Power Supply Design for Renesas R-Car M3 Using LP87565-Q1 and LP8732-Q1

This document details the design considerations of a power solution for the Renesas R-Car M3x SoC (system-on-chip) power rails using the LP87565-Q1 and LP8732-Q1 power management ICs. Additional TLV733P-Q1 LDOs are used for the peripheral rails. This power solution assumes an input voltage of 5 V (+/-5%). If the system input voltage is higher, for example a car battery, a buck converter as a pre-regulator should be used to generate a supply voltage of 5 V.

The LP87565-Q1 has four buck converters configured to work as dual 2-phase converters. LP8732-Q1 has two 2 A buck converters and two 300 mA LDOs. These devices are OTP programmable, meaning default register values are set in TI production line to desired values and it is also possible to control registers through I²C after power-up. Contact TI sales for samples with specific OTP settings. I²C configurable samples are available with part numbers LP875650RNFTQ1 and LP873200RHDRQ1. See the [LP8756x-Q1 Configuration Guide](#) and [LP8733-Q1 and LP8732-Q1 Configuration Guide](#) for details how to use these I²C configurable devices.

This power solution is an example how R-Car M3x required rails can be powered with TI PMICs. Sequencing is handled through programmable startup/shutdown delays of the PMICs and GPIOs and it only requires a single Enable signal from the system to initiate the sequencing. This power solution is possible to customize and optimize based on the actual use case regarding SoC variant, current requirements, used peripherals, and so forth.

This solution supports DVFS for core rail through I²C bus and also DDR backup feature (I²C configurable).

1 Design Parameters

[Table 1](#) shows the power rails, load requirements, and startup/shutdown sequencing requirements and [Section 7](#) shows typical measurement data.

Table 1. Design Parameters

VOLTAGE (V)	RAIL NAME	MAX LOAD (mA)	SOURCE	STARTUP DELAY (ms)	SHUTDOWN DELAY (ms)
1.82	DDR0_1.8V	300	#1 LP8732 LDO0	5	15
	DDR1_1.8V	300	#1 LP8732 LDO1	5	15
1.1	VDDQVA_DDR0	2000	#1 LP8732 Buck0	11	9
	VDDQVA_DDR1	2000	#1 LP8732 Buck1	11	9
1.8	VDDQ18	500	#2 LP8732 Buck0	10	10
	VDDIO_1V8	30	#1 TLV733P-Q1	2	18
	VDDQVA_SD1	35	#2 TLV733P-Q1	12	8
	VDDQVA_SD2	35	#3 TLV733P-Q1	12	8
	VDDQVA_SD3	35	#4 TLV733P-Q1	12	8
3.3	VDDQVA_SD0	35	#2 LP8732 LDO0	12	8
	VDDQ33	1200	#2 LP8732 Buck1	9	11
	VDDIO_3V3	30	#5 TLV733P-Q1	2	18
0.9	VDD_DVFS	8000	LP87565 Buck0+1	8	12
0.82	VDD	8000	LP87565 Buck2+3	6	14
2.5	VDDQ25_ETH	40	#2 LP8732 LDO1	10	10
-	nRESET (PGOOD)	-	PGOOD / GPIO	22	0

2 Power Solution

Figure 1 shows an example block diagram of LP87565x-Q1, 2 pcs LP8732x-Q1, and 5 pcs TLV733P-Q1 devices powering the R-Car M3-W power rails.

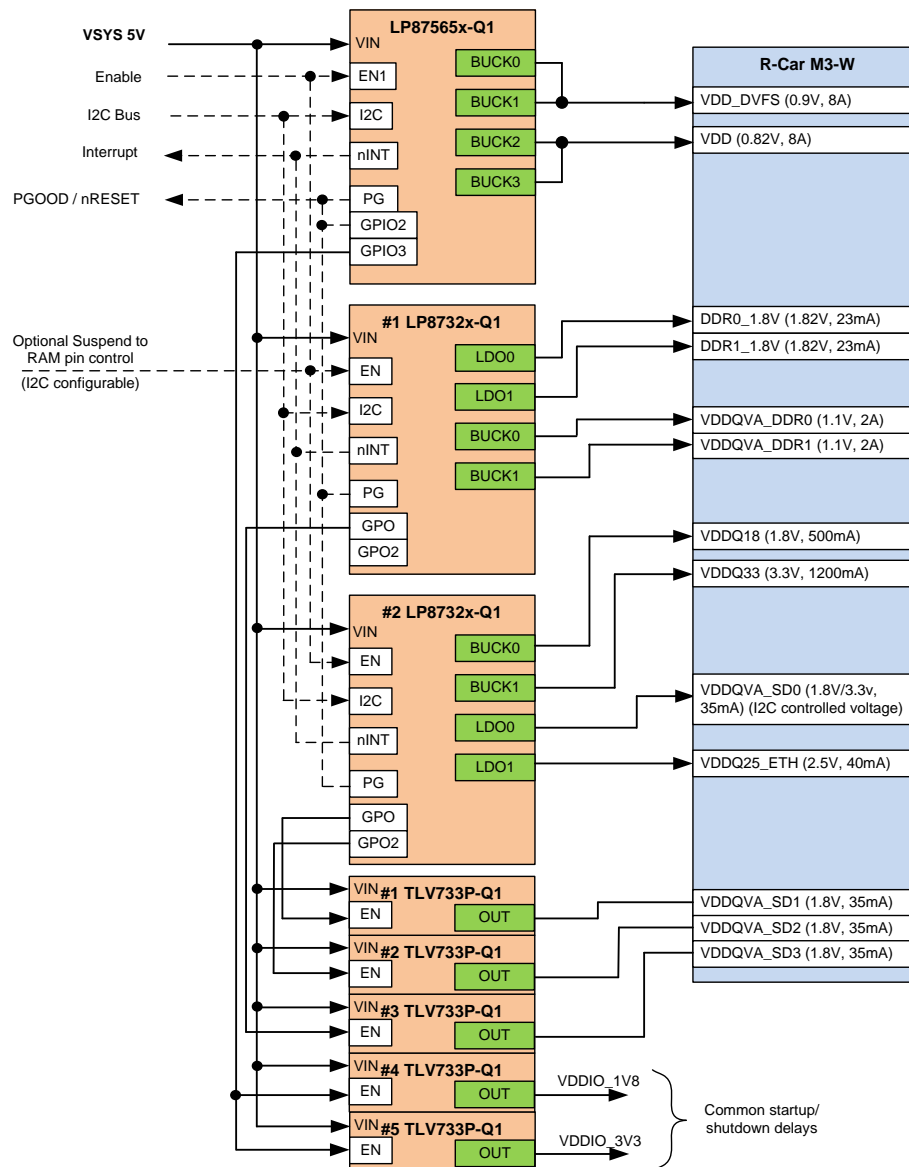


Figure 1. R-Car M3W Power Solution Block Diagram

Main features:

- After the devices are powered, the microcontroller can set the EN pin high to initiate the startup sequence.
- Startup delays are controlled internally in the LP87565-Q1 and LP8732-Q1 logic and TLV733P-Q1s are controlled with PMIC GPIOs.
- I²C can be used to read status registers and reset interrupts.
- All PMIC devices have dedicated I²C slave address so they can share the same I²C bus. Note: If you are using generic I²C configurable PMICs, the LP873200RHDRQ1 would have to be used with pin-to-pin compatible LP873300RHDRQ1 to achieve unique slave ID.
- PGOOD signals act as nRESET signal for the SoC and LP87565-Q1 GPIO2 keeps the signal low at startup for predefined time.

- Voltage control (1.8 V / 3.3 V) VDDQVA_SD0 rail done through I²C bus
- DDR backup functionality through I²C control. Core rail (VDD_DVFS) DVFS support through I²C

3 Sequencing

3.1 Startup

Figure 2 shows an example startup timing of the power rails and corresponding signals.

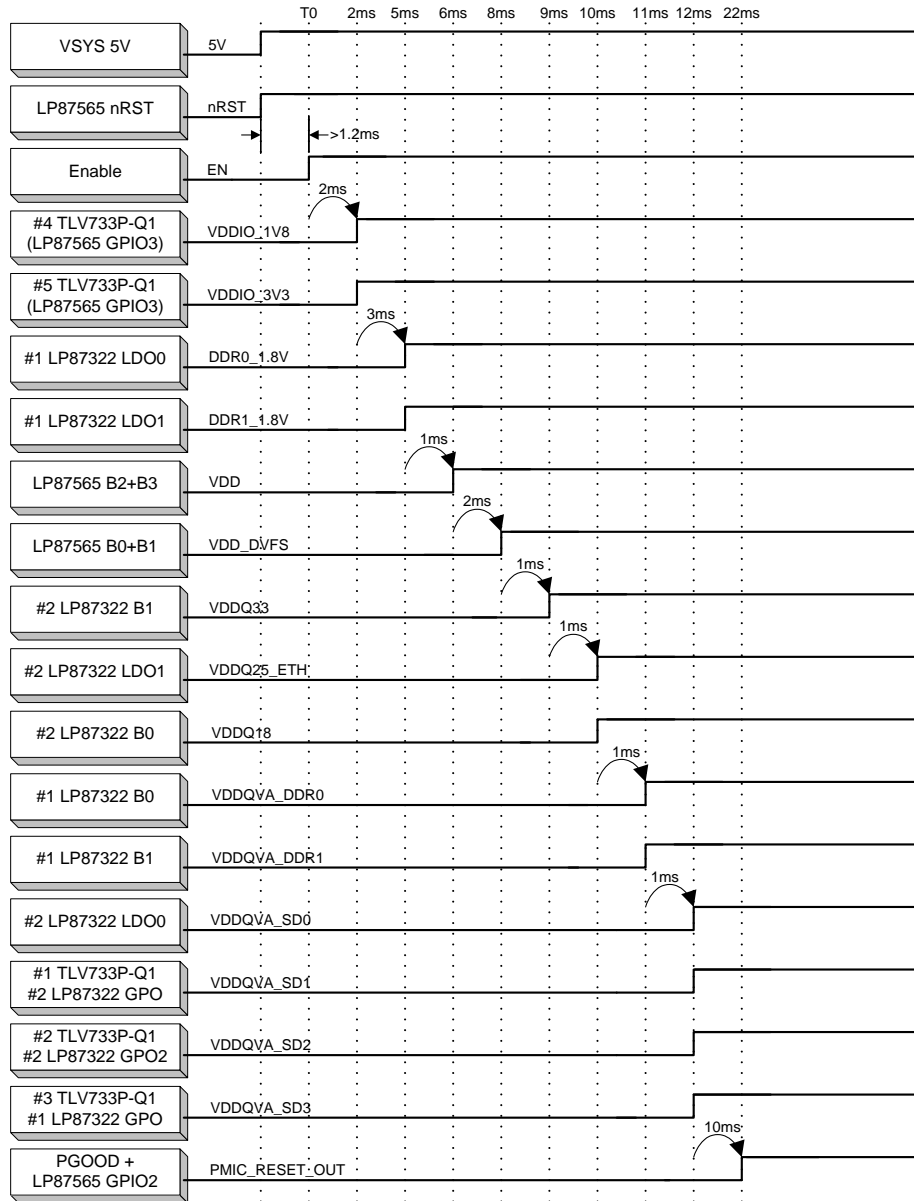


Figure 2. R-Car M3-W Power Startup Timing Diagram

3.2 Shutdown

Figure 3 shows an example of shutdown timing of the power rails and corresponding signals.

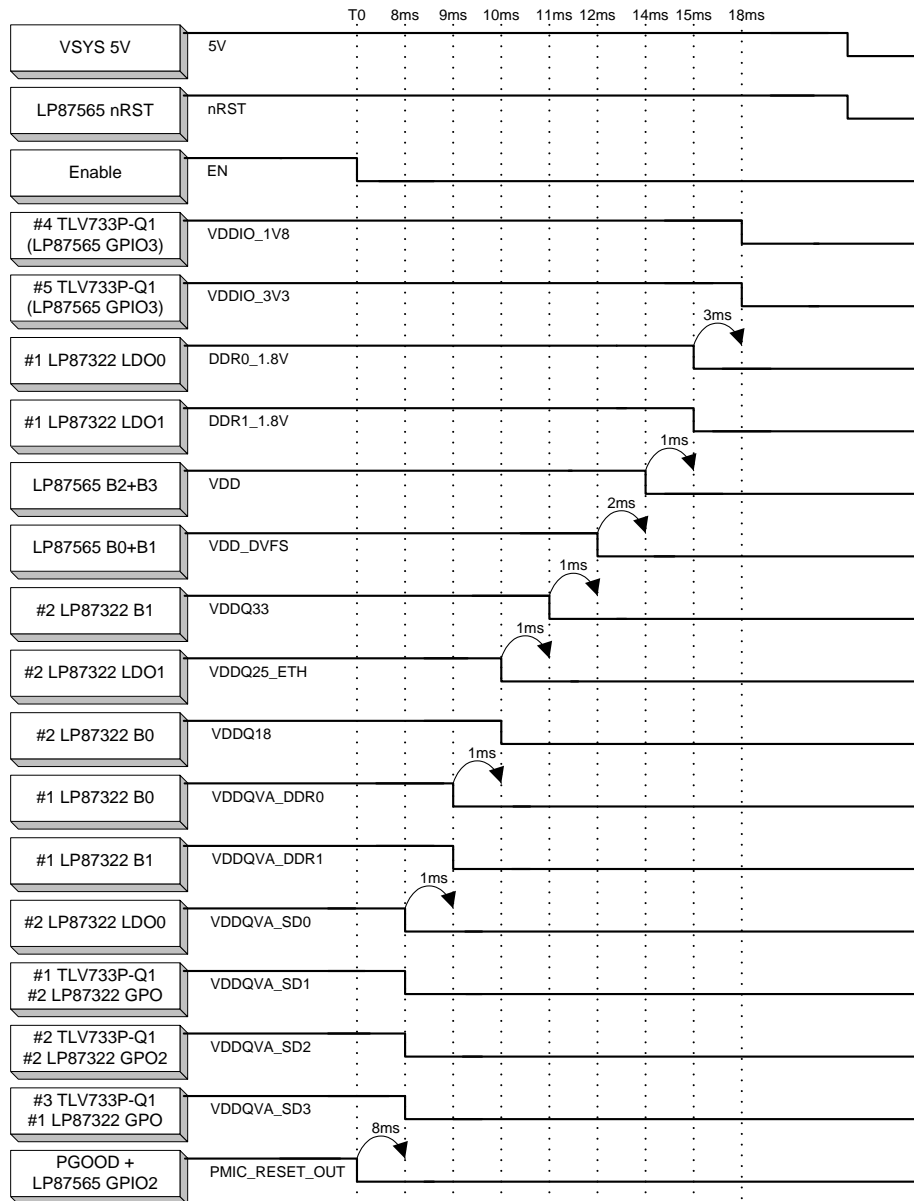


Figure 3. Shutdown Timing Diagram

4 Schematic

Figure 4 through Figure 8 show the R-Car M3-W power tree schematic with critical components. Snubbers are needed for LP87565-Q1 when input voltage of the system is >4 V, otherwise they are optional.

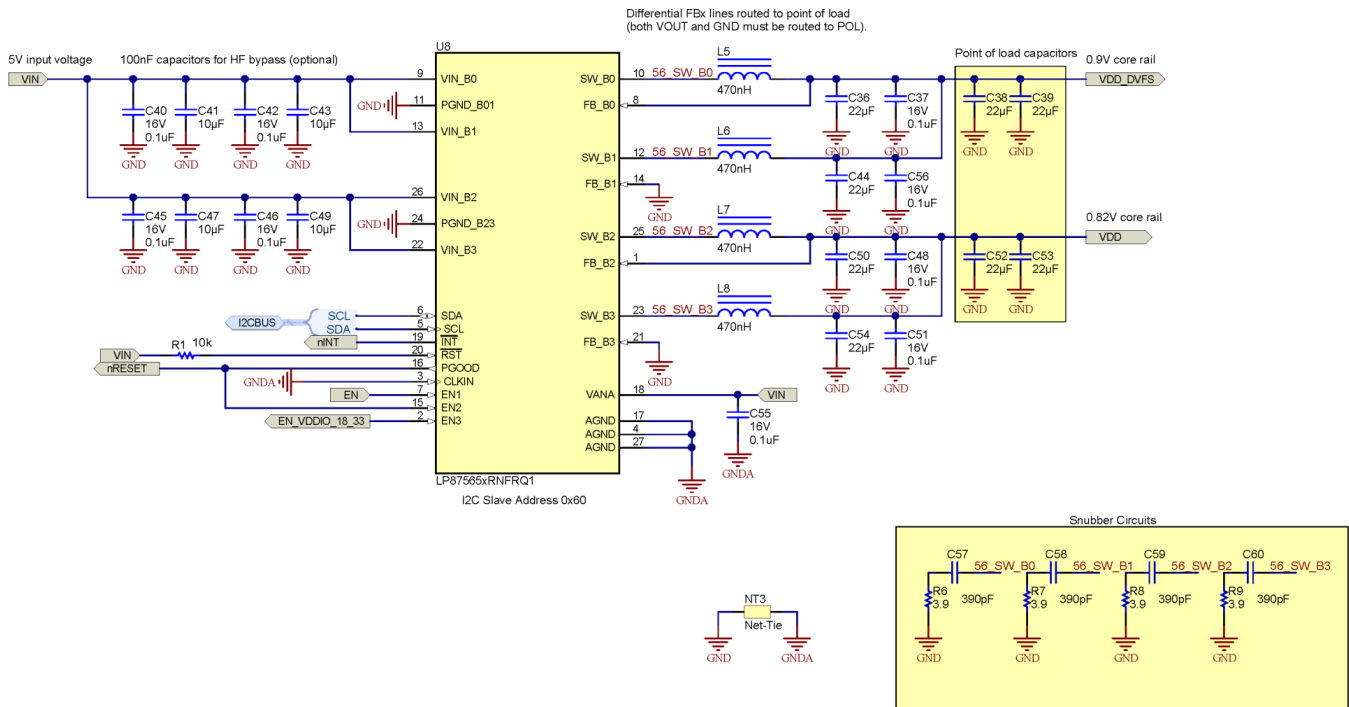


Figure 4. LP87565x Schematic

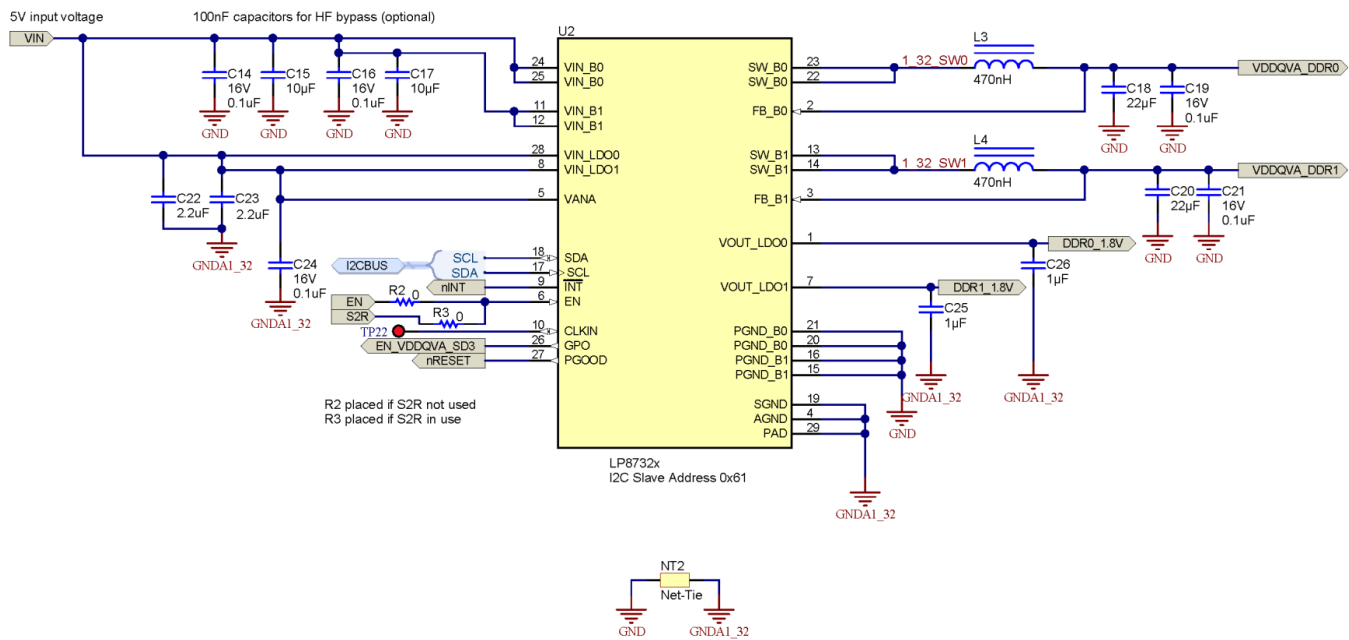


Figure 5. LP8732x-1 Schematic

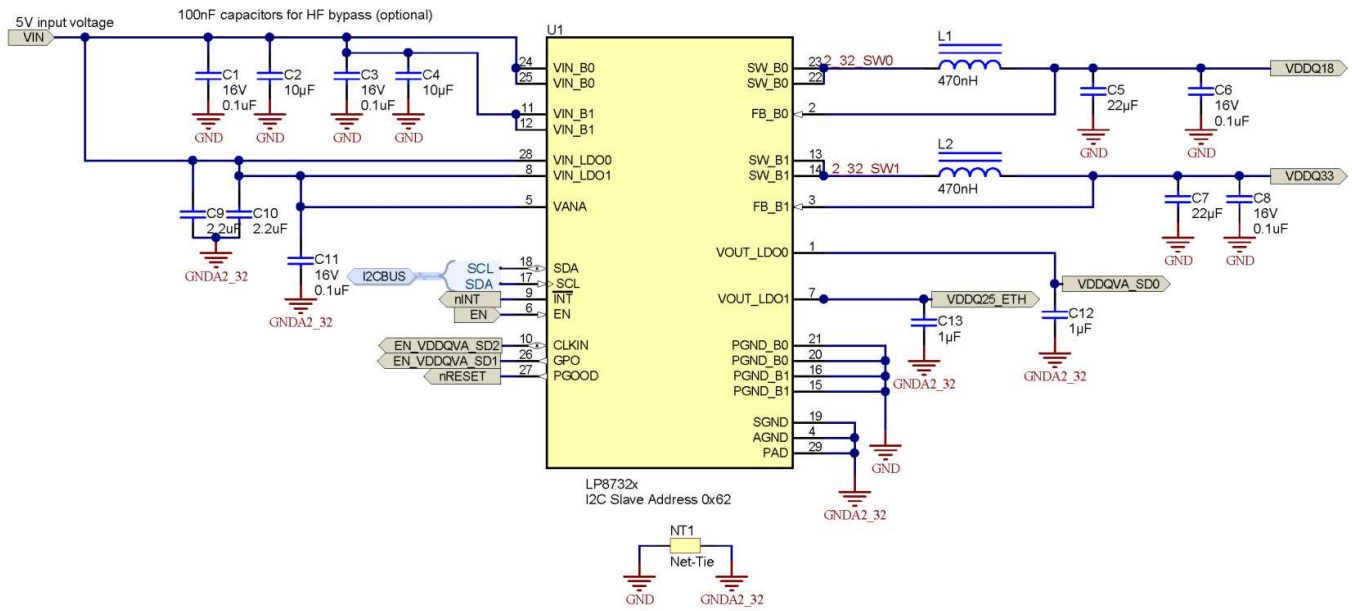


Figure 6. LP8732x-2 Schematic

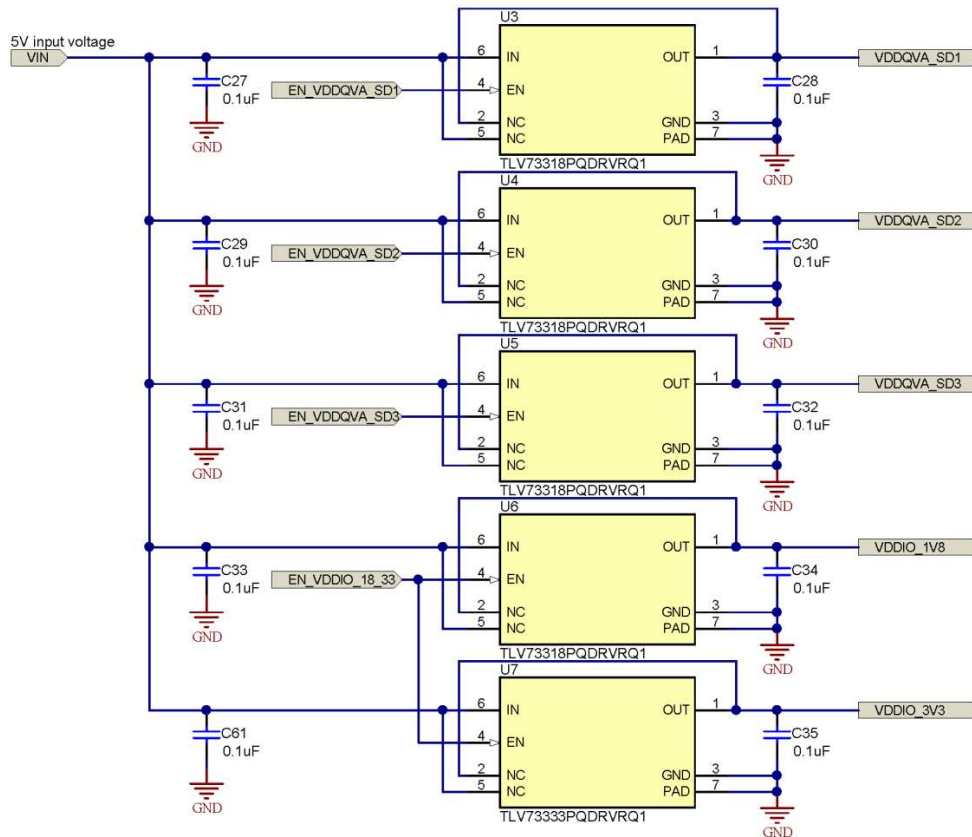


Figure 7. TLV733P-Q1LDO Schematic

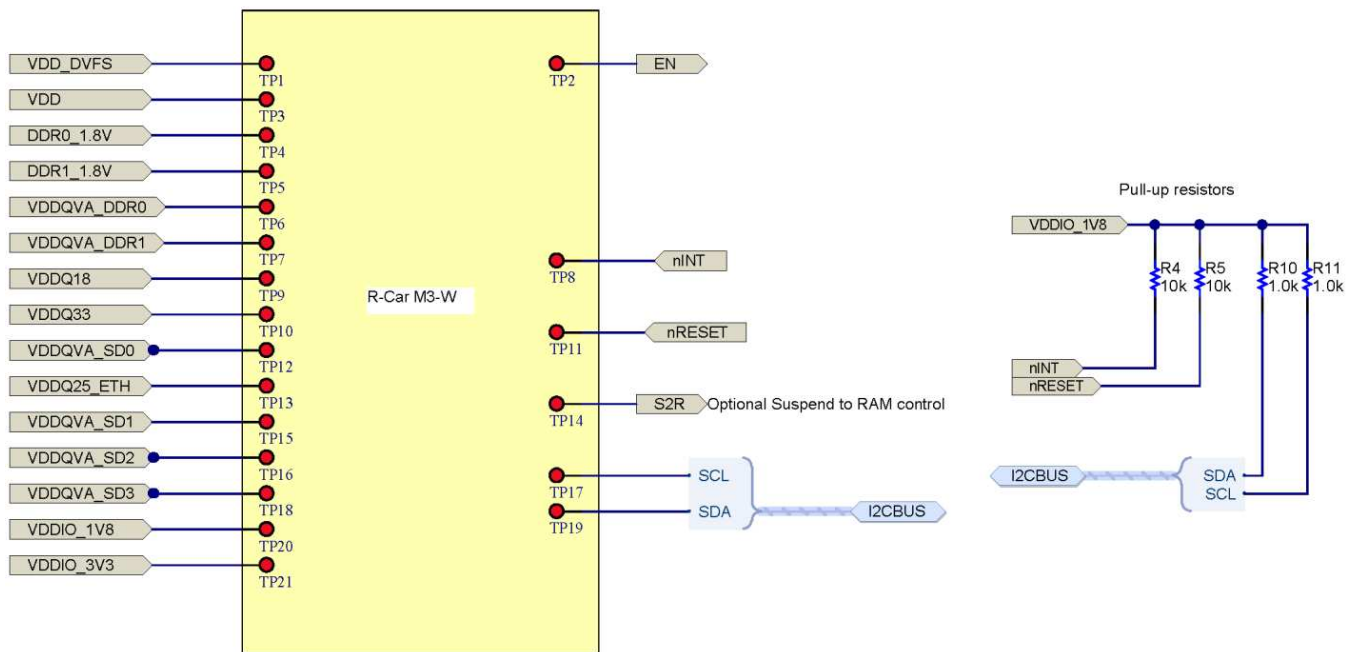


Figure 8. Connections to R-Car M3-W

5 Software Drivers

This solution supports DVFS for core rail through I²C bus and also DDR backup feature (I²C configurable).

Linux drivers for the LP875x and LP873x are available in public git repository. These can be used to help integrate the LP875x / LP873x control to system software:

LP8756x

- <https://github.com/torvalds/linux/blob/master/drivers/mfd/lp87565.c>
- <https://github.com/torvalds/linux/blob/master/drivers/regulator/lp87565-regulator.c>
- <https://github.com/torvalds/linux/blob/master/drivers/gpio/gpio-lp87565.c>

LP873x

- <https://github.com/torvalds/linux/blob/master/drivers/mfd/lp873x.c>
- <https://github.com/torvalds/linux/blob/master/drivers/regulator/lp873x-regulator.c>
- <https://github.com/torvalds/linux/blob/master/drivers/gpio/gpio-lp873x.c>

Note: Every header file is in the “include” folder starting from the root directory. So once in “include folder”, you can navigate to the relevant header file. For example, here is the LP87565.h file:

<https://github.com/torvalds/linux/blob/master/include/linux/mfd/lp87565.h>.

6 Recommended External Components

Table 2 shows the recommended external components to use in this solution with the LP87565-Q1, LP8732-Q1, and TLV733P-Q1s. It also shows the total solution size, including the PMIC device and the external components.

Table 2. Bill of Materials

COUNT	VENDOR	PART NUMBER	SYSTEM COMPONENT	W (mm)	L (mm)	H (mm)	UNIT AREA ⁽¹⁾	TOTAL BOARD AREA ⁽¹⁾
1	TI	LP87565x-Q1	Configurable 4-phase PMIC	4.00	4.50	0.90	27.50	27.50
4	Murata	DFE252012P D-R47M	LP87565x Inductor 0.47 μ H, I _{max} 4.0 A, R _{dc} typ 21m Ω	2.50	2.00	1.20	10.50	42.00
4	Murata	GCM21BR71 A106KE22	LP87565x SMPS Input Capacitor 10 μ F, 10 V, 10%	2.00	1.25	1.25	6.75	27.00
4	Murata	GCM31CR71 A226KE02	LP87565x SMPS Output Capacitor 22 μ F, 10 V, 10%	3.20	1.60	1.80	10.92	43.68
13	Murata	GRT31CC80J 476KE13	Point of load Capacitor 47 μ F, 6.3 V, 10%.	3.20	1.60	1.60	10.92	141.96
1	Murata	GCM155R71C 104KA55D	LP87565x Input Capacitor 0.1 μ F, 16 V, 10%	1.00	0.50	0.50	3.00	3.00
4	TDK	CGA2B2C0G1 H391J050BA	LP87565x Snubber capacitor, 390 pF	1.00	0.50	0.50	3.00	12.00
4	Vishay-Dale	CRCW04023 R90JNED	LP87565x Snubber resistor, 3R9	1.00	0.50	0.50	3.00	12.00
2	TI	LP8732x-Q1	Configurable PMIC with 2 Bucks and 2 LDOs	5.00	5.00	0.90	36.00	72.00
4	Murata	DFE252012P D-R47M	LP87322x Inductor 0.47 μ H, I _{max} 4.0 A, R _{dc} typ 21m Ω	2.50	2.00	1.20	10.50	42.00
4	Murata	GCM21BR71 A106KE22	LP87322x SMPS Input Capacitor 10 μ F, 10 V, 10%	2.00	1.25	1.25	6.75	27.00
4	Murata	GCM31CR71 A226KE02	LP87322x SMPS Output Capacitor 22 μ F, 10 V, 10%	3.20	1.60	1.60	10.92	43.68
4	Murata	GCM188R70J 225KE22	LP87322x LDO Input Capacitor 2.2 μ F, 6.3 V, 10%	1.60	0.80	0.90	4.68	18.72
4	Murata	GCM188R71C 105KA64	LP87322x LDO Output Capacitor 1.0 μ F, 16 V, 10%	1.60	0.80	0.90	4.68	18.72
1	Murata	GCM155R71C 104KA55D	LP87322x Input Capacitor 0.1 μ F, 16 V, 10%	1.00	0.50	0.50	3.00	3.00
4	TI	TLV733P-Q1	TLV733P-Q1 Low Dropout Regulator	2.00	2.00	0.80	9.00	45.00
4	Murata	GCM155R71C 104KA55D	TLV733P-Q1 Input Capacitor 0.1 μ F, 16 V, 10%	1.00	0.50	0.50	3.00	15.00
4	Murata	GCM155R71C 104KA55D	TLV733P-Q1 Output Capacitor 0.1 μ F, 16 V, 10%	1.00	0.50	0.50	3.00	15.00
TOTAL								609.26 mm ²
Routing area calculated with 0.3 routing factor								261.11 mm ²
Total area								870.37 mm ²

⁽¹⁾ Assuming 1 mm keep-out around each component, and multiplying by component count

7 Measurements

Test data can be found in the Application Curves section of the [LP8756x-Q1 16A Buck Converter With Integrated Switches Data Sheet](#) and the [LP8732xx-Q1 Dual High-Current Buck Converter and Dual Linear Regulator Data Sheet](#).

Additional bench test data for efficiency in specific conditions for this power tree can be seen in this section.

Measurements were taken on the LP87565Q1EVM and LP8732Q1EVM with default components.

 


Figure 9. LP87565-Q1 Efficiency with $V_{in} = 5\text{ V}$, 25°C , $V_{out} = 0.85\text{ V}$

 


Figure 10. LP8732-Q1 Efficiency with $V_{in} = 5\text{ V}$, 25°C

8 Conclusion

With this presented solution with the LP87565-Q1 and LP8732-Q1 PMICs, it is possible to meet power requirements for R-Car M3 application processor while maintaining good efficiency. Sequencing is handled in PMICs and only one EN signal is needed from the controller. Solution is compact due to minimum number of external components. I²C control allows DVFS for core rail and DDR Backup features.

9 References

See these references for additional information:

1. Texas Instruments, [LP8756x-Q1 16A Buck Converter With Integrated Switches Data Sheet](#) (SNVSB22)
2. Texas Instruments, [LP8732xx-Q1 Dual High-Current Buck Converter and Dual Linear Regulator Data Sheet](#) (SNVSB63)
3. Texas Instruments, [LP8756x-Q1 Configuration Guide](#) (SNVU590)
4. Texas Instruments, [LP8733-Q1 and LP8732-Q1 Configuration Guide](#) (SNVU582)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated