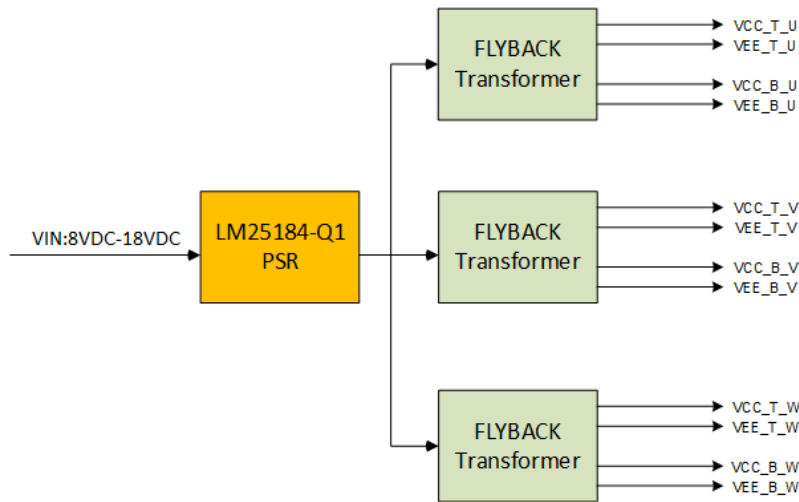


Multi-Output Primary-Side Regulated Flyback Reference Design for Automotive IGBT Gate Driver Applications




1 Description


This reference design provides an isolated power supply for an automotive IGBT gate driver. The primary-side regulated flyback controller LM25184-Q1 is used to avoid an optocoupler and improve system reliability. Three transformers are used to achieve multiple outputs and facilitate flexible system layout.



Block Diagram

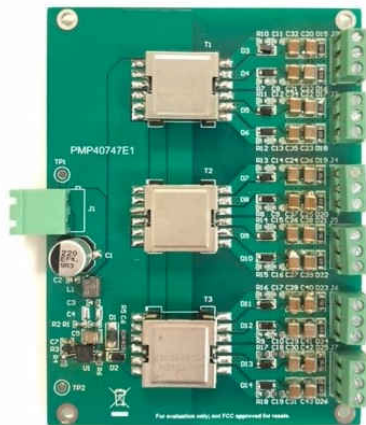

Top Photo

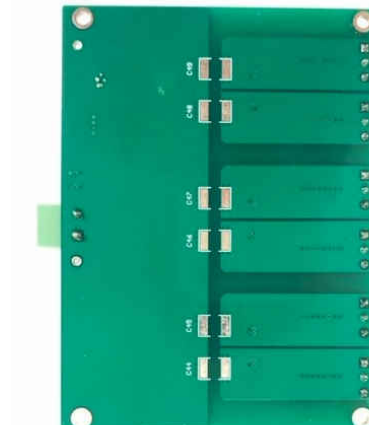

Bottom Photo

2 Test Prerequisites

2.1 Voltage and Current Requirements

Table 2-1. Voltage and Current Requirements

Parameter	Specifications
Input Voltage	8 V–18 VDC (12 V nom)
Output Voltage	6 × (+15 V, –8.2 V)
Maximum Output Current	100 mA

2.2 Required Equipment

- Multimeter (voltage): Fluke 287C
- Multimeter (current): Fluke 287C
- DC Source: Chroma 62012P-100-50
- E-Load: Chroma 63105A module
- Oscilloscope: Tektronix DPO3054
- Electrical Thermography: Fluke TiS55

2.3 Considerations

For better cross regulation, all outputs have a fixed 1-mA dummy load. According to inverter gate driver applications, only 3 × (+15 V, –8.2 V) outputs are loaded, and the other 3 × (+15 V, –8.2 V) outputs work at no load (with 1-mA dummy load).

2.4 Dimensions

The board dimensions are 100 mm (length) × 75 mm (width) × 10mm (height).

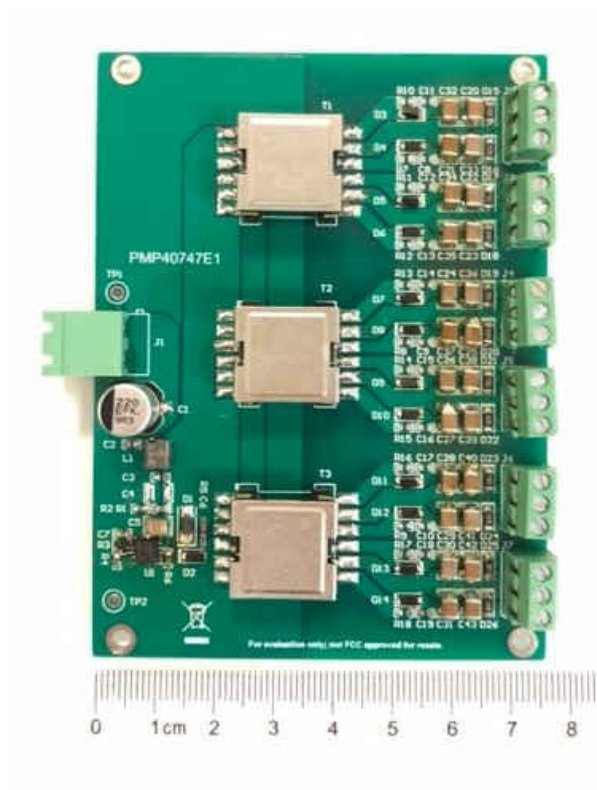


Figure 2-1. Dimension

3 Testing and Results

3.1 Efficiency Graphs

The following figure shows the efficiency graph.

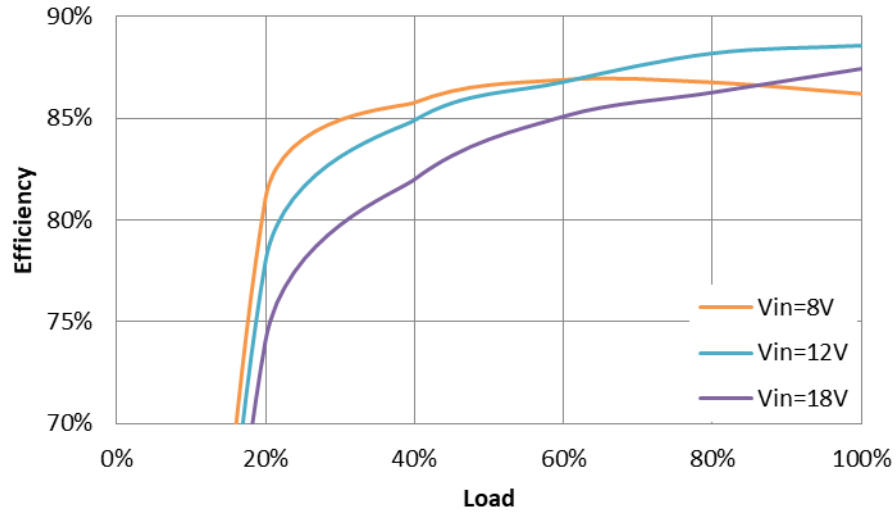


Figure 3-1. Efficiency Graph

3.2 Cross Regulation

The cross regulation is tested by adjusting the six loaded outputs (VCC_T and VEE_B), and the other six outputs (VCC_B and VEE_T) work at no load.

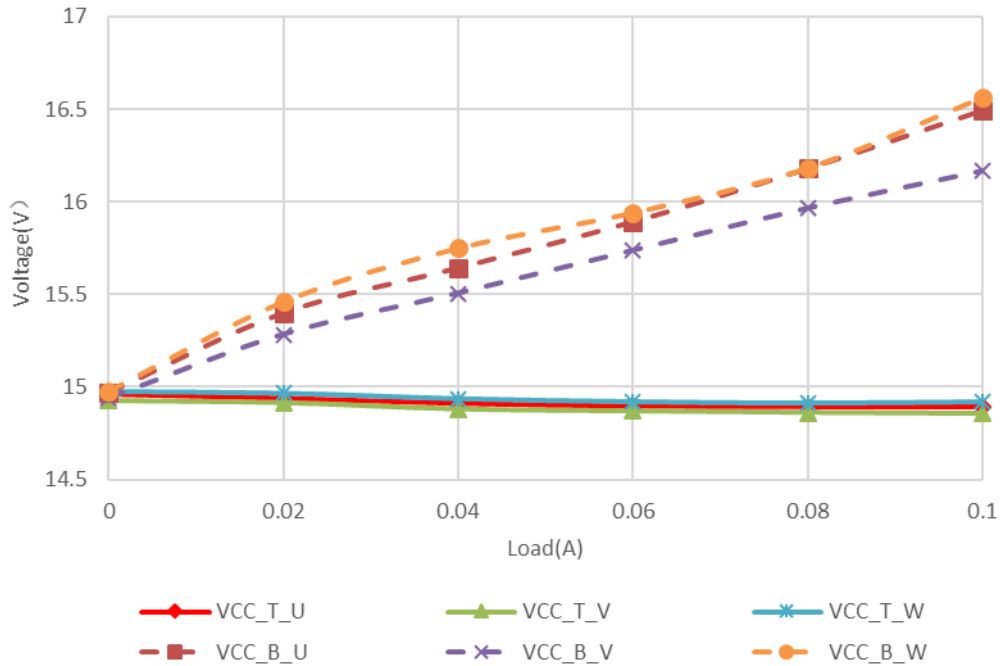


Figure 3-2. Cross Regulation of VCC_T and VCC_B

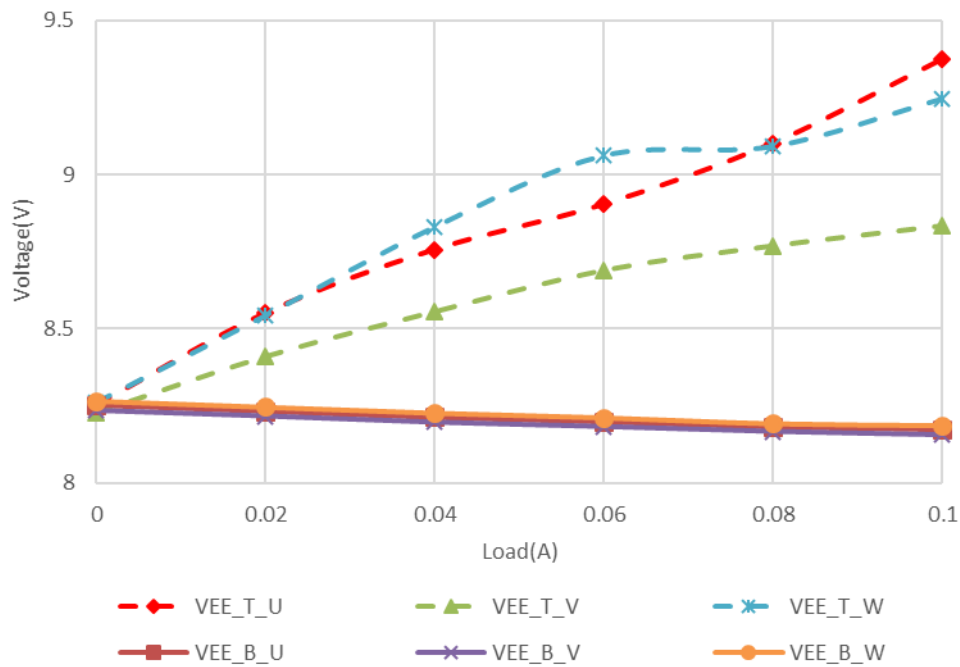


Figure 3-3. Cross Regulation of VEE_T and VEE_B

3.3 Thermal Images

The following photos show the thermal images.

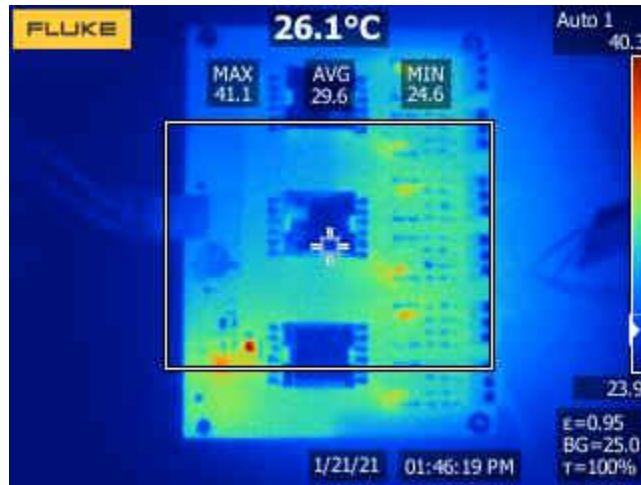


Figure 3-4. Thermal Top

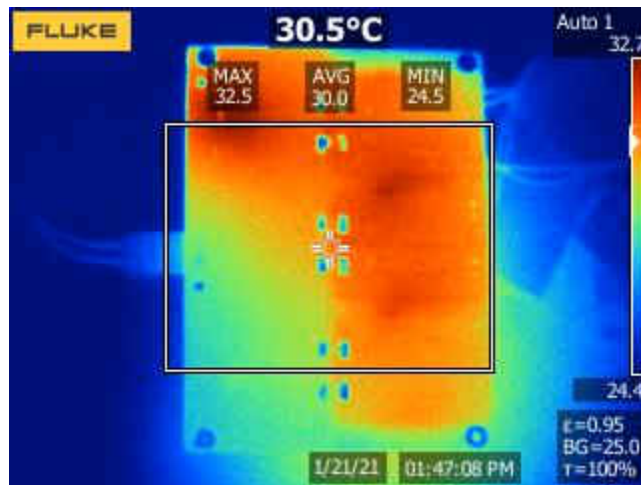


Figure 3-5. Thermal Bottom

4 Waveforms

4.1 Switching

Switching behavior is shown in the following figures.

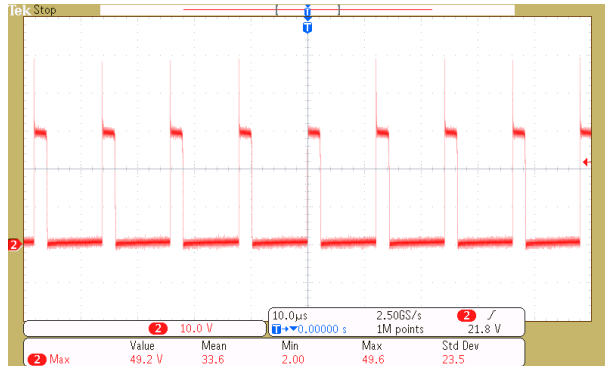


Figure 4-1. 8-V Input, no Load

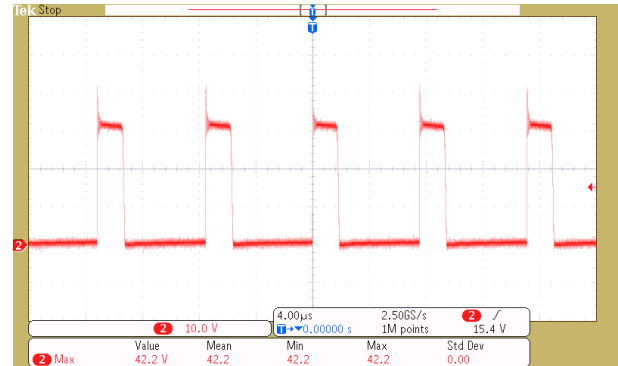


Figure 4-2. 8-V Input, VCC_T and VEE_B With 100-mA Load

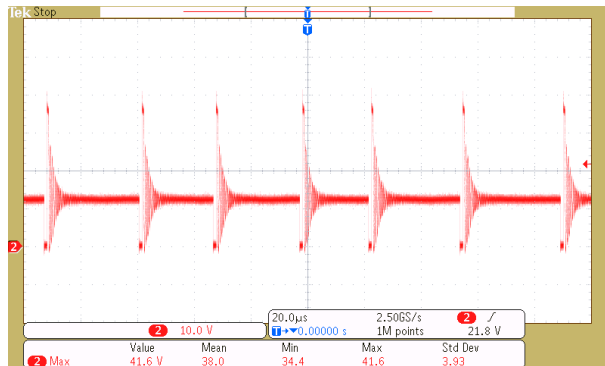


Figure 4-3. 12-V Input, no Load

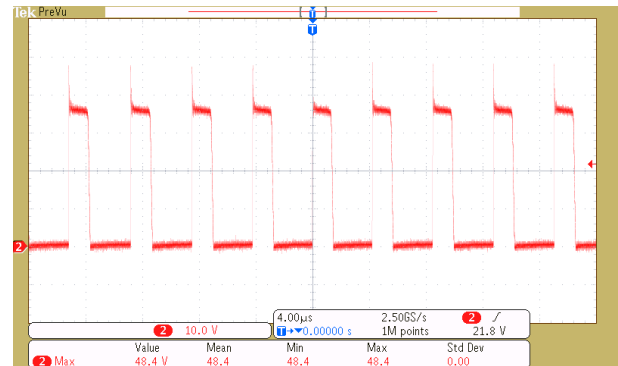


Figure 4-4. 12-V Input, VCC_T and VEE_B With 100-mA Load

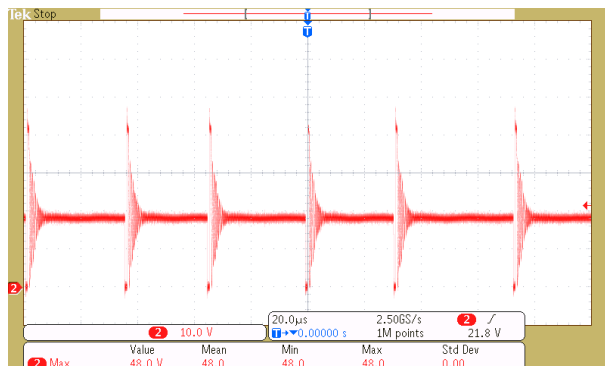


Figure 4-5. 18-V Input, no Load


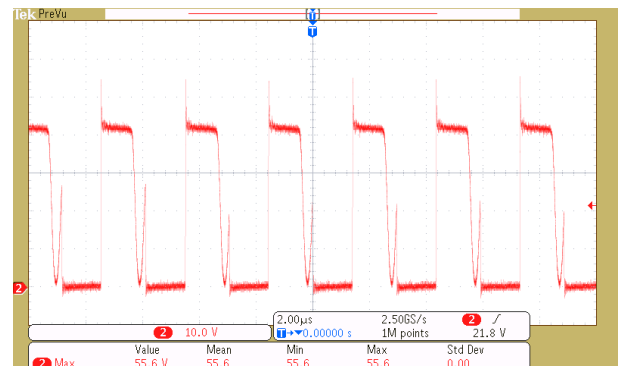


Figure 4-6. 18-V Input, VCC_T and VEE_B With 100-mA Load


4.2 Output Voltage Ripple

Output voltage ripple is shown in the following figures. The input voltage is set to 12 V.

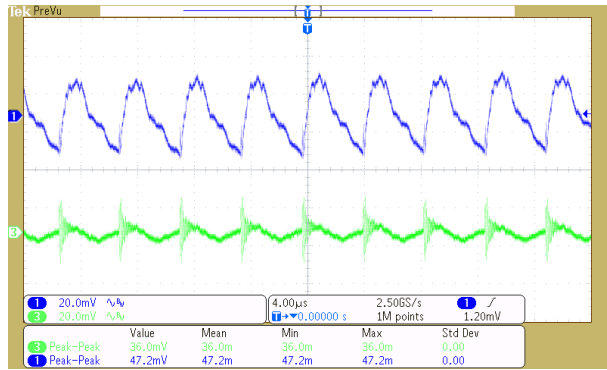


CH2: V_{CC_T_U} CH3: V_{VEE_T_U}

Figure 4-7. 12-V Input, V_{CC_T_U} at Full Load, V_{VEE_T_U} at No Load

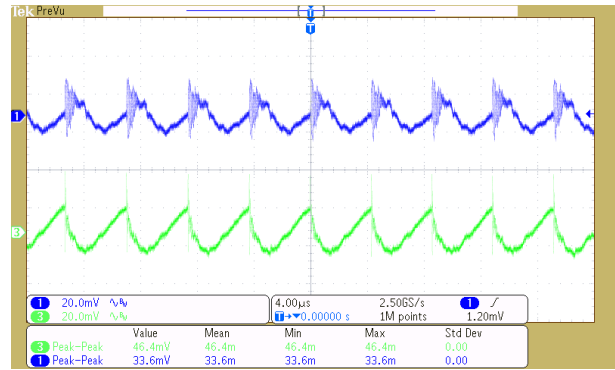


CH2: V_{CC_B_U} CH3: V_{VEE_B_U}

Figure 4-8. 12-V Input, V_{CC_B_U} at no Load, V_{VEE_B_U} at Full Load

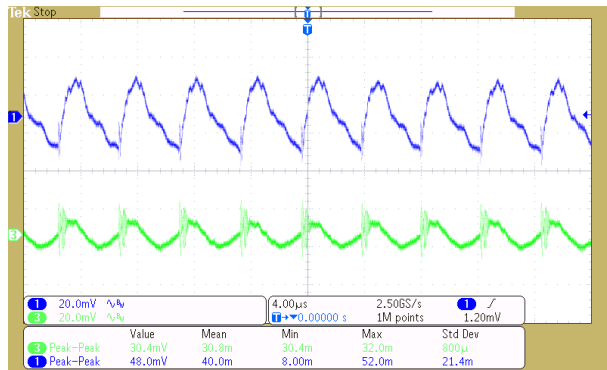


CH2: V_{CC_T_V} CH3: V_{VEE_T_V}

Figure 4-9. 12-V Input, V_{CC_T_V} at Full Load, V_{VEE_T_V} at No Load

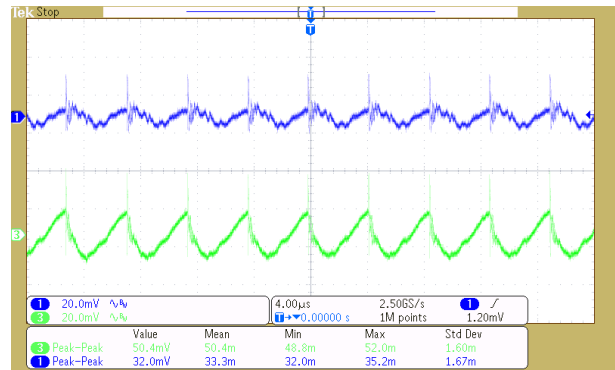


CH2: V_{CC_B_V} CH3: V_{VEE_B_V}

Figure 4-10. 12-V Input, V_{CC_B_V} at No Load, V_{VEE_B_V} at Full Load

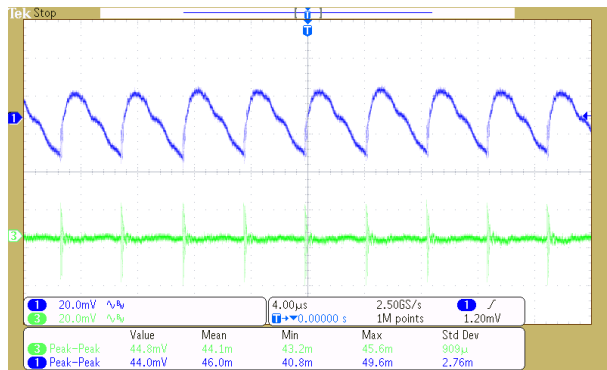

CH2: V_{CC_T_W} CH3: V_{VEE_T_W}

Figure 4-11. 12-V Input, V_{CC_T_W} at Full Load, V_{VEE_T_W} at No Load

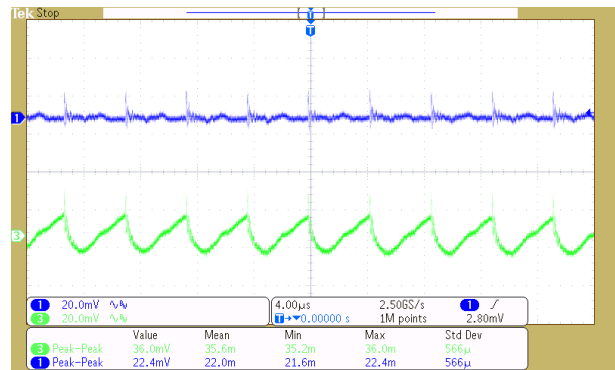


CH2: V_{CC_B_W} CH3: V_{VEE_B_W}


Figure 4-12. 12-V Input, V_{CC_B_W} at No Load, V_{VEE_B_W} at Full Load

4.3 Load Transients

Load transient response is shown in the following figures. The slew rate is set to 0.1 A/ μ s.

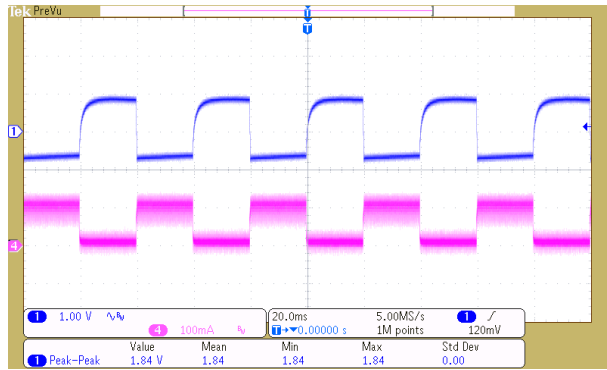

CH1: V_{VCC_T_U} CH4: I_{vcc_T_U}
Figure 4-13. 12-V Input, VCC Output 0 A → 0.1 A

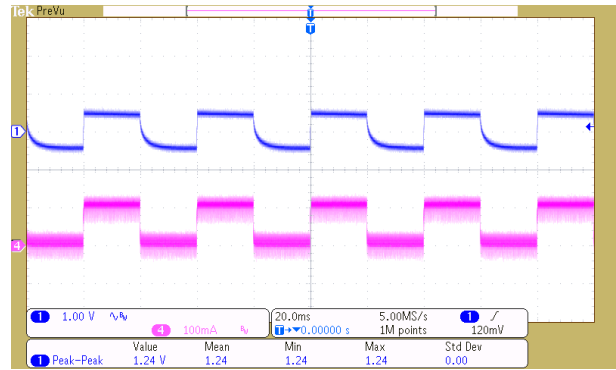

CH1: V_{VEE_B_U} CH4: I_{VEE_B_U}
Figure 4-14. 12-V Input, VEE Output 0.1 A → 0 A

4.4 Start-up Sequence

Start-up shows the start-up behavior.

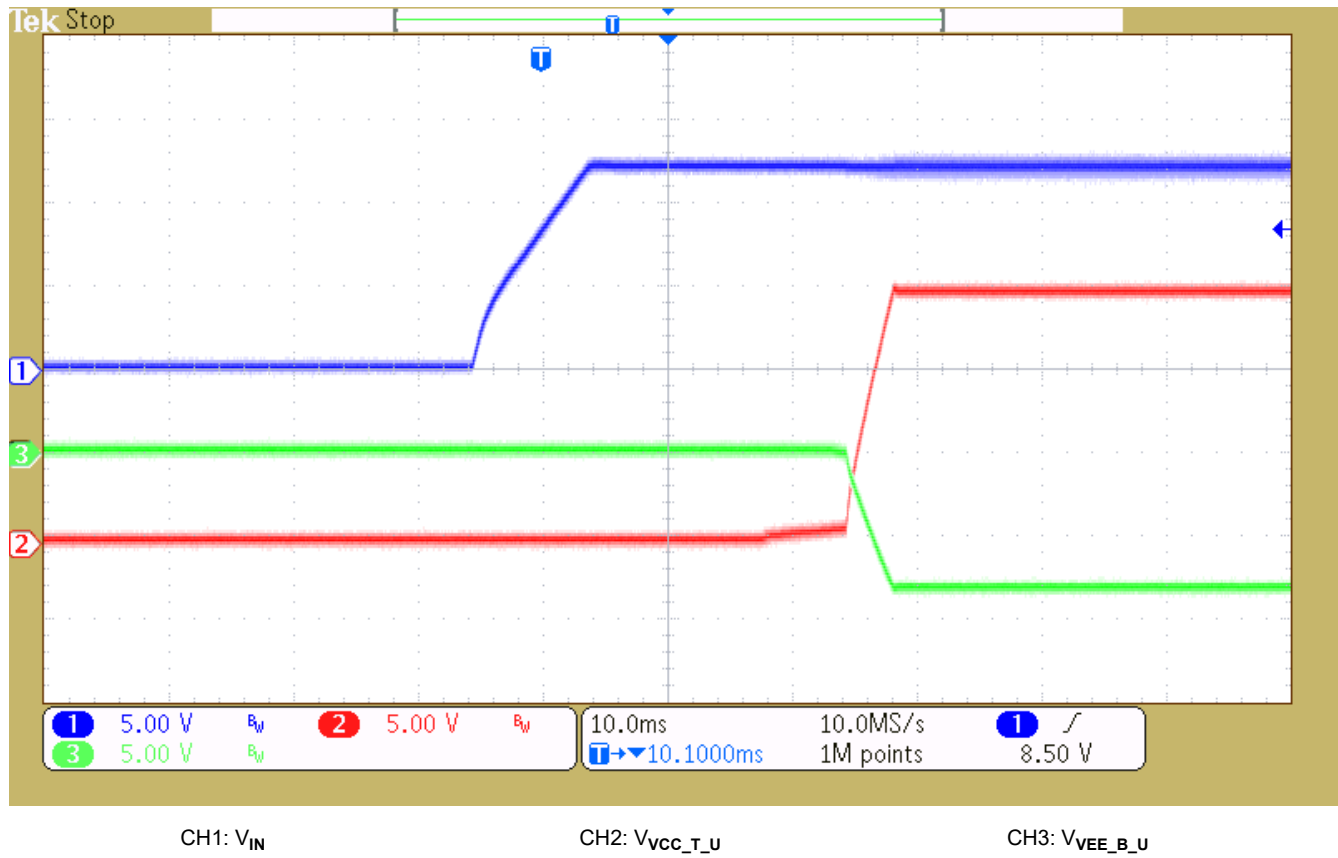


Figure 4-15. Start-up

4.5 Undervoltage Protection

Undervoltage shows the undervoltage protection.

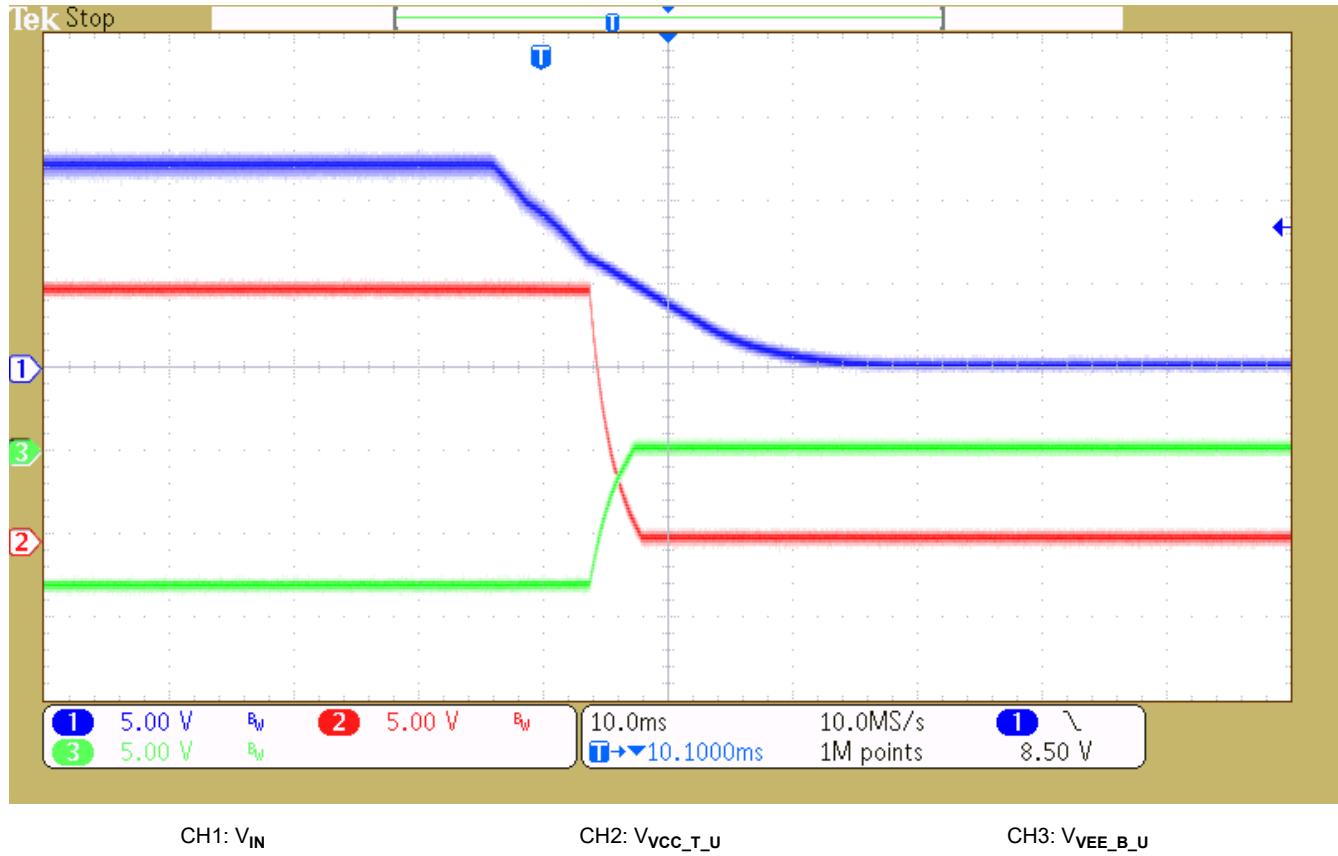


Figure 4-16. Undervoltage

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated