

TI Designs – Precision: Verified Design

Capacitive Load Drive Solution using an Isolation Resistor



TI Designs – Precision

TI Designs – Precision are analog solutions created by TI's analog experts. Verified Designs offer the theory, component selection, simulation, complete PCB schematic & layout, bill of materials, and measured performance of useful circuits. Circuit modifications that help to meet alternate design goals are also discussed.

Design Resources

- [Design Archive](#)
- [TINA-TI™](#)
- [OPA192](#)
- [OPA140](#)
- [OPA170](#)
- [OPA171](#)
- [OPA172](#)
- [OPA180](#)
- [OPA209](#)
- [OPA320](#)
- [OPA340](#)
- [OPA350](#)
- [OPA365](#)



- All Design files
- SPICE Simulator
- Product Folder
- Product Folder
- Product Folder
- Product Folder
- Product Folder
- Product Folder
- Product Folder
- Product Folder
- Product Folder
- Product Folder
- Product Folder

Circuit Description

This design can be used to drive capacitive loads such as cable shields, reference buffers, MOSFET gates, and diodes. The circuit uses an isolation resistor (R_{iso}) to stabilize the output of an op amp. R_{iso} modifies the open loop gain of the system to ensure the circuit has sufficient phase margin. The OPA192 is highlighted because it can drive large capacitive loads using a small isolation resistor.



  [Ask The Analog Experts](#)
[WEBENCH® Design Center](#)
[TI Designs – Precision Library](#)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

TINA-TI is a trademark of Texas Instruments
 WEBENCH is a registered trademark of Texas Instruments

1 Design Summary

The design requirements are as follows:

- Supply Voltage: 30 V (+/-15 V)
- Capacitive Loads: 100 pF, 1000 pF, 0.01 μ F, 0.1 μ F, 1 μ F

The design goals and performance are summarized in Table 1. Figure 1 depicts the transient response of the OPA192 driving a 0.1 μ F load capacitance (C_{load}) using an isolation resistor (R_{iso}) of 6.2 Ω to obtain a percent overshoot (PO) of 23.1% and corresponding phase margin (PM) of 45.2°.

Table 1: Comparison of Design Goals and Measured Performance

	Capacitive Load	100 pF		1000 pF		0.01 μ F		0.1 μ F		1 μ F	
	Phase Margin Goal	45°	60°	45°	60°	45°	60°	45°	60°	45°	60°
OPA192	Riso (Ω)	47.0	360.0	24.0	100.0	20.0	51.0	6.2	15.8	2.0	4.7
	Measured Overshoot (%)	23.2	10.4	22.5	9.0	22.1	8.7	23.1	8.6	21.0	8.6
	Calculated PM	45.1°	58.1°	45.8°	59.7°	46.1°	60.1°	45.2°	60.2°	47.2°	60.2°

 


Figure 1: OPA192 Transient Response, $C_{load}=0.1 \mu$ F, $R_{iso}=6.2 \Omega$, PM=45.2°

2 Theory of Operation

Figure 2 depicts a unity-gain buffer driving a capacitive load. Equation (1) shows the transfer function for the circuit in Figure 2. Not depicted in Figure 2 is the open-loop output impedance of the op amp, R_o .

 


Figure 2: Unity-Gain Buffer with R_{iso} Stability Compensation

$$T(s) = \frac{1 + C_{load} \times R_{iso} \times s}{1 + (R_o + R_{iso}) \times C_{load} \times s} \quad (1)$$

The transfer function in Equation (1) has a pole and a zero. The frequency of the pole (f_p) is determined by $(R_o + R_{iso})$ and C_{load} . R_{iso} and C_{load} determine the frequency of the zero (f_z). A stable system is obtained by selecting R_{iso} such that the rate of closure (ROC) between the open loop gain (A_{ol}) and $1/\beta$ is 20 dB/decade. [1] Figure 3 depicts the concept. For further information, please consult References [1]-[3]. Note that the $1/\beta$ curve for a unity-gain buffer is 0 dB.

 


Figure 3: Unity-gain Amplifier with R_{iso} Compensation

ROC stability analysis is typically simulated. The validity of the analysis depends on multiple factors, especially the accurate modeling of the open-loop output impedance of the amplifier (R_o).

In addition to simulating the ROC, a robust stability analysis includes a measurement of the circuit's percent overshoot and ac gain peaking using a function generator, oscilloscope, and gain/phase analyzer. Phase margin is then calculated from these measurements. Table 2 shows the percent overshoot and ac gain peaking that correspond to phase margins of 45° and 60°. The theory behind these values is in Appendix B and the corresponding software simulation is located in the design file.

Table 2: Phase Margin vs. Overshoot and AC Gain Peaking

Phase Margin	Overshoot (%)	AC Gain Peaking (dB)
45°	23.3	2.35
60°	8.8	0.28

3 Component Selection

This Precision Design intends to provide R_{iso} values for a variety of op amps and capacitive loads. Table 3 lists the op amps and some of their characteristics. The OPA192 is featured because of its ability to drive large capacitive loads using a small isolation resistor.

Table 3: Selected Op Amps

Op Amp	V _{supply} Range (V)	I _q @ 25°C (max, mA)	V _{os} @ 25°C (max, μV)	V _{os} Drift (max, μV/C)	V _n @ 25°C (typ, nV/√Hz)	BW (typ, MHz)	Notes
OPA192	4.5 – 36	1.2	25	0.5	5.5	10	RRI/O, Low Noise
OPA140	4.5 – 36	2	120	1	5.1	11	RRO, JFET input, Low Noise
OPA170	2.7 – 36	0.145	1800	2	19	1.2	RRO, Value Line
OPA171	2.7 – 36	0.595	1800	2	14	3.0	RRO, Value Line
OPA172	4.5 – 36	1.8	1000	1.5	7	10	RRO, Low Power
OPA180	4.0 – 36	0.525	75	0.35	10	2	RRO, Low Noise, Zero-Drift
OPA209	4.5 – 36	2.5	150	3	2.2	18	RRO, Low Noise
OPA320	1.8 – 5.5	1.6	150	5	8.5	20	RRI/O, Low Noise
OPA340	2.7 – 5.5	0.95	500	2.5 (typ)	25	5.5	RRI/O, SR=6V/μs
OPA350	2.7 – 5.5	7.5	500	4 (typ)	15	38	RRI/O, SR=22V/μs
OPA365	2.2 – 5.5	5	200	1 (typ)	13	50	RRI/O, SR=25V/μs

4 Simulation

ROC analysis (or ac analysis) is used to determine an approximate value of R_{iso} . Figure 4 depicts the TINA-TI™ schematic topology used in ROC analysis. This topology is thoroughly discussed in [2].

 


Figure 4: TINA-TI™ Circuit used for ROC Stability Analysis

Figure 5 shows the corresponding ROC analysis of V_{oa} in Figure 4 with SW1 closed. Note that the ROC is ~ 40 dB/decade and the phase margin is only 8.4° . While a phase margin of 8.4° is technically stable, it is not a robust design. Variation in process and environmental conditions may reduce the phase margin such that the system becomes unstable. Therefore, a phase margin of at least 45° is recommended.

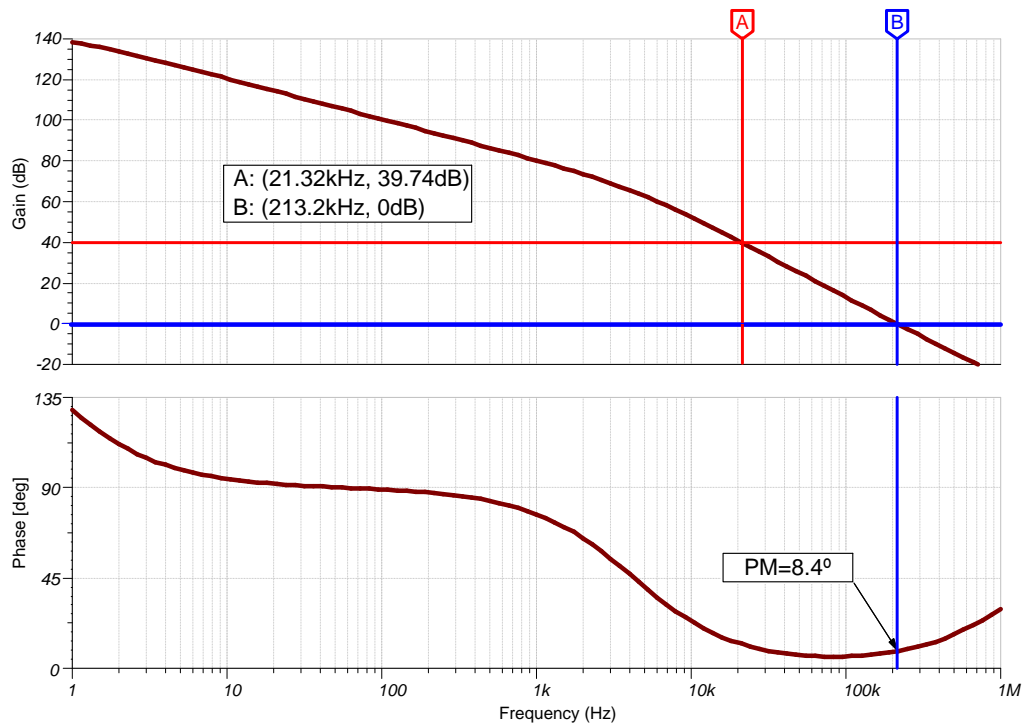


Figure 5: OPA192, $C_{load}=0.1 \mu\text{F}$, $R_{iso}=0.0 \Omega$, $PM=8.4^\circ$

Placing a zero at the frequency where $A_{ol}=20$ dB, as shown in Figure 6, adds $\sim 90^\circ$ of phase margin. [3] Further analysis will refine the location of the zero to reduce the value of R_{iso} while maintaining a stable system.

 


Figure 6: Frequency of Zero for Increased Phase Margin

R_{iso} is calculated as shown in Equation (2).

$$R_{iso} = \frac{1}{2 \times \pi \times f_z \times C_{load}} = \frac{1}{2 \times \pi \times 67.04\text{kHz} \times 0.1\mu\text{F}} = 23.74\Omega \quad (2)$$

Setting R_{iso} in Figure 4 to 23.7 Ω (nearest 1% standard value) and opening SW1 yields the ROC analysis shown in Figure 7. Notice the ROC and phase margin indicate a stable system.

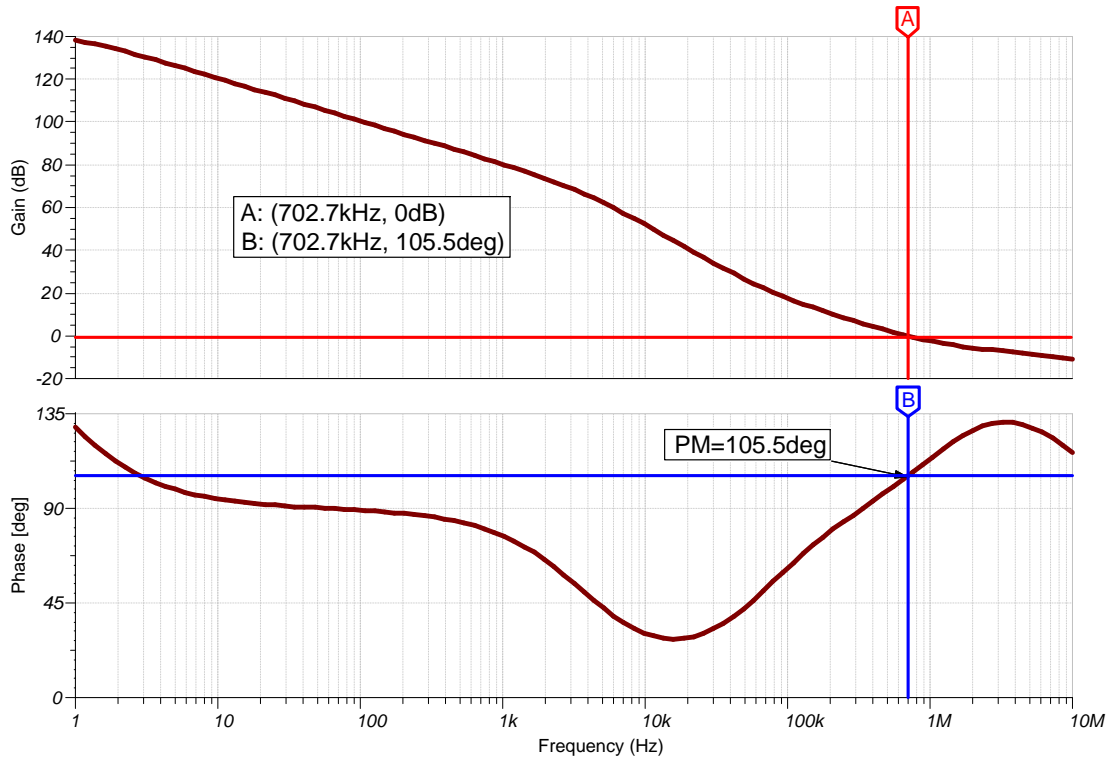


Figure 7: OPA192, $C_{load}=0.1 \mu\text{F}$, $R_{iso}=23.7 \Omega$, $PM=105.5^\circ$

One drawback to stabilizing capacitive loads using an isolation resistor is dc accuracy. [2] If the op amp is required to supply significant current, a voltage drop will develop across R_{iso} . Therefore it is recommended to minimize R_{iso} to increase dc accuracy.

However, reducing R_{iso} will also reduce phase margin. 45° and 60° of phase margin are commonly used in practical designs. [1]

The values of R_{iso} that correspond to phase margins of $\sim 45^\circ$ and $\sim 60^\circ$ were determined empirically and are depicted in Figure 8 and Figure 9, respectively.

 


Figure 8: OPA192, $C_{load}=0.1 \mu F$, $R_{iso}=4.87 \Omega$, $PM=44.7^\circ$

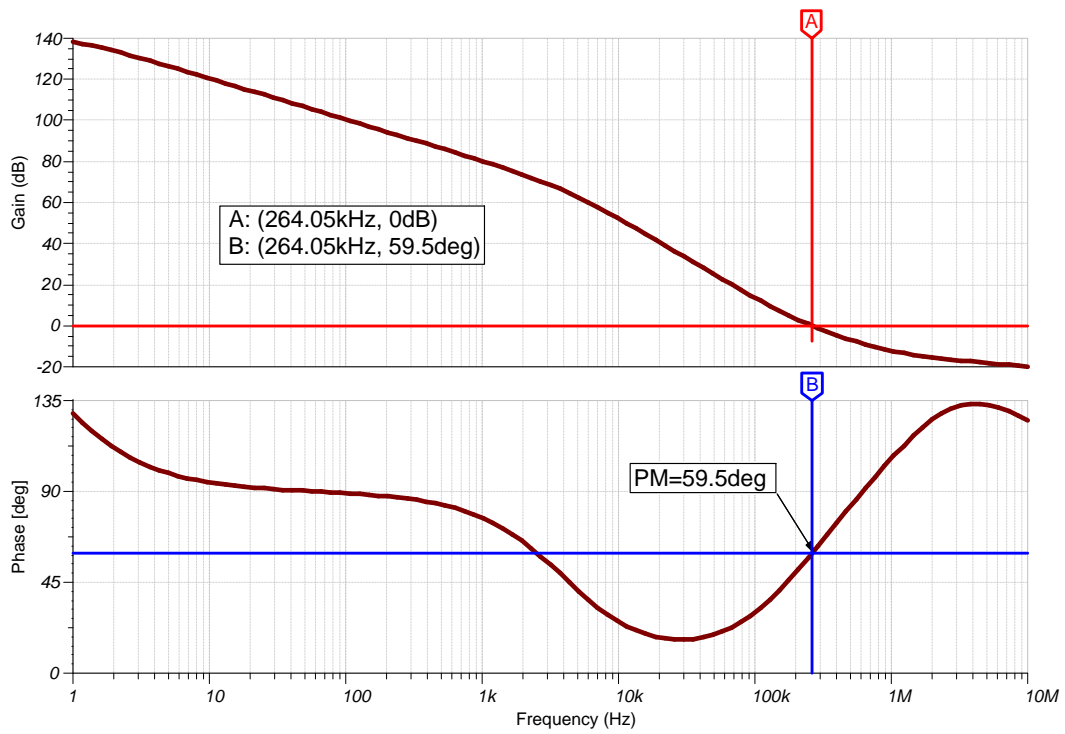


Figure 9: OPA192, $C_{load}=0.1 \mu F$, $R_{iso}=7.15 \Omega$, $PM=59.5^\circ$

Component tolerance also affects the phase margin of the system. The simulation in Figure 10 shows a reduction in phase margin of 1.3° given R_{iso} and C_{load} tolerances of 1% and 5%, respectively. Appendix D contains additional simulations of component tolerance on phase margin.

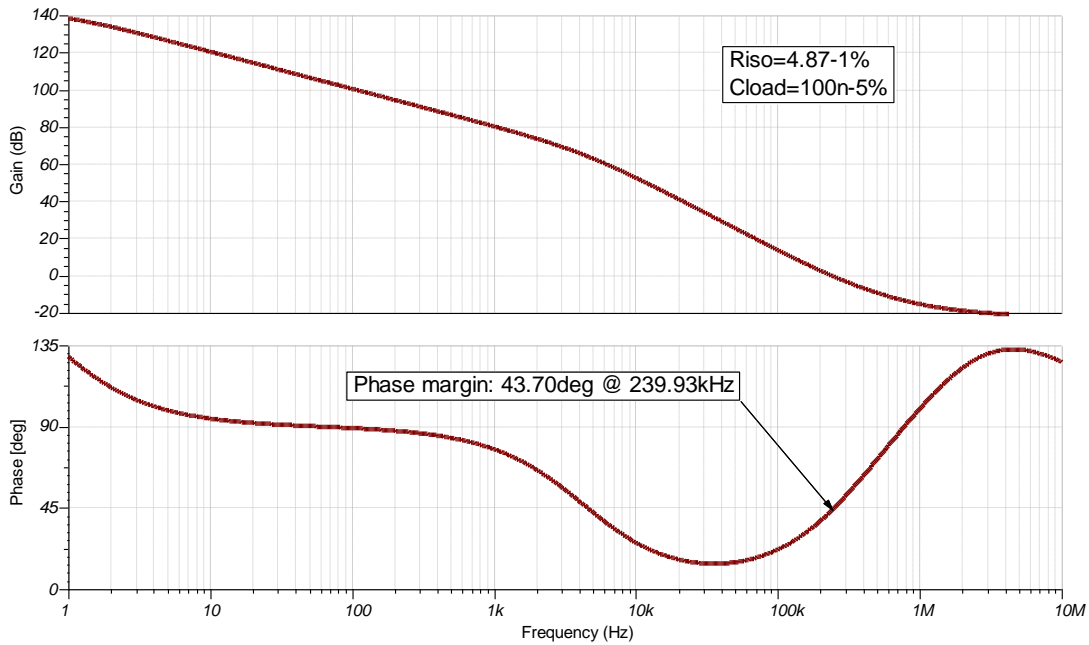


Figure 10: OPA192, $C_{load}=100 \text{ nF}-5\%$, $R_{iso}=4.87 \Omega-1\%$, $PM=43.7^\circ$

5 PCB Design

The PCB schematic and bill of materials can be found in Appendix A.

5.1 PCB Layout

The PCB shown in Figure 11 is composed of two layers with signals and power routed on the top layer. The remainder of the top layer was poured with ground copper and stitched to a solid ground plane on the bottom layer. The bottom layer is a solid ground plane to ensure a low impedance path for return currents. General guidelines for PCB layout were followed. For example, input signal trace lengths were kept to a minimum and decoupling capacitors were placed close to the power pins of the device.

 


Figure 11: PCB Layout

6 Verification & Measured Performance

6.1 Transient Response

Figure 12 shows the transient response to a 10 mVpp step input where $C_{load}=0.1 \mu F$ and $R_{iso}=4.87 \Omega$. The overshoot measured at V_{opa} is 29.62%, which corresponds to a phase margin of 39.4° . The equations in Appendix B were used to calculate phase margin given percent overshoot.

 


Figure 12: OPA192, $C_{load}=0.1 \mu F$, $R_{iso}=4.87 \Omega$, $PM=39.4^\circ$

Many factors can cause this discrepancy, including passive element tolerances, A_{oi} and R_o variation due to process shifts, and measurement/PCB non-idealities.

To achieve a phase margin of $\sim 45^\circ$, R_{iso} was increased to 6.2Ω . The resulting transient response is shown in Figure 13.

 


Figure 13: OPA192, $C_{load}=0.1 \mu F$, $R_{iso}=6.2 \Omega$, $PM=45.2^\circ$

For some scenarios (e.g. large capacitive loads), the magnitude of the input stimulus was reduced until the output response had a waveform similar to Figure 13. For more information, please refer to [4].

6.2 AC Response

Figure 14 depicts the ac response of the OPA192 when $C_{load}=0.1 \mu F$ and $R_{iso}=6.2 \Omega$. The ac gain peaking is 2.5 dB, which corresponds to a phase margin of 44.2° . These results correlate with the phase margin reported in Figure 8.

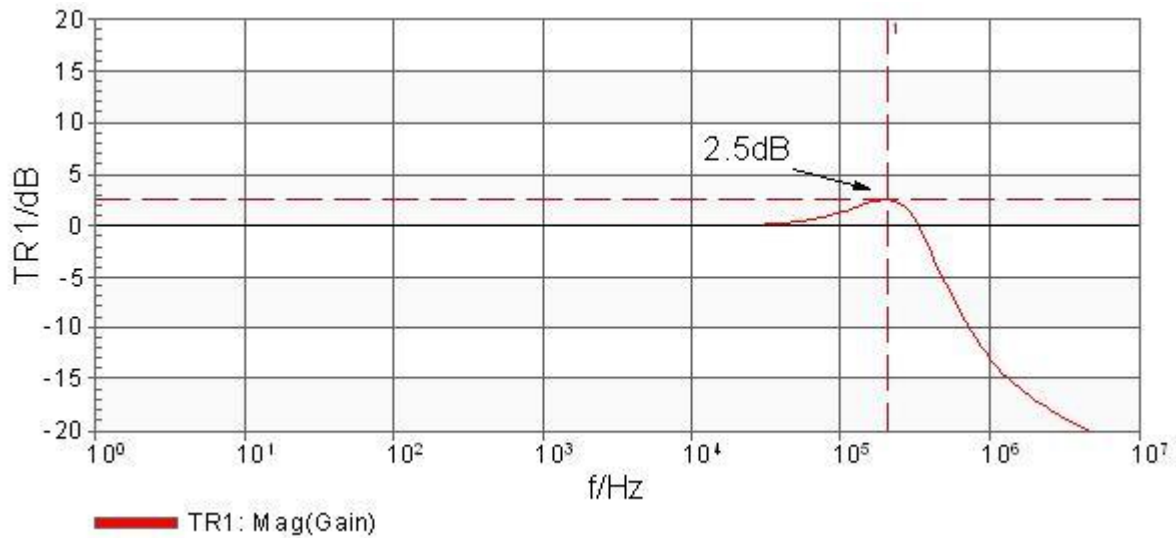


Figure 14: OPA192, $C_{load}=0.1 \mu F$, $R_{iso}=6.2 \Omega$, $PM=44.2^\circ$

6.3 R_{iso} vs. C_{load}

Using the described methodology, the values of R_{iso} that yield phase margins of 45° and 60° for various capacitive loads were determined. The results are shown in Figure 15.

 


Figure 15: OPA192, R_{iso} vs. C_{load}

Additional R_{iso} vs. C_{load} graphs for various op amps can be found in Appendix C.

It is sometimes desirable to know the phase margin for a capacitive load without R_{iso} compensation. Figure 16 depicts the phase margin for a variety of capacitive loads where $R_{iso}=0\ \Omega$. Note that the OPA192 can deliver reasonable PM for larger capacitive loads than most op amps.

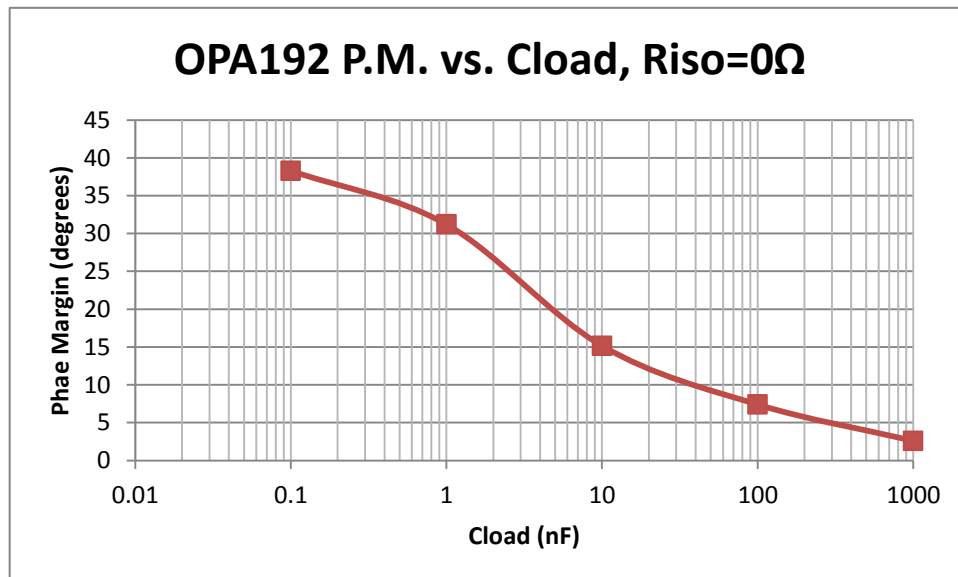


Figure 16: OPA192, PM vs. C_{load} , $R_{iso}=0\ \Omega$

7 Modifications

As mentioned earlier, one drawback to R_{iso} compensation is dc accuracy. One alternative is ' R_{iso} with dual feedback' compensation, as shown in Figure 17. This technique has an additional feedback path that corrects for the voltage drop across R_{iso} . The design of this compensation technique is discussed in references [1]-[3].

 


Figure 17: R_{iso} with Dual Feedback

8 About the Authors

Pete Semig is an Analog Applications Engineer in the Precision Linear group at Texas Instruments. He supports Texas Instruments' difference amplifiers & instrumentation amplifiers. Prior to joining Texas Instruments in 2007, he earned his B.S.E.E. and M.S.E.E. from Michigan State University in 1998 & 2001, respectively. From 2001-2007 he was a faculty member in Michigan State University's Department of Electrical & Computer Engineering where he taught a variety of courses and laboratories.

Timothy Claycomb was an intern for the Precision Linear group at Texas Instruments. He currently is an undergraduate student pursuing a B.S. in Electrical Engineering at Michigan State University and will graduate in December of 2013.

9 Acknowledgements & References

The authors would like to acknowledge Collin Wells and Mike Mock for their technical contributions to this design.

1. S. Franco, *Design with Operational Amplifiers and Analog Integrated Circuits, 3rd Edition*. McGraw-Hill, 2002.
2. T. Green. (Accessed 2013, October 22). *Operational Amplifier Stability Parts 1-10*. Available: http://www.en-genius.net/site/zones/acquisitionZONE/technical_notes/acqt_092407
3. C. Wells, *Operational Amplifier Stability, Technology Day Presentation, 2012*.
4. C. Wells. (Accessed 2013, December 2). *Transient Stability Testing: Watch Your Step*. Available: http://www.planetanalog.com/author.asp?section_id=3117&doc_id=560860

Appendix A.

A.1 Electrical Schematic

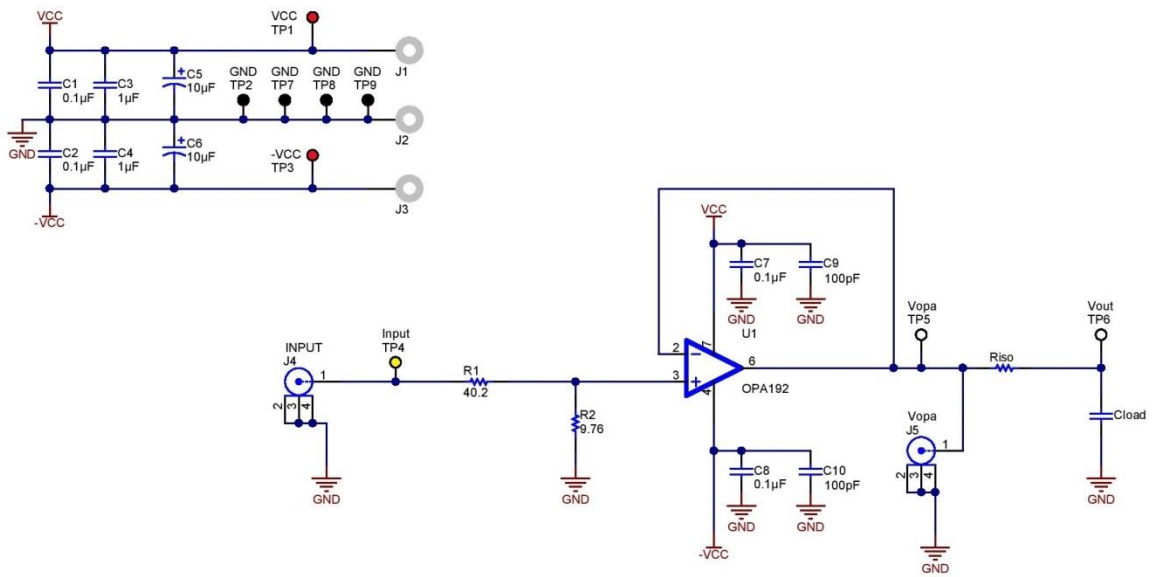


Figure A-1: Electrical Schematic

A.2 Bill of Materials

	QTY	Designator	Value	Description	Manufacturer	Manufacturer PN	DigiKey PN
1	1	U1	OPA192	Op Amp, SOIC-8	Texas Instruments		
2	1	Riso	Various	RES, 0.25W, 1206	Various	Various	Various
3	1	Cload	Various	CAP, CERM, 1206	Various	Various	Various
4	1	TP6	Vout	TEST POINT PC COMPACT .063"D WHT	Keystone	5007	5007K-ND
5	1	TP5	Vopa	TEST POINT PC COMPACT .063"D WHT	Keystone	5007	5007K-ND
6	1	TP4	Input	TEST POINT PC COMPACT .063"D YLW	Keystone	5009	5009K-ND
7	2	TP1, TP3	VCC, -VCC	TEST POINT PC COMPACT .063"D RED	Keystone	5005	5005K-ND
8	4	TP2, TP7, TP8, TP9	GND	TEST POINT PC COMPACT .063"D BLK	Keystone	5006	5006K-ND
9	1	R2	9.76	RES, 9.76 ohm, 1%, 0.25W, 1206	Vishay-Dale	CRCW12069R76FKEA	541-9.76FFCT-ND
10	1	R1	40.2	RES, 40.2 ohm, 1%, 0.25W, 1206	Vishay-Dale	CRCW120640R2FKEA	541-40.2FCT-ND
11	2	J4, J5	Input, Vopa	CONN BNC JACK R/A 50 OHM PCB	TE Connectivity	1-1337543-0	A97553-ND
12	3	J1, J2, J3	VCC, GND, -VCC	JACK NON-INSULATED .218"	Keystone	575-4	575-4K-ND
13	2	C9, C10	100pF	CAP, CERM, 100pF, 100V, +/-5%, COG/NPO, 1206	AVX	12061A101JAT2A	478-1444-1-ND
14	2	C5, C6	10uF	CAP, TA, 10uF, 25V, +/-10%, 0.5 ohm, SMD	AVX	TPSC106K025R0500	478-1762-1-ND
15	2	C3, C4	1uF	CAP, CERM, 1uF, 100V, +/-10%, X7R, 1206	MuRata	GRM31CR72A105KA01L	490-3909-1-ND
16	4	C1, C2, C7, C8	0.1uF	CAP, CERM, 0.1uF, 100V, +/-20%, X7R, 1206	AVX	12061C104MAT2A	478-3786-1-ND
17	4	U94, U95, U96, U97	N/A	MACHINE SCREW PAN PHILLIPS 4-40	B&F Fastener	PMSSS 440 0025 PH	H703-ND
18	4	U90, U91, U92, U93	N/A	STANDOFF HEX 4-40THR ALUM 1L"	Keystone	2205	2205K-ND

Figure A-2: Bill of Materials

Appendix B.

B.1 Percent Overshoot and AC Gain Peaking vs. Phase Margin

Percent overshoot and ac gain peaking are related to phase margin (ϕ_m) via damping ratio (ζ). Equation (3) and Figure 18 depict the relationship between ζ and phase margin.

$$\phi_m(\zeta) := \frac{180}{\pi} \operatorname{atan} \left[2 \cdot \zeta \cdot \left(\sqrt{\frac{1}{4 \cdot \zeta^4 + 1} - 2 \cdot \zeta^2} \right) \right] \quad (3)$$

where $\zeta := 0.0, 0.001 \dots 0.707$ (4)

 


Figure 18: Damping Ratio vs. Phase Margin

Percent overshoot and ac gain peaking relate to phase margin as shown by Equation(5), Equation (6), and Figure 19.

$$PO(\zeta) := 100 \cdot \exp\left(\frac{-1\pi \cdot \zeta}{\sqrt{1 - \zeta^2}}\right) \quad (5)$$

$$GP(\zeta) := 20 \cdot \log\left(2 \cdot \frac{Q(\zeta)^2}{\sqrt{4 \cdot Q(\zeta)^2 - 1}}\right) \quad (6)$$

where

$$Q(\zeta) := \frac{1}{2 \cdot \zeta} \quad (7)$$

 


Figure 19: PO and GP vs. Phase Margin

Calculate percent overshoot and ac gain peaking (in dB) for 45° of phase margin as follows:

Given $\zeta := 0$ (8)

$$\frac{180}{\pi} \operatorname{atan}\left[2 \cdot \zeta \cdot \left(\frac{1}{\sqrt{4 \cdot \zeta^4 + 1 - 2 \cdot \zeta^2}}\right)\right] = 45 \quad (9)$$

$$\zeta_{45} := \operatorname{Find}(\zeta) \quad \zeta_{45} = 0.42 \quad (10)$$

$$PO_{45} := 100 \cdot \exp\left(\frac{-\pi \cdot \zeta_{45}}{\sqrt{1 - \zeta_{45}^2}}\right) = 23.321 \quad (11)$$

$$GP_{45} := 20 \cdot \log\left(2 \cdot \frac{Q(\zeta_{45})^2}{\sqrt{4 \cdot Q(\zeta_{45})^2 - 1}}\right) = 2.35 \quad (12)$$

Repeat the calculations to determine percent overshoot and ac gain peaking for 60° of phase margin.

B.2 Phase Margin vs. Percent Overshoot

After measuring the percent overshoot of a transient analysis, Equations 13 to 15 can be used to calculate the corresponding phase margin.

$$\text{PO} := 23.32\% \quad (13)$$

$$\zeta := \frac{-\ln\left(\frac{\text{PO}}{100}\right)}{\sqrt{\pi^2 + \left(\ln\left(\frac{\text{PO}}{100}\right)\right)^2}} = 0.42 \quad (14)$$

$$\phi_{\text{PM}} := \frac{180}{\pi} \text{atan} \left[2 \cdot \zeta \cdot \left(\frac{1}{\sqrt{4 \cdot \zeta^4 + 1 - 2 \cdot \zeta^2}} \right) \right] = 45 \quad (15)$$

Appendix C.

All measured data values can be found in the design file archive. If no data points exist for 100pF scenario, the amplifier does not require an isolation resistor for stable operation. If no data points exist for 1μF scenario, the isolation resistor required for stable operation is less than 1 Ω.

C.1 OPA140

 


Figure 20: OPA140, R_{iso} vs. C_{load}

C.2 OPA170

 


Figure 21: OPA170, R_{iso} vs. C_{load}

C.3 OPA171

 


Figure 22: OPA171, R_{iso} vs. C_{load}

C.4 OPA172

 


Figure 23: OPA172, R_{iso} vs. C_{load}

C.5 OPA180

 


Figure 24: OPA180, R_{iso} vs. C_{load}

C.6 OPA209

 


Figure 25: OPA209, R_{iso} vs. C_{load}

C.7 OPA320

 


Figure 26: OPA320, R_{iso} vs. C_{load}

C.8 OPA340

 


Figure 27: OPA340, R_{iso} vs. C_{load}

C.9 OPA350

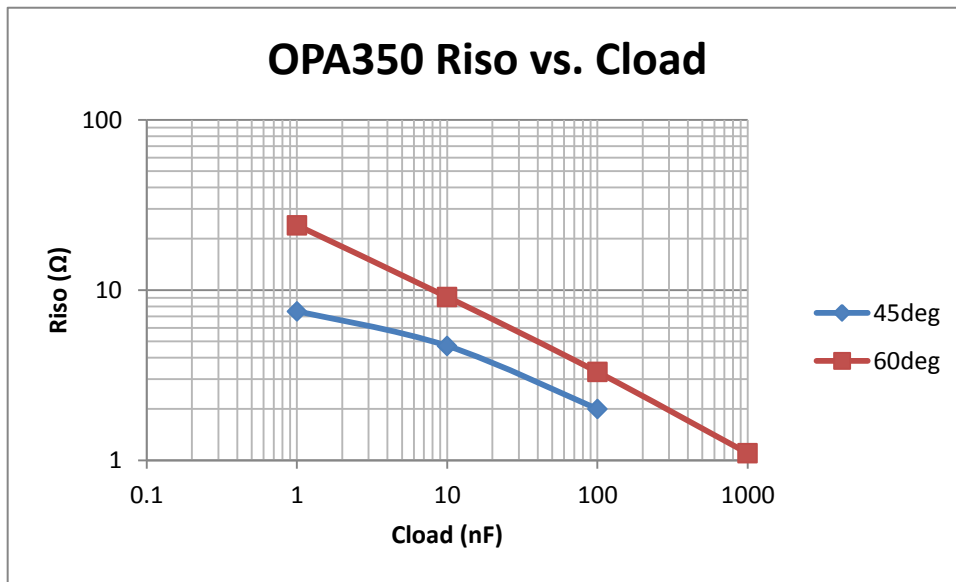


Figure 28: OPA350, R_{iso} vs. C_{load}

C.10 OPA365

 


Figure 29: OPA365, R_{iso} vs. C_{load}

Appendix D. Passive Tolerance Simulations

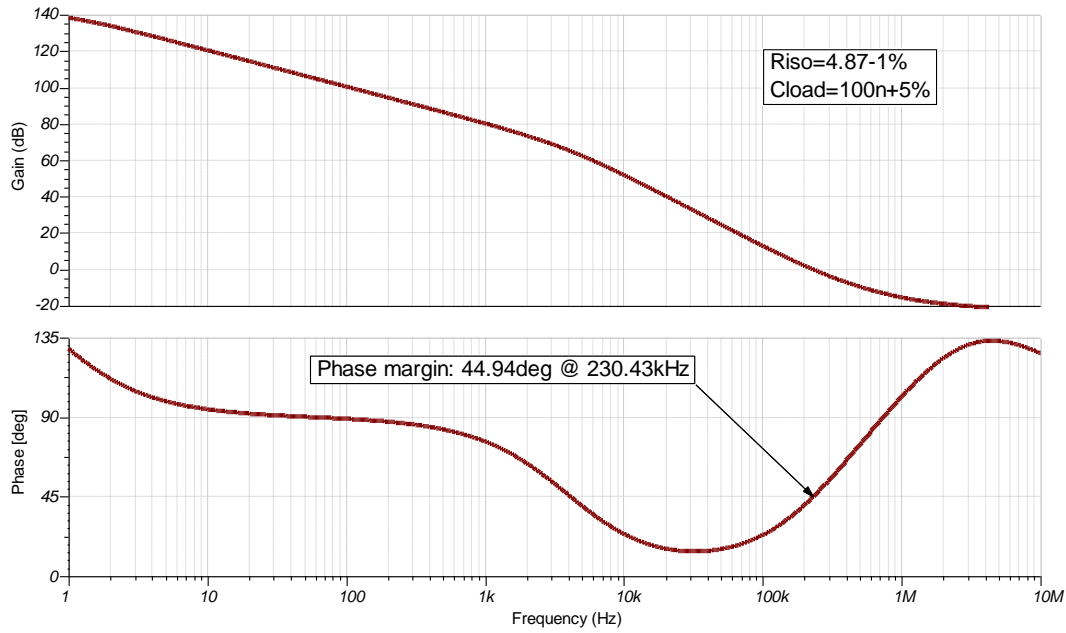


Figure 30: OPA192, $C_{load}=100\text{ nF}+5\%$, $R_{iso}=4.87\ \Omega-1\%$, $PM=44.94^\circ$

 


Figure 31: OPA192, $C_{load}=100\text{ nF}-5\%$, $R_{iso}=4.87\ \Omega+1\%$, $PM=44.36^\circ$

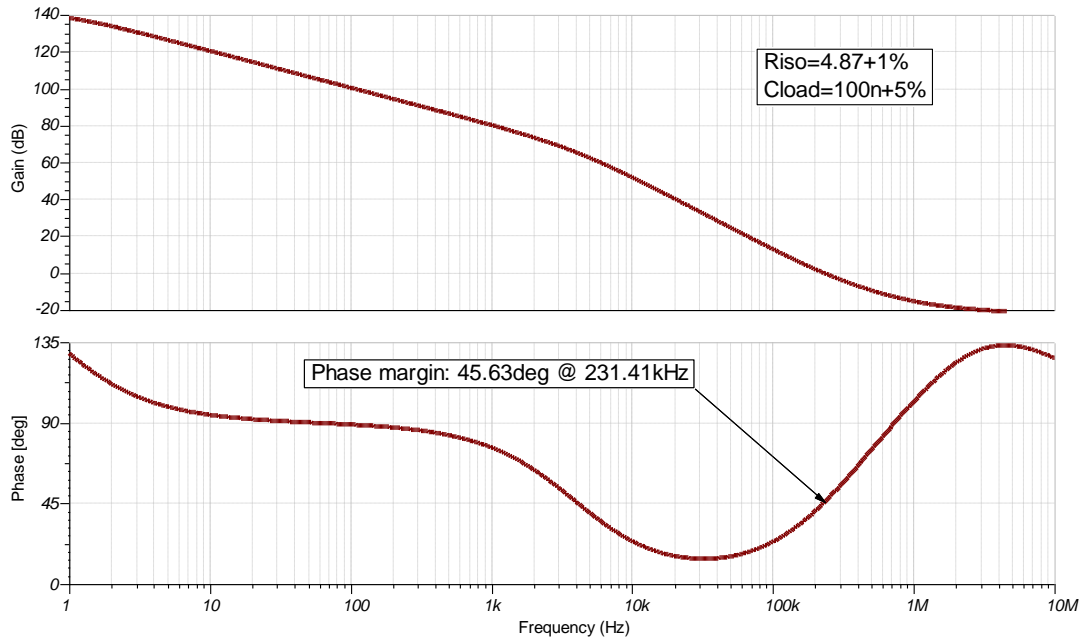


Figure 32: OPA192, $C_{load}=100\text{ nF}+5\%$, $R_{iso}=4.87\ \Omega+1\%$, $PM=45.63^\circ$

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.