

# TI Designs: TIDA-00302

## Transient Robustness for Current Shunt Monitor



### TI Designs

TI Designs are analog solutions created by TI's analog experts. Reference designs offer the theory, component selection, and simulation of useful circuits. Circuit modifications that help to meet alternate design goals are also discussed.

### Circuit Description

This high-side current shunt monitor is used to measure the voltage developed across a current-sensing resistor when current passes through it. Additionally, an external protection circuit is implemented to provide surge and fast-transient protection and demonstrate the different immunity levels to IEC61000-4-4 and IEC61000-4-5.



### Design Resources

[Design Archive](#)  
[TINA-TI™](#)  
[INA210](#)

All Design files  
 SPICE Simulator  
 Product Folder



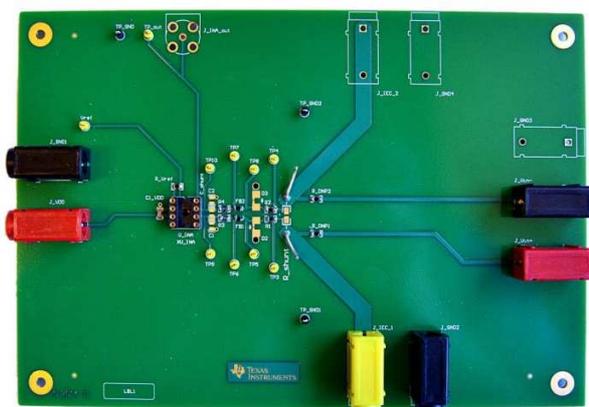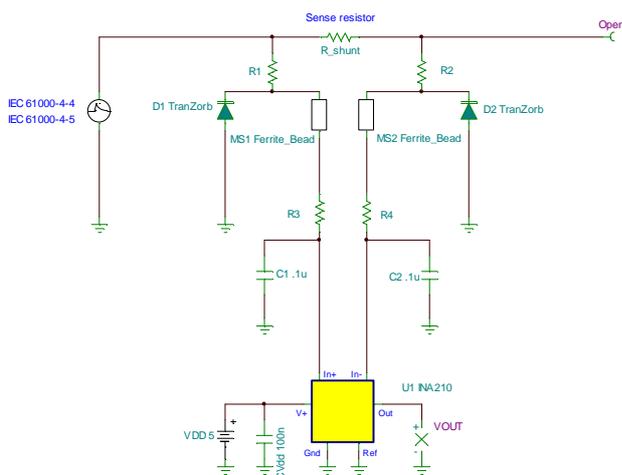[Ask The Analog Experts](#)  
[WEBENCH® Design Center](#)  
[TI Precision Designs Library](#)



**An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.**

TINA-TI is a trademark of Texas Instruments  
 WEBENCH is a registered trademark of Texas Instruments

## 1 Design Summary


The design requirements are as follows:

- Supply Voltage: 5V
- Input: IEC-61000-4 and IEC-61000-5


The goals for this design are to provide immunity to the IEC-61000-4 and IEC-61000-5 suite of tests without damaging the INA210 from overstress. Pre- and post- measurements were completed to ensure survivability. Multiple configurations were used to different performance levels as well as a device without external protection.

**Table 1. Comparison of Design Goals and Simulated Performance**

	Goal	Simulated
IEC-61000-4 MAX (kV)	4kV	4kV
IEC-61000-5 MAX (kV and I)	4kV 50 Ohms	4kV 50 Ohms

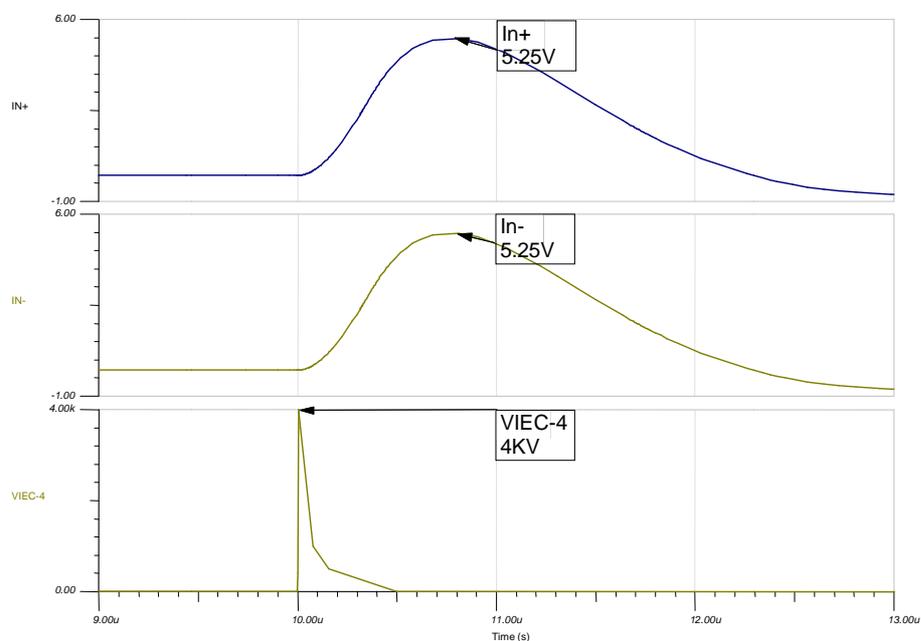


**Figure 1: IEC-61000-4 MAX (kV) Simulated Performance**

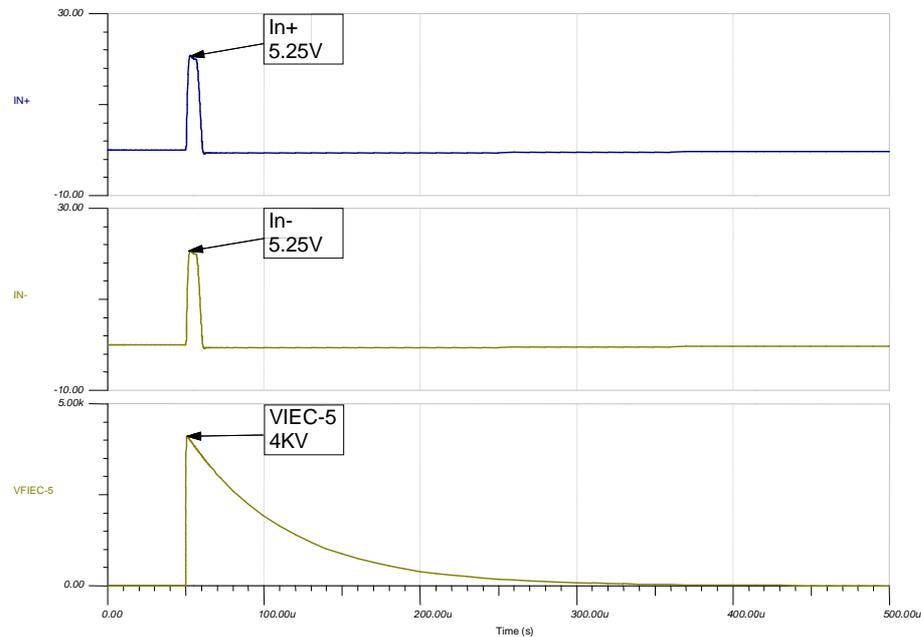

**Figure 2: IEC-61000-5 MAX (kV and I) Simulated Performance**

## 1.1 Equations

The addition of external series resistance creates an additional error in the measurement so the value of these series resistors should be kept to 10 $\Omega$  or less to reduce impact to accuracy. The internal bias network shown in Figure 3 present at the input pins creates a mismatch in input bias currents when a differential voltage is applied between the input pins. If additional external series filter resistors are added to the circuit, the mismatch in bias currents results in a mismatch of voltage drops across the filter resistors. This mismatch creates a differential error voltage that subtracts from the voltage developed at the shunt resistor. This error results in a voltage at the device input pins that is different than the voltage developed across the shunt resistor. Without the additional series resistance, the mismatch in input bias currents has less of an effect on device operation.

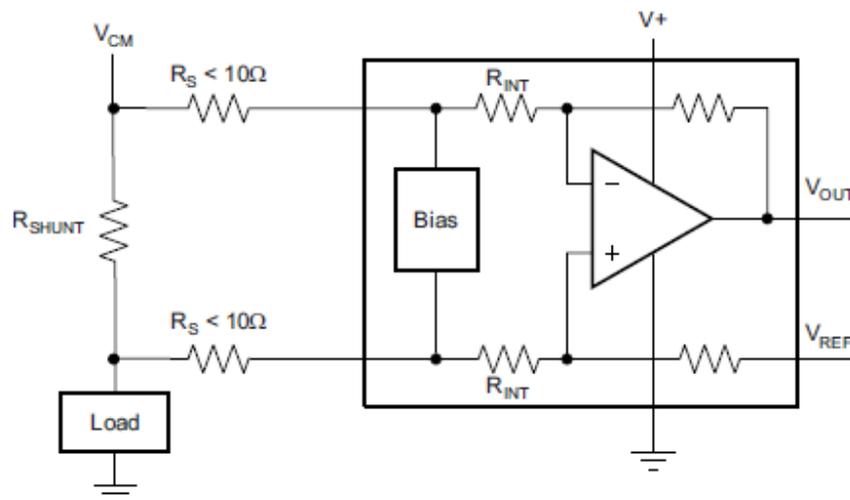

**Figure 3: Gain Error Associated Input Filter Resistance**

$$\text{Gain Error Factor} = \frac{(1250 * R_{INT})}{(1250 * R_S) + (1250 * R_{INT}) + (R_S * R_{INT})}$$

$$\text{Gain Error (\%)} = 100 - (100 * \text{Gain Error Factor})$$

## 2 Theory of Operation

### 2.1 Analog Front End Protection Circuit

The INA210-INA215 are 26-V, common-mode, zero-drift topology, current-sensing amplifiers that can be used in both low-side and high-side configurations. These specially-designed, current-sensing amplifiers are able to accurately measure voltages developed across current-sensing resistors on common-mode voltages that exceed the supply voltage powering the device. Current can be measured on input voltage rails as high as 26 V while the device can be powered from supply voltages as low as 2.7 V.

Many transient signals or radiated emissions common in industrial applications can cause electrical overstress (EOS) damage or other disruptions to unprotected systems. IEC61000-4-4 and IEC6100-4-5 voltage sources were used to test the robustness of each design option to find the optimal immunity. These are common industry test used in testing electrical devices.

This design expands on the section describing protection of the INA210 with common-mode transients above 26V in a high-side current sense configuration. The application uses attenuation and diversion to reduce the voltage level of the transient signal. Different values and configurations of the base design were used to show the different levels of protection and weakest link.

Attenuation uses primarily passive inductors and resistors to attenuate high-frequency transients and to limit series current. Ferrite beads (specialized inductors) can be used in series and are useful to maintain DC accuracy while still delivering the ability to limit current from high frequency transients. This application uses ferrite beads to block high frequency transients.

Diversion capitalizes on the fast speed of the transient or voltage properties of the transient signals. Transient voltage suppressor (TVS) diodes can be used to clamp the transient within supply voltages or capacitors to divert fast transient energy to ground. TVS diodes are helpful to protect against the IEC transients because they break down very quickly and often feature high power ratings which are critical to survive multiple transient strikes.

## 2.2 IEC61000-4-4

IEC61000-4-4 is the burst immunity, or electrically fast transient (EFT) test. This test simulates day to day switching transients from various sources in a typical industrial application space. The test is performed on power, signal, and earth wires – or a subset depending on what is appropriate for the Device Under Test (DUT).

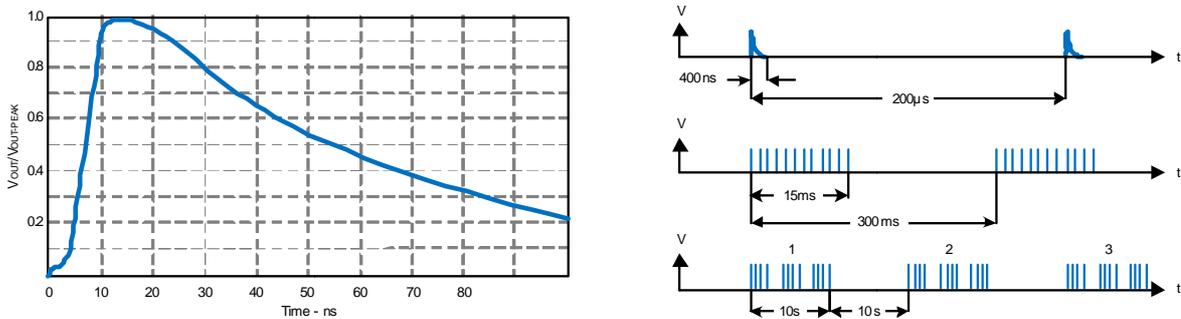


Figure 4: IEC-61000-4

The electrical fast transient is described in terms of a voltage across a 50Ω load from a generator having a nominal dynamic source impedance of 50Ω. The output occurs as a burst of high voltage spikes at a repetition rate of 5kHz. The burst length is defined as 15ms with bursts repeated every 300ms. Each individual burst pulse is a double exponential waveform with a rise time of 5ns and a total duration of 50ns. For the high-side current configuration only positive bursts were used.

## 2.3 IEC61000-4-5

IEC61000-4-5 addresses the most severe transient conditions on both power and data lines. These are transient caused by lightning strikes and switching. Switching transients may be the result of power system switching, load changes in power distribution systems, or short circuit fault conditions. Lightning transients may result from a direct strike or induced voltages and currents due to an indirect strike. The

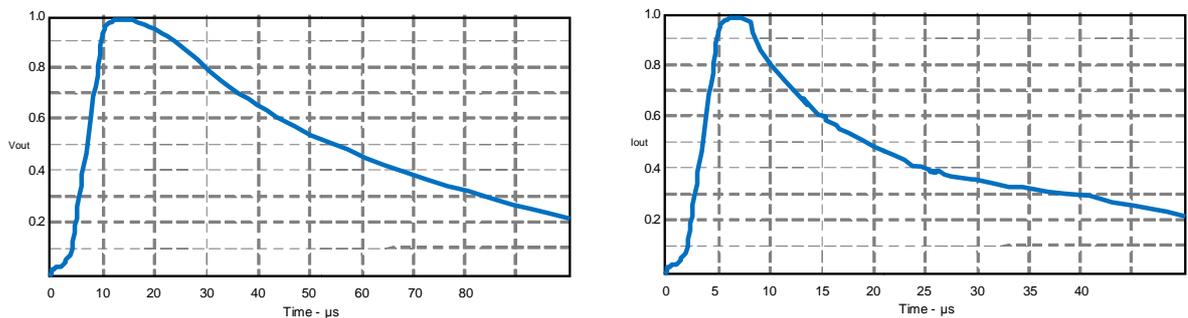


Figure 5: IEC-61000-5 Voltage Impulse and Current Impulse

The IEC 61000-4-5 standard defines a transient entry point and a set of installation conditions. The transient is defined in terms of a generator producing a given waveform and having specified open circuit voltage and source impedance. Two surge waveforms are specified: 50μs open-circuit voltage waveform and the 20μs short-circuit current waveform.

### 3 Component Selection

The components selected for the design were chosen based on the data section describing protection of the INA210 with common-mode transients above 26V in a high-side current sense configuration. Resistors (R1 and R2) limit current into TVS diodes (VD1 and VD2) which provides a diversion path. Next, the ferrite beads (MS1 and MS2) attenuate the signal into C4 and C5 (which also provide a diversion path). Lastly, R3 and R4 are used to attenuate ringing between the ferrite beads and the capacitor. There were 10 different configurations tested.

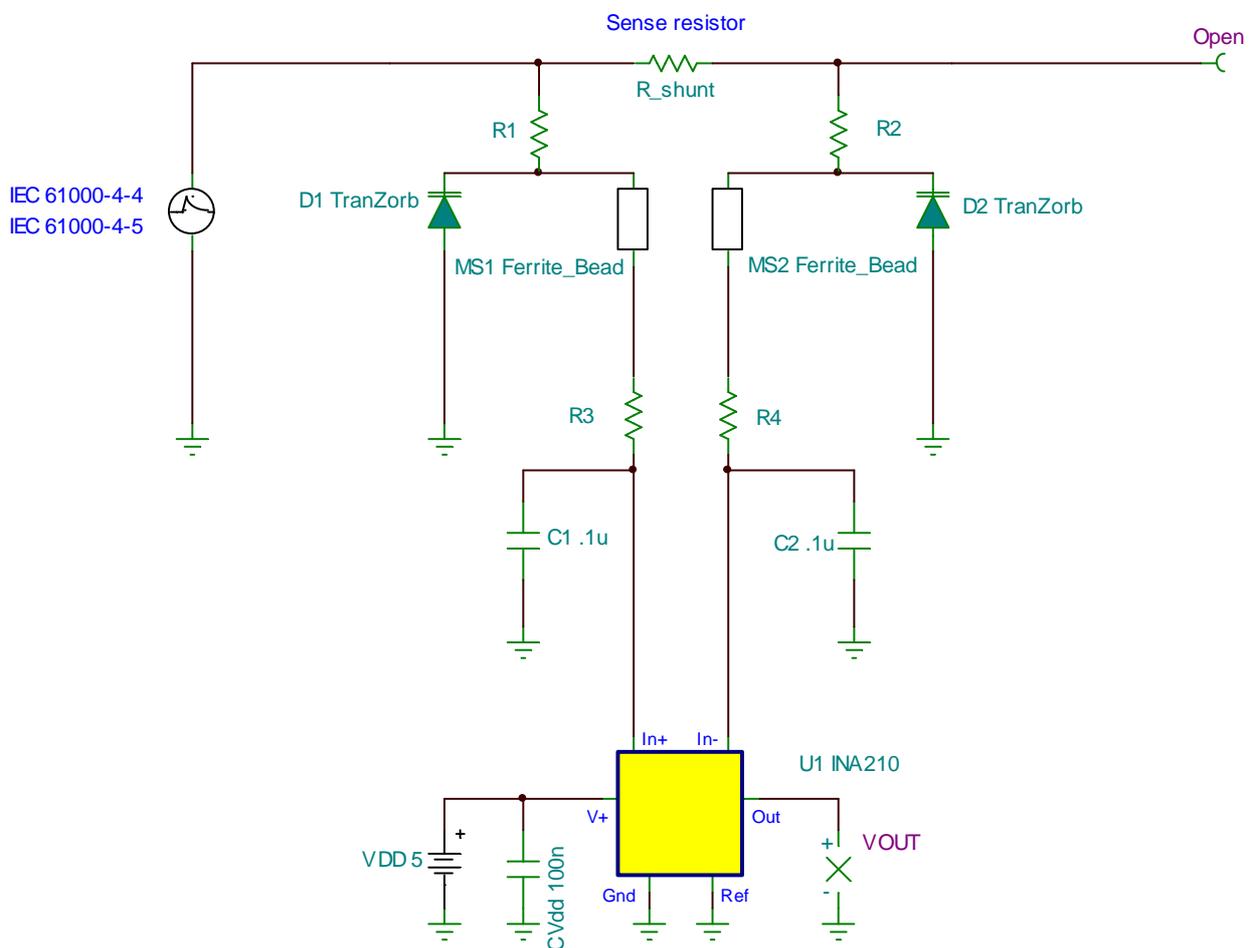


Figure 6: Base Schematic

### **3.1 TVS (Transient Voltage Suppressor)**

A TVS is typically used in sensitive electronics for protection against voltage transients induced by inductive load switching and lighting, especially for automotive load dump protection application. These devices can be selected for bidirectional clamping or unidirectional. Using the maximum input voltage into the INA210 will set the MAX clamping voltage of the TVS selected. Next, use the Min Breakdown voltage to set the usable common mode voltage of the application (leakage current into the TVS needs to be small as not to create offset across R1/R2). Lastly, the Max peak current needs to be selected to set how much power will be absorbed by shunting the current.

A TVS of 25.2V MAX (800mV below the Abs Max of the INA210), Min Breakdown voltage of 17.1 and peak current of 24A was selected to achieve the highest common mode voltage input and IEC rating.

### **3.2 Ferrite Bead**

The voltage input uses a ferrite bead between the R1/R2 and R3/R4 for the same purpose as an inductor to block current at high frequency. Resistance in the input path will result in gain error; since the impedance of the ferrite bead is only large at high frequency, low frequency and DC accuracy is maintained while the impedance blocks fast transients.

The selected ferrite for the highest IEC rating has a dc impedance of 40 m $\Omega$  and an impedance of 600  $\Omega$  at 100 MHz.


### 3.3 Component Configuration

**Table 1. Component Configuration Table**


Configuration #	R1/R2	VD1/VD2	MS1/MS2	R3/R4	C4/C5
1	1 $\Omega$	P6SMB18A 25.2V 24A	445-2206-1-ND 2A	9 $\Omega$	0.1 $\mu$ F 50V
2	5 $\Omega$	P6SMB18A 25.2V 24A	445-2206-1-ND 2A	5 $\Omega$	0.1 $\mu$ F 50V
3	7 $\Omega$	P6SMB18A 25.2V 24A	445-2206-1-ND 2A	3 $\Omega$	0.1 $\mu$ F 50V
4	7 $\Omega$	uClamp1201H 25V 8A	445-2166-1-ND 500mA	3 $\Omega$	0.1 $\mu$ F 50V
5	10 $\Omega$	uClamp1201H 25V 8A	Shorted	0 $\Omega$	Removed
6	10 $\Omega$	uClamp1201H 25V 8A	Shorted	0 $\Omega$	0.1 $\mu$ F 50V
7	10 $\Omega$	Removed	445-2166-1-ND 500mA	0 $\Omega$	0.1 $\mu$ F 50V
8	0 $\Omega$	P6SMB18A 25.2V 24A	445-2206-1-ND 2A	5 $\Omega$	0.1 $\mu$ F 50V
9	0 $\Omega$	P6SMB18A 25.2V 24A	445-2206-1-ND 2A	3 $\Omega$	0.1 $\mu$ F 50V
10	0 $\Omega$	uClamp1201H 25V 8A	445-2166-1-ND 500mA	3 $\Omega$	0.1 $\mu$ F 50V

## 4 Simulation

Many simulations were completed to find the best configuration. Configuration #1 had the best response and immunity to transient signals IEC61000-4-4 and IEC61000-4-5. The current through D1 and D2 were within device specifications and would survive. Voltages at IN+/- were also well within data sheet limits for the INA210.

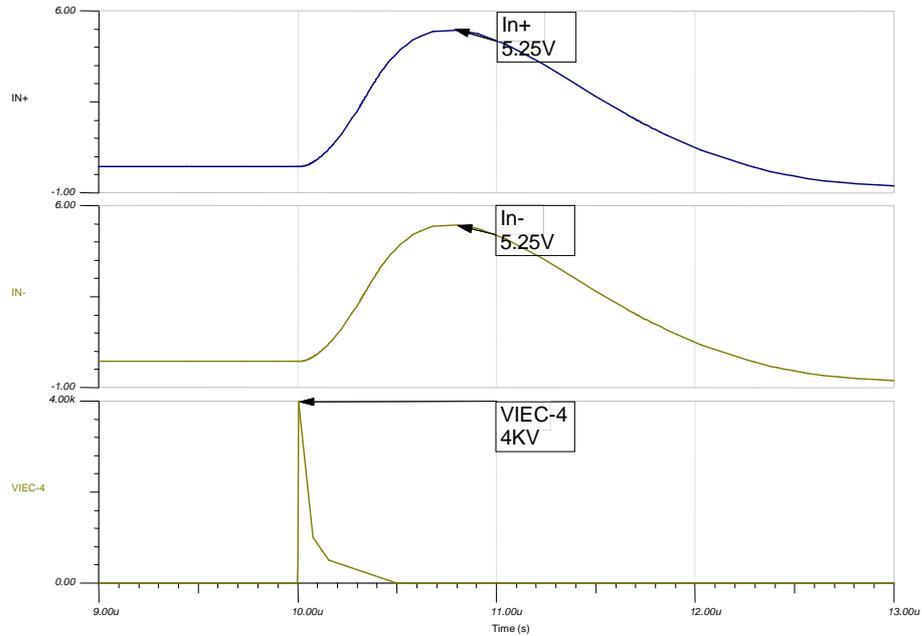

**Figure 7: IEC-61000-4 MAX (kV)**

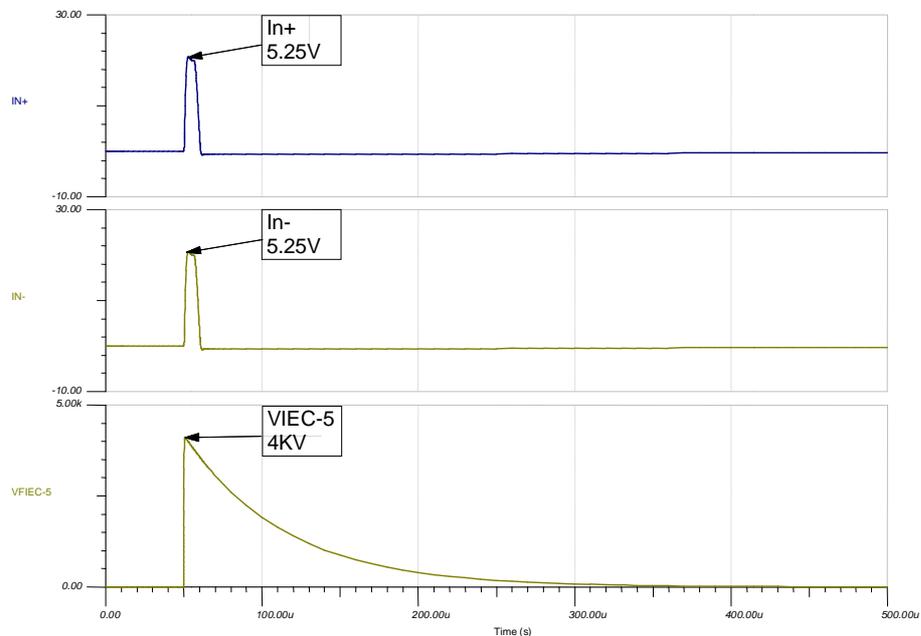

**Figure 8: IEC-61000-5 MAX (kV and I)**

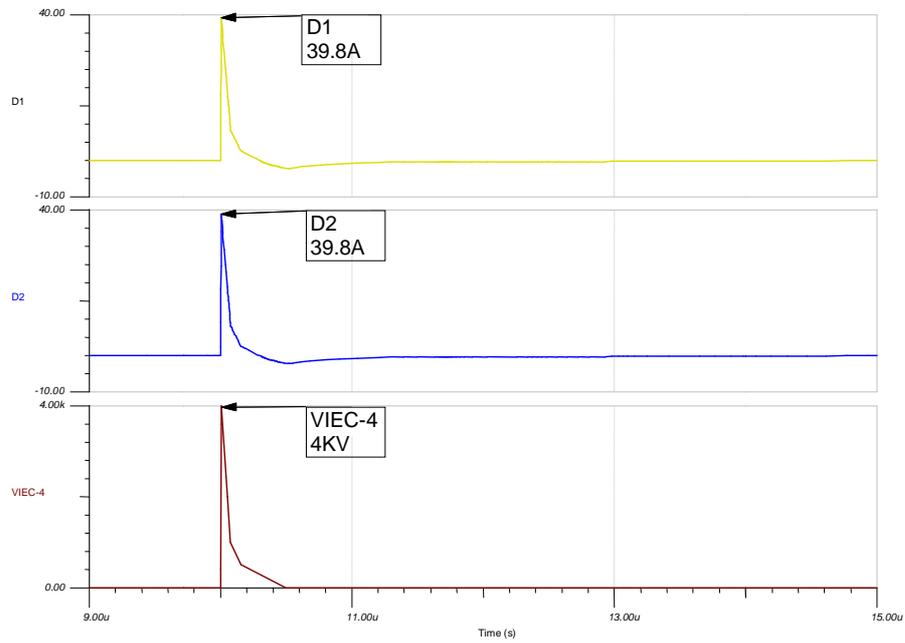


Figure 9: IEC-61000-4 MAX (kV) D1 & D2

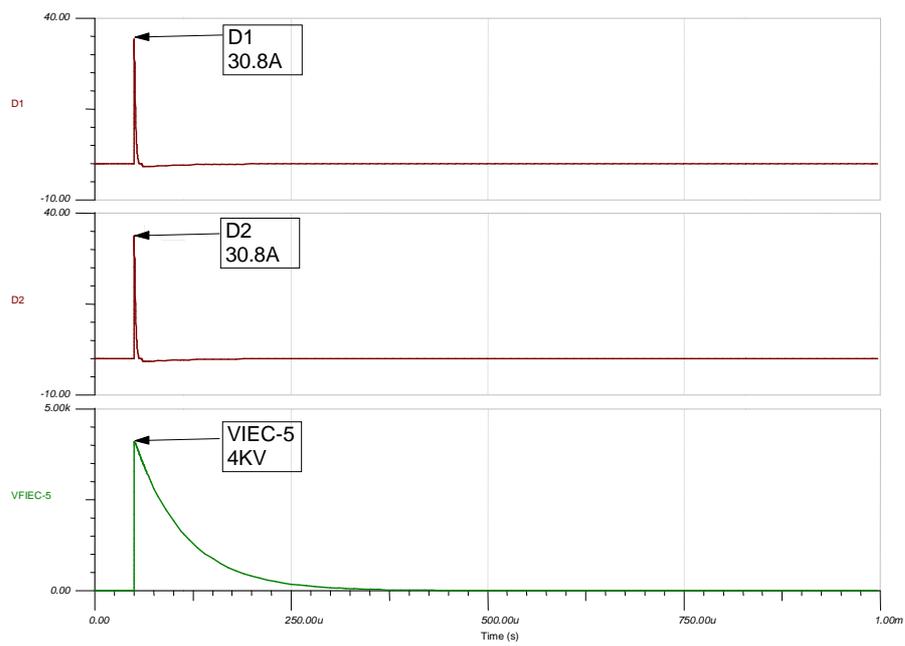


Figure 10: IEC-61000-5 MAX (kV and I) D1 & D2

## 5 PCB Design

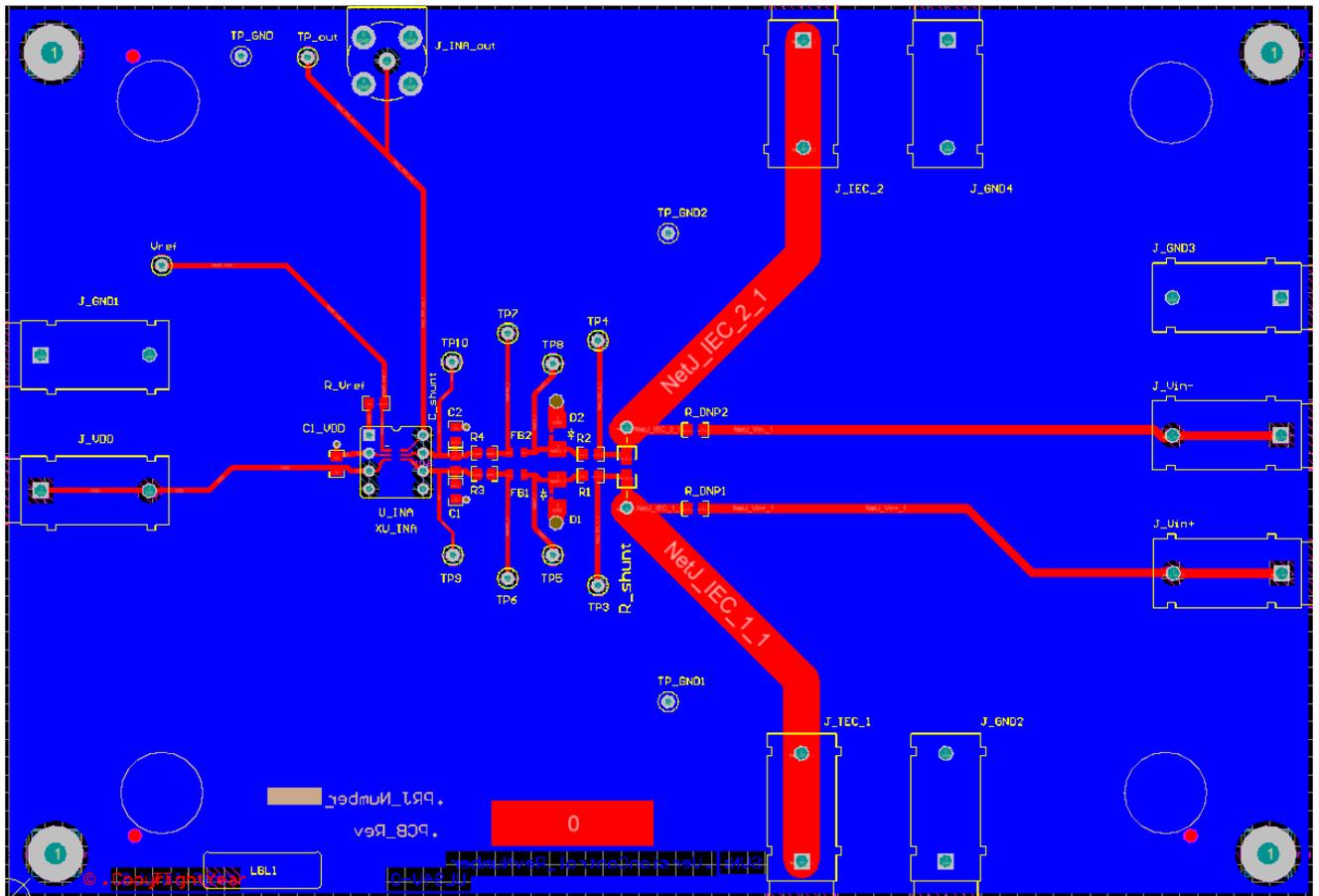


Figure 11: Top Level Board Layout



## 6 Certification Testing Results

### 6.1 IEC61000-4-4 Results

**Table 2. IEC610004-4 Table**

Configuration	Pass	Fail	Device failure
Device Only	875V	900V	INA210
1	4KV	None	R1 & R2
2		Below 2KV	R1 & R2
3	2KV	2.5KV	R1 & R2
4	2KV	3KV	R1 & R2
5	3KV	4KV	R1 & R2
6	3KV	4KV	R1 & R2
7	3KV	4KV	R1 & R2
8	4KV	None	D2 & D3 (TVS)
9	4KV	None	D2 & D3 (TVS)
10	4KV	None	D2 & D3 (TVS)

## 6.2 IEC61000-4-5 Results

**Table 3. IEC610004-5 Table**

Configuration	Pass	Fail	Device failure
Device Only	Did not pass	Below 200V 50 Ohms	INA210
1	400V 8.8 Ohms	500V 8.8 Ohms	R1 & R2
2	220V 8.8 Ohms	250V 8.8 Ohms	R1 & R2
3	250V 8.8 Ohms	300V 8.8 Ohms	R1 & R2
4		Below 200V 8.8 Ohms	R1 & R2
5	300V 8.8 Ohms	350V 8.8 Ohms	R1 & R2
6	300V 8.8 Ohms	400V 8.8 Ohms	R1 & R2
7		Below 200V 8.8 Ohms	R1 & R2
8	3KV 2 Ohms	4KV 2 Ohms	D2 & D3 (TVS)
9	3KV 2 Ohms	4KV 2 Ohms	D2 & D3 (TVS)
10	250V 8.8 Ohms	300V 8.8 Ohms	D2 & D3 (TVS)

### 6.3 Conclusion

From the result data, it is clear that the weakest links are the R1/R2 which are in the current path. R3/R4 were inconsequential to protection and could be minimized to 1 Ohm to reduce gain error. By reducing the resistance the power across the resistor is reduced. The Ferrite Beads were only successful when the transient signal was in nanosecond time periods (IEC61000-4-4) but did not offer any protection in slow microsecond transients (IEC61000-4-5). Capacitors C1/C2 were also not effective when signals where in microseconds. Lastly, the most effective component used to protect the INA210 from voltage transients were the TVS diodes D1/D2. Depending on the amount of current that the TVS must absorb, PCB area and cost will determine the robustness of the overall transient protection circuit.

The simulated wave forms did not match the measured waveforms for IEC61000-4-4 (Appendix B). They far exceeded the clamping voltage of the TVS but did survive. TVS have a delay time to hold clamp the voltage for a fast transient and will not clamp the voltage to the MAX clamping voltage. The INA210 has an ESD rating of +/-2kV this offers some protection against fast transients and is why the INA210 could survive fast transient potentials of up to 875V. The measured results the maximum voltage at VIN+/- was approximately half of the INA210 stand alone survivable voltage.

## 7 Modifications

The output protection circuit described in this design is specifically tailored to the INA210 and associated family of devices with up to 26 V Common-Mode range. Modifying the Common-Mode range used in this design may require the selection of different components, such as lower breakdown voltage diodes. Discrete solutions that use multiple integrated circuits may also need to choose different components for appropriate protection. Consideration of gain and offset errors used with series resistance will also need to be taken into account as well as current leakage from the protection diodes.

Furthermore, the protection circuit in this design is only intended to be applied to IEC61000-4-4 and IEC61000-4-5. Other immunity tests are not considered for this design and may require additional components to handle the power levels associated with them.

## 8 About the Author

Jamieson Wardall is an applications engineer in the sensing group at Texas Instruments where he supports temperature and current sensing products and applications. Jamieson has over fifteen years of professional experience in semiconductor industry with a multitude of device experience. Jamieson received his BSEE from California State University Sacramento and MSEE from Arizona State University.

## 9 Acknowledgements & References


The author wishes to acknowledge NTS ([National Technical Systems](#)) in Plano, TX for their assistance performing the electromagnetic compatibility tests.

1. *IEC Publication 61000-4-4 “Electromagnetic Compatibility (EMC) – Part 4-4: Testing and Measurement Techniques – Electrical Fast Transient/Burst Immunity Test,” International Electrotechnical Commission, 2012.*
2. *IEC Publication 61000-4-5 “Electromagnetic Compatibility (EMC) – Part 4-5: Testing and Measurement Techniques – Surge Immunity Test,” International Electrotechnical Commission, 2012.*

## Appendix A.

### A.1 IEC61000-4-4/5 Photos


Figure A-1: IEC61000-4-4/5 Setup

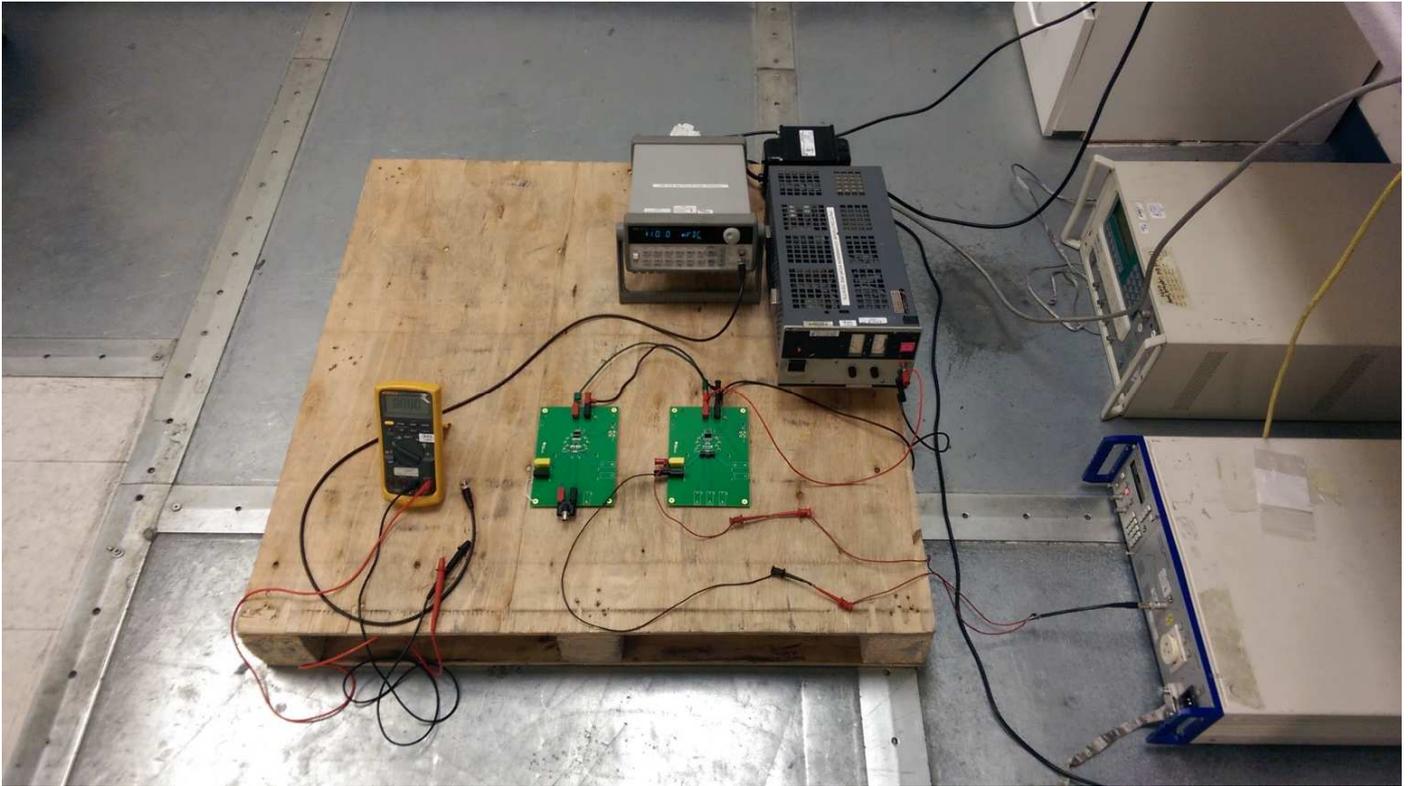

## Appendix B.

### B.1 IEC61000-4-4 Scope Plots

Table B-1: Configuration #1 2kV

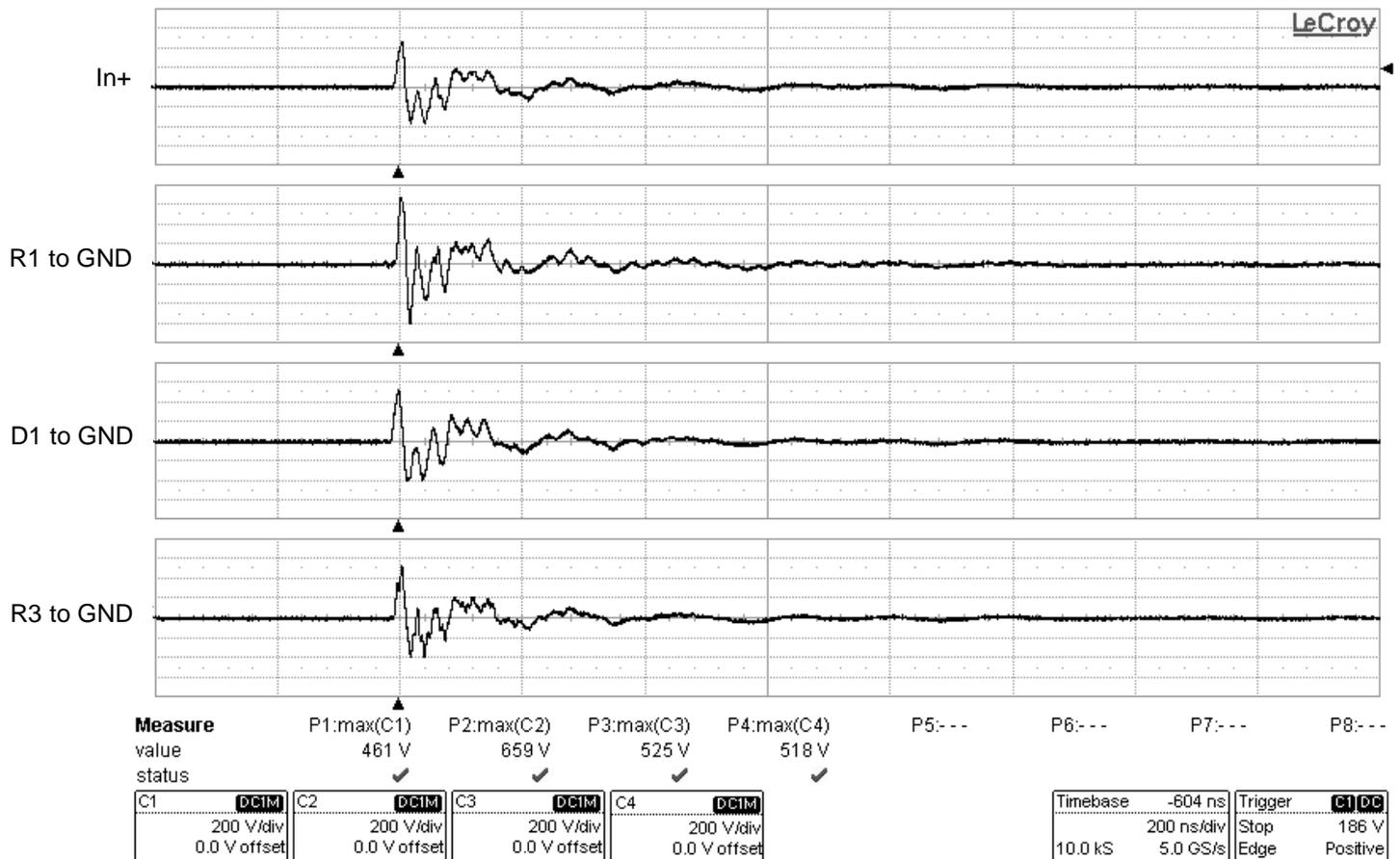

**Table B-2: Configuration #8 2kV**



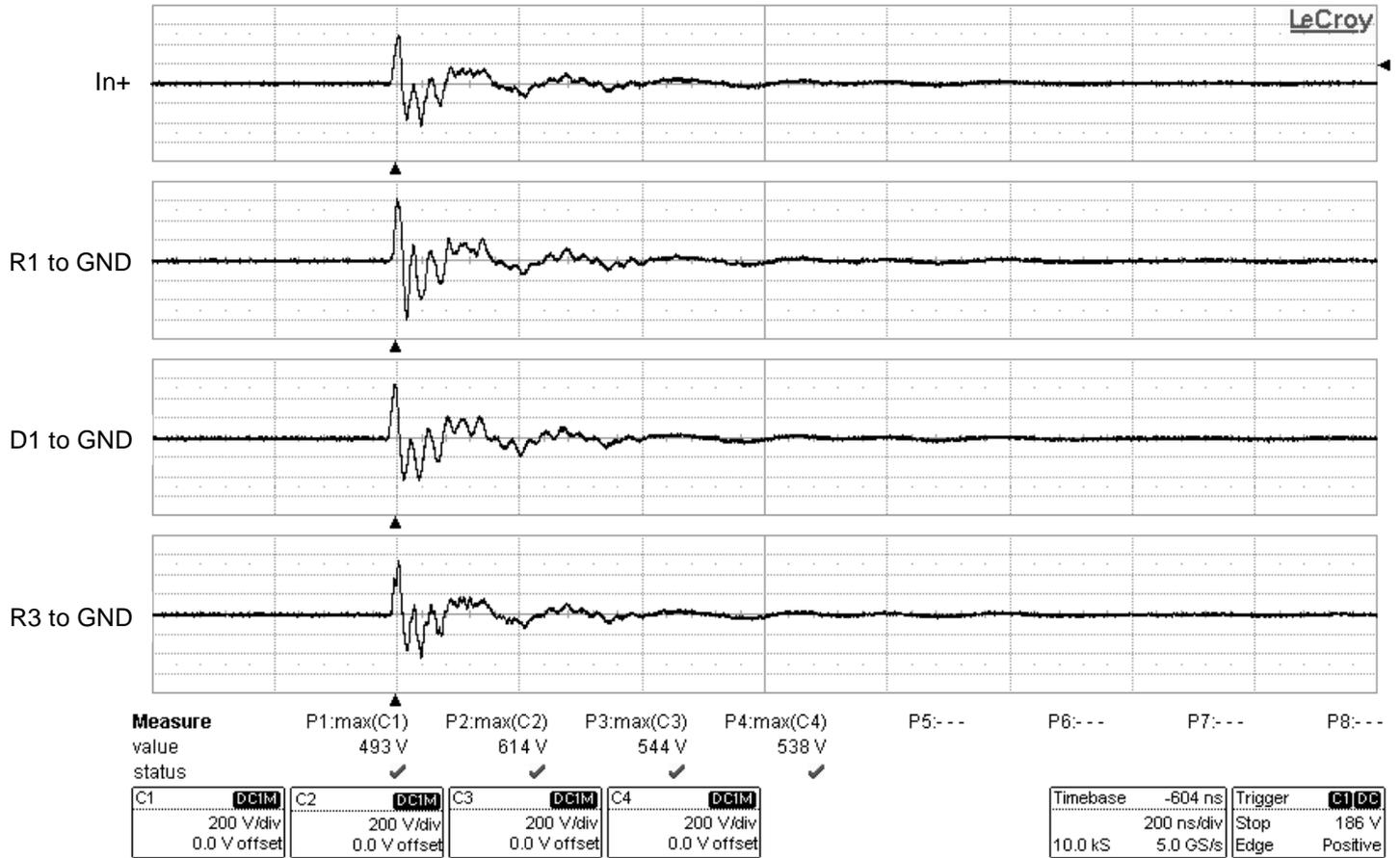


Table B-3: Configuration #9 2kV

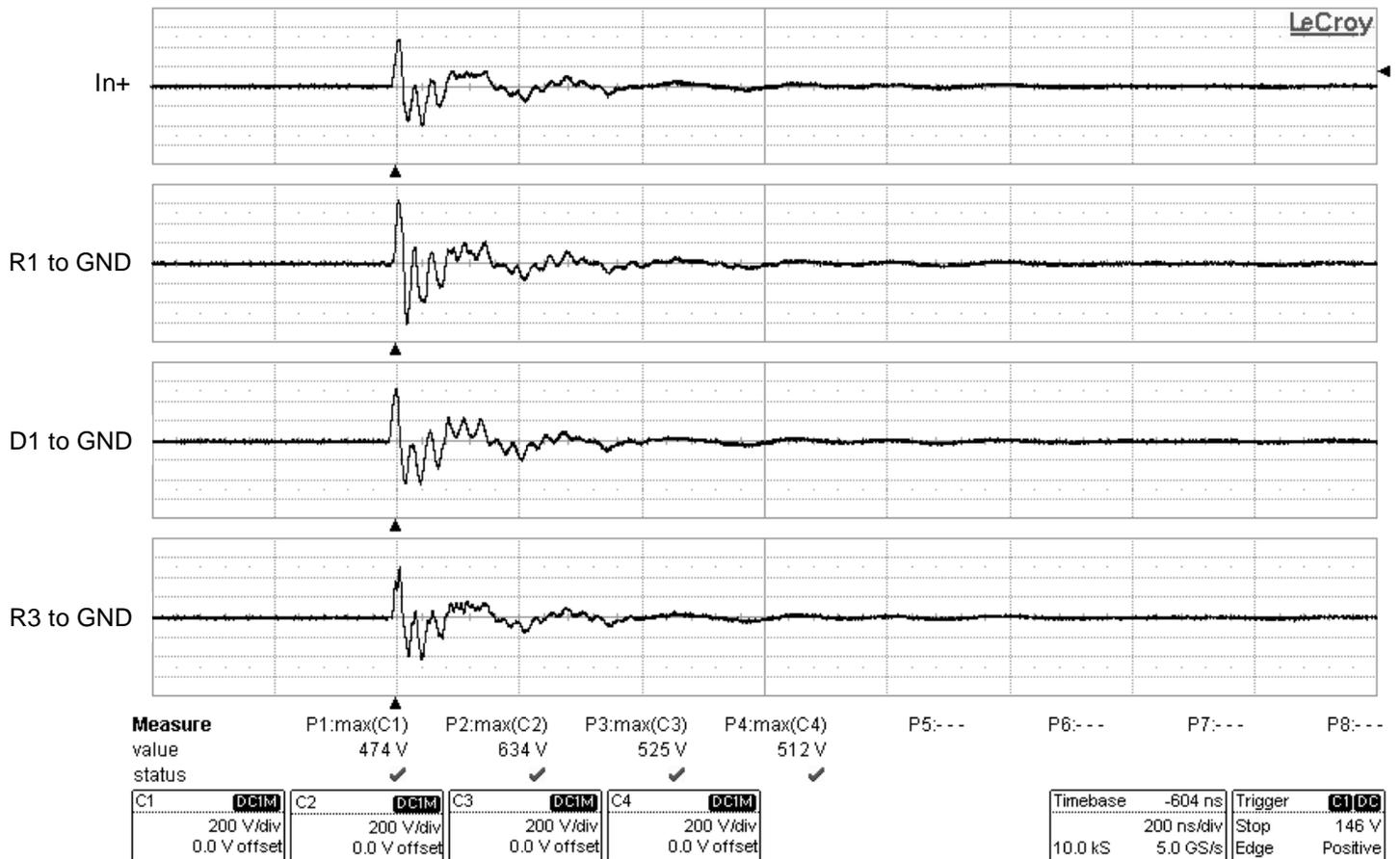

**Table B-4: Configuration #10 2kV**

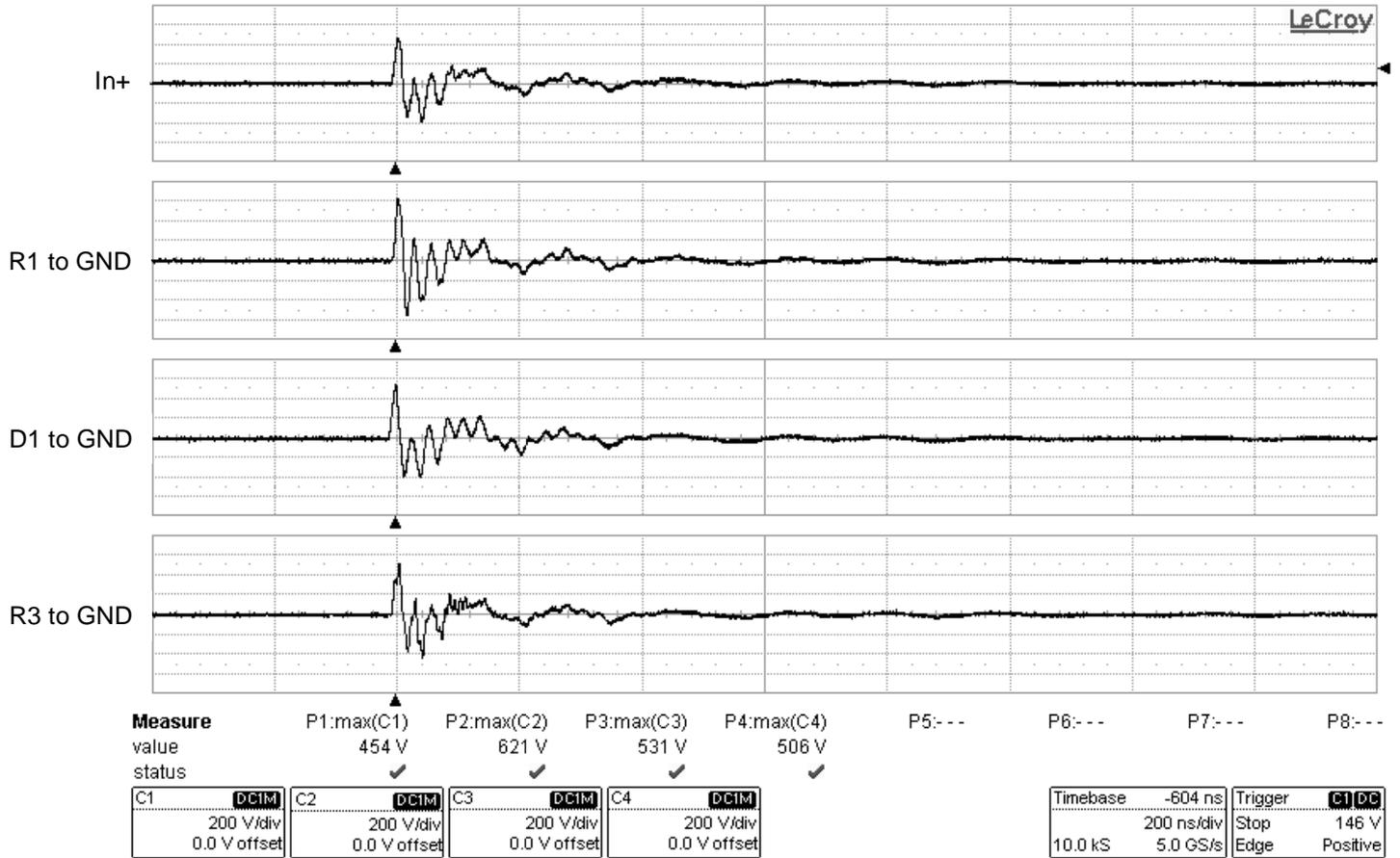

## Appendix C.

### C.1 IEC61000-4-5 Scope Plots

Table C-1: Configuration #1 200 V 8.8 Ohms

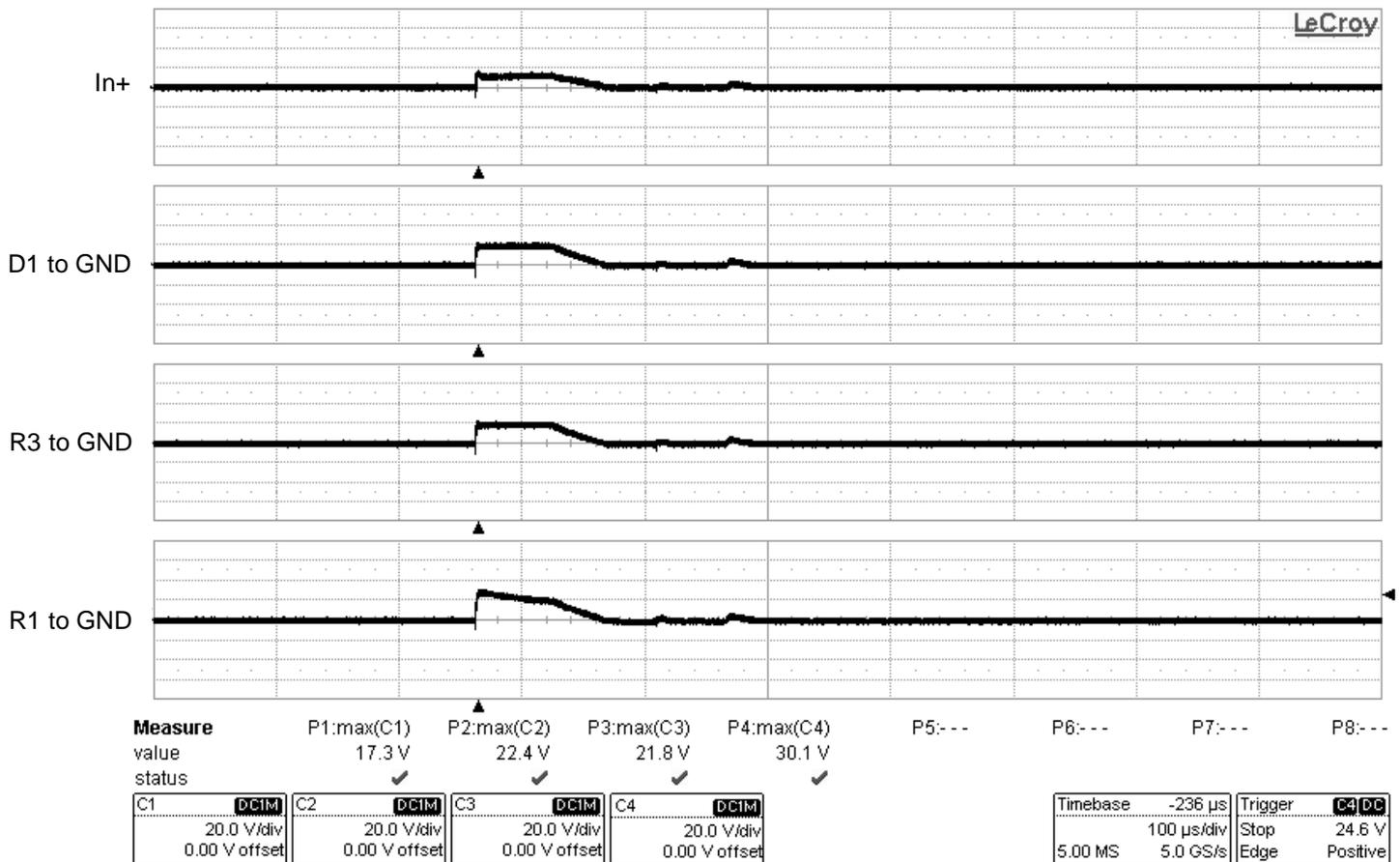


Table C-2: Configuration #8 200 V 8.8 Ohms

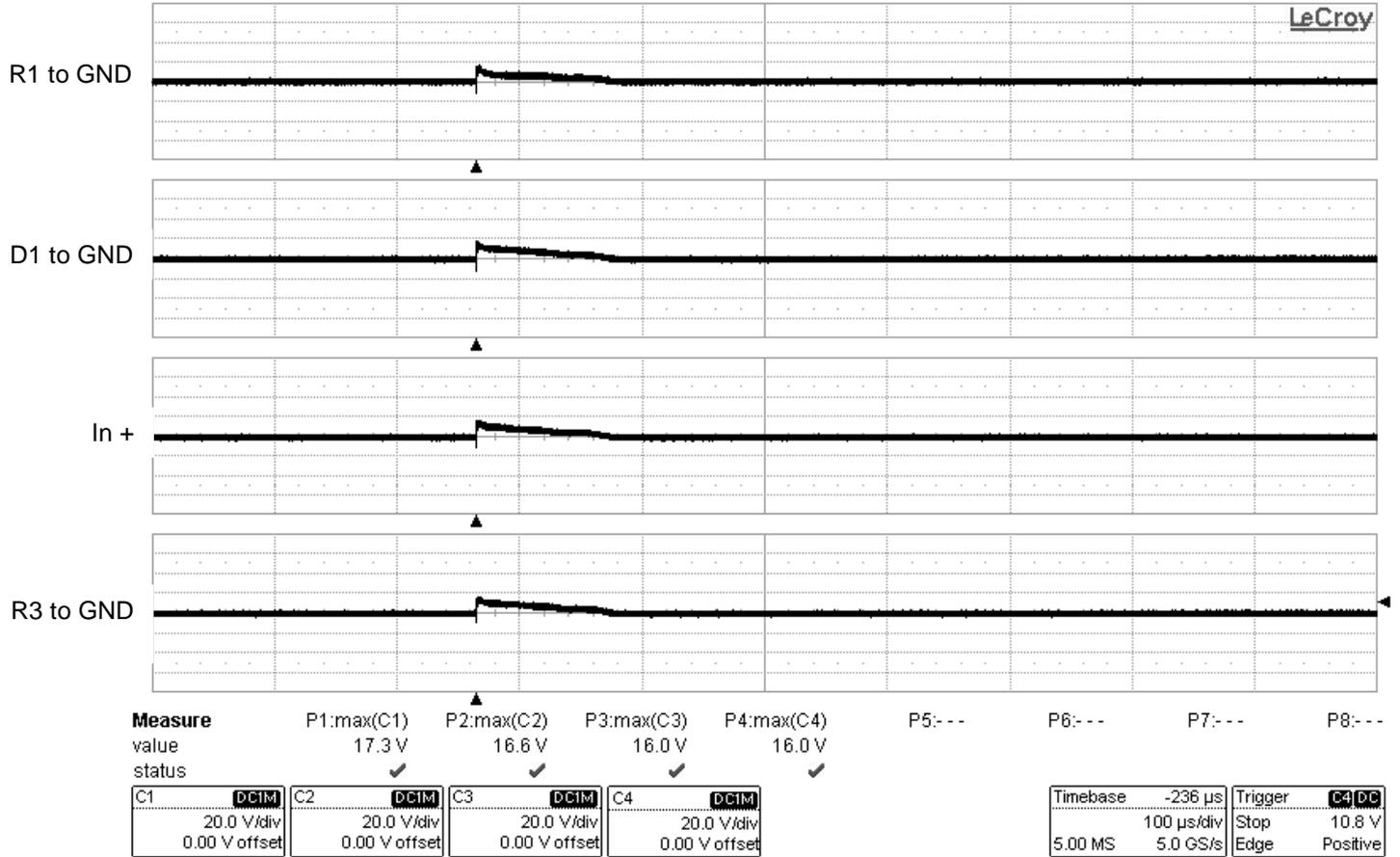


Table C-3: Configuration #9 200 V 8.8 Ohms


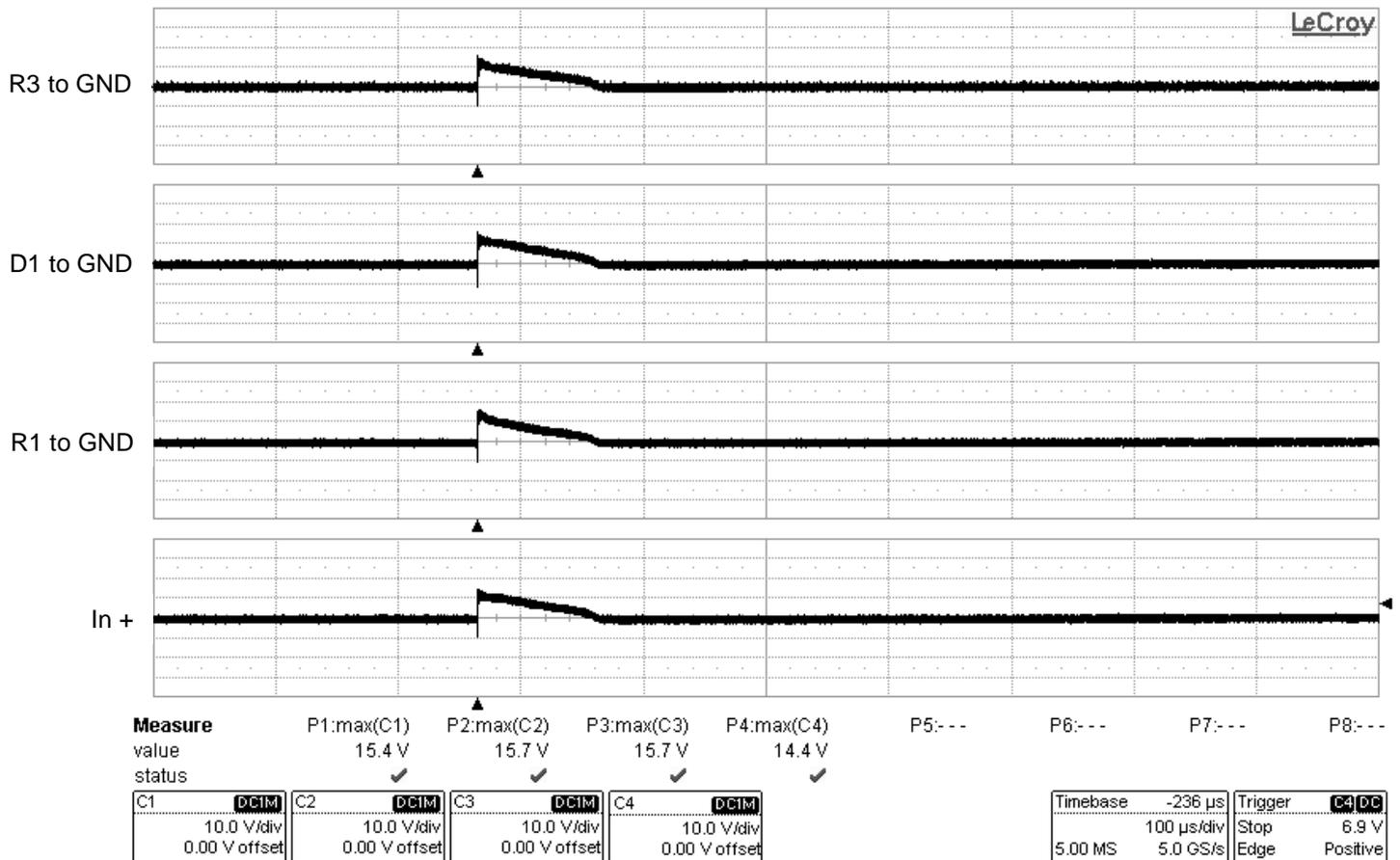


Table C-4: Configuration #10 200 V 8.8 Ohms

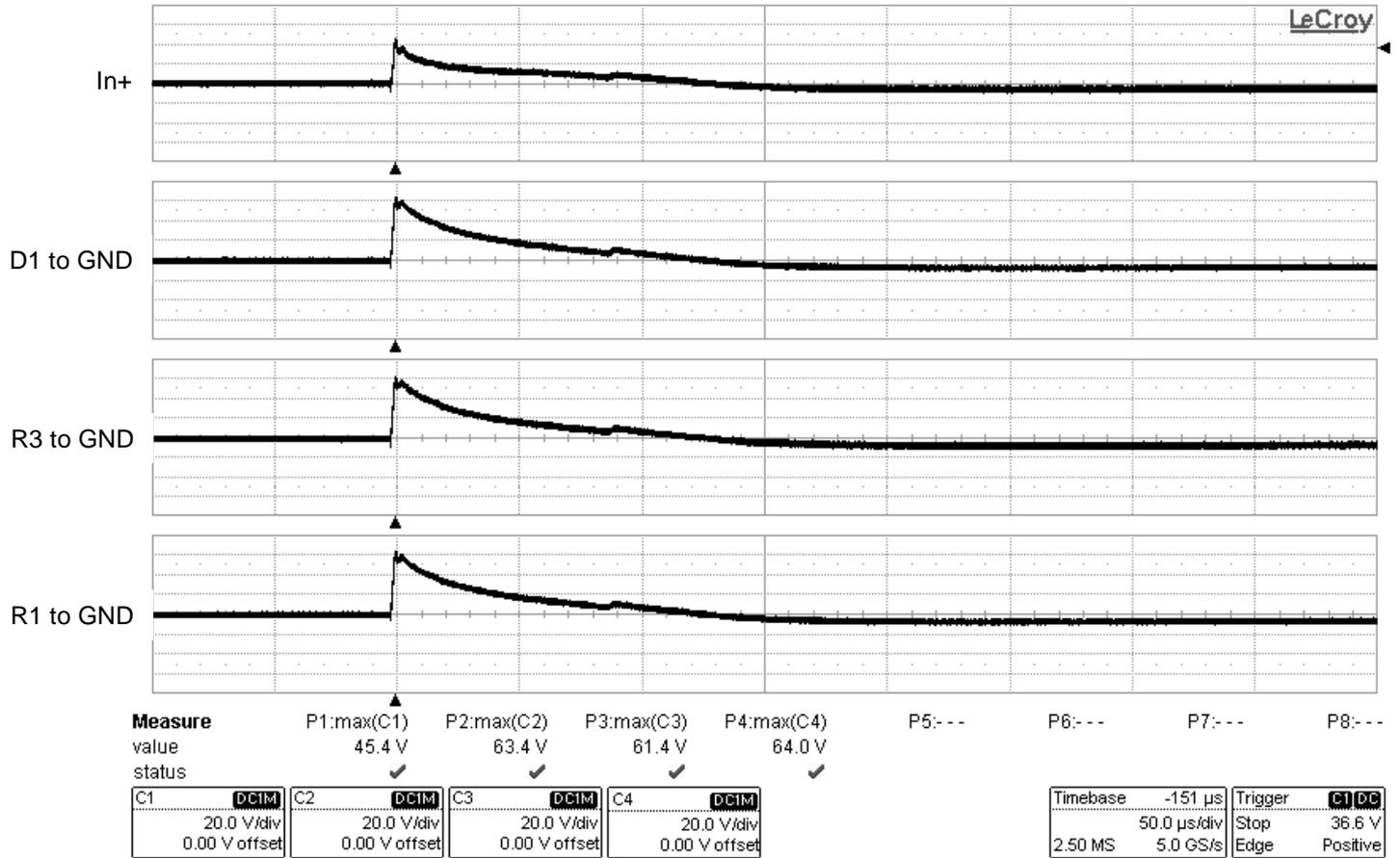

## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.