

TI Designs: PMP9770 Reference Guide

LCD Bias Power Reference Design with TPS61085



TI Designs

TI Designs are analog solutions created by TI's analog experts. Reference designs offer the theory, component selection, and simulation of useful circuits. Circuit modifications that help to meet alternate design goals are also discussed.

Circuit Description

This reference design delivers a low cost LCD bias power circuit using the boost converter IC TPS61085. The solution provides all four voltages required by the thin film transistor (TFT) LCD display. The TPS61085 boost converter generates the AVDD voltage. Two external charge pump circuits provide the positive VGH and negative VGL bias voltage for the TFT. One external op-amp LM7321MF acts as a high current buffer, it provides the VCOM voltage for the TFT backplane.


Design Resources

[Design Page](#)
[TPS61085](#)
[LM7321](#)

All Design files
 Product Folder
 Product Folder



 [Ask The Analog Experts](#)
[WEBENCH® Design Center](#)
[TI Precision Designs Library](#)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

TINA-TI is a trademark of Texas Instruments
 WEBENCH is a registered trademark of Texas Instruments

1 Introduction

There already exists some IC which can offer an integrated solution to meet all the voltages required by thin film transistor (TFT) LCD displays. But this kind of IC usually is expensive. So, some customers prefer cheap discrete solution yet hope to keep the small size at the same time.

This reference design illustrates a low cost discrete solution which can meet all the voltage requirements for TFT LCD displays with the TPS61085 and other external components. Additionally, a high current buffer realized by the LM7321MF is also provided for the TFT backplane.

2 LCD Bias Power Reference Design with TPS61085

2.1 Power Specification

The following table gives out the input voltage (V_{in}) range and all the voltages required by a TFT LCD display. This is the design target for this reference design.

Table 1. Input & Output Parameter

	Voltage	Maximum Current
V_{in}	2.7-3.9V	--
AVDD	10V	100mA
VGH	17V	10mA
VGL	-7V	10mA
VCOM	5V	20mA

2.2 Reference Design Schematic

 


Figure 1. Schematic for LCD bias power with TPS61085

2.3 Frequency Selection

FREQ is the frequency selection pin. The TPS61085 operates at 650kHz when the FREQ pin is connected to the GND pin and at 1.2MHz when the FREQ pin is connected to the IN pin. In this reference design, 1.2MHz frequency is preferred because higher frequency results in smaller inductor size and capacitor size.

2.4 Inductor Selection

The main parameter of an inductor is the saturation current. The saturation current of the selected inductor should be higher than the peak switch current at heavy load (including load transients).

$$P_{o(max)} = P_{AVDD} + P_{VGH} + P_{VGL} + P_{VCOM} = 1.34W \quad (1)$$

As the total output power is small, we can take the inductor ripple current about 60% of the average inductor current. Suppose efficiency $\eta=0.8$, then the peak switch current is:

$$I_{in(peak)} = I_{in(avg)} + I_{in(avg)} \cdot \frac{0.6}{2} = \frac{P_{o(max)}}{V_{in(min)} \cdot \eta} \cdot \left(1 + \frac{0.6}{2}\right) = 0.806A \quad (2)$$

Considering 20% margin, the saturation current should be higher than 1A.

The inductor value can be calculated by the following equation:

$$L = \left(\frac{V_{in(min)}}{V_o}\right)^2 \cdot \left(\frac{V_o - V_{in(min)}}{I_o \cdot f_s}\right) \cdot \left(\frac{\eta}{0.6}\right) \approx 4.7\mu H \quad (3)$$

Where:

Vin(min)	Minimum input voltage
Vo	Output voltage AVDD(10V)
Io	Maximum output current equivalent at AVDD(Vo=10V)
fs	Switching frequency(1.2MHz)

Another important factor is the inductor type. At high switching frequencies of 1.2 MHz, inductor core loss, proximity effect and skin effect become very important, the self-resonant frequency of the inductor should be higher than the 1.2MHz operation frequency. Finally, the DC resistance (DCR) should be as low as possible to minimize the power loss.

2.5 Output Voltage Setting of AVDD, VGH, VGL & VCOM

The output voltage AVDD is set by an external resistor divider R1 and R3 (Figure 1). Typically, a minimum current of 50 μ A flowing through the feedback divider gives good accuracy. Using 16.2K Ω resistance for R1, R3 can be calculated as:

$$R_3 = R_1 \cdot \left(\frac{V_o}{V_{FB}} - 1\right) \approx 115k\Omega \quad (4)$$

Vo	Output voltage AVDD (10V)
----	---------------------------

VFB Feedback regulation voltage (1.238V)

The output voltage VGH is calculated as:

$$V_{GH} = V_{Z(D2)} - V_{Q1(be)} \quad (5)$$

VZ(D2) Zener diode D2 voltage

VQ1(be) NPN transistor Q1's base-emitter voltage

To meet VGH = 17V target, a 18V rating, ±2% tolerance zener diode MM3Z18VB is selected as D2. From Vz VS. Iz curve, the zener voltage from Iz=2mA to Iz=5mA is nearly the same. Considering the conversion efficiency, 2.1mA Iz is selected in this design:

$$I_{Z(D2)} = \frac{(2V_o - V_d) - V_{Z(D2)}}{R_5} \approx 2.1mA \quad (6)$$

Vo Output voltage AVDD (10V)

Vd The voltage drop of D4 (BAT54SLT1G), Vd=0.32V @ 25°C

R5 810 Ω

The temperature coefficient (Sz) of the MM3Z18VB is 14.4mV/K, so the minimum zener voltage at -25°C and the maximum zener voltage at 85°C is:

$$V_{D2(min)} = 18 - 0.0144 \times 50 = 17.28V \quad (7)$$

$$V_{D2(max)} = 18 + 0.0144 \times 60 = 18.86V \quad (8)$$

NPN transistor Q1's base-emitter voltage (by the test) Vbe = 0.78V at -25°C, and Vbe = 0.499V at 85°C, so:

$$V_{GH(min)} = 17.28 - 0.78 = 16.5V \quad (9)$$

$$V_{GH(max)} = 18.86 - 0.499 = 18.36V \quad (10)$$

The output voltage VGL is calculated as:

$$V_{GL} = -V_{Z(D3)} + V_{Q2(eb)} \quad (11)$$

VZ(D3) Zener diode D3 voltage

VQ2(eb) PNP transistor Q2's emitter-base voltage

To meet VGL = -7V target, a 7.5V rating, ±2% tolerance zener diode MM3Z7V5B is selected as D3. The working current Iz of D3 is calculated as:

$$I_{Z(D3)} = \frac{(V_o - V_d) - V_{Z(D3)}}{R_4} \approx 2.2mA \quad (12)$$

Vz(D3) Zener diode D3 (MM3Z7V5B) voltage, Vz(D3) = 7.5V @ 25°C

R4 1kΩ

The temperature coefficient (Sz) of the MM3Z7V5B is 4mV/K, so the minimum zener voltage at -25°C and the maximum zener voltage at 85°C is:

$$V_{D3(\min)} = 7.5 - 0.004 \times 50 = 7.3V \quad (13)$$

$$V_{D3(\max)} = 7.5 + 0.004 \times 60 = 7.74V \quad (14)$$

PNP transistor Q2's emitter-base voltage (by the test) $V_{eb}=0.783V$ at -25°C, and $V_{eb}=0.495V$ at 85°C, so:

$$V_{GL(\min)} = -7.74 + 0.495 = -7.245V \quad (15)$$

$$V_{GL(\max)} = -7.3 + 0.783 = -6.517V \quad (16)$$

The output voltage VCOM is set by the resistor R7, R9 and the potentiometer R6. Adjusting R6 gets the required 5V output of the VCOM buffer.

2.6 Output Capacitor Selection

The output cap C5 & C6 for AVDD can be calculated with the following equation:

$$C_{out(AVDD)} = \frac{V_o - V_{in(\min)}}{V_o \cdot f_s} \cdot \frac{I_{out}}{\Delta V_{out}} \quad (17)$$

ΔV_{out} Output voltage ripple

Considering the capacitance derating under certain DC bias, two 10uF ceramic capacitors in parallel is fit for the $\Delta V_o=20mV$ application.

2.7 Compensation Circuit

The COMP pin is the output of the internal trans-conductance error amplifier. The following equation can be used to calculate R2 and C4 (Figure 1).

$$R_2 = \frac{110 \cdot V_{in(\min)} \cdot V_o \cdot C_{out(AVDD)}}{L \cdot I_{out}} \quad (18)$$

$$C_4 = \frac{V_o \cdot C_{out(AVDD)}}{7.5 \cdot I_{out} \cdot R_2} \quad (19)$$

R2=39k and C4=3.3nF are used in this reference design.

2.8 Buffer Amplifier Selection

LM7321 is used as the buffer amplifier for the VCOM power. The maximum load current should be within the output current capability of the LM7321 (35mA minimum sourcing current and 50mA minimum sinking current for 10V supplies).

3 PCB Layout

This reference design is implemented in a 3cm×1.55cm and 2-layers PCB. All the components are placed on the top layer. Figure 2 shows the top layer and top silk screen. Figure 3 shows the layout of the bottom layer.

 


Figure 2 Top layer and Top Silkscreen

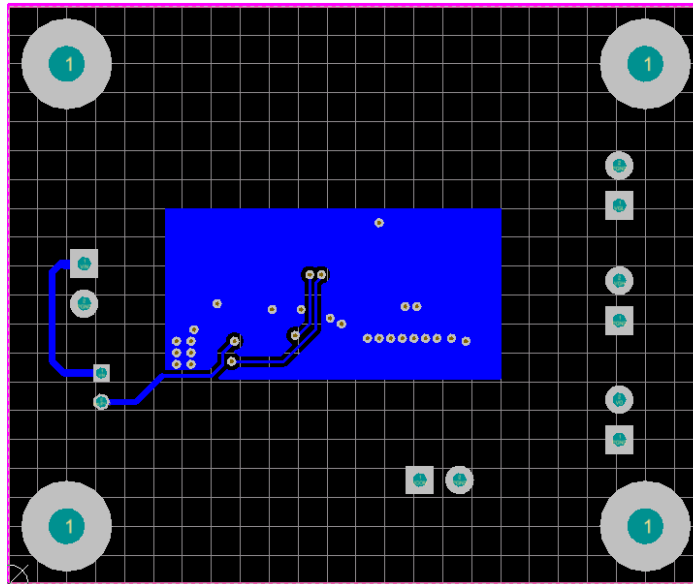


Figure 3 Bottom layer

4 Test Result

Figure 4.1 and Figure 4.2 show the SW pin voltage of the TPS61085 and the current of the inductor L1 at $V_{in}=3.3V$.

 


Figure 4.1 PWM switching at light load

 


Figure 4.2 PWM switching at heavy load

Figure 5.1 shows AVDD and VCOM voltage ripple at heavy load ($I_{AVDD}=100mA$ & $I_{VCOM}=20mA$). Figure 5.2 shows VGL and VGH voltage ripple with 10mA load respectively.

 


Figure 5.1 AVDD and Vcom voltage ripple

 


Figure 5.2 VGL and VGH voltage ripple

Figure 6.1 shows the startup waveform of AVDD, VGH voltage, and inductor current. Figure 6.2 shows the startup waveform of VGL, VCOM voltage, and inductor current. The load condition is: $I_{AVDD}=100mA$, $I_{VCOM}=20mA$, $I_{VGH}=1mA$, $I_{VGL}=1mA$.

 


Figure 6.1 AVDD, VCOM and IL startup waveform

 


Figure 6.2 VGL, VCOM and IL startup waveform

Figure 7.1 shows the no load to full load (0mA to 100mA) transient response of AVDD. Figure 7.2 shows the no load to full load (0mA to 20mA) transient response of VCOM.

 


Figure 7.1 AVDD load transient response

 


Figure 7.2 Vcom load transient response

Figure 8 shows the buffer amplifier's output voltage VCOM versus sinking & sourcing current ICOM.

Figure 9 shows AVDD voltage versus output current IAVDD.

 


Figure 8 VCOM VS. ICOM

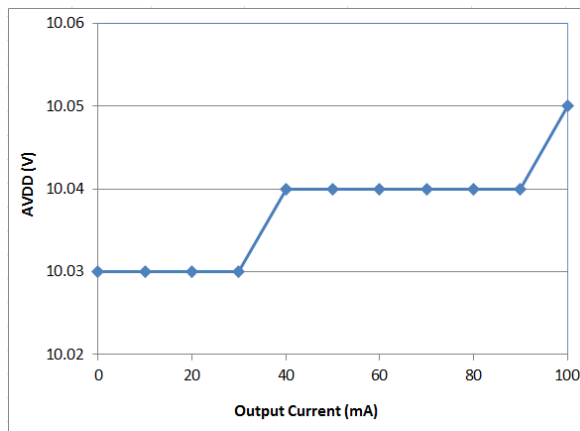


Figure 9 AVDD VS. IAVDD

Figure 10 shows the VGH voltage versus output current I_VGH.

Figure 11 shows the VGL voltage versus output current I_VGL.

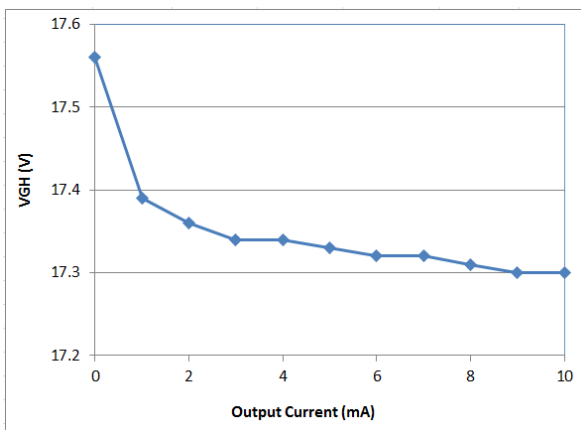


Figure 10 VGH VS. IGH

 


Figure 11 VGL VS. IGL

Figure 12 shows the efficiency versus load current I_{AVDD} ($I_{COM}=0$, $I_{VGH}=I_{VGL}=0$) at $V_{in}=3.3V$.

 


Figure 12 Efficiency VS. Load Current

5 Further Discussion

In this reference design, the output voltage V_{GH} is lower than twice of the $AVDD$ voltage, the output voltage V_{GL} is higher than $-AVDD$ voltage, so we can get the target V_{GH} and V_{GL} value with the charge pump circuit shown in figure 1. If an application needs a higher V_{GH} voltage, a positive charge pump tripler can be used to generate $3AVDD$. For a lower negative V_{GL} voltage requirement, a two-order charge pump inverter can be used to generate $-2AVDD$.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.