

Table of Contents:

History / Updates	page 1
Efficiency / losses at Vout set to 1.0V	page 2
Bode Plot	page 3
Step load & load dump response	pages 4
<i>Details of step load & load dump</i>	pages 5-6
Output ripple at 1.0V, 139A load & Start up	page 7
Thermal images: 160A & 132A load with airflow	pages 8-9
Main switching waveform	page 10

This design was tested at 210A peak and 160A steady state output current. For 4 phases that is 52.5A peak per phase. The TPS40428 only allows current fault threshold to be set at 50A. To avoid faults at or near max load, the current sense gain was increased from 500uOhms, the standard for CSD95378B Smart Power to 700uohms to make the TPS40428 think current was actually 30% less and avoid faults being triggered at or near peak loads.

The CSD95378B power stage is rated for up to 90A peak.

The TPS40428 controller current sense input is rated to 600mV max when operated in Smart Power mode. At the 50A threshold with 700uohms setting, the actual peak current will be 70A which is well under the CSD95378B max rating. The voltage on the TPS40428 controller current sense input will be this 70A times 5mV/A or 350mV, well within the 600mV limit.

For applications in which peak electrical current is 150A or less this current sense gain change is not needed. General “best practice” is to set current limit fault threshold at 130 to 150 percent of max application current.


Testing was done on model t1, which was then shipped to customer. Control was finalized afterwards to improve dynamic response, and tests in performance areas that could be affected by control loop were repeated on model t3 here and are shown in this report. They include Bode plot, step load & load dump response, output ripple and start up. Dynamic load tester was not changed. Hence, waveforms from model t1 were used for details of step load / load dump on pages 5 & 6.

Efficiency and Losses: **model t1**: 12Vin, Vout set at 1.0V
 Close in Vin & Vout senses, 12V 5" fan to give about 200 LFM or 1 M/S airflow

Vin Volts	Iin A	Vout Volts	Iout A	% Efficiency	Losses in W
12.06	0.039	off			
12.121	15.646	1.019	160.32	86.1	26.279
12.023	13.385	1.0183	138.84	87.9	19.547
12.05	12.61	1.018	132.04	88.5	17.534
12.035	11.37	1.0175	120.00	89.2	14.738
12.04	9.343	1.016	100.00	90.3	10.890
12.035	7.398	1.015	80.00	91.2	7.835
12.06	5.512	1.014	60.00	91.5	5.635
12.03	3.705	1.0125	40.00	90.9	4.071
12.05	1.900	1.011	20.00	88.3	2.675
12.01	1.027	1.011	10.00	82.0	2.224
12.07	0.178	1.010	0	0.0	2.148

Model t1:
 307kHz dropping to 305.5kHz when running at 160A and hot
 Current sense changed to 0.7mOhms from 0.5mOhms to allow >50A per phase:

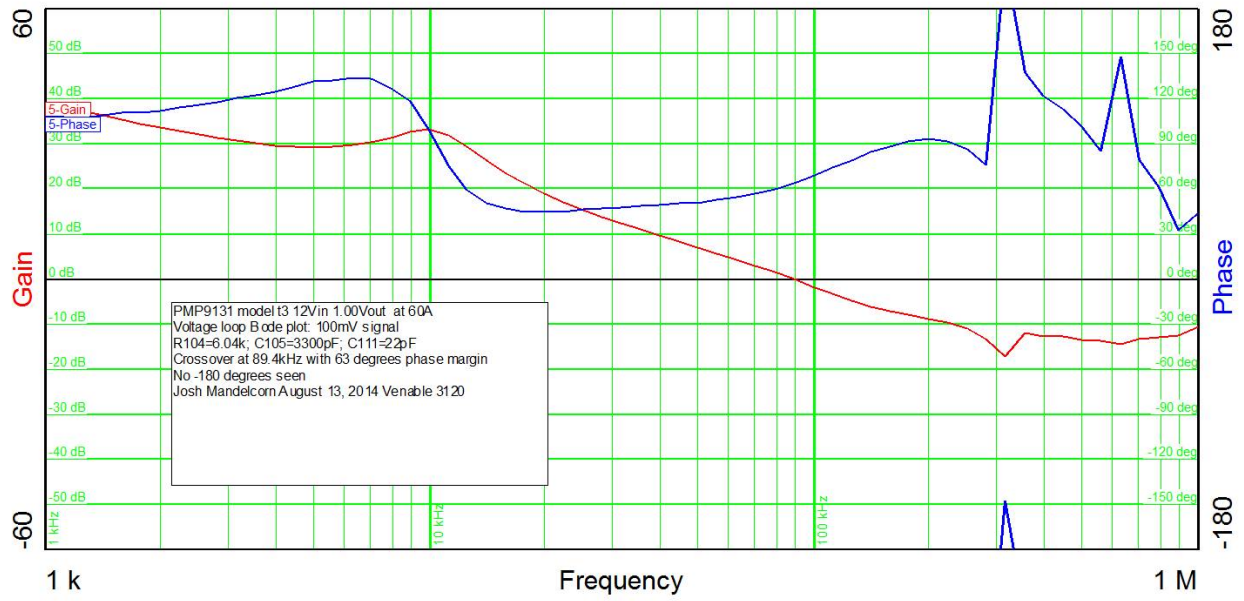
Bode plot of Voltage control loop 12Vin 1.0Vout at 60A: **model t3**



Model t3 with 210nH inductors and loop adjusted to 90kHz crossover: 1.0Vout
 Output caps: 10x 470uF 9mOhms plus 8x 100uF 6.3V 1210 sized ceramics
 The 75A static load is an external load bank, the 135A dynamic load is on the board. See page 4 of the schematic.


Step load response from 75A to 210A, a 135A step in ~ 10usec: 30mV peak undershoot

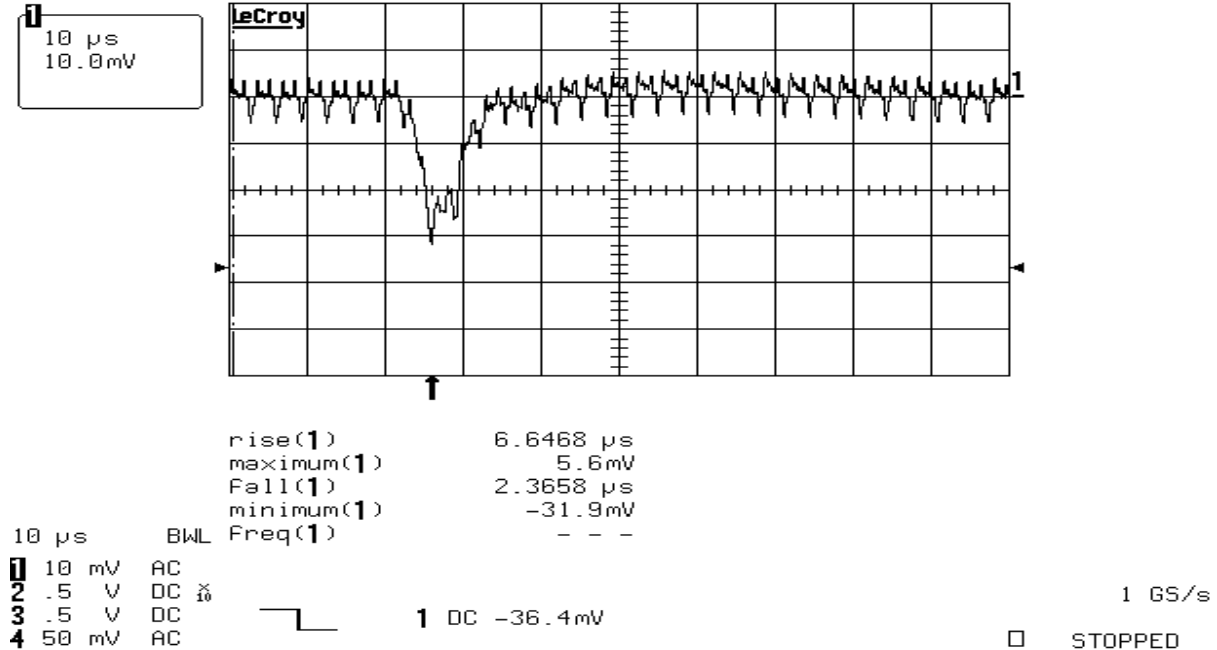13-Aug-14 Reading Floppy Disk Drive
 17:02:59



Load dump from 210A to 75A 12.0Vin; a 135A Dump in ~4usec 60mV overshoot


13-Aug-14
 17:05:34

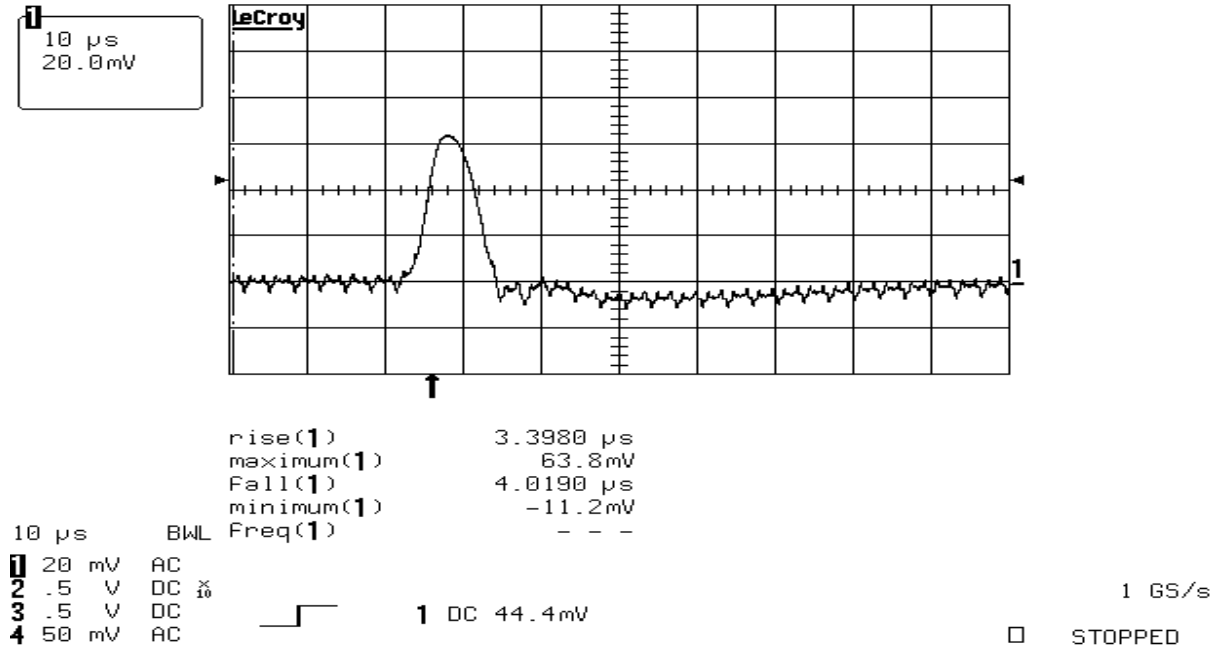

Waveforms across resistors in dynamic load bank used to calculate step load current and speed: There are two resistor paths from Vout; R302 and R301. Hence, the total load step is the sum of both. Here scope ground on Vout side of resistor.

Step load across 2mOhms R302 or 65A in all in about 10usec 1.0Vout model t1

17-Mar-14
16:59:16

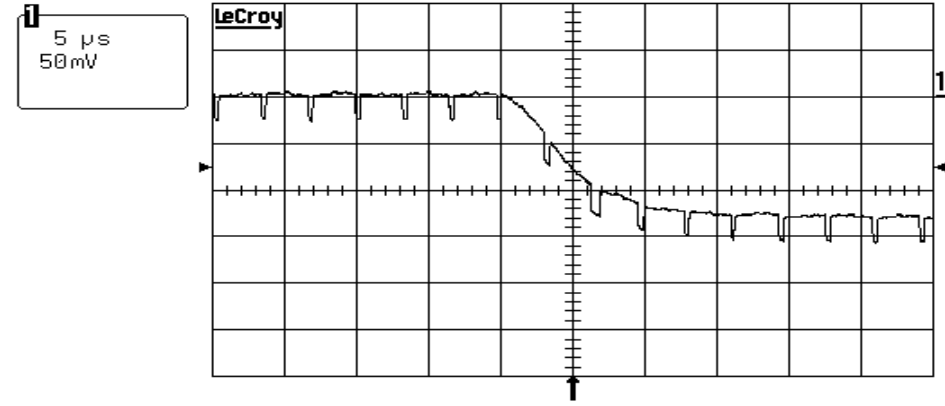

pkpk(1) 164.1mV
rms(1) 89.60mV
rise(1) - - -
Fall(1) 4.6854 µs
Freq(1) - - -

5 µs BWL
1 50 mV DC
2 50 mV AC
3 50 mV AC
4 50 mV AC



1 DC -74mV


1 GS/s

STOPPED

q

Step load across 2mOhms R301 or 70A in all in about 10usec

17-Mar-14
16:59:51

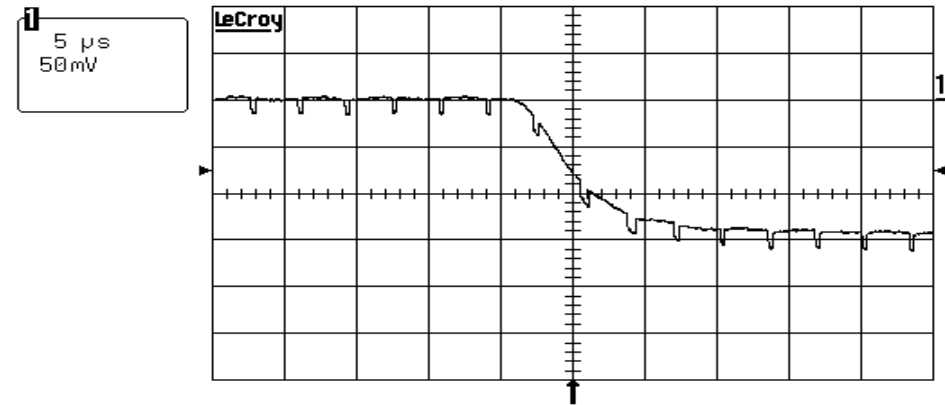

pkpk(1) 167.2mV
rms(1) 96.63mV
rise(1) - - -
Fall(1) 6.6643 µs
Freq(1) - - -

5 µs BWL
1 50 mV DC
2 50 mV AC
3 50 mV AC
4 50 mV AC



1 DC -74mV

1 GS/s


STOPPED

Load strings are in parallel driven by same FET: Hence, 135A in ~10usec

Waveforms across resistors in dynamic load bank used to calculate load dump current and speed: There are two resistor paths from Vout; R302 and R301. Hence, the total load dump is the sum of both. Here scope ground on Vout side of resistor.


Load dump across 2mOhms R302 or 65A in all in about 4usec 1.0Vout model t1

17-Mar-14
17:03:22

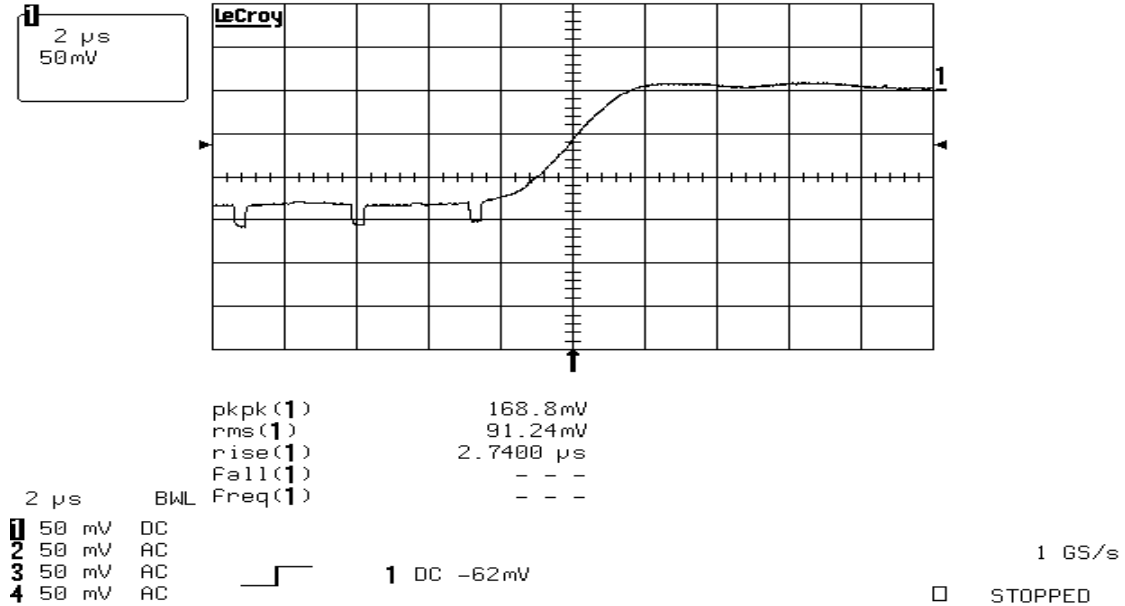

q Load dump across 2mOhms R301 or 70A in all in about 4usec


17-Mar-14
17:03:48

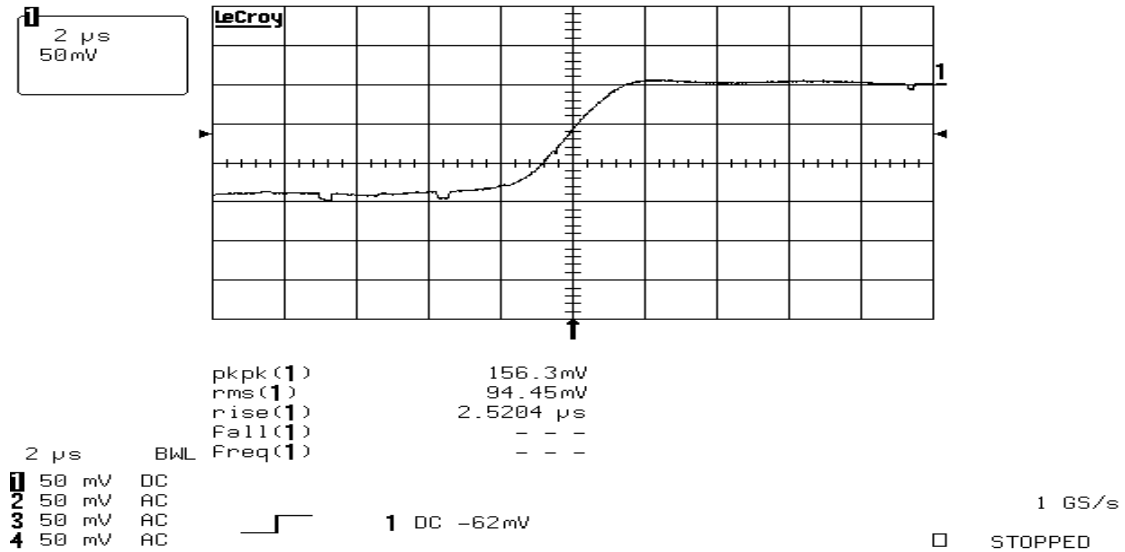

Load strings are in parallel driven by same FET: Hence, 135A in ~4usec

Output ripple at 12.0Vin and 139A off 1.0Vout at C128: **model t3** 7.2mV p-p 20MHz BW


13-Aug-14
17:08:30

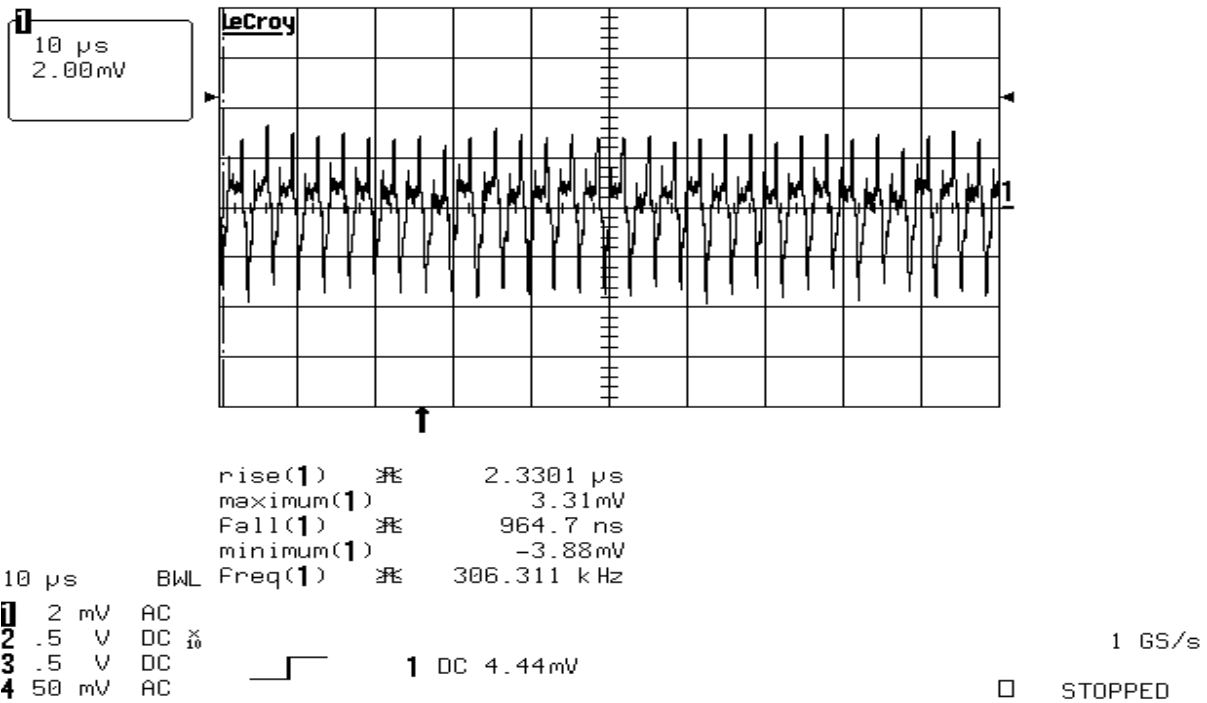

Qq

Start up with no pre bias: **model t3** 1.0Vout

13-Aug-14
17:13:06

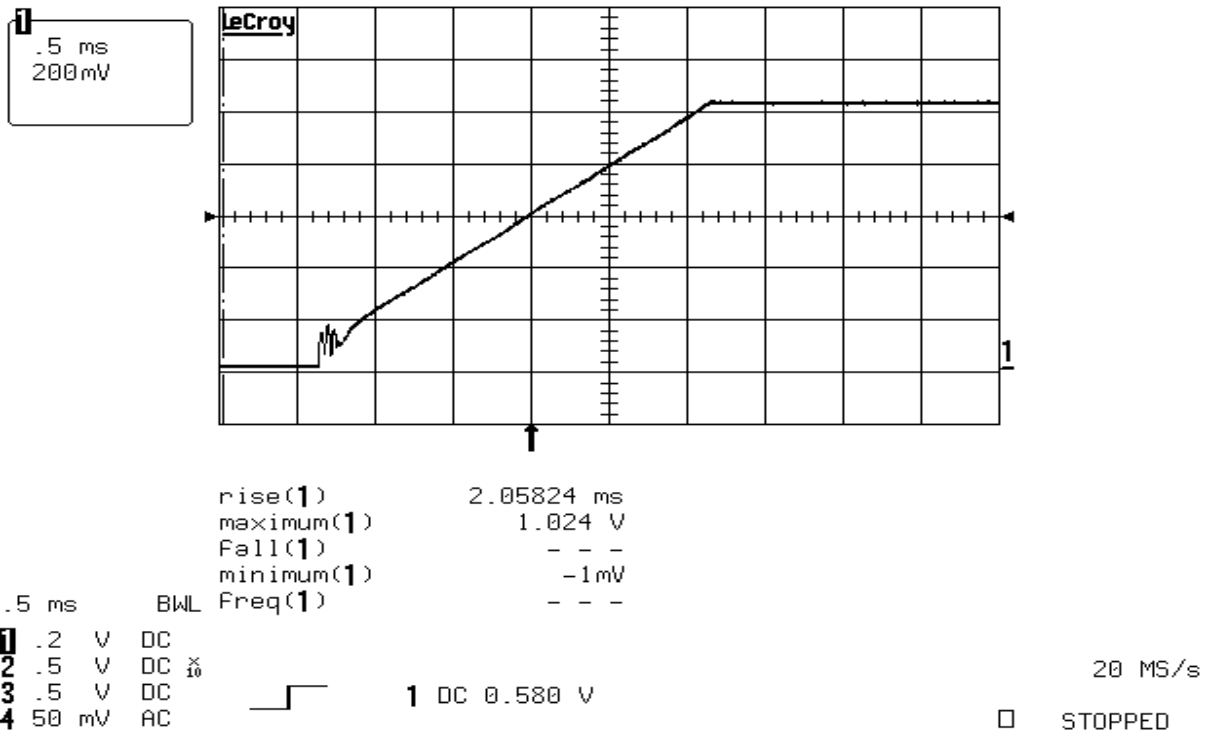

Thermal Image:

PMP9131 1.0V **160A** off 12.1Vin 305.5kHz / phase **model t1**

Strong 5" fan 12Vin 6" away on right side of model: 200 to 400 LFM estimated

Ambient ~22 deg. C; hotspot PWB path from third Q

Q Surfaces from fan & U102: 68; 74.5; 76.4; 71.7

Inductor tops 49, 53, 55, 54

Snubbers: 60, 69, 71, 68

Controllers TPS40428s 47 & 50



Qq

PMP9131 12Vin 1.0vout **132A** ~200 LFM airflow **model t1**: Lower current than previous page, but also slower fan speed to approximate 200 LFM. Fan is also to the right of model.

17.5W on PCB / assy

FETs & nearby PCB 58 to 62 degrees C

Inductor tops 48 to 50

Ambient 21-23 degrees C




Qq

Major waveforms: **model t1**

12vin load stepped from 45A to 180A & back. Scope trigger increased slowly to capture highest peak of 20.0V: channel 2 shown (U103 pin 6 VSW). Same 20V seen on channels 1 & 3. Channel 4 max was 19V.

18-Mar-14
20:07:44

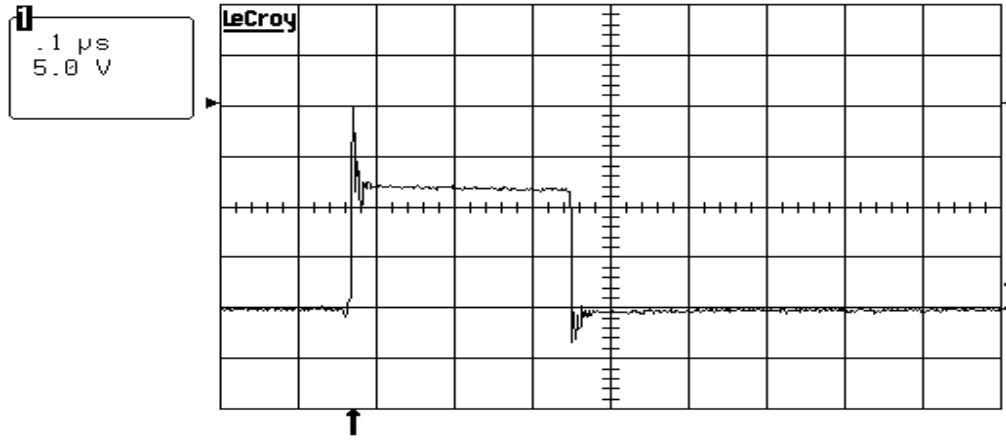

pkpk(1) 23.44 V
maximum(1) 20.00 V
rise(1) 2.1 ns
Fall(1) 1.8 ns
minimum(1) -3.44 V

.1 μs

1 .5 V DC $\tilde{\tilde{x}}$
2 50 mV AC
3 50 mV AC
4 50 mV AC




1 DC 20.4 V

1 GS/s

STOPPED

12Vin: load stepped from 75A to 210A & back. Scope trigger increased slowly to capture highest peak of 20.0V: channel 1 shown (U102 pin 6 VSW). Same 20V seen on channels 2 & 3. Channel 4 max was 19V.

18-Mar-14
20:17:43

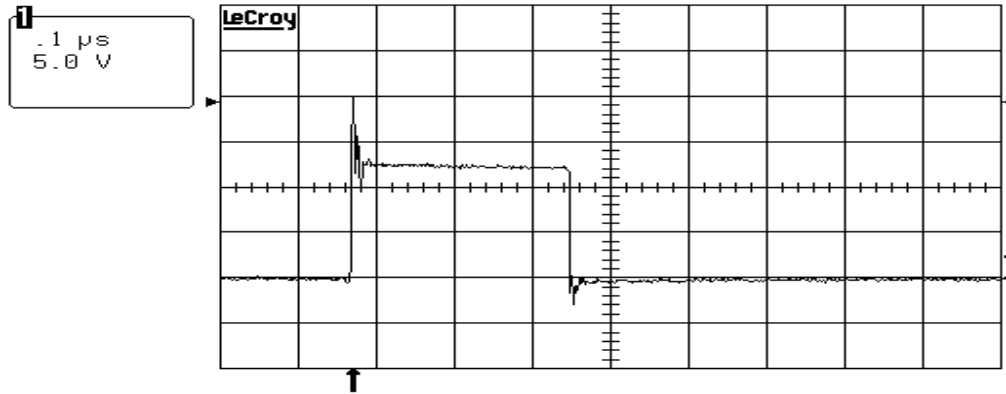

pkpk(1) 22.97 V
maximum(1) 20.00 V
rise(1) 2.0 ns
Fall(1) 2.0 ns
minimum(1) -2.97 V

.1 μs

1 .5 V DC $\tilde{\tilde{x}}$
2 50 mV AC
3 50 mV AC
4 50 mV AC



1 DC 19.4 V

1 GS/s

STOPPED

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.