

Design Considerations

TIDA-00503 Automotive LED Backlight 2P/4P-3S and 4P-2S SEPIC Design

Design

The TIDA-00503 is a reference design using the LP8861-Q1 LED driver in a SEPIC configuration used to drive 2, 3, or 4 parallel strings of 3 or 2 LEDs in series. The LED driver operates at a switching frequency of 2.2MHz for a smaller overall footprint and all components are limited to <3mm in height.

A standard LP8861-Q1 SEPIC EVM was modified and used along with a LED load board to generate the test report. The original design used a coupled inductor that did not meet the desired 3mm maximum height requirement and was replaced by two smaller single inductors. The switching frequency and maximum output voltage resistor settings were updated and the aluminum electrolytic input and output capacitors were replaced with lower profile ceramic capacitors.

Inductor Selection:

The TIDA-00503 reference design has a maximum height limitation of 3mm. For this reason, two single inductors were used vs a coupled inductor to provide the best tradeoffs to meet the height restriction.

“Power Stage Designer™ Tools” can be used for the SEPIC inductance calculation:
<http://www.ti.com/tool/powerstage-designer>.

Setting the switching frequency:

The LP8861-Q1 can operate at any switching frequency between 250kHz and 2.2MHz. The TIDA-00503 uses a higher switching frequency to enable the use of smaller passive components with the tradeoff of slightly lower system efficiency. Solving the equation below with $f_{sw} = 2.2\text{MHz}$ and choosing the closest standard value, $R_{FSET} = 24\text{k}\Omega$.

$$f_{sw} = 67600 / (R_{FSET} + 6.4)$$

Where:

f_{sw} – switching frequency, kHz

R_{FSET} – frequency setting resistor, k Ω

Choosing the maximum output voltage:

Maximum output voltage should be chosen based on the maximum voltage required for the LED strings. It is recommended that the maximum voltage is about 30% higher than the maximum LED string voltage. The LEDs used in our design have a maximum voltage of 3.4V. For 3 series LED/string configuration we designed our maximum output voltage to be $(3 * 3.4V) * 1.3 = 13.26V$. And from the equation below, we can solve for $R1 = 249\text{k}\Omega$.

$$V_{\text{MAX BOOST}} = \left(\frac{V_{\text{BG}}}{R2} + 0.0387 \right) \times R1 + V_{\text{BG}}$$

Where:

$$V_{\text{BG}} = 1.2\text{V}$$

R2 recommended value is 130 k Ω

Resistors values are in k Ω

Higher output currents:

The maximum LED current per string in a 4-channel application is 100mA/ch. In applications requiring fewer channels and higher currents, the LP8861-Q1's outputs can be tied together to drive higher current. In our application, for 2 parallel strings with 200mA/string, we tied OUT1 to OUT2 and OUT3 to OUT4.

Layout Guidelines

Here are some main points from the LP8861-Q1 IC datasheet to help the PCB layout work:

- Current loops need to be minimized:
 - For low frequency the minimal current loop can be achieved by placing the boost components as close to the SW and PGND pins as possible. Input and output capacitor grounds need to be close to each other to minimize current loop size
 - Minimal current loops for high frequencies can be achieved by making sure that the ground plane is intact under the current traces. High frequency return currents try to find route with minimum impedance, which is the route with minimum loop area, not necessarily the shortest path. Minimum loop area is formed when return current flows just under the “positive” current route in the ground plane, if the ground plane is intact under the route
- GND plane needs to be intact under the high current boost traces to provide shortest possible return path and smallest possible current loops for high frequencies
- Current loops when the boost switch is conducting and not conducting needs to be on the same direction in optimal case
- Inductor placement should be so that the current flows in the same direction as in the current loops. Rotating the inductor 180° changes current direction
- Use separate power and noise free grounds. Power ground is used for boost converter return current and noise free ground for more sensitive signals, like LDO bypass capacitor grounding as well as grounding the GND pin of LP8861-Q1 itself.
- Boost output feedback voltage to LEDs need to be taken out “after” the output capacitors, not straight from the diode cathode.
- LDO 1 μF bypass capacitor as close to the LDO pin as possible
- Input and output capacitors need strong grounding (wide traces, many vias to GND plane)
- If two output capacitors are used they need symmetrical layout to get both capacitors working ideally
- Output ceramic capacitors have DC-bias effect. If the output capacitance is too low, it can cause boost to become instable on some loads and this increases EMI. DC bias characteristics need to

be obtained from the component manufacturer; it is not taken into account on component tolerance. X5R/X7R capacitors are recommended.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.