

Traction Inverters – A Driving Force Behind Vehicle Electrification



Audrey Dearien
Applications manager
Isolated gate drivers

Krunal Maniar
Product marketing engineer
Isolated precision ADCs

VC Kumar
Marketing manager
Sitara™ processors

Waqar Mehmood
Marketing manager
C2000™ real-time microcontrollers

The careful design of traction inverters for hybrid electric vehicles (HEVs) and electric vehicles (EVs) can help enable faster motor speeds, higher efficiency and a smaller system size while maintaining power density. New technologies allow automakers to create the vehicle of the future with longer range and optimum performance.

At a glance

Traction inverter design trends and relevant semiconductor technologies and components are discussed in depth.

1 **Exploring EV traction inverter design trends**

Understand the trends currently enabling high-performance, efficient and reliable traction inverter systems.

2 **Driving efficiency with fast current-sensing feedback loops and high-speed controllers**

Learn why the current-sensing feedback loop has such an effect on vehicle speed and performance.

3 **How gate drivers and bias supplies can support increased EV ranges**

Silicon carbide (SiC) metal-oxide semiconductor field-effect transistors (MOSFETs) and high voltages, when paired with the right components, improve the EV driving experience.

Exploring EV traction inverter design trends

A traction inverter converts battery energy into power that controls torque and speed, giving it the most influence over an EV's range, performance and driving experience. Torque is proportional to motor size, while

power provides torque and speed. Keeping power constant, if you want to reduce the motor size and torque, you need to increase the speed. This is a challenge, as component sizes typically increase with power level and torque, especially if there are design inefficiencies such as losses from mechanical or electrical nonidealities. It becomes important, then, to reduce not only the size of the motor, but also the electrical system to the traction inverter itself.

In order to extend driving range and reduce motor size and weight without compromising the power level, a traction motor needs to be able to run at higher speeds (>30,000 rpm). This requires fast sensing and processing, as well as the efficient conversion of DC to AC voltages. To achieve these goals, traction inverter design trends include using advanced control algorithms, employing SiC MOSFETs for the switching transistors in the power stage, using high-voltage 800-V batteries and integrating multiple subsystems to obtain high power densities.

Driving efficiency with fast current-sensing feedback loops and high-speed controllers

One way to improve the EV driving experience, which includes steady cruise control, responsive acceleration and deceleration, and a quieter cabin experience, is to improve the overall accuracy and reliability of the current-sensing feedback loop. This control loop is the pathway that the sensed currents take from the output of the traction inverter's phases, back through isolated precision amplifiers and through the microcontroller

(MCU) for processing. This journey finally results in the signals that come back to the control output of the traction inverter. Optimizing the motor-control loop enables fast and precise feedback so that the motor

can react quickly to changes in speed or torque. The highlighted portion in **Figure 1** shows the motor-control loop.

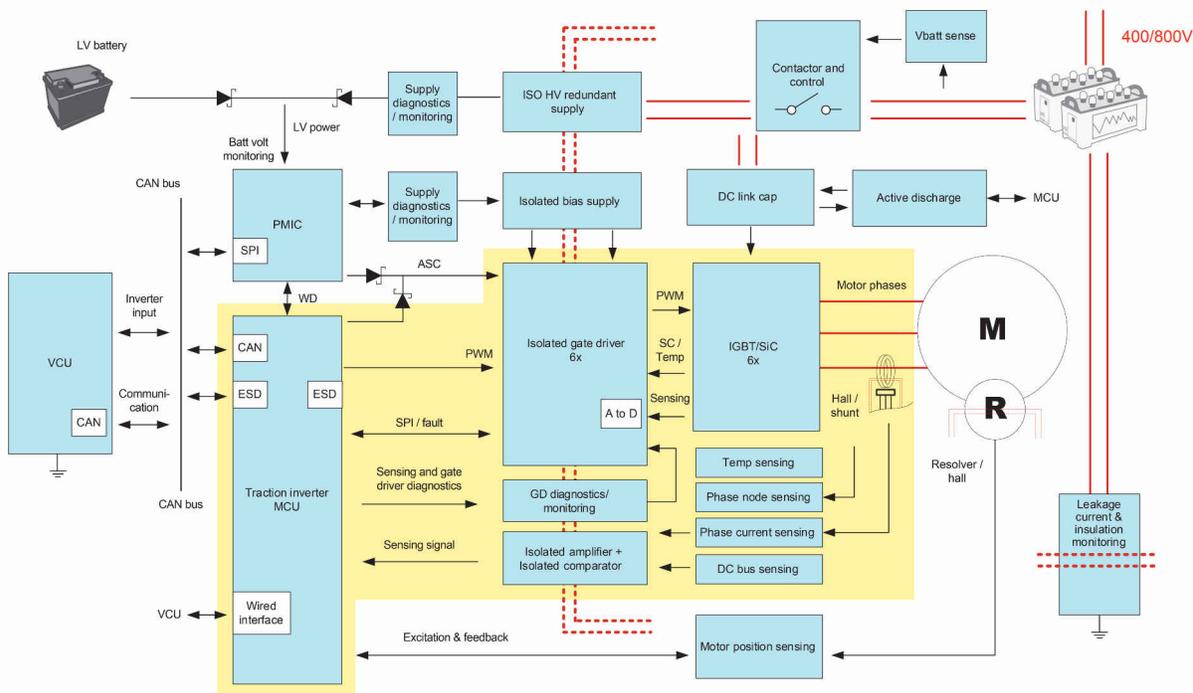


Figure 1. Traction inverter block diagram, with the motor-control loop and power stage highlighted in yellow.

As detailed in **Figure 2**, isolated semiconductor components typically isolate the power and control circuits in a traction inverter. Three isolated amplifiers or modulators measure motor currents through a shunt resistor and feed the signals to an MCU’s algorithm for field-oriented control (FOC). The need to increase motor speeds requires a higher-bandwidth current-sensing feedback loop, which means that the in-phase current must generate a modified inverter output as quickly as possible. The latency of the current-sensing feedback loop is a priority, especially because power transistor switching frequencies (the insulated gate bipolar transistors [IGBTs]/SiC MOSFETs in **Figure 1**) are increasing to tens of kilohertz, and control signals must change the pulse width, cycle by cycle, in order to enable a high rotational speed. Noise generated by high currents also affects loop reliability.

Given that the isolated amplifiers are positioned right next to the source of noise, it is important that they operate reliably, with minimal noise interference between the power and control circuits. This is why galvanically isolated amplifiers that offer high transient noise immunity between the power ground and signal ground are necessary in the current-sensing loop. With proper component selection, an accurate current-sensing loop can limit the harmonic distortion of the three current phases to support smooth motor speed and torque control during acceleration and braking conditions. The accuracy of the current-sensing loop also helps prevent electrical losses and minimizes vibrations while driving. Isolated amplifiers such as the **AMC1300B-Q1** and **AMC1311B-Q1** and isolated modulators such as the **AMC1306M25** and **AMC1336** support accurate current and voltage measurements with over 200 kHz of bandwidth along with latency of less

than 2 μs and galvanic isolation with common-mode transient immunity (CMTI) over 100 $\text{kV}/\mu\text{s}$.

The MCU must take the given three-phase current measurements through an analog-to-digital converter (ADC) to quickly digitize the measurements and feed through the main algorithm to generate pulse-width modulation (PWM) for the traction inverter's output. The FOC algorithm often used in motor-control designs requires complex math, such as fast Fourier transform (FFT) and trigonometric operations. This leads to high processing bandwidth requirements, especially for switching frequencies of 20 kHz and more.

It is important to distribute the power loads of the MCU so that it can handle both the motor control

and safety functions for the traction inverter. A high-speed FOC implementation enables more headroom to the power and processing capability within the MCU to process both motor control and functional safety features. Real-time MCUs such as the C2000™ [TMS320F28377D](#), [TMS320F28386D](#), [TMS320F280039C](#) and Sitara™ [AM2634-Q1](#) effectively provide fast control-loop performance, with help from a >3-MSPS ADC for sensing and processing power from multiple optimized cores to perform complex control math quickly. Tightly integrated high-resolution PWMs for actuation help generate precise duty cycles for optimized motor control. When optimized for traction inverters, these stages (ADC input, FOC algorithm execution and PWM write) combine to achieve <4- μs control-loop latency.

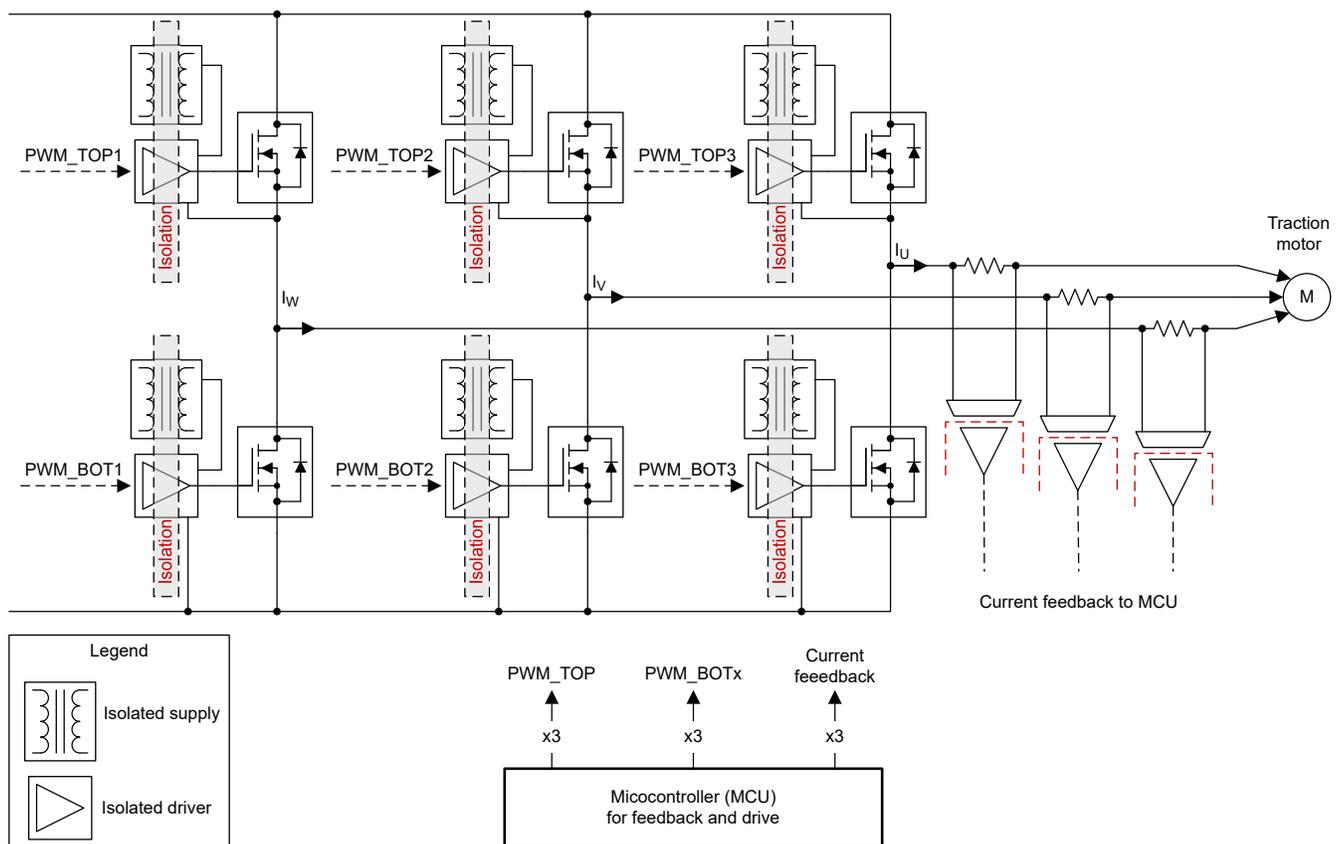


Figure 2. The current-sensing feedback loop in a traction inverter.

How gate drivers and bias supplies can support increased EV ranges

The control signals generated by the MCU and the current-sensing loop are fed to the power stage, which is the link between the battery and the motor. The power stage comprises a high-voltage DC bus decoupled by a large capacitor bank tied to three phases of power transistors, such as IGBTs or SiC MOSFETs. The power stage should have minimal power losses when translating the DC voltage to AC and be small in size in order to use the battery efficiently, which increase a vehicle's driving range. This is a challenge, however, since components with increased voltage and power are naturally larger. Fortunately, technological breakthroughs have made it possible to keep the same component size for higher power levels.

Two factors influence traction inverter size: the type of high-voltage transistor and the voltage level of the battery. SiC MOSFETs have lower switching losses and a smaller die size when compared to IGBTs with the same voltage rating, which is why some engineers are using SiC MOSFETs in their traction inverter designs. When SiC transistors are controlled properly, they operate with

fewer losses and higher reliability across all conditions in which the inverter operates, such as temperature, speed and torque, to enable increased driving ranges.

While SiC MOSFETs are more efficient, like any transistor they will experience some power loss when switching, and those switching losses can impact the efficiency of the traction inverter. The edges of voltage and current during the switching transients overlap and generate power losses, as shown in **Figure 3**. A high gate-driver output current results in the fast charge and discharge of the SiC FET gate to enable low power loss. It is not always the best idea to switch as fast as possible, however, given variations in switch behavior over temperature, current and voltage. The fast transitions of voltage across a SiC FET, namely the transient voltages (dv/dt) of the drain-to-source voltage (V_{DS}), generate voltage overshoot and electromagnetic interference (EMI) in the form of conducted ground currents. The motor itself can suffer from high dv/dt given the potential for short circuits in the capacitance between the windings. Gate-driver circuitry can control both power losses and switching transients.

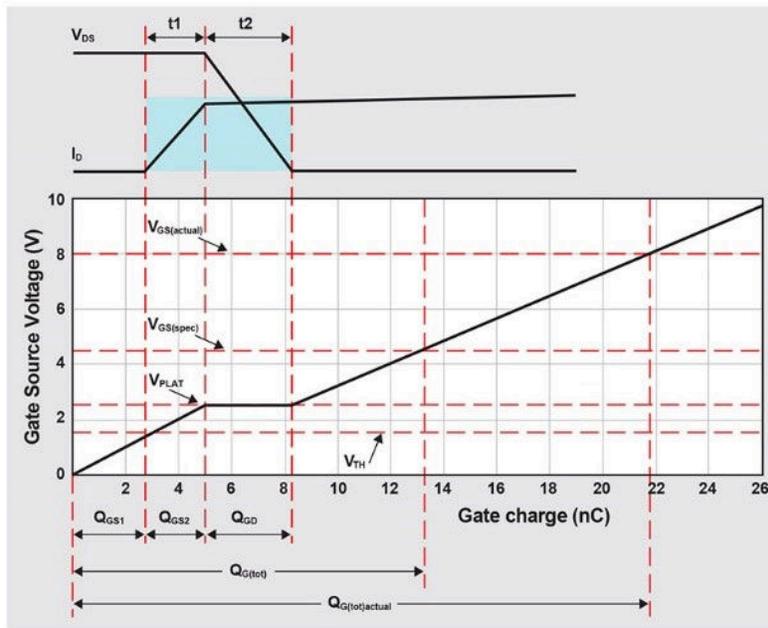


Figure 3. Turn-on charging profile of a MOSFET and resulting switching losses caused by V_{DS} and I_D overlap.

Using gate resistance to control the gate driver's output source and sink current helps optimize the trade-off between dv/dt and power losses. **Figure 4** shows an implementation of a gate driver with an adjustable output drive strength to optimize for changes in SiC MOSFET slew rates across temperature and current.

Adjustability is beneficial to traction inverter performance because it enables lower EMI and lower losses, resulting in higher efficiency that helps increase driving ranges. Because TI's **UCC5870-Q1** and **UCC5871-Q1** gate drivers have 30-A drive strength, it is very easy to implement an adjustable gate-drive solution based on changing and optimizing the gate resistance. In addition, their galvanic isolation and 100-kV/ μ s CMTI enable ease of use in high-voltage applications using fast-switching SiC technologies.

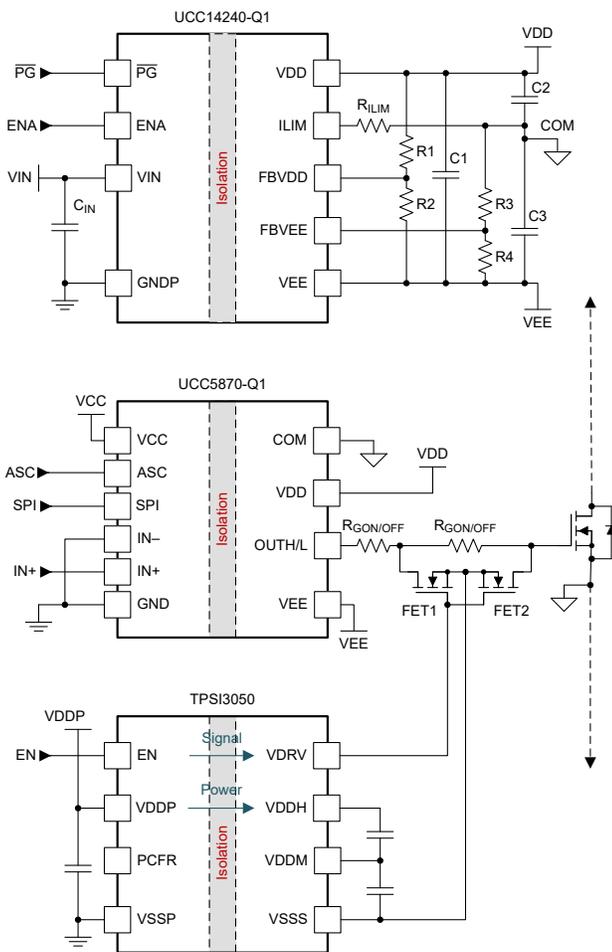


Figure 4. Block diagram of an adjustable gate-driver output circuit using the UCC5870-Q1, powered by the UCC14240-Q1.

The voltage level of the battery also influences the amount of dv/dt present in the system, and creates challenges when designers need to minimize EMI and choose components that can meet isolation safety standards while maintaining the same power density and area. SiC MOSFETs support high breakdown voltages $>1,200$ V in small die sizes, which enables a power-dense solution for 800-V EV battery applications.

Supporting the gate voltage requirements for high-voltage SiC MOSFETs becomes challenging when the power supply needs isolation and good regulation. The impact of the gate voltage is evident from the current-voltage characteristic curve of a SiC MOSFET, shown in **Figure 5**, where a higher gate-to-source voltage (V_{GS}) results in a steeper curve in its linear region. A steeper curve means a lower drain-to-source on-resistance ($R_{DS(on)}$) to minimize conduction losses and avoid thermal runaway.

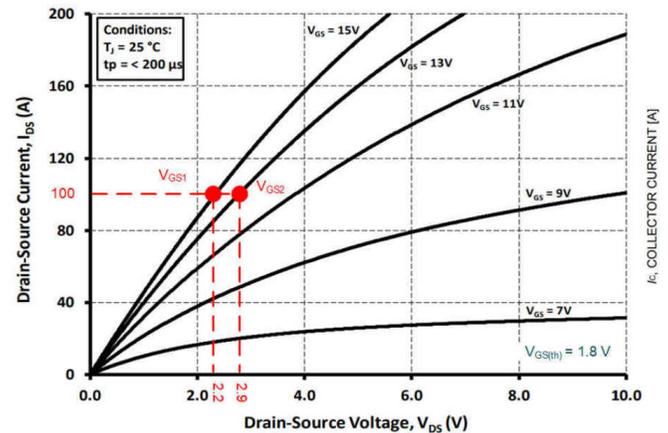


Figure 5. SiC MOSFET voltage and current characteristics based on the V_{GS} .

The isolated bias supply that provides power and voltage to the gate driver should maintain a proper positive gate voltage during fast transients and be able to support negative voltages to keep the SiC FET safely off. Transformers with semiconductor switching controllers are often used to generate isolated power supplies. Their complex design, however, directly impacts the performance of the power stage from both the electrical efficiency and EMI perspectives.

The interwinding capacitance results in higher common-mode currents that lead to the generation of EMI where lower capacitance is necessary, but trade-offs between size, voltage ratings and efficiency require more time to design.

With integrated power modules such as the UCC14241-Q1 and UCC1420-Q1, the primary-to-secondary isolated capacitance can be well controlled at <3.5 pF, enabling a CMTI of >150 V/ns for fast-switching SiC MOSFETs. HEV/EV subsystem design is trending toward further integration, such as combining the traction inverter with a DC/DC converter. The UCC14241-Q1 can achieve an approximately 40% smaller bill-of-materials (BOM) area than a typical bias supply solution with a flyback converter, as shown in **Figure 6**. The height compared to the discrete transformer design is substantially lower, leading to a lower center of gravity and a higher vibration tolerance. All of these factors contribute to the reliability and longevity of traction inverter systems, while providing the correct voltages to efficiently drive the power transistors.

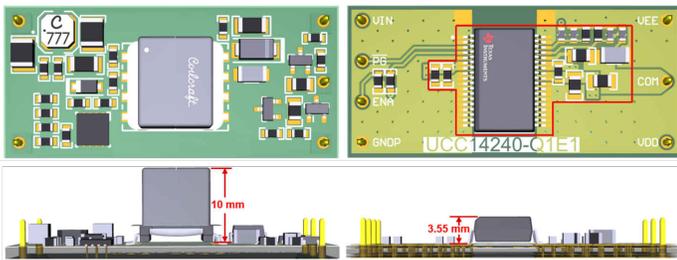


Figure 6. BOM area and height comparison between typical a flyback converter bias solution and the UCC14240-Q1.

Conclusion

EVs are driving technology innovations across the board, from processing to power semiconductors. Motor control and powertrain designs have a direct influence on EV ranges and driving performance. The combination of accurate current sensors and smart MCUs with real-time control are able to help reduce latency and improve the accuracy of the motor-control loop, enabling smooth speed and torque transitions. With reduced harmonics distortion, the electrical efficiency and range

improve; so do motor vibrations, which help prevent an uncomfortable drive.

Traction inverter power density and efficiency enabled by the adoption of SiC MOSFETs and 800-V technology allow the integration of various powertrain functions and ultimately increased range per charge. TI's wide portfolio of integrated semiconductor technologies enable flexibility for automakers and Tier-1 suppliers to achieve high performance and low cost.

Learn more about traction inverter technology:

- The [High-Voltage Traction Inverter](#) landing page on TI.com.
- [ASIL D Safety Concept-Assessed High-Speed Traction, Bidirectional DC/DC Conversion Reference Design](#).
- The [Automotive SPI-Programmable Gate Driver and Bias Supply with Integrated Transformer Reference Design](#).

Learn more about TI products for traction inverter systems:

- [C2000](#) real-time MCUs.
- The [AM2634-Q1](#) Arm® Cortex®-R5F MCU.
- The [UCC5870-Q1](#) advanced, programmable isolated gate driver.
- [UCC14240-Q1](#) DC-DC modules with integrated transformers.
- Texas Instruments: [AM263x for Traction Inverters](#).
- Texas Instruments: [AM263x Benchmark and Analysis for Traction Systems](#).

Other contributors to this paper include:

- Han Zhang, Systems engineer
- Sean Murphy, Product marketing engineer
- Robert Martinez, Systems engineer
- Dongbin Hou, Systems engineer
- Francisco Lauzurique, Applications engineer

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

Arm® and Cortex® are registered trademarks of Arm Limited (or its subsidiaries) in the US and/or elsewhere.
All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated