

# LMV822,LMV932

*A Quick Sine Wave Generator*



Literature Number: SNOA839

## Technology Edge

### A Quick Sine Wave Generator

By Walter Bacharowski, Amplifier Applications Engineer

In various design and test situations, a sine wave signal with an arbitrary frequency may be needed. The following design, and [accompanying Excel spreadsheet](#) implement a sine wave generator that can be quickly assembled with a dual op amp and small number of resistors and capacitors. Figure 1 shows the schematic for the quick sine wave generator:

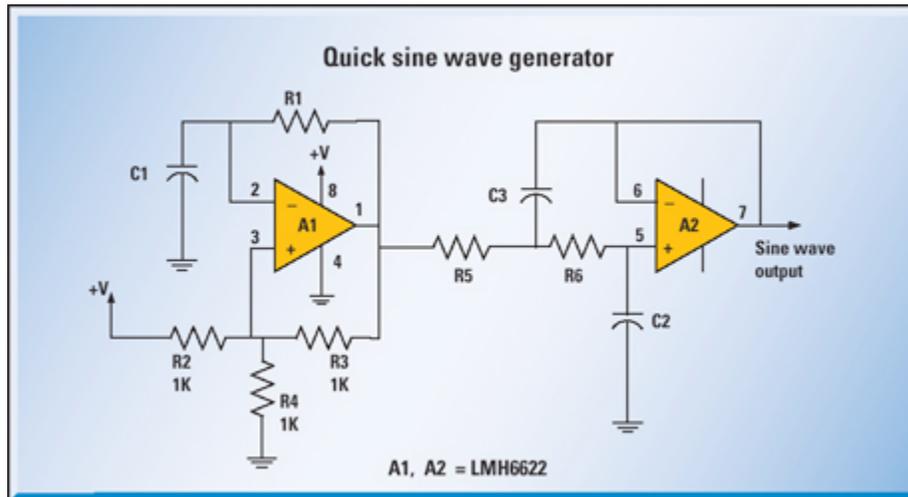


Figure 1

This circuit generates a sine wave by first generating a square wave, at the required frequency, with amplifier A1 that is configured as an astable oscillator with the frequency determined by R1 and C1. The two-pole low pass filter, using A2, filters the square wave output from A1. The filter is a unity gain Sallen-Key filter with its cut off frequency equal to the square wave frequency from A1. The square wave is made up of the fundamental frequency and the odd harmonics of the fundamental frequency. The filter removes most of the harmonic frequencies and the fundamental frequency remains at the output of A2. The fundamental frequency component of a square wave is about 1.27 times the peak amplitude of the square wave and the amplitude of the sine wave output will be approximately 87 percent of the peak of the square wave. The peak of the square wave will depend on the amplifier's supply voltage and the output swing specification of the amplifier. Additionally, the peak of the square and the sine wave will track changes in the amplifier's supply voltage.

In this design, the frequency is specified along with the value of C1 and based on these values, the values of R1, C2, C3, R4, and R5 are calculated. The values of R2, R3 and R4 are 1K Ohms and should be matched in value to help minimize errors in the actual frequency of operation compared to the calculated frequency of operation.

The equations for the component selection follow. The frequency, F, is the required sine wave frequency. The value for C1 is selected arbitrarily, with a value of 0.001  $\mu$ fd being a good initial value for 1 MHz. The other component values are calculated as follows:

$$C2 = C1$$

$$C3 = 2C1$$

$$R1 = \frac{1/2 F}{.693 \cdot C1}$$

$$R6 = R5$$

$$R5 = \frac{1}{8.8856 \cdot F \cdot C1}$$

An [Excel speed sheet is available online](#) that will calculate the component values given the frequency and C1. The spreadsheet will also give the nearest 1% resistor values to the calculated resistor values. Given that the required frequency is 1 MHz and C1 is 0.001 µfd, the following is an example of the spreadsheet results:

Frequency =	1000000		Calculated value	Nearest 1% resistor value
C1 =	0.001			
		R1 =	721.5	715
		C3 =	0.002	
		R5 = R6 =	112.5	113

$$F = 1 \text{ MHz}$$

$$C1 = 0.001 \text{ } \mu\text{fd}$$

$$C2 = 0.001 \text{ } \mu\text{fd}$$

$$C3 = 0.002 \text{ } \mu\text{fd}$$

$$R1 = 715\Omega$$

$$R5 = 113\Omega$$

$$R6 = 113\Omega$$

The accuracy of the actual frequency of operation, compared to the calculations, will be dependent on the tolerance of the components used around amplifier A1. The tolerance of the component value used around A2 will affect the filter's pole locations and will affect the amplitude of the filtered sine wave.

The Excel spreadsheet will calculate component values given the frequency required and the value of C1 and is easy to use. Enter the frequency, in Hz, in cell B2 and enter the capacitance of C1 in µfd, in cell B4. The other component will be calculated with the resistance in Ohms and the capacitance in µfd.

The characteristics of the amplifier selected will also affect the range of component values selected. In the example, a high-speed amplifier is being used and the resistor values should be kept low (below about 15 K W) to minimize the effects of the input bias currents of this type of amplifier. High-bandwidth amplifiers will need power supply bypass capacitors and component layout may affect performance. If a lower frequency oscillator is required, a lower bandwidth amplifier such as the [LMV822](#) or [LMV932](#) could be used. The lower input bias currents of these devices will work with a wider range of resistor values and component placement is not as critical. The bandwidth of the amplifier should be at least 10 times the

frequency of oscillation. Assembling the circuit using the calculated component values has the following performance, see Figure 2:

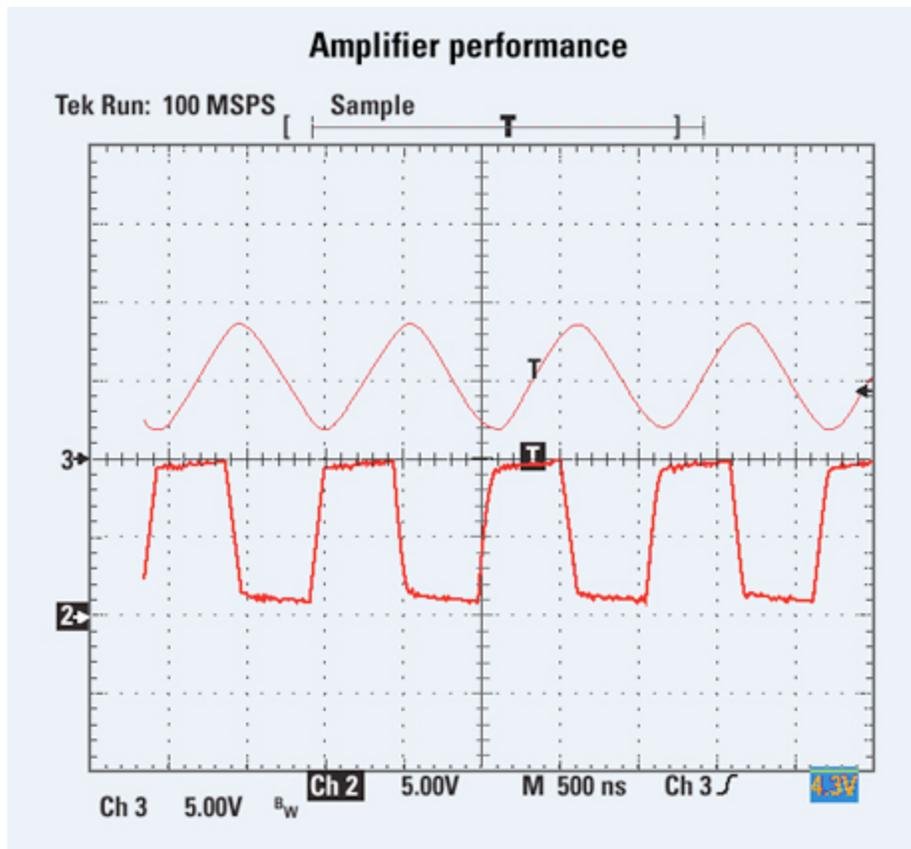


Figure 2  
Oscillator Output (Pin1) and Sine Wave Output (Pin7) Waveforms

For more information visit the [Amplifiers Featured Community](#)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated