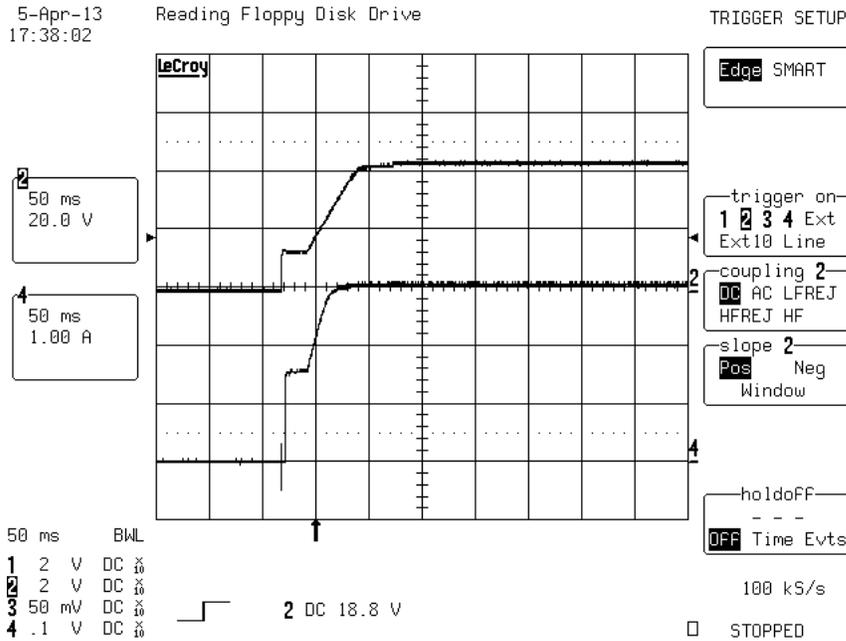


1 Startup

The startup waveform for the 44 volts is shown in the figure below. The input is 14 volts. The lower trace is the load current




2 EFFICIENCY

Vin	Iin	Pin	Vout	Iout	Pout	efficiency
14	3.36	47.04	44.1	1	44.1	93.75
14	6.7	93.8	44.1	2	88.2	94.02985
14	9.95	139.3	44.1	3	132.3	94.97487
14	13.34	186.76	44.1	4	176.4	94.45277
14	16.55	231.7	44.1	5	220.5	95.16616
14	19.9	278.6	44.1	6	264.6	94.97487
14	23.1	323.4	44.1	7	308.7	95.45455

3 Load step response

9-Apr-13
17:30:37

Reading Floppy Disk Drive

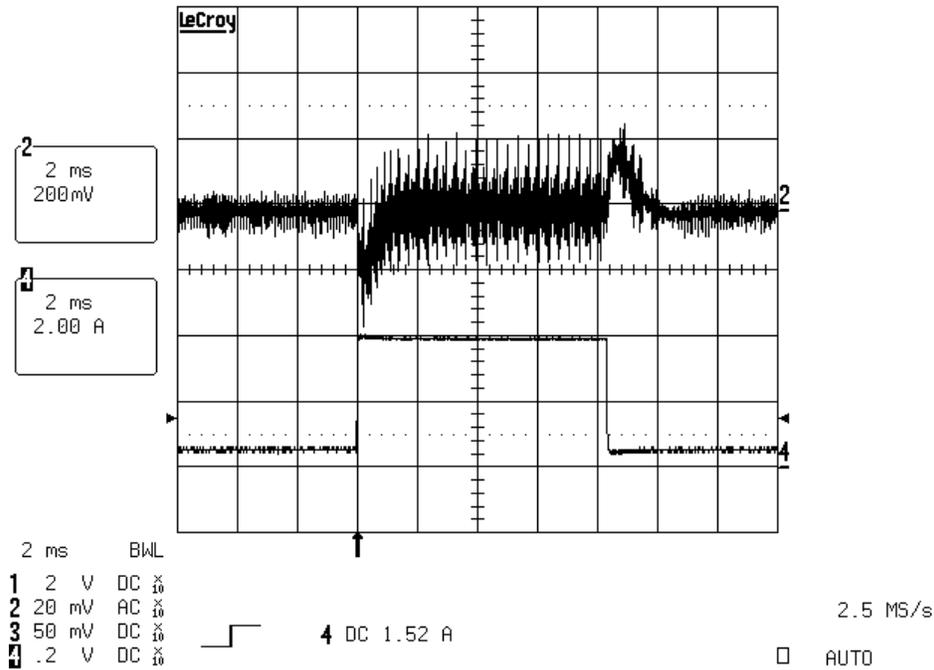


The bottom trace is a output current step, and top is the 44 volt output response.

4 Input voltage turn on and over voltage

Under voltage lock out is 8 volts and over voltage lock out is 17.8 volts.
Note that these values can be adjusted using R3,R12,R7,R11.

4 Drain wave forms

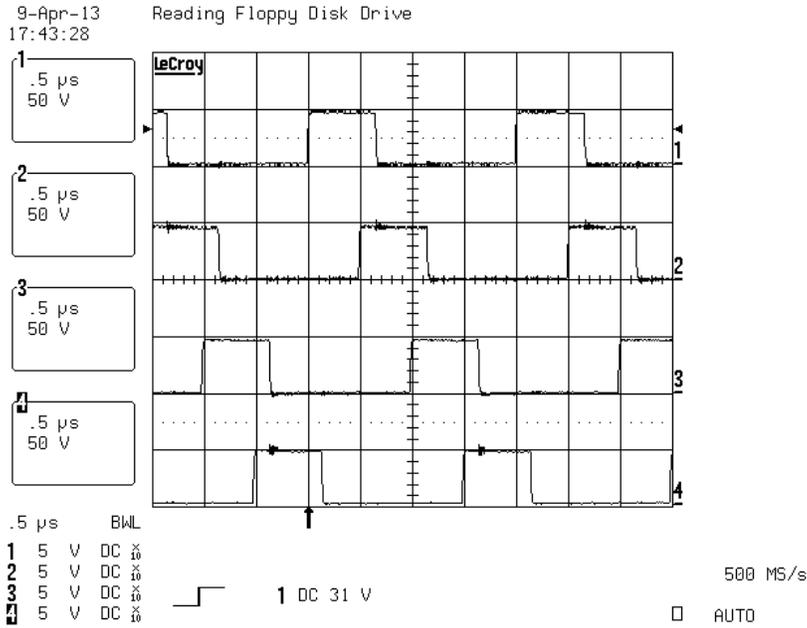

The four FET drains at 4 amp load

4/09/13


PMP9637 Test Results

5 Output ripple

9-Apr-13
17:49:54

Reading Floppy Disk Drive

1
.5 μ s
100mV

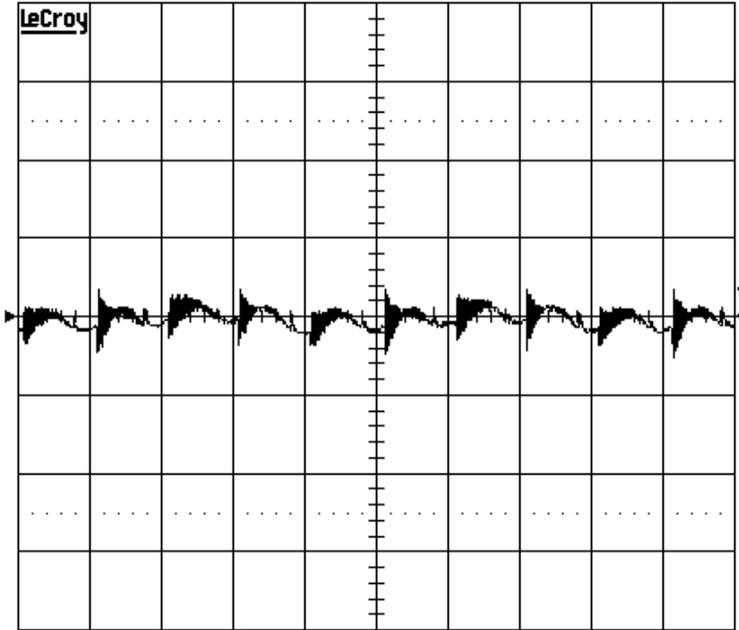

.5 μ s BWL

- 1** 10 mV AC \times $\frac{10}{10}$
- 2** 5 V DC \times $\frac{10}{10}$
- 3** 5 V DC \times $\frac{10}{10}$
- 4** 5 V DC \times $\frac{10}{10}$




1 DC 2mV


500 MS/s

STOPPED

6 Power Supply Rejection

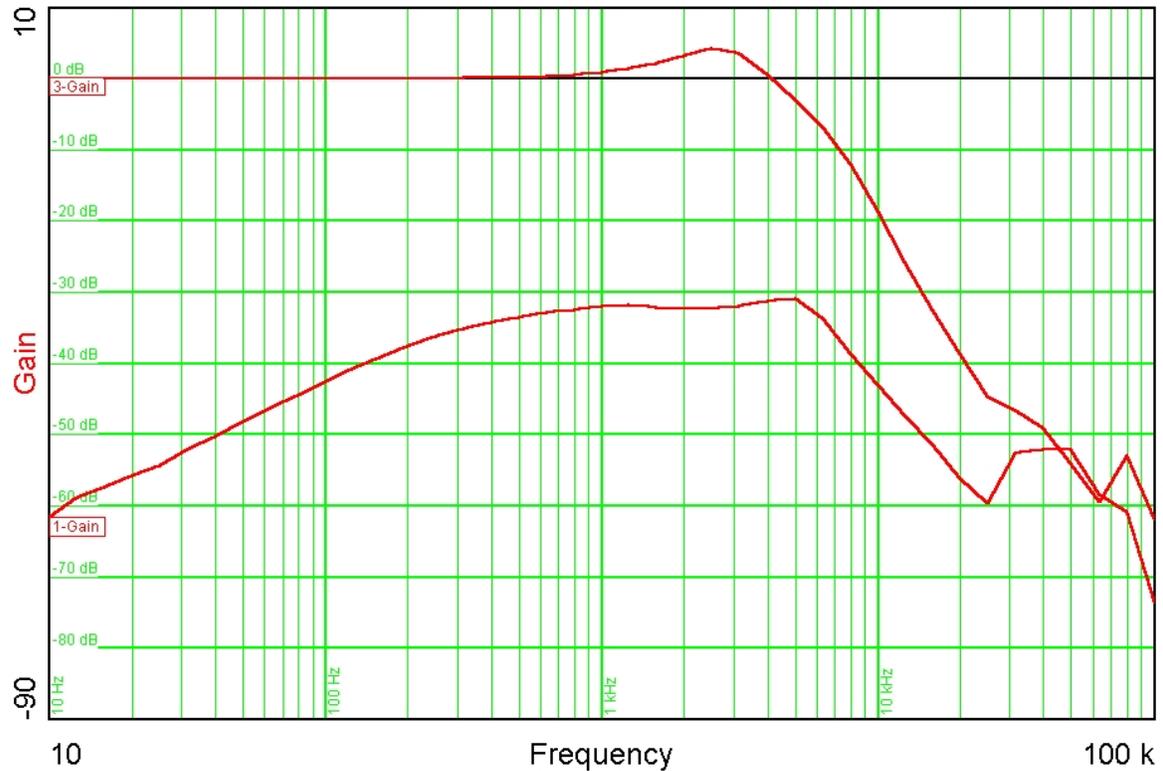

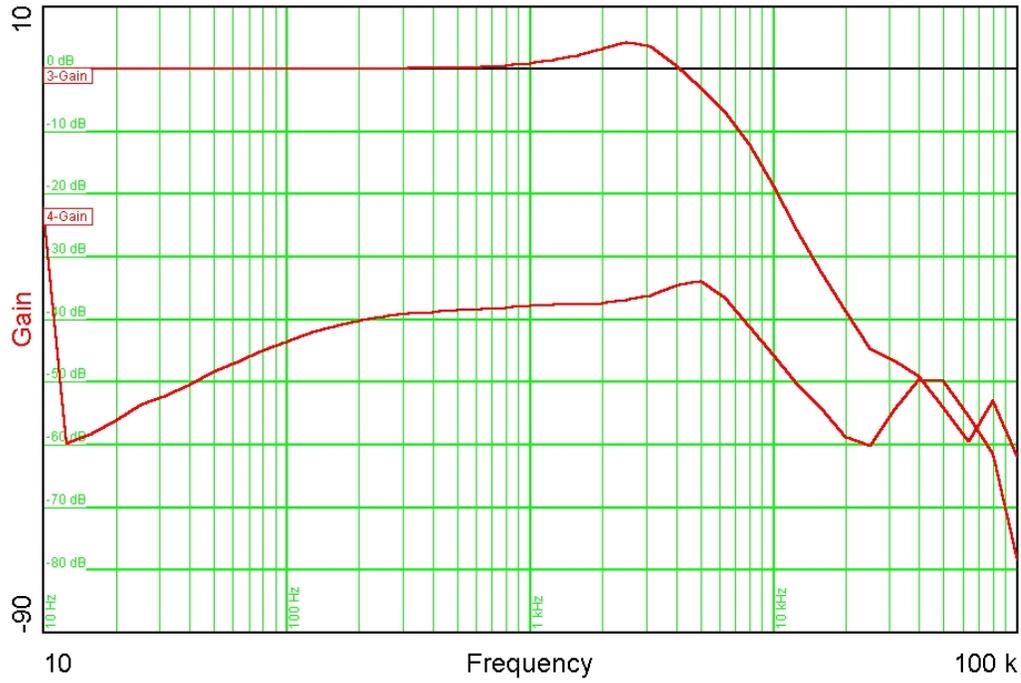The top trace is the output /input with the boost disabled, which shows no power supply rejection except at higher frequencies due to the attenuation of the output filter. The bottom trace is the output/ input with the boost operating.




This is the same as above except that I increased the mid-band loop gain by 6 db, which resulted in a 6 db improvement in power supply rejection.

4/09/13

PMP9637 Test Results

7 Photo

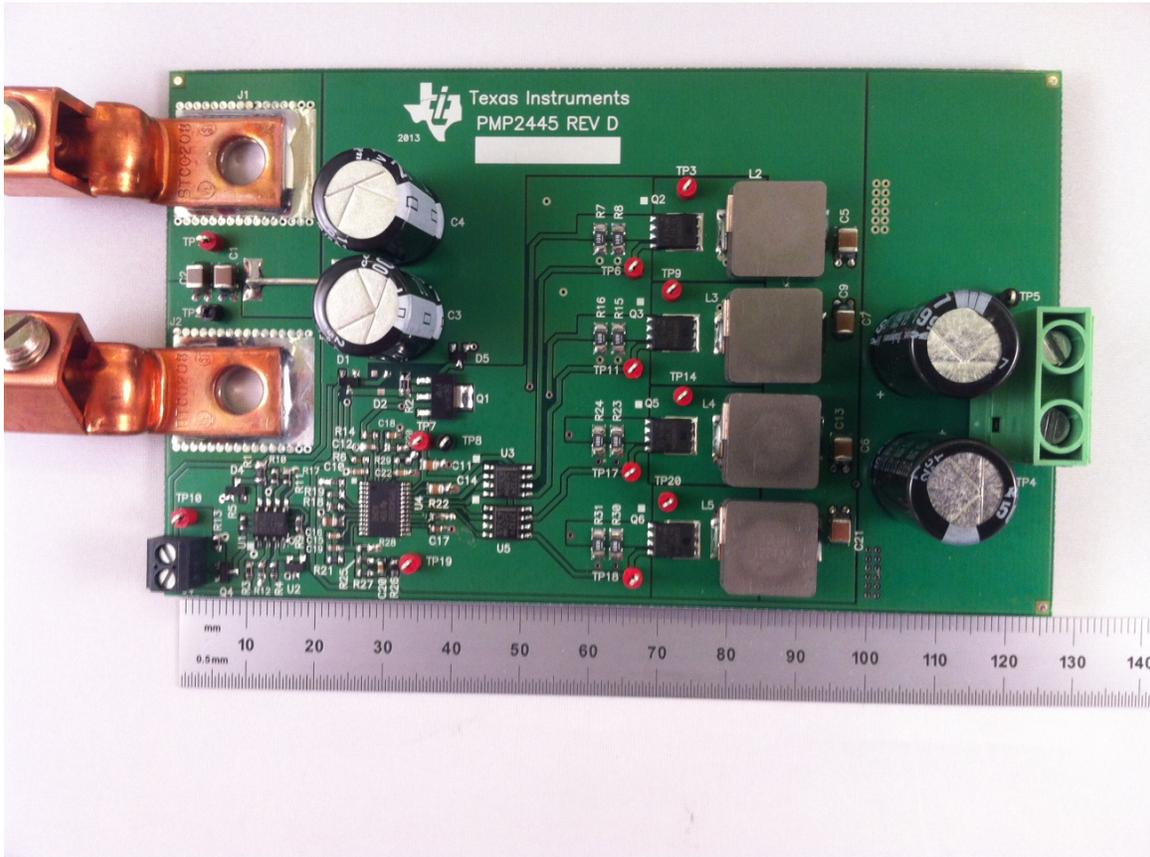

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated