

3 ways to close the control loop for totem-pole bridgeless PFC



Bosheng Sun

Introduction

Among all power factor correction (PFC) topologies, totem-pole bridgeless PFC provides the best efficiency; therefore, it is widely used in servers and data centers. However, closing the current control loop of a continuous conduction mode (CCM) totem-pole bridgeless PFC is not as straightforward as it is for a traditional PFC. A traditional PFC operating in CCM employs an average current-mode controller [1], as shown in Figure 1, where V_{REF} is the voltage-loop reference, V_{OUT} is the sensed PFC output voltage, G_V is the voltage loop, V_{IN} is the sensed PFC input voltage, I_{REF} is the current-loop reference, I_{IN} is the sensed PFC inductor current, G_I is current loop, and d is the duty ratio of pulse-width modulation (PWM). Since the bridge rectifier is used in a traditional PFC, all these values are positive, and current feedback signal I_{IN} is the rectified input current signal.

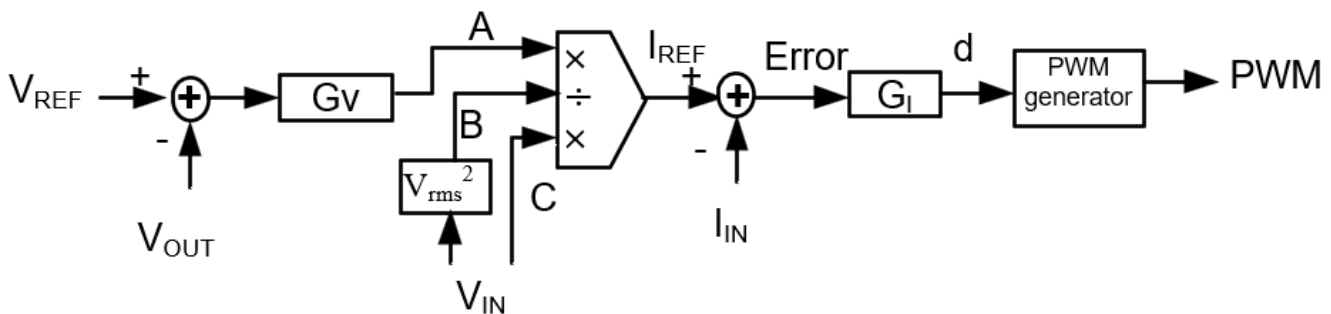


Figure 1. Average current-mode controller for PFC where all the parameters listed have positive values and I_{IN} is the rectified input current signal. Source: Texas Instruments

New feedback signal

Since the inductor current in the totem-pole bridgeless PFC is bidirectional, the current-sense method used in traditional PFC will not work. Instead, you will need a bidirectional current sensor such as Hall-effect sensor to sense the bidirectional inductor current and provide a feedback signal to the control loop.

The output of the Hall-effect sensor will not 100% match the sensed current, though. For example, if the sensed current is a sine wave, then the output of the Hall-effect sensor is a sine wave with a DC offset, as shown in Figure 2. Thus, you can't use it as the feedback signal in the current-mode controller shown in Figure 1, and you will have to modify the controller to accommodate this new feedback signal. In this power tip, I'll describe three ways to close the current control loop with this new feedback signal.

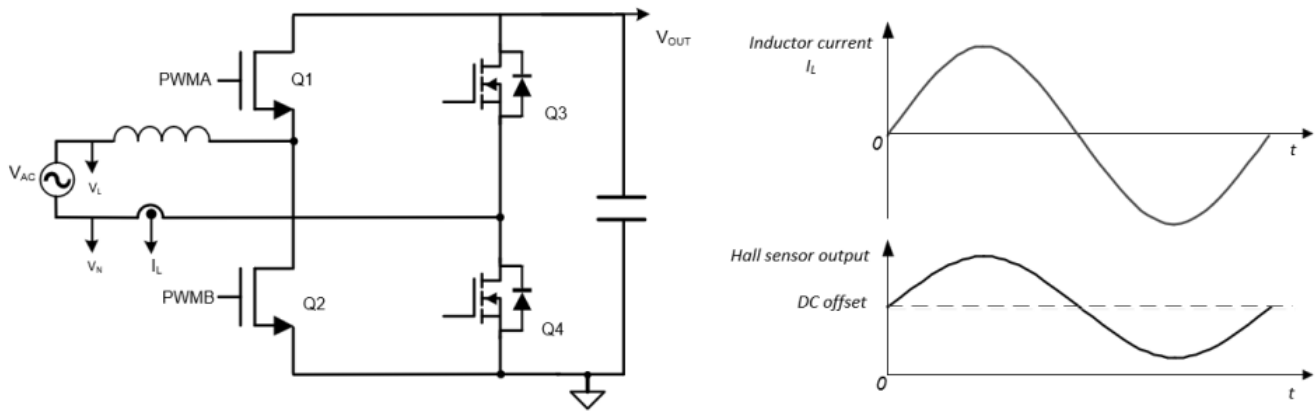


Figure 2. Totem-pole bridgeless PFC and its current-sense signal showing that the Hall-effect sensor output will not 100% match the sensed current. Source: Texas Instruments

Method 1: Controllers without a negative loop reference

Some digital controllers, such as the [UCD3138](#) from Texas Instruments (TI), use a hardware state machine to implement the control loop; therefore, all of the input signals to the state machine must be greater or equal to zero. In such cases, follow these steps to close the current control loop:

1. Sense the AC line and AC neutral voltage through two analog-to-digital-converters (ADCs) separately.
2. Use firmware to rectify the sensed V_{AC} signal, as shown in Equation 1 and [Figure 3](#).

$$\begin{aligned} &\text{if } (V_L > V_N) * V_{IN} = V_L - V_N \\ &\text{else } V_{IN} = V_N - V_L \end{aligned} \quad (1)$$

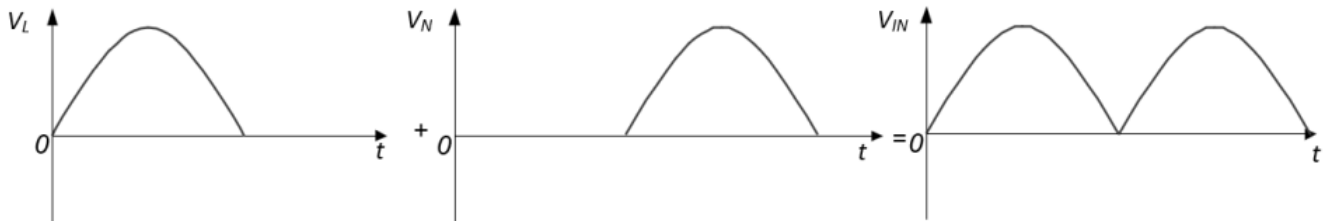


Figure 3. Using the firmware shown in Equation 1 to rectify the sensed input voltage V_{AC} . Source: Texas Instruments

3. Calculate the sinusoidal reference, V_{SINE} , using the same method as when calculating I_{REF} in traditional PFC, as shown in Equation 2 and [Figure 4](#).

$$V_{SINE} = \frac{G_V \times V_{IN}}{V_{IN_RMS}^2} \quad (2)$$

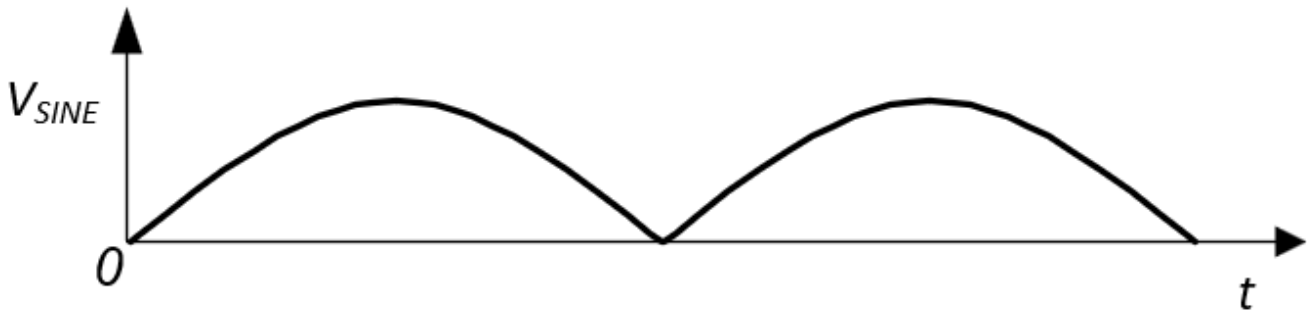


Figure 4. Calculating a sinusoidal reference (V_{SINE}) using the same method as when calculating I_{REF} in traditional PFC. Source: Texas Instruments

4. Use a Hall-effect sensor output as the current feedback signal I_{IN} directly (Equation 3).

$$I_{IN} = \text{Hall-effect sensor output} \quad (3)$$

5. During the positive AC cycle, if you compare the shape of V_{SINE} and the Hall-effect sensor output, they have the same shape. The only difference is the DC offset. Use Equation 4 to calculate the current-loop reference, I_{REF} .

$$I_{REF} = V_{SINE} + \text{DC offset} \quad (4)$$

6. The control loop has standard negative feedback control. Use Equation 5 to calculate the error that goes to the control loop:

$$\text{Error} = I_{REF} - I_{IN} \quad (5)$$

7. During the negative AC cycle, if you compare the shape of V_{SINE} and the Hall-effect sensor output, the difference is not only the DC offset; their shapes are opposite as well. Use Equation 6 to calculate the current-loop reference, I_{REF} .

$$I_{REF} = \text{DC offset} - V_{SINE} \quad (6)$$

8. During the negative AC cycle, the higher the inductor current, the lower the value of the Hall-effect sensor output. The control loop needs to change from negative feedback to positive feedback. Use Equation 7 to calculate the error going to the control loop.

$$\text{Error} = I_{IN} - I_{REF} \quad (7)$$

Method 2: A pure firmware-based controller

For a pure firmware-based digital controller such as the TI C2000 microcontroller, the control loop is implemented with firmware, which means that the internal calculation parameters can be positive or negative. In such cases, follow these steps to close the current control loop:

1. Sense the AC line and AC neutral voltage through two ADCs. Then use the line voltage to subtract the neutral voltage to obtain V_{IN} , as shown in Equation 8 and [Figure 5](#).

$$V_{IN} = V_L - V_N \quad (8)$$

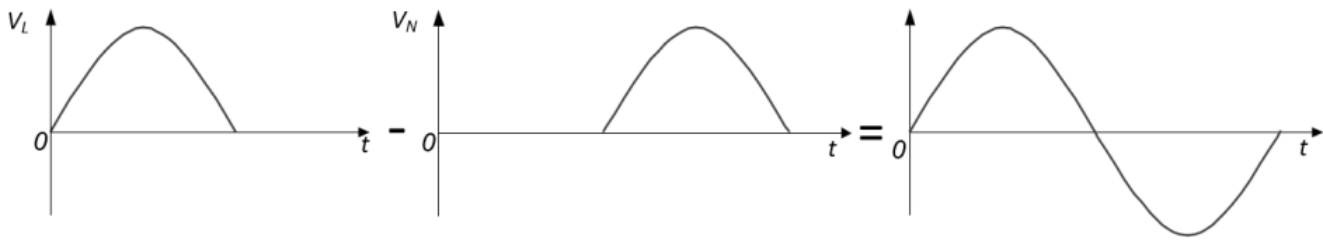


Figure 5. Calculating V_{IN} after using the line voltage to subtract the neutral voltage. Source: Texas Instruments

- Calculate the sinusoidal current-loop reference, I_{REF} , using the same method as in traditional PFC, as shown in Equation 9 and Figure 6.

$$I_{REF} = \frac{G_V \times V_{IN}}{V_{IN_RMS}^2} \quad (9)$$

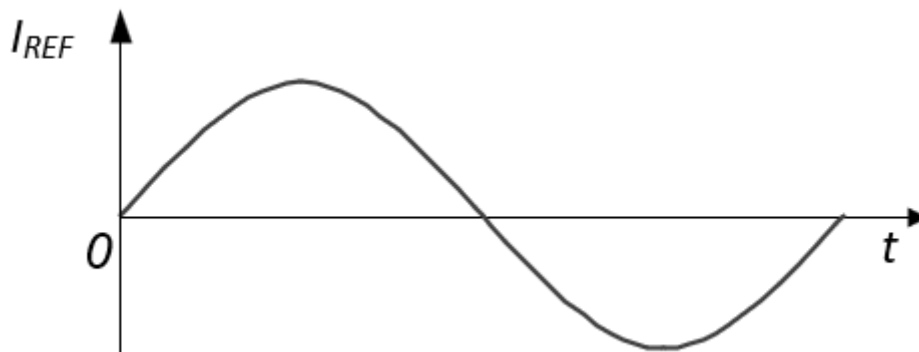


Figure 6. Calculating I_{REF} using the same method as the traditional PFC. Source: Texas Instruments

- If you compare the shape of I_{REF} and the Hall-effect sensor output, they have the same shape; the only difference is the DC offset. Use Equation 10 to calculate the input current feedback signal, I_{IN} . Figure 7 shows the waveform.

$$I_{IN} = \text{Hall sensor output} - \text{DC offset} \quad (10)$$

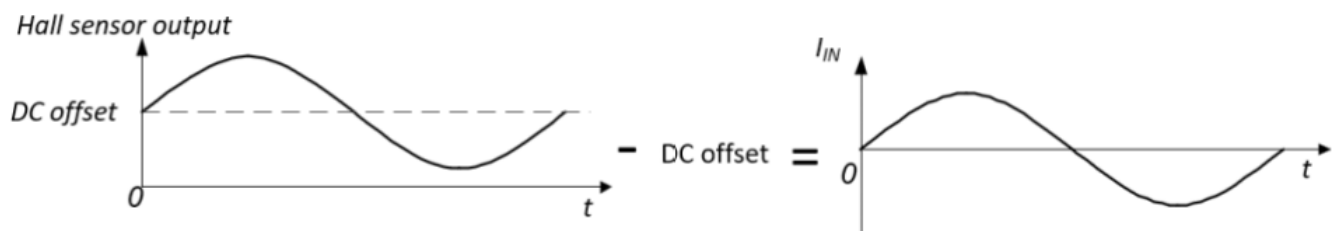


Figure 7. The waveform of the Hall sensor output and DC offset to calculate I_{IN} . Source: Texas Instruments

- During the positive AC cycle, the control loop has standard negative feedback control. Use Equation 11 to calculate the error going to the control loop:

$$\text{Error} = I_{REF} - I_{IN} \quad (11)$$

- During the negative AC cycle, the higher the inductor current, the lower the value of the Hall-effect sensor output; thus, the control loop needs to change from negative feedback to positive feedback. Use Equation 12 to calculate the error going to the control loop.

$$Error = I_{IN} - I_{REF} \tag{12}$$

Method 3: Duty-ratio feedforward control

Total harmonic distortion (THD) requirements are becoming stricter, especially in server and data-center applications. Reducing THD necessitates pushing the control-loop bandwidth higher and higher. High bandwidths reduce phase margins, resulting in loop instability. The limited PFC switching frequency also prevents bandwidths from going very high. To solve this problem, you can add a precalculated duty cycle to the control loop to generate PWM; this is called duty-ratio feedforward control (d_{FF}) [2], [3].

For a boost topology operating in CCM mode, Equation 13 calculates d_{FF} as:

$$d_{FF} = \frac{V_{OUT} - V_{IN}}{V_{OUT}} \tag{13}$$

This duty-ratio pattern effectively produces a voltage across the switch whose average over a switching cycle is equal to the rectified input voltage. A regular current-loop compensator changes the duty ratio around this calculated duty-ratio pattern. Since the impedance of the boost inductor at the line frequency is very low, a small variation in the duty ratio produces enough voltage across the inductor to generate the required sinusoidal current waveform so that the current-loop compensator does not need to have a high bandwidth.

Figure 8 depicts the resulting control scheme. Adding the calculated d_{FF} to the traditional average current-mode control output, d_I , results in the final duty ratio, d , used to generate the PWM waveform to control PFC.

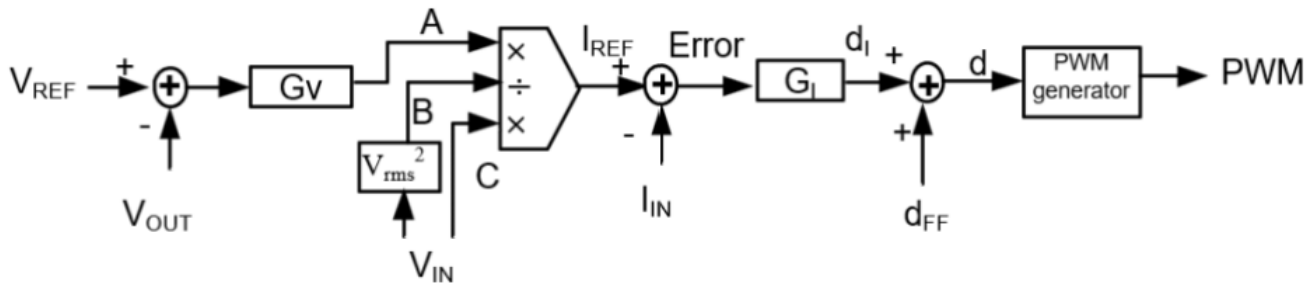


Figure 8. Duty-ratio feedforward control for PFC where adding the calculated d_{FF} to the traditional average current-mode control output, d_I , results in the final duty ratio, d , used to generate the PWM waveform to control PFC. Source: Texas Instruments

To leverage the advantages of d_{FF} in a totem-pole bridgeless PFC, follow these steps to close the current loop:

1. Follow steps 1, 2, 3, 4 and 5 from Method 2.
2. Calculate d_{FF} , as shown in Equation 14. Since V_{IN} is a sine wave and its value is negative in a negative AC cycle, use its absolute value for the calculation.

$$d_{FF} = \frac{V_{OUT} - |V_{IN}|}{V_{OUT}} \tag{14}$$

3. Use Equation 15 to add d_{FF} to the G_I output, d_I , and obtain the final d .

$$d = d_I + d_{FF} \tag{15}$$

You can also use d_{FF} control for a hardware state machine-based controller; for details, see reference [2].

Closing the current loop

Closing the current loop of a totem-pole bridgeless PFC is not as straightforward as in a traditional PFC; it may also vary from controller to controller. This power tip can help you eliminate the confusion around control-loop implementations in a totem-pole bridgeless PFC, and choose the appropriate method for your design.

Related Content

- [Power Tips #108: Current sensing considerations in a bridgeless totem pole PFC](#)
- [A comparison of interleaved boost and totem-pole PFC topologies](#)
- [Power Tips #116: How to reduce THD of a PFC](#)
- [Power Tips #132: A low-cost and high-accuracy e-meter solution](#)

References

1. Dixon, Lloyd. “[High Power Factor Preregulator for Off-Line Power Supplies](#).” Texas Instruments Power Supply Design Seminar SEM600, literature No. SLUP087, 1988.
2. Sun, Bosheng. “[Duty Ratio Feedforward Control of Digitally Controlled PFC](#).” Power Systems Design, Dec. 3, 2014.
3. Van de Sype, David M., Koen De Gussemé, Alex P.M. Van den Bossche, and Jan A. Melkebeek. “[Duty-Ratio Feedforward for Digitally Controlled Boost PFC Converters](#).” Published in IEEE Transactions on Industrial Electronics 52, no. 1 (February 2005): pp. 108-115.

Previously published on EDN.com.

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2025, Texas Instruments Incorporated