

Power Supply Design Seminar

The Right-Half-Plane Zero — A Simplified Explanation

Topic Categories:
Basic Switching Technology
Feedback Loop Compensation

Reproduced from
1986 Unitrode Power Supply Design Seminar
SEM500, Topic C2
TI Literature Number: SLUP084

© 1986 Unitrode Corporation
© 2011 Texas Instruments Incorporated

**Power Seminar topics and online power-
training modules are available at:
power.ti.com/seminars**

The Right-Half-Plane Zero — A Simplified Explanation

Lloyd H. Dixon, Jr.

In small signal loop analysis, poles and zeros are normally located in the left half of the complex s -plane. The Bode plot of a conventional or left-half-plane zero has the gain magnitude rising at 20 dB/decade above the zero frequency with an associated phase lead of 90° . This is the exact opposite of a conventional pole, whose gain magnitude decreases with frequency and the phase lags by 90° . Zeros are often introduced in loop compensation networks to cancel an existing pole at the same frequency; likewise poles are introduced to cancel existing zeros in order to maintain total phase lag around the loop less than 180° with adequate phase margin.

The right-half-plane (RHP) zero has the same 20 dB/decade rising gain magnitude as a conventional zero, but with 90° phase lag instead of lead. This characteristic is difficult if not impossible to compensate. The designer is usually forced to roll off the loop gain at a relatively low frequency. The crossover frequency may be a decade or more below what it otherwise could be, resulting in severe impairment of dynamic response.

The RHP zero never occurs in circuits of the buck family. It is encountered only in flyback, boost and Cuk circuits, and then only when these circuits are operated in the continuous inductor current mode.

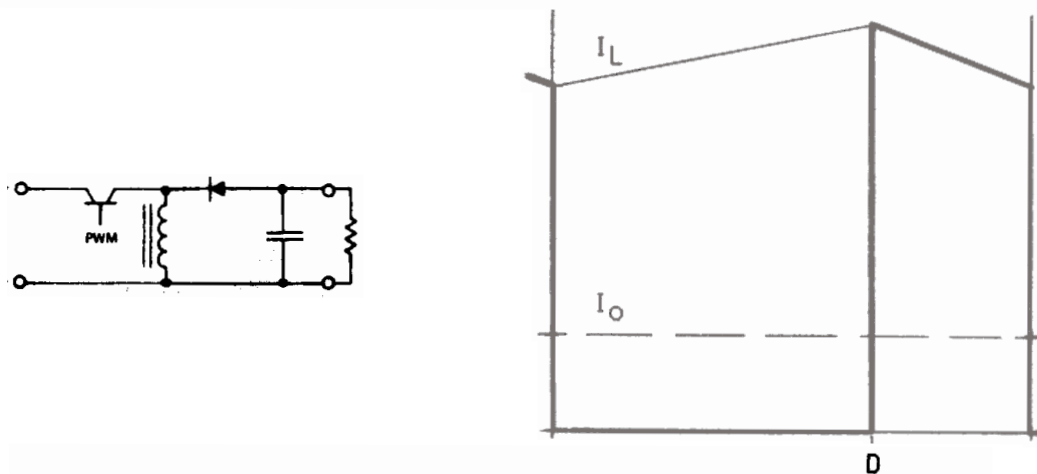


Figure 1 -- Flyback Circuit, Continuous Inductor Current Mode

Figure 1 shows the basic flyback circuit operating in the continuous mode with its current waveforms. In flyback as well as boost circuits, the diode is the output element. All current to the output filter capacitor and load must flow through the diode, so the steady-state DC load current must equal the average diode current. As shown in the Fig. 1 waveforms, the inductor current equals the peak diode current, and it flows through the diode only during the "off" or free-wheeling portion of each cycle. The average diode current (and load current) therefore equals the average inductor current, I_L , times $(1-D)$, where D is the duty ratio (often called duty cycle).

If D is modulated by a small AC signal, \hat{d} , whose frequency is much smaller than the switching frequency, this will cause small changes in D from one switching cycle to the next. Figure 2 shows the effects of a small increase in duty ratio (during the positive half-cycle of the applied signal).

The first effect is that the temporarily larger duty ratio causes the peak inductor current to increase each switching cycle, with an accompanying increase in the average inductor current. If the signal frequency is quite low, the positive deviation in duty ratio will be present for many switching cycles. This results in a large cumulative increase in inductor current, whose phase lags \hat{d} by 90° . This change in inductor current flows through the diode during the "off" time causing a proportional change in output current, in phase with the inductor current.

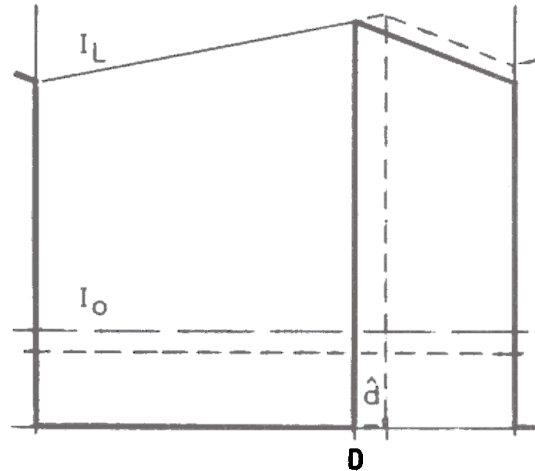


Figure 2

The second effect is more startling: The temporary increase in duty ratio during the positive half-cycle of the signal causes the diode conduction time to correspondingly decrease. This means that if the inductor current stays relatively constant, the average diode current (which drives the output) actually decreases when the duty ratio increases. This can be clearly seen in Figure 2. In other words, the output current is 180° out of phase with \hat{d} . This is the circuit effect which is mathematically the right-half-plane zero. It dominates when the signal frequency is relatively high so that the inductor current cannot change significantly.

Duty Ratio Control Equations: The equations for the flyback circuit are developed starting with the voltage V_L across the inductor, averaged over the switching period:

$$V_L = V_i D - V_o(1-D) = (V_i + V_o)D - V_o \quad (1)$$

Modulating the duty ratio D by a small AC signal \hat{d} whose frequency is much smaller than the switching frequency generates an AC inductor voltage, \hat{v}_L :

$$\hat{v}_L = (V_i + V_o)\hat{d} + \hat{v}_o(1-D) \approx (V_i + V_o)\hat{d} \quad (2)$$

Assuming V_i is constant, \hat{v}_L is a function of \hat{d} and of \hat{v}_o , the AC voltage across the output filter capacitor. At frequencies above filter resonance, \hat{v}_o becomes much smaller than \hat{v}_L , and the second term may be omitted.

AC inductor current, \hat{i}_L , varies inversely with frequency and lags \hat{v}_L by 90° . Substituting Eq. 2 for \hat{v}_L gives \hat{i}_L in terms of \hat{d} :

$$\hat{i}_L = \frac{\hat{v}_L}{j\omega L} = -j \frac{(V_i + V_o)}{\omega L} \hat{d} \quad (3)$$

Referring to Figure 1, the inductor provides current to the output through the diode only during the "off" portion of each cycle:

$$I_o = I_L(1-D) \quad (4)$$

Differentiating Eq. 4, the AC output current, \hat{i}_O , has two components (ref. Fig. 2 discussion) -- one component in phase with \hat{i}_L and the other 180° out of phase with \hat{d} :


$$\hat{i}_O = \hat{i}_L(1-D) - I_L\hat{d} \quad (5)$$

Substituting Eq. 3 for \hat{i}_L gives \hat{i}_O in terms of the control variable \hat{d} . In a continuous mode flyback circuit, $(1-D) = V_i/(V_i+V_O)$:

$$\hat{i}_O = -j \frac{(V_i+V_O)(1-D)}{\omega L} \hat{d} - I_L\hat{d} = -j \frac{V_i}{\omega L} \hat{d} - I_L\hat{d} \quad (6)$$

The first term is the inductor pole, which dominates at low frequency. Its magnitude decreases with frequency and the phase lag is 90°. At a certain frequency the magnitudes of the two terms are equal. Above this frequency, the second term dominates. Its magnitude is constant and the phase lag is 180°. This is the RHP zero occurring at frequency ω_z where the magnitudes are equal.

Figure 3 is a Bode plot of Eq. 6 (arbitrary scale values). Above f_z , the rising gain characteristic of the RHP zero cancels the falling gain of the inductor pole, but the 90° lag of the RHP zero adds to the inductor pole lag, for a total lag of 180°. The Bode plot of the entire power circuit would also include the output filter capacitor pole, which combines with the inductor pole resulting in a second order resonant characteristic at a frequency well below the RHP zero. The ESR of the filter capacitor also results in an additional conventional zero.

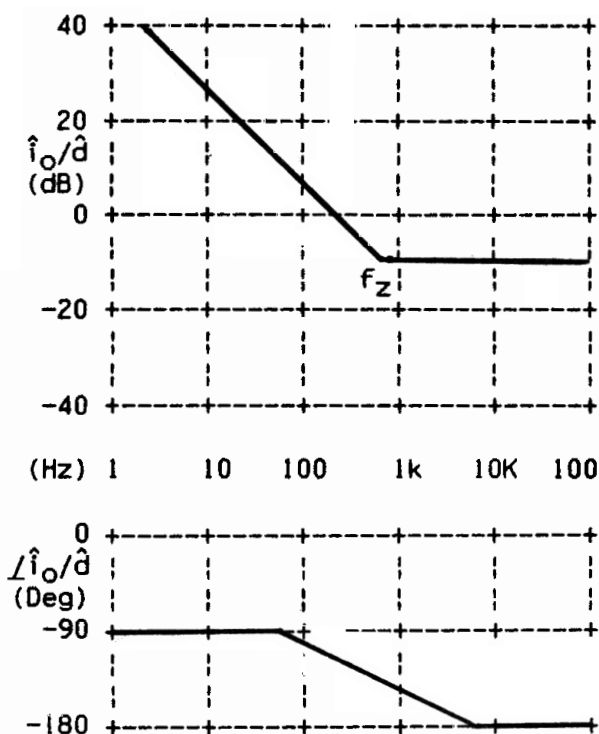

Figure

The RHP zero frequency is calculated by equating the magnitudes of the two terms in Eq. 6, and solving for ω_z :

$$\omega_z = \frac{V_i}{L I_L} \quad (7)$$

Substitute Eq. 4 for I_L , V_O/R_O for I_O .

In a flyback circuit, $V_i/V_O = (1-D)/D$; $(1-D) = V_i/(V_i+V_O)$:

$$\omega_z = \frac{R_O V_i(1-D)}{L V_O} = \frac{R_O (1-D)^2}{L D} = \frac{R_O V_i^2}{L V_O(V_i+V_O)} \quad (8)$$

Current Mode Control Equations: Equations 1, 2, 4, and 5 pertain to the flyback continuous mode power circuit, and are valid for any control method including current mode control. Eq. 3 is valid for current mode control, but it applies to the inner, current control loop. Solve Eq. 3 for \hat{d} in terms of \hat{i}_L and substitute for \hat{d} in Eq 5:

$$\hat{i}_O = \hat{i}_L(1-D) - j \frac{\omega L I_L}{(V_i+V_o)} \hat{i}_L = \frac{V_i}{(V_i+V_o)} \hat{i}_L - j \frac{\omega L I_L}{(V_i+V_o)} \hat{i}_L \quad (9)$$

Equations 6 and 9 are the same, except that in Eq. 6 the control variable is \hat{d} for duty ratio control, while in Eq. 9 the control variable is \hat{i}_L established by the inner loop and consistent with current mode control.

Unlike Eq. 6 for duty ratio control, the first term in Eq. 9 is constant with frequency and has no phase shift. This term dominates at low frequency. It represents the small signal inductor current which is maintained constant by the inner current control loop, thus eliminating the inductor pole. The second term *increases* with frequency yet the phase lags by 90°, characteristic of the RHP zero. It dominates at frequencies above ω_z where the magnitudes of the two terms are equal. The RHP zero frequency ω_z may be calculated by equating the two terms of Eq. 9. The result is the same as Eq. 7 for duty ratio control.

Figure 4 is the Bode plot of Eq. 9. The output filter capacitor will of course add a single pole and an ESR zero. Because the inductor pole is eliminated by the inner loop, the outer voltage control does *not* have a 2-pole resonant (second order) characteristic. However, the RHP zero is clearly still present with current mode control.

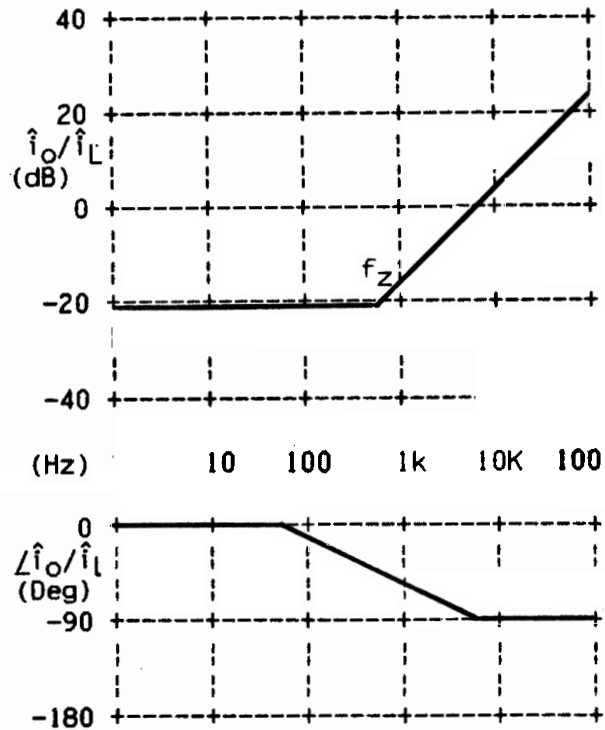


Figure 4

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+(49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm
Direct Email	asktexas@ti.com

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Note: Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A122010

E2E and Unitrode are trademarks of Texas Instruments. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated