

## **Power Supply Design Seminar**

# **Feedback in the Fast Lane — Modeling Extending Current-Mode Control in High-Frequency Converters**

Topic Categories:  
**Low-Voltage, Non-Isolated Buck  
Feedback Loop Compensation**

Reproduced from  
2006 Texas Instruments Power Supply Design Seminar  
SEM1700, Topic 3  
TI Literature Number: SLUP277

© 2006, 2011 Texas Instruments Incorporated

**Power Seminar topics and online power-  
training modules are available at:  
[power.ti.com/seminars](http://power.ti.com/seminars)**



# Feedback in the Fast Lane

## Modeling Extending Current-Mode Control in High-Frequency Converters

Brian Lynch, Texas Instruments

### ABSTRACT

*Conventional small-signal analysis of current-mode control, combined with classical loop measurement techniques, has guided power supply designers for nearly thirty years. As switching frequencies increase to the megahertz range, timing delays introduced by circuit components begin to affect overall loop response creating discrepancies between measured and predicted results. Using the example of a buck converter, this paper re-examines a small-signal current-mode control model from a circuit analysis perspective, discusses circuit parameter effects on loop performance and in particular, investigates the effect on the open loop gain of the modulator.*

### I. INTRODUCTION

State-space averaging eliminates switching elements by averaging the contributions of each circuit topology they create. This technique enables analysis of switching power supply feedback loops by the use of relatively simple small-signal analysis techniques. Previous discussions of averaged modeling,<sup>[1][2]</sup> provide guidance in applying the technique. For example, the output filter must contain a double pole far below the converter switching frequency to ensure the validity of the model. A linear equivalent to the pulse width modulator (PWM) then replaces the pulse generating circuit, allowing analysis of the system in the frequency domain. By necessity, design, or because the effects were negligible at low operating frequencies, earlier modeling efforts simplified analysis by ignoring influences such as circuit propagation delay and complex pole-zero output filters. These factors become increasingly significant as switching frequencies and closed loop bandwidths increase. The following discussion revisits the averaged model from a circuit analysis perspective and investigates the effects physical circuit characteristics impart on feedback loop performance.

The approach followed is to model a simple DC/DC converter with voltage-mode control (VMC) operating in continuous conduction mode, and then increases the complexity of the model on a systematic basis each time pausing to review the change to the previous system. The addition of current feedback produces in an updated model for a current-mode control (CMC) DC/DC converter extendable to any buck-derived topology. The TPS40180 DC/DC buck controller incorporating both voltage-mode and current-mode modulation elements serves as the vehicle for an illustrative example. (See Appendix A). Predicted results from the completed model favorably compare with lab measurements for a converter operating at 1 MHz.

## II. DEVELOPMENT OF THE NEW MODEL

### A. Review of a Simple System

Fig. 1 illustrates a voltage-mode synchronous buck converter and the equivalent small-signal block diagram. In this block diagram, the error amplifier and compensation components form blocks  $K_{EA}$  and  $K_{FB}$ . The pulse width modulator, drivers, and MOSFET switches become an averaged circuit block,  $K_{PWM}$ . The output filter and the load combine to form filter block  $X_{LC}$ .

The closed loop response of the system equals, (See Appendix B):

$$T_V(s) = V_{IN} \times K_{FB} \times K_{EA}(s) \times K_{PWM} \times X_{LC}(s) \quad (1)$$

Once the output filter and modulator satisfy the converter design requirements, the feedback network,  $K_{FB}K_{EA}$ , must ensure the closed loop response meets stability requirements. Other authors provide full details of techniques<sup>[3][4]</sup> for synthesizing feedback networks to stabilize a system. This paper focuses on the effect of high frequency operation upon the modulator and filter blocks, or more specifically, the control-to-output transfer function  $V_{OUT}/V_C$ .

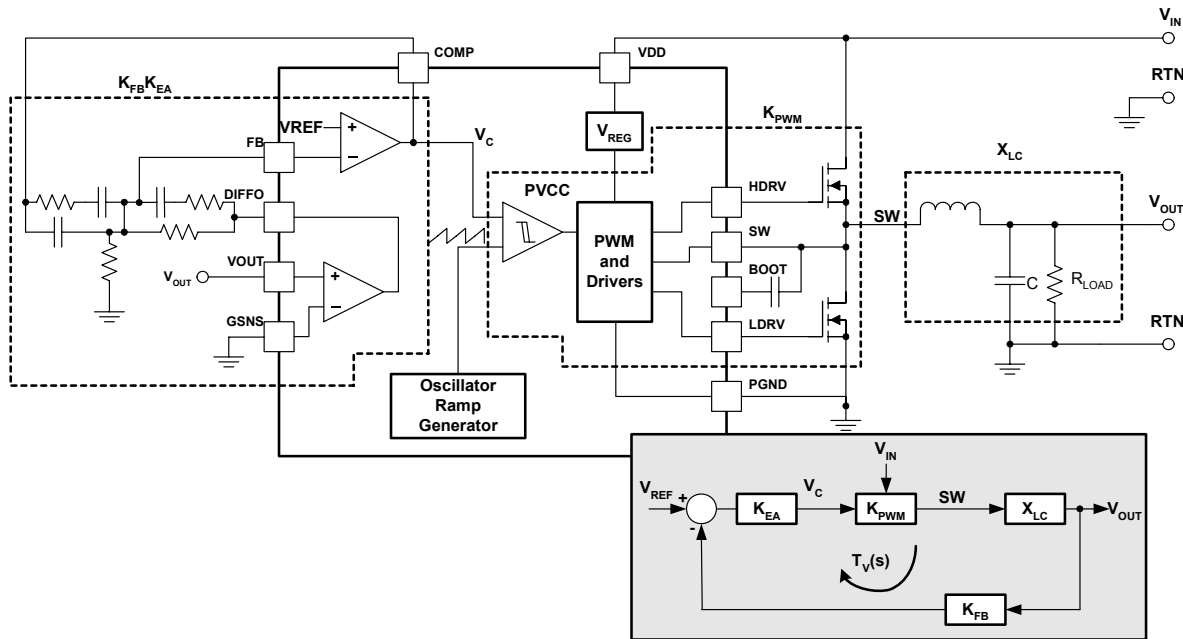


Fig. 1. VMC buck converter schematic and block diagram.

## B. Modulator Gain

Fig. 2 illustrates a typical VMC PWM comparator with the associated waveforms. An oscillator derived saw tooth waveform compared to a control signal generates a pulse-width-modulated signal. Of keen interest is the transfer function of the control voltage ( $V_C$ ) to the switching node ( $SW$ ).

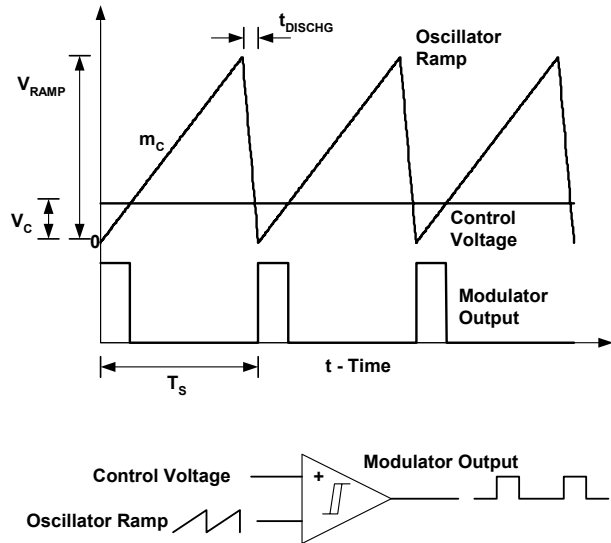


Fig. 2. VMC modulation.

An averaged model linearizes the PWM block, negating all switching effects, leaving only a simple linear relationship:

$$V_{OUT} = V_{IN} \times D \quad (2)$$

In the ideal case, and assuming continuous conduction mode operation, the output voltage is equal to the product of the input voltage and the duty cycle ( $D$ ). A change in the duty cycle translates to an equivalent change in the *average* voltage at the SW node, and ultimately, to a similar change in the output voltage. Simplistically, a change in the control voltage ( $V_C$ ) translates to a change in the duty cycle. The averaged model requires knowledge of this relationship between duty cycle and control voltage. Given that the duty cycle equals the control voltage divided by the peak-to-peak voltage of the ramp ( $V_{RAMPp-p}$ ) the control to duty cycle gain ( $K_{PWM}$ ) equals

$$K_{PWM} = \frac{\Delta D}{\Delta V_C} = \frac{\Delta D}{\Delta D \times V_{RAMPp-p}} = \frac{1}{m_c \times T_s} \quad (3)$$

In the last term of equation (3), the product of the *slope* of the modulator ramp and a *time interval* replaces the *amplitude* of the modulator ramp. The relevant time interval is the switching period less a ramp discharge time. The benefits of this substitution become evident in Section III, where current feedback and circuit parameter effects modify the PWM gain. For the example controller,

$$K_{PWM} = \frac{1}{\frac{0.5V}{1\mu s - 0.1\mu s} \times (1\mu s)} = 1.8 \times \frac{1}{V} \quad (4)$$

### C. Output Filter

Many models assume ideal components when determining the L-C corner frequency. In practice, the output filter comprises a much more complicated circuit. The inductor has winding resistance, and there may be different types of capacitors used, each with ESR and ESL characteristics that place a complex array of poles and zeros in frequencies of interest. A realistic output filter model as in Fig. 3 includes each component with its relevant parasitic elements.

In this model, the effective resistances of the switch and synchronous rectifier MOSFET are included into the filter block to account for variances in equivalent source loss due to duty cycle.

$$Z_{IN} = R_{DS(on\_sw)} \times D + R_{DS(on\_sr)} \times (1 - D) \quad (5)$$

A simple voltage divider then creates the output filter transfer function:

$$X_{LC}(s) = \frac{Z_{OUT}(s)}{Z_{OUT}(s) + Z_L(s) + Z_{IN}} \quad (6)$$

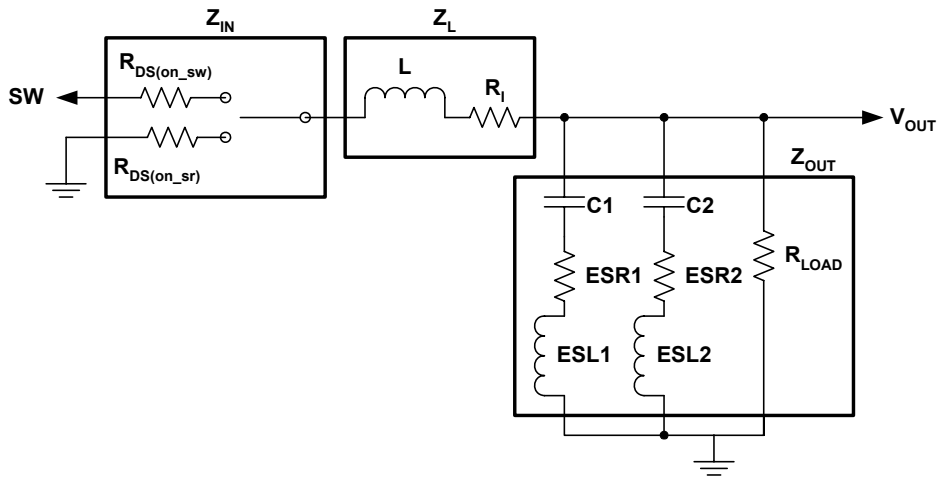


Fig. 4. Output filter schematic including parasitic elements.

Where  $Z_{OUT}(s)$ ,  $Z_{IN}$ ,  $Z_L(s)$  are the series and parallel combined impedances of the components within the dashed boxes in Fig. 3. Fig. 3 plots the filter transfer function for an ideal case in which all parasitic influences of ESR, ESL, and  $R_{DS(on)}$  are set to zero, and for a more practical case where parasitic elements are included.

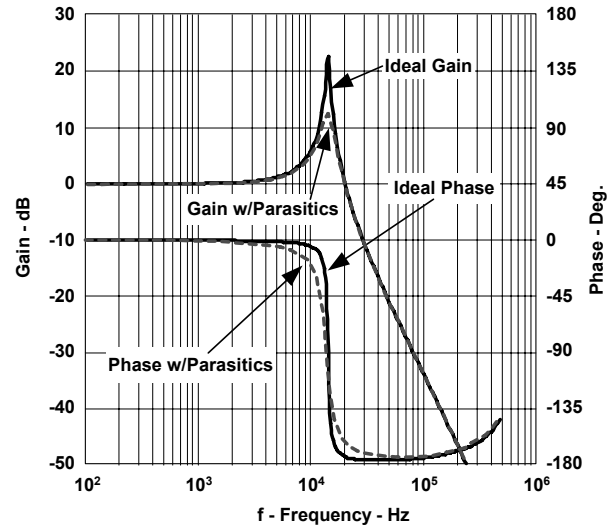


Fig. 3. Transfer function of the filter in Fig. 3.

The MOSFET resistance in series with the output inductor contributes an additional loss term that dampens the Q of the filter and attenuates the output voltage. The additional damping may affect the overall phase margin, depending on the selection of the final loop crossover frequency and the magnitude of the losses. This gain loss corresponds to a control correction required to maintain DC regulation. The degree of this correction becomes clear from a more realistic approximation of the duty cycle:

$$D = \frac{V_{OUT} + I_{OUT} \times (R_{DS(on\_sr)} + Rl)}{V_{IN} - I_{OUT} \times (R_{DS(on\_sw)} - R_{DS(on\_sr)})} \quad (7)$$

For the example, evaluation of equation (7) estimates the amount of change in duty cycle in a change from no load to full load. Under no load condition, the duty cycle will be  $3.3/12 = 27.5\%$ , and under fully loaded conditions:

$$D_{FULL\_LOAD} = \frac{3.3 + 5 \times (5.5m + 2.2m)}{12 - 5 \times (5.5m - 4.5m)} = 27.9\% \quad (8)$$

The difference between these two represents a 0.4% increase in duty cycle due to filter and MOSFET conduction losses. This calculation gives a good first-order approximation of the difference in duty cycle, and thus the gain loss. One should consider this effect when compensating a converter over a wide range of loads.

#### D. Control to Output

The filter and PWM blocks together create the control-to-output transfer function. With this, and the desired response of the overall loop, a designer can synthesize a suitable error amplifier compensation network. Fig. 5 shows the control-to-output frequency responses for the example converter using voltage-mode control at input voltages of 5 V and 12 V. Note that the gain  $X_{CO}(s)$  depends linearly upon the input voltage  $V_{IN}$ :

$$X_{CO}(s) = \frac{V_{OUT}(s)}{V_C(s)} = V_{IN} \times K_{PWM} \times X_{LC}(s) \quad (9)$$

 


Fig. 5. Control-to-output transfer function.

### III. PEAK CURRENT FEEDBACK

The previous section examined the control-to-output transfer function for voltage-mode control. The next step increases the complexity of the system by adding current feedback.

Fig. 6 depicts the schematic and block diagram of a buck controller containing an inner current feedback loop. The schematic illustrates one of several peak-current feedback topologies. Other topologies, including peak MOSFET current sensing uses the same analysis. Current feedback adds three new blocks to the diagram: current sense,  $X_i(s)$ , current gain,  $K_{CS}(s)$ , and sampling gain  $H_e(s)$ <sup>[5]</sup>. The current-sense transfer function and the current-sense gain both have counterparts in a physical design. The sampling gain, which has no such physical counterpart, allows the application of a discrete-time function (in this case, current sampling) to a continuous-time analysis.

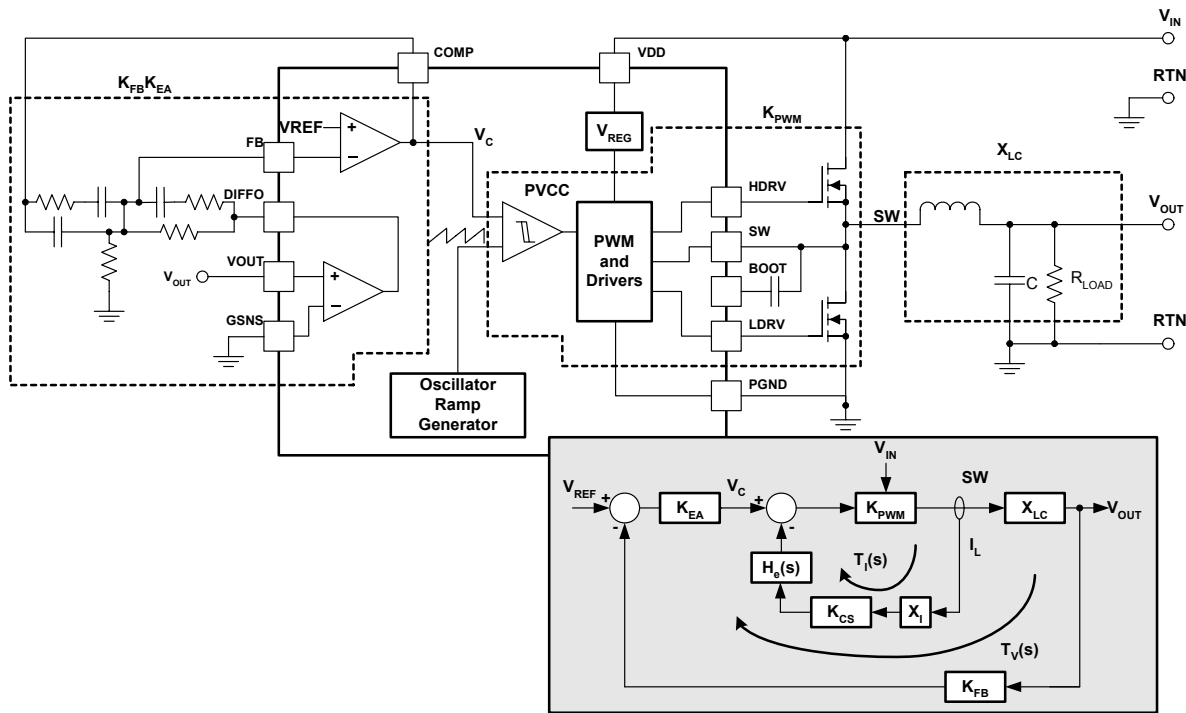


Fig. 6. CMC buck converter schematic and block diagram.

### A. Sampling Gain

Since a peak current-mode controller acts as a first order sample and hold circuit, the sampling gain equals:

$$H_e(s) = \frac{s \times T_s}{e^{s \cdot T_s} - 1} \quad (10)$$

 


Fig. 7.  $H_e(s)$ .

The sampling gain introduces a gain boost and a phase lag beginning at about 1/10th the switching frequency. Fig. 7 indicates that the phase lag reaches  $90^\circ$  at about half of the switching frequency (or 500 kHz in this example). This effect predicts possible sub-harmonic oscillation in current-mode converters.

### B. Current Sensing

This analysis divides the current feedback signal into two portions: a small-signal AC transfer characteristic and the slope information used to determine the modulator gain.

The current-sense AC transfer characteristic represents the small-signal current feedback to the control system. The transfer function derived using nodal analysis includes the effects of the complex filter model. Fig. 8 illustrates two methods of output current sensing, one method (upper), uses a resistor in series with the output inductor to sense current directly. The other method, (lower), uses an R-C network across the inductor to construct a signal similar to the inductor current waveform. (See Appendix C).

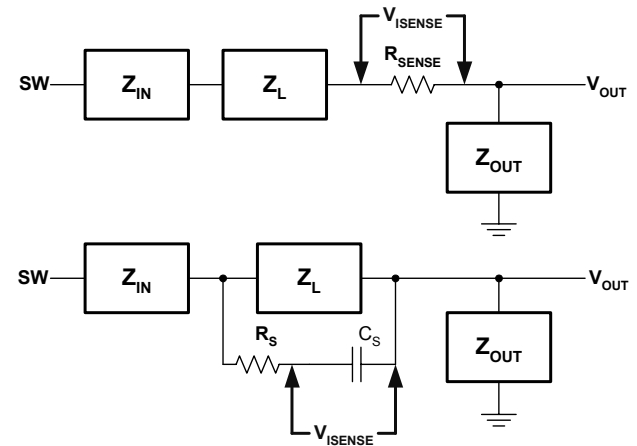


Fig. 8. Output current sensing.

By extending the methodology of Section II., sub section C, the duty cycle to current sense transfer function for simple resistor sensing equals:

$$X_i(s) = \frac{\Delta V_{ISENSE}}{\Delta V_{SW}} = \frac{R_{SENSE}}{Z_{LOAD}(s) + Z_{IN}(s) + Z_L(s) + R_{SENSE}} \quad (11)$$

and for R-C sensing equals:

$$X_i(s) = \frac{\Delta V_{ISENSE}}{\Delta V_{SW}} = \frac{1}{\left[ Z_{LOAD}(s) + Z_{IN}(s) + R_S \times \left( 1 + \frac{Z_{LOAD}(s) + Z_{IN}(s)}{Z_L(s)} \right) \right] \times s \times C_S + \frac{Z_{LOAD}(s) + Z_{IN}(s)}{Z_L(s)} + 1} \quad (12)$$

### C. Modulator Gain

The VMC modulator gain depends on both the control voltage and the slope of the oscillator ramp. Current feedback sums the control voltage with a saw tooth waveform which has a slope proportional to the slope of the inductor current. Fig. 9 shows a physical embodiment of a modulator in which the current feedback signal, scaled by a transconductance amplifier, subtracts from the error amplifier output voltage. Comparison of this composite signal with the oscillator ramp generates the PWM signal. This analysis depends only upon the relative slopes of the intersecting waveforms. Thus, a modulator that sums the current feedback signal with the oscillator ramp waveform produces the same results as the modulator of Fig. 9. This approach differs from others in that current feedback modifies a VMC system, rather than the reverse.

Referring to Fig. 8 and assuming  $V_{ISENSE}$  is small in amplitude compared to the switching waveform at SW, the slope of the current signal for direct resistor sensing equals (see equation (13)) and for R-C sensing equals (see equation (14)).

The effects of input voltage and load current variation appear in the equation for the on-time slope of the inductor current, and therefore they also appear in the expression for the modulator gain.

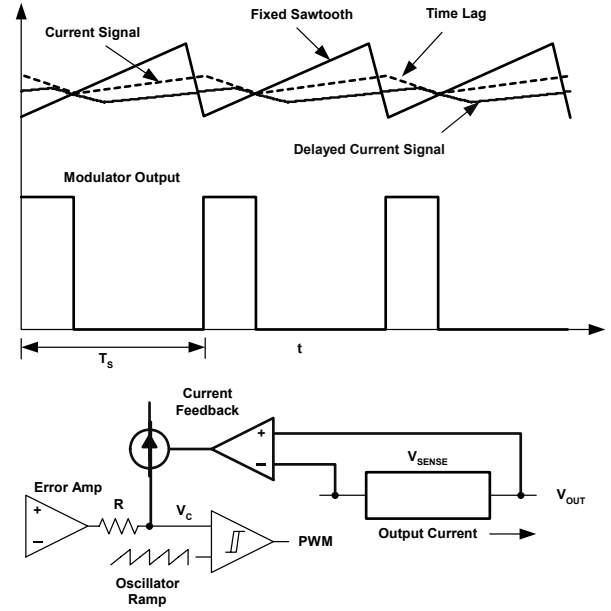


Fig. 9. Current feedback into the modulator.

For the example using R-C sensing, and assuming for now that  $K_{CS}(s)$  is 12.5 over the frequency range, (see equation (15)).

The PWM gain now includes the effect of current feedback, decreasing modulator gain by an amount proportional to the slope of the current signal as shown in equation (16).

$$m_n = \frac{V_{IN} - V_{OUT} - I_{OUT} \times (R_{DS(on\_sw)} + R_L + R_{SENSE})}{L} \times R_{SENSE} \times K_{CS}(s) \quad (13)$$

$$m_n = \frac{V_{IN} - V_{OUT} - I_{OUT} \times (R_{DS(on\_sw)} + R_L)}{R_S \times C_S} \times K_{CS}(s) \quad (14)$$

$$m_n = \frac{12 - 3.3 - 5 \times (5.5m + 2.2m)}{9.1k\Omega \times 100n} \times 12.5 = 119 \frac{mV}{\mu s} \quad (15)$$

$$K_{PWM} = \frac{1}{(m_c + m_n) \times T_s} = \frac{1}{\left(\frac{0.556V}{1\mu s} + \frac{0.119V}{1\mu s}\right) \times (1\mu s)} = 1.48 \frac{1}{V} \quad (16)$$

### D. Completing the Current Loop

The completed current loop ( $T_i(s)$  in Fig. 6) described by the equation below is plotted in Fig. 10 for input voltages of 5 V and 12 V. The slope increases with increasing input voltage, in accordance with equation (14). However, the magnitude of this increase is less than that of the input voltage itself. The current loop gain therefore shows only a moderate increase with increasing input voltage. There is no phase change with a change in input voltage.

$$T_i(s) = V_{IN} \times K_{PWM} \times X_i(s) \times K_{CS}(s) \times H_e(s) \quad (17)$$

 


Fig. 10. Current loop gain,  $T_i(s)$ .

### E. Control-to-Output Gain

The control-to-output transfer function of Fig. 6 equals:

$$X_{CO}(s) = \frac{V_{OUT}(s)}{V_C(s)} = \frac{V_{IN} \cdot K_{PWM}(s) \times X_{LC}(s)}{1 + T_i(s)} \quad (18)$$

This equation makes clear the effect of the inner current loop on the overall transfer function. A current loop gain of zero reduces the transfer function to that of voltage-mode control (equation (9)). In this example, the small amount of current feedback further reduces the Q of the output filter.

Fig. 11 illustrates the control-to-output transfer function of equation (18) at input voltages of 5 V and 12 V. The gain increases modestly with increasing input voltage because of the relatively small amount of current feedback in this example. The control-to-output gain of a pure CMC modulator incorporating no VMC ramp would vary less over the input voltage range. The control-to-output gain of a pure VMC without any current feedback would vary more over the input voltage range.

 


Fig. 11. Control to output transfer function.

#### IV. INCLUDING COMPONENT PARAMETER EFFECTS

Having completed the basic model derivation, we now consider the effects certain component parameters have upon the control-to-output response.

##### A. Delay in PWM Path

Signals require time to propagate from the input terminals of the PWM comparator to the SW node. The PWM comparator, the PWM latch, the gate drivers, and even the power transistors themselves, each delay the signal by a finite amount. The accumulation of these time delays appears in the small-signal model as a phase lag. Incorporating a propagation time  $t_{DELAY}$  into the modulator gain gives:

$$K_{PWM}(s) = \frac{e^{-s \times t_{delay}}}{(m_C + m_n) \times T_s} \quad (19)$$

The illustrative example assumes a switching frequency of 1 MHz and a unity gain bandwidth goal of 200 kHz. The controller propagation delay of 100 ns adds to the 111-ns turn-on delay of the switch MOSFET<sup>[6]</sup> to generate a phase lag of 17° at 200 kHz (Fig. 12.). This phase lag significantly complicates efforts to obtain 45° of phase margin at the desired unity gain bandwidth.

 


Fig. 12. Impact of PWM time delay.

##### B. Delay in the Current Sense Path

A signal delay also occurs in the current sense amplifier ( $K_{CS}$  in Fig. 6.). If the converter PWM on-time becomes shorter than the sum of the current sense and PWM delay times, then the current feedback slope at the time of PWM “decision” changes from the desired positive value seen during the on-time (Fig. 13. top), to a negative value seen during the off-time (Fig. 13. bottom). This in turn causes a step change in modulator gain, which if sufficiently large, can cause loop instabilities near that operating point.

 
 


Fig. 13. Impact of current sensing delay.

To estimate the delay in the current sense path, evaluate the current sense amplifier gain-bandwidth curve at the switching frequency. This gives a first-order approximation of the delay through the amplifier even though the signal is not sinusoidal. In practice, this procedure requires first writing a transfer function based on the unity gain bandwidth and the open loop gain listed in the data sheet, and then evaluating this transfer function at the switching frequency to determine the propagation delay.

For the illustrative example, the amplifier transfer function approximately equals:

$$K_{CS}(s) = \frac{gm \times R}{1 + \frac{s}{2\pi \times \frac{UGBW}{gm \times R}}} \quad (20)$$

$$K_{CS}(Fs) = \frac{625 \mu F \times 20 k\Omega}{1 + \frac{2j\pi \times 1MHz}{2\pi \times \frac{30MHz}{625 \mu F \times 20 k\Omega}}} = 10.65 + 4.44j \quad (21)$$

Dividing the argument (phase angle) by the switching frequency yields the time delay.

$$t_{DELAY} = \frac{\arg(K_{CS}(s))}{2\pi \times Fs} \quad (22)$$

$$t_{DELAY} = \frac{\arg(K_{CS}(1MHz))}{2\pi \times 1MHz} = 64 ns \quad (23)$$

To obtain the total time delay, add the amplifier delay to the PWM delay previously obtained. For the example, the total time delay equals 64 ns + 211 ns, or 275 ns. The modulator gain will therefore pass through a step change at

$$K_{PWM} = \frac{1}{(m_C + m_f) \times T_s} = \frac{1}{\left(\frac{0.556V}{1\mu s} + \frac{-0.047V}{1\mu s}\right) \times (1\mu s)} = 1.96 \frac{1}{V} \quad (24)$$

$$m_f = \frac{V_{OUT} + I_{OUT} \times (R_{DS(on-sr)} + R_L)}{R_S \times C_S} \times K_{CS} = \frac{3.3 + 5 \times (4.2m + 2.2m)}{9.1k\Omega \times 100n} \times 12.5 = \frac{0.046V}{\mu s} \quad (25)$$

a pulse width of 275 ns. Instability may occur at this point. On “either side” of this transition area, the gain will be constant. It is only with pulse widths at the decision point of the modulator that the gain will be unstable.

For the example, the PWM gain changes from the value of 1.48/V computed to a new value shown in equation (24).

At the transition point of 275 ns, and where  $S_f$ , the “off time” slope of the current waveform is shown in equation (25).

At 12-volt input, the gain shift becomes:

$$\Delta K = 20\log(1.96 - 1.48) = 6.6 dB \quad (26)$$

The gain shift increase of 6.6 dB in the current loop results in only a 1.5 dB gain increase in the control-to-output transfer function and a phase increase of only 3.6° (Fig. 14).

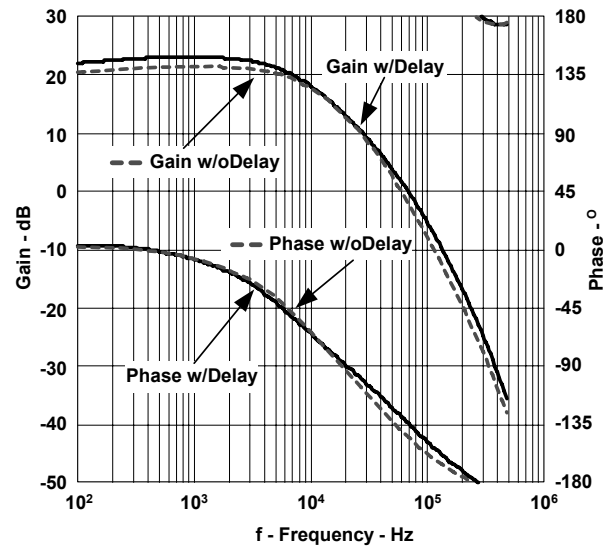


Fig. 14. Control to output due to modulator gain shift.

## V. COMPARISON TO MEASUREMENT

Comparison of measured and predicted results puts the model to the test. The TPS40180 incorporates current-mode control with a large voltage-compensating ramp. Appendix A gives the details of the test circuit. The predicted results of the model developed in this paper closely follow the actual measurements of control-to-output gain and phase (Fig. 15.). By contrast, results predicted by previous models, correlate poorly with measured results at both low and high frequencies.

 


Fig. 15. Control to output comparison of results.

This converter, operating at a switching frequency of 1 MHz and a crossover frequency of 200 kHz, exhibits a gain 6 dB less, and a phase margin 24° degrees less, than previous models predict. The new model accurately predicts converter performance and thus reduces the number of design iterations required to achieve satisfactory results.

## VI. CONCLUSIONS

As switching frequencies edge into the megahertz region, the effects of time lag and component bandwidth become significant contributors to converter loop behavior, creating the need for a more comprehensive analysis. The feedback loop model described deviates from traditional analysis by examining a system from a different perspective. In particular, 1) the small-signal feedback of the current sense signal follows as a function of the averaged signal fed to the filter network, and 2) the modulator gain equation now includes gain change and time delay effects. Arguably, where this analysis lacks direct insight into pole-zero locations and their effect on loop stability, it does allow better understanding of parameter variation effects upon loop performance.

## REFERENCES

1. V.Vorperian, *Simplified Analysis of PWM Converters Using the Model of the PWM Switch: Parts I and II*, VPEC Newsletter "Current", 1988
2. R.B. Ridley, *An Accurate and Practical Small-Signal Model for Current-mode Control*, Ridley Engineering, Inc., 1999
3. D. Venable, *Optimum Feedback Amplifier Design For Control Systems*, (date unknown)
4. D. Mitchell, R. Mammano, *Designing Stable Control Loops*, TI-Unitrode Seminar SEM-1400, 2001 (SLUP173)
5. A.R.Brown, R.D. Middlebrook, *Sampled-Data Modeling of Switching Regulators*, Power Electronics Specialists Conference proceedings, 1981
6. L. Balogh, *Design and Application Guide for High Speed MOSFET Gate Drive Circuits*, TI-Unitrode Seminar SEM-1400, 2001 (SLUP169)

## APPENDIX A. DC/DC CONVERTER EXAMPLE

A DC/DC converter using a prototype TPS40180 controller serves to correlate the model to an actual circuit. The converter is a 12-V to 3.3-V, 5-A DC/DC converter operating at 1 MHz. Important to the design evaluation are the following parameters:

### CIRCUIT PARAMETERS

Input voltage	$V_{IN} = 12 \text{ V}$
Output voltage	$V_{OUT} = 3.3 \text{ V}$
Output current	$I_{OUT} = 5 \text{ A}$
Output inductor	$L = 1.3 \text{ } \mu\text{H}$ with DCR $R_l = 2.2 \text{ m}\Omega$
Bulk output capacitors	$C_1 = 2 \times 47 \text{ } \mu\text{F}$ each with ESR1 = 3 m $\Omega$ and ESL1 = 4 nH
High frequency output capacitor	$C_2 = 1.0 \text{ } \mu\text{F}$ with ESR2 = 2 m $\Omega$ and ESL2 = 3 nH
Upper switch MOSFET	Q1 = Si4866 with $R_{DS(on, sw)} = 5.5 \text{ m}\Omega$
Synchronous rectifier	Q2 = Si4336 with $R_{DS(on, sr)} = 4.2 \text{ m}\Omega$
Current sensing network	$C_s = 100 \text{ nF}$ , $R_s = 9.1 \text{ k}\Omega$

In addition to the circuit parameters listed above, the controller exhibits the following characteristics of importance:

### CONTROLLER CHARACTERISTICS

Oscillator ramp amplitude	$V_{RAMPp-p} = 500 \text{ mV}_{p-p}$
Oscillator ramp discharge time	$T_{DISCH} = 100 \text{ ns}$
Modulator-to-gate drive output delay time	$T_{DELAY} = 100 \text{ ns}$
Current sense amplifier	Unity gain bandwidth = 30 MHz, $g_m = 625 \text{ } \mu\text{S}$ working into a 20-k $\Omega$ resistor
Gate drive voltage	5 V
Gate drive impedance	1 $\Omega$



## APPENDIX B. DEFINITION OF SYMBOLS

$C_s$	Capacitor used to generate current equivalent ramp
$D$	Duty cycle of the converter
$H_e$	Sampling gain
$I_{OUT}$	Converter (average) DC output current
$K_{CS}$	Current sense amplifier gain
$K_{EA}$	Compensated error amplifier transfer function
$K_{FB}$	Output voltage divider gain
$K_{PWM}$	Pulse width modulator gain
$L$	Output filter inductor inductance
$m_C$	Slope of the modulator ramp, $V_{RAMP}$
$m_f$	Slope of current feedback waveform during the switch off time
$m_n$	Slope of current feedback waveform during the switch on time
$R_{DS(on\ sr)}$	On-resistance of synchronous rectifier MOSFET
$R_{DS(on\ sw)}$	On-resistance of upper switch MOSFET
$R_L$	Inductor DC resistance
$R_s$	Resistor used in RC sensing circuit
$R_{SENSE}$	Output current sense resistor
$s$	Frequency in radians
$t_{DELAY}$	Accumulated delay of modulator, drivers, and MOSFET turn-on
$T_{DISCH}$	PWM sawtooth discharge time
$T_s$	Switching period
$T_i$	Current loop gain
$T_v$	Voltage loop gain
$V_C$	Duty cycle control voltage (usually the output of the compensated error amplifier)
$V_{IN}$	Input voltage to converter
$V_{ISENSE}$	Voltage representation of the output current –feedback to the control loop
$V_{OUT}$	Converter output voltage
$V_{RAMPp-p}$	VMC modulator ramp amplitude for PWM
$V_{SW}$	Equivalent average voltage at the switching node (SW) of the converter
$X_{CO}$	Converter control-to-output transfer function
$X_i$	Current sense transfer function
$X_{LC}$	Output filter transfer function
$Z_{IN}$	Equivalent impedance of switching MOSFETs
$Z_L$	Impedance of the output filter inductor
$Z_{LOAD}$	Parallel impedance of the output capacitors and the load
$Z_{OUT}$	Impedance of the output capacitor(s) in parallel with the load

- The suffix (s) appended to a variable indicates it is a function of frequency.
- A  $\Delta$  preceding a variable represents an incremental change in the variable's value.

## APPENDIX C. DERIVATION OF R-C SENSING

By placing an R-C network across the inductor of an output filter, the voltage generated across the capacitor ( $C_S$  in Fig. 17.), will be a saw tooth waveform with a slope proportional to the input voltage. With proper selection of the values of the resistor and capacitor, the slope of the voltage across the capacitor will match the slope of the current through the inductor. Although this method does not measure output ripple current directly, the slope information developed is accurate enough for many feedback loop designs.

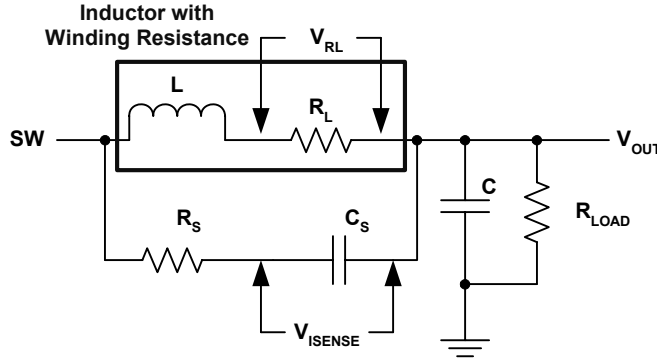


Fig. 17. R-C sensing.

Assuming the voltages  $V_{ISENSE}$  and  $V_{RL}$  are small compared to  $V_{SW}$  and  $V_{OUT}$ , the voltage across the equivalent inductor resistance equals:

$$V_{R_L} = (V_{SW} - V_{OUT}) \times \frac{R_L}{R_L + 2\pi f S \times L} \quad (27)$$

and the capacitor voltage equals:

$$V_{ISENSE} = (V_{SW} - V_{OUT}) \times \frac{1}{2\pi f S \times C_S \times R_S + 1} \quad (28)$$

Equating the two equations gives:

$$V_{ISENSE} = V_{R_L}; \frac{1}{2\pi f S \times C_S \times R_S + 1} = \frac{R_L}{R_L + 2\pi f S \times L} \quad (29)$$

Given the inductor (value and winding resistance) and arbitrarily selecting a value for  $C_S$  (0.1  $\mu\text{F}$  is typical) the value of  $R_S$  equals:

$$R_S = \frac{L}{R_L} \times \frac{1}{C_S} \quad (30)$$

For the example,

$$R_S = \frac{1.3 \mu\text{F}}{2.2 \text{ m}} \times \frac{1}{0.1 \mu\text{F}} = 5.9 \text{ k}\Omega \quad (31)$$

Interestingly, an  $R_S C_S$  combination that *does not* match the  $L/R_L$  time constant can provide additional gain or attenuation of the current feedback signal. Exploration of equation (12) indicates that not only will the PWM gain be affected by a mismatch of time constants (via the adjustment of slope of the feedback signal) but also at low frequencies, there will be a gain shift where the low frequency dominance of the  $R_L + sL$  term is overshadowed by the series  $R_S C_S$  term. Fig. 18 illustrates an example of the effect when the  $R_S C_S$  time constant assumes a lower inductor resistance than is actually being used. This may occur if the sensing connection points include PCB trace resistance, or the resistance of the inductor increases with elevated temperature. This example assumes a 1.5-m $\Omega$  inductor resistance, resulting in a calculated  $R_S$  of 9.1 k $\Omega$ . The mismatch in time constants results in a low-frequency gain error.

 


Fig. 18. RC mismatch to L/R.

At very low frequencies, the resistance of the inductor (2.2 m $\Omega$ ) dominates the impedance. As the sweep frequency is increased, there is a transition to the impedance dominated by  $L/R_S C_S = 1.2$  m $\Omega$ . The transition frequencies (at  $R/L = 318$  Hz and  $1/R_S C_S = 175$  Hz) are low enough that the effect on closed loop performance is negligible. An understanding of the effect however, explains peculiar phenomena such as the increase in gain from 100 Hz to 1200 Hz as depicted in Fig. 15.

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI E2E™ Community Home Page

[e2e.ti.com](http://e2e.ti.com)

## Product Information Centers

<b>Americas</b>	Phone	+1(972) 644-5580
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>

### Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+(49) (0) 8161 80 2045
Internet	<a href="http://support.ti.com/sc/pic/euro.htm">support.ti.com/sc/pic/euro.htm</a>
Direct Email	<a href="mailto:asktexas@ti.com">asktexas@ti.com</a>

### Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>
	Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>

### Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a> or <a href="mailto:ti-china@ti.com">ti-china@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A122010

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)