

# Laser and Modulator Biasing Power Circuit for Optical Module Systems



Data Converters

Mohana Chavan and Luis Brum

## Design Objective

Design a cost-effective, efficient, small, competitive circuit to consolidate AMC60704 power supply rails for biasing *current output digital-to-analog converters* (IDAC) and *voltage output digital-to-analog converters* (VDAC).



Input Supply	Operating Range		Recommended Device
	Minimum	Maximum	
PVDD	1.5V	2.2V	TPS62825A
VSS	-5.5V	-2.5V	LM27761

## Design Description

This circuit design creates a method to allow one main 3.3V power supply to supply multiple AMC60704 inputs. Important supplies are PVDD which supplies the IDAC that biases the lasers in an electro-absorption modulated laser (EML). Another important supply is VSS which is the input that supplies the VDAC in the negative range because VSS is used for biasing the electro-absorption modulator (EAM) in an EML.

Placing DC/DC converters on the PVDD and VSS rails allow the designers to provide a 3.3V supply and the converters step down and invert the input voltage to the desired value in range for PVDD and VSS. The suggested TPS6285A and LM27761 devices are small, low-cost, and efficient DC/DC converters that can step down and invert input voltages for PVDD and VSS. This design can be used in optical module applications for 400G. Additionally, 800G designs can be created but the 800G design requires an extra AMC60704 and LM27761 device.


*Design Objective*

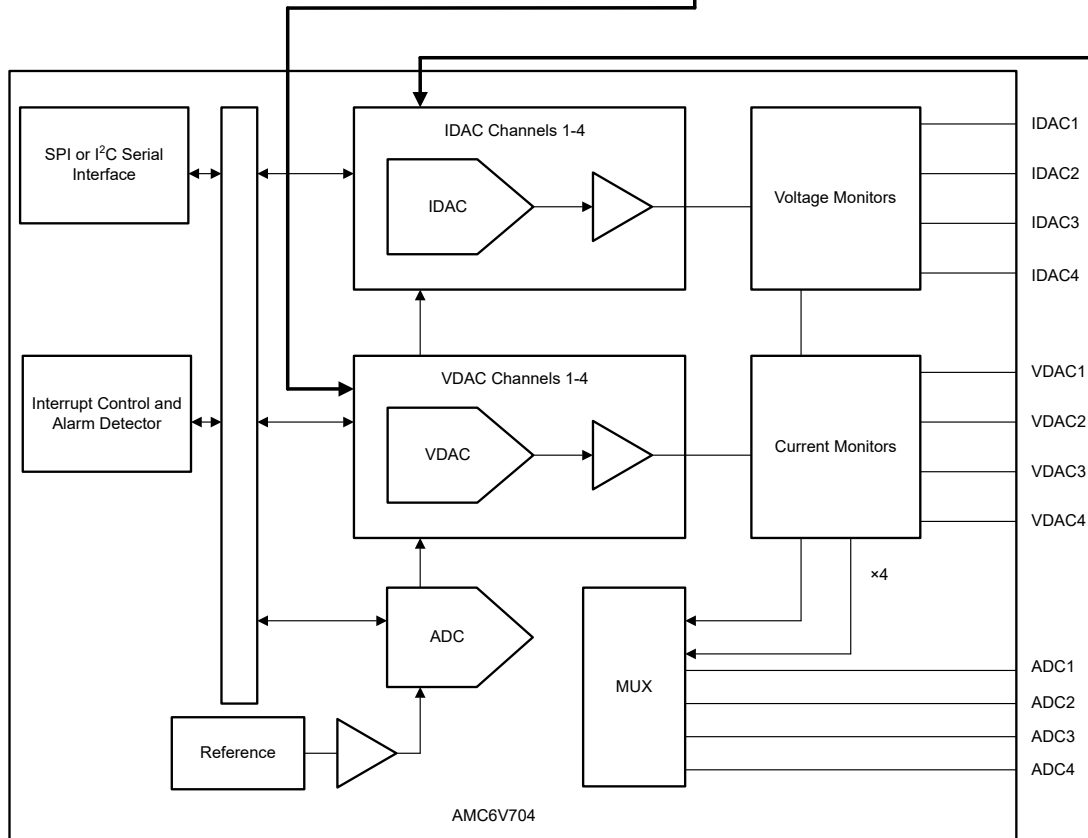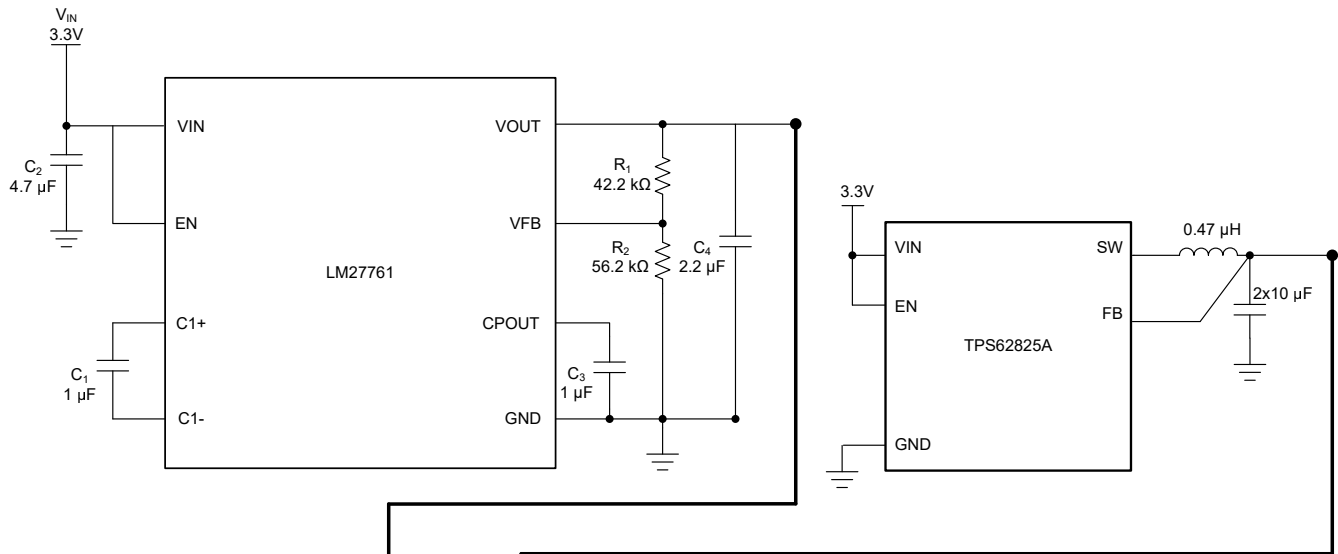

**Application Block Diagram**

### Design Notes

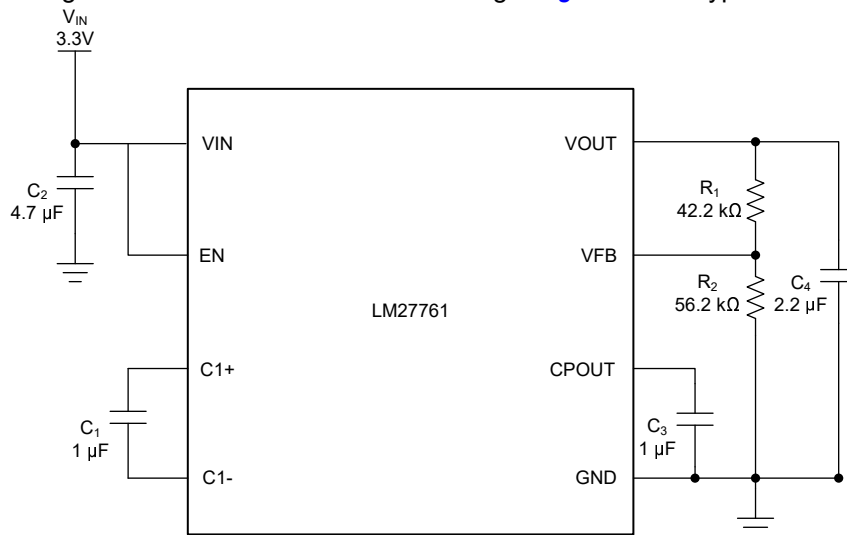1. This design focuses on EML applications, thus VCC, the positive rail is grounded.
2. This design can be used in 400G applications. Additionally, an 800G design can be created but the 800G design requires an extra AMC60704 and LM27761.
3. For biasing the VDACS in an EML application, the operating range for the VSS is rail is -2.5V to -5.5V. This circuit design uses -3.3V to supply the VDACS.
4. The AMC60704 has four VDAC channels each capable of a 50mA output. In 400G applications, all 4 channels are used. This circuit design uses all four VDAC channels.
5. The LM27761 has a maximum output current of 250mA and a configurable output range of -1.5V to -5V making the device a good fit for the VSS rail. The following *image* shows a typical LM27761 schematic.




### LM27761

6. The output voltage of the LM27761 is externally configurable. The values of R<sub>1</sub> and R<sub>2</sub> determine the output voltage setting. Use [Equation](#) to calculate the output voltage. The value for R<sub>2</sub> must be no less than 50kΩ.

$$V_{OUT} = -1.22V \times \left( \frac{R_1 + R_2}{R_1} \right)$$

- This design operates at -2.85V VSS, thus R<sub>1</sub>= 30.1kΩ and R<sub>2</sub> = 39kΩ, to allow enough headroom for current sourcing.
7. Different output capacitance values can be used to reduce charge pump ripple, shrink the design size, or cut the cost of the design. In typical applications, a 4.7μF low-ESR ceramic charge-pump output capacitor (C<sub>3</sub>) is recommended.
  8. Increasing the input capacitance results in a proportional decrease in input voltage ripple. Input voltage, output current, and flying capacitance also affect input ripple levels to some degree. A 4.7μF low-ESR ceramic capacitor is recommended on the input.
  9. Flying capacitance can impact both output current capability and ripple magnitudes. In typical high-current applications, 0.47μF or 1μF 10V low-ESR ceramic capacitors are recommended for the flying capacitors.
  10. The LDO output capacitor (C<sub>4</sub>) value and the ESR affect stability, output ripple, output noise, PSRR and transient response. The LM27761 only requires the use of a 2.2μF ceramic output capacitor for stable operation.
  11. For biasing the IDACS in an EML application, the operating range for the PVDD rail is 1.5V to 2.2V. This circuit design uses 1.8V to supply the IDACS.
  12. The AMC6V704 has four IDAC channels each with a 200mA full scale output. The maximum output current for the IDACS is 800mA.
  13. The TPS62825A is selected for this design because the device has a maximum output current of 2A and adjustable output voltage range from 0.6V to 4V. These converters maintain a continuous conduction mode operation and keep the output voltage ripple very low across the whole load range. The following *image* shows a typical TPS62825A schematic.

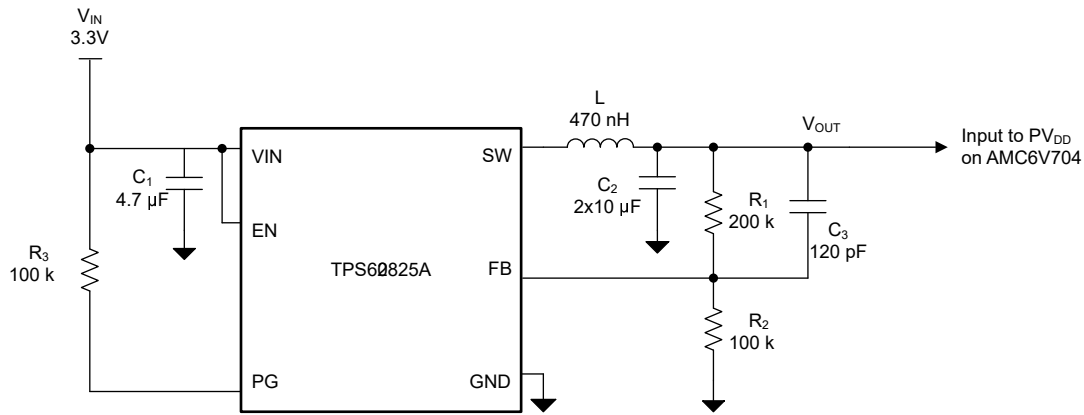
**TPS62825A Schematic**

14. Use the following [equation](#) to set the output voltage on the TPS62825A.

$$R1 = R2 \times \left( \frac{V_{OUT}}{V_{FB}} - 1 \right)$$


where

- $V_{FB}$  is 0.6V

15.  $R_2$  must not be greater than 100kΩ to achieve high efficiency at light load while providing acceptable noise sensitivity. The following [equation](#) shows how to compute the value of the feedforward capacitor,  $C_3$  for a given  $R_2$  value. For the recommended 100kΩ value for  $R_2$ , a 120pF feedforward capacitor is used.

$$C_3 = \frac{12\mu}{R_2}$$


16. Considering the DC-bias derating the capacitance, the minimum effective output capacitance,  $C_2$ , is 10μF for the TPS62825A.
17. A minimum effective input capacitance,  $C_1$ , of 3μF must be present, though a larger value reduces input current ripple. A 4.7μF input capacitor is used for the TPS62825A.
18. Adding the TPS62825A to the system, the power dissipation of the IDACs is now a function of the TPS62825A output voltage and current output, PVDD supply voltage, the current output, and the voltage of the IDAC pin. The power dissipation is calculated using [this equation](#). The  $V_{HEADROOM}$  voltage is calculated as the difference between PVDD and  $V_{IDACx}$ .

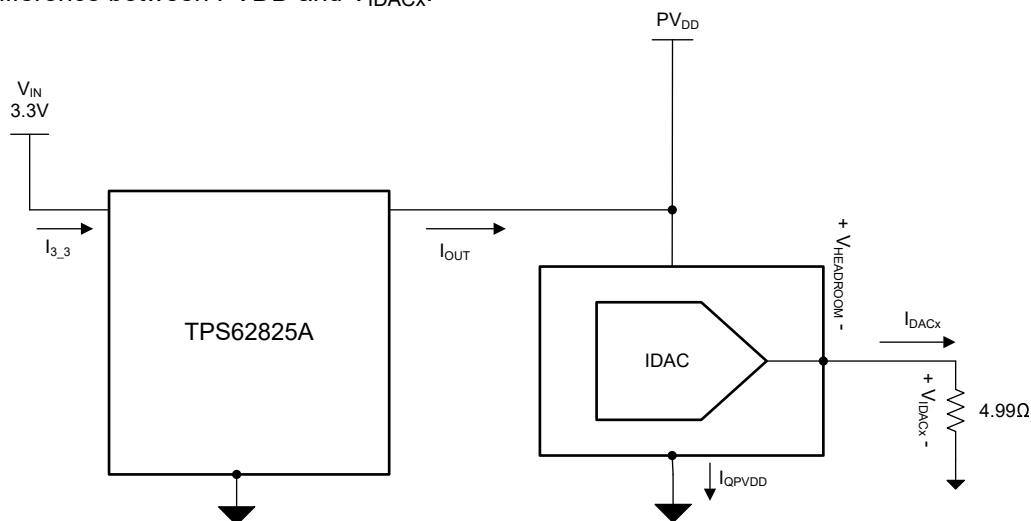
**PVDD Power Dissipation**

19.  $P_{TPS62825A} = 3.3V \times I_{3.3} - [P_{VDD} \times I_{OUT} + P_{VDD} \times I_{QPVD} + \sum I_{DAC0} - 3\{V_{HEADROOM} \times I_{DACx}\}]$
- The power dissipation can be reduced by minimizing the voltage difference,  $V_{HEADROOM}$ , between PVDD supply and  $V_{IDAC}$ . The minimum PVDD is 1.5V.
  - The output load can be calculated using the following equation.

$$LOAD = \frac{V_{IDAC}}{I_{DAC}}$$

 20. *Package Size Comparison* shows the products used in this design. Selecting the key passive components was previously discussed. For more complete details, see the product data sheet. A key requirement for this design is small package size due to high channel density within an optical module. The following *image* shows the package size comparison.




**Package Size Comparison**

21. To compete in this market, this design creates a low-cost answer against integrated devices.

## Design Measurements

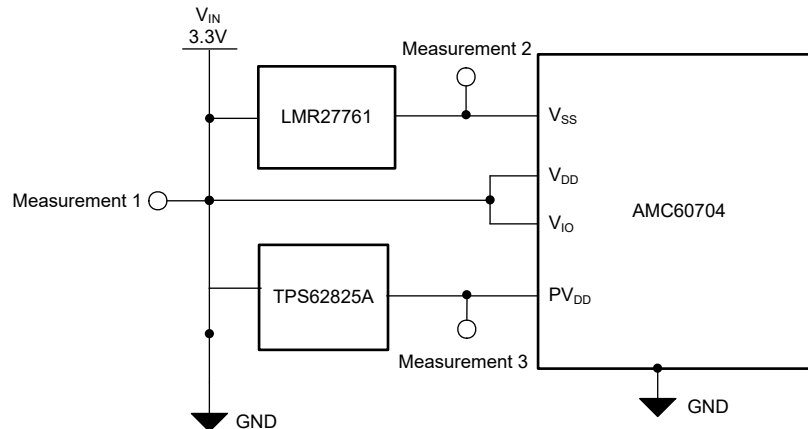
### Test 1: Power Supply Ramp-Up Response

*Power Supply Ramp-Up Response* shows the power supply ramp-up response test setup and test points.



 **Power Supply Ramp-Up Response**


The *Power Supply Ramp-Up Response* graph shows the time required after a power-on trigger occurs for the power supplies in the system to respond. The Tektronix TBS 2000B oscilloscope was used to probe each power supply input to measure the ramp-up for this test.




**Power Supply Ramp-Up Response**
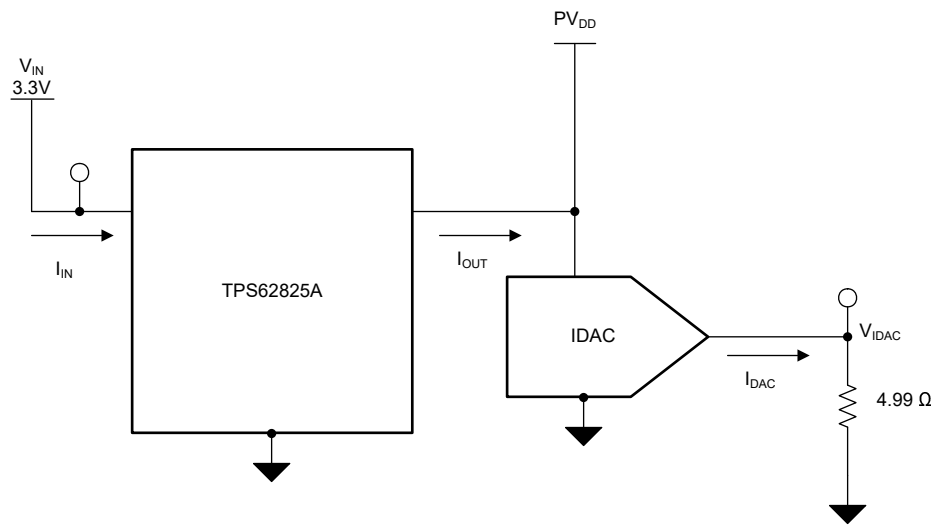
### Test 2: Power Efficiency of System vs IDAC


This efficiency test measures the power dissipation at the input supply of the TPS62825A against the power dissipation of the IDAC with a  $4.99\Omega$  load. As the IDAC codes change, the output of the IDAC as well as the input power changes. *IDAC Test Setup* shows the setup for this test.




**IDAC Test Setup**

 

**IDAC Efficiency vs IDAC Output**

 


**IDAC Power vs IDAC Output**

 


**IDAC System Power vs IDAC Output**
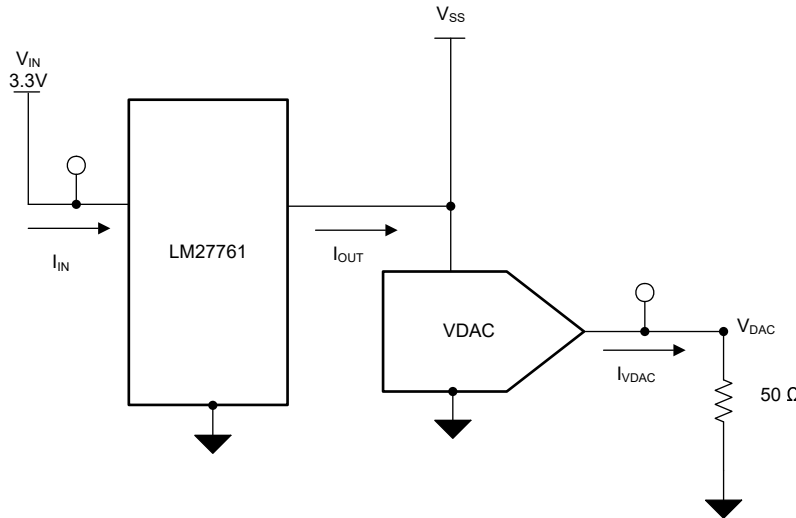
### Test 3: Power Efficiency of System vs VDAC

This test shows the power dissipation of the input supply from the LM27761 and the output of the VDAC. The following *image* shows the setup and test points. Using a DMM in a current measurement configuration, measuring the input current of the LM27761 can be used to calculate the power of the system. By changing the VDAC codes, the output of the VDAC changes as well as the system current. Placing a load resistor at the output allows for the calculation of the current flowing through the load. For a maximum output current of 50mA at full scale voltage output of  $-2.5V$ , the maximum resistive load is  $50\Omega$ .




VDAC Test Setup

 


 VDAC Efficiency vs VDAC Current Drive Output





 **VDAC System Power vs VDAC Current Drive Output**



**VDAC System Power vs Load Power**

## Design Featured Devices

Device	Key Features	Link	Other Possible Devices
AMC6V704	Optical controller with four 200mA current DACs, four voltage-output DACs and a multichannel ADC	<a href="#">AMC6V704</a>	<a href="#">AMC60704</a>
TPS62825A	2.4V to 5.5V input, 2A step-down converter with forced PWM in 1.5mm × 1.5mm VSON-HR package	<a href="#">TPS62825A</a>	<a href="#">TPSM82822</a>
LM27761	Low-noise regulated inverter with integrated LDO for an input voltage in the range of 2.7V to 5.5V	<a href="#">LM27761</a>	<a href="#">LM27762</a>

## Additional Resources

- Texas Instruments, [TPS6282xAEVM-126 Evaluation Module User's Guide](#)
- Texas Instruments, [LM27761EVM User's Guide](#)
- Texas Instruments, [Low-noise charge pumps make it easy to create negative voltages technical article](#)
- Texas Instruments, [AMC6V704 Evaluation Module User's Guide](#)
- Texas Instruments, [AMC6V704 4-Channel Optical Monitor and Controller With Current and Voltage Output DACs and Multichannel ADC Data Sheet](#)
- Texas Instruments, [AMC6V704EVM Evaluation Board Tool Page](#)

For direct support from TI Engineers, use the [TI E2E™](#) community.

## Trademarks

E2E™ is a trademark of Texas Instruments.

All trademarks are the property of their respective owners.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2025, Texas Instruments Incorporated