

TI Designs: TIDA-01255

Automotive Reinforced Isolation CAN Reference Design



Description

The TIDA-01255 design is built for isolated CAN communication, which is widely used in automotive environments. In hybrid and electric vehicles (HEV/EVs), a complete high-voltage network is floating with respect to the chassis ground. Isolation is required for the power and communication channels interfaced between floating high- to low-voltage systems. The TIDA-01255 design supports applications with a simple isolated transformer driver to transfer power. This TI Design has a low-transmission delay, which reduces the loop delay and supports higher baud rates of the CAN.

Resources


- | | |
|-----------------------------|----------------|
| TIDA-01255 | Design Folder |
| TCAN1042-Q1 | Product Folder |
| SN6501-Q1 | Product Folder |
| ISO7731-Q1 | Product Folder |
| TPS76350-Q1 | Product Folder |
| TMS570 | Product Folder |

Features



- Flexible High-Speed CAN Communication
- Low Loop Delay (Typically 136 ns) to Support High-Speed Arbitration Rates
- 750-mW Power Transfer With 3-kV Isolation
- Reinforced Digital Isolation
- ± 70 -V Bus Fault Protection
- Cost-Conscious Termination With Internal ESD Protection
- Compliant With ISO 11898-2 CAN Standard

Applications

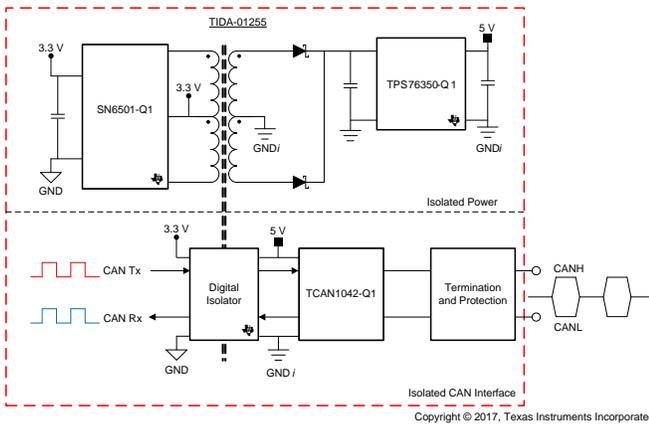- Cell Supervision Systems
- Battery Control Units
- Hybrid Electric Vehicles (HEV/EVs)



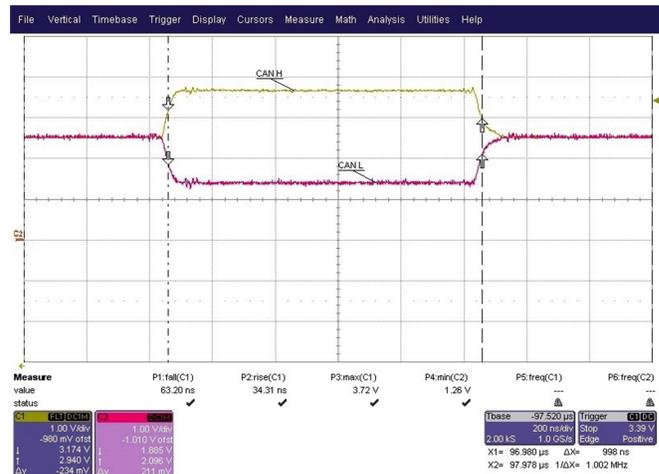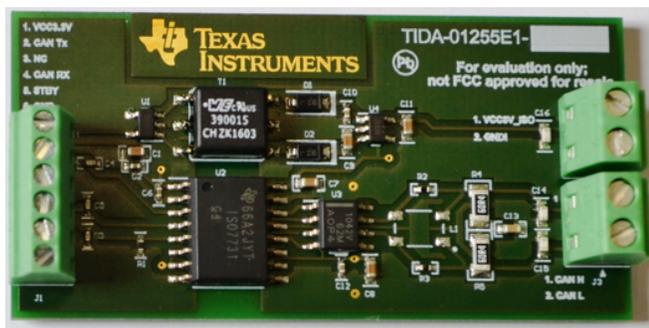Copyright © 2017, Texas Instruments Incorporated





An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 System Description

A Controller Area Network (CAN) is widely used in automotive industry to replace the complex wiring harness with a two-wire bus. It is highly immune to electrical interference and it has ability to self-diagnose and repair data errors. These features have led to CAN's popularity and extended its application in building automation, medical, and manufacturing. The TIDA-01255 design is targeted to improve the system and CAN performance for automotive isolated ground applications such as cell supervision units, battery control units, inverters, chargers, and so on.

CAN manages message collision and provides a unique proving ground for protocol compliance in any application. Any CAN node may begin to transmit when the bus is free, and two or more nodes may begin to transmit simultaneously. Arbitration is the process by which these nodes battle for control of the bus. Proper arbitration is critical to CAN performance because this is the mechanism that guarantees that message collisions do not reduce bandwidth or cause messages to be lost. Each data or remote frame begins with an identifier, which assigns the priority and content of the message. As the identifier is broadcast, each transmitting node compares the value received on the bus to the value being broadcast. The higher priority message during a collision has a dominant bit earlier in the identifier. Therefore, if a transmitting node senses a dominant bit on the bus in place of the recessive bit it transmitted, it interprets this as another message with higher priority transmitting simultaneously. This node suspends transmission before the next bit and automatically retransmits when the bus is idle.

The evolution of automotive architectures and need for efficient power train and vehicle control mechanisms increased the demand for the number of nodes in vehicles (both passenger and commercial). Improvement in safety architectures increases demand for internal diagnosis and data sharing between multiple nodes with faster response times. The number of nodes to transmit and data loads push the limits of the CAN baud rates while staying within its advantages of reliable robust communication. CAN FD (flexible data rate) is one such flavor of CAN communications, which gained popularity for its flexibility of retaining the features of basic CAN (no change to physical layer) and supports high data rates with little rise in system cost.

Loop delays and round-trip delays are limiting factors in determining arbitration and data speeds (b/s) in classical CAN. In CAN FD, loop delay and network propagation delay are the major limiting factors during the arbitration phase. During the data phase, a secondary sampling point plays an important role for synchronizing data in transmitters. Transceiver delay compensation, which is nothing but a loop delay and offset, is used to check the previously transmitted data with secondary sample registers and check for bit errors.

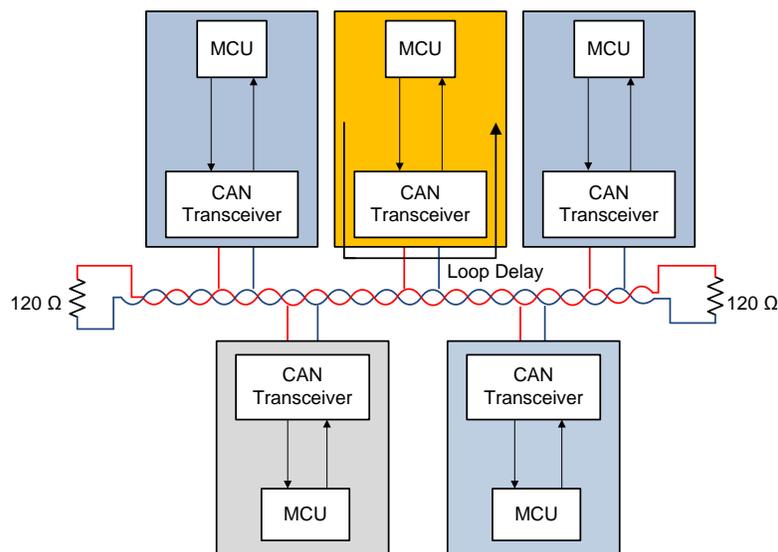


Figure 1. Typical CAN Network

In typical ICE vehicles, loop delay and round-trip delay are straight forward to configure the transceiver delay compensation.

- Transceiver delay compensation = Loop delay + Offset

Factors to influence loop delay in a typical CAN (non-isolated):

- Impedance of controller to transceiver interface
- Transceiver Tx-Rx delay time (dominant or recessive)
- CAN bus impedance

HEV/EV or 48-V systems are isolated from chassis ground based on system architecture. Power and communication interfaces are isolated in high-voltage systems; ground loops are just insulated for 48-V applications. Based on the design of control units, CAN transceivers are isolated from micro controllers as shown in Figure 2. In this case, transceiver delay compensation is increased based on the delay in the digital isolator.

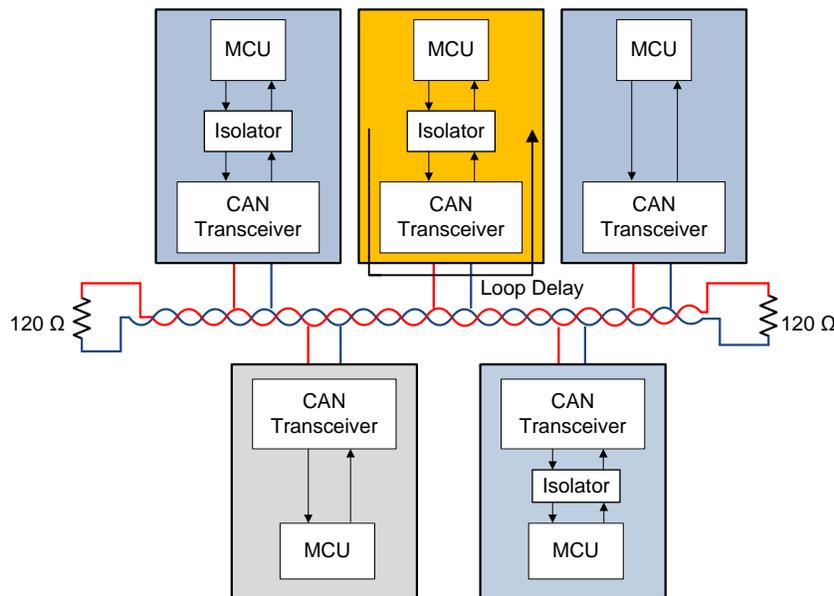


Figure 2. Isolated HEV/EV or 48-V Systems

Factors to influence loop delay in an isolated CAN:

- Impedance of controller to digital isolator
- Propagation delay of digital isolator
- Impedance of digital isolator to CAN interface
- Transceiver Tx-Rx delay time (dominant or recessive)
- CAN bus impedance

Digital isolators play an important role in calculating loop delay. The propagation delay of digital isolators has to account twice for the loop delay calculations in isolated CAN communication bus. Neglecting the bus and controller impedance loop delay of isolated CAN is shown in Figure 3.

Transceiver loop delay compensation = 2 × Propagation delay of isolator + Loop delay of Tx to Rx of CAN transceiver

In a multi-master system such as CAN, it is also important to consider the round-trip delay, which supports in gaining the arbitration of communication bus when two nodes starts transmission at the same time. The maximum round-trip delay or propagation delay in HEV/EV depends on the topology or mounting location of various electronic control units in the vehicle.

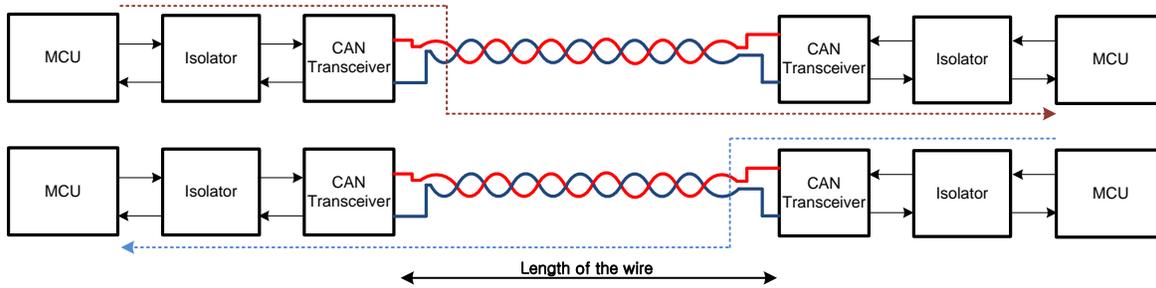


Figure 3. Round-Trip Delay in HEV/EV

Factors to influence round-trip or propagation delay in isolated CAN:

- Impedance of controller to digital isolator
- Propagation delay of digital isolator
- Impedance of digital isolator to CAN interface
- Transceiver Tx-Rx delay time (dominant or recessive)
- CAN bus impedance
- Length of the wire

Based on the CAN physical layer, round-trip delay can be less significant. Neglecting the impedance delays and internal software delays, the approximate round-trip delay of two isolated CAN ECUs can be calculated as per the following equation:

$$\text{Round-trip delay} = 2 \times (\text{Propagation delay of digital isolator 1} + \text{Propagation of CAN1 Tx to bus} + \text{Propagation delay of wire} + \text{Propagation delay of CAN2 bus to Rx} + \text{Propagation delay of digital isolator 2})$$

1.1 Key System Specifications

Table 1. Key System Specifications

PARAMETER	CONDITIONS	MIN	TYP	MAX
TIDA-01255 loop delay	CAN1 Tx to CAN1 Rx	—	136 ns	—
Dominant Tx to CAN bus	$R_L = 60 \Omega, C_L = 4.7 \text{ nF}$	—	67 ns	—
Recessive Tx to CAN bus	1-m wire with $R_L = 60 \Omega, C_L = 4.7 \text{ nF}$	—	69 ns	—
Dominant CAN1 Tx to CAN2 Rx	$R_L = 60 \Omega, C_L = 4.7 \text{ nF}$	—	115 ns	—
Recessive CAN1 Tx to CAN2 Rx	$R_L = 60 \Omega, C_L = 4.7 \text{ nF}$	—	151 ns	—
Rise time of CANH	1-m wire with $R_L = 60 \Omega, C_L = 4.7 \text{ nF}$	30 ns	33 ns	34.31 ns
Fall time of CANH	1-m wire with $R_L = 60 \Omega, C_L = 4.7 \text{ nF}$	60.4 ns	64 ns	66 ns
Operating current of TIDA-01255	CAN baud rate: 500 kbps Isolated supply: 3.3 V	—	12 mA	—
Current flowing while SCB at CAN lines	Battery voltage = 14 V Tx = Low, CAN dominant state	—	0.862 mA	—
Current flowing while SCG at CAN lines	Tx = Low, CAN dominant state	—	0.189 mA	—
Current flowing while SCG at CAN lines during communication at 2 Mbps	Communication is working fine	—	1.29 mA	—
Current flowing while CAN lines are shorted to battery with -14 V	No damages to CAN lines	—	1.257 mA	—

2 System Overview

2.1 Block Diagram

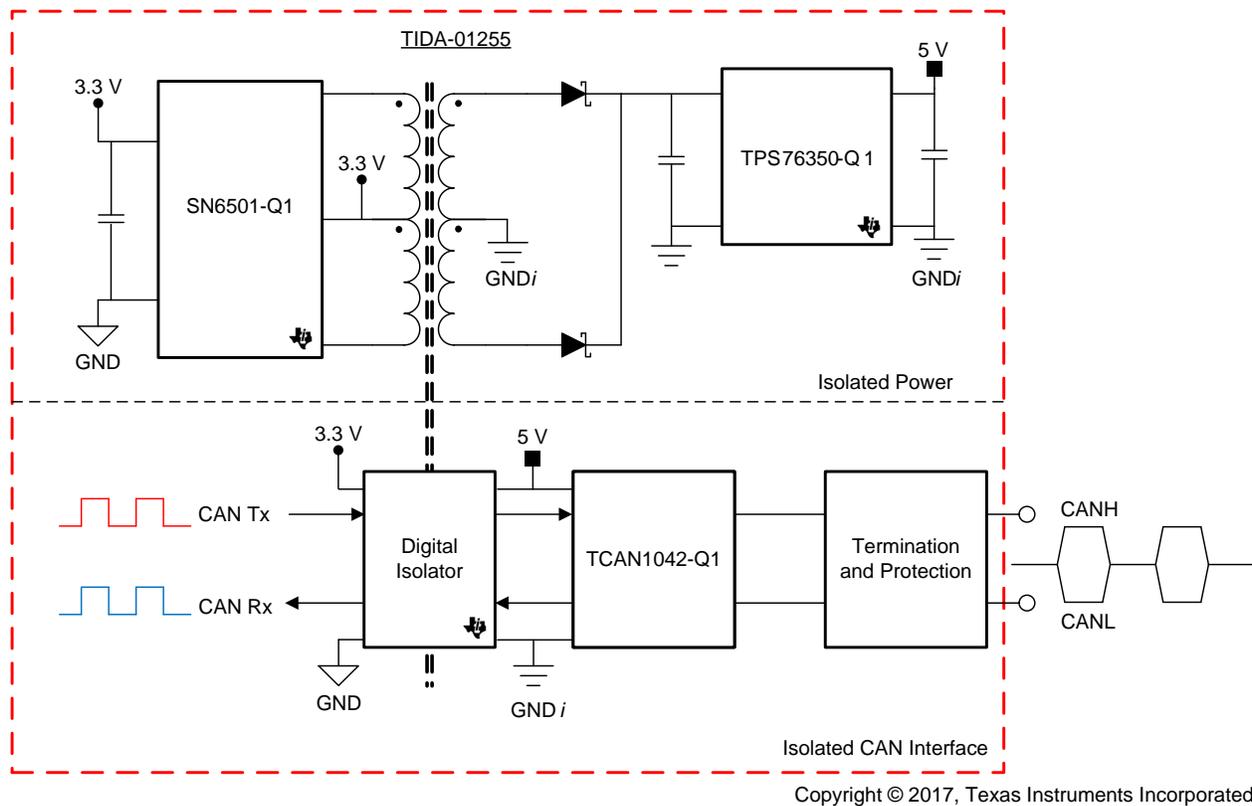


Figure 4. TIDA-01255 Block Diagram

2.2 Highlighted Products

2.2.1 TCAN1042-Q1

This CAN transceiver family meets the ISO 11898-2 (2016) High-Speed CAN physical layer standard. All devices in the TCAN1xxx family are designed for use in CAN FD networks up to 2 Mbps. Devices with part numbers that include the "G" suffix are designed for data rates up to 5 Mbps, and versions with the "V" suffix have a secondary power supply input for I/O level shifting the input pin thresholds and RXD output level. This family has a low-power standby mode with remote wake request feature. Additionally, all devices include many protection features to enhance device and network robustness.

Key features of the TCAN1042-Q1 include:

- AEC Q100: Qualified for automotive applications
- Supports 2-Mbps CAN FD and "G" options support 5 Mbps
- Short and symmetrical propagation delay times and fast loop times for enhanced timing margin
- High impedance bus and logic terminals
- HBM ESD protection: ± 16 kV
- IEC ESD protection: up to ± 15 kV
- Bus fault protection: ± 58 V (non-H variants) and ± 70 V (H variants)
- Undervoltage protection on VCC and VIO (V variants only) supply terminals
- Typical loop delay: 110 ns

2.2.2 ISO7731-Q1

The ISO7731-Q1 is a high-performance, triple-channel digital isolator with 5000- V_{RMS} (DW package) and 2500- V_{RMS} (DBQ package) isolation ratings per UL 1577. This device has reinforced insulation ratings according to VDE, CSA, TUV and CQC. The ISO7731-Q1 provide high electromagnetic immunity and low emissions at low power consumption, while isolating CMOS or LVCMOS digital I/Os. Each isolation channel has a logic input and output buffer separated by a silicon dioxide (SiO₂) insulation barrier. This device comes with enable pins that can be used to put the respective outputs in high impedance for multi-master driving applications and to reduce power consumption. The ISO7731-Q1 device has two forward and one reverse-direction channel. If the input power or signal is lost, the default output is high for devices without the suffix F and low for devices with the suffix F.

Key features of the ISO7731-Q1 include:

- AEC-Q100 qualified with -40°C to 125°C ambient operating temperature
- Signaling rate up to 100 Mbps
- Wide supply and level translation from 2.25 to 5.5 V
- Low power consumption, typical 1.5 mA per channel at 1 Mbps
- Low propagation delay: 11 ns typical (5-V supplies)
- Isolation barrier life: > 40 years
- Reinforced insulation per DIN V VDE V 0884- 10 (VDE V 0884-10):2006-12
- 5000- V_{RMS} (DW) and 2500- V_{RMS} (DBQ) isolation rating per UL 1577
- TUV certification according to EN 60950-1 and EN 61010-1

2.2.3 SN6501-Q1

The SN6501-Q1 is a transformer driver designed for low-cost, small form-factor, isolated DC-DC converters using push-pull topology. The device includes an oscillator that feeds a gate drive circuit. The gate drive, comprising a frequency divider and a break-before-make (BBM) logic, provides two complementary output signals that alternately turn the two output transistors on and off. The output frequency of the oscillator is divided down by an asynchronous divider that provides two complementary output signals with a 50% duty cycle. A subsequent BBM logic inserts a dead time between the high-pulses of the two signals. The resulting output signals, present the gate-drive signals for the output transistors. As shown in Figure 5, before either one of the gates can assume logic high, there must be a short time period during which both signals are low and both transistors are high impedance. This short period, known as BBM time, is required to avoid shorting out both ends of the primary.

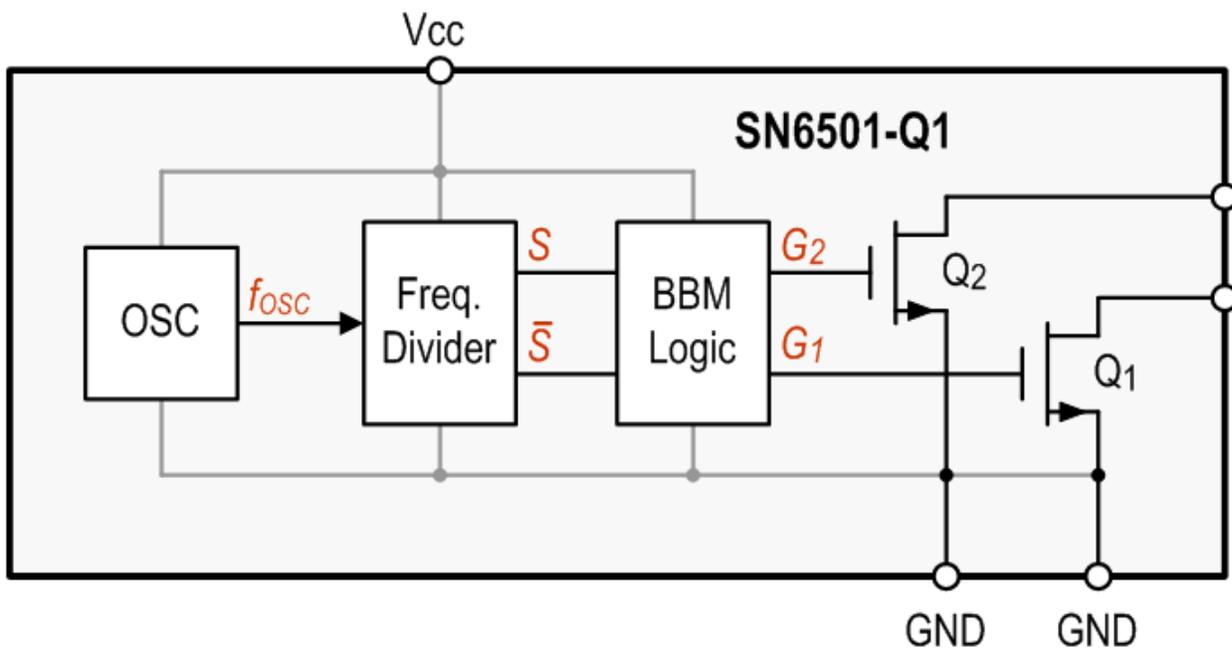


Figure 5. SN6501-Q1 Block Diagram

Key features of the SN6501-Q1 include:

- AEC-Q100 qualified with -40°C to 125°C ambient operating temperature
- Push-pull driver for small transformers
- High primary-side current drive, 5-V supply: 350 mA (max)
- High primary-side current drive, 3.3-V supply: 150 mA (max)
- Single 3.3- or 5-V supply
- Low ripple on rectified output permits small output capacitors
- Device HBM ESD Classification Level H2
- Device CDM ESD Classification Level C4B
- Small 5-pin SOT-23 package

2.2.4 TPS67350-Q1

The TPS763xx-Q1 family of low-dropout (LDO) voltage regulators offers the benefits of LDO voltage, low-power operation, and miniaturized packaging. These regulators feature LDO voltages and quiescent currents compared to conventional LDO regulators. A combination of new circuit design and process innovation has enabled the usual PNP pass transistor to be replaced by a PMOS pass element. Because the PMOS pass element behaves as a low-value resistor, the dropout voltage is low—typically 300 mV at 150 mA of load current (TPS76333-Q1)—and is directly proportional to the load current. Because the PMOS pass element is a voltage-driven device, the quiescent current is low (140 μ A maximum) and stable over the entire range of output load current (0 to 150 mA). Intended for use in portable systems such as laptops and cellular phones, the LDO voltage feature and low-power operation result in a significant increase in system battery operating life.

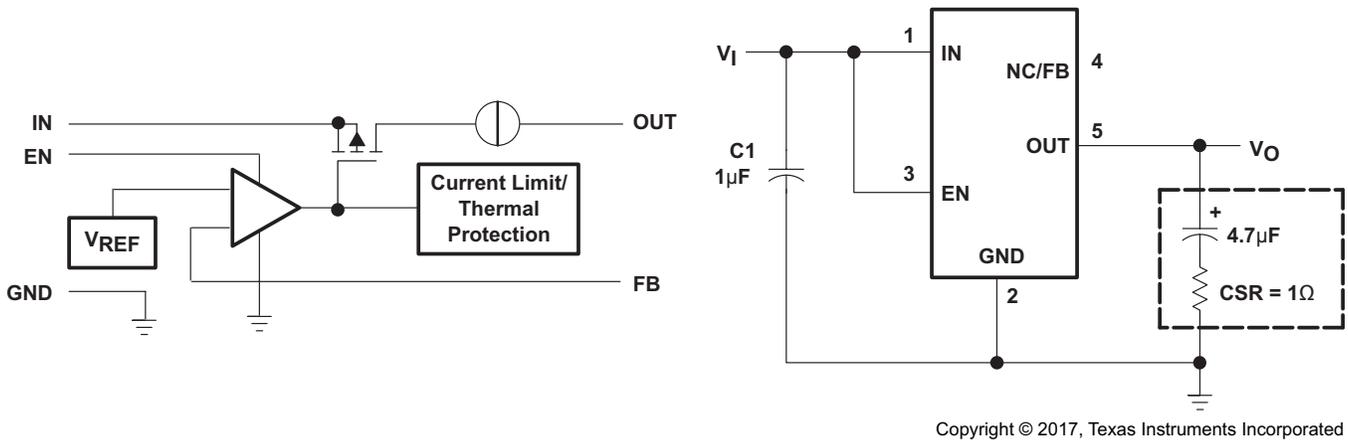


Figure 6. TPS67350-Q1 Block Diagram and Application Circuit

Key features of the TPS67350-Q1 include:

- AEC-Q100 qualified with -40°C to 125°C ambient operating temperature
- 150-mA LDO
- Dropout voltage, typically 300 mV at 150 mA
- Thermal protection and overcurrent limitation
- Less than 2- μ A quiescent current in shutdown mode

3 System Design Theory


The Automotive Reinforced Isolation CAN Reference Design consists of the following subsystems:

- Isolated Power Supply
- Isolated Communication
- CAN FD Communication

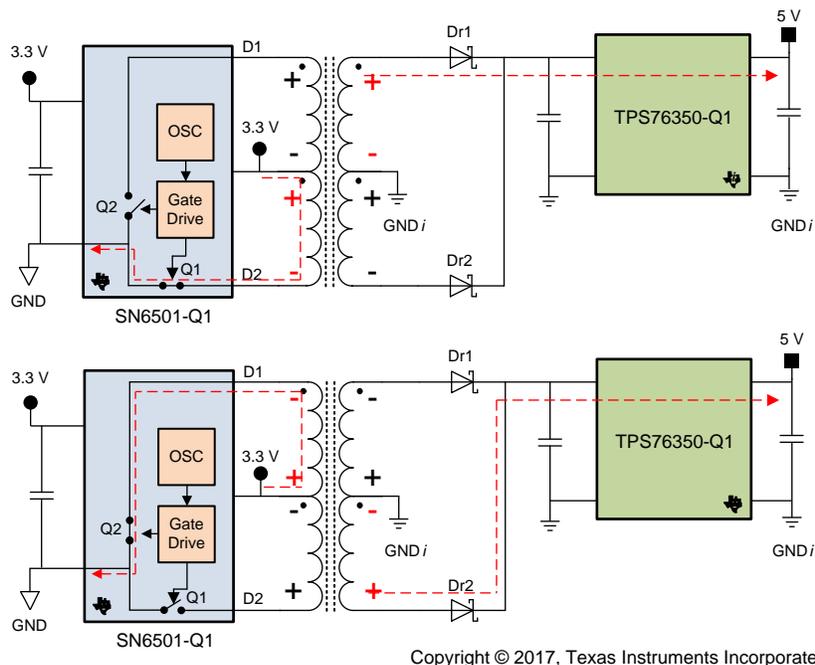3.1 Isolated Power Supply

Typical automotive batteries available in the market are 12 V, 24 V, 48 V, 100 V, 400 V, and 800 V. The list is not limited to the voltages specified in this design guide; they are based on application power levels of such batteries, which vary. Based on the application and design architecture, power can be derived (buck/boost) from local batteries. In few system architectures, energy will be transferred across isolation to support application or increase safety. Considering cost and performance, there are multiple approaches to get the required power across isolation.

The transformer driver is the simple, cost-effective, and efficient solution for isolated power transfers ≤ 2 W. The SN6501-Q1 is an automotive low-noise transformer driver is used for this TI Design. The SN6501-Q1 is a push-pull converter require transformers with center taps to transfer power from the primary to the secondary.



Copyright © 2017, Texas Instruments Incorporated

Figure 7. SN6501-Q1 Working Principle

The SN6501-Q1 consists of an oscillator that feeds a gate drive circuit. The gate drive, comprising a frequency divider and a break-before-make (BBM) logic, provides two complementary output signals that alternately turn the two output transistors on and off (Q1, Q2). The output frequency of the oscillator is divided down by an asynchronous divider that provides two complementary output signals with a 50% duty cycle. BBM logic maintains a dead-time between the high pulses of the two signals. The resulting output signals present the gate drive signals for the output transistors. This short period, known as BBM time, is required to avoid shorting out both ends of the primary.


As shown in [Figure 7](#) when Q1 conducts, it creates a ground path for lower primary end of the center tap, 3.3 V drives a current through the lower half of the primary to ground. Current flowing in the primary winding of transformer will create magnetic flux which will cut the secondary winding. Based on the wiring of the transformer (shown as a dot convention), current will be flowing in the secondary coil. Dr1 is forward biased when Q1 is closed. The secondary current flows through Dr1, charges the capacitor, LDO (TPS76350-Q1), and returns through the load impedance back to the center tap or ground. A similar scenario repeats when Q2 is ON, resulting current flowing in Dr2. Based on the turns ratio and frequency of the SN6501-Q1, unregulated power is transferred across the isolation barrier.

The TPS76350-Q1 uses a PMOS pass element to reduce both dropout voltage and supply current. The PMOS pass element is a voltage-controlled device that does not require increased drive current as output current increases. The supply current of the TPS76350-Q1 is essentially constant from no load to maximum load. Current limiting and thermal protection prevent damage by excessive output current or power dissipation. The device switches into a constant-current mode at approximately 1 A; further load reduces the output voltage instead of increasing the output current. The thermal protection shuts the regulator off if the junction temperature rises above 165°C. Recovery of the LDO is automatic when the junction temperature drops approximately 25°C below the high temperature trip point. The PMOS pass element includes a back diode that safely conducts reverse current when the input voltage level drops below the output voltage level. Thus, the isolated supply is protected and regulated to 5 V and limited to 150 mA of the load current.

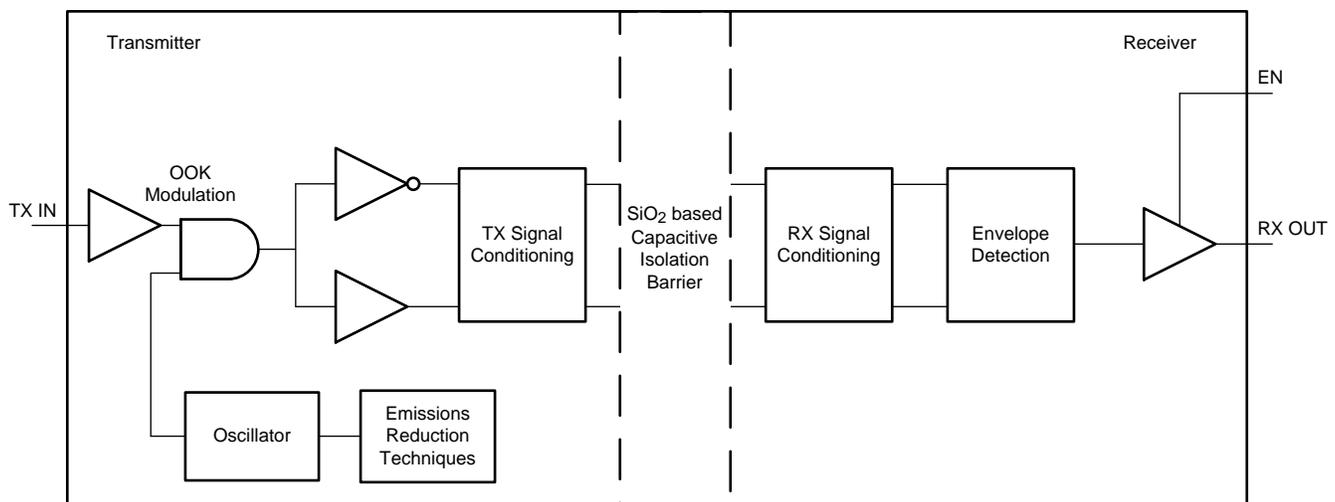3.2 Isolated Communication

Isolation is typically required to prevent DC and unwanted AC currents between two parts of a system, while allowing signal and power transfer between those two parts. Electronic devices and semiconductor ICs used for isolation are called isolators. In general, an isolator can be abstracted as comprising of a high-voltage isolation component or barrier, a transmitter (TX) to couple signal into one side of the isolation component, and a receiver (RX) to convert the signal available on the other side of the isolation component into digital levels (see [Figure 8](#)).

Isolation became mandatory in automotive industry due to the inception of high-voltage and multiple battery topologies. Considering the safety aspects in HEV/EV, there is a need to carry heavy payloads of data in less time to sync the status in various high-voltage components. The ISO 7731-Q1 uses on-off keying (OOK) based isolation communication architecture, which supports the reliable isolated data transfer at faster rates (see [Figure 9](#)).



Copyright © 2016, Texas Instruments Incorporated

Figure 8. Conceptual Block Diagram

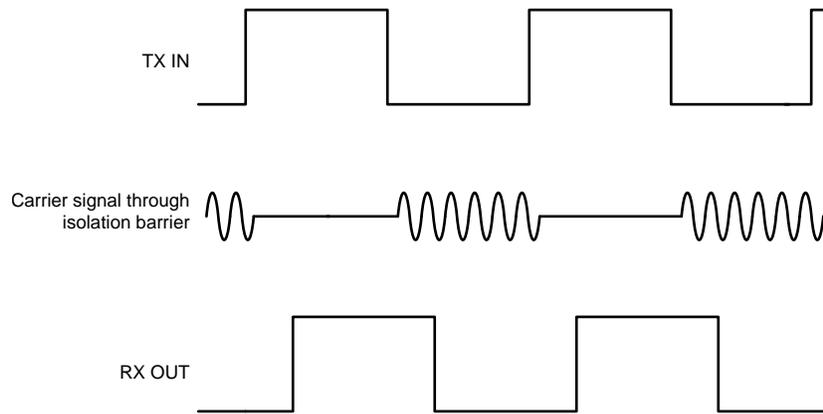


Figure 9. OOK Mechanism in ISO 7731-Q1

As per OOK architecture, incoming digital bitstream is modulated with an internal spread spectrum oscillator clock to generate OOK signaling, such that one of the input states is represented by transmission of a carrier frequency, and the other state by no transmission. This modulated signal is coupled to the isolation barrier and appears in an attenuated form on the receive side. The receive path consists of a pre-amplifier to gain up the incoming signal followed by an envelope detector that serves as a demodulator to regenerate the original digital pattern. The TX and RX signal conditioning circuits are used to improve the common-mode rejection of the channel resulting in better common-mode transient immunity (CMTI). Spread spectrum feature of the architecture will support emissions reduction. ISO 7731-Q1 with a wide body package can withstand $5000 V_{RMS}$ or $3600 V_{PEAK}$.

A typical propagation delay of 11 ns supports the safety and achieve high data rates up to 100 Mbps.

3.3 CAN FD Communication

CAN controllers play a significant role in configuring the CAN communication bus. Based on in-vehicle network topologies, there can be multiple CAN communication buses in a car. They can be classified based on various parameters such as function of electronic control units (body, powertrain, infotainment, ADAS, and so on), type of CAN, baud rates, and ground loops. Typically, CAN 2.0 can support data rates up to 500 kbps, CAN FD architectures can support data rates up to 5 Mbps and greater. While retaining core features of CAN, CAN FD comes up with greater benefits in data baud rates with a short rise in complexity and cost.

CAN FD had an impact on the microcontroller, crystal, and transceiver and little extent on the wiring harness (to support the EMC for high dates). The physical layer of CAN controllers needs to support the change in baud rates. Due to increased data rates, an appropriate crystal needs to be selected to support the CAN timings and error handling. CAN transceiver selection plays an important role for the EMC on CAN bus and delay calculations in CAN timing.

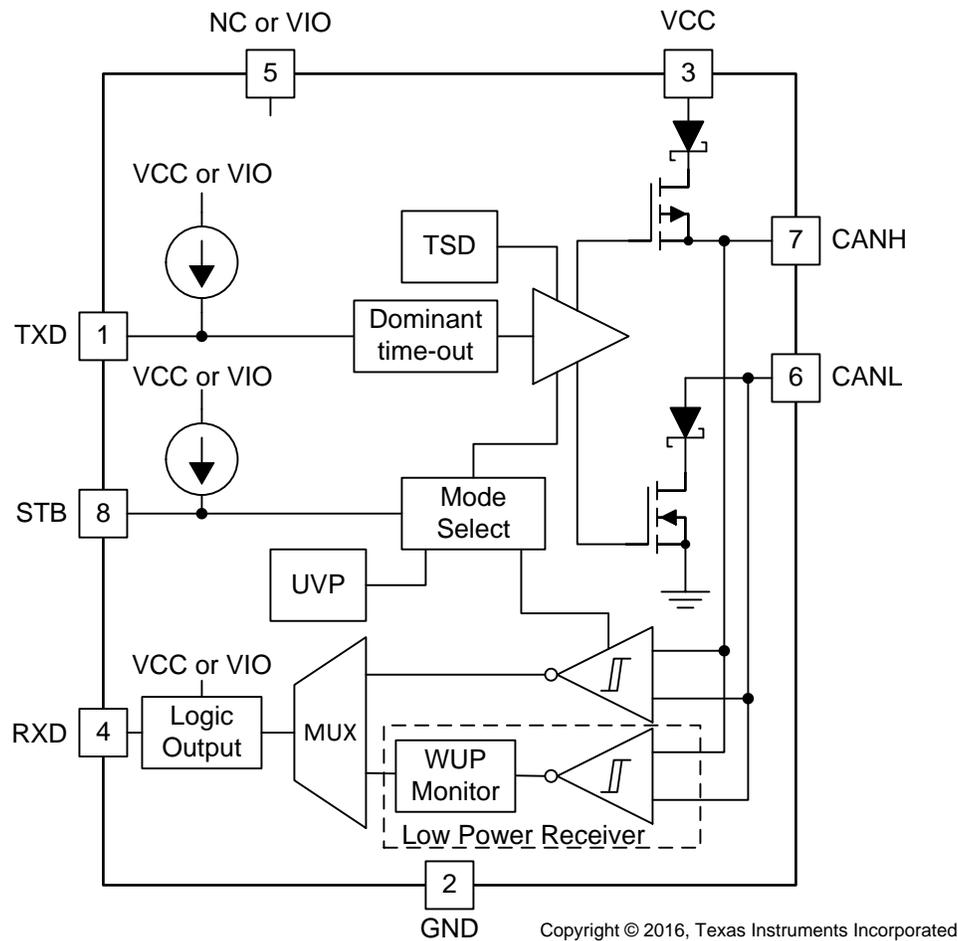


Figure 10. TCAN1042-Q1 CAN Transceiver


The TCAN1042-Q1 CAN transceiver meets the ISO 11898-2 (2016) High-Speed CAN physical layer standard (see [Figure 10](#)). It is designed to support the high data rates up to 5 Mbps (G-version). The device has options to be compatible with 3.3- and 5-V TTL input by selecting the V_{IO} pin voltage appropriately. The dominant time out feature enables the CAN communication bus to be error free due to error in the microcontroller. If a dominant bit is being transmitted by the microcontroller, due to internal software or hardware issues, the controller does not respond any more, and the CAN transceiver will free up the communication bus after the dominant time out delay (minimum 1.2 ms or max 3.8 ms). The wake up monitor circuit allows low-power modes to the CAN transceiver and electronic control units. This feature saves the need for an external wake up pin and wire and allows the system to stay in standby mode. With an appropriate wake up pattern, electronic control units can be retrieved to a run state from sleep or standby states.

Thermal shutdown and short circuit current limit features in the TCAN1042-Q1 improves the reliability and robustness of CAN communication. During thermal shutdown, the device turns off the CAN driver circuits, thus blocking the TXD-to-bus transmission path, so CANH and CANL are biased to the recessive level during a thermal shutdown and the receiver-to-RXD path remains operational. CAN bus driver pins are protected by a short-circuit limit feature irrespective of the state of the input (dominant or recessive).

Transceiver delay plays an important role for the bit timing calculations in CAN FD. The total loop delay of the transceiver is typically 110 ns and worst case 175 ns, which is good enough to support high data rates.

4 Getting Started Hardware and Software

4.1 Hardware

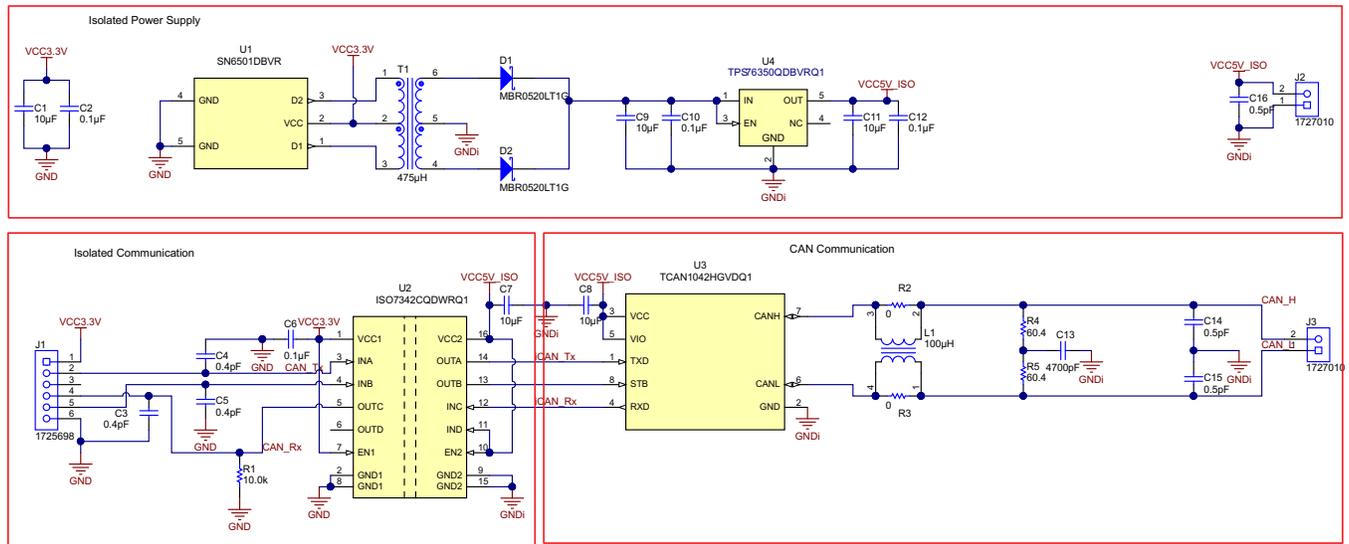

Copyright © 2017, Texas Instruments Incorporated

Figure 11. TIDA-01255 Schematic

The SN6501-Q1 can be used to generate the isolated power less than 1 W. This can be used to generate the bias power, sensors, or light isolated loads (to power few IC's).

- Input power: 3.3 V, 150 mA
- Output power: 5 V, 100 mA

Detailed steps for designing the SN6501-Q1 are provided in the device datasheet. T1 is selected with a 1:2 ratio, which gives max regulated voltage from 6 to 7 V on the secondary side (pins 6,4 of T1). After the diode drop (D1,D2), the voltage at input of the TPS76350-Q1 will be around 6.5 V. The regulated output voltage of 5 V is generated from U4 of the TPS76350-Q1.

- C1,C2 are the filter capacitors, which are placed near the VCC pin of U1 of the SN6501-Q1.
- T1 is a center tapped transformer connected U1 is selected based on input and output voltage. A 475- μ H SMT transformer from 760390015 has been used for T1.
- D1 and D2 are Schottky diodes that are used for low forward voltage drop and rectify the output voltage.
- U4 of the TPS76350-Q1 is used to regulate the output voltage from the transformer driver, whereas C9,C10, C11, and C12 should be placed close to the U4 and are used to filter the output voltage.
- C6, C7 are the decoupling capacitors used for ISO 7731-Q1. C3, C4, and C5 are ESD capacitors used only on this board, based on ECU's layout these capacitors can be placed or neglected.
- U2 of ISO 7731-Q1 supports reinforced signal isolation for transferring CAN Tx, CAN Rx, and standby pins from controller to U3 (TCAN1042-Q1).

Either the common-mode choke L1 or bypass resistors R2,R3 are populated on the PCB. The common-mode choke is placed on the PCB based on EMC requirements of the ECU. R4, R5 and C13 is the popular split resistor termination used for CAN communication. C14 and C15 are the nominal ESD capacitors to be placed near the connector.

Table 2 lists the important parameters for designing the isolated CAN interface with the TIDA-01255 design.

Table 2. Isolated CAN Calculations

PARAMETER	MIN (ns)	TYP (ns)	MAX (ns)
Propagation delay of isolator (ISO7731-Q1)	6.0	11	16.0
Transceiver propagation delay time of TCAN1042-Q1 ($R_L = 60 \Omega$, $C_L = 100 \text{ pF}$)	—	110	175.0
Propagation delay of Tx to CAN bus	—	55	75.0
Propagation delay of CAN bus to Rx	—	50	65.0
Propagation delay of physical 1-m copper wire (estimation)	4.8	5	5.3
Approximate loop delay CAN message with TIDA-01225	—	132	208.0
Approximate round trip delay of CAN message with two TIDA-01255 boards located 30 m apart	—	454	556.0

4.2 Software

Software for the CAN is developed and generated based on customer requirements and the microcontroller of the ECU. The CAN calculation table can be used for internal baud rate calculations. TIDA-01255 hardware can be tested directly interfacing with the microcontroller of the ECU. The TIDA-01255 can be tested directly by interfacing with TMS570 LaunchPad™ devices.

Hardware Abstraction Layer Code Generator (HALCoGen) and Code Composer Studio™ (CCS) can be used to generate the software to test the CAN interface. Follow the instructions provided in Hercules™ LaunchPad.

1. Download and Install [HALCoGen](#), [Code Composer Studio](#).
2. Open the HALCoGen SW → File → New → Project.
3. Select the microcontroller family for the LaunchPad. Select the appropriate device. Give the user defined project name and select a location to save the project.

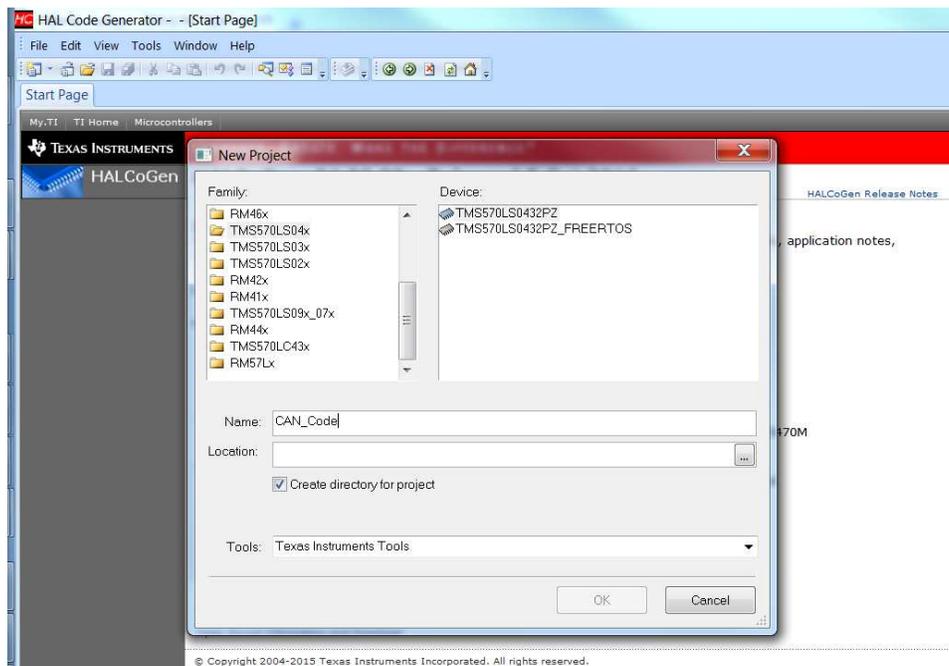


Figure 12. HALCoGen Project Creation

4. Select the driver enable, and unmark all drivers. Based on the scope of the project, select the appropriate drivers such as CAN, GIO, SCI, ADC, and so on.

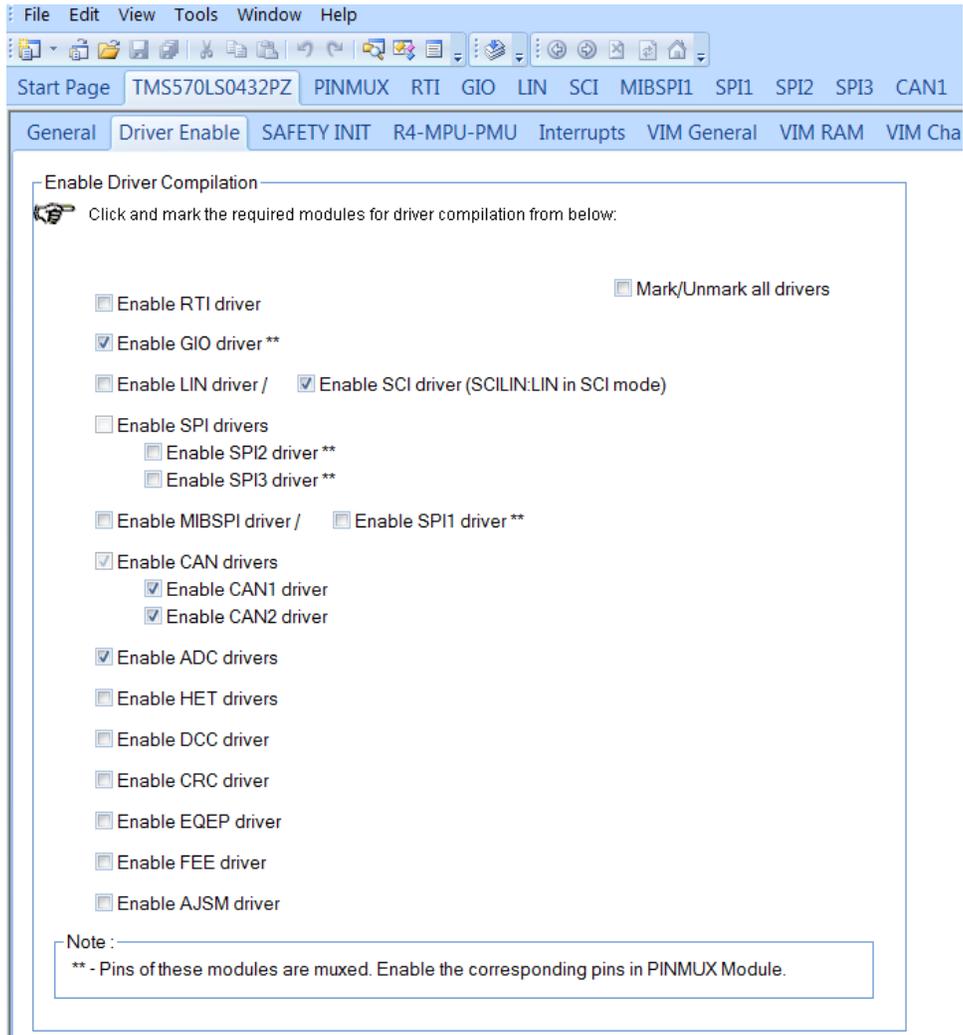


Figure 13. HALCoGen Enable Driver

5. Edit the settings for the drivers such as SCI, CAN1, and CAN2. Update the bit rate as per the design, check the propagation delay for the given baud rate, and complete the system settings.

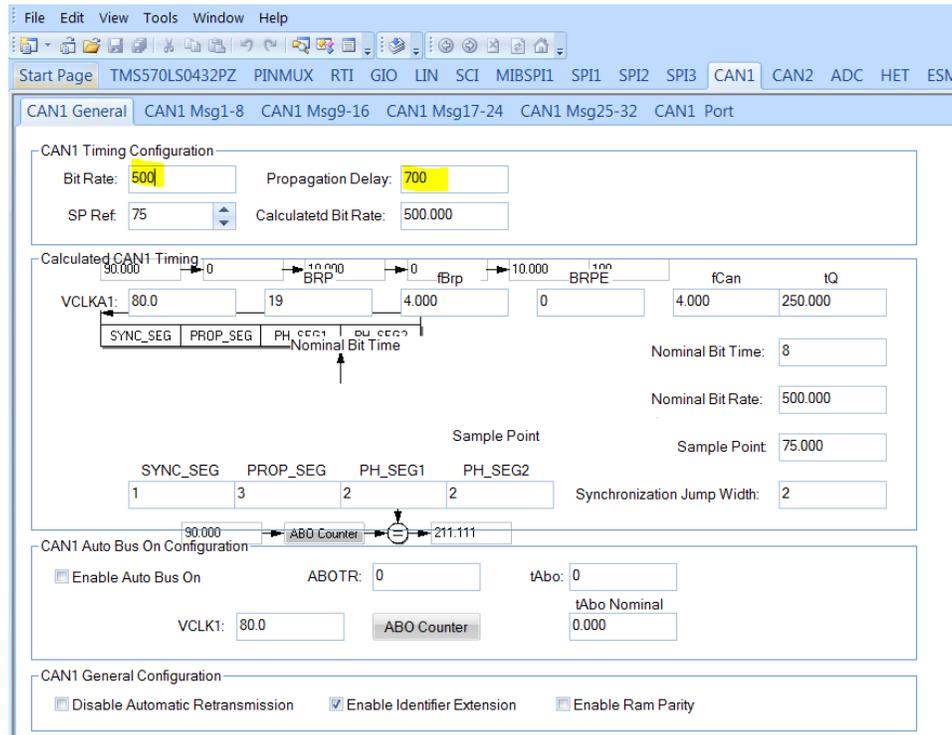


Figure 14. HALCoGen CAN Configuration

6. Generate the code in HALCoGen by pressing F5.
7. Open CCS. Press File → New → Project → CCS project under Code Composer Studio.

8. Select the target and device as per the family of LaunchPad. Select the connection type as per the LaunchPad interface to PC. Provide the same project name and location that was given in HALCoGen. Select the empty project without any main.c and press Finish to create the CCS project.

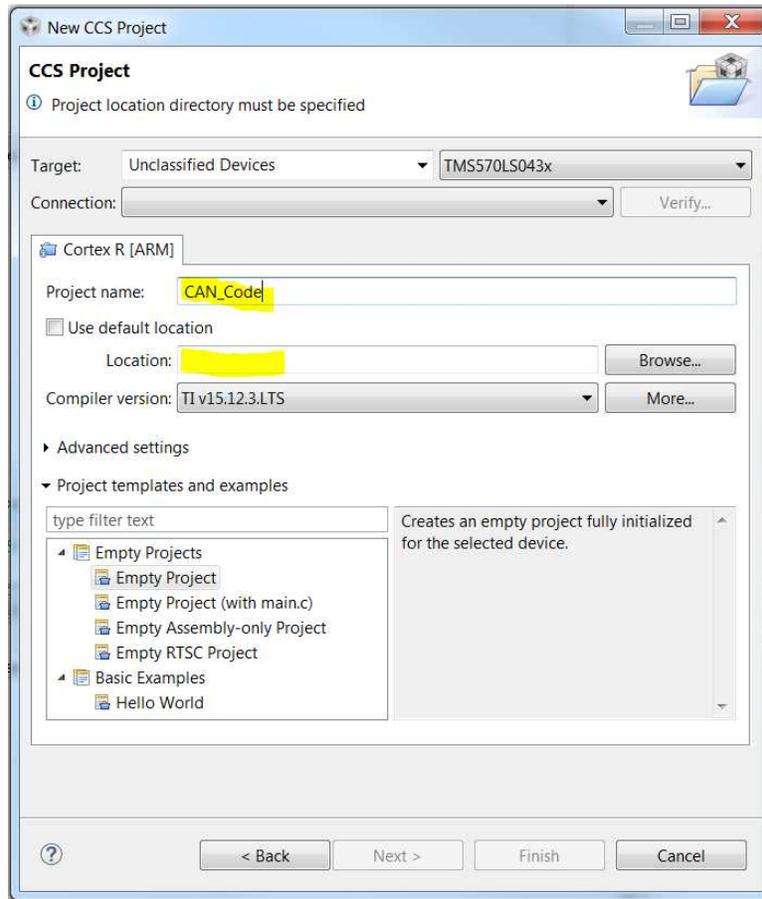


Figure 15. CCS Project Creation

9. Include the files created in HALCoGen, right click on the Project → Properties → Build → ARM compiler → Include options → Add the path of include folder generated from HALCoGen.

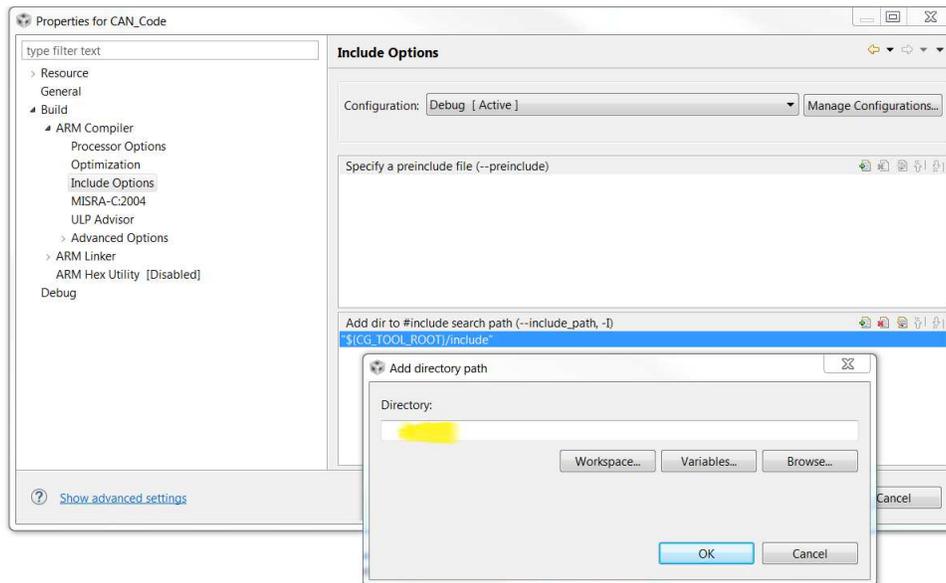


Figure 16. CCS Include Files

10. Start writing the user code section in the sys_main.c file. Build and load the code in CCS to the target LaunchPad and test the CAN communication.

5 Testing and Results


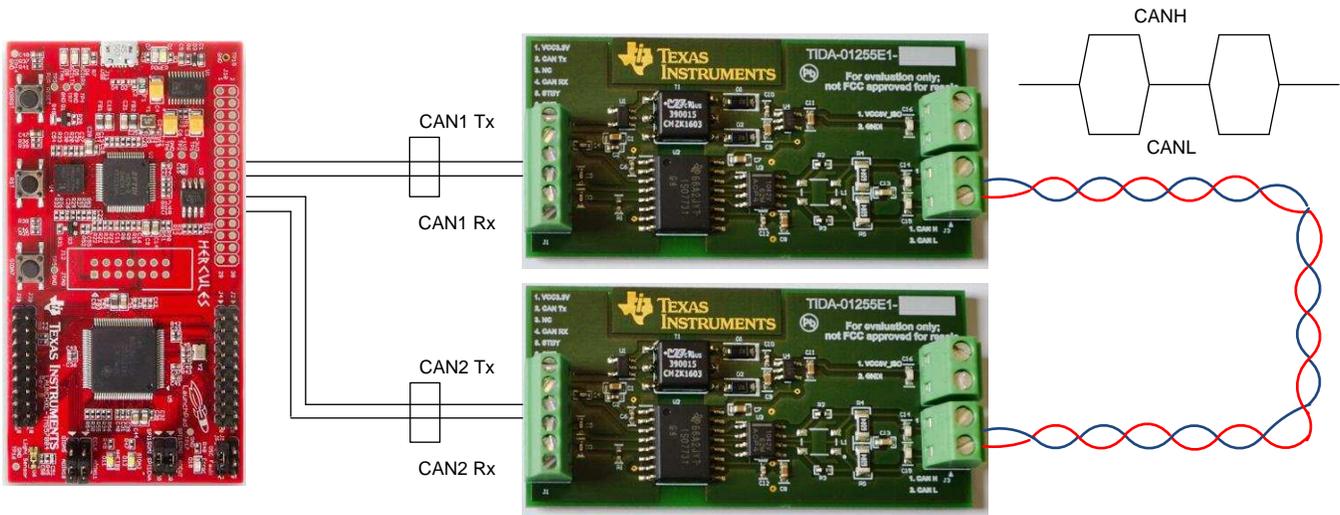


Figure 17. Test Setup for TIDA-01255

The TIDA-01255 design was tested using the TMS570LS04x LaunchPad. Two TIDA-01255 boards are connected as shown in [Figure 17](#).

- Software is built in CCS in such a way that data is sent from "CAN1", which is acknowledged by "CAN2" of the same LaunchPad. A laptop is used to monitor the registers and communication of LaunchPad.
- Baud rate of CAN communication is set in HALCoGen. The latest files are built and loaded into launch to check the performance of the TIDA-01255.
- Twisted pair wiring harness with different lengths is used to connect the CANH and CANL.
- Tests are performed for different configurations of wire lengths and baud rates.

5.1 Operational Tests

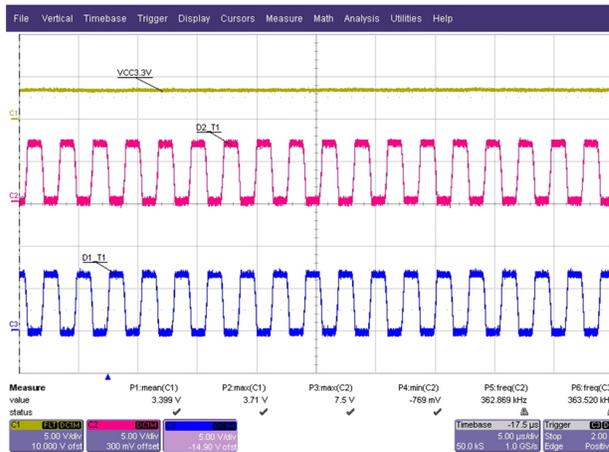


CH1: VCC3.3V
 CH2: D2 pin of SN6501-Q1 primary
 CH3: D1 pin of SN6501-Q1 primary

NOTE: Isolated power primary side

Max of D1,D2 = 7.5 V
 Min of D1,D2 = 0.769 V
 Frequency of D2 = 362 kHz
 Frequency of D1 = 363 kHz

Figure 18. SN6501-Q1 Primary Side

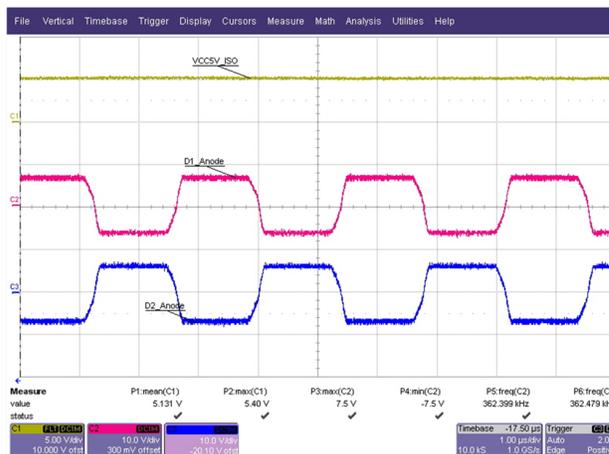


CH1: VCC3.3V
 CH2: Anode pin of D1, secondary side
 CH3: Anode pin of D2, secondary side

NOTE: Isolated power secondary side

Max of D1,D2 = 7.5 V
 Min of D1,D2 = 0.769 V
 Frequency of D2 = 362 kHz
 Frequency of D1 = 362 kHz

Figure 19. SN6501-Q1 Secondary Side

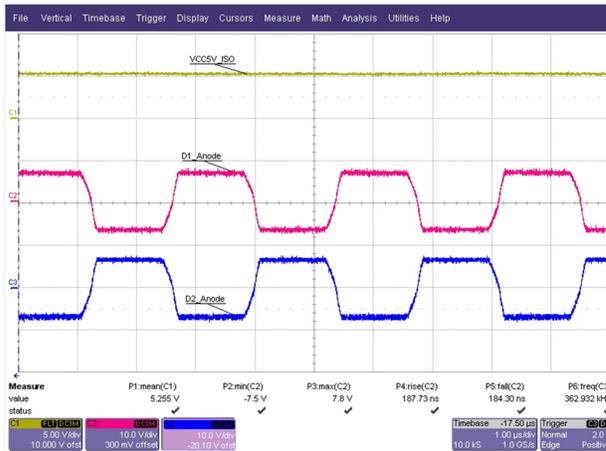


CH1: VCC3.3V
 CH2: Anode pin of D1, secondary side
 CH3: Anode pin of D2, secondary side

NOTE: Isolated power secondary side

Max of D1,D2 = 7.5 V
 Min of D1,D2 = 0.769 V
 Frequency of D2 = 362 kHz
 Rise time of D1,D2 = 187 ns
 Fall time of D1,D2 = 184 ns

Figure 20. SN6501-Q1 Secondary Side (Rise and Fall Times)

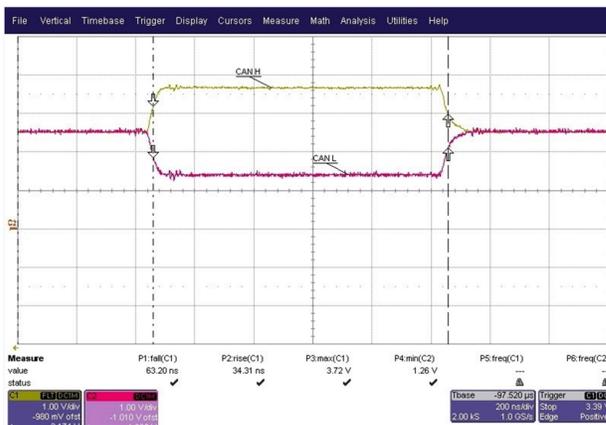


CH1: CAN high
 CH2: CAN low

NOTE: CAN message with 1-m wire, ground wire along with CANH and CANL

Recessive of CANH and CANL = 2.5 V
 Dominant of CANH = 3.72 V (Max)
 Dominant of CANL = 1.26 V (Min)
 Rise time of CANH = 34.31 ns
 Fall time of CANH = 63.20 ns

Figure 21. CAN Message With Common Ground

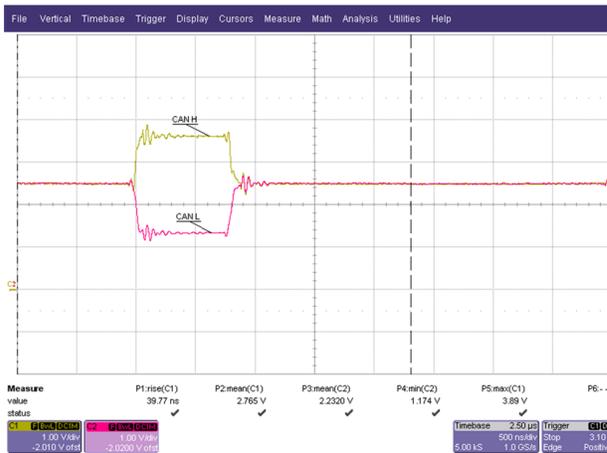


CH1: CAN high
CH2: CAN low

NOTE: CAN message with 1-m wire, no ground wire; only CANH and CANL are connected

Recessive of CANH and CANL = 2.5 V
Dominant of CANH = 3.89 V (max)
Dominant of CANL = 1.174 V (min)
Rise time of CANH = 40 ns

Figure 22. CAN Message Without Common Ground

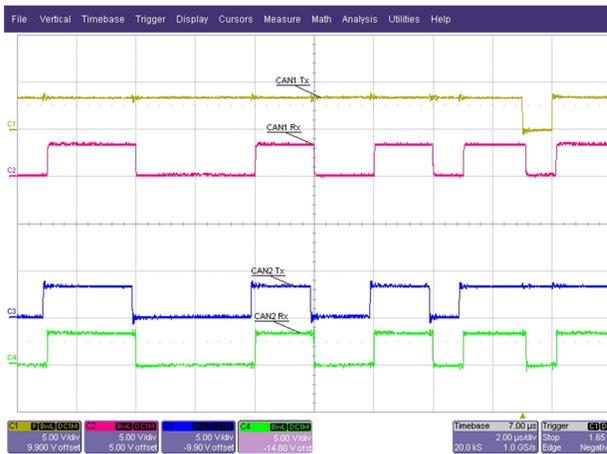


CH1: CAN1 Tx
CH2: CAN1 Rx
CH3: CAN2 Tx
CH4: CAN2 Rx

NOTE: CAN message with 1-m wire, messages from CAN2 and ACK from CAN1

Figure 23. CAN Message Without Common Ground (CAN1 ACK)

5.2 Performance Tests

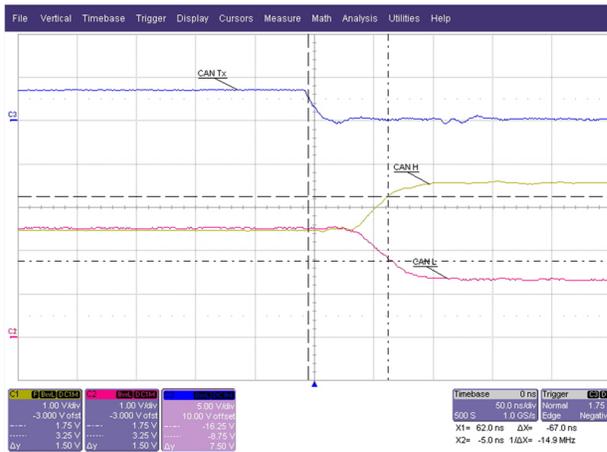


CH1: CAN high
CH2: CAN low
CH3: CAN Tx

NOTE: CAN message with 1-m wire, TIDA-01255 propagation delay (recessive to dominant)

Dominant: Delay of Tx to CAN = 67 ns

Figure 24. TIDA-01255 Tx to CAN (Recessive to Dominant)

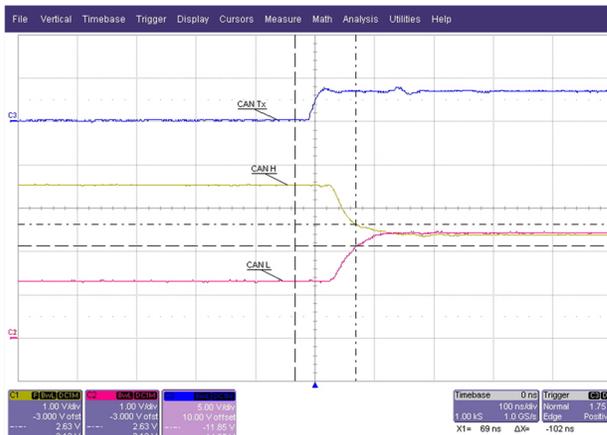


CH1: CAN high
CH2: CAN low
CH3: CAN Tx

NOTE: CAN message with 1-m wire, TIDA-01255 propagation delay (dominant to recessive)

Recessive: Delay of Tx to CAN = 69 ns (approximately)

Figure 25. TIDA-01255 Tx to CAN (Dominant to Recessive)

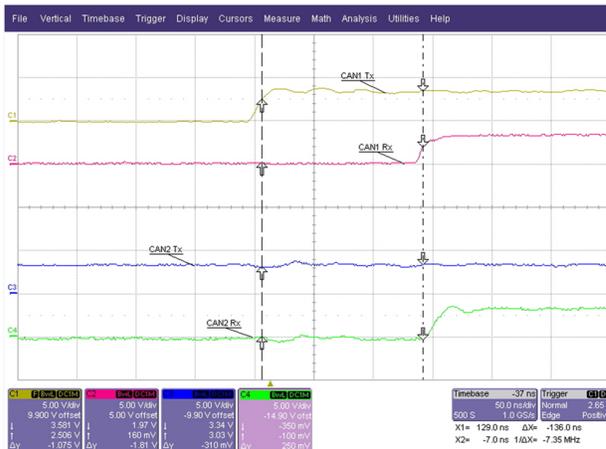


CH1: CAN1 Tx
 CH2: CAN1 Rx
 CH3: CAN2 Tx
 CH4: CAN2 Rx

NOTE: CAN message with 1-m wire, loop delay of TIDA-01255 CAN1 Tx to Rx

Loop delay of TIDA-01255 = 136 ns (approximately)

Figure 26. TIDA-01255 Loop Delay

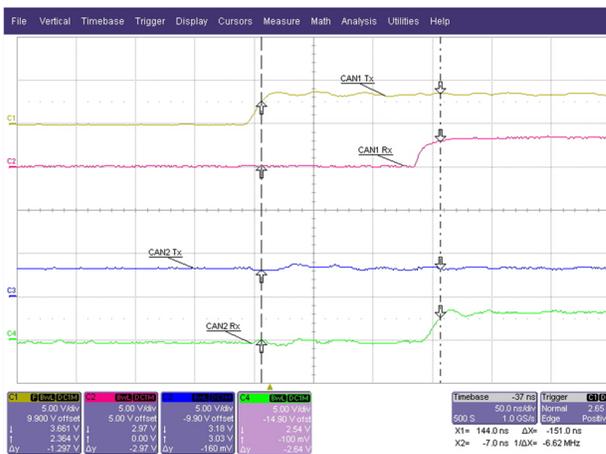


CH1: CAN1 Tx
 CH2: CAN1 Rx
 CH3: CAN2 Tx
 CH4: CAN2 Rx

NOTE: CAN message with 1-m wire, transmission delay from one TIDA-01255 to another (half of round trip delay with 1-m wire)

Recessive: Delay of CAN1 Tx to CAN2 Rx = 151 ns (approximately)

Figure 27. TIDA-01255 Half Round-Trip Delay (Recessive)

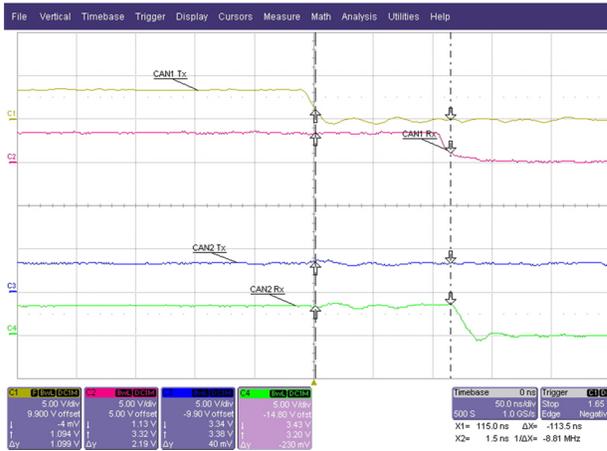


CH1: CAN1 Tx
 CH2: CAN1 Rx
 CH3: CAN2 Tx
 CH4: CAN2 Rx

NOTE: CAN message with 1-m wire, transmission delay from one TIDA-01255 to another (half of round trip delay with 1-m wire)

Dominant: Delay of CAN1 Tx to CAN2 Rx = 115 ns (approximately)

Figure 28. TIDA-01255 Half Round-Trip Delay (Dominant)

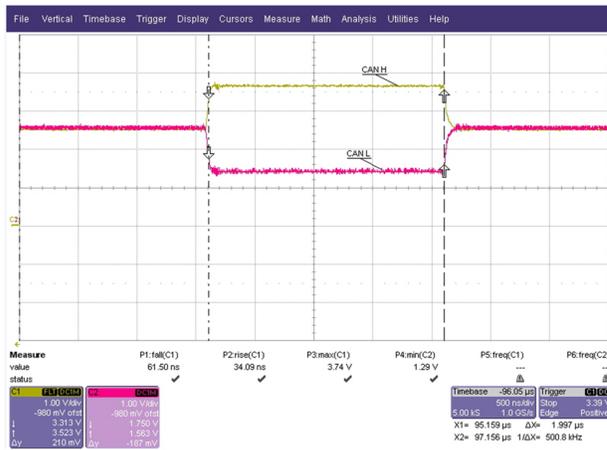

CH1: CANH
 CH2: CANL

NOTE: 500-kbps CAN message, 1-m twisted pair wiring harness

Dominant: Delay of CAN1 Tx to CAN2 Rx = 115 ns (approximately)

Figure 29. TIDA-01255 500 kbps (Single Bit)



CH1: CANH
CH2: CANL

NOTE: 500-kbps CAN message, 1-m twisted pair wiring harness

Recessive of CANH and CANL = 2.5 V
Dominant of CANH = 3.73 V (max)
Dominant of CANL = 1.26 V (min)
Rise time of CANH = 33.98 ns
Fall time of CANH = 66.34 ns

Figure 30. TIDA-01255 500 kbps (Multiple Bits)



CH1: CANH
CH2: CANL

NOTE: 1-Mbps CAN message, 1-m twisted pair wiring harness

Recessive of CANH and CANL = 2.5 V
Dominant of CANH = 3.72 V (Max)
Dominant of CANL = 1.26 V (Min)
Rise time of CANH = 34.31 ns
Fall time of CANH = 63.20 ns

Figure 31. TIDA-01255 1 Mbps

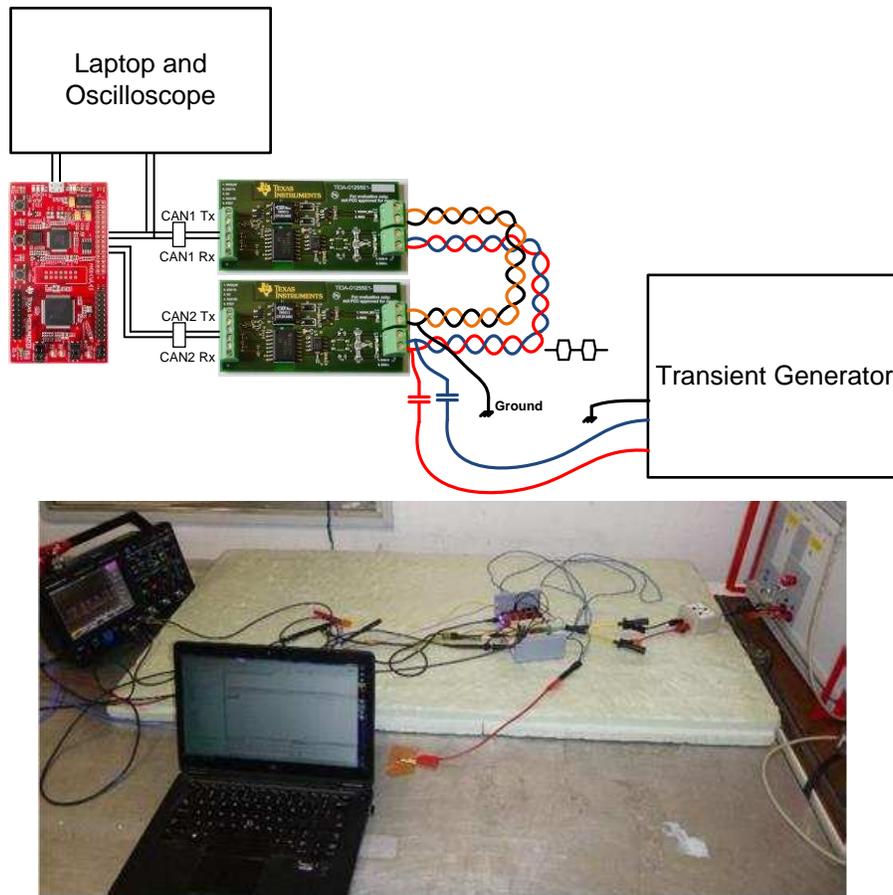


Figure 34. Capacitive Coupling Test Setup

NOTE: Harness length = 1.7 m

An oscilloscope is used to monitor CAN1 Tx and CAN1 Rx. The laptop is used to control and monitor the TMS570 LaunchPad to get the status of the CAN. The setup box is used to couple the transient with a 100-nF capacitance from the transient generator to the CAN wiring harness. As two TIDA-01255 boards are connected back to back, DCC tests are performed only once for each test leg.

Table 3. Transient Immunity Test Results

TEST CASE	VOLTAGE LEVEL (V)	TEST DURATION (MIN)	OBSERVATION
DCC Slow –	–45	5	TIDA-01255 works fine. No impact on CAN communication. Performance A
DCC Slow +	45	5	TIDA-01255 works fine. No impact on CAN communication. Performance A
DCC Slow –	–85	1	TIDA-01255 works fine. No impact on CAN communication. Performance A
DCC Slow +	85	1	TIDA-01255 works fine. No impact on CAN communication. Performance A

5.3.2 RF Immunity: Bulk Current Injection

RF immunity of ECUs are done with the proper application software based on the type of systems (engine EMS, vehicle control unit, body control, transmission control, battery control, DC-DC, inverter, OBC, and so on). Critical parameters of the system are monitored and measured during the RF immunity tests. Communication of safety critical nets is important, which is not expected to disturb while performing these tests. Based on the type of end system, performance and pass criteria is defined for the bulk current immunity tests. The TIDA-01255 is tested with just an CAN application layer software, which does not include supervisor or watchdog systems. Performance of the TIDA-01255 and TCAN1042-Q1 can be different when used with an end application software.

Bulk current injection (BCI) tests are performed in an external test house as per ISO 11452-4.

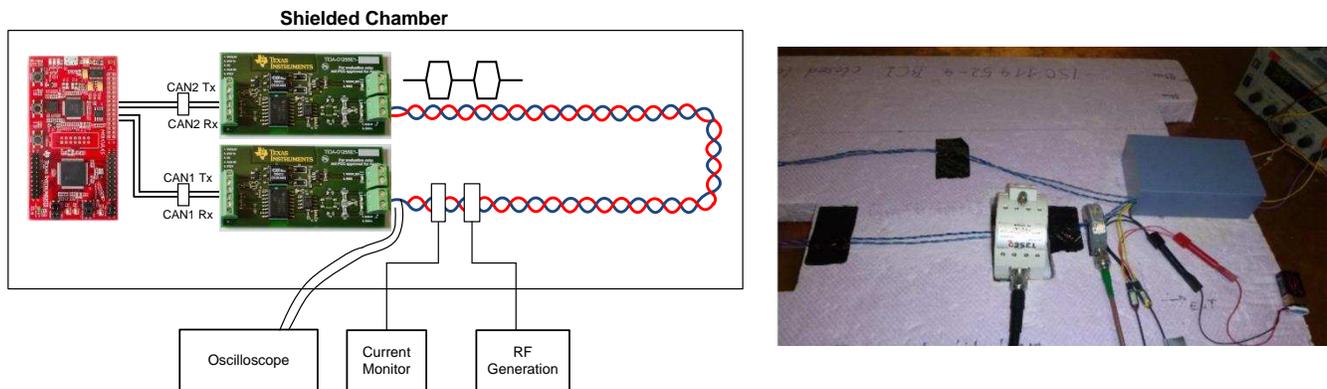


Figure 35. BCI Setup and Injector Probe at 15 cm

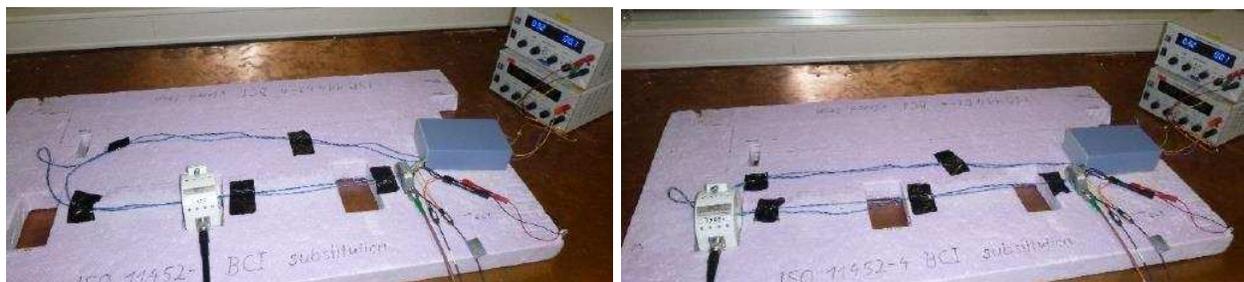


Figure 36. BCI Test Setup for Injector Probes at 45 and 75 cm

Table 4. BCI Test Parameters

PARAMETER	DESCRIPTION		
Frequency modulation	Continuous Wave AM (1 kHz, 80 %)		
Frequency steps	300 kHz for 0.1 to 1 MHz	1 MHz for 1 to 200 MHz	2 MHz for 200 to 400 MHz
Dwell time	2 sec		
Distance of EuT – Clamp	15 cm	45 cm	75 cm

Table 5. BCI Test Plan

TEST LEVEL	FREQUENCY RANGE (MHz)	CATEGORY 1 dB(μ A)	CATEGORY 2 dB(μ A)	CATEGORY 3 dB(μ A)
Level 2	0.1 to 2.38	90	90	Not specified
	2.38 to 15	106-20 log(15/f)	106-20 log(15/f)	
	15 to 88	106	106	
	88 to 400	106-10 log(f/88)	106-10 log(f/88)	
Level 1	0.1 to 2.38	82	90	90
	2.38 to 15	98-20 log(15/f)	102-20 log(15/f)	106-20 log(15/f)
	15 to 88	98	102	106
	88 to 400	98-10 log(f/88)	102-10 log(f/88)	106-10 log(f/88)

BCI tests results for the TIDA-01255 with a 500-kbps CAN baud rate are as follows:

- Category 2 Level 1 for 15 cm, no damage to components. The TIDA-01255 is working fine upon reset. *Performance C* is achieved.
- Category 3 Level 1 for 15 cm, no damage to components. The TIDA-01255 is working fine upon reset. *Performance C* is achieved.
- Category 2 Level 1 for 45 cm, no damage to components. The TIDA-01255 is working fine upon reset. *Performance C* is achieved.
- Category 2 Level 1 for 75 cm, no damage to components. The TIDA-01255 is working fine upon reset. *Performance C* is achieved.

Tests are done on the LaunchPad with basic software without any supervisor or watchdog system. Performance of the TCAN1042-Q1 and system can be improved by using software built for relevant control units.

5.3.3 RF Emissions

RF emission tests are done on the TIDA-01255 in an anechoic chamber at the EMC test house. The LaunchPad is flashed with different software that enable CAN communication at different baud rates. More details are available upon request.

5.3.4 ESD

Testing has been performed in accordance with ISO 10605. Tests are carried out in a shielded chamber. Test setup is done as per [Figure 37](#).

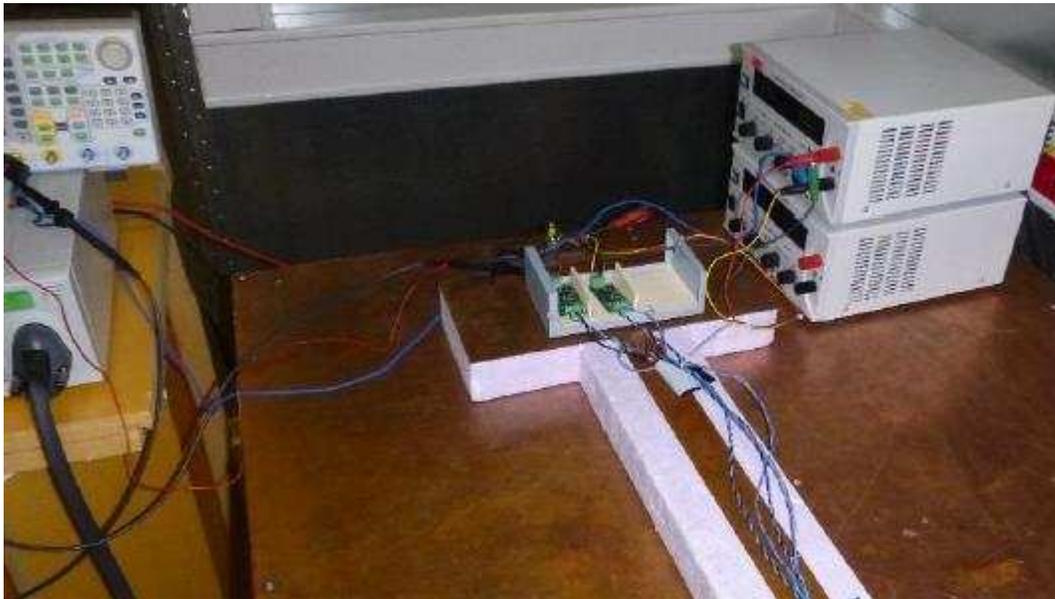


Figure 37. ESD Test Setup

ESD tests are performed with two TIDA-01255 boards connected back to back as shown in [Figure 37](#). Wire length is 1.7 m.

Table 6. ESD Test Results

DISCHARGE SEQUENCE	TYPE OF DISCHARGE	VOLTAGE LEVEL (kV)	RESULT
1	Contact discharge C = 330 pF, R = 2 kΩ	4	Performance A
2		-4	Performance A
3	Air discharge C = 330 pF, R = 2 kΩ	4	Performance A
4		-4	Performance A
5	Contact discharge C = 330 pF, R = 2 kΩ	8	Performance A
6		-8	Performance A
7	Air discharge C = 330 pF, R = 2 kΩ	8	Performance A
8		-8	Performance A
9	Air discharge C = 330 pF, R = 2 kΩ	15	Performance A
10		-15	Performance A

No disturbance happened to CAN communication. CAN waveforms are monitored in the oscilloscope while ESD tests are being performed. Both TIDA-01255 boards were working fine after completing all ESD tests.

6 Design Files

6.1 Schematics

To download the schematics, see the design files at [TIDA-01255](#).

6.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01255](#).

6.3 PCB Layout Recommendations

For the optimal performance of the system, follow best practices of designing the PCB. Isolated power and CAN lines are critical, which affect the performance of the system.

- Place U1 SN6501-Q1 near to the transformer T1. Take care to have short traces and symmetry from D1, D2 to T1.

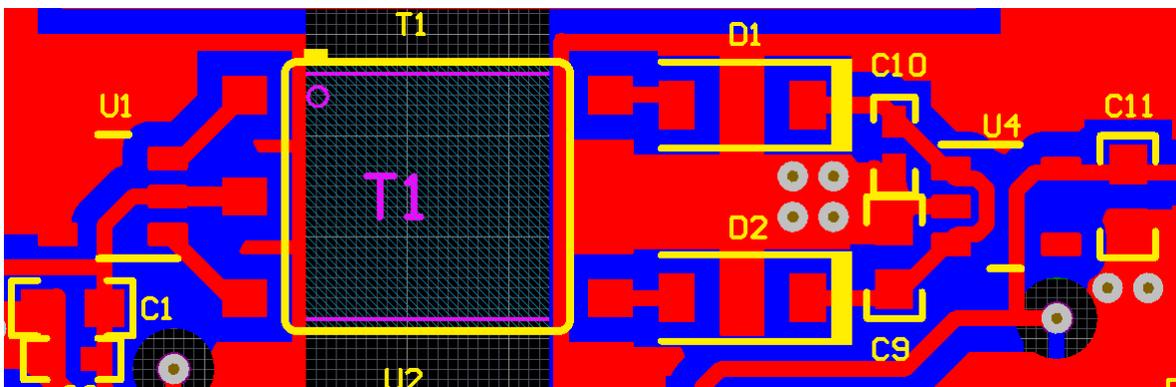


Figure 38. Isolated Power Supply

- As shown in [Figure 38](#), Schottky diodes D1 and D2 are in symmetry and to be placed with less track length to avoid high trace inductances.
- Based on the number of layers of the PCB, there should be vias or short resistance path to isolated ground to the ground pins of the center tapped transformer and LDO.
- Creepage distance of the isolated sections should be defined based on the customer requirements. Based on the type of material, creepage distance will vary on the PCB. For more details of layout recommendations, see the [Digital Isolator Design Guide](#) (SLLA284).

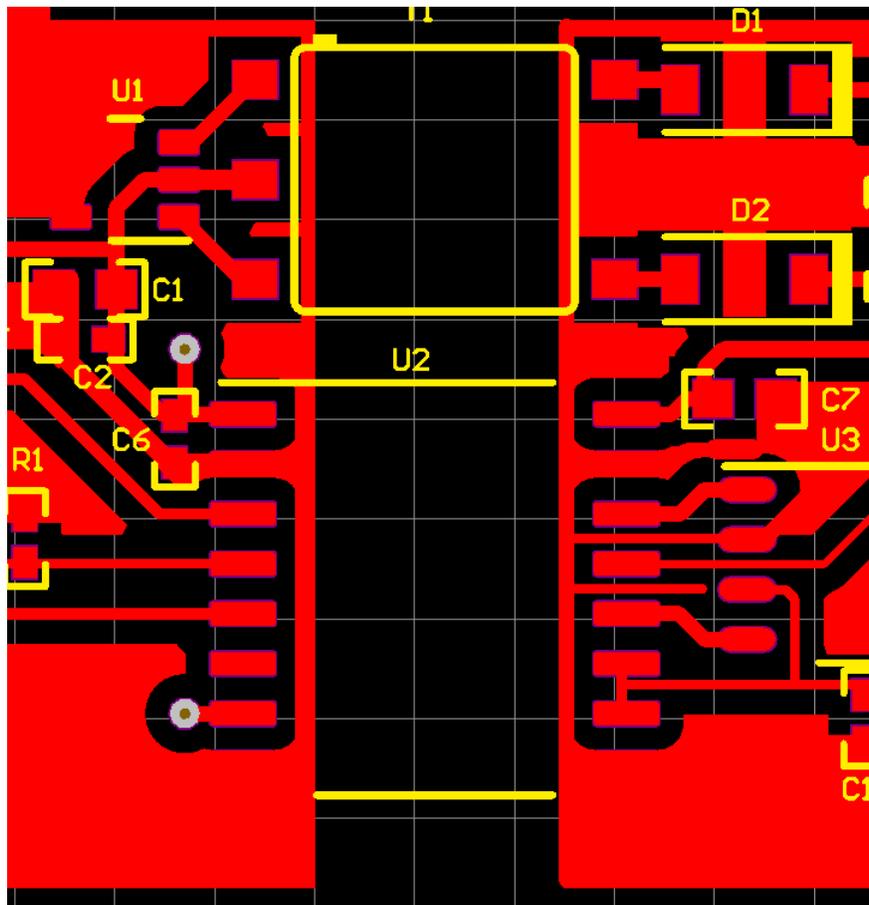


Figure 39. Isolated Section

- To avoid any interference with the signal lines, it is good to shield the outer layers of the isolated section as shown in [Figure 39](#).
- Layout of the CAN signals has to be done carefully to avoid any impedance mismatch for the CAN high and CAN low lines. Symmetry and shielding of the CAN signals from the controller, digital isolator, and transceiver are important.

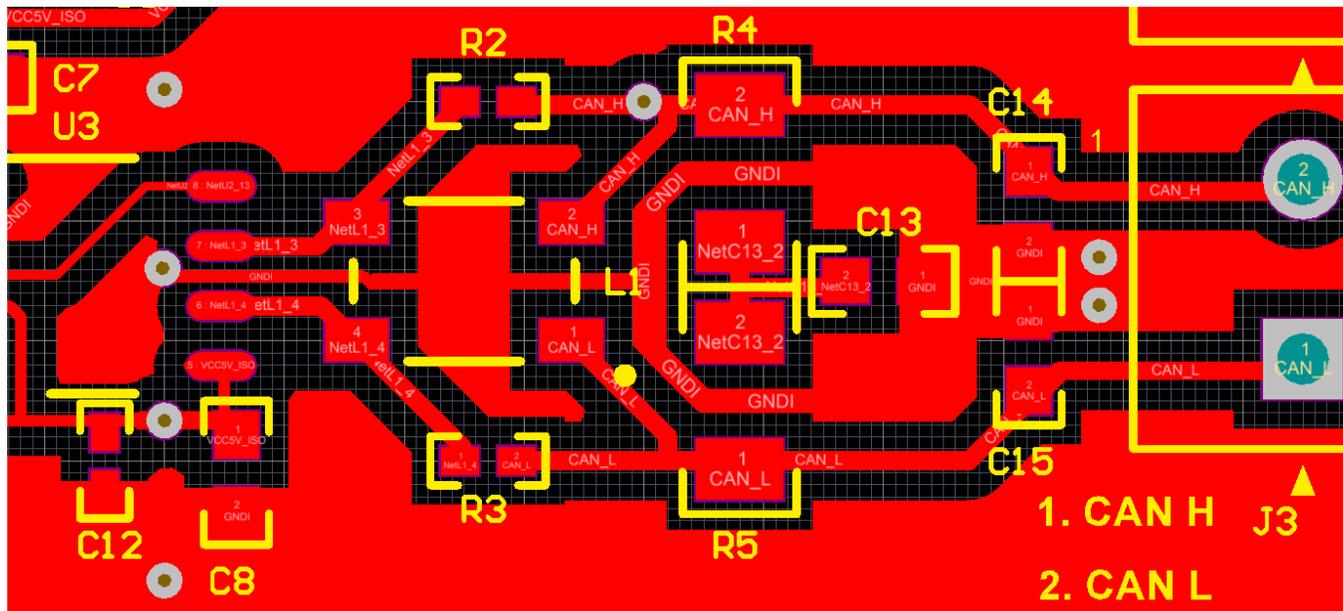


Figure 40. TCAN1042-Q1 Interface Circuit

- CAN termination layout is critical for the operation of CAN communication. Placement of CAN termination resistors R4 and R5 along with common-mode capacitor C13 play an important role for the low-pass filter of CAN messages.
- Place the ESD capacitor or special ESD suppression diodes close to the connector pins.

6.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01255](#).

6.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01255](#).

6.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01255](#).

6.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01255](#).

7 Software Files

To download the software files, see the design files at [TIDA-01255](#).

8 Related Documentation

1. Texas Instruments, [Controller Area Network Physical Layer Requirements](#) , Application Report (SLLA270)
2. Texas Instruments, [Common Mode Chokes in CAN Networks: Source of Unexpected Transients](#) , Application Report (SLLA271)
3. Texas Instruments, [SN6501 Multi-Transformer EVM User's Guide](#) (SLLU174)

8.1 Trademarks

LaunchPad, Code Composer Studio, Hercules are trademarks of Texas Instruments. All other trademarks are the property of their respective owners.

9 About the Author

RAMA KAMBHAM (Rama Chandra Reddy) is an automotive system engineer working in Texas Instruments Deutschland. Rama brings to this role his extensive experience in battery management systems and engine management systems in the automotive domain. Rama earned his bachelor of engineering degree from Osmania University Hyderabad, India.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated