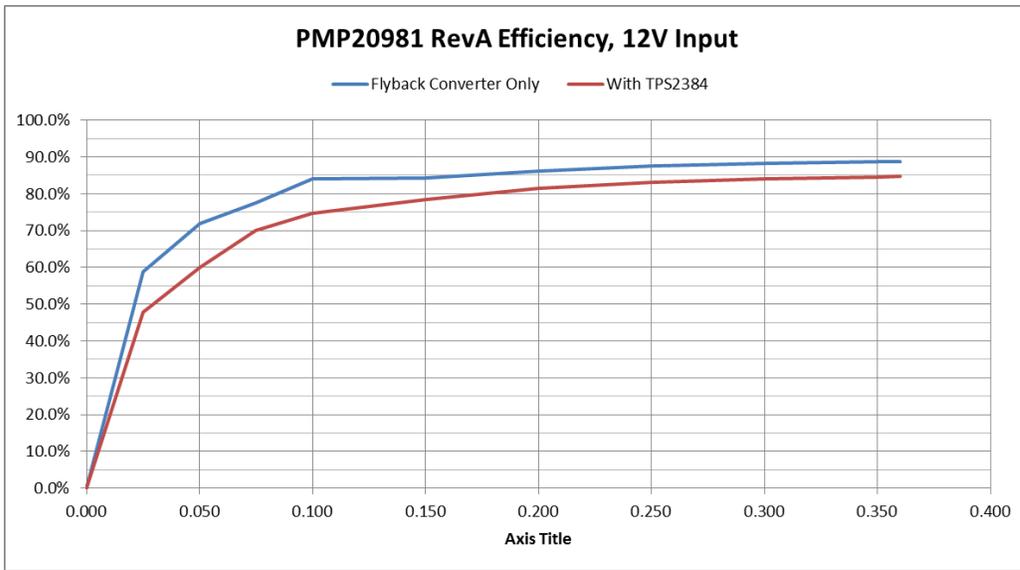


All testing performed with 12VIN, 360mA load, and 20MHz BW unless otherwise noted.


**Efficiency**

-----TPS2384 not connected-----					----With TPS2384 and PMP11254 Load			
J2/J3	J2	J1	J1	J2	J3	J1	J1	J3
<u>I</u> <sub>out</sub>	<u>V</u> <sub>out</sub>	<u>I</u> <sub>in</sub>	<u>V</u> <sub>in</sub>	<u>Eff</u>	<u>V</u> <sub>out</sub>	<u>I</u> <sub>in</sub>	<u>V</u> <sub>in</sub>	<u>Eff</u>
0.000	47.91	0.059	12.00	0.0%	47.94	0.112	12.00	0.0%
0.025	47.91	0.170	12.00	58.7%	47.90	0.209	12.00	47.7%
0.050	47.91	0.278	12.00	71.8%	47.85	0.332	12.00	60.1%
0.075	47.91	0.386	12.00	77.6%	47.80	0.426	12.00	70.1%
0.100	47.92	0.475	12.00	84.1%	47.75	0.533	12.00	74.7%
0.150	47.92	0.711	12.00	84.2%	47.65	0.759	12.00	78.5%
0.200	47.92	0.928	12.00	86.1%	47.55	0.974	12.00	81.4%
0.250	47.92	1.140	12.00	87.6%	47.44	1.189	12.00	83.1%
0.300	47.92	1.358	12.00	88.2%	47.33	1.407	12.00	84.1%
0.350	47.92	1.576	12.00	88.7%	47.22	1.629	12.00	84.5%
0.360	47.92	1.620	12.00	88.7%	47.20	1.672	12.00	84.7%




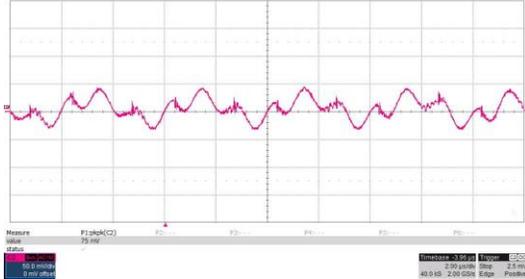**Ripple and Noise**

Output Ripple (C31/C32)  
50mV/div, 2usec.div  
Measured 75mVpp:




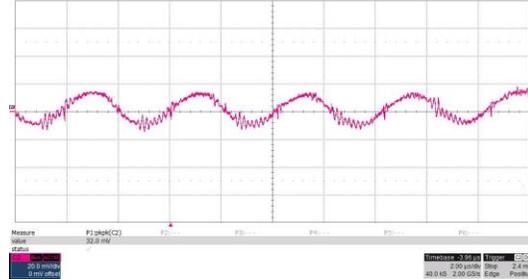Input Ripple (J1)  
20mV/div, 2usec.div  
Measured 32mVpp:




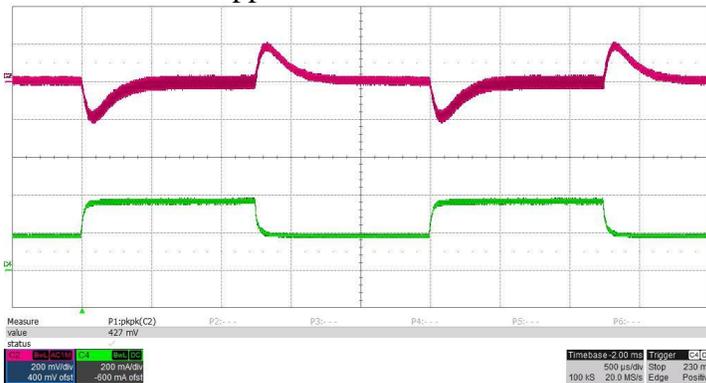**Dynamic Loading**

Output Load Step; 180mA to 360mA load step; Slew Rate = 250mA/usec  
200mV/div, 200mA/div, 500usec/div  
Measured 427mVpp across J2:




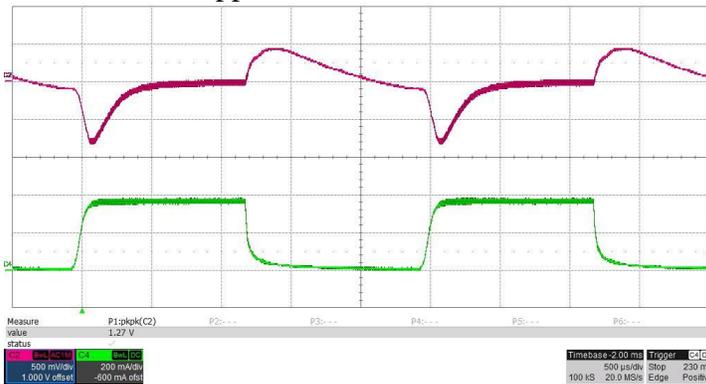Output Load Step; 0mA to 360mA load step; Slew Rate = 250mA/usec  
500mV/div, 200mA/div, 500usec/div  
Measured 1.27Vpp across J2:




**Turn On Response**

360mA Load, 2msec/div, 10V/div:

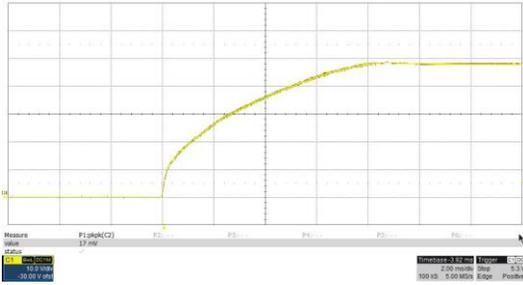


0A Load, 2msec.div, 10V/div:

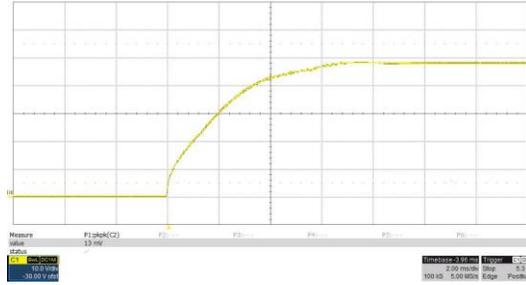

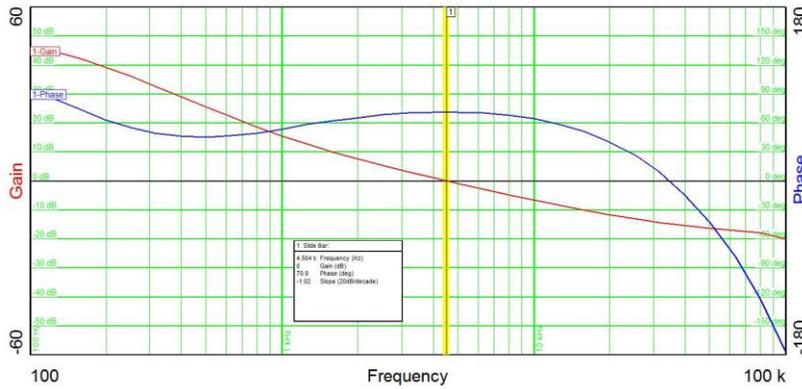**Loop Stability**

The measured Bode plot of the converter with a 360mA load (at J2) is shown below (with the TPS2384 connected):




Bandwidth: 4.5 KHz

Phase Margin: 70 degrees

Gain Margin: 14dB

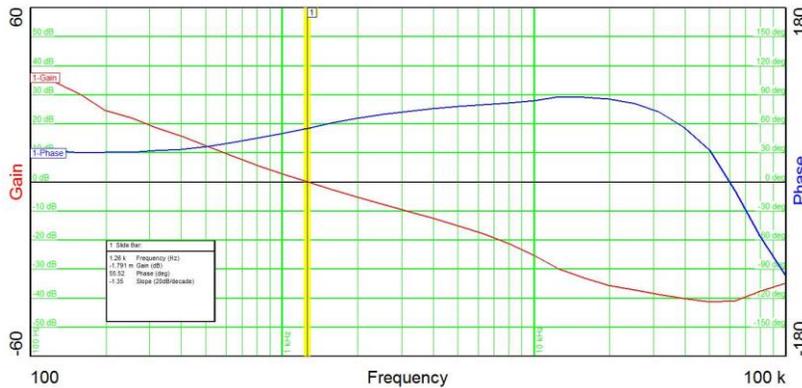The measured Bode plot of the converter with a 0mA load is shown below (with the TPS2384 connected). The TPS2384 provides approximately 636mW load:




Bandwidth: 1.2 KHz

Phase Margin: 55 degrees

Gain Margin: 41dB

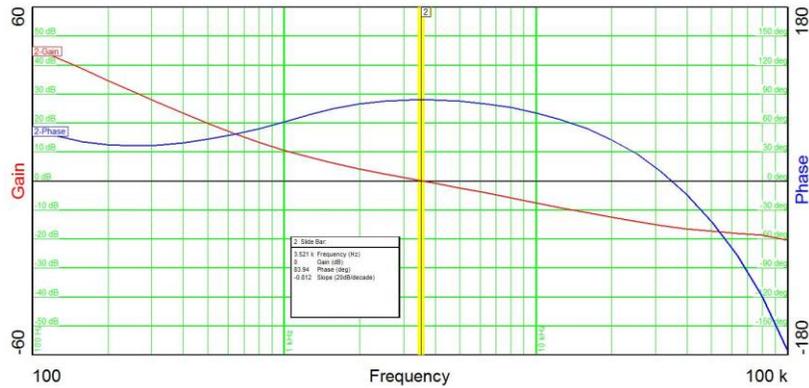The measured Bode plot of the converter with a PoE load of 360mA is shown below.



Bandwidth: 3.5 KHz


Phase Margin: 83 degrees

Gain Margin: 17dB


### Thermal Plot

Thermal plots measured with PoE load of 360mA at J3.

Top:

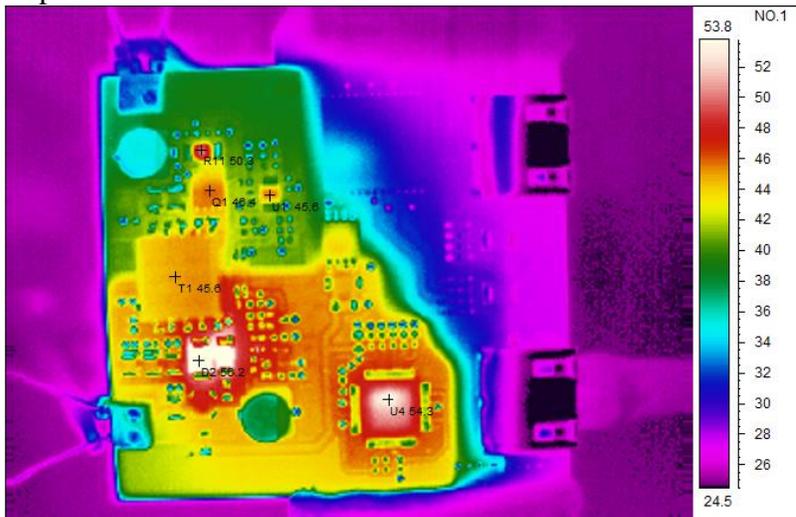

Bottom:

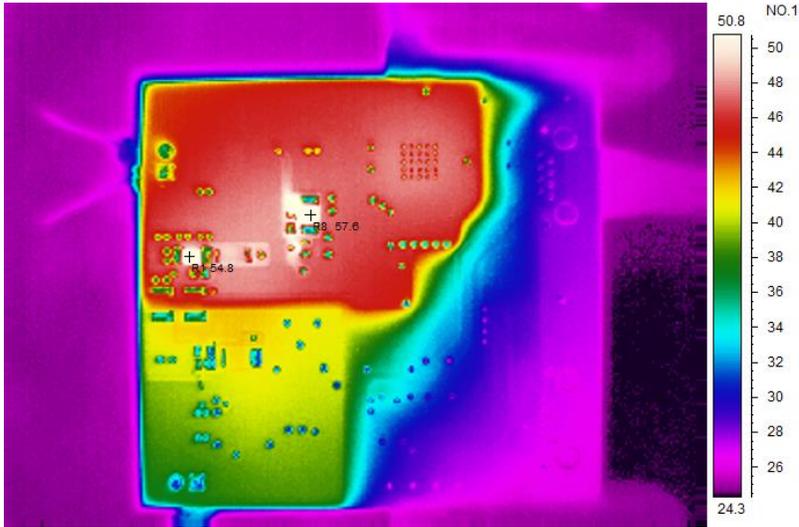


**Photo**

Top:



Bottom:

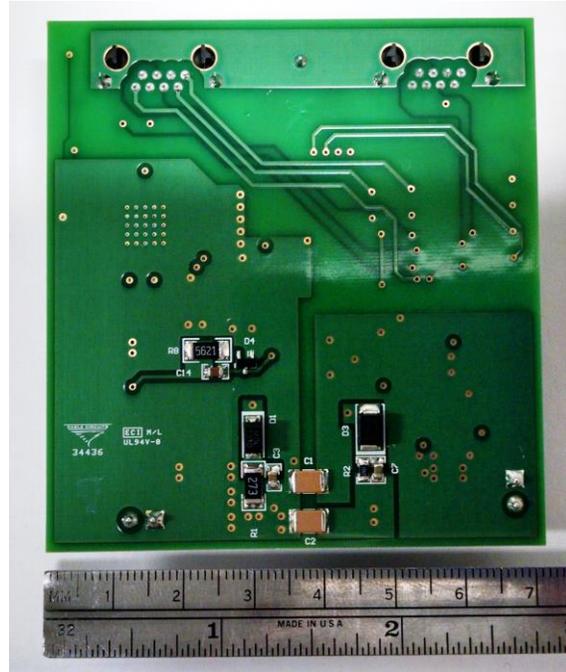

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated