

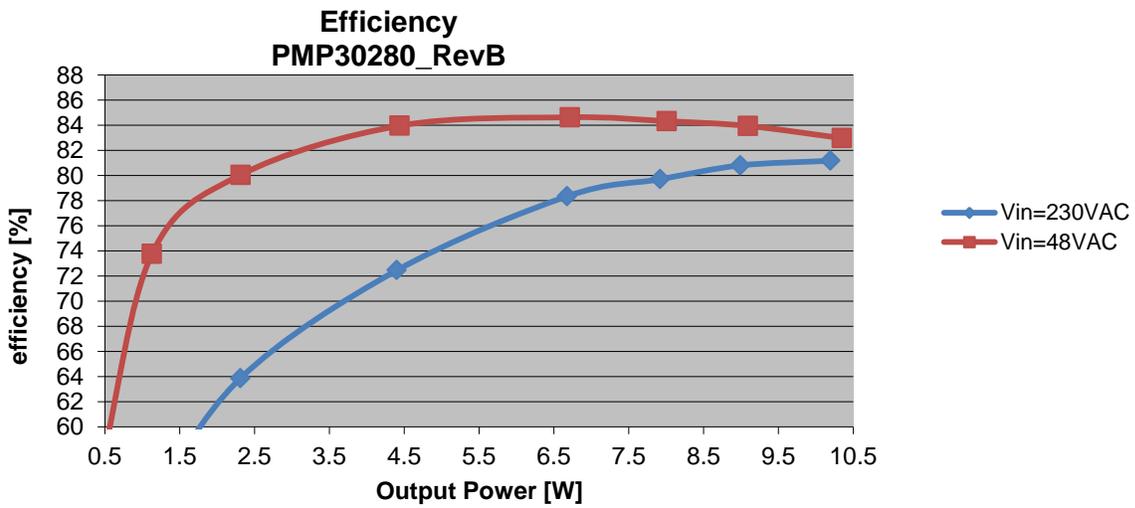


1 Efficiency and Load regulation

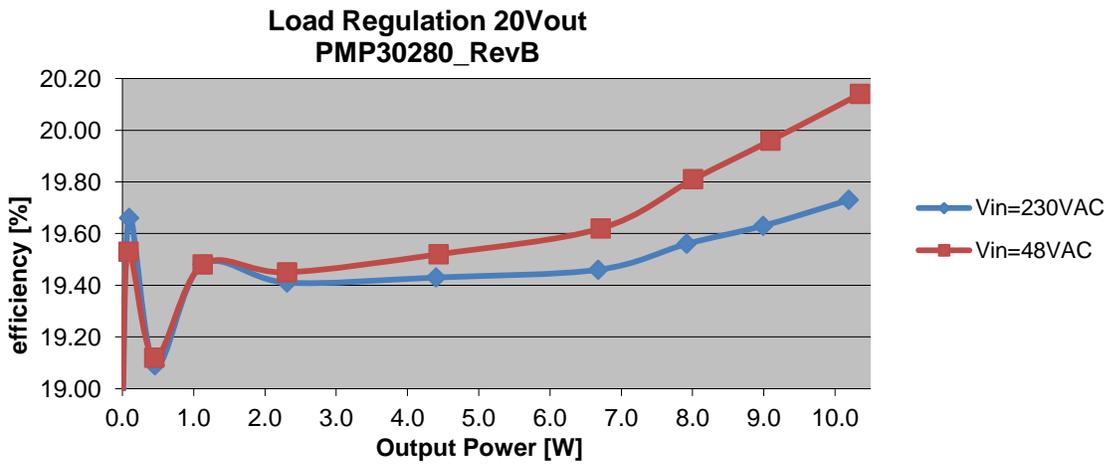

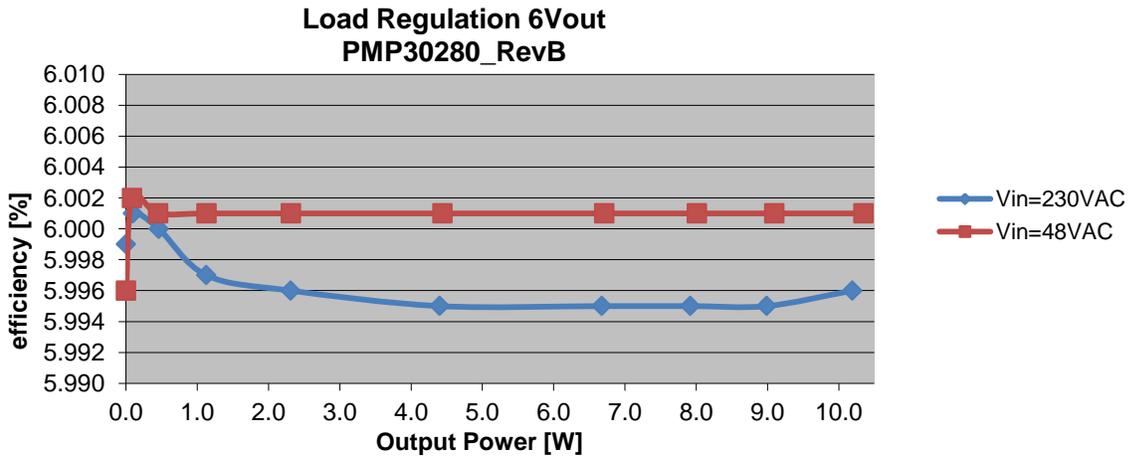

2 Startup


Input voltage = 40VAC

Output Power = 10.2W



Input voltage = 230VAC

Output Power = 10.2W

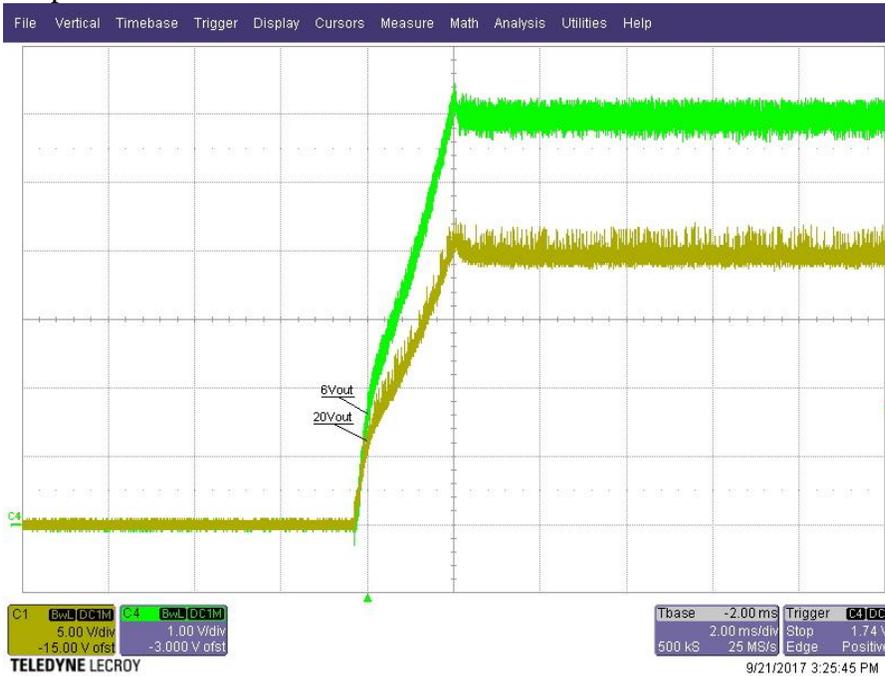

3 Shutdown

Input voltage = 230VAC

Output Power = 10.2W



4 Input Bulk Voltage

Input voltage = 40VAC



Output Power = 10.2W



5 Switch Node


Input voltage = 40VAC

Output Power = 10.2W

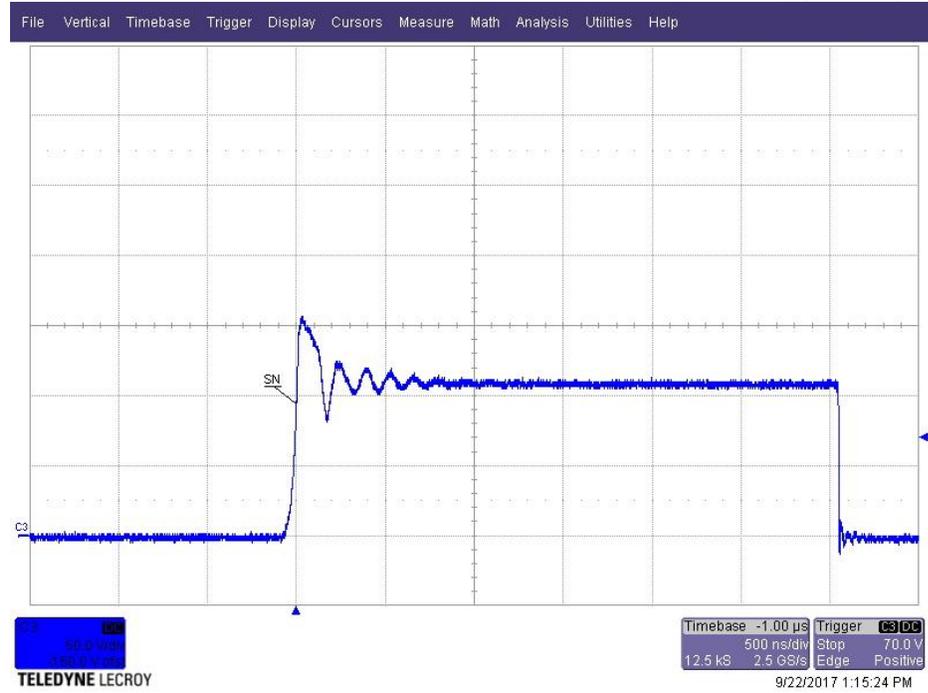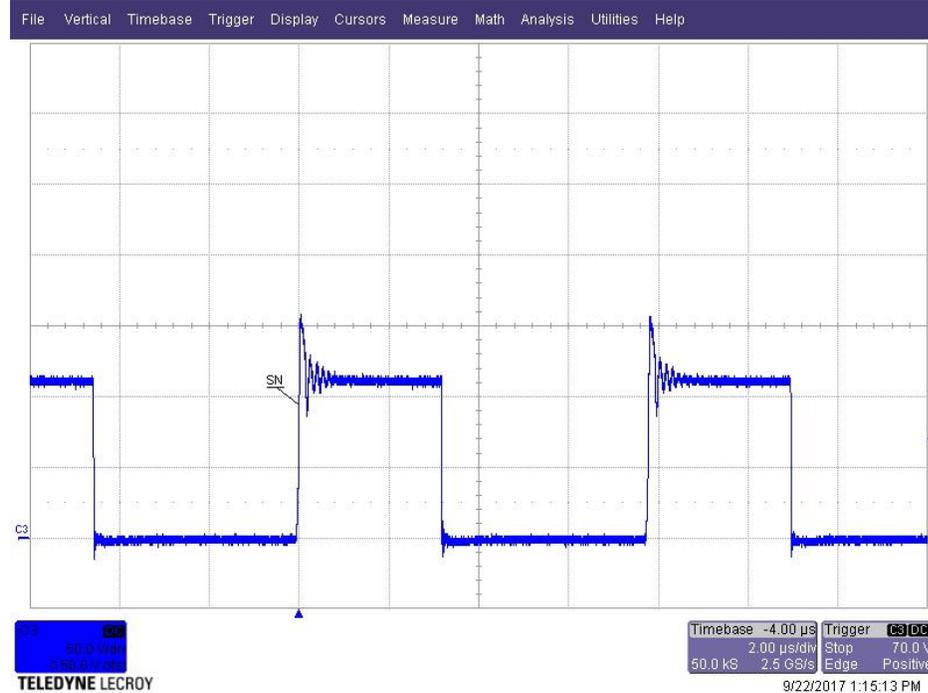

Input voltage = 273VAC

Output Power = 10.2W

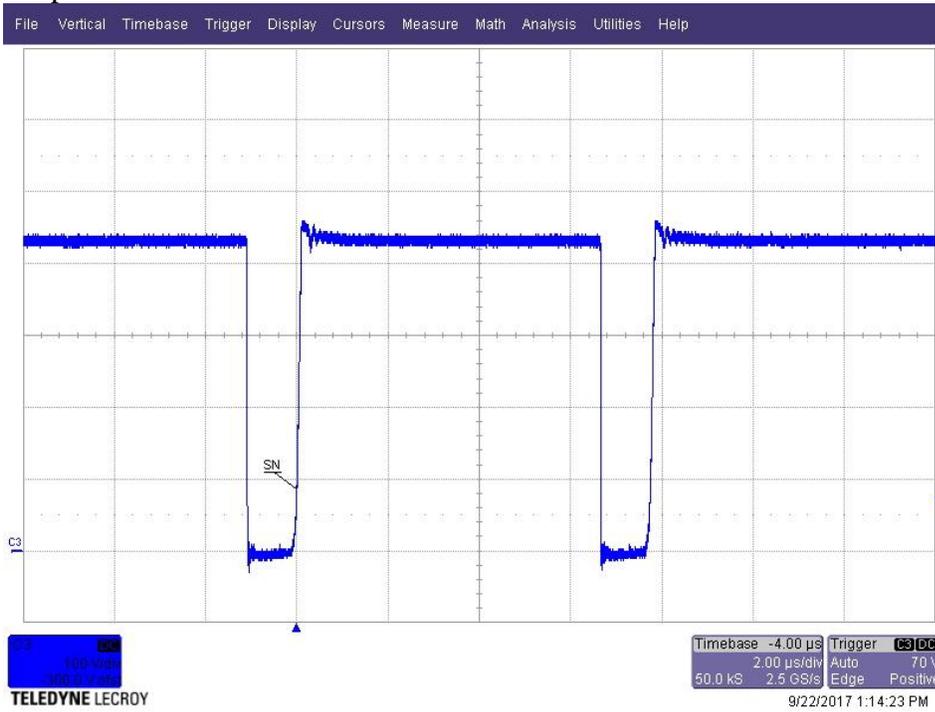


6 Output Ripple

6.1 6V Output

Input voltage = 230VAC


Output Power = 10.2W

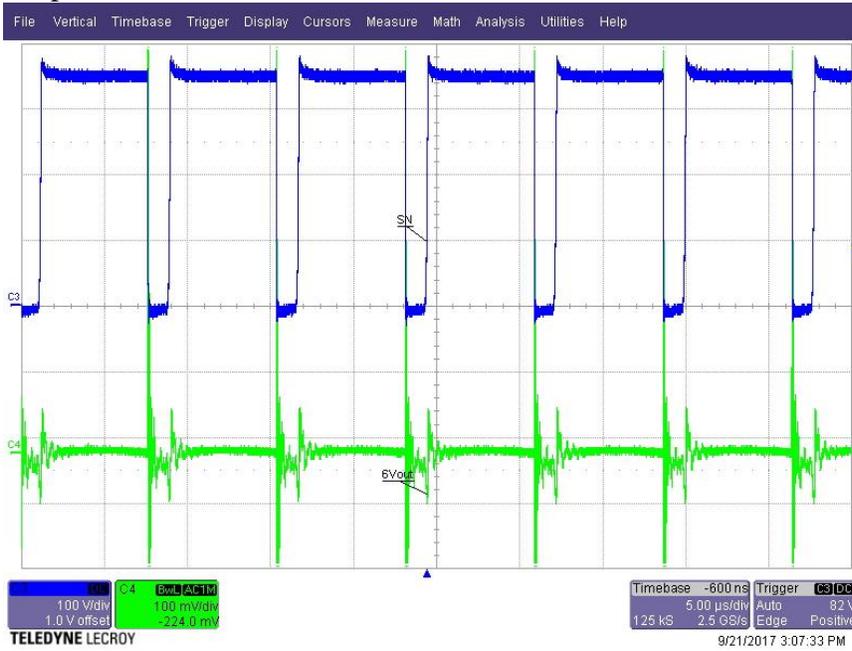


6.2 20V Output

Input voltage = 230VAC

Output Power = 10.2W

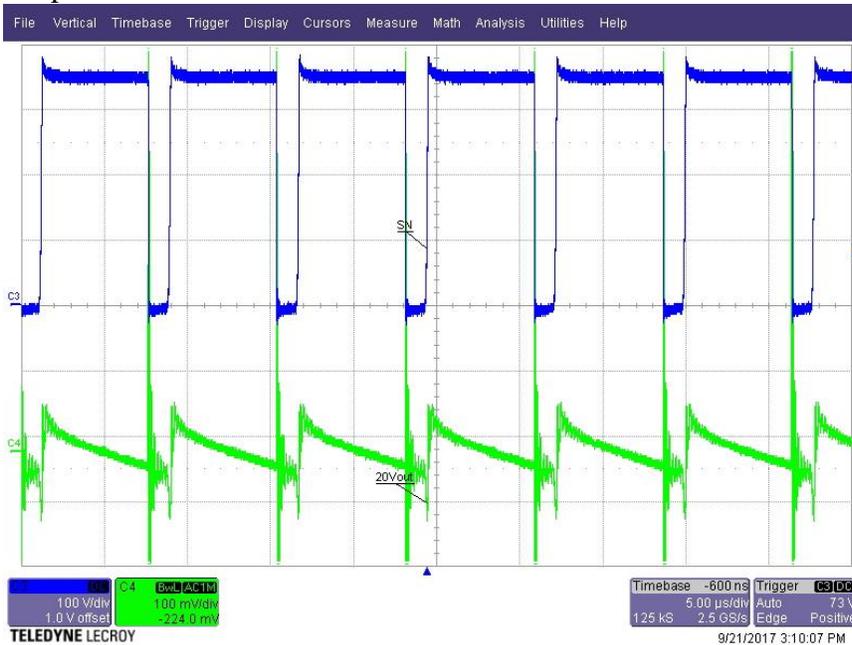

7 Control Loop Frequency Response

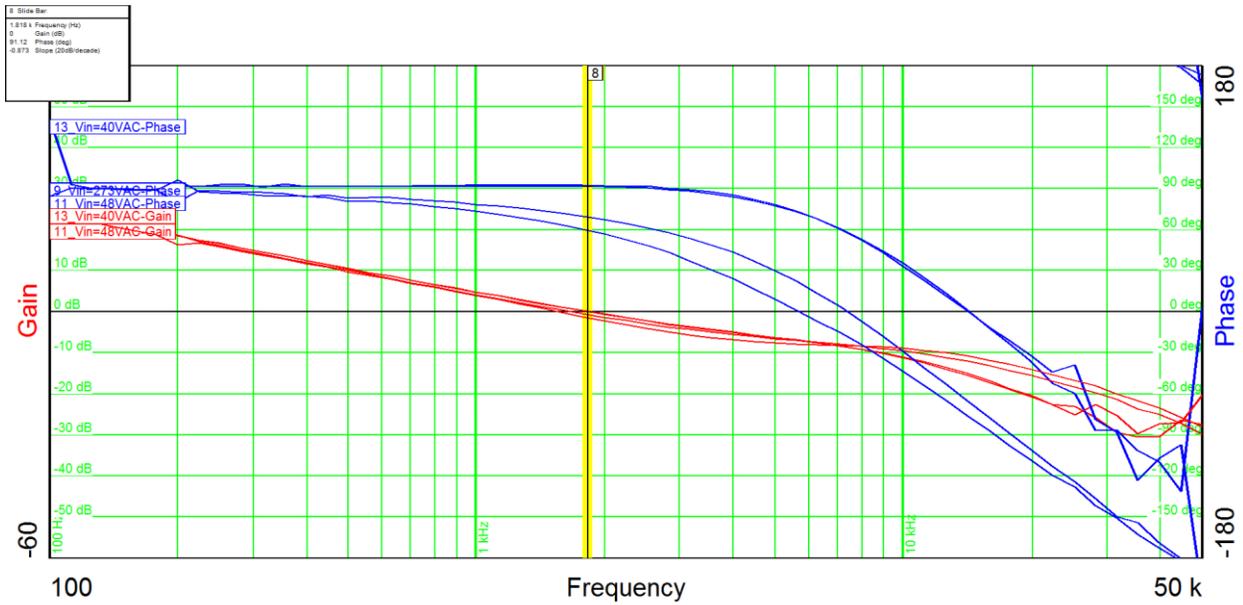

Input Voltage = 40VAC
 Output Power = 10.2W
 Phase margin = 64°
 Bandwidth = 1.5kHz

Input Voltage = 48VAC
 Output Power = 10.2W
 Phase margin = 71°
 Bandwidth = 1.7kHz

Input Voltage = 230VAC
 Output Power = 10.2W
 Phase margin = 91°
 Bandwidth = 1.8kHz

Input Voltage = 273VAC
 Output Power = 10.2W
 Phase margin = 92°
 Bandwidth = 1.8kHz

8 Load step

8.1 6V Output

Input voltage = 48VAC

6Vout Load current = 0.1A to 1.2A



Input voltage = 230VAC


6Vout Load current = 0.1A to 1.2A



9 Thermal Analysis


The images below show the infrared images taken from the FlexCam after 15min at full load output power.

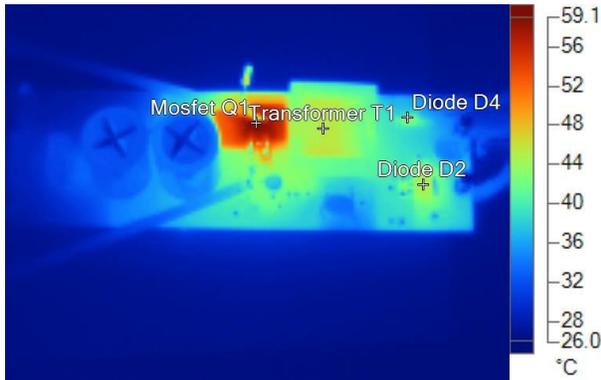Input voltage = 273VAC
 Output Power = 10.2W
 Ambient temperature = 25°C
 No heatsink, no airflow



Top Vin=273VAC_1118.is2


Name	Temperature	
Diode D2	45.2°C	
Mosfet Q1	59.1°C	
Transformer T1	45.8°C	
Diode D4	42.4°C	

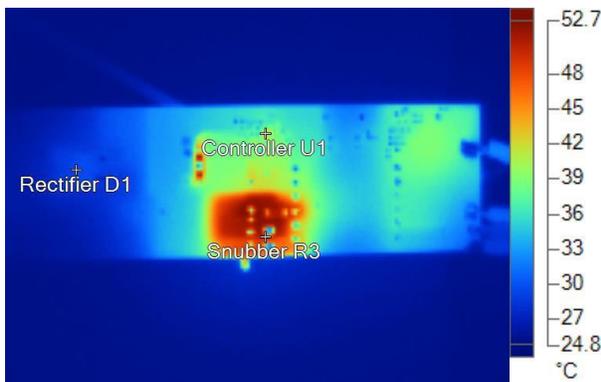

Bottom Vin=273VAC_1115.is2


Name	Temperature	
Rectifier D1	29.9°C	
Snubber R3	50.1°C	
Controller U1	41.9°C	

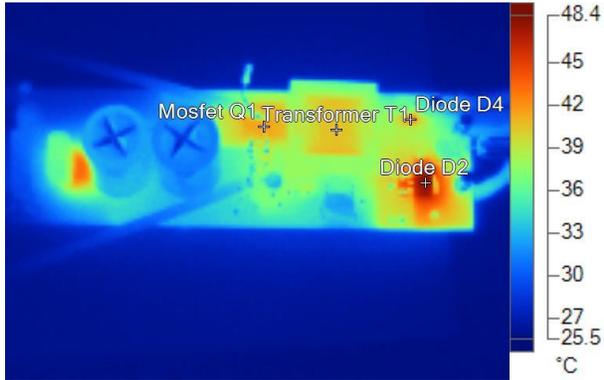Input voltage = 40VAC
 Output Power = 10.2W
 Ambient temperature = 25°C
 No heatsink, no airflow



Top Vin=40VAC_1117.is2

Name	Temperature
Mosfet Q1	41.6°C
Transformer T1	40.5°C
Diode D4	42.1°C
Diode D2	48.4°C

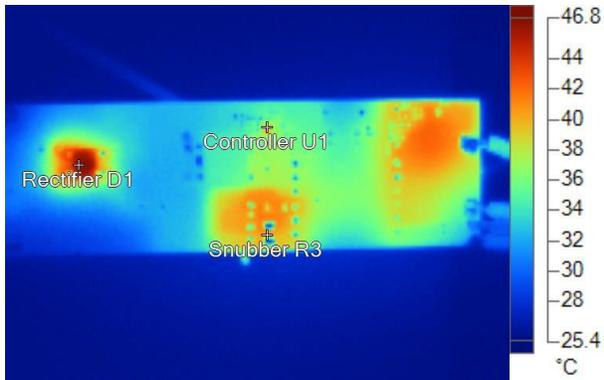

Bottom Vin=40VAC_1116.is2

Name	Temperature
Rectifier D1	46.6°C
Snubber R3	40.9°C
Controller U1	39.9°C


10 EMI Measurement

The graph below shows the conducted emission EMI noise and the EN55022 Class-B Quasi-Peak limits (measurement from the worst case line). The measurement is not certified. The board was connected to a LISN and an isolation transformer; the load was a power resistor. The receiver was set to Quasi-peak detector, 10 KHz bandwidth. The negative terminal of the converter has been connected to the ground of the LISN.

Input voltage = 230VAC

Output Power = 10.2W

	Ref Lvl	RBW	10 kHz	RF Att	0 dB
	90 dB μ V	VBW	100 kHz	Unit	dB μ V
		SWT	52 s		

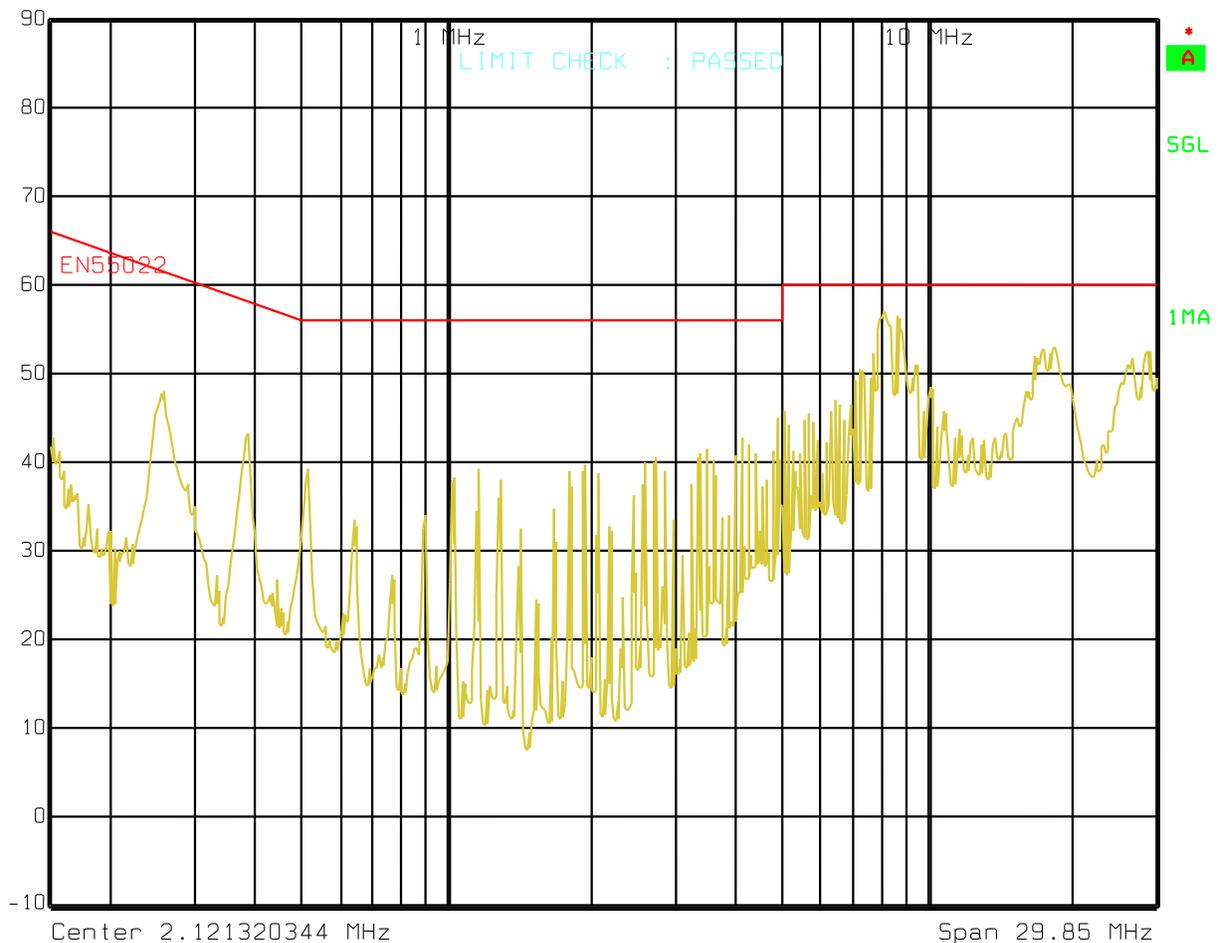

Date: 1.JAN.1997 1:15:47

PMP30280_RevB Test Results




Input voltage = 48VAC

Output Power = 10.2W



Ref Lvl
90 dB μ V

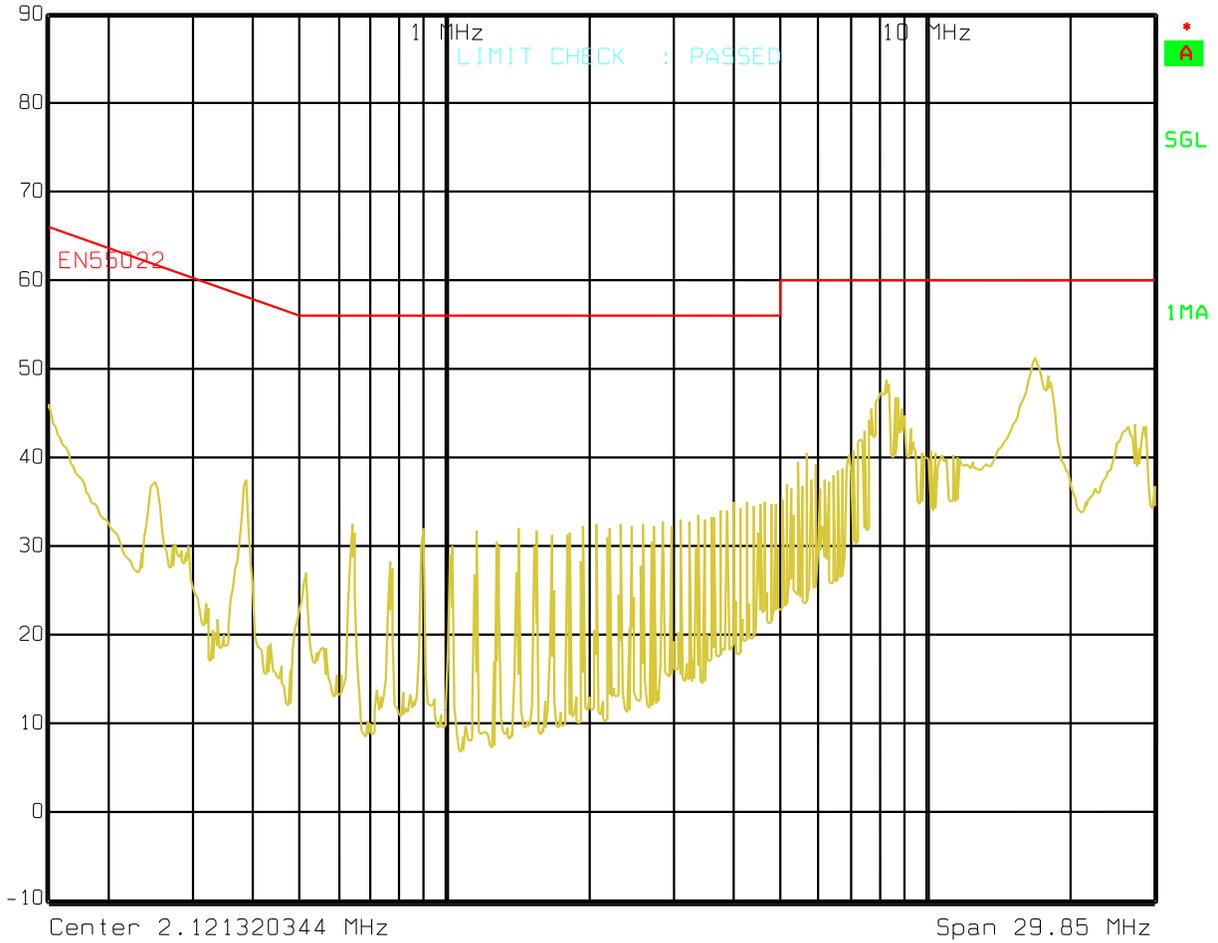RBW 10 kHz RF Att 0 dB
VBW 100 kHz
SWT 13 s Unit dB μ V



Date: 1.JAN.1997 1:13:44

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated