

ADC08D1500,ADC14DS080

Send High-Speed ADC Data Remotely And Quietly Using LVDS



Literature Number: SNAA093

Send High-Speed ADC Data Remotely And Quietly

Application Brief 124

Robert LeBoeuf

Highlights

- **Integrated LVDS Output Drivers Onboard the ADC**
- **Minimal Number of Wires Required at the ADC Output**
- **Differential Signaling for Minimal Common Mode Interference**
- **Smaller Number of Data Lines Saves PCB Space**

In the world of Analog-to-Digital conversion, it is often desired to transport the digital data downstream using a minimal group of wires. This problem is sometimes addressed by using ADCs that are serial data output capable. This solution however, has its set of challenges. Serial output ADCs are often lower speed due to the limitations inherent with traditional serial busses. Such busses often use single-ended signaling, which can become a source of EMI for surrounding circuitry. They can also be subjected to common-mode noise from surrounding circuitry, which can induce errors in the data transmission.

One way of overcoming some of these problems is to use an LVDS (Low Voltage Differential Signal) data bus. *Figure 1* shows a block diagram of an ADC with an LVDS output, driving an ASIC or a deserializer:

Advertisement

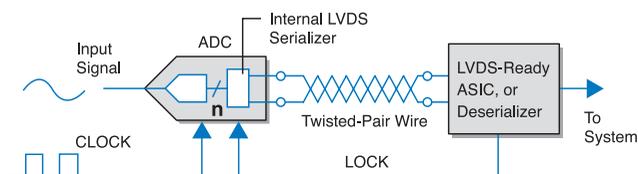


Figure 1: Block Diagram

Here the ADC outputs a serial data stream using the LVDS signal format. At the receiver end, an LVDS-ready ASIC, or a deserializer recovers the n-Bit output.

During the power-up sequence, the ADC and the receiver go through a two-step initialization sequence. This initialization refers to the synchronization of the PLLs that would be contained in each chip. First, the receiver locks to a frequency provided by an oscillator. The ADC PLL locks to CLKIN. After this, the ADC

sends out a data sequence referred to as a 'SYNC' pattern. This is a pattern of any number of ones followed by the same number of zeros, clocked at the output data rate. The PLL inside the receiver locks to this SYNC pattern, and sends a 'LOCK' signal back to the ADC. This signals the ADC that the receiver is locked, and is ready for incoming data. The output data is composed of a 'start-bit' which is always a '1', n bits of data, and a 'stop-bit' which is always a '0'. *Figure 2* shows a flow chart that summarizes this sequence:

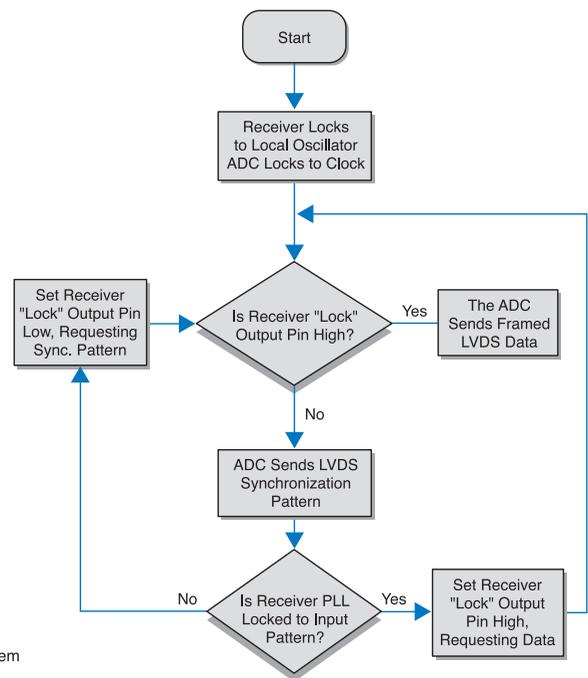


Figure 2: Flow Chart

This FRAME is therefore made up of $n+2$ bits. The datastream frequency is therefore $(n+2) \times f_{\text{sample}}$. The receiver may keep receiving data as long as its PLL remains locked. If it slips out of lock, the LOCK line is set low, and the ADC is asked for the synchronization pattern again.

The output drivers of the ADC are current sources capable of driving a 100Ω twisted-pair line, a PCB slot line or microstrip line. *Figure 3* shows two typical termination schemes that are used near the receiver:

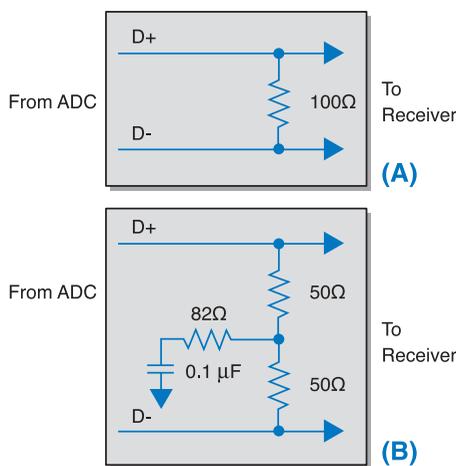


Figure 3: Typical Termination Scheme

Figure 3A shows a simple termination scheme. The resistor terminates the line from the ADC reducing any reflections that may occur. It also provides a load that the current sources need to produce the output signal. *Figure 3B* also shows a simple termination scheme, but offers a common mode resistance to dampen the cable if needed. This method is a little less common. In addition to a minimal number of wires between the ADC and the deserializer, the differential signal format keeps the magnetic fields tightly contained around the transmission line. This reduces the EMI of these wires, which may cause problems in nearby circuitry.

National Semiconductor offers LVDS output ADCs to simplify your demanding data bus requirements. To learn more, please visit our Web site at www.national.com/adc.

National Semiconductor
 2900 Semiconductor Dr.
 PO Box 58090
 Santa Clara, CA 95052
 1-800-272-9959

Visit our Web site at:
www.national.com

For more information,
 send email to:
new.feedback@nsc.com

 **National
 Semiconductor**
 The Sight & Sound of Information

Additional Information

www.national.com/adc

Visit **The National Edge**, our online technical journal for an archive of Application Briefs and other interesting information.
edge.national.com

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated