

LM3242 DSBGA Evaluation Board

1 Introduction

The LM3242 evaluation board is a working demonstration of an adjustable step down DC-DC converter optimized for powering RF power amplifiers (PAs) from a single Lithium-Ion cell. Output voltage is set using a VCON analog input for controlling power levels and efficiency of the RF PA.

2 Operating Conditions


The device will operate under the following conditions:

- V_{IN} range: 2.7V to 5.5V
- V_{OUT} range: 0.4V to 3.6V
- VCON range: 0.16V to 1.44V
- V_{OUT} equation: $V_{OUT} = 2.5 \times VCON$
- I_{OUT} range: 0 mA to 750 mA

3 Package

The LM3242 is available in a 9-bump (0.4 mm pitch) lead-free DSBGA (1.355 mm x 1.48 mm x 0.6 mm) package. The total solution size of the LM3242 and external components is $\approx 7.1 \text{ mm}^2$.

4 Typical Application Circuit

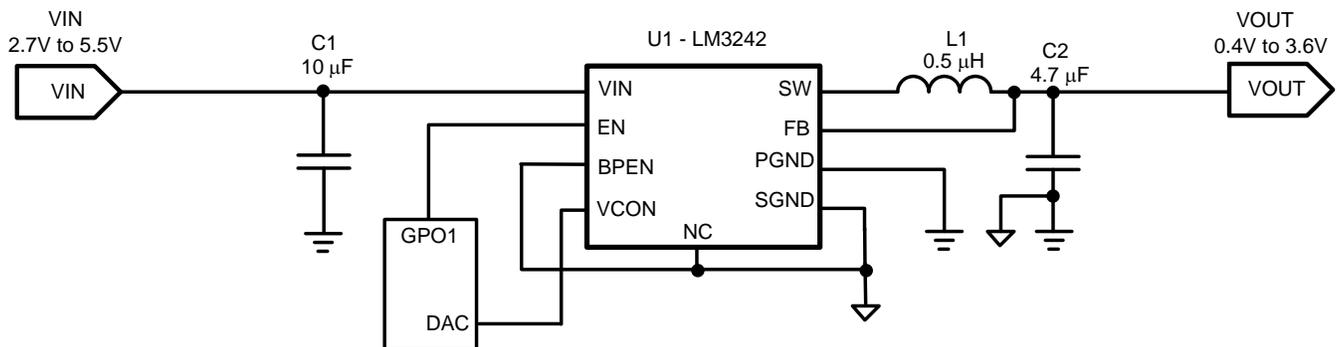

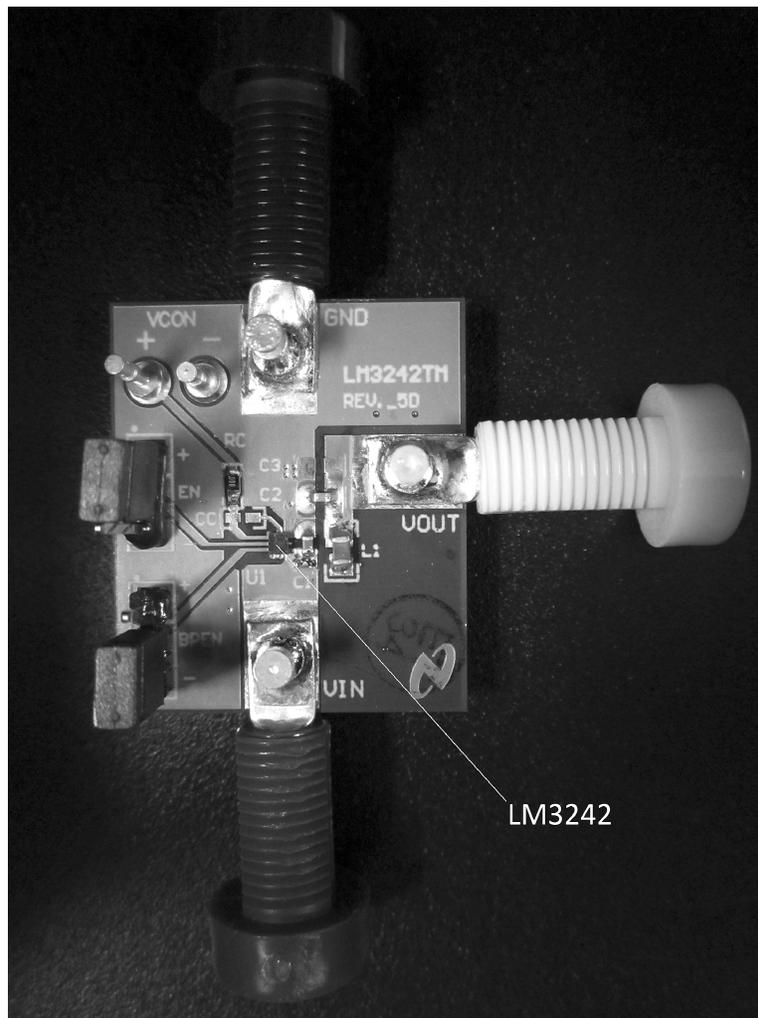
5 Bill of Materials (BOM) For Typical Configurations

Table 1. Bill of Materials (BOM) ⁽¹⁾

Designator	Model	Description	Manufacturer
C1	CL05A106MQ5NUNC	10 μ F, 6.3V, 0402	Samsung
C2	CL05A475MQ5NRNC	4.7 μ F, 6.3V, 0402	Samsung
L1	MIPSZ2012D0R5M	0.5 μ H, 2.0 x 1.2 x 1.0 mm	FDK
C4	GRM32ER60J107ME	100 μ F, 6.3V, 1210	Murata
U1	LM3242	Buck DC/DC Converter	Texas Instruments

⁽¹⁾ If the battery voltage source is not on the same PC board as the LM3242, you should employ a 100 μ F ceramic cap between VIN and GND terminals of the board to reduce effects of wire impedance. If considering use of the LM3242 in a system design, see the *PCB Board Layout Considerations* section of the *LM3242 6MHz, 750mA Miniature, Adjustable, Step-Down DC-DC Converter With Auto Bypass for RF Power Amplifiers Data Sheet* ([SNOSB48](#)). For a list of additional recommended external components, see the *LM3242 6MHz, 750mA Miniature, Adjustable, Step-Down DC-DC Converter With Auto Bypass for RF Power Amplifiers Data Sheet* ([SNOSB48](#)).

6 Evaluation Board Layout


Figure 1. LM3242 Evaluation Board

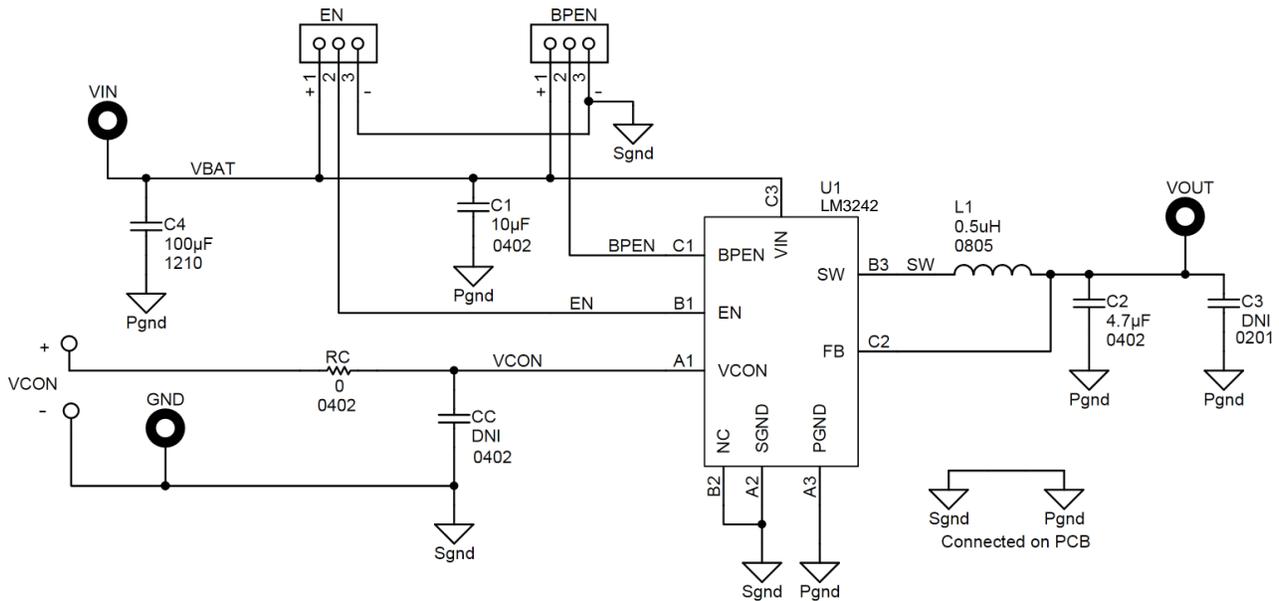


Figure 2. LM3242 Evaluation Board Schematic

7 Power Up Sequence

1. Ensure EN jumper at “EN/-” and BPEN jumper at “BPEN/-” positions prior to powering the evaluation board.
2. Power up VIN (within the range of 2.7V to 5.5V).
3. Set VCON for $V_{OUT} = 2.5 \times V_{CON}$ (within the specification of $V_{OUT} = 0.4V$ to $3.6V$)
 - (a) Example: $V_{CON} = 1.0V$ will give the result of $V_{OUT} = 2.5 \times 1.0V = 2.5V$.
4. Set EN jumper to “+/EN”.
5. Measure V_{OUT} .

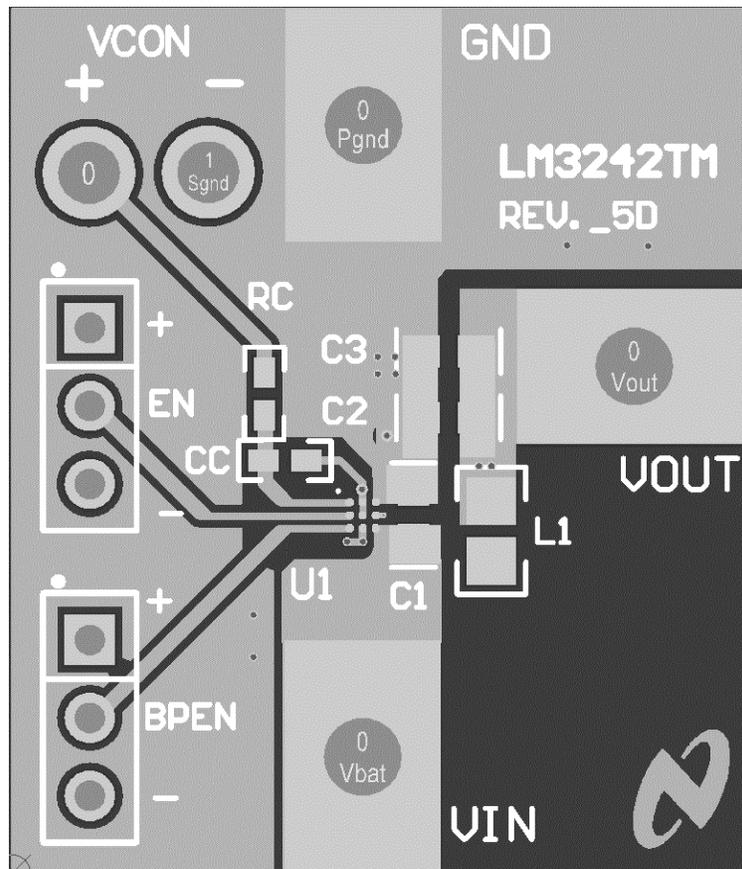


Figure 3. Top Layer: All Components on Top Layer

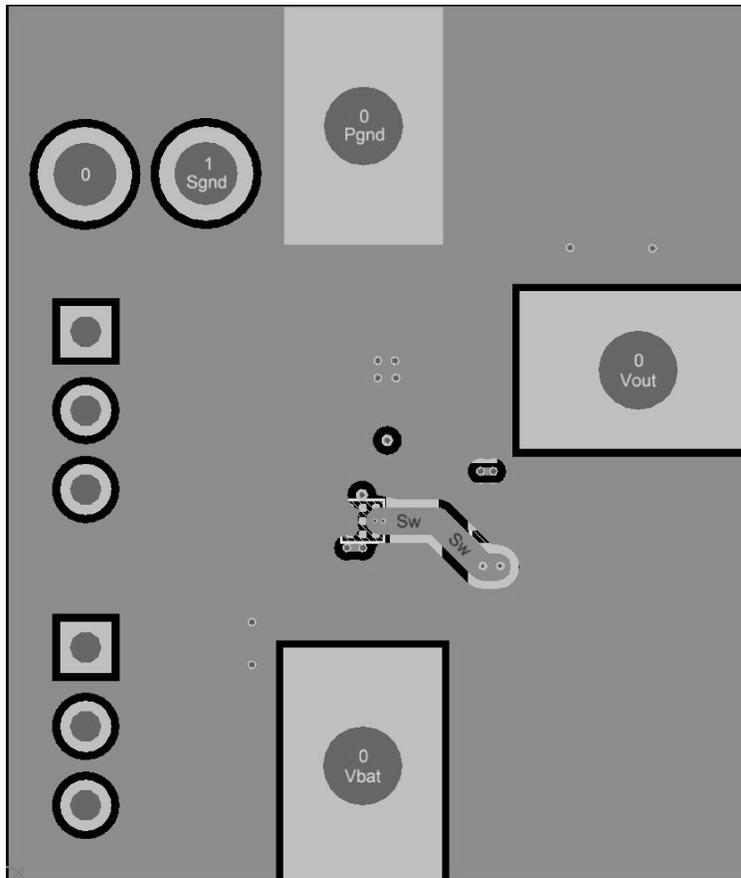


Figure 4. Mid Layer 1: Switching Path and Power Ground Plane

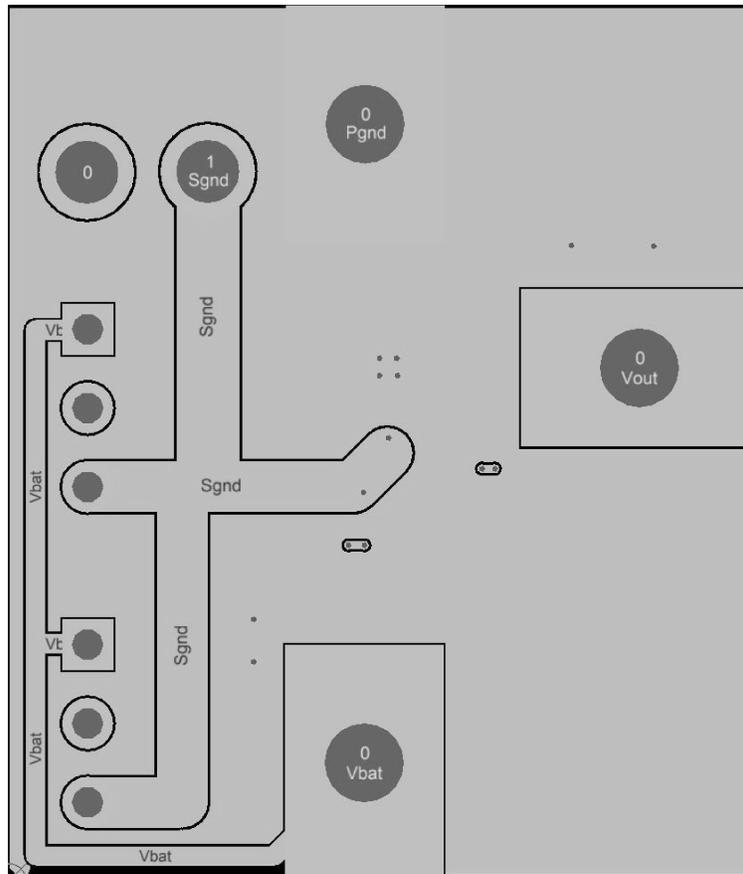


Figure 5. Mid Layer 2: Isolated Signal Ground and Power Ground Plane

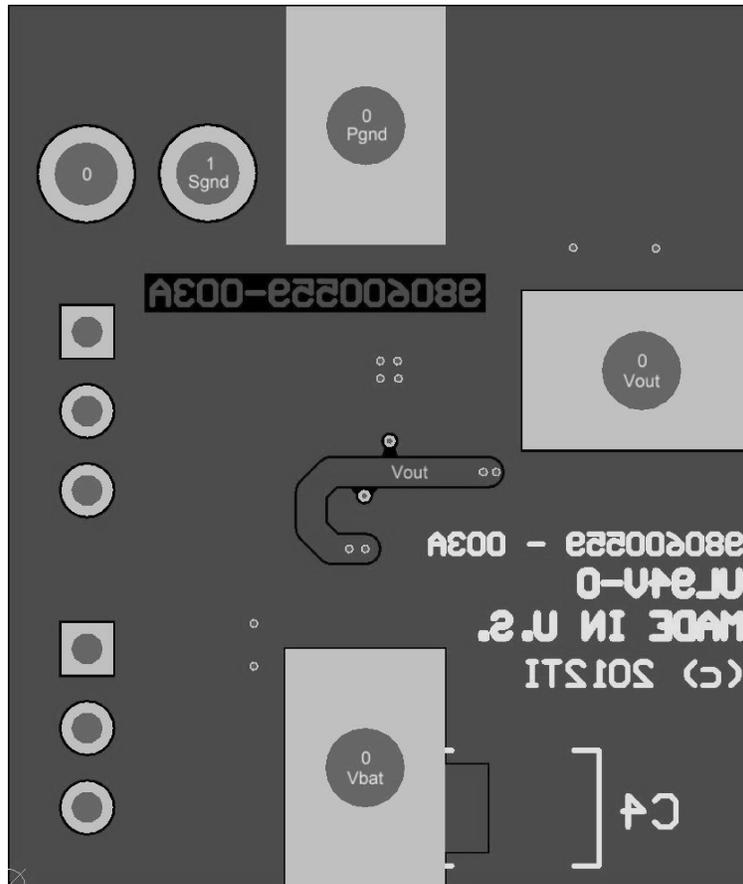


Figure 6. Bottom Layer: Feedback Path and Power Ground Plane

8 Connection Diagram and Package Mark Information

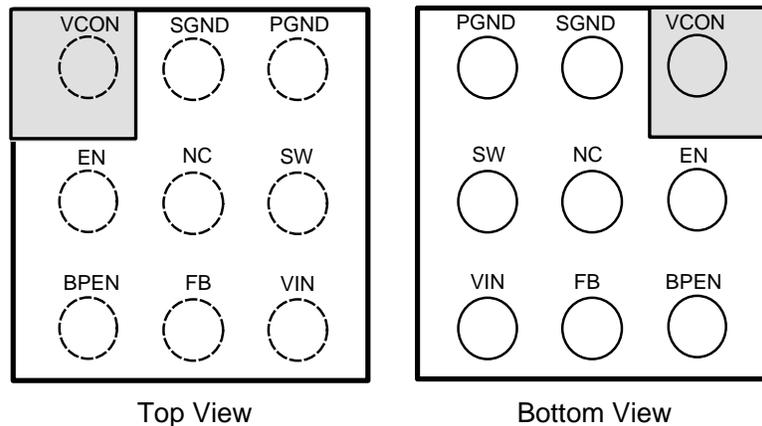


Figure 7. Connection Diagram

9 Pin Descriptions

Pin No	Name	Description
A1	VCON	Voltage Control Analog input. VCON controls VOUT in PWM and ECO modes. VCON may also be used to force bypass condition by setting $VCON > VIN/2.5$.
A2	SGND	Signal Ground for analog and control circuitry.
A3	PGND	Power Ground for the Power MOSFETs and gate drive circuitry.
B1	EN	Enable Input. Set this digital input high for normal operation. For shutdown, set low. Do not leave EN pin floating.
B2	NC	Do not connect to PGND directly -- internally connected to SGND. Connect to SGND or leave floating.
B3	SW	Switching Node connection to the internal PFET switch and NFET synchronous rectifier. Connect to an inductor with a saturation current rating that exceeds the maximum Switch Peak Current Limit specification of the LM3242.
C1	BPEN	Bypass Enable input. Set this digital input high to force bypass operation. For normal operation with automatic bypass, set low or connect to ground. Do not leave this pin floating.
C2	FB	Feedback Analog Input and Bypass FET output. Connect to the output at the output filter capacitor.
C3	VIN	Voltage supply input for SMPS converter.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com