PMP21455

Fitted	Description	Designator	PartNumber	Quantity	Manufacturer	ackageReferen	Value
Fitted	Printed Circuit Board	!PCB1	PMP20708	1	Any		
	CAP, CERM, 10 µF,		C2042)/ED4)/406//00				
Citta d	35 V, +/- 10%, X5R, 0805	C1, C2	C2012X5R1V106K08 5AC	2	TDK	0805	10
Fitted	CAP ALUM 8.2UF	C1, C2	JAC	2	TDK	0803	10uF
Fitted	20% 400V SMD	C3, C4	ULR2G8R2MNL1GS	2	Nichicon		8.2uF
	CAP, CERM, 10 µF,						
	10 V, +/- 10%, X7R,	cc. c7	C2012X7R1A106K12	_	TDV	0005	
Fitted	0805 CAP, CERM, 1 µF, 16	C6, C7	5AC	2	TDK	0805	10uF
	V,+/- 10%, X6S,		C1005X6S1C105K05				
Fitted	0402	C8	OBC	1	TDK	0402	1uF
	CAP, CERM, 1 µF, 16						
	V, +/- 10%, X6S,		C1005X6S1C105K05				
Fitted	0402	C15	0BC	1	TDK	0402	1uF
Fitted	CAP ALUM 39UF					D6.3xL11.2m	
	20% 35V RADIAL	C100	EEU-FC1V390	1	Panasonic	m	39uF
	CAP, CERM, 22 μF, 25 V,+/- 10%, X5R,		GRM31CR61E226KE				
Fitted	1206	C101, C102	15L	2	MuRata	1206	22uF
Filleu	DIODE GEN PURP		15L	2	ON	1200	2201
	250V 200MA				Semiconduct		
Fitted	SOD323	D1, D3, D4	BAS21HT1G	3	or	SOD-323	250V
	Diode, Switching-						
	Bridge, 600V, 0.5A,						
Fitted	MiniDIP	D2	RH06-T	1	Diodes Inc.	MiniDIP	1.15V
	Diode, Superfast Rectifier, 600 V, 1 A,				Comchip		
Citta d	3.5x1.6mm	D5	CSFMT108-HF	1	Technology	3.5x1.6mm	600V
Fitted	5.5x1.011111	5		1	Rohm	SOD323, 2-	600V
	DIODE ZENER 4.7V				Semiconduct		
Fitted	100MW VMD2	D6	VDZT2R4.7B	1	or	1.9x1.45mm,	4.7V
	Diode, Zener, 200 V,				Vishay-		
	800 mW, AEC-Q101,				Semiconduct		
Fitted	DO-219AB Jumper Wire, 300mil	D8	BZD27C200P-E3-08	1	or	DO-219AB	200V
	spacing, Orange,					300 mil	
Fitted	pkg of 200	J1	923345-03-C	1	3M	Jumper Wire	
FILLEO	MOSFET, N-CH, 600		525545 05 C	1	5141	Jumper Wire	
	V, 0.021 A, AEC-				Infineon		
Fitted	Q101, SOT-23	Q1	BSS126 H6906	1	Technologies	SOT-23	600V
	RES, 1.00, 1%, 0.1 W,		CRCW06031R00FKE				
Fitted	0603	R1	А	1	Vishay-Dale	0603	1.00
	RES, 20.0 k, 1%,	D 2	CRCW040220K0FKE			0.402	
Fitted	0.063 W, 0402 RES, 5.1 k, 5%, 0.063	R2	D CRCW04025K10JNE	1	Vishay-Dale	0402	20.0k
Fitted	W, 0402	R5	D	1	Vishay-Dale	0402	5.1k
FILLED	RES, 0, 5%, 0.25 W,		CRCW12060000Z0E	· · ·	tishay Dale	070L	J. IK
Fitted	1206	R6	A	1	Vishay-Dale	1206	0
	RES, 9.09 k, 1%,		CRCW04029K09FKE		-		
Fitted	0.063 W, 0402	R7	D	1	Vishay-Dale	0402	9.09k
	RES, 3.74 k, 1%,		CRCW04023K74FKE				
Fitted	0.063 W, 0402	R9	D	1	Vishay-Dale	0402	3.74k
F '11 - 1	RES, 1.54 k, 1%,	D10	CRCW04021K54FKE		Vichov Dala	0402	1 5 41
Fitted	0.063 W, 0402	R10	D	1	Vishay-Dale	0402	1.54k

	RES, 10.0 k, 1%,		CRCW040210K0FKE				
Fitted	0.063 W, 0402	R11, R100	D	2	Vishay-Dale	0402	10.0k
	RES, 0, 5%, 0.125 W,		CRCW08050000Z0E				
Fitted	0805	R12	A	1	Vishay-Dale	0805	0
	VARISTOR 470V						
Fitted	1.2KA DISC 7MM	RV1	B72207S301K111	1	EPCOS Inc	10mm Radial	423V
	Transformer, 450 uH,				Wurth	17.66x13.72m	
Fitted	SMT	T1	750316908	1	Elektronik	m	450uH
	Test Point,					Red Miniature	
Fitted	Miniature, Red, TH	TP1, TP3, TP4	5000	3	Keystone	Testpoint	
	Test Point,					Black	
Fitted	Miniature, Black, TH	TP2, TP5, TP6	5001	3	Keystone	Miniature	
	700-V Lowest						
	Quiescent Current						
	Off-Line Switcher,				Texas		
Fitted	D0007A	U1	UCC28881DR	1	Instruments	D0007A	
					Vishay-	SMD, 4-Leads,	
	OPTOISOLATOR				Semiconduct	Body	
Fitted	5.3KV TRANS 4SMD	U3	SFH6186-4T	1	or	4.83x6.81mm,	
						SOD323, 2-	
	Zener Diode 500mW				Rohm	Leads, Body	
	±3% Surface Mount				Semiconduct	1.9x1.45mm,	
Not Fitted	SOD-323HE	D9	TFZVTR24B	0	or	No Polarity	24V
	RES, 1.00 k, 1%,		CRCW04021K00FKE				
Not Fitted	0.063 W, 0402	R8	D	0	Vishay-Dale	0402	1.00k

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ('TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your noncompliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products http://www.ti.com/sc/docs/stdterms.htm), evaluation modules, and samples (http://www.ti.com/sc/docs/stdterms.htm), evaluation

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2018, Texas Instruments Incorporated