
Test Report: PMP30352 Pre-Regulator Reference Design for Automotive LED-Headlamp Drivers

TEXAS INSTRUMENTS

Description

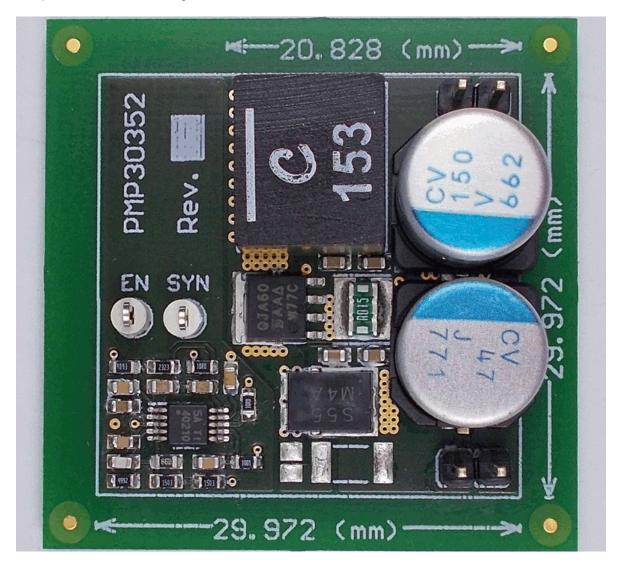This pre-regulator reference design delivers up to 45 W output power for automotive LED-headlamp drivers. For an input voltage range of 9.0 V to 16.0 V the design can support an output voltage of 45.0V with a load current of 1.0 A. An optional external dithering function is also available.



53

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements


PARAMETER	SPECIFICATIONS				
V _{IN}	9.0 V - 16.0 V (5.0 V - 24.0 V operational)				
V _{OUT}	45.0V @ 1.0 A				
Nominal switching frequency	350 kHz (up to 390 kHz with dithering)				

2



2 Testing and Results

2.1 Efficiency Graphs

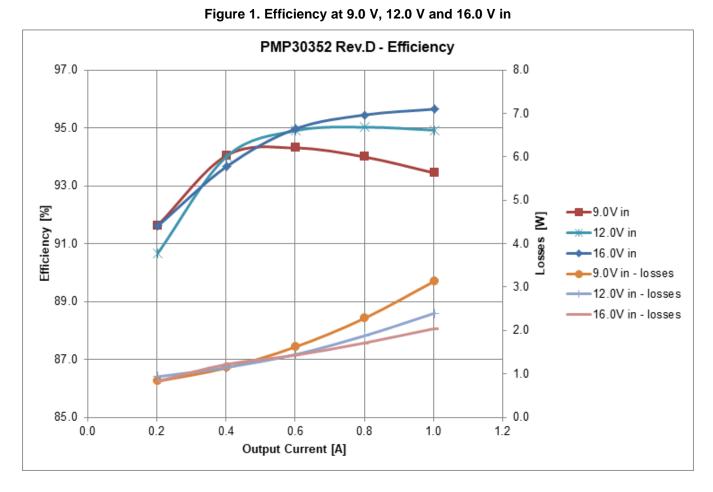

2.2 Efficiency Data

Table 2	. Efficiency	data for	the 9	.0 V	input
---------	--------------	----------	-------	------	-------

Voltage [V]	Current [A]	Power [W]	Voltage [V]	Current [A]	Power [W]	Losses [W]	Efficiency [%]
8.998	1.0997	9.8951	44.93	0.2018	9.0669	0.828	91.6
8.998	2.126	19.1297	44.82	0.4014	17.9907	1.139	94.0
8.997	3.167	28.4935	44.71	0.601	26.8707	1.623	94.3
8.997	4.225	38.0123	44.63	0.8006	35.7308	2.282	94.0
8.997	5.317	47.8370	44.57	1.0029	44.6993	3.138	93.4

Table 3. Efficiency data for the 12.0 V input

Voltage [V]	Current [A]	Power [W]	Voltage [V]	Current [A]	Power [W]	Losses [W]	Efficiency [%]
12	0.8349	10.0188	45.01	0.2018	9.0830	0.936	90.7
12	1.599	19.1880	44.94	0.4014	18.0389	1.149	94.0
12	2.367	28.4040	44.86	0.6009	26.9564	1.448	94.9
12	3.144	37.7280	44.78	0.8006	35.8509	1.877	95.0
12	3.937	47.2440	44.72	1.0028	44.8452	2.399	94.9

TIDT058–December 2018 Submit Documentation Feedback Pre-Regulator Reference Design for Automotive LED-Headlamp Drivers 3




Testing and Results

Voltage [V]	Current [A]	Power [W]	Voltage [V]	Current [A]	Power [W]	Losses [W]	Efficiency [%]
15.99	0.6205	9.9218	45.04	0.2018	9.0891	0.833	91.6
15.99	1.206	19.2839	45.01	0.4013	18.0625	1.221	93.7
15.99	1.779	28.4462	44.95	0.601	27.0150	1.431	95.0
15.99	2.355	37.6565	44.9	0.8005	35.9425	1.714	95.4
15.99	2.94	47.0106	44.84	1.0028	44.9656	2.045	95.6

 Table 4. Efficiency data for the 16.0 V input

2.3 Thermal Images



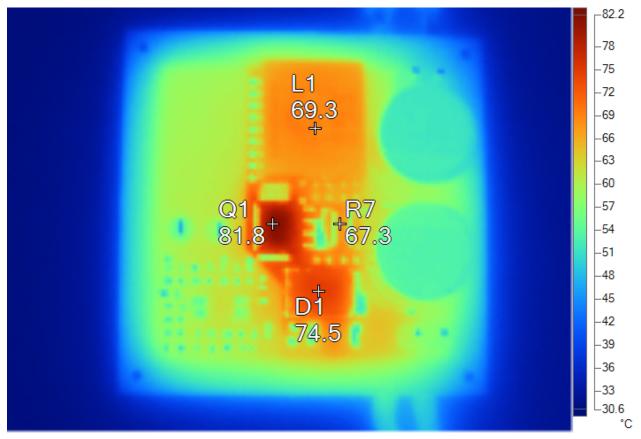

2.4 Dimensions

4


Circuit: smaller than 30 mm x 30 mm



3 Waveforms

3.1 Switching

Figure 3. Switching Node at 12.0 Vin, 45.0 V out and 1.0 A load current.

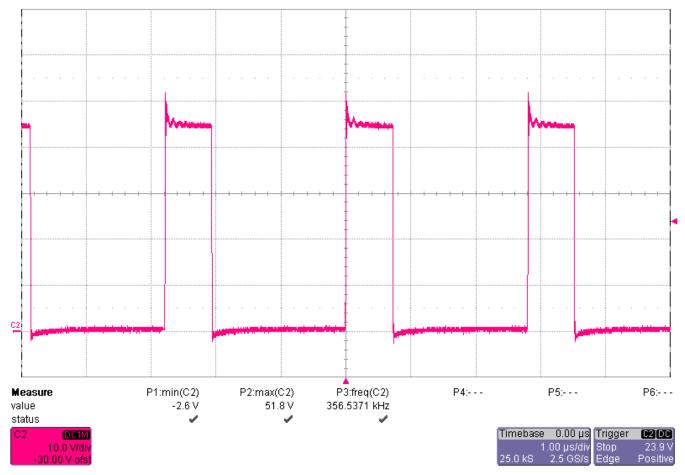

• Ch2: Switching node signal [scale: 10.0V/div, 1.0us/div]

5

3.2 Output Voltage Ripple

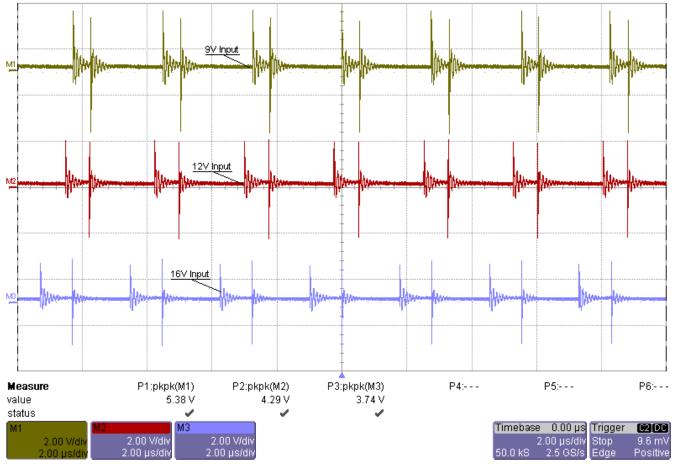


Figure 4. AC-coupled output voltage signal at 9.0V, 12.0V and 16.0V in.

• M1: 5.38 V peak-peak ripple [scale: 2.0 V/div, 2.0us/div]

• M2: 4.29 V peak-peak ripple [scale: 2.0 V/div, 2.0us/div]

• M3: 3.74 V peak-peak ripple [scale: 2.0 V/div, 2.0us/div]



3.3 Input Voltage Ripple

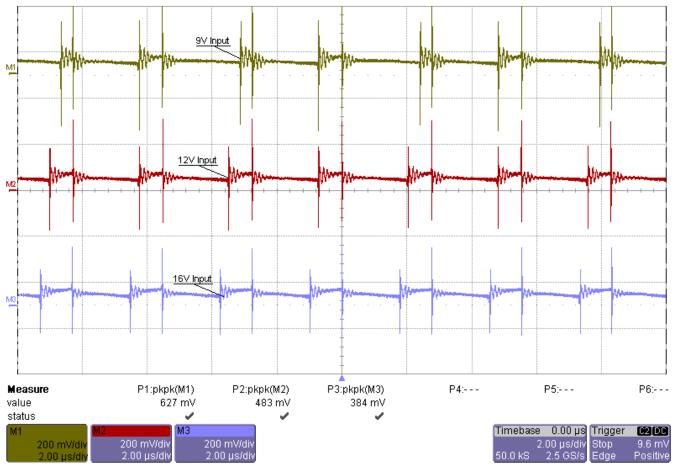


Figure 5. AC-coupled input voltage signal at 9.0V, 12.0V and 16.0V in.

• M1: 627 mV peak-peak ripple [scale: 200 mV/div, 2.0us/div]

• M2: 483 mV peak-peak ripple [scale: 200 mV/div, 2.0us/div]

• M3: 384 mV peak-peak ripple [scale: 200 mV/div, 2.0us/div]

Waveforms



Waveforms

3.4 Bode Plot

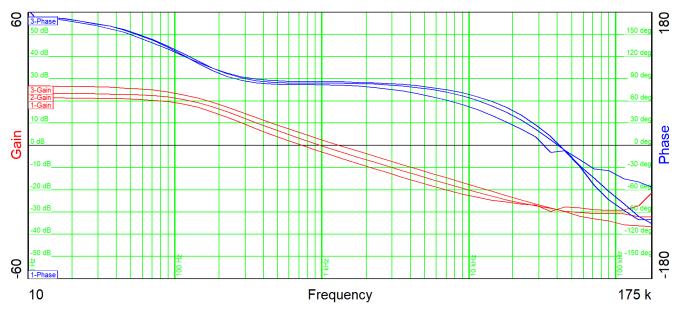


Figure 6. Bode plot at 9.0 V, 12.0 V and 16.0 V in.

- 9.0V in, 1.0A load current: fco 726Hz, 82deg phase margin, -29dB gain margin
- 12.0V in, 1.0A load current: fco 974Hz, 84deg phase margin, -29dB gain margin
- 16.0V in, 1.0A load current: fco 1.31kHz, 86deg phase margin, -29dB gain margin



3.5 Load Transients

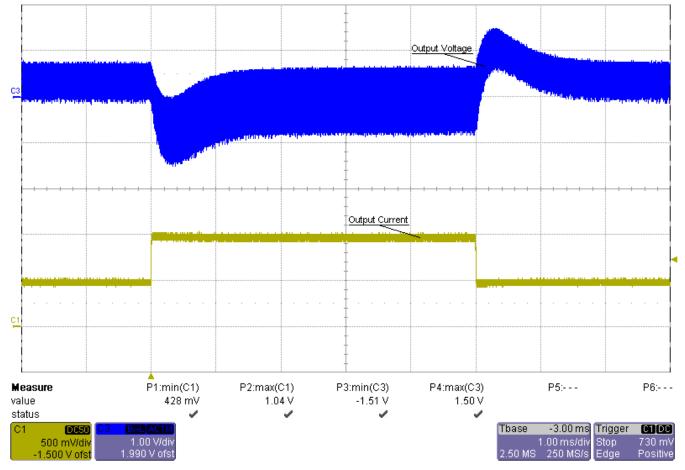


Figure 7. Load transient from 0.5 A to 1.0 A at 12.0 V in results in 1.51 V undershoot (3.3%) and 1.50 V overshoot (3.3%).

• Ch1: output current) [scale: 0.5A/div, 1.0ms/div]

• Ch3: AC-coupled output voltage, bw limited (20MHz) [scale: 1.0V/div, 1.0ms/div]

Copyright © 2018, Texas Instruments Incorporated

9

Waveforms



Waveforms

www.ti.com

3.6 Start-up Sequence

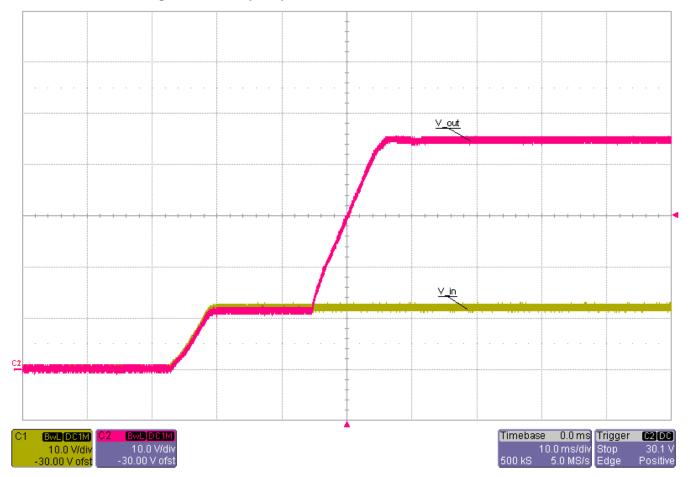


Figure 8. Start-up sequence at 12.0 V in with no load attached.

• Ch1: input voltage [scale: 10.0V/div, 10.0ms/div]

• Ch2: output voltage [scale: 10.0V/div, 10.0ms/div]



3.7 Undervoltage Protection

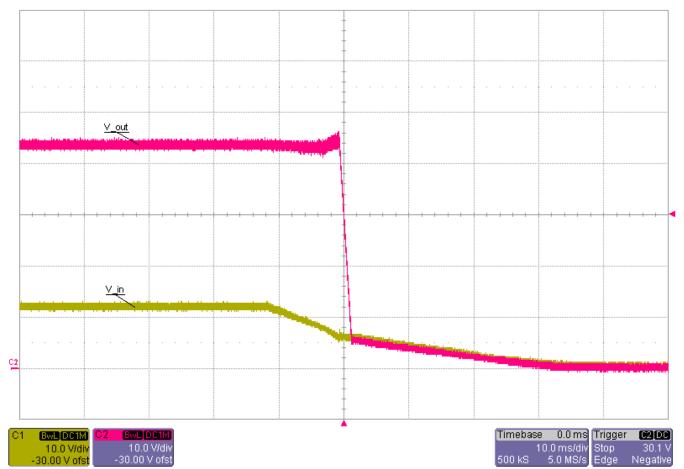


Figure 9. Undervoltage protection with a 1.0 A load attached.

• Ch1: input voltage [scale: 10.0V/div, 10.0ms/div]

Ch2: output voltage [scale: 10.0V/div, 10.0ms/div]

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (https://www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2021, Texas Instruments Incorporated