

1 Description

TIDA-00512 (3138ALLCEVM-150) together with 3138ACC32EVM-149 is an EVM of LLC resonant half-bridge DC-DC power converter with digital control using UCD3138A device. UCD3138A device is located on the board of 3138ACC32EVM-149. 3138ACC32EVM-149 is a daughter card and serves all LLC resonant converter required control functions with preloaded firmware. For details of firmware please contact TI. TIDA-00512 accepts DC line input from 350Vdc to 400Vdc, and outputs nominal 12Vdc with full load output power 340W, or full output current 29A.

2 Performance Specification

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNITS
Input Characteristics					
Voltage operation range		350		400	VDC
Input UVLO On			325		VDC
Input UVLO Off			310		VDC
Input current	Input = 350VDC, Full Load = 29A			1.2	A
Input current	Input = 380VDC, Full Load = 29A			1.1	A
Input current	Input = 400VDC, Full Load = 29A			1.0	A
Output Characteristics					
Output voltage, VOUT	No Load to Full Load		12		VDC
Output load current, IOU	350 to 400VDC			29	A
Output voltage ripple	380VDC and Full Load = 29A		200		mVpp
Output over current	Operation 10s then latch-off shutdown	30			A
Systems Characteristics					
Switching frequency	Resonant Mode	35		150	kHz
	PWM Mode		150		kHz
Peak efficiency	380VDC, Full Load = 20A		94.85		%
Full load efficiency	380VDC, Load = 29A		94.20		%
Operating temperature	Natural Convection		25		°C
Firmware					
Device ID (Version)	UCD3138A				
Filename	3138ALLCEVM_150_150205.x0				

3 Test Setup

3.1 Test Equipment

DC Voltage Source: capable of 350 to 400Vdc, adjustable, with minimum power rating 400W, or current rating not less than 2A, with current limit function. The DC voltage source to be used should meet IEC60950 reinforced insulation requirement.

DC Multimeter: 1 unit capable of 0 to 400VDC input range, four digits display preferred; and 1 unit capable of 0 to 15VDC input range, four digits display preferred.

Output Load: DC load capable of receiving 0 to 15VDC, 0 to 30A, and 0 to 360W or greater, with display such as load current and load power.

Current-meter, DC, optional in case the load has no display, 1 unit, capable of 0 to 30A.

Oscilloscope: capable of 500MHz full bandwidth, digital or analog, if digital 5Gs/s or better

Fan: 200 to 400 LFM forced air cooling is recommended, but not a must

Recommended Wire Gauge: capable of 30A, or better than #14 AWG, with the total length of wire less than 8 feet (4 feet input and 4 feet return).

4 Performance Data and Typical Characteristic Curves

Figure 1 through 14 present typical performance curves for TIDA-00512.

4.1 Efficiency

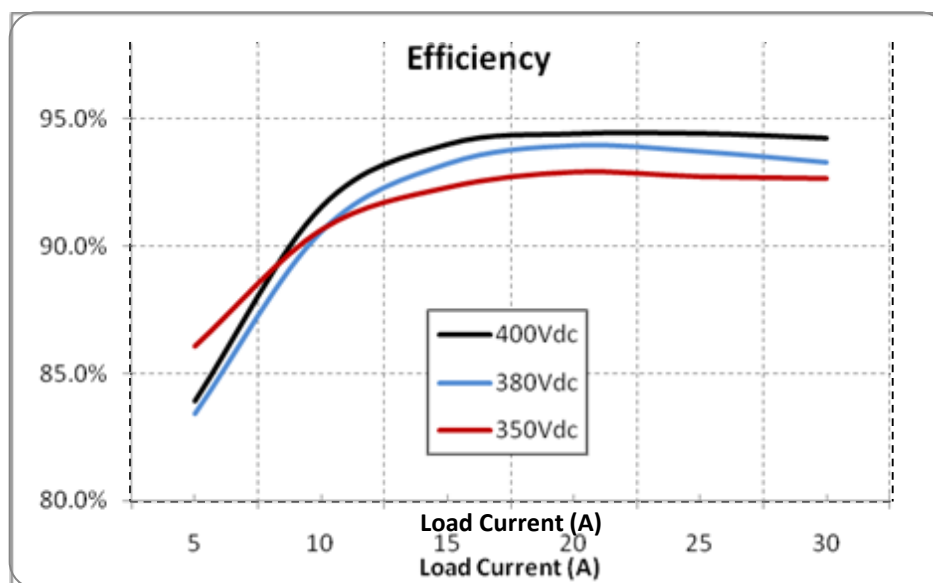


Figure 1. TIDA-00512 Efficiency

4.2 Load Regulation

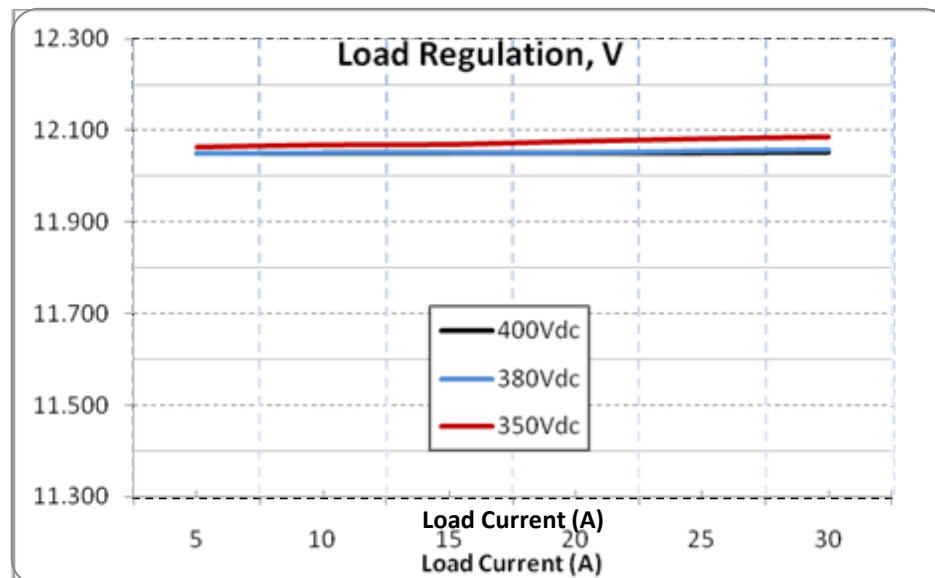


Figure 2. TIDA-00512 Load Regulation

4.3 Switching Frequency Control

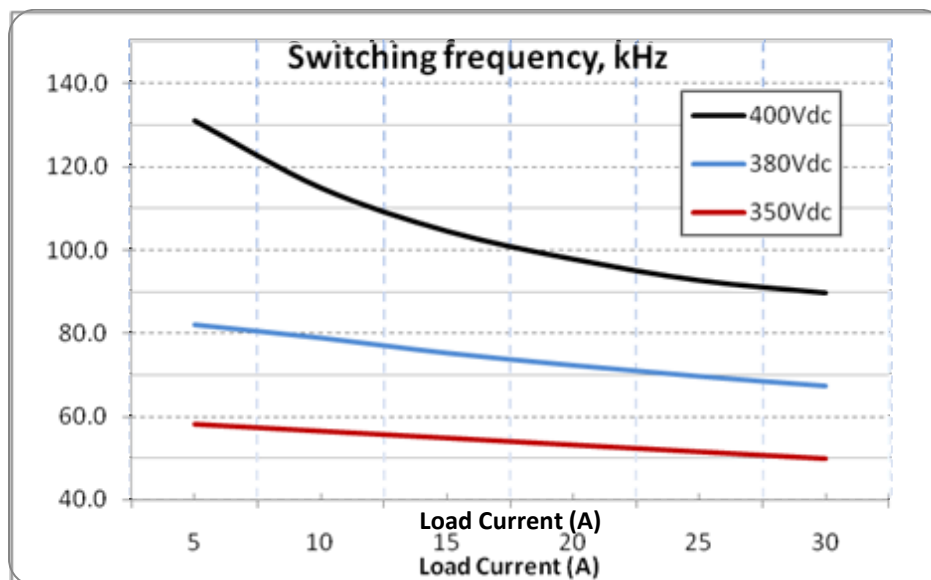


Figure 3. Switching Frequency Control in LLC Mode

4.4 Load Operation with LLC and PWM

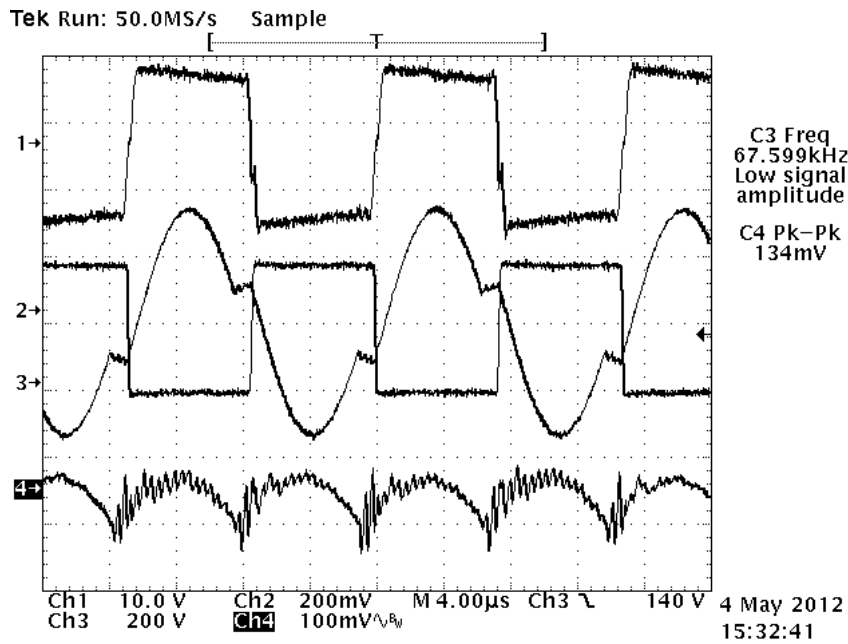


Figure 4. LLC Resonant Mode Operation at Full Load

(Ch1 = Vgs of Q7, Ch2 = Current in Resonant Network, 2A/div, Ch3 = Vds of Q7, Ch4 = Vo Ripple)

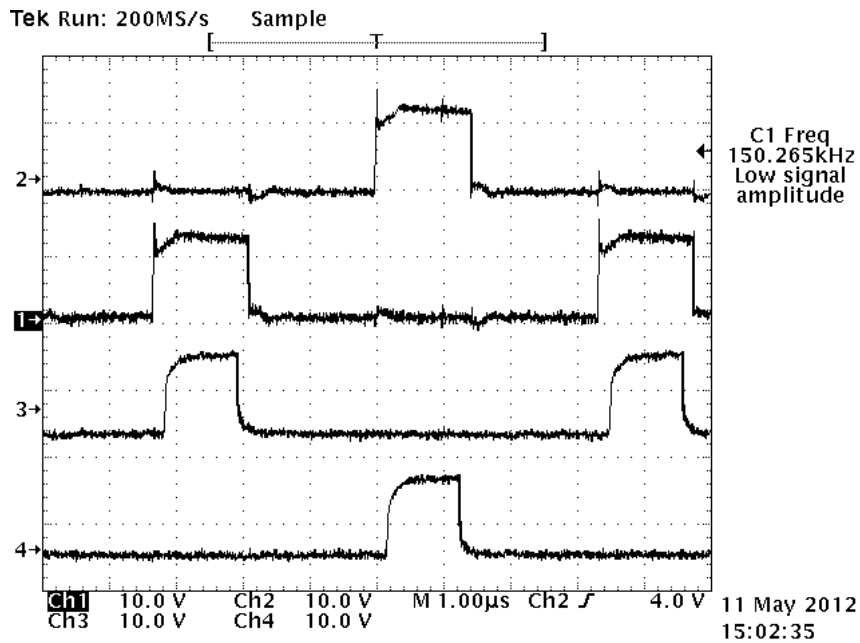


Figure 5. PWM Mode Operation after Fsw = 150kHz

(Ch1 = Vgs of Q7, Ch2 = Vgs of Q6, Ch3 = Vgs of SR2, Ch4 = Vgs of SR3)

4.5 Very Light Load Operation at High Line of Input

(Ch1 = Vgs, Q7, Ch2 = Vgs, Q6, Ch3 = Vgs, SR1, Ch4 = Vgs, SR2)

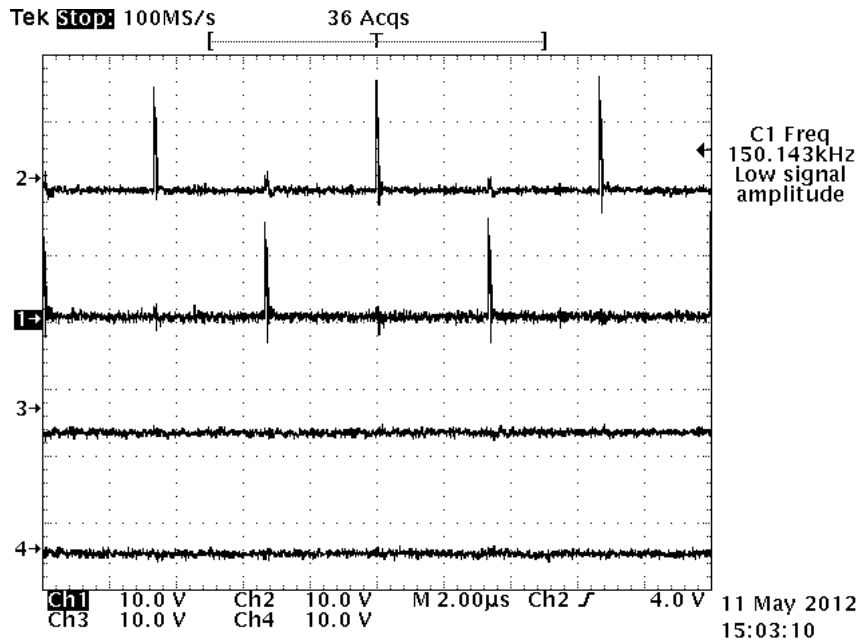


Figure 6. PWM Control at 400VDC Input and Light Load (SR off)

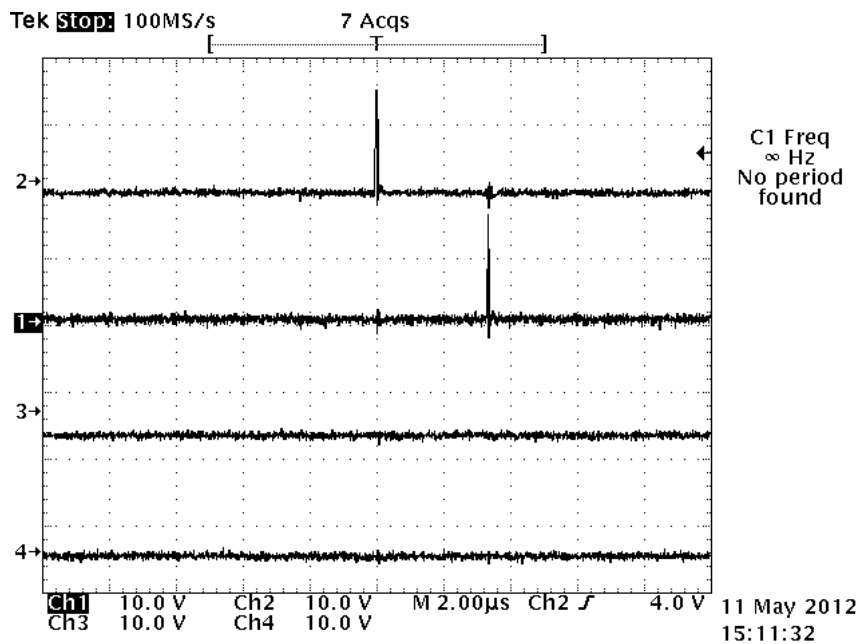


Figure 7. PWM Control with SR Off and Pulse Skipping

4.6 Output Voltage Ripple

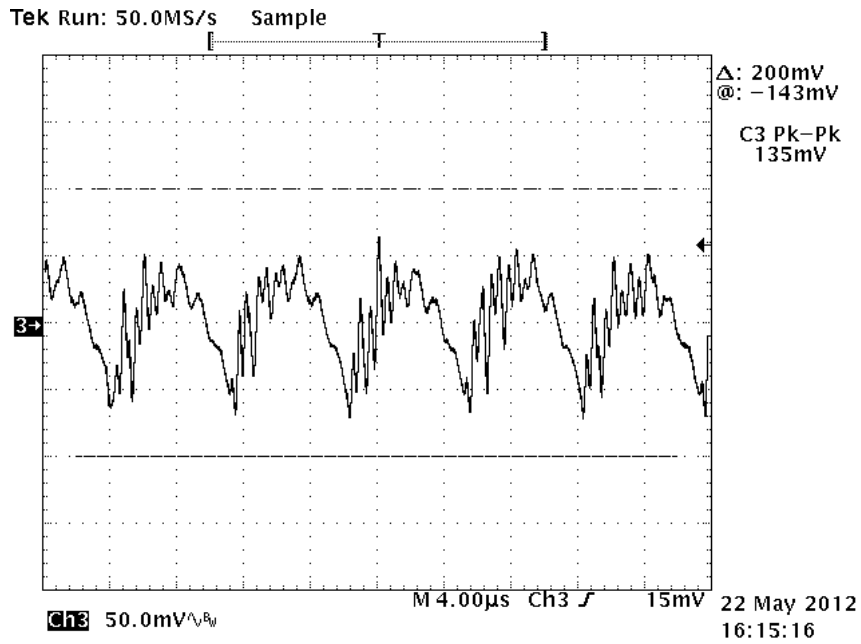


Figure 8. Output Voltage Ripple 380VDC and Full Load

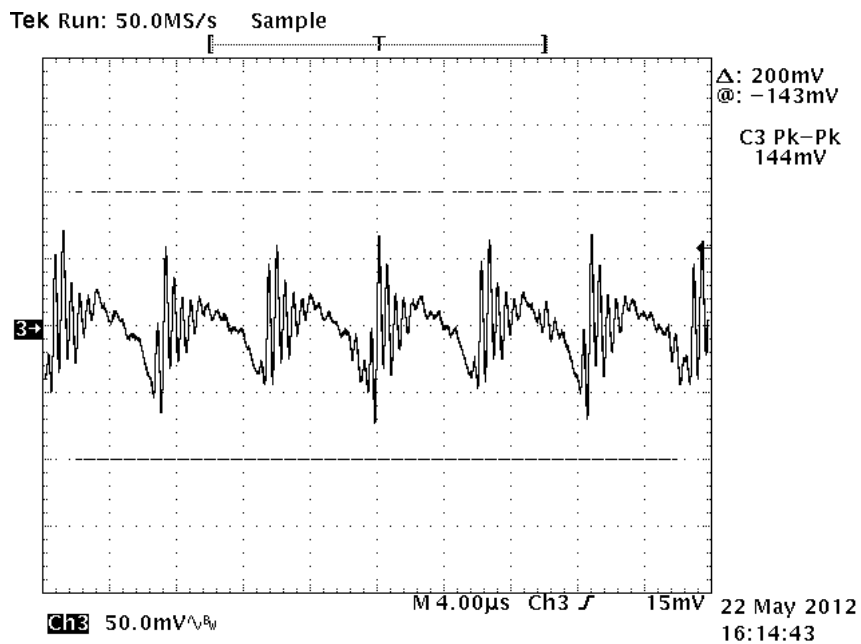


Figure 9. Output Voltage Ripple 380VDC and Half Load

4.7 Output Turn On

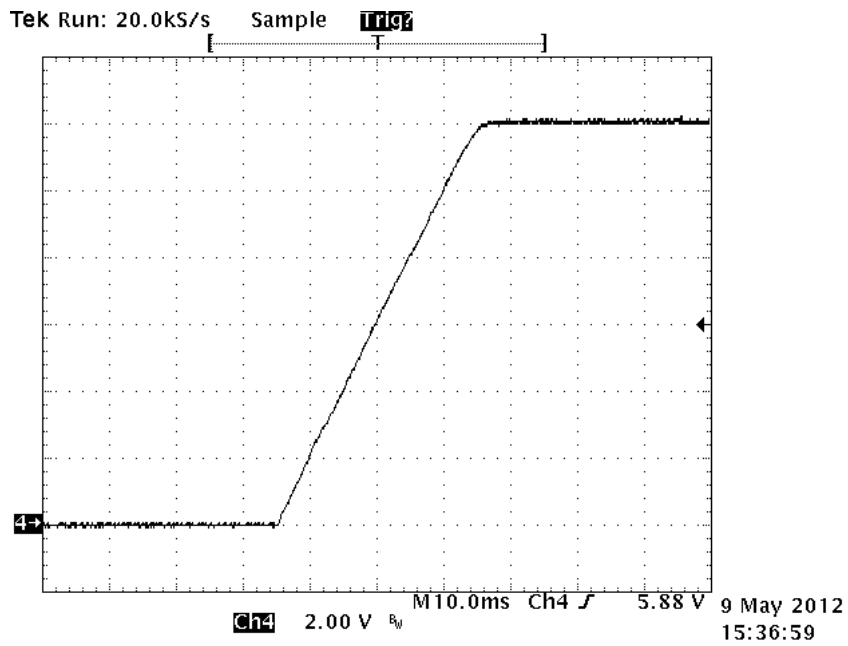


Figure 10. Output Turn On 380VDC with Load Range

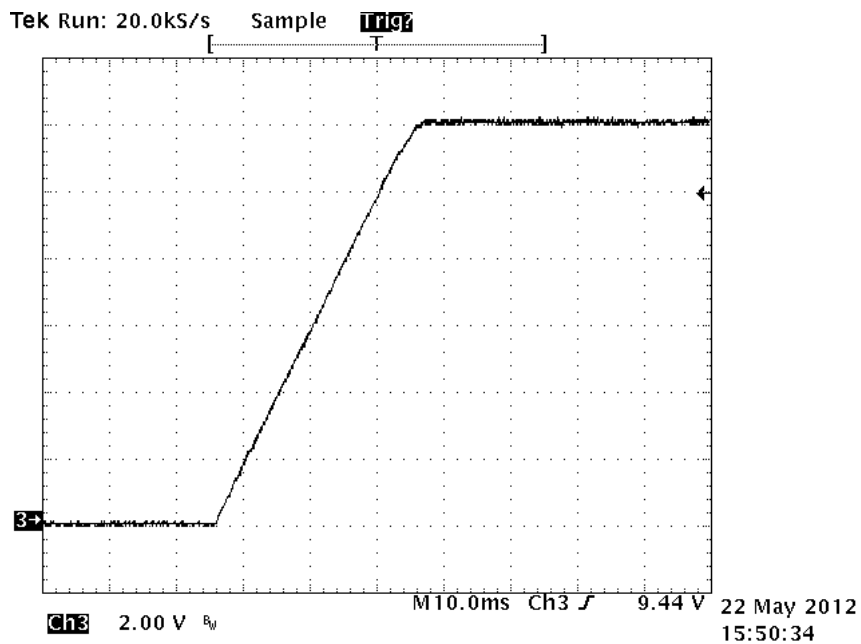


Figure 11. Output Turn On 350VDC with Load Range

4.8 Other Waveforms

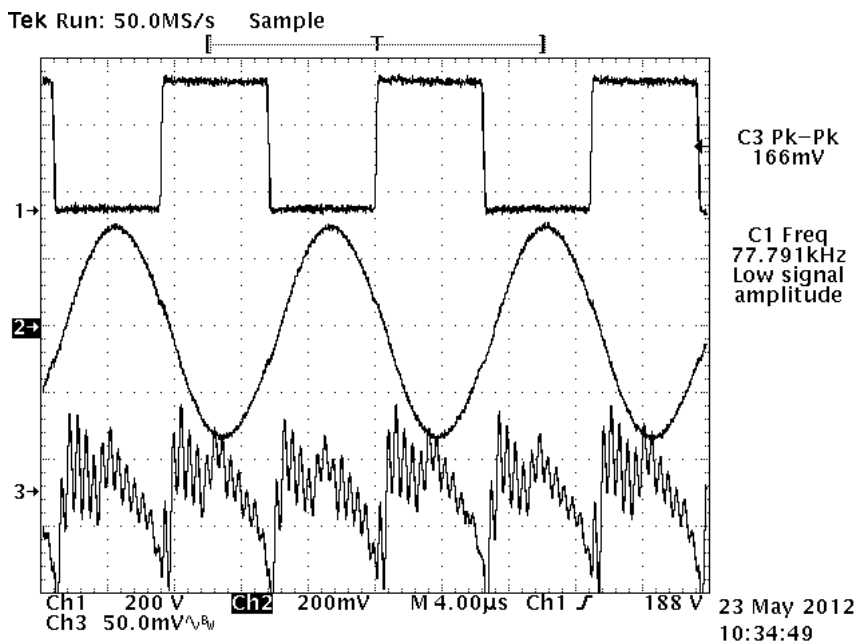


Figure 12. 380VDC and 30A before OCP Latch-off Shutdown

(Ch1 = Vds of Q7, Ch2 = Current of Resonant Network, Ch3 = Vo Ripple)

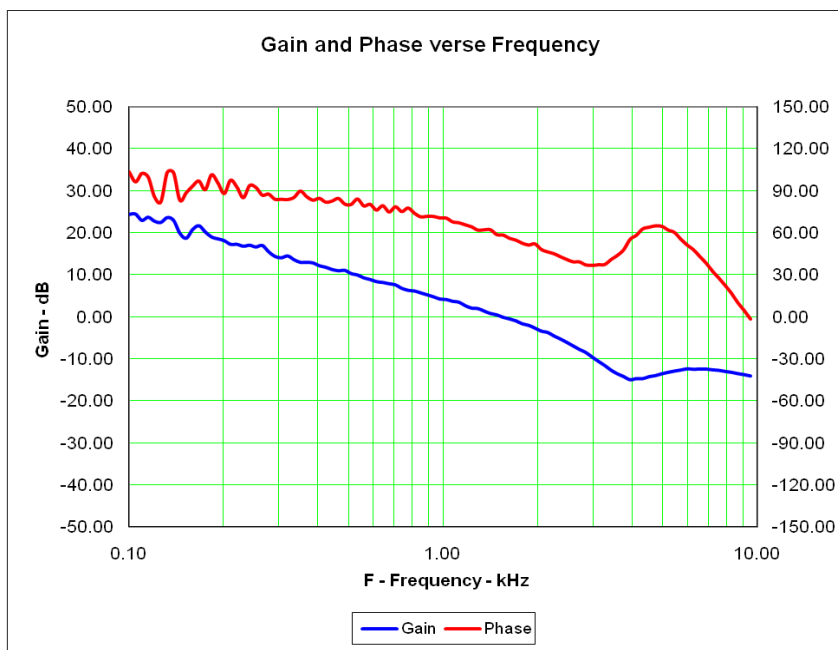


Figure 13. Control Loop Bode Plots at 380VDC and Full Load

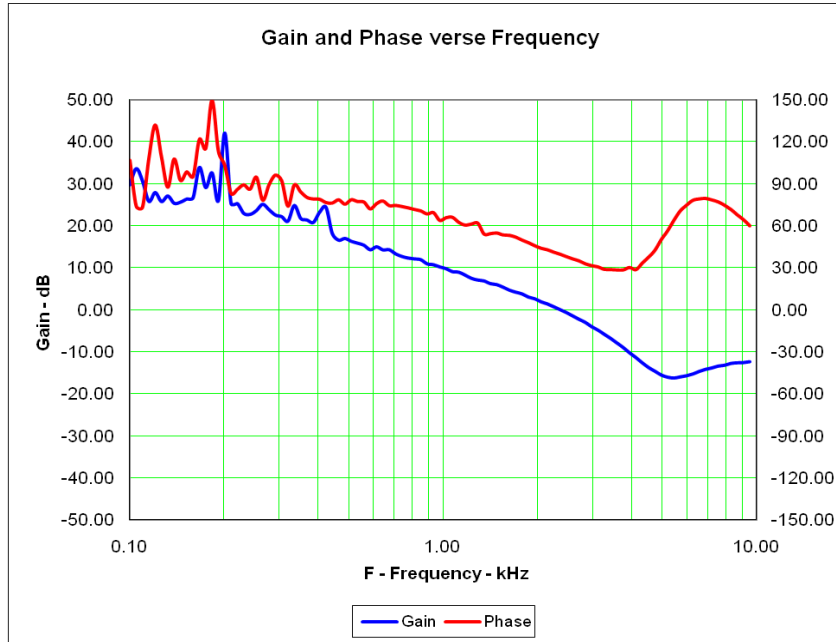


Figure 14. Control Loop Bode Plots at 400VDC and Full Load

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.