

ADC081000

Ultra-High Speed ADCs Revolutionize Digital Receiver Design



Literature Number: SNAA099

Technology Edge

Ultra-High Speed ADCs Revolutionize Digital Receiver Design

By Paul McCormack, Applications Engineer

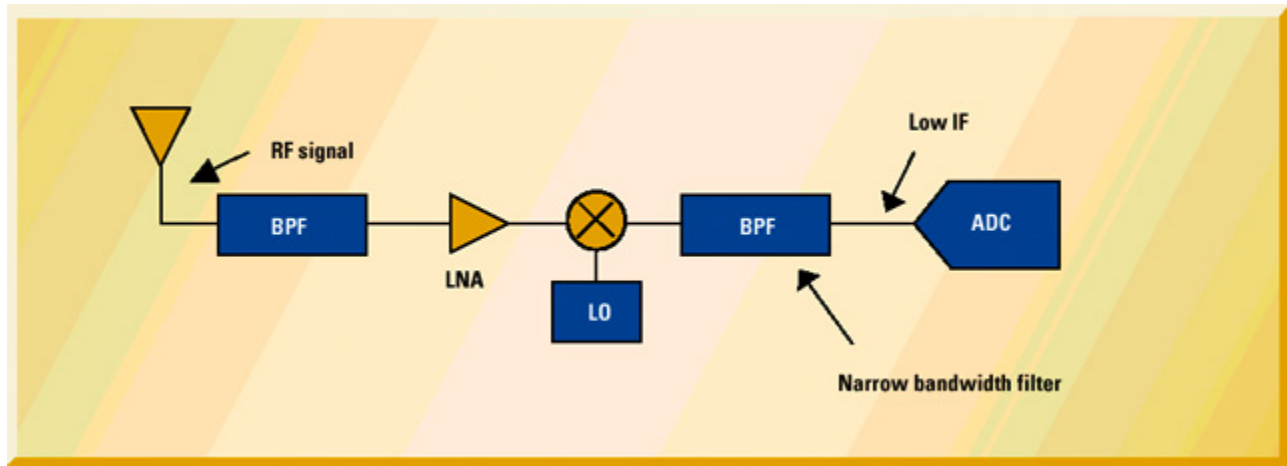


Figure 1: Conventional receiver (front end)

This article demonstrates how ultra high-speed, high-analog input bandwidth ADCs can be used in digital receivers to replace RF tuners and also to offer functionality not possible with current receivers. The conventional receiver architecture requires an RF tuner for channel selectivity in the analog domain prior to digitization and digital signal processing. The limiting factors of such an architecture are the analog input bandwidth and sampling frequency of the ADC. Until now, it has not been possible to obtain cost-effective ADCs with 1 GHz + analog input bandwidth and 1 GSPS + sampling frequency. Replacing RF tuners with a high-performance ADC such as the ADC081000 allows simultaneous digitization of the entire RF input signal. This also results in a reduction in power consumption, cost and area associated with receivers containing multiple bulky RF tuners.

The ADC081000 is an 8-bit 1 GSPS, 1.6 GHz, analog input bandwidth ADC. Manufactured on a 0.18 μm CMOS process, it is the first of its kind on the market. The majority of ultra high-speed ADCs to date are manufactured with BiCMOS processes. Compared with CMOS transistors, bipolar devices have lower offset voltages and higher gain, making them the traditional choice - particularly at high frequencies - for designing analog front ends. However, due to higher current requirements, the resultant power consumption of a bipolar device is much higher than its CMOS equivalent. In real terms, the [ADC081000](#) consumes approximately 1.4W. The lowest power BiCMOS equivalent ADC on the market represents a thermal nightmare in terms of heat dissipation and heat sink requirements, as it consumes over 3W. Not compromising dynamic performance, the ADC081000 meets the dynamic range specifications required of communications systems and high performance test instrumentation and delivers over 7.5 ENOB well past Nyquist.

Conventional Receivers

The RF signal received at the antenna is first down converted for digitization. Figure 1 shows a simple RF down conversion stage that converts the input RF frequency directly to the first IF. Normally the IF is undersampled, i.e. sampled at less than the Nyquist rate. It is worth mentioning that the process of harmonic folding that occurs in undersampling applications results in every sampled image 'folding' back into the frequency spectrum below $FS/2$ ($FS = \text{ADC sampling frequency}$). For example, the process of undersampling mixes the 36 MHz input at the ADC output down to 4 MHz at its output ($2 FS - F_{IN} = 4 \text{ MHz}$).

The ADC analog input bandwidth is usually quite small (10 – 400 MHz) so for a wide bandwidth system, channel selectivity has to be performed prior to digitization as shown in Figure 1.

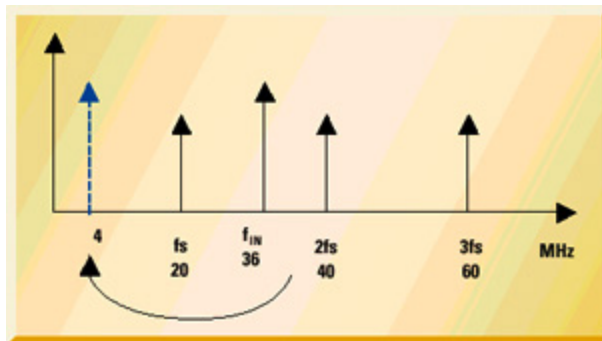


Figure 2: Undersampling in the ADC mixes f_{IN} to $< FS/2$.

System Limitation

The ADC is the limiting block in signal chain. Due to its low analog input bandwidth, channels must be filtered in the analog domain before ADC digitization.

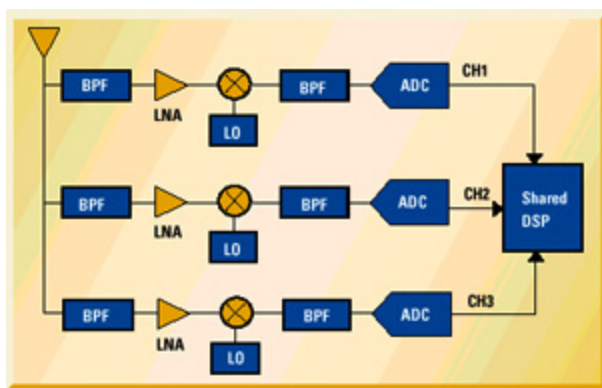


Figure 3: Multiple tuner approach

Using a multiple tuner approach, three channels can be simultaneously digitized. This is a costly solution due to the number of down-conversion stages required, and the system is still limited by the sampling frequency and analog input bandwidth of the ADCs.

In Figure 4, the ADC081000 has sufficient analog input bandwidth to digitize the entire input signal range. Channel selectivity can now be performed in the digital domain. This eliminates the need for multiple tuners prior to the ADC as shown in Figure 3.

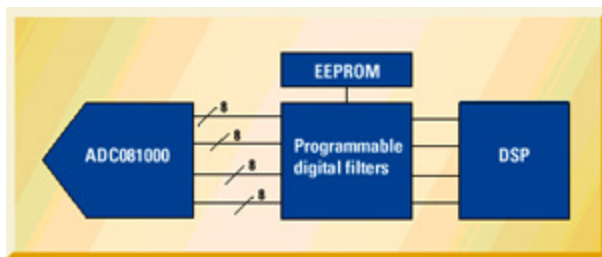


Figure 4

Figure 5 demonstrates how sampling at a much higher frequency such as 1 GSPS makes it possible to filter the digital data and retrieve the information modulated onto any of the carriers in a multi carrier system. Note that the carrier frequencies above $FS/2$ mix down to below $FS/2$, e.g. a carrier at 850 MHz mixes down to 150 MHz. The sampling frequency can be offset from 1 GSPS to accurately control the harmonic folding and thereby aid the subsequent digital filtering process.

The digital filters perform channel selectivity. All of the digitized channels are available at the ADC outputs and the filter coefficients for X number of channels are stored in the EEPROM.

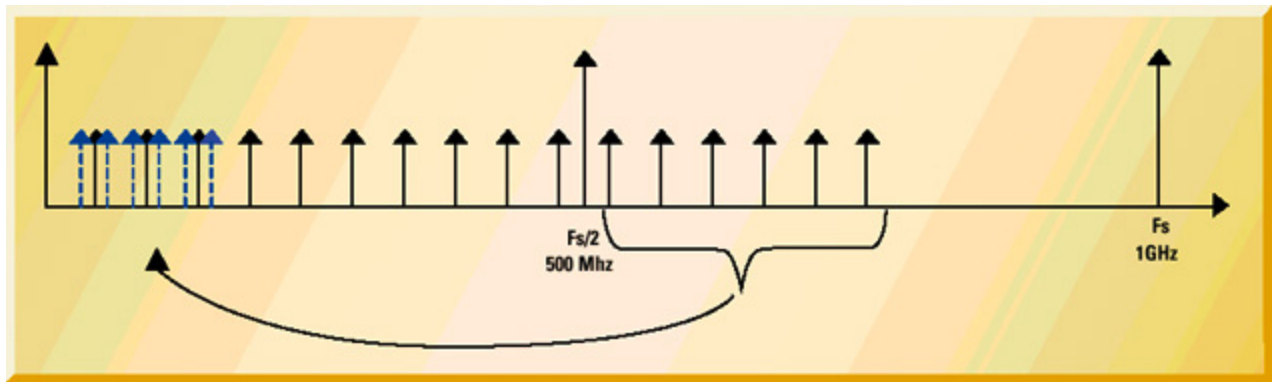


Figure 5: Sampling at 1 GSPS benefits channel selectivity

ADC081000 benefits in digital receiver applications	
Analog input bandwidth	1.6 GHz
Sampling frequency	1 GSPS
Low voltage and low power	1.4W at 1.9V
Small size (considerable saving over multiple tuner approach)	LQFP-128

For more information on ADCs visit the [ADC Featured Community](#)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated