

Solving Signal Integrity Challenges with USB 2.0 Redrivers

ABSTRACT

This application report examines why the use of a redriver is needed for signal conditioning in a USB 2.0 system design, and how to incorporate a redriver to simplify designs and meet USB 2.0 compliance.

Contents

1	Introduction	1
2	USB 2.0 Signal Integrity Challenges	2
3	Choosing to Use a USB 2.0 Redriver	2
4	Redrivers in Automotive	2
5	Summary.....	3
6	References	3

List of Figures

1	Signal Integrity Degradation.....	1
2	Flow-through Design	2
3	TUSB217 Signal Recovery	3

List of Tables

Trademarks

All trademarks are the property of their respective owners.

1 Introduction

Since its inception in 1996, Universal Serial Bus (USB) has become one of the most successful wired interfaces adopted by wide range of electronics devices and equipment across industries, such as personal electronics, automotive, industrial and enterprise systems. Even though USB data rates have evolved to support higher bandwidths over the years, currently achieving 10 Gbps per lane, it has kept the backwards compatibility of the USB 2.0 specification with up to 480 Mbps data rate for many low bandwidth applications. Even at the lower USB high speed data rate of 480 Mbps, USB signals are subject to signal degradation over cables, trace loss, and passive components in the data path, which can result in USB 2.0 compliance failures. [Figure 1](#) shows an example.

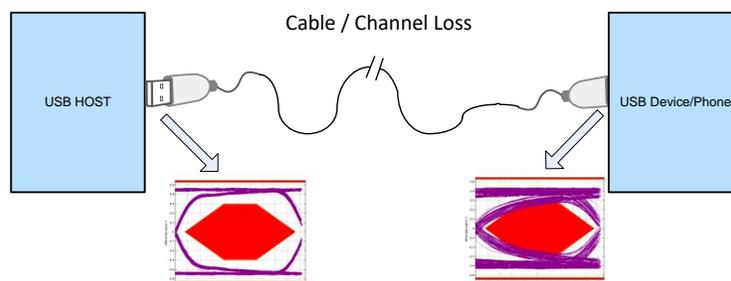


Figure 1. Signal Integrity Degradation

2 USB 2.0 Signal Integrity Challenges

USB 2.0 supports up to 480 Mbps high speed data rate along with battery charging protocols. It is a DC coupled system with wide signal swing. The USB 2.0 data path typically has many passive and active components such as switches, charging controllers, and protection devices. These components as well as connector, trace, and cable loss all contribute to the signal integrity challenges which need to be overcome in order to pass the stringent eye mask specification for USB 2.0 compliance.

3 Choosing to Use a USB 2.0 Redriver

Whether or not to use a signal conditioner in a system has always been a debate during the initial system design due to cost and board space constraints. Using a redriver can be the simplest type of signal conditioning, which also provides low latency. To ease the design effort and increase design flexibility, a USB2 redriver with small form factor and flow through trace routing can be used in the board design.

Figure 2 shows the flow-through design.

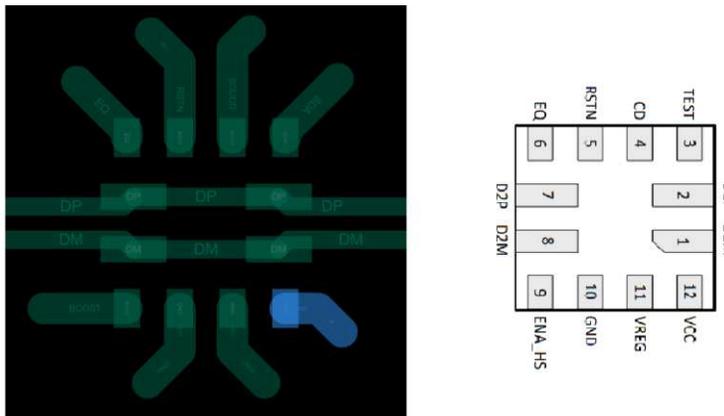


Figure 2. Flow-through Design

This allows the board designer to create one PCB board which can be populated with or without the USB2 redriver, depending on the performance needs. The board can be assembled initially without a redriver mounted. If the system were to initially fail the compliance testing, then the redriver can be easily populated on the PCB board to achieve instant compliance without the need to re-spin the board, saving valuable time and improving speed time to market cycle. The TUSB212 is an example of such a USB2 redriver. It does not break the USB 2.0 (D+ and D-) signals, and can easily be added on to the PCB to help pass USB compliance.

4 Redrivers in Automotive

Many automotive applications require long cable reach for smart phone data communication and charging between head unit or media hub ports. Some requirements include the ability to pass a near-end USB 2.0 compliance eye diagram at the connector located at the far end of the cable, that is The Remote Port. The TUSB217 can be implemented to enable support of up to a five meter cable to pass USB 2.0 near-end eye testing, CarPlay, and Android auto compliance.

Figure 3 shows a passing near-end eye diagram using the TUSB217 with a 5-m cable. The TUSB217 is also capable of passing the near-end eye diagram across various different cable lengths up to 5 m with a single configuration (with typical 28AWG USB cables).

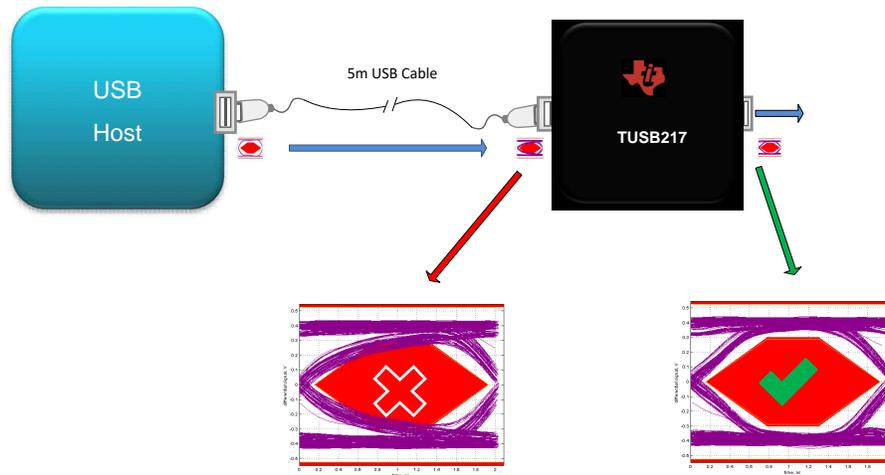


Figure 3. TUSB217 Signal Recovery

5 Summary

The Texas Instruments USB2 redriver family provides a highly efficient signal conditioning solution for wide varieties of applications to achieve instant USB compliance.

The TUSB217 is the high performance redriver capable of recovering the signal loss from a five meter cable to aid in passing USB 2.0 and CarPlay compliance testing.

The TUSB212 has a small footprint with flow through trace routing to ease the design effort and help achieve instant USB compliance.

6 References

- Texas Instruments, [TUSB212 USB 2.0 High Speed Conditioner Data Sheet](#)
- Texas Instruments, [TUSB217-Q1 USB High Speed Signal Conditioner Data Sheet](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated