

TI-RSLK

Texas Instruments Robotics System Learning Kit



TEXAS INSTRUMENTS




Module 6

Lecture: General Purpose Input Output – MSP432

General Purpose Input Output

You will learn in this module

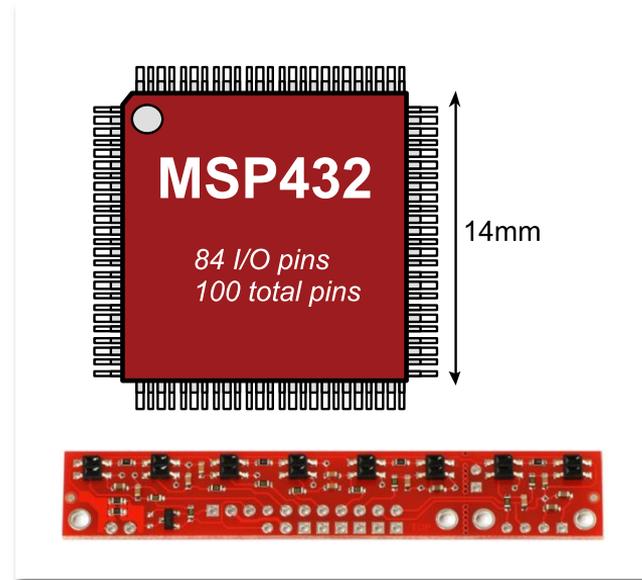- Review fundamentals of C programming namely :
 - Functions, parameters, conditionals, loops
 - Integer calculations, Time delays
- General Purpose Input Output
 - Positive and negative logic
 - Direction register
 - Input, output, friendly
 - Input/output current and voltage on pins
- Implement a two-layer input interface
 - Low-level input/output to line sensor
 - Mid-level sensor integration





Overview of Input/Output

Digital

- GPIO General Purpose Input Output
- UART Universal asynchronous receiver/transmitter
- SPI Serial peripheral interface
- I2C Inter-integrated circuit

Timer



- TimerA Periodic interrupts, input capture, and output
- Timer32 Periodic interrupts

Analog

- ADC14 Analog to digital converter
- Analog Comp Compare two analog signals




MSP432 Input/Output

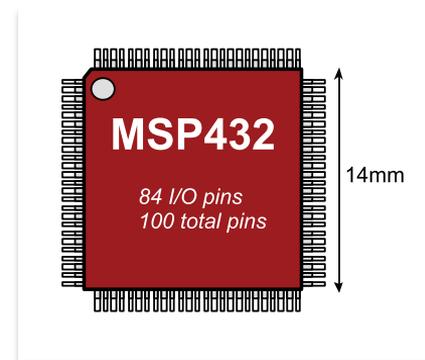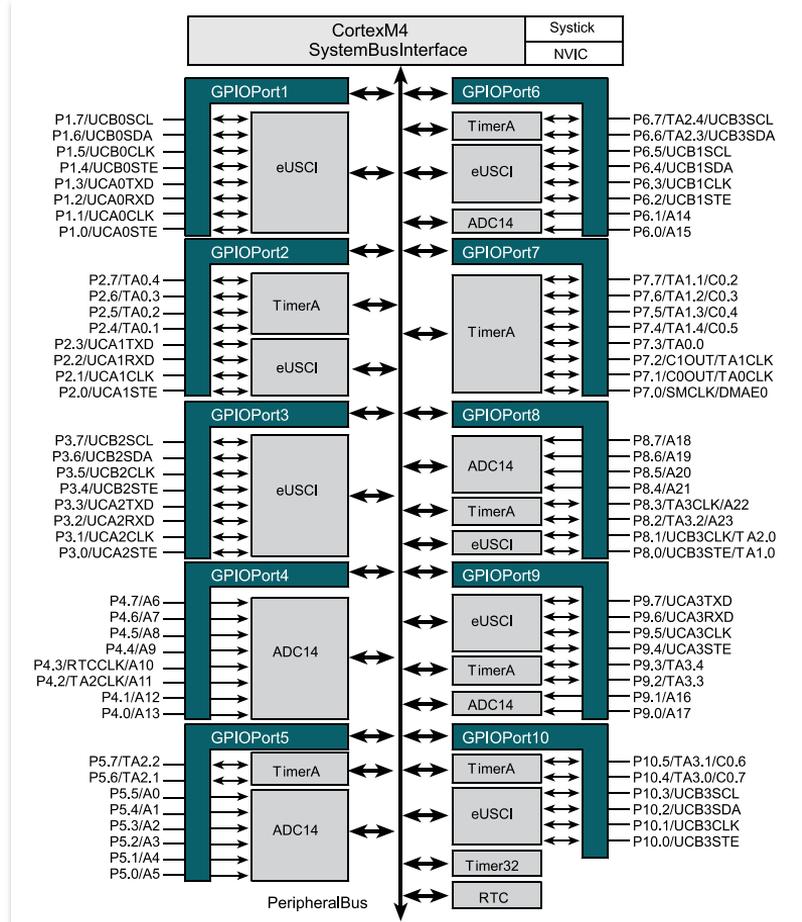




MSP432 LaunchPad

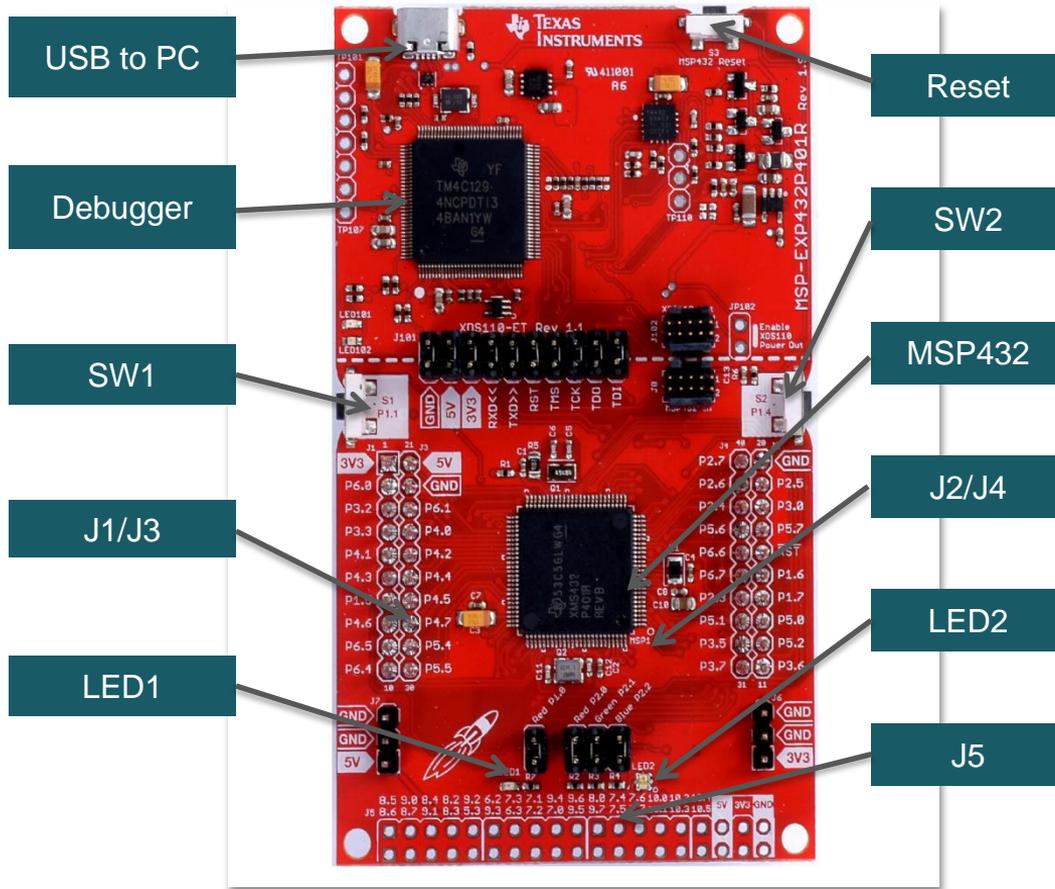







Negative logic: low voltage means true

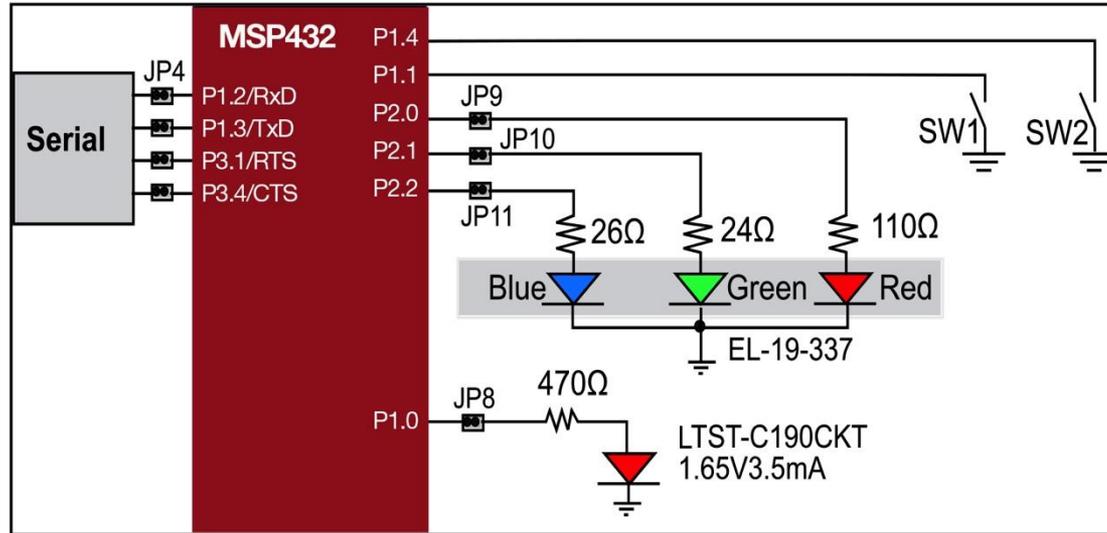

Positive logic: high voltage means true

Digital Interfacing (Circuit Model)

Voltage ↔ Digital

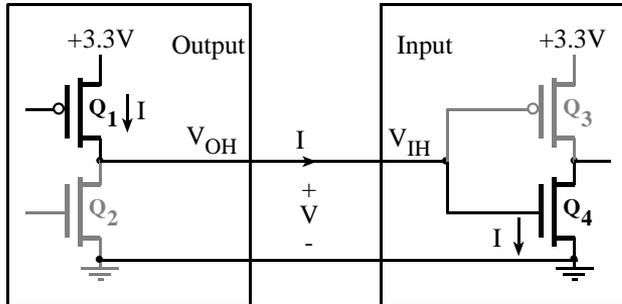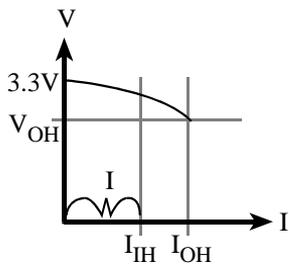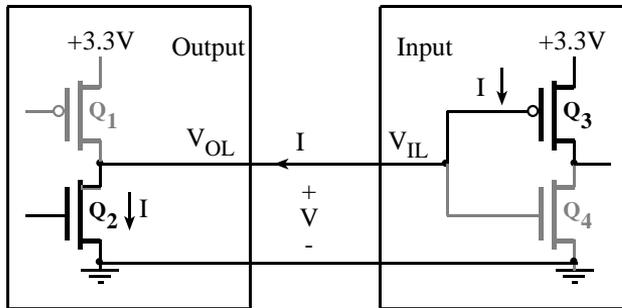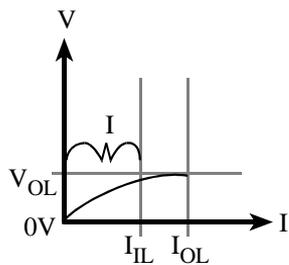


$V_{OL} \leq V_{IL}$ for all inputs and $V_{OH} \geq V_{IH}$ for all inputs
 $I_{OL} \geq \sum I_{IL}$ for all inputs and $I_{OH} \geq \sum I_{IH}$ for all inputs



Digital Interfacing (Voltages)

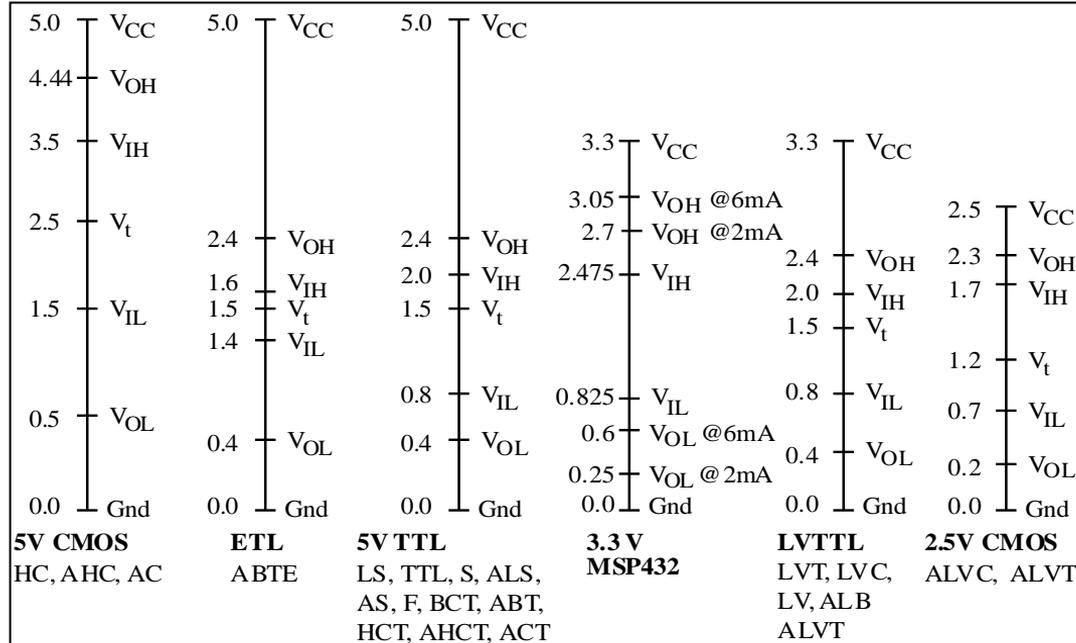Not 5V tolerant, all inputs must be 0 to 3.3V



$$V_{OL} \leq V_{IL} \text{ for all inputs} \quad \text{and} \quad V_{OH} \geq V_{IH} \text{ for all inputs}$$

$$I_{OL} \geq \sum I_{IL} \text{ for all inputs} \quad \text{and} \quad I_{OH} \geq \sum I_{IH} \text{ for all inputs}$$



Digital Interfacing (Currents)

| Family | Example | I_{OH} | I_{OL} | I_{IH} | I_{IL} |
|----------------------|----------|----------|----------|------------|-----------|
| Standard TTL | 7404 | 0.4 mA | 16 mA | 40 μ A | 1.6 mA |
| Schottky TTL | 74S04 | 1 mA | 20 mA | 50 μ A | 2 mA |
| Low Power Schottky | 74LS04 | 0.4 mA | 4 mA | 20 μ A | 0.4 mA |
| High Speed CMOS | 74HC04 | 4 mA | 4 mA | 1 μ A | 1 μ A |
| Adv High Speed CMOS | 74AHC04 | 4 mA | 4 mA | 1 μ A | 1 μ A |
| MSP432 regular drive | MSP432 | 6 mA | 6 mA | 20 nA | 20 nA |
| MSP432 high drive | MSP432 | 20 mA | 20 mA | 20 nA | 20 nA |
| TM4C 8mA-drive | TM4C123 | 8 mA | 8 mA | 2 μ A | 2 μ A |
| TM4C 12mA-drive | TM4C1294 | 12 mA | 12 mA | 2 μ A | 2 μ A |


Increased drive strength on P2.0, P2.1, P2.2, and P2.3

$$V_{OL} \leq V_{IL} \text{ for all inputs} \quad \text{and} \quad V_{OH} \geq V_{IH} \text{ for all inputs}$$
$$I_{OL} \geq \sum I_{IL} \text{ for all inputs} \quad \text{and} \quad I_{OH} \geq \sum I_{IH} \text{ for all inputs}$$



Summary

- General Purpose Input Output
 - Voltage ↔ Digital
 - Positive and negative logic
 - Pins
 - Ports
- Interfacing
 - Voltage/current
 - Input/output

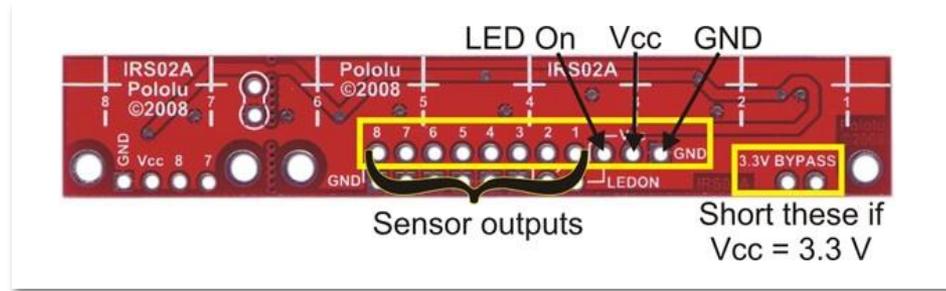



Module 6


Lecture: General Purpose Input Output - Programming



General Purpose Input Output – Programming


You will learn in this module

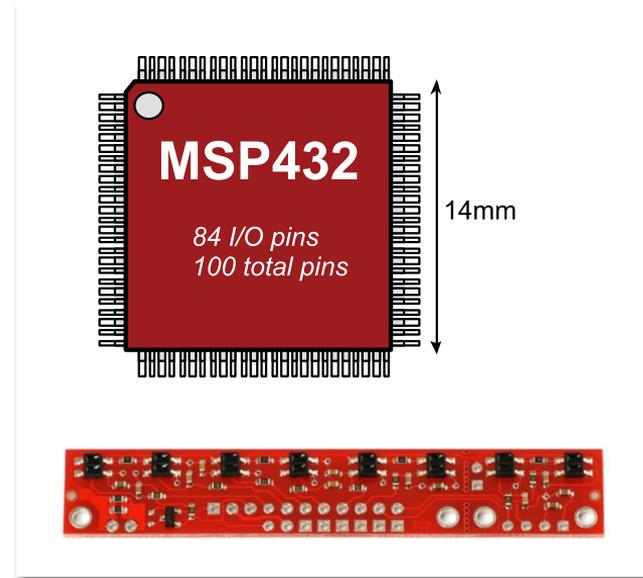- General Purpose Input Output
 - Direction register
 - Input,
 - Output,
 - Friendly
- Implement a two-layer input interface
 - Low-level input/output to line sensor
 - Mid-level sensor integration






MSP432 Input Initialization

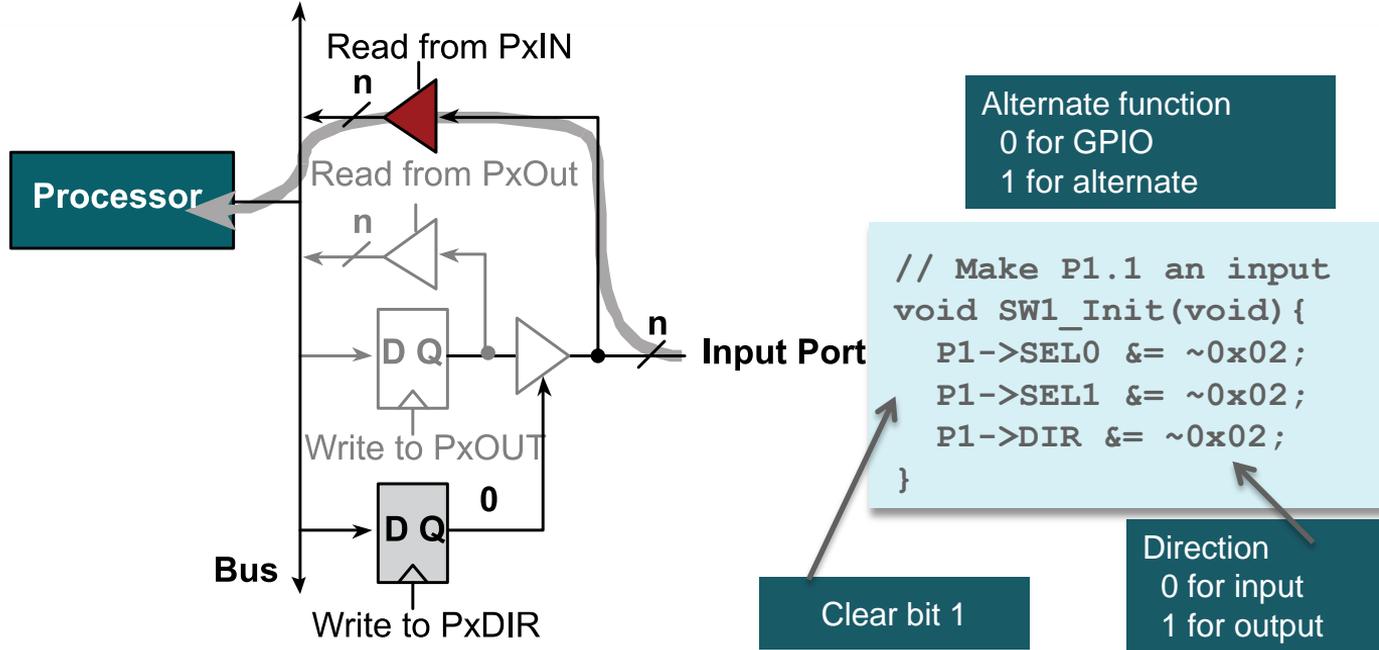

Friendly means just changes the bits you need,
without changing the bits you do not need.




MSP432 Input

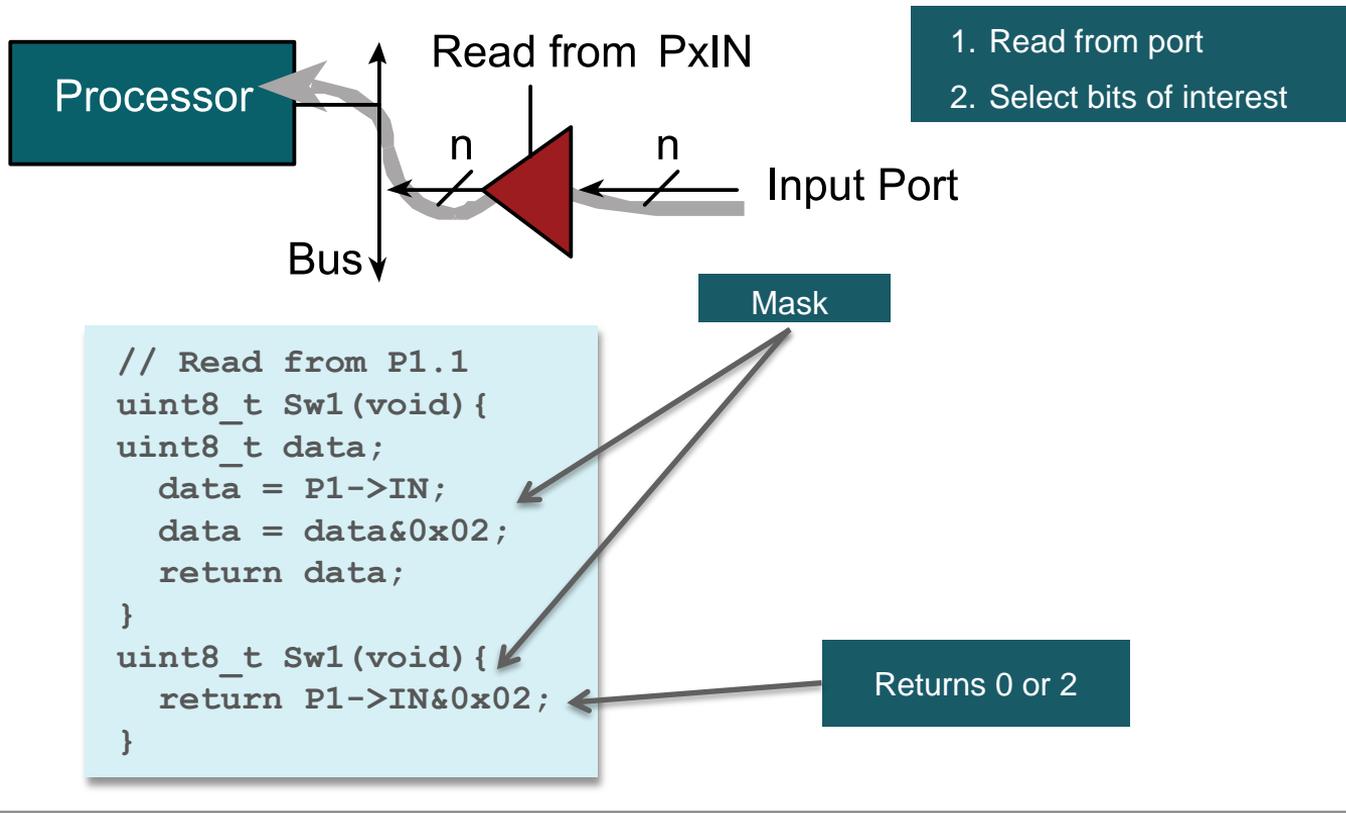




MSP432 Output Initialization

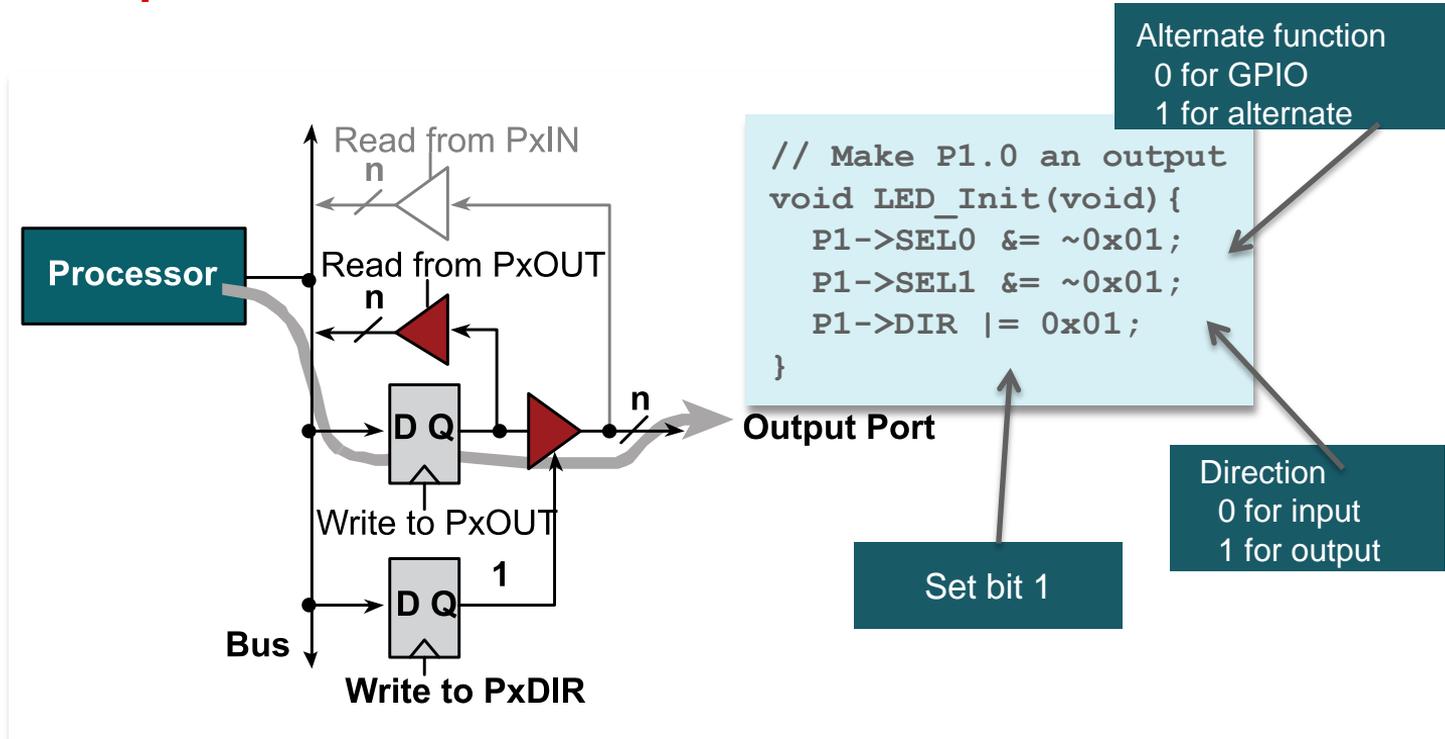

Friendly means just changes the bits you need,
without changing the bits you do not need.



MSP432 Output

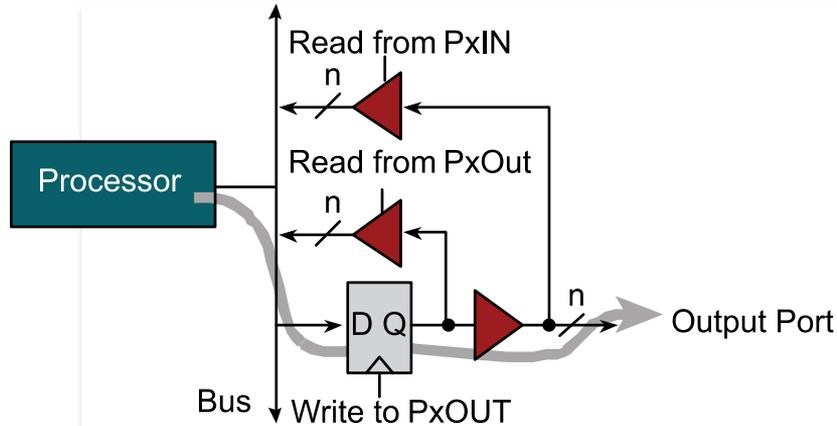

1. Read from port
2. Clear bits of interest
3. Set/clear bits of interest
4. Write back to port

```
void LED(uint8_t new) {
    uint8_t old;
    old = P1->OUT;
    old = old & (~0x01);
    new = new | old;
    P1->OUT = new;
}


void LED(uint8_t new) {
    P1->OUT = (P1->OUT & (~0x01)) | new;
}
```

Friendly

Friendly means just changes the bits you need, without changing the bits you do not need.



Solid State Relay Interface

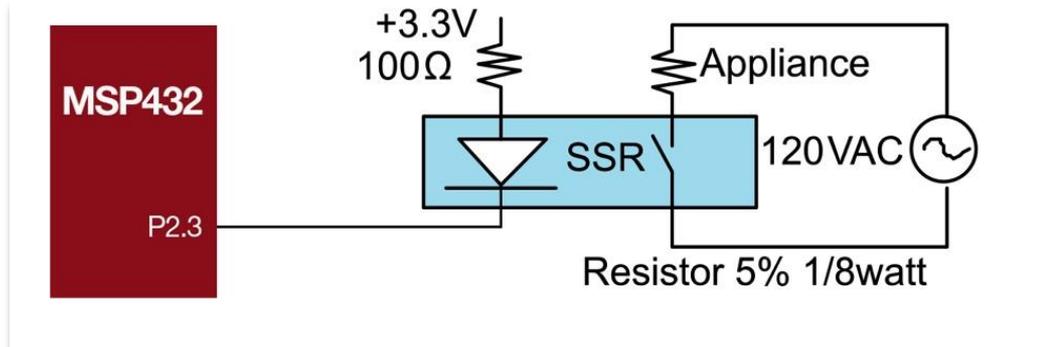


```
void SSR_Init(void) {  
    P2->SEL0 &= ~0x08;  
    P2->SEL1 &= ~0x08; // GPIO  
    P2->DIR |= 0x08;   // make pin out  
    P2->DS |= 0x08;   // high current  
}  
void SSR_On(void) {  
    P2->OUT &= ~0x08; // P2.3=0  
}  
void SSR_Off(void) {  
    P2->OUT |= 0x08;  // P2.3=1  
}
```


Negative logic



Optical Sensor Interface

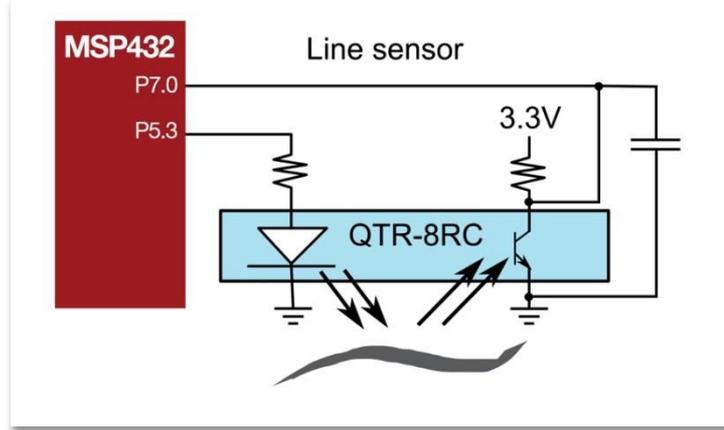

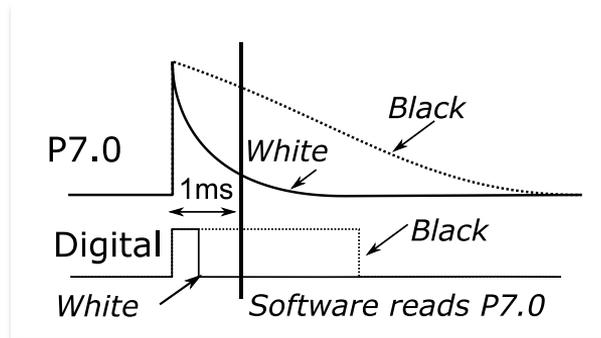1. P5.3 output high
2. P7.0 output high
3. Wait 10 us
4. P7.0 input
5. Wait 1 ms
6. Read P7.0
7. P5.3 output low






Summary

- General Purpose Input Output
 - Voltage ↔ Digital
 - Positive and negative logic
- Initialization
 - Alternate function
 - Direction register
 - Pullup/pulldown registers
 - Increase drive strength
- Input
 - Read and mask
- Output
 - *Friendly*: Read, set/clear and write

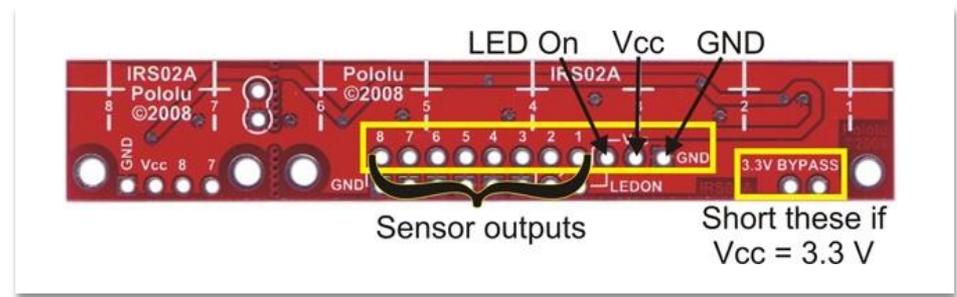1. Line sensor
2. Bump sensors
3. Motor direction
4. LCD output
5. Tachometer input
6. Ultrasonic I/O
7. BLE
8. Wifi



IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated