
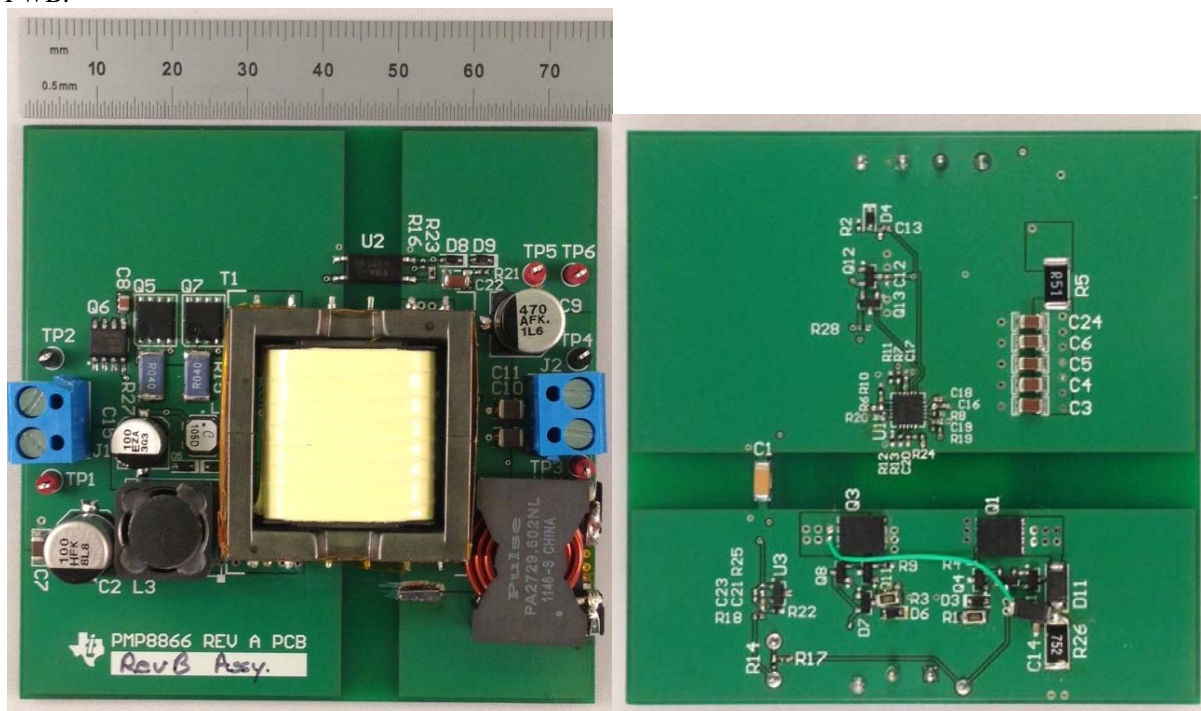


1 Photo

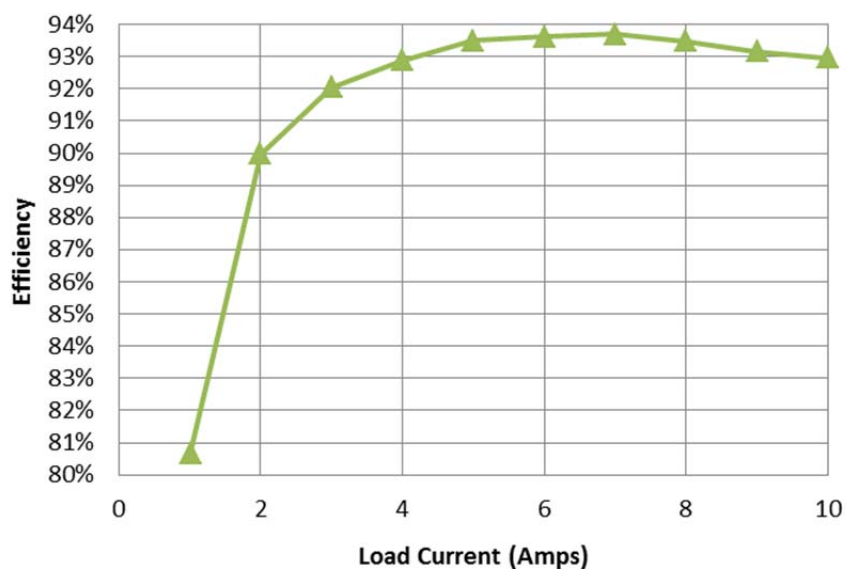The photographs below show the top and bottom views of the PMP8866 Rev B demo board. The circuit is built on a PMP8866 Rev A PWB.



2 Efficiency



I _{out}	V _{out}	V _{in}	I _{in}	P _{out}	Losses	Efficiency
0.000	11.99	24.0	0.126	0.00	3.024	0.0%
1.011	11.99	24.0	0.626	12.12	2.902	80.7%
2.003	11.99	24.0	1.112	24.02	2.677	90.0%
3.003	11.99	24.0	1.630	36.01	3.114	92.0%
3.993	11.98	24.0	2.146	47.84	3.668	92.9%
5.003	11.98	24.0	2.671	59.94	4.168	93.5%
6.007	11.98	24.0	3.203	71.96	4.908	93.6%
7.00	11.98	24.0	3.729	83.86	5.636	93.7%
8.00	11.98	24.0	4.272	95.84	6.688	93.5%
9.00	11.98	24.0	4.822	107.82	7.908	93.2%
10.00	11.98	24.0	5.37	119.80	9.080	93.0%


3 Input Under-Voltage Lock-Out

The turn-on and turn-off input voltages were measured and recorded below.

Turn-On	18.2 V
Turn-Off	17.8 V


4 Thermal Images

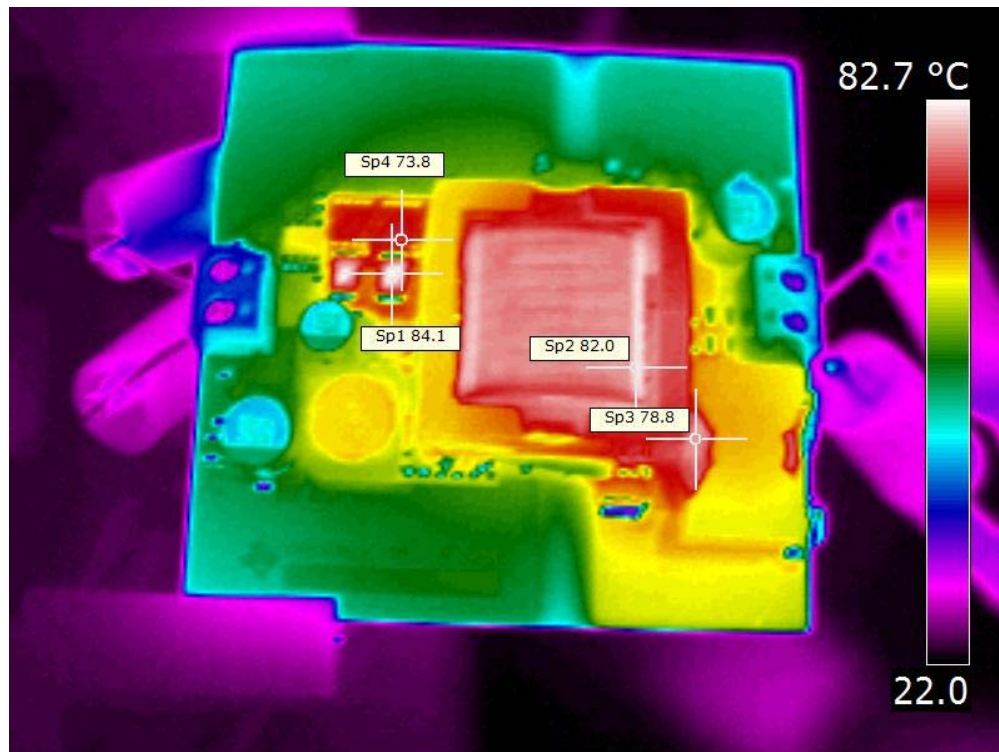The ambient temperature was 25C with no forced air flow. The output was loaded with 10A. The input was 24V.






5 Startup – 24V Input, No Load

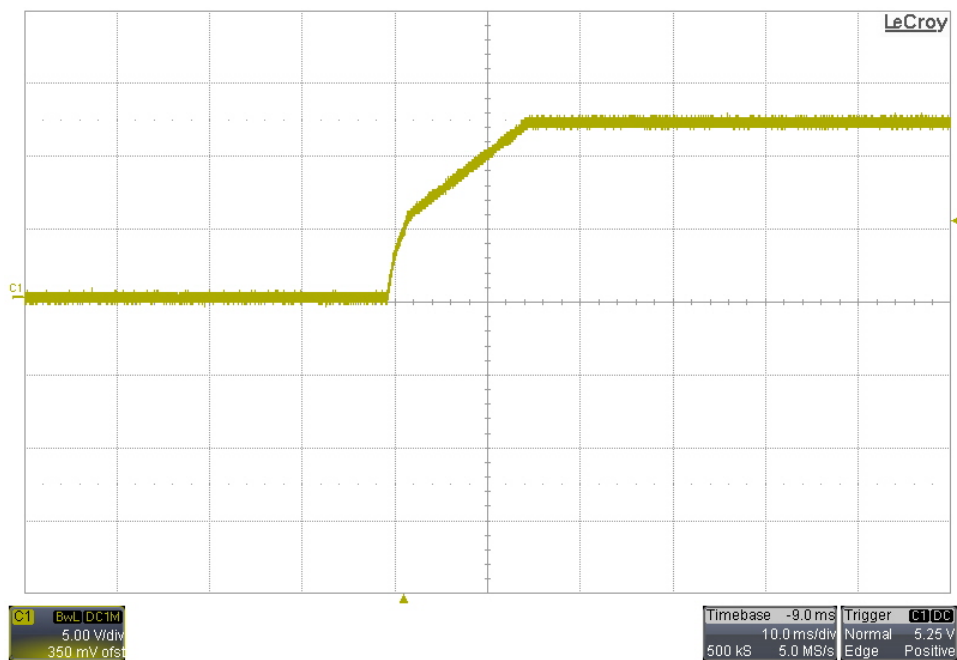


6 Startup – 24V Input, 1Ω Load

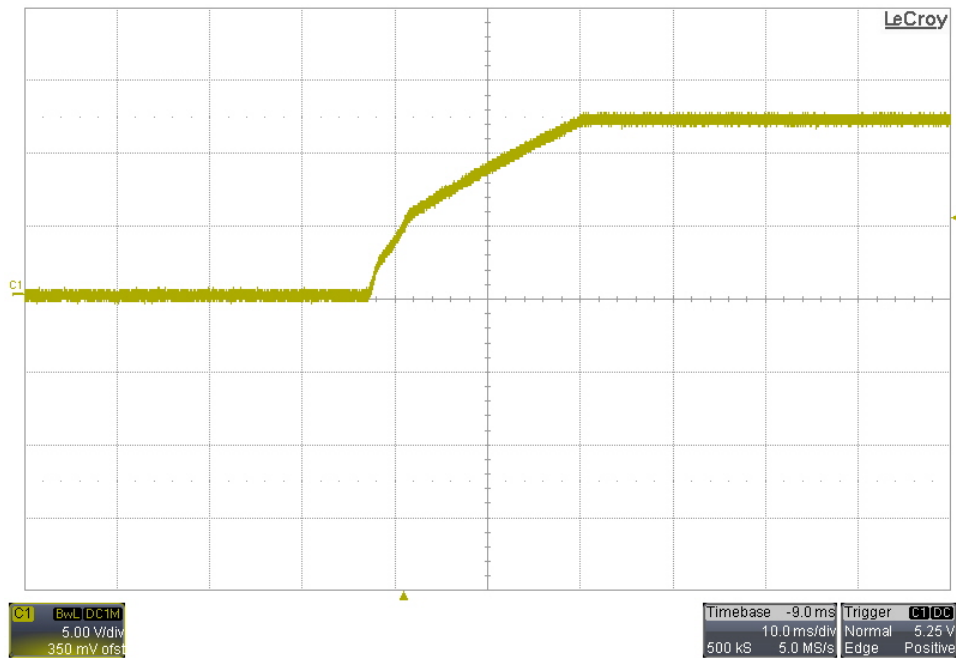

7 Output Ripple Voltage

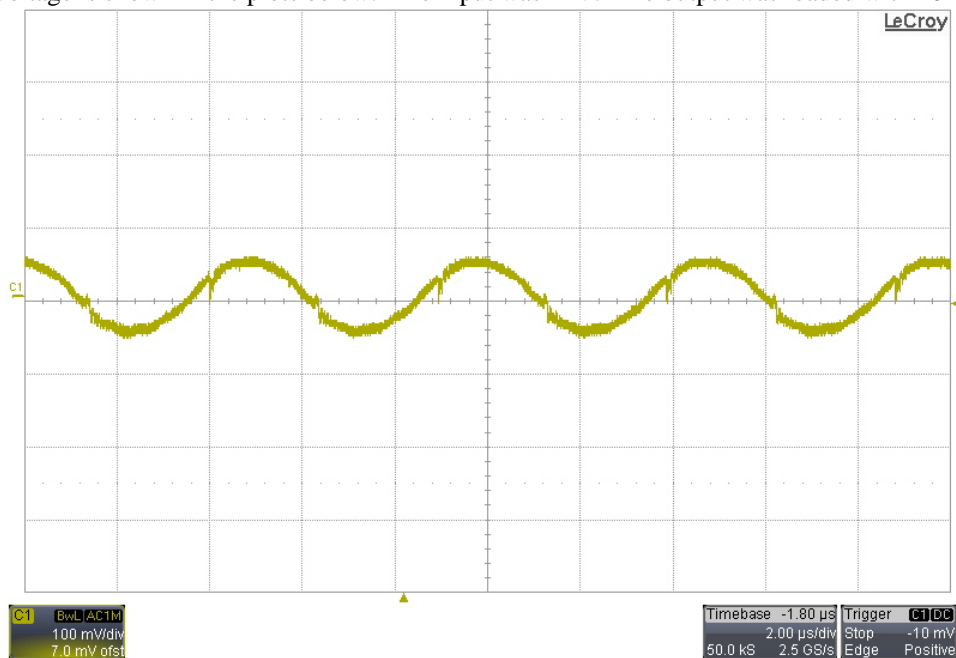
The output ripple voltage is shown in the plots below. The input was 24V. The output was loaded with 10A.




8 Frequency Response

The frequency response of the feedback loop is shown below. For the gain/phase plot #1, the input was set to 19V. For the gain/phase plot #2, the input was set to 30V. The output was loaded with 10A.

8.1 Measured Across R14

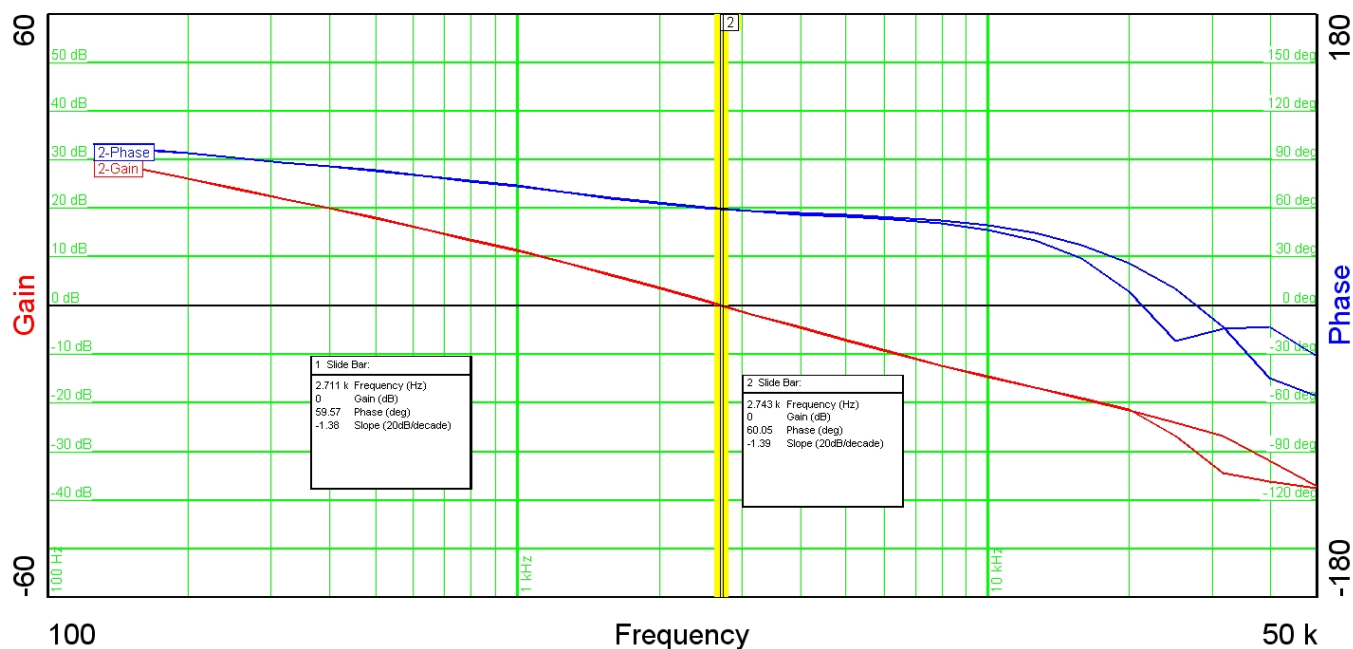


8.2 Measured Across R17

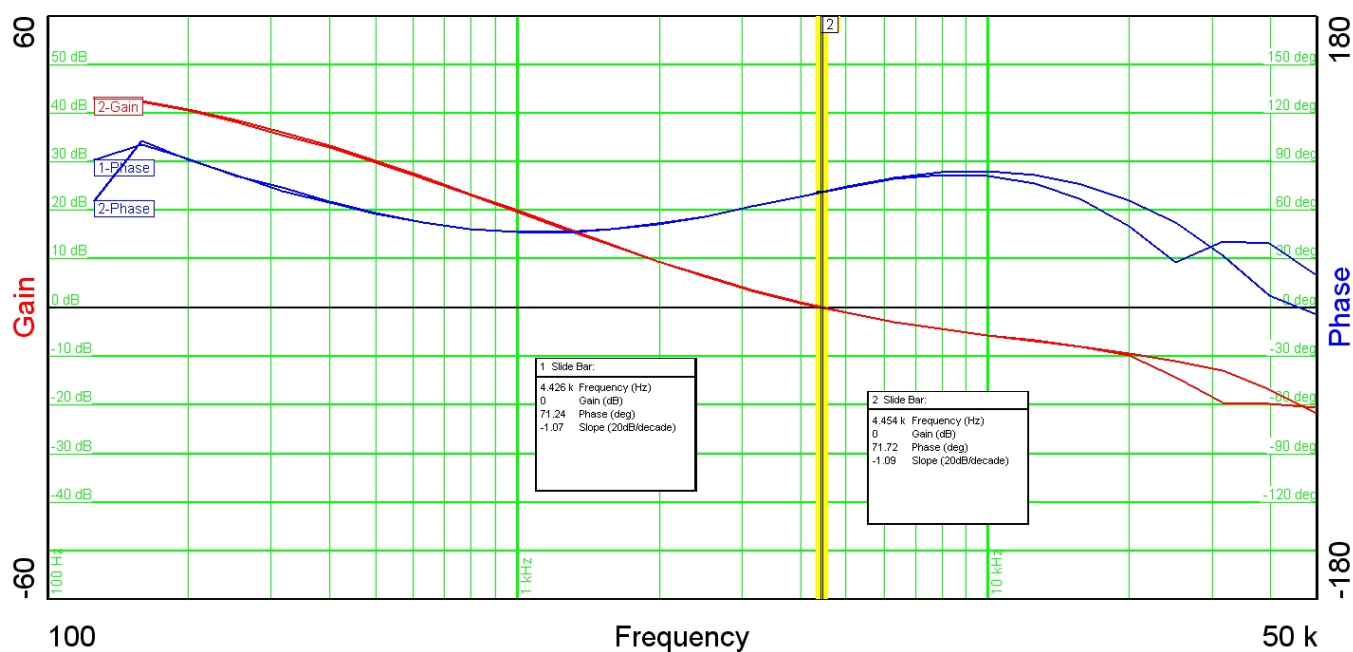

9 Load Transients

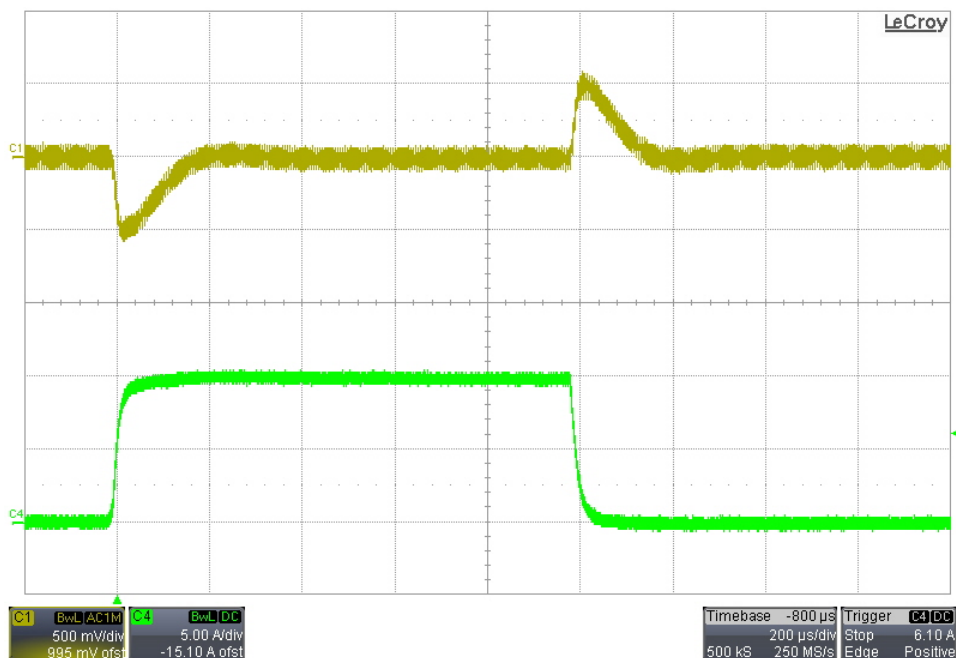
The response to a load step from 0A to 10A is shown in the images below. The input was 24V. Channel 1: Vout (ac coupled); Channel 4: Iout




10 Switching Waveforms

For the images below show the output was loaded with 10A.

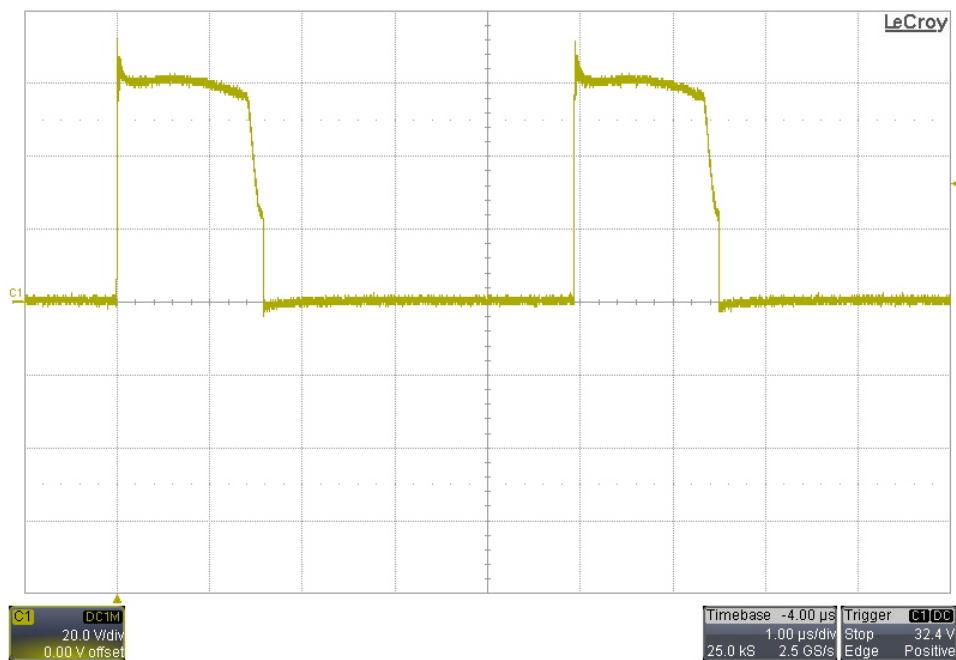10.1 Primary FETs (Q5 & Q7) Vds – 19V Input




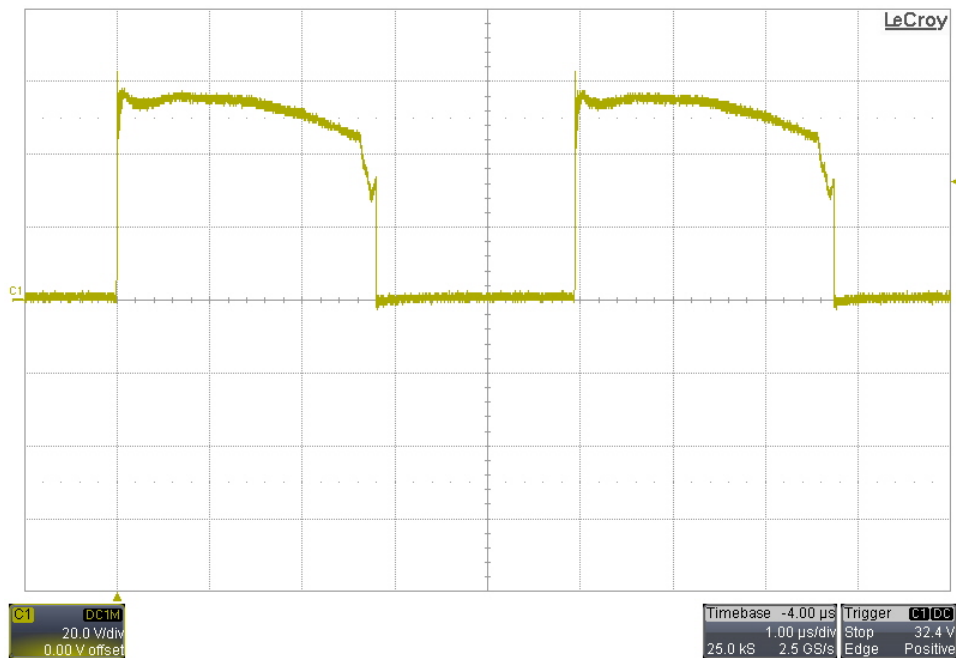10.2 Primary FETs (Q5 & Q7) Vds – 30V Input




10.3 Q1 & Q3 Synchronous FETs – 19V Input

Channel 1 – Q1 Vds; Channel 2 – Q3 Vds

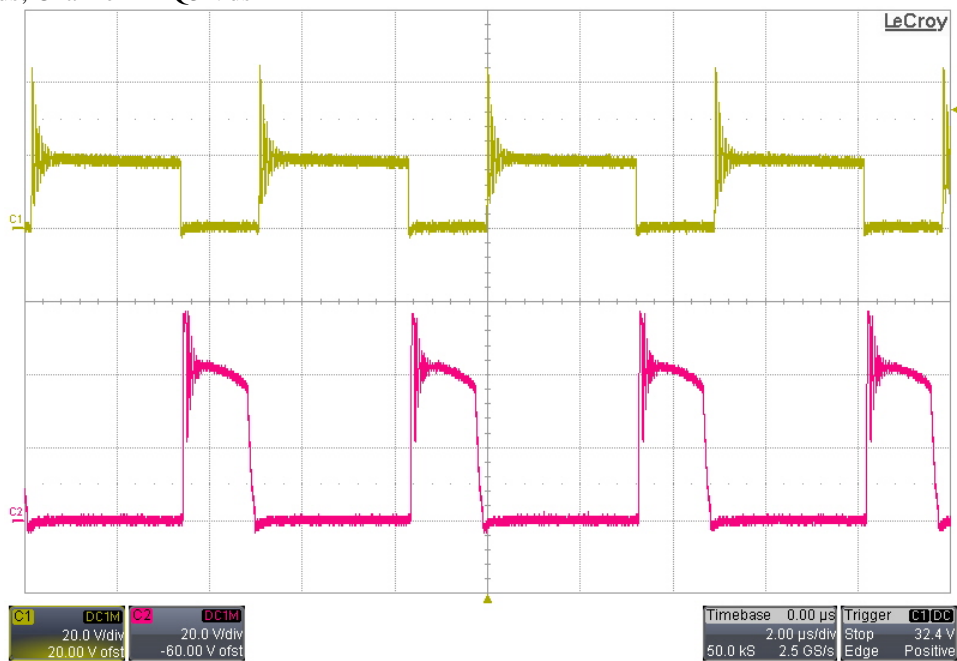

10.4 Q1 & Q3 Synchronous FETs – 30V Input

Channel 1 – Q1 Vds; Channel 2 – Q3 Vds

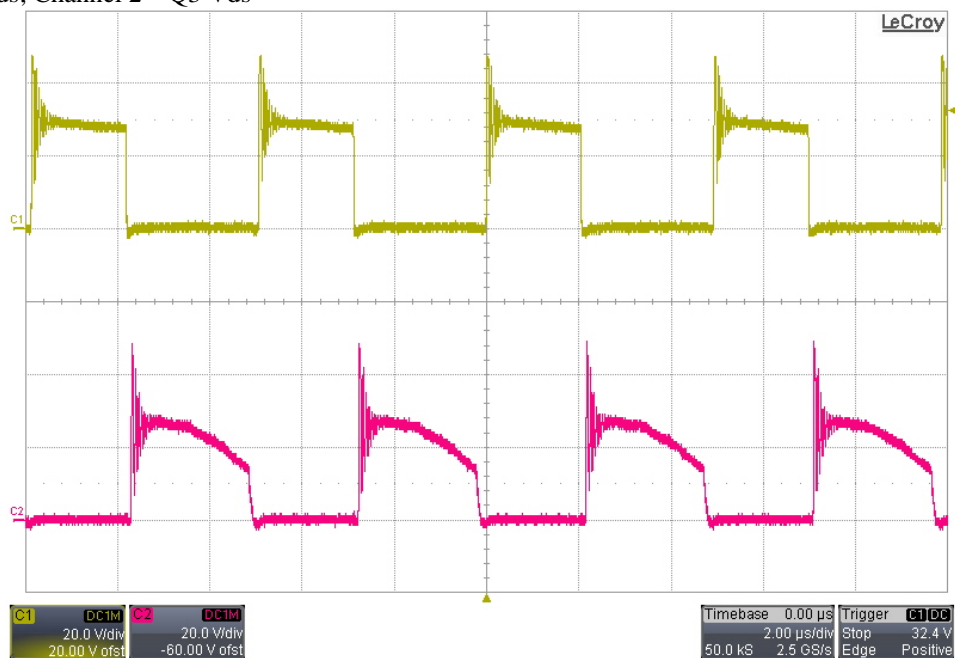

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated