

** TEXAS INSTRUMENTS Bill of Materials

TI DESIGNS

TIDA-00145

Automotive Brushed Motor Driver for Power Folding Side Mirrors (DRV8801EVM)

							_
Designator	Value	Designator	Description	Manufacturer	MFG Part Number	Size	
C1, C2, C3, C4, C10, C15, C18, C21	0.1 uF	C1, C2, C3, C4, C10, C15,	CAP .10UF 25V CERAMIC X7R	Kemet	C0805C104K3RACTU	0805	
C5	100uf	C5	CAP 100UF 63V ELECT SMG RAD	United Chemicon	ESMG630ELL101MJC5	RB 5.0mm/12.5mm	
C6	.22uf	C6		TDK Corporation	C2012X7R1E224K	0805	
C9	10uF	C9		Nichicon	UVR1E100MDD	RB .1/.250	
D1, D2, D3	Red LED	D1, D2, D3		Stanley	HBR1105W-TR	1206	
J1	14 pin Header Connector	J1		ANY	PBC07DAAN	HDR2X7 0.100"	
J2, J3	Power Conn	J2, J3		Shore Tech	OSTTA024163	5.08 mm	
J4	USB Conn	J4		Molex	67068-8000	USB B	
J5	2 pin Header Connector	J5	Single Line, 2 Pos, 100 mil pitch Header Connector	ANY	PBC02SAAN	HDR1X2 0.100"	
J6, JMP1	3 pin Header Connector	J6, JMP1	Single Line, 3 Pos, 100 mil pitch Header Connector	ANY	PBC03SAAN	HDR1X3 0.100"	
L1	10mH	L1		Steward	MI0805K400R-10	0805	
PCB1	5" x 2" CPG002 PCB Bare Board	PCB1		Selected PCB Vendor	CPG002	5" x 2"	
R1	2.2K	R1		Yageo	RC0805JR-072K2L	0805	
R2	330	R2		стѕ	766163331GP	SMD	
R3	4.7K	R3		Yageo	RC0805JR-074K7L	0805	
R4, R8	3.3K	R4, R8	RES 3.3K OHM 1/8W 5% 0805 SMD	Yageo	RC0805JR-073K3L	0805	
R5	.2	R5		Vishay	WSL2512R2000FEA	2512	
R11	196K	R11	RES 196K OHM 1/8W 1% 0805 SMD	Panasonic	ERJ-6ENF1963V	0805	
R12	110K	R12	RES 110K OHM 1/8W 5% 0805 SMD	Yageo	RC0805JR-07110KL	0805	
51	Push Button	S1	SWITCH LIGHT TOUCH 4.3MM 100GF	Panasonic	EVQ-11A04M	4.3 mm	
TP1	1	TP1		Keystone	5005	Test Point 0.052"	
P2	1	TP2		Keystone	5006	Test Point 0.052"	
S1, TS2, TS5, TS6, TS7, TS8, TS9,	White	TS1, TS2, TS5, TS6, TS7,		Keystone	5002	Test Point 0.040"	
S17	Black	TS17		Keystone	5001	Test Point 0.040"	
ΓS18	Red	TS18		Keystone	5003	Test Point 0.040"	
U1		U1		Texas Instruments	MSP430F1232IDW	28-SOIC	
U2	Driver	U2	IC DMOS FUL-BRDG MOTOR	Texas Instruments	DRV8800PWP	HTSSOP-16	

Designator	Value	Designator	Description	Manufacturer	MFG Part Number	Size	Quantity
U4		U4	750 mA LDO 8-SOIC	Texas Instruments	TPS77701D	8-SOIC	1
U6		U6	IC USB TO SERIAL UART 28-	FTDI	FT232RL R	28-SSOP	1
Y1	32.768 KHz	Y1	CRYSTAL 32.768 KHZ 12.5PF	Citizen	CMR200T32.768KDZF-	SMD	1
							55

TI DESIGNS

TIDA-00145

Automotive Brushed Motor Driver for Power Folding Side Mirrors (DRV8872EVM)

•	Value	Designator		Manufacturer	MFG Part Number	Size
PCB1		!PCB1		Any	MDBU006	0805
:1	0.1uF	C1		Kemet	C0603C104M4RACTU	RB 5.0mm/12.5mm
	0.04	100.00	20%, X7R, 0603		00000\/400\/EDAOTII	200=
2, C7	0.01uF	C2, C7	CAP, CERM, 0.01 μF, 50 V, +/-	Kemet	C0603X103K5RACTU	0805
	47	00	10%, X7R, 0603	Danasaria	FFF FK4 1470D	DD 4/050
3	47uF	C3	CAP, AL, 47 µF, 63 V, +/- 20%, 0.65 ohm, SMD	Panasonic	EEE-FK1J470P	RB .1/.250
4	10. 5		· ·	Tata Walan	LIMICOGEARTACOKAAT	1000
4	10uF	C4	CAP, CERM, 10 µF, 50 V, +/-	Taiyo Yuden	UMK325AB7106KM-T	1206
5	1uF	C5	10%, X7R, 1210 CAP, CERM, 1 μF, 50 V, +/-	AVX	08055C105KAT2A	HDR2X7 0.100"
)	lur	C5	10%, X7R, 0805	AVA	00000C100KA12A	
6	2.2uF	C6		Kemet	C0603C225K8PACTU	5.08 mm
	2.241	00	10%, X5R, 0603	Tromot	00000022010171010	0.00 11111
8	0.1uF	C8	CAP, CERM, 0.1 µF, 100 V, +/-	Kemet	C0805C104K1RACTU	USB B
			10%, X7R, 0805			
1, D2	40V	D1, D2		Vishay-Siliconix	MSS1P4-M3/89A	HDR1X2 0.100"
			MicroSMP			
3	Red	D3	LED, Red, SMD	Lite-On	LTST-C190CKT	HDR1X3 0.100"
, H2, H3, H4		H1, H2, H3, H4	Bumpon, Hemisphere, 0.44 X	3M	SJ-5303 (CLEAR)	0805
			0.20, Clear			
, J2		J1, J2	Terminal Block, 6A, 3.5mm	On-Shore Technology	ED555/2DS	5" x 2"
, J6		J3, J6	Header, 100mil, 3x1, Tin, TH	Sullins Connector Solutions	PEC03SAAN	0805
, J7		J4, J7	Header, 1x1, Tin, TH	Sullins Connector Solutions	PEC01SAAN	SMD
i		J5	Header, 100mil, 2x1, Tin, TH	Sullins Connector Solutions	PEC02SAAN	0805
L1		LBL1	Thermal Transfer Printable	Brady	THT-14-423-10	0805
	3.40Meg	R1	RES, 3.40 M, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06033M40FKEA	2512
	-					
2	10.0k	R2	RES, 10.0 k, 1%, 0.1 W, 0603	Panasonic	ERJ-3EKF1002V	0805
3	1.07Meg	R3	RES, 1.07 M, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06031M07FKEA	0805
	3			,		
	50k	R4	TRIMMER, 50k ohm, 0.5W, TH	Bourns	3386P-1-503TLF	4.3 mm
5, R7	0	R5, R7		Vishay-Dale	CRCW06030000Z0EA	Test Point 0.052"
	0.15	R6	· · · · · ·	Stackpole Electronics Inc	CSRN2512FKR150	Test Point 0.052"
8	10k	R8	RES, 10k ohm, 5%, 0.1W, 0603	•	CRCW060310K0JNEA	Test Point 0.040"
•			100001111, 070, 0.144, 0000	Violity Daio	ONO VIOLOGIALA	1.00(1.011(0.040
9	390	R9	RES, 390 ohm, 5%, 0.1W, 0603	Vishav-Dale	CRCW0603390RJNEA	Test Point 0.040"
			1720, 030 01111, 370, 0.177, 0003	Violity Daie	ONO V OOO OOO OO OOO OOO	TOSET OIRE U.U-U
H-J1, SH-J2	1x2	SH-J1, SH-J2	Shunt, 100mil, Gold plated,	3M	969102-0000-DA	Test Point 0.040"
- ,	_		Black		33332	
P1, TP2, TP3, TP4, TP5, TP6, TP7,	SMT	TP1, TP2, TP3, TP4, TP5,		Keystone	5016	28-SOIC
,, 0,, 0, 0, 7,		TP6, TP7, TP8, TP9	1. John Jane, Compact, Civil	1.10,010110	100.10	1-0 00.0

Designator	Value	Designator	Description	Manufacturer	MFG Part Number	Size	Quantity		
TP10		TP10	1mm Uninsulated Shorting Plug, 10.16mm spacing, TH	Harwin	D3082-05	HTSSOP-16	1		
U1		U1	Single Output LDO, 100 mA, Adjustable 1.2 to 18.5 V Output, 3 to 60 V Input, with Enable and Power Good, 8-pin MSOP (DGN), -40 to 125 degC, Green (RoHS & no Sb/Br)	Texas Instruments	TPS7A1601DGNR	8-SOIC	1		
U2		U2	LinCMOS Timer, D0008A	Texas Instruments	TLC555CD	28-SSOP	1		
U3		U3	H-Bridge PWM Motor Driver with Fault Reporting, DDA0008H	Texas Instruments	DRV8872DDAR	SMD	1		
FID1, FID2, FID3		FID1, FID2, FID3	Fiducial mark. There is nothing to buy or mount.	N/A	N/A		0		
R10	200k	R10	TRIMMER, 200k ohm, 0.5W, TH	Bourns	3386P-1-204TLF		0		
Approved Notes							48		
		1. These assemblies are ESD sensitive, ESD precautions shall be observed.							
		2. These assemblies must be clean and free from flux and all contaminants.							
		Use of no clean flux is not acceptable.							
		3. These assemblies must comply with workmanship standards IPC-A-610 Class 2.							
		4. Ref designators marked with an asterisk ("*") cannot be substituted.							
		All other components can	be substituted with equivalent MFC	G's components.					

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ('TI") reference designs are solely intended to assist designers ("Designer(s)") who are developing systems that incorporate TI products. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.

Tl's provision of reference designs and any other technical, applications or design advice, quality characterization, reliability data or other information or services does not expand or otherwise alter Tl's applicable published warranties or warranty disclaimers for Tl products, and no additional obligations or liabilities arise from Tl providing such reference designs or other items.

TI reserves the right to make corrections, enhancements, improvements and other changes to its reference designs and other items.

Designer understands and agrees that Designer remains responsible for using its independent analysis, evaluation and judgment in designing Designer's systems and products, and has full and exclusive responsibility to assure the safety of its products and compliance of its products (and of all TI products used in or for such Designer's products) with all applicable regulations, laws and other applicable requirements. Designer represents that, with respect to its applications, it has all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. Designer agrees that prior to using or distributing any systems that include TI products, Designer will thoroughly test such systems and the functionality of such TI products as used in such systems. Designer may not use any TI products in life-critical medical equipment unless authorized officers of the parties have executed a special contract specifically governing such use. Life-critical medical equipment is medical equipment where failure of such equipment would cause serious bodily injury or death (e.g., life support, pacemakers, defibrillators, heart pumps, neurostimulators, and implantables). Such equipment includes, without limitation, all medical devices identified by the U.S. Food and Drug Administration as Class III devices and equivalent classifications outside the U.S.

Designers are authorized to use, copy and modify any individual TI reference design only in connection with the development of end products that include the TI product(s) identified in that reference design. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of the reference design or other items described above may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS AND OTHER ITEMS DESCRIBED ABOVE ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY DESIGNERS AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS AS DESCRIBED IN A TI REFERENCE DESIGN OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

Tl's standard terms of sale for semiconductor products (http://www.ti.com/sc/docs/stdterms.htm) apply to the sale of packaged integrated circuit products. Additional terms may apply to the use or sale of other types of TI products and services.

Designer will fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of Designer's non-compliance with the terms and provisions of this Notice.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2016, Texas Instruments Incorporated