

Experimental Results

Specifications

- Line Voltage = 88VAC ~ 269VAC
- Line Frequency = 47 ~ 63Hz
- Output voltage regulation
 - +3.3V Rail: +/-10%
 - -3.3V Rail: -10% to +50%
- Output ripple voltage
 - +3.3V rail : < 30mV
 - -3.3V rail : < 150mV
- Output load Current
 - Minimum load current
 - +3.3V Rail: 10mA (relay off, 31xx in idle connected, incl LED)
 - -3.3V Rail: 2mA < 150mV for -3.3V rail.
 - Normal load current
 - +3.3V Rail: 300mA (incl relay)
 - -3.3V Rail: 4mA
 - Maximum load current
 - +3.3V Rail: 600mA (incl relay)
 - -3.3V Rail: 6mA
- Efficiency = > 75%
- Topology: Single-stage flyback

1 Efficiency

1.1.1 No Load Input Power		115Vac	10.75mW
		230Vac	18.7mW
Overall Efficiency at Minimum Load	> 75%, For +3.3V Rail: 10mA (relay off, 31xx in idle connected, incl LED) For -3.3V Rail: 2mA	115Vac 230Vac	57.66% 55%
Efficiency at Nominal Load	> 75%	115Vac 230Vac	72.46% 70.4%
Efficiency at Maximum Load	>75%	115Vac 230Vac	72.71% 71.29%


2 Output Voltage regulation

2.1.1 Nominal Voltage	+3.3V and -3.3V		
Regulation Tolerance	For +3.3V Rail: +/-10% For -3.3V Rail: -10% to +50%		
Minimum Current	For +3.3V Rail: 10mA (relay off, 31xx in idle connected, incl LED) For -3.3V Rail: 2mA	90Vac 115Vac 230Vac 264Vac	3.23/-3.196 3.24/-3.198 3.23/-3.189 3.23/-3.188
Nominal Current	For +3.3V Rail: 300mA (incl relay) For -3.3V Rail: 4mA	90Vac 115Vac 230Vac 264Vac	3.23/3.58 3.235/3.58 3.23/-3.58 3.23/-3.58
Maximum Current	For +3.3V Rail: 600mA (incl relay) For -3.3V Rail: 6mA	90Vac 115Vac 230Vac 264Vac	3.249/-3.735 3.248/-3.733 3.25/-3.74 3.25/-3.754

3 Output ripple Voltage


Ripple (mVpp – 1MHz) Maximum Load	< 30mV for +3.3V rail.	90Vac 115Vac 230Vac 264Vac	40mV 39.7mV 45mV 45.3mV
	< 150mV for -3.3V rail.	90Vac 115Vac 230Vac 264Vac	5mV 5.1mV 6.5mV 7.9mV
	LF Worst Case Ripple, 110mA load +3.3V	220Vac	45mV

4 Output ripple voltage waveform

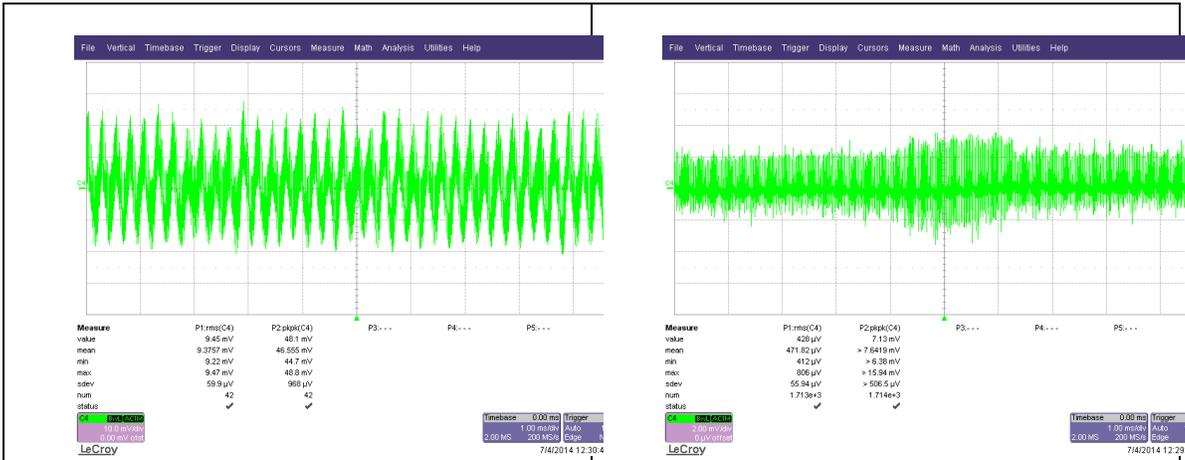

3.3V 264V 600mA Load Ripple and Noise


-3.3V 264V 6mA Load Ripple and Noise

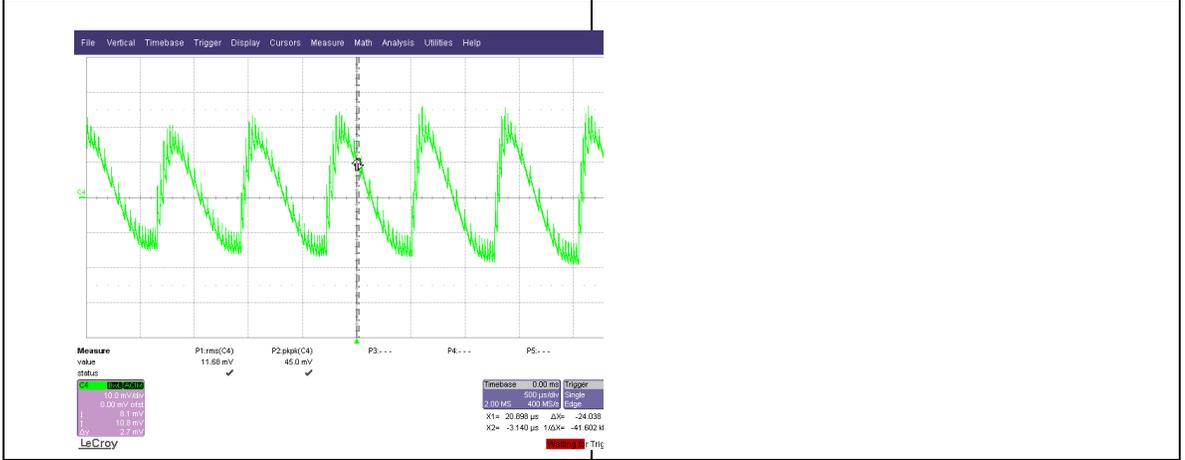

3.3V 220Vac 110mA Load Ripple and Noise

5 Dynamic Load Regulation


Dynamic Load Regulation (mV)	< 100mV for +3.3V rail for 50mA to 400mA step		
	< 300mV for -3.3V rail.		

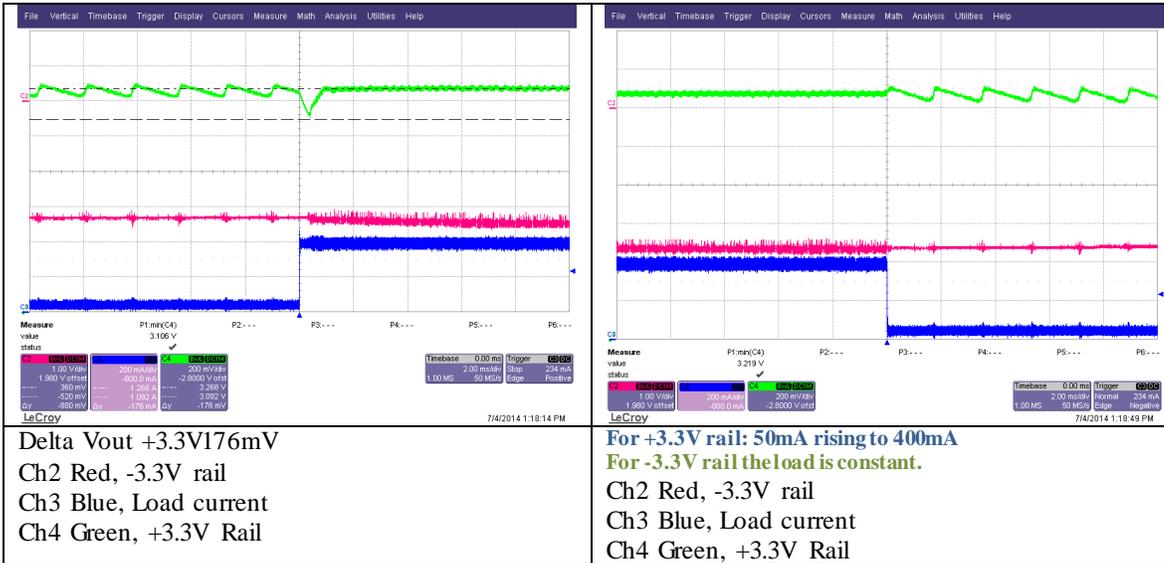

6 Turn-on Time

Turn-on Time	<0.5sec	90Vac	120ms
Maximum Overshoot at Turn-on	Within 3.7V for +3.3V rail. Within 6V for -3.3V rail.	3.3V	<4V

Current Limit	650mA	680mA	
----------------------	--------------	--------------	--

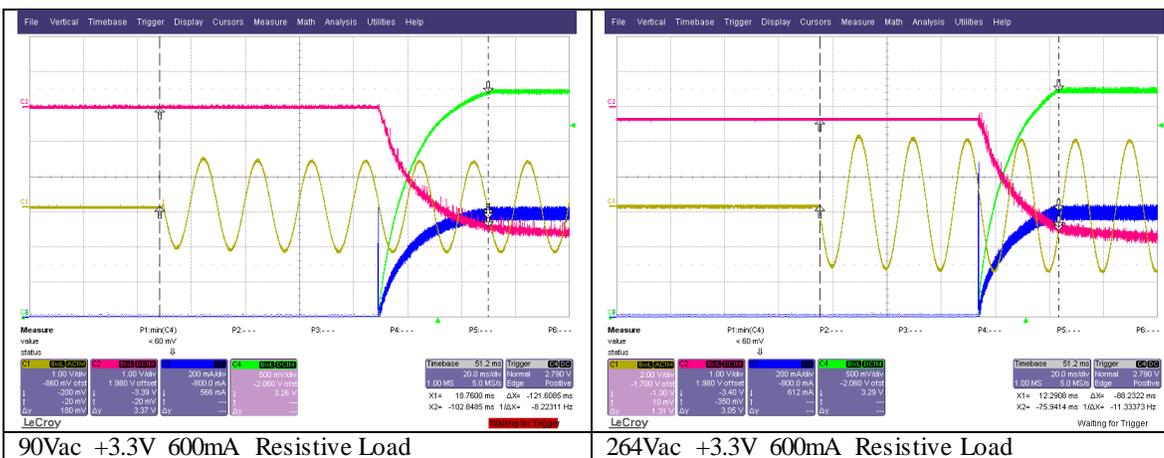

Turn-on Time	<0.5sec	90Vac	120ms
Maximum Overshoot at Turn-on	Within 3.7V for +3.3V rail. Within 6V for -3.3V rail.	3.3V	<4V



7 Agency Approvals

Designs will be designed but not tested for specified agency approvals.

7.1.1 Safety	
EMI	EN61000-4-5, EN61000-4-12
Other	Cispr22 conducted & radiated

8 Conducted EMC

Würth Transformer rev 02

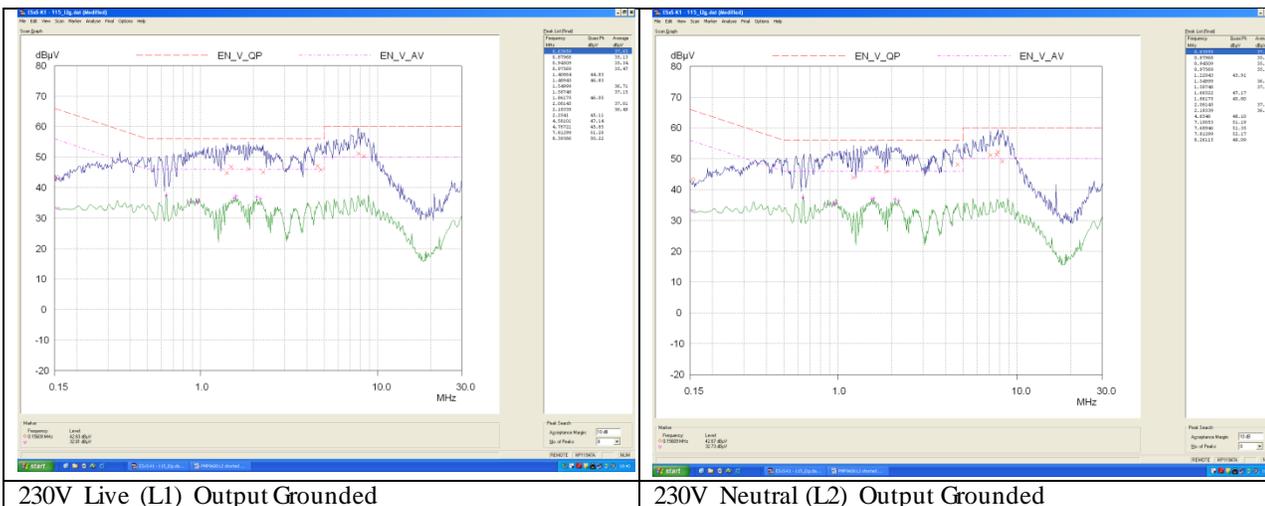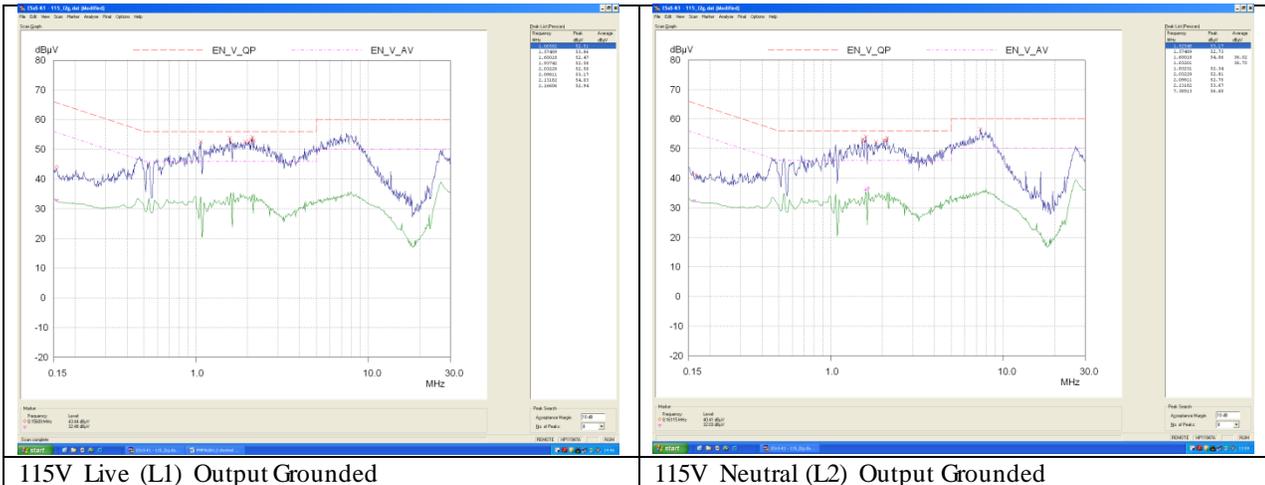

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated