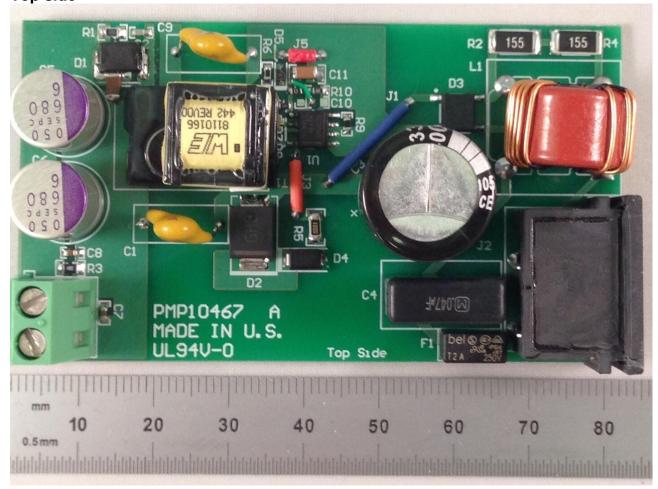


### 1 Photo

The photographs below show the PMP10467 Rev A assembly. This circuit was built on a PMP10467 Rev A PCB.


### Top side




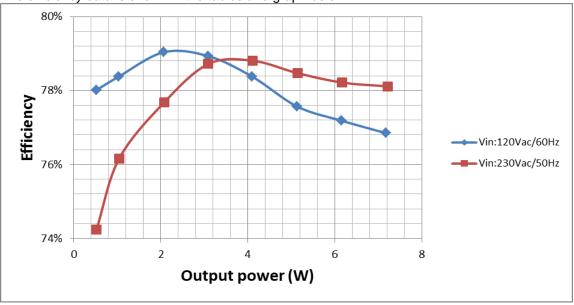
# 2 Converter Efficiency

The efficiency data is shown in the tables and graph below.



# $V_{in}$ =120 $V_{AC}$ /60Hz

Vin(ac)	lin(A)	Pin(W)	Vout(V)	lout(A)	Pout(W)	Eff. (%)
120.10	0.16699	9.331	5.122	1.40	7.171	76.85%
120.11	0.14507	7.968	5.125	1.20	6.150	77.18%
120.16	0.12270	6.611	5.123	1.00	5.128	77.57%
120.18	0.09959	5.227	5.121	0.80	4.097	78.38%
120.20	0.07723	3.916	5.143	0.60	3.091	78.93%
120.24	0.05417	2.620	5.177	0.40	2.071	79.04%
120.27	0.02959	1.320	5.173	0.20	1.035	78.38%
120.27	0.01634	0.671	5.183	0.10	0.523	78.02%
120.28	0.00228	0.022	5.209	0.00	0.000	0.00%

### $V_{in}=230V_{AC}/50Hz$


Vin(ac)	lin(A)	Pin(W)	Vo1(V)	Io1(A)	Pout(W)	Eff. (%)
230.00	0.10322	9.226	5.144	1.40	7.207	78.11%
230.00	0.08993	7.889	5.142	1.20	6.170	78.22%
230.10	0.07623	6.545	5.136	1.00	5.136	78.47%
230.10	0.06235	5.209	5.125	0.80	4.105	78.81%
230.10	0.04873	3.928	5.145	0.60	3.092	78.72%
230.10	0.03469	2.668	5.181	0.40	2.072	77.68%
230.10	0.01944	1.363	5.190	0.20	1.038	76.16%
230.10	0.01125	0.700	5.199	0.10	0.520	74.24%
230.10	0.00333	0.035	5.216	0.00	0.000	0.00%



# 3 Thermal Images

The thermal images below show a top view and bottom view of the board. The ambient temperature was  $20^{\circ}$ C with no forced air flow. The output was at full load: 5V/1.4A.


### 3.1 $V_{in}=120V_{AC}/60Hz$

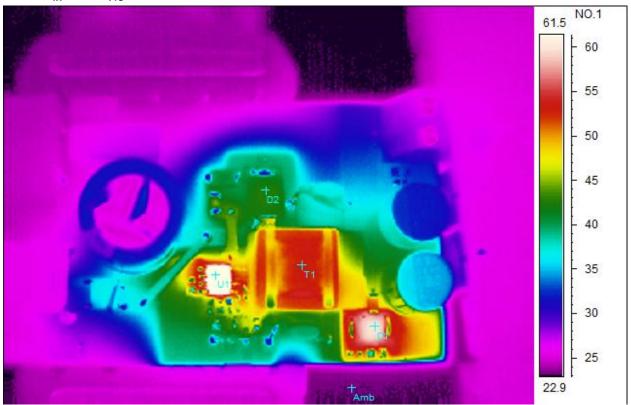

Spot analysis	Value
U1Temperature	73.4°C
T1Temperature	53.8°C
D1Temperature	60.4°C
D2Temperature	43.6°C
Amb Temperature	23.3°C


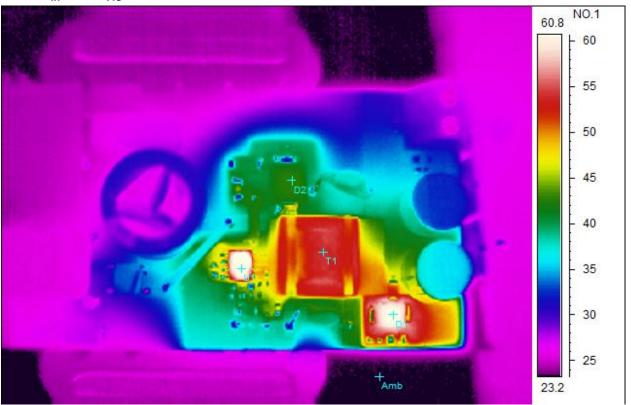
# 3.2 V<sub>in</sub>=230V<sub>AC</sub>/50Hz



Spot analysis	Value
U1Temperature	62.6°C
T1Temperature	54.7°C
D1Temperature	61.2°C
D2Temperature	43.6°C
Amb Temperature	23.2°C




# 4 Startup

The output voltages at startup are shown in the images below.

### 4.1 Start Up @ 120V<sub>AC</sub>/60Hz: 5V/1.4A.



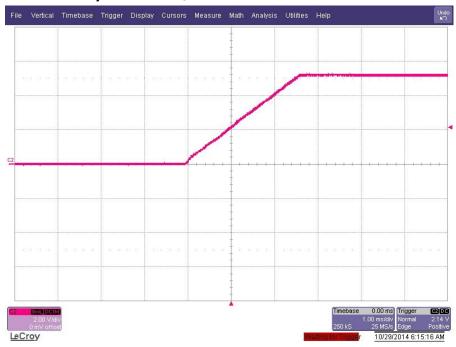
### 4.2 Start Up @ 120 V<sub>AC</sub> /60Hz: no load.





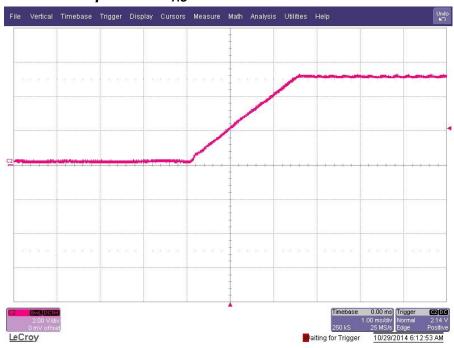
# 4.3 Start Up @ 230 V<sub>AC</sub> /50Hz: 5V/1.4A.


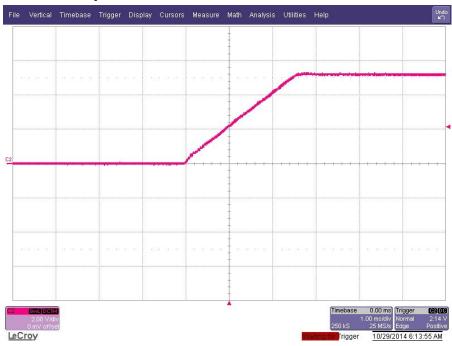
### 4.4 Start Up @ 230 V<sub>AC</sub> /50Hz: no load.






# 5 Output Ripple Voltages

The output ripple voltages are shown in the plots below.

### 5.1 120 V<sub>AC</sub> /60Hz - 5V/1.4A


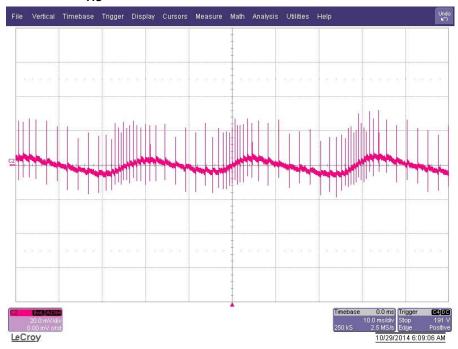
### 5.2 $120 V_{AC} / 60 Hz - 5 V / No load$






# $5.3 \quad 230 \ V_{AC} / 50 Hz - 5 V / 1.4 A$



### 5.4 230 $V_{AC}$ /50Hz - 5V/ No load

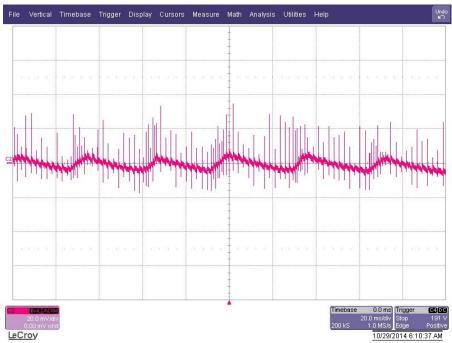



# 6 Load Transient

The image below shows  $5V_{out}$  voltage response to a **0.7A** to **1.4A** load transient at a  $120V_{AC}/60Hz$  input.






# 7 Switching Waveforms

The images below show key switching waveforms of PMP10467RevA. The waveforms are measured with 5V/1.4A full load.

### 7.1 Primary MOSFET U1 pin8 @ 85 V<sub>AC</sub> /60Hz


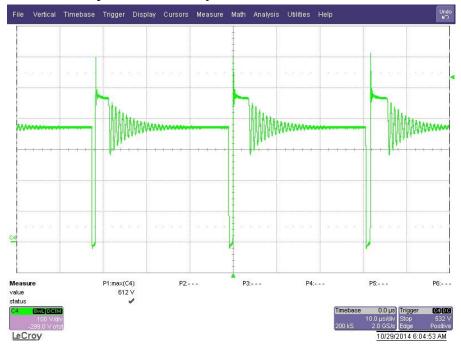
### 7.2 Primary MOSFET U1 pin8 @ 265 V<sub>AC</sub> /50Hz



#### IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (https://www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2021, Texas Instruments Incorporated