

# PMP4497 Test Results

# 1 General

#### 1.1 PURPOSE

This report provides the detailed data and waveforms for evaluating and verifying the PMP4497. The PMP4497 is the 48V to 1.0V/40A DC-DC converter with the GaN module LMG5200 and the D-Cap+ controller TPS53632. It delivers up to 1.0V/40A output power. The converter could provide high efficiency with the good performance, which makes it an ideal choice for computer & server, FPGA and ASIC power supply. For testing applications, cooling airflow is required.

### 1.3 TEST EQUIPMENTS


Multi-meter: Fluke Multimeter 287C, Agilent 34401A

DC Source: TDK-Lambda


Oscilloscope: WaveSurfer 104Mxs-B

1.4 Testing Setup Photos

#### **Testing Setup**

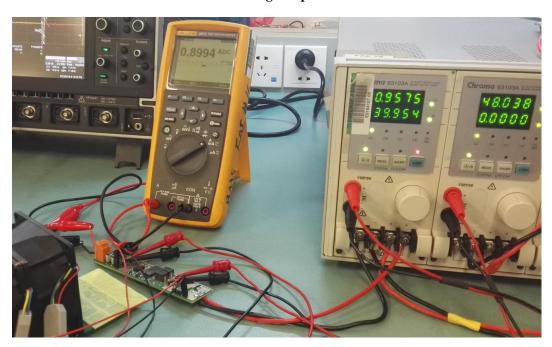

Top View of the Board

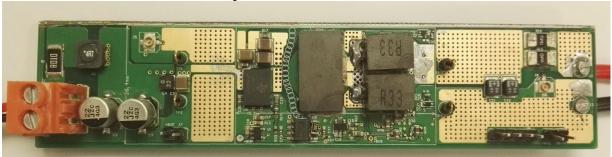




# 2 INPUT & Output CHARACTERISTICS 2.1: Efficiency vs Output Current 1.0V/40A Output Efficiency, @600kHz, without Controller Loss


Vin (V)	lin (A)	Vout (V)	lout (A)	Eff. (%)
36V Input				
36.249	0.0119	1.001	0.0	0.4(W)
36.240	0.0391	1.001	1.0	70.7%
36.221	0.1511	1.001	5.0	91.5%
36.190	0.2949	1.001	10.0	93.8%
36.160	0.4430	1.001	15.0	93.8%
36.131	0.5942	1.000	20.0	93.2%
36.099	0.7499	0.999	25.0	92.2%
36.071	0.9097	0.999	30.0	91.3%
36.036	1.0718	0.999	35.0	90.5%
36.000	1.2391	0.999	40.0	89.6%
48V Input				
48.183	0.0138	1.001	0.0	0.7(W)
48.175	0.0340	1.001	1.0	61.1%
48.159	0.1180	1.001	5.0	88.1%
48.140	0.2253	1.001	10.0	92.3%
48.115	0.3359	1.001	15.0	92.9%
48.094	0.4486	1.000	20.0	92.7%
48.069	0.5638	0.999	25.0	92.1%
48.045	0.6821	0.999	30.0	91.4%
48.024	0.8028	0.999	35.0	90.7%
47.998	0.9255	0.999	40.0	89.9%
60V Input				
60.034	0.0154	1.001	0.0	0.9(W)
60.033	0.0317	1.001	1.0	52.6%
60.016	0.0987	1.001	5.0	84.5%
60.003	0.1844	1.001	10.0	90.5%
59.983	0.2729	1.001	15.0	91.8%
59.963	0.3629	1.000	20.0	91.9%
59.948	0.4547	0.999	25.0	91.6%
59.931	0.5487	0.999	30.0	91.1%
59.906	0.6442	0.999	35.0	90.6%
59.886	0.7421	0.999	40.0	89.9%


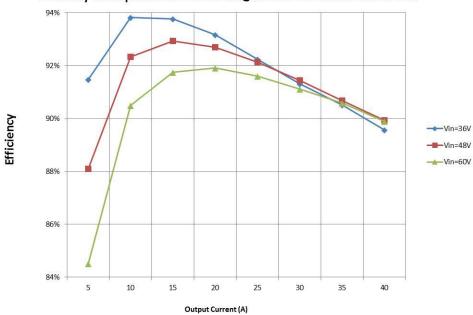
### Efficiency vs Output Current LMG5200@600kHz without Controller Loss



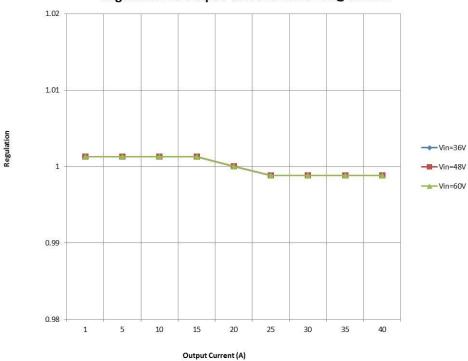
# Regulation vs Output Current LMG5200@600kHz





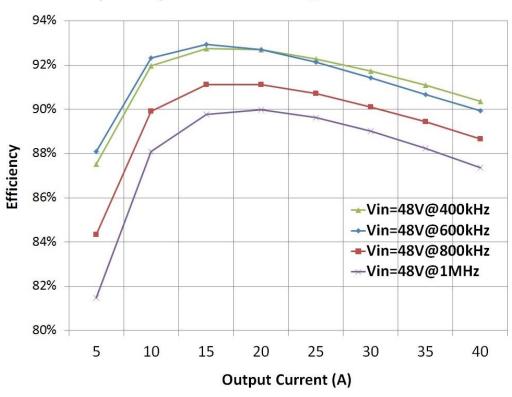
# **Efficiency Curve without Controller Loss vs. Frequency**

Efficiency vs. Output Current LMG5200@Vin=48V without controller loss



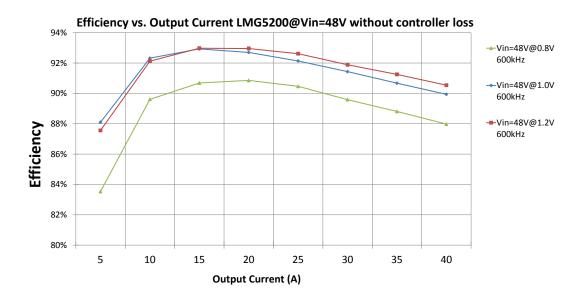
# Efficiency Curve without Controller Loss vs. Output Voltage





# **Efficiency Curve with Controller Loss vs. Output Current**
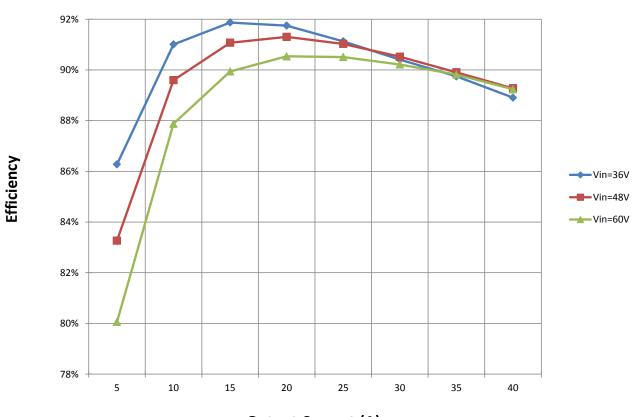
# Efficiency vs. Output Current LMG5200@600kHz With Controller Loss




**Output Current (A)** 



# 2.2: Start Up & Shut Down Waveforms


### 48V Input with Full Load & No Load

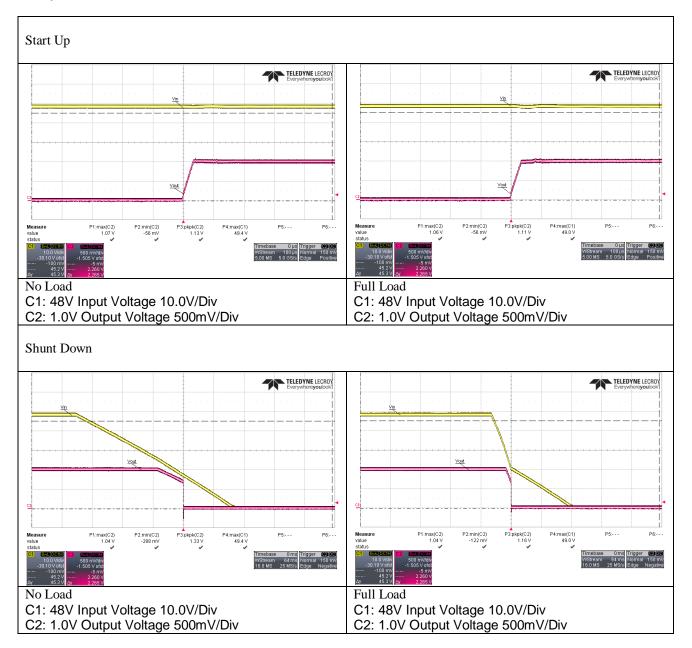




# 2.3: Output Ripple & Noise



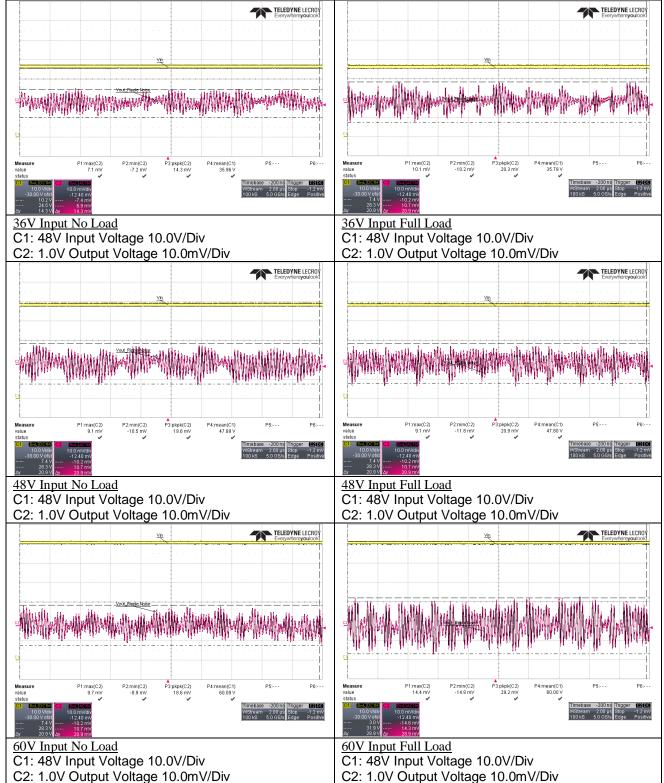




# 2.4: Dynamic Load Waveforms

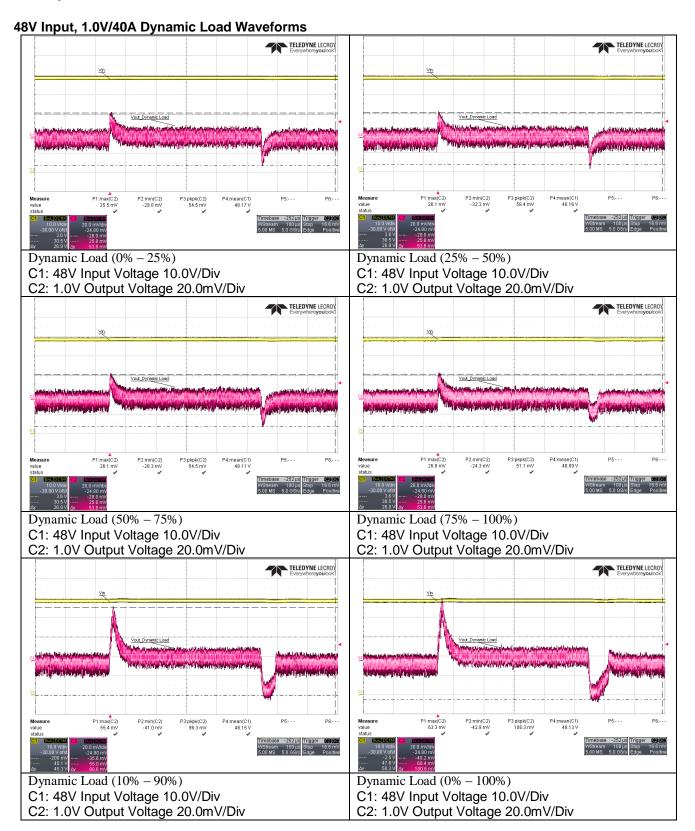



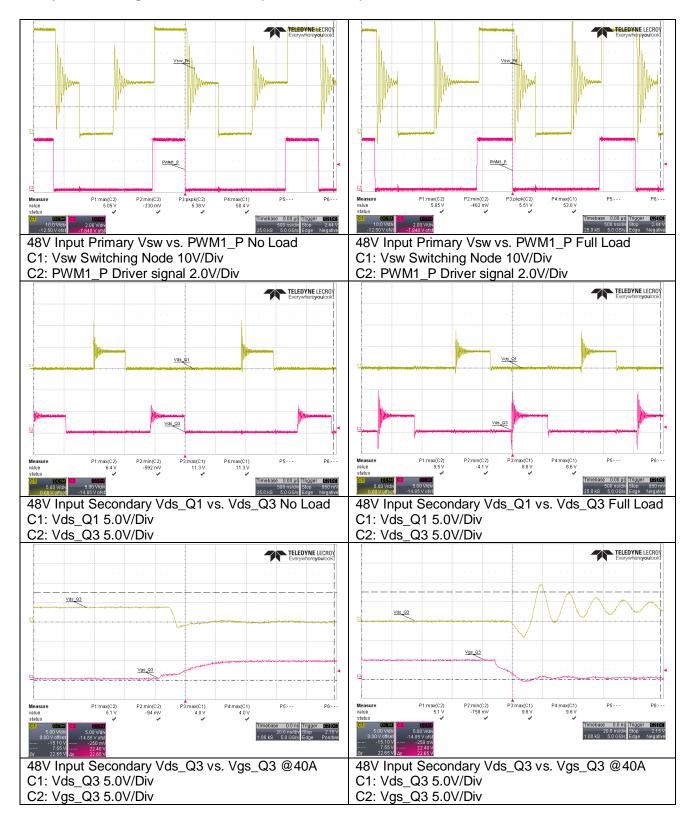
## 48V Input, Switching Node Waveforms (Full Bandwidth)






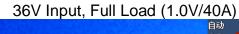
# 3 IR Scan Thermal Gradient (With Fan Cooling, $\approx$ 1m/s)





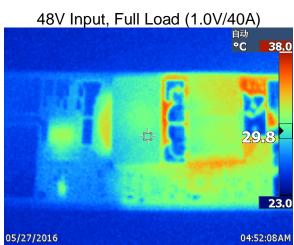

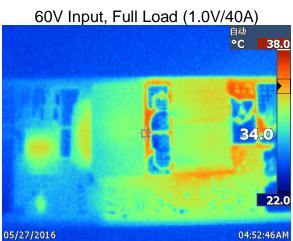

### IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (https://www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2021, Texas Instruments Incorporated