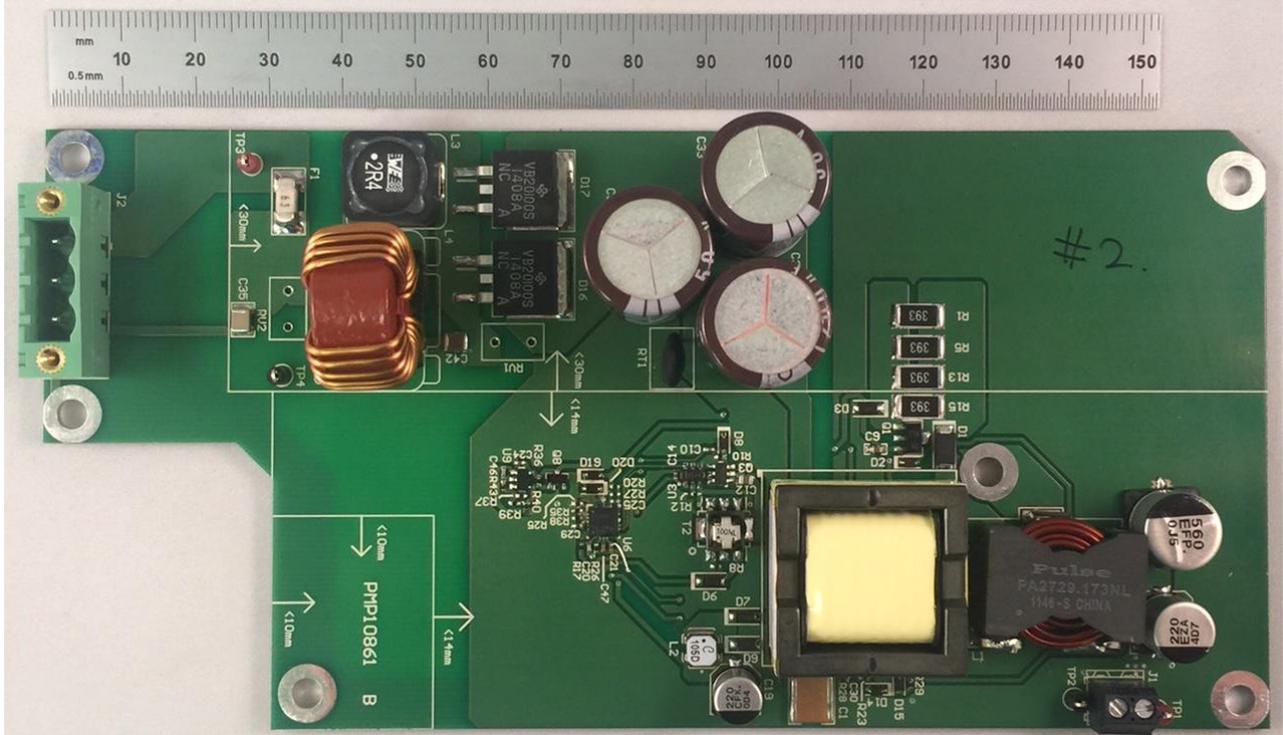



1 Photo

The photographs below show the PMP10861 Rev B assembly. This circuit was built on a PMP10861 Rev B PCB.

Top side




Bottom side

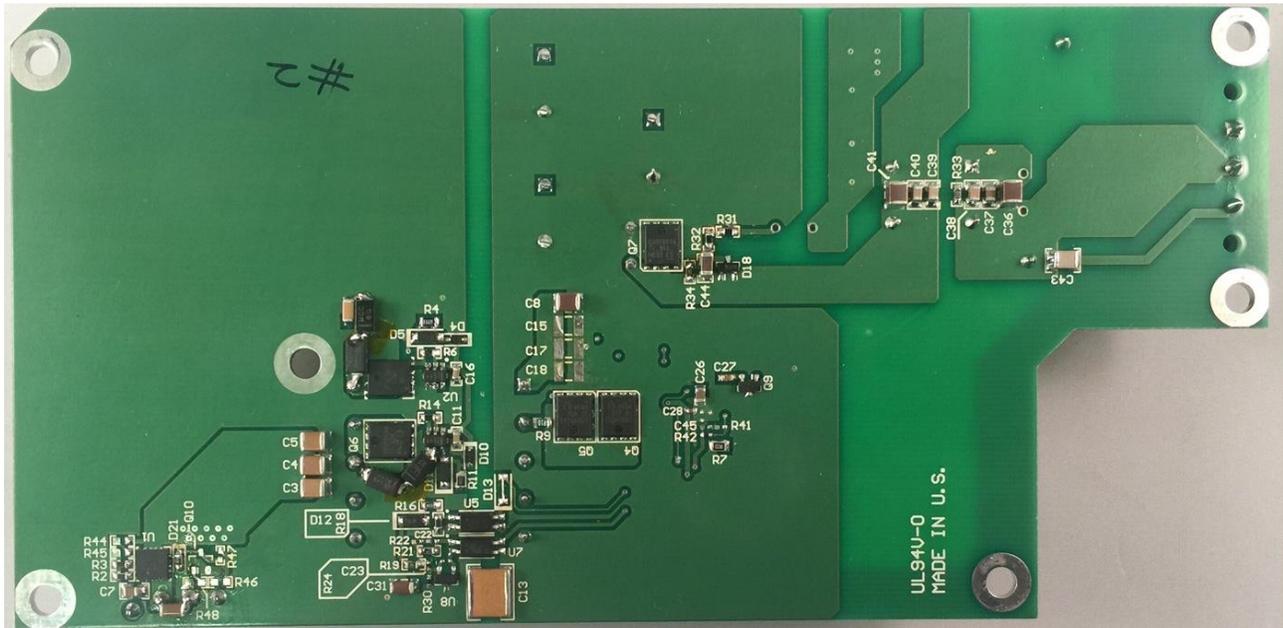

2 Converter Efficiency

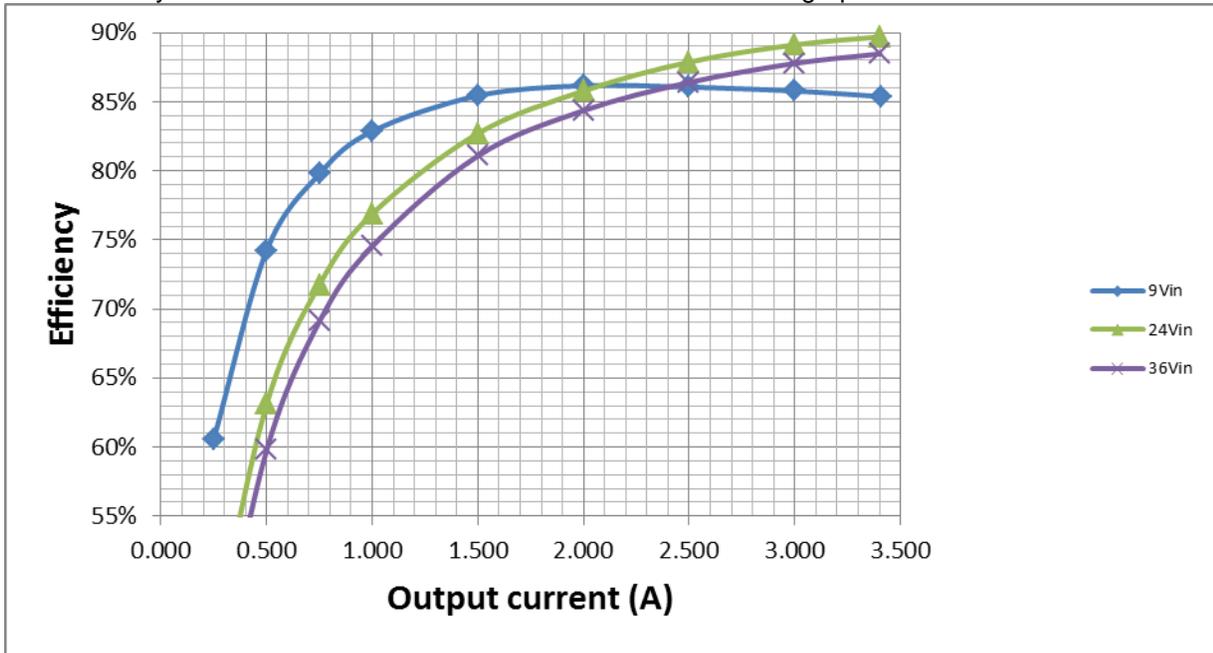The efficiency data of PMP10861Rev B was tested as shown in the graph and tables below.



9V_{in}

V _{in} (V)	I _{in} (A)	P _{in} (W)	V _{out} (V)	I _{out} (A)	P _{out} (W)	Eff. (%)
9.04	5.231	47.288	11.84	3.410	40.374	85.38%
9.04	4.586	41.457	11.85	3.001	35.562	85.78%
9.04	3.813	34.470	11.87	2.499	29.663	86.06%
9.04	3.053	27.599	11.89	2.000	23.780	86.16%
9.04	2.313	20.910	11.91	1.500	17.865	85.44%
9.04	1.594	14.410	11.93	1.001	11.942	82.87%
9.03	1.243	11.224	11.94	0.750	8.955	79.78%
9.03	0.89	8.037	11.95	0.499	5.963	74.20%
9.03	0.545	4.921	11.96	0.249	2.978	60.51%
9.03	0.206	1.860	11.97	0.000	0.000	0.00%

24V_{in}

Vin(V)	Iin(A)	Pin(W)	Vo1(V)	Io1(A)	Pout(W)	Eff. (%)
24.02	1.871	44.941	11.84	3.405	40.315	89.71%
24.02	1.662	39.921	11.86	3.000	35.580	89.13%
24.02	1.407	33.796	11.88	2.500	29.700	87.88%
24.02	1.155	27.743	11.9	2.000	23.800	85.79%
24.02	0.9	21.618	11.92	1.500	17.880	82.71%
24.02	0.647	15.541	11.94	1.001	11.952	76.91%
24.02	0.52	12.490	11.95	0.750	8.963	71.76%
24.02	0.395	9.488	11.96	0.501	5.992	63.15%
24.02	0.27	6.485	11.97	0.249	2.981	45.96%
24.02	0.147	3.531	11.98	0.000	0.000	0.00%


36V_{in}

Vin(V)	Iin(A)	Pin(W)	Vo1(V)	Io1(A)	Pout(W)	Eff. (%)
36.03	1.264	45.542	11.84	3.403	40.292	88.47%
36.03	1.125	40.534	11.86	3.000	35.580	87.78%
36.03	0.954	34.373	11.88	2.500	29.700	86.41%
36.03	0.783	28.211	11.9	2.000	23.800	84.36%
36.03	0.612	22.050	11.92	1.500	17.880	81.09%
36.03	0.445	16.033	11.94	1.001	11.952	74.54%
36.03	0.36	12.971	11.95	0.750	8.963	69.10%
36.03	0.278	10.016	11.96	0.501	5.992	59.82%
36.03	0.196	7.062	11.97	0.251	3.004	42.54%
36.03	0.113	4.071	11.98	0.000	0.000	0.00%

3 Thermal Images


The thermal images below show a top view and bottom view of the board at 24V input. The ambient temperature was 20°C with no forced air flow. The output was loaded with 12V/3.4A.

Top Side

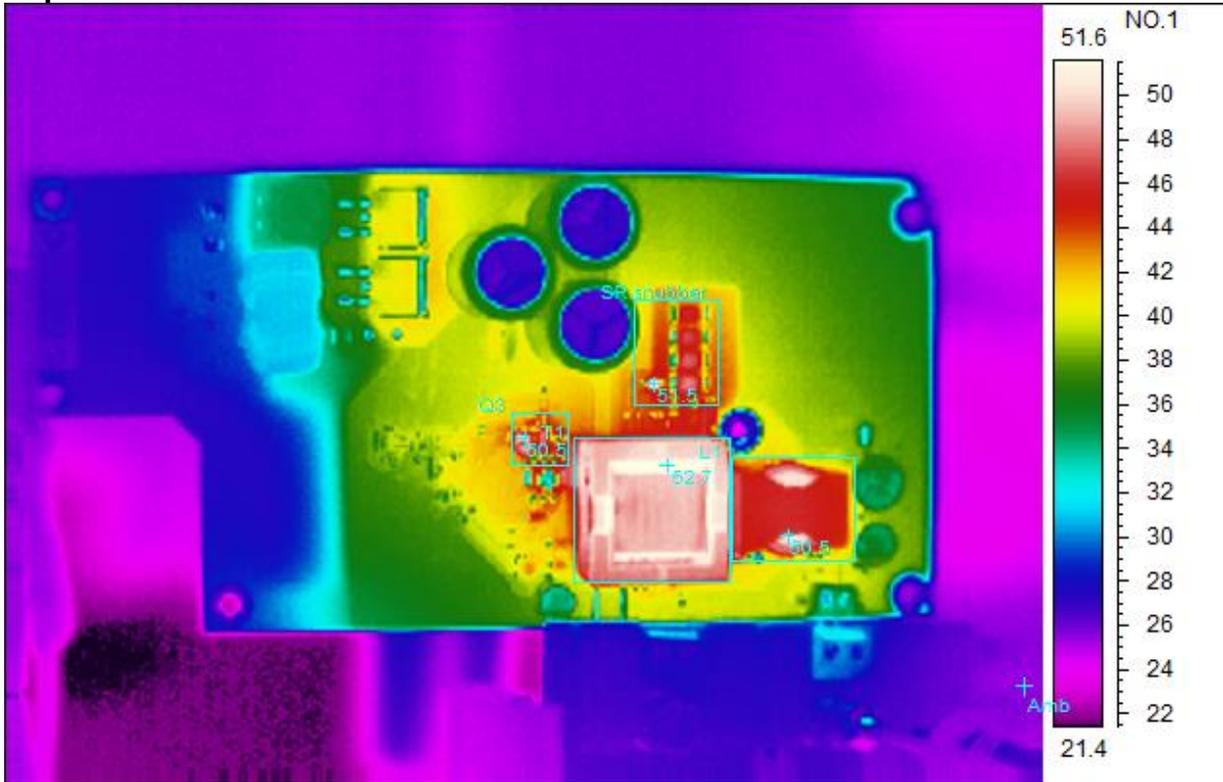

Spot analysis	Value
Amb Temperature	25.8°C
Area analysis	Value
T1Max	52.7°C
L1Max	50.5°C
Q3Max	50.5°C
SR snubberMax	51.5°C

Bottom Side

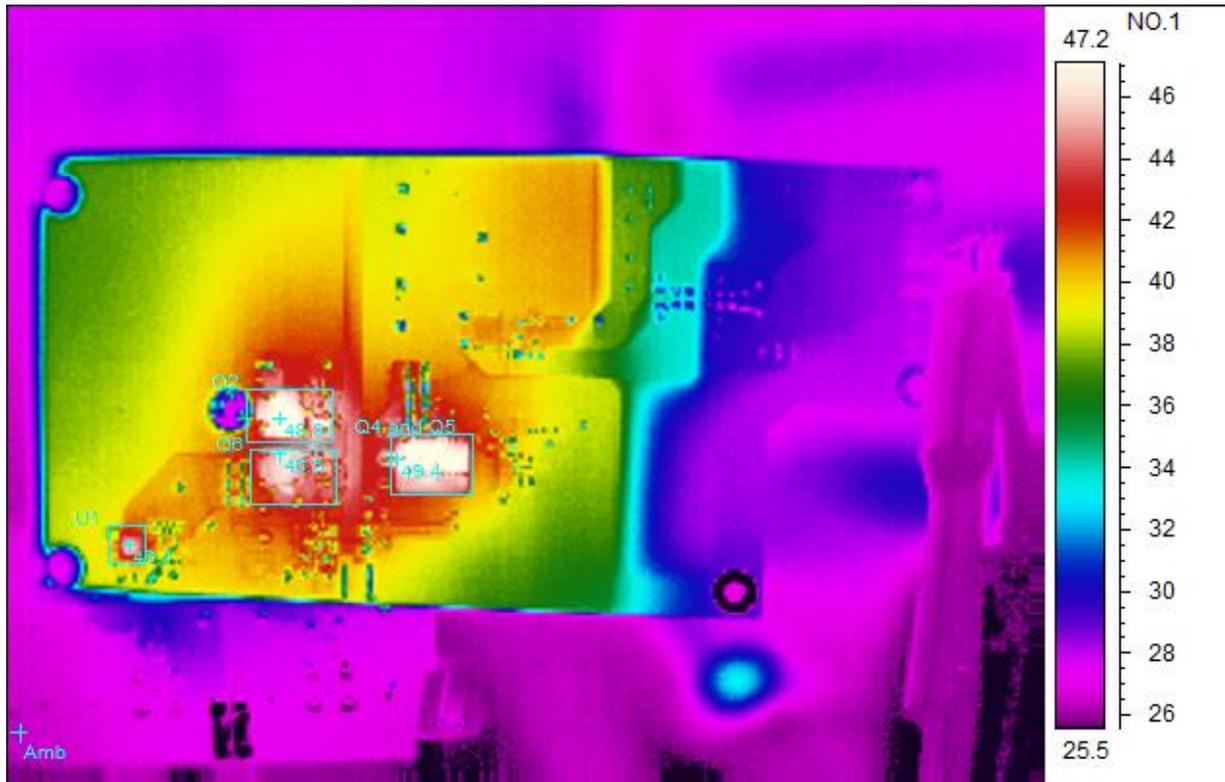


Spot analysis	Value
Amb Temperature	26.5°C
Area analysis	Value
Q2Max	48.9°C
Q6Max	46.5°C
Q4 and Q5Max	49.4°C
U1Max	46.1°C

4 Startup


The output voltages at startup are shown in the images below.

4.1 Full load startup @ 9V_{in}, 12V_{out}/3.4Ω load.

CH1: V_{in}, CH4: V_{out}

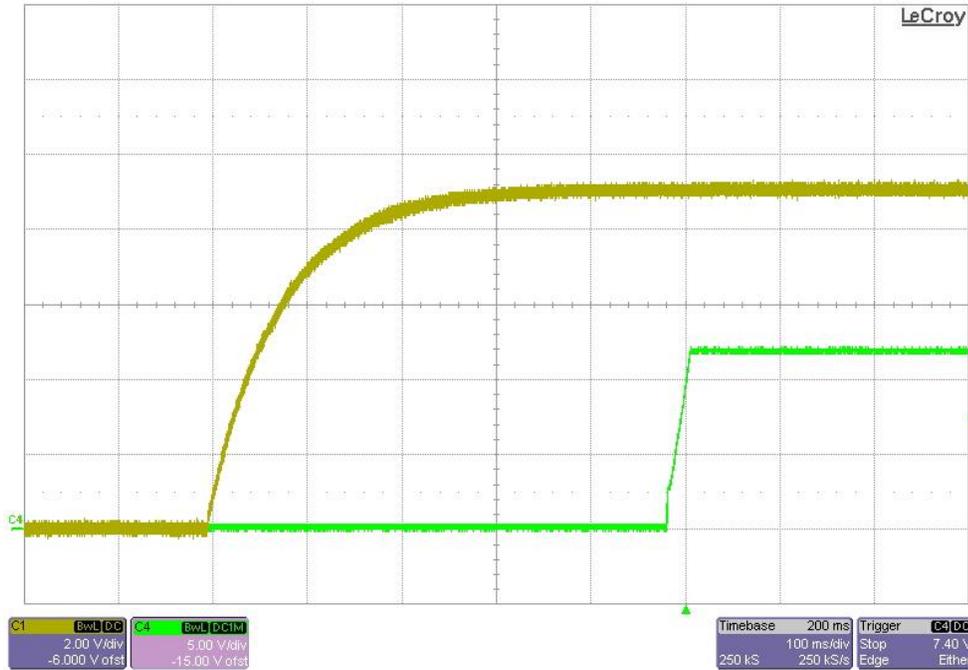


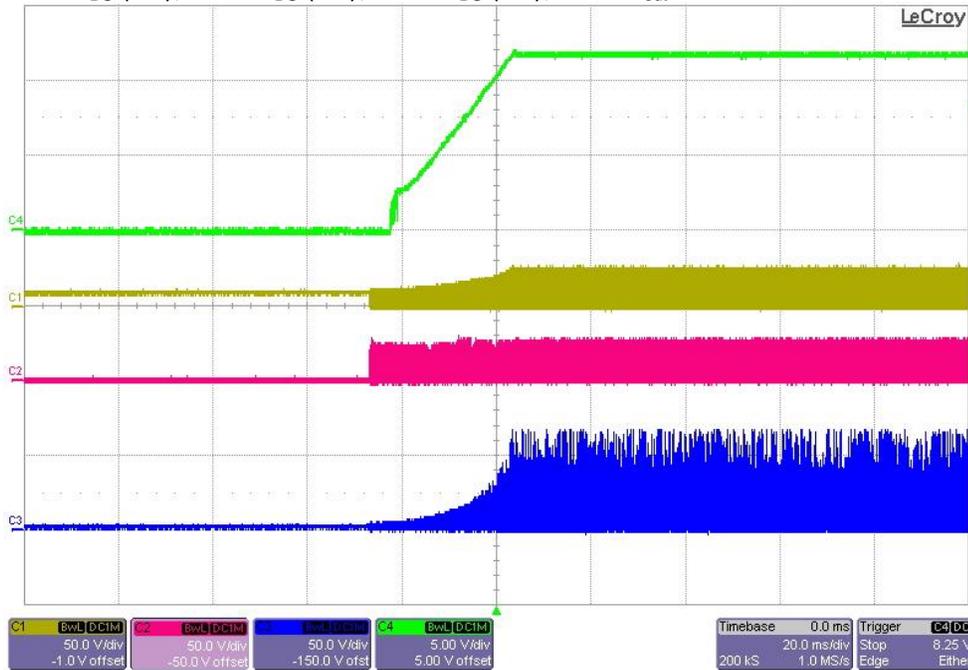CH1: V_{DS} (Q4), CH2: V_{DS} (Q2), CH3: V_{DS} (Q6), CH4: V_{out}



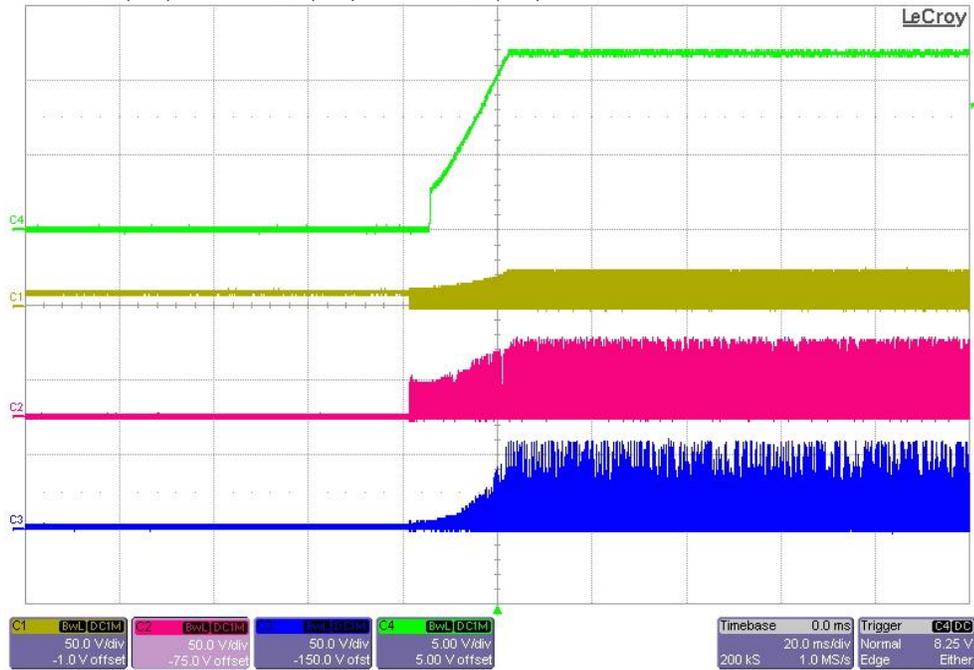
4.2 No load startup @ 9V_{in}, 12V_{out}/0A.

CH1: V_{DS} (Q4), CH2: V_{DS} (Q2), CH3: V_{DS} (Q6), CH4: V_{out}




4.3 Full load startup @ 24V_{in}, 12V_{out}/3.4Ω load.

CH1: V_{in}, CH4: V_{out}

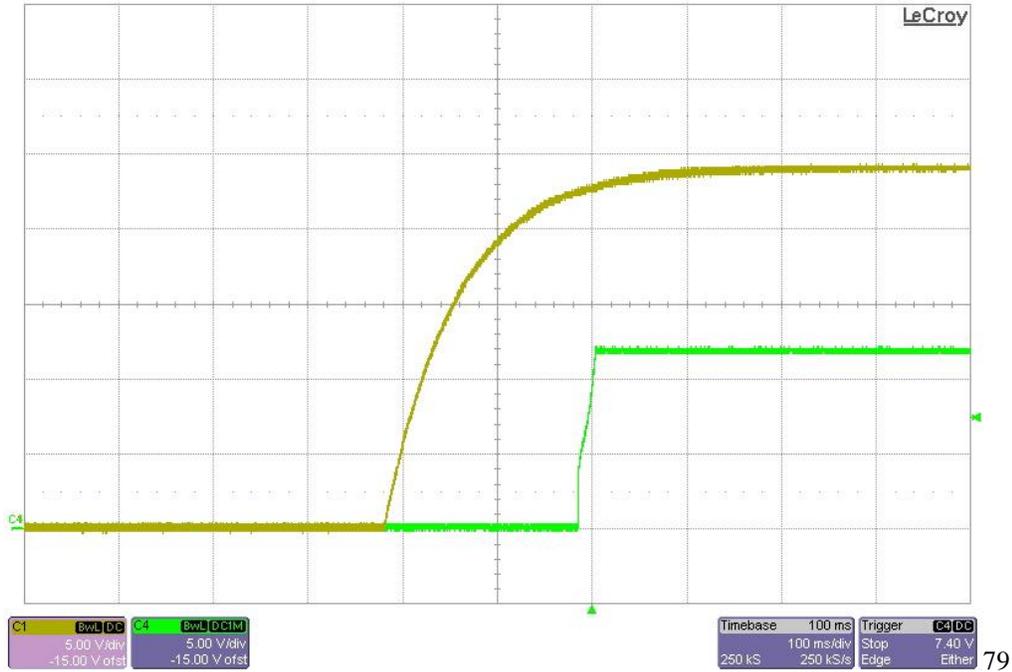


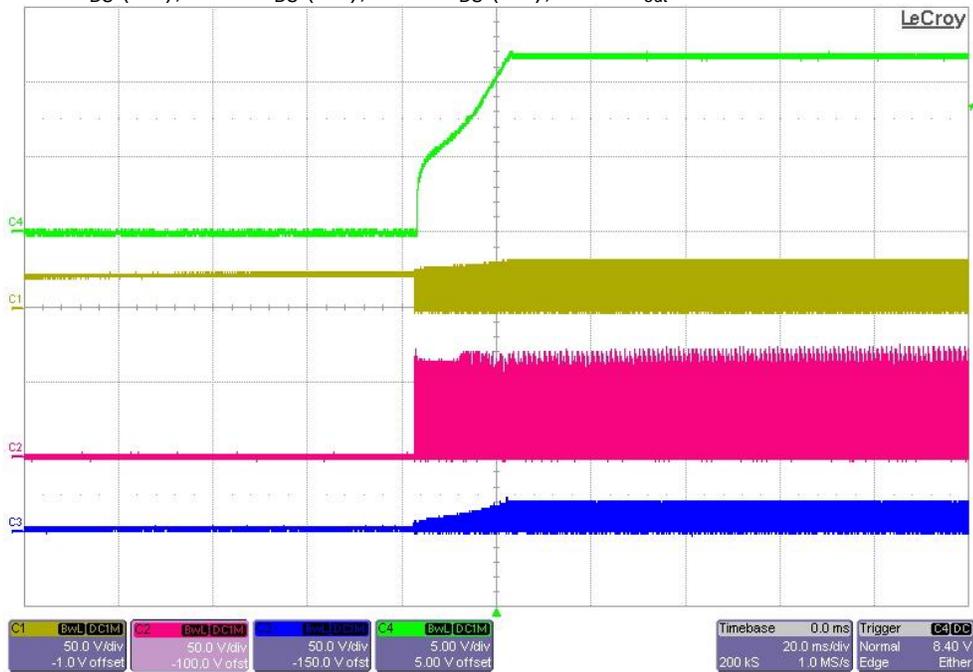CH1: V_{DS} (Q4), CH2: V_{DS} (Q2), CH3: V_{DS} (Q6), CH4: V_{out}



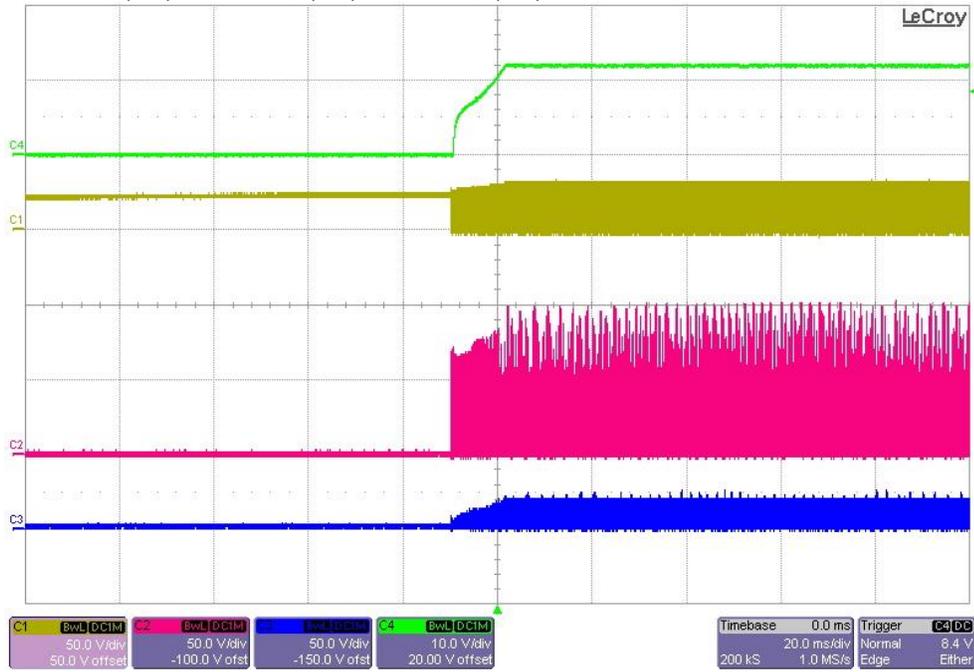
4.4 No load startup @ 24V_{in}, 12V_{out}/0A.

CH1: V_{DS} (Q4), CH2: V_{DS} (Q2), CH3: V_{DS} (Q6), CH4: V_{out}




4.5 Full load startup @ 36V_{in}, 12V_{out}/3.4Ω load.

CH1: V_{in}, CH4: V_{out}

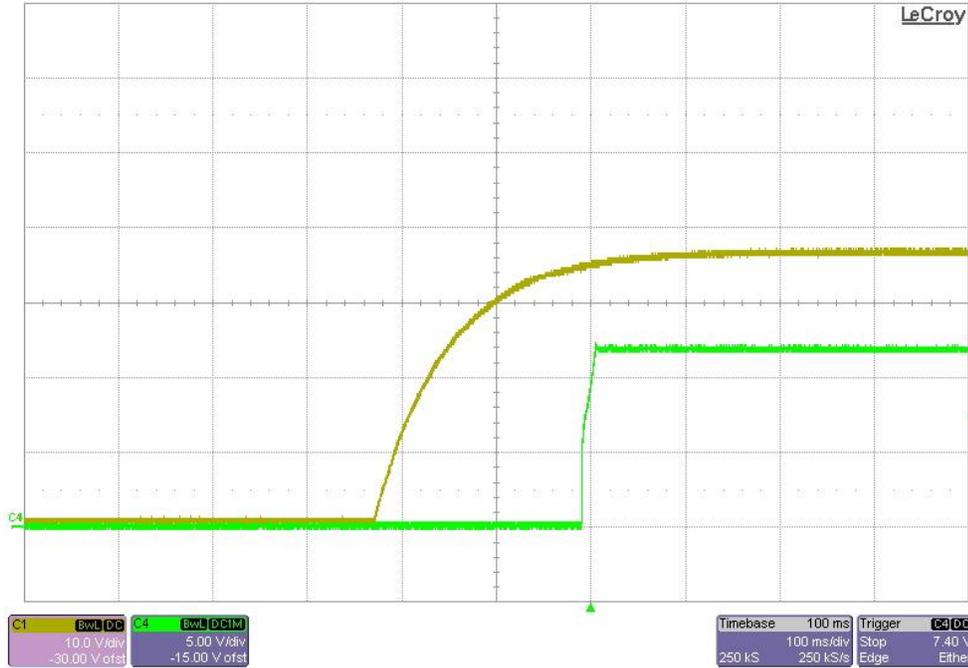


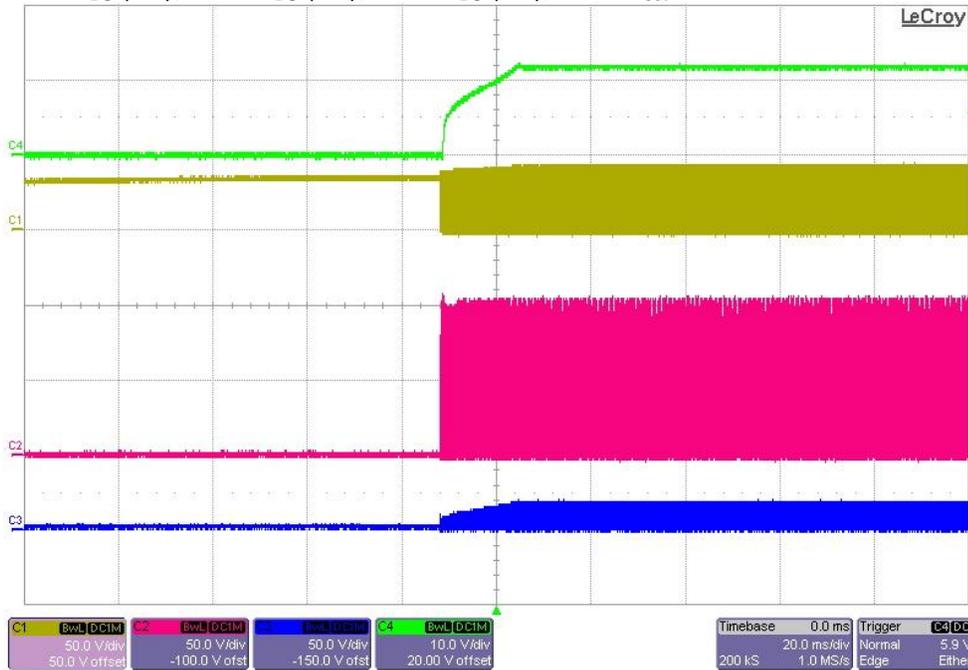CH1: V_{DS} (Q4), CH2: V_{DS} (Q2), CH3: V_{DS} (Q6), CH4: V_{out}



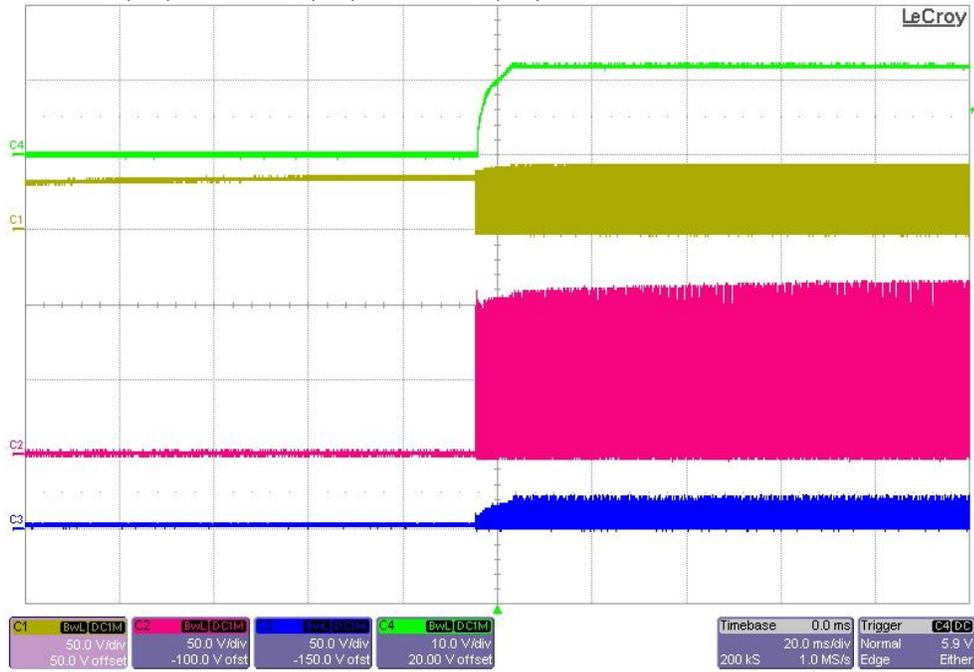4.6 No load startup @ 36V_{in}, 12V_{out}/0A.

CH1: V_{DS} (Q4), CH2: V_{DS} (Q2), CH3: V_{DS} (Q6), CH4: V_{out}




5 Turn-off

The output voltages at turn-off with 3.4Ω load resistor are shown in the images below.

5.1 9V_{in}

CH1: V_{in}, CH4: V_{out}

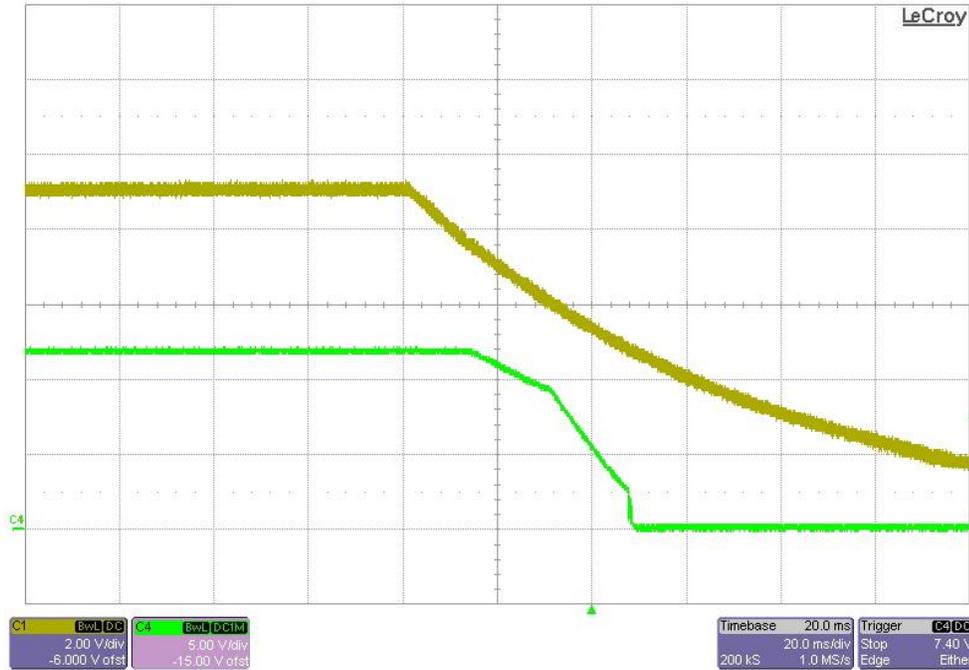


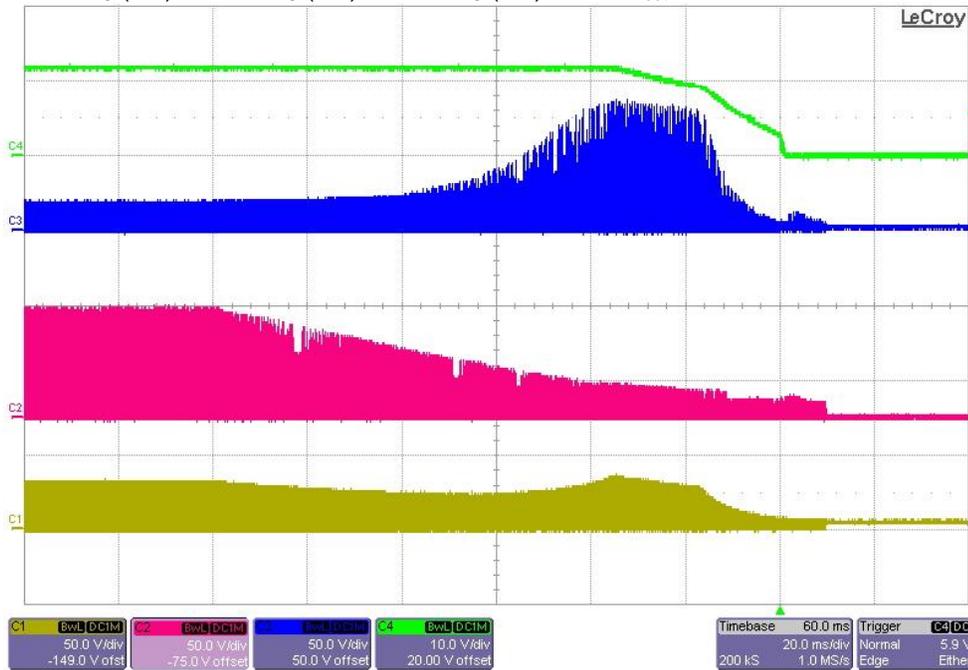5.2 24V_{in}

CH1: V_{in}, CH4: V_{out}




CH1: V_{DS} (Q4), CH2: V_{DS} (Q2), CH3: V_{DS} (Q6), CH4: V_{out}




5.3 36V_{in}

CH1: V_{in}, CH4: V_{out}

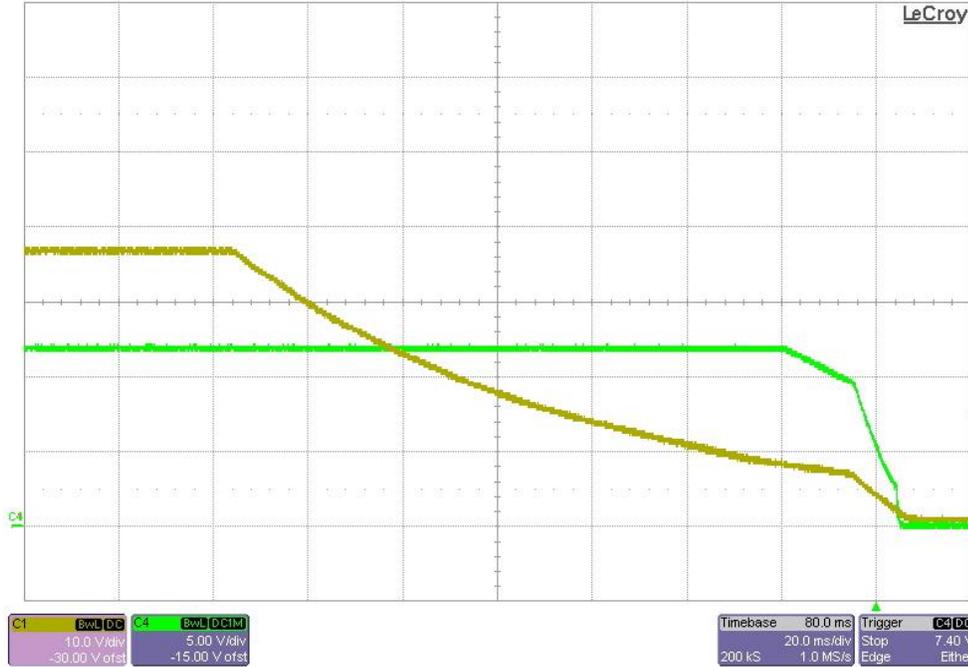

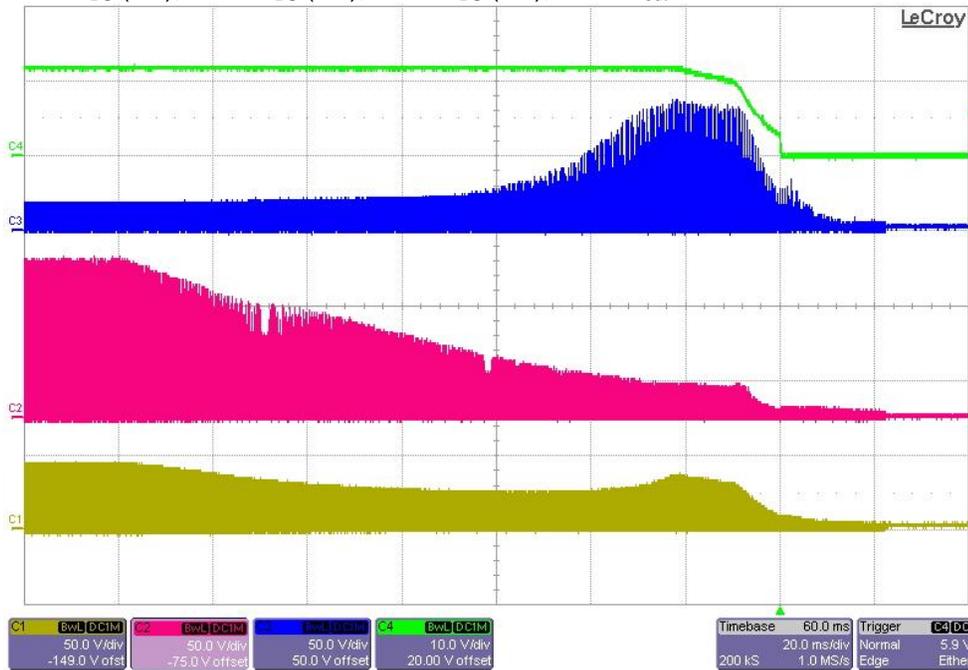
CH1: V_{DS} (Q4), CH2: V_{DS} (Q2), CH3: V_{DS} (Q6), CH4: V_{out}




6 Output Ripple Voltages

The output ripple voltages are shown in the plots below with 3.4A full load. Waveforms are measured with 200MHz full oscilloscope bandwidth.


6.1 9V_{in}

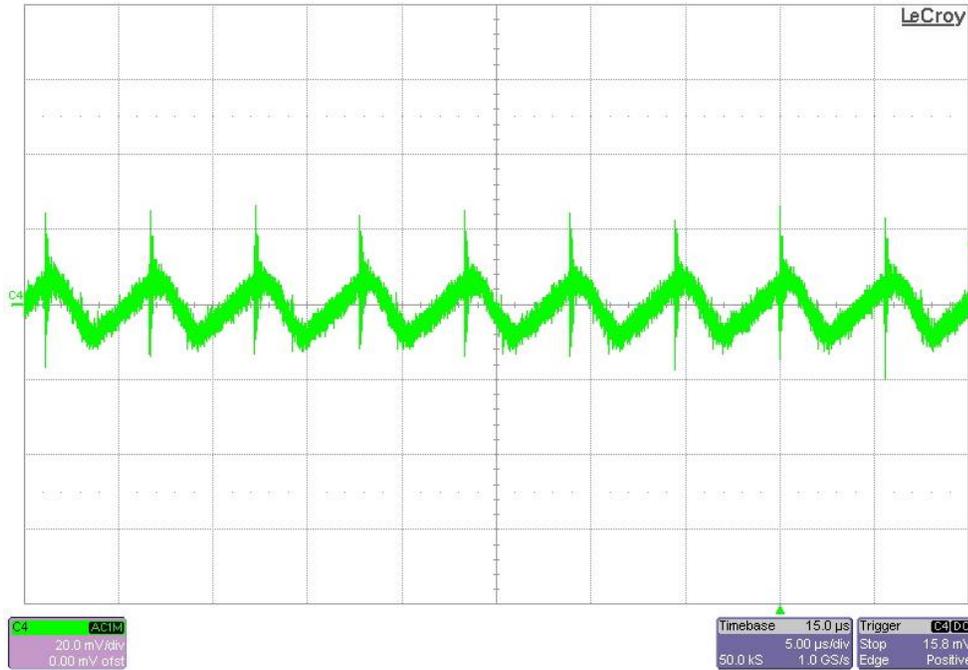

6.2 24V_{in}

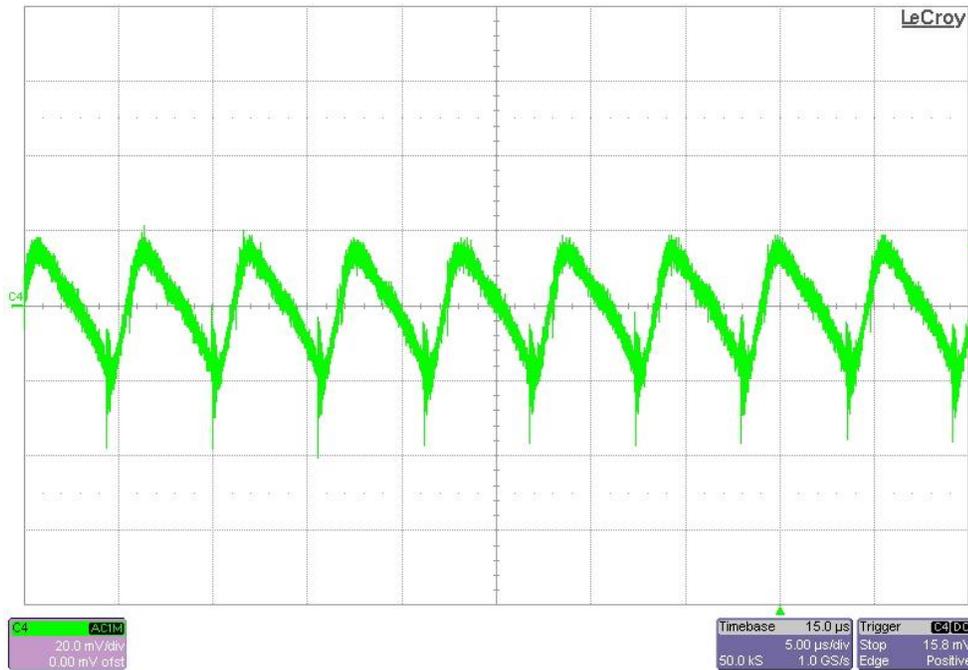

6.3 36V_{in}

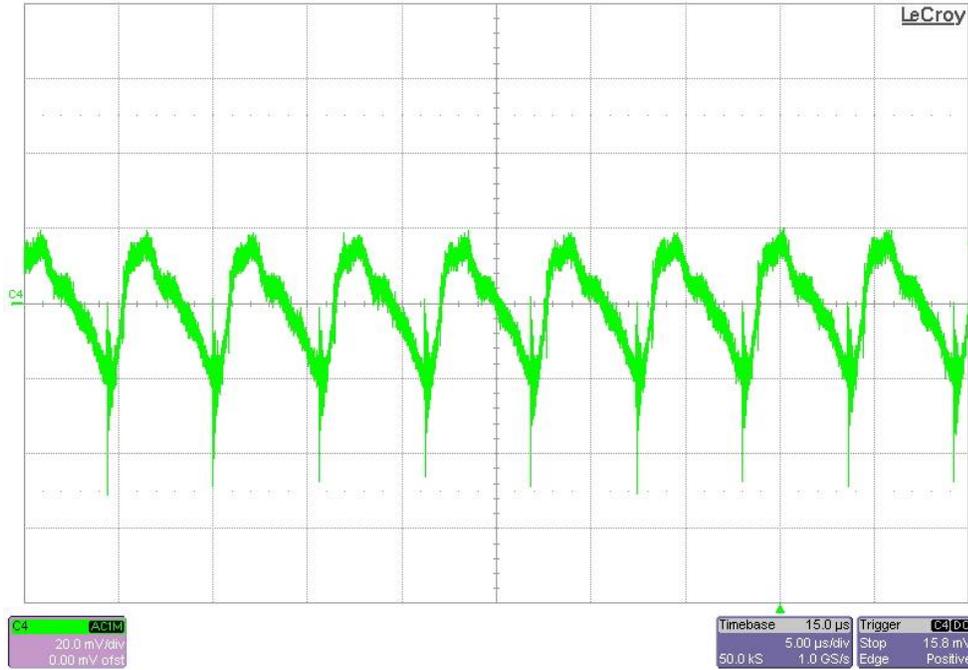


7 Frequency Response

The image below shows the frequency responses under different input/output conditions.

7.1 9V_{in}

Curve 1 is measured at 3.4A load.


Curve 2 is measured at no load.

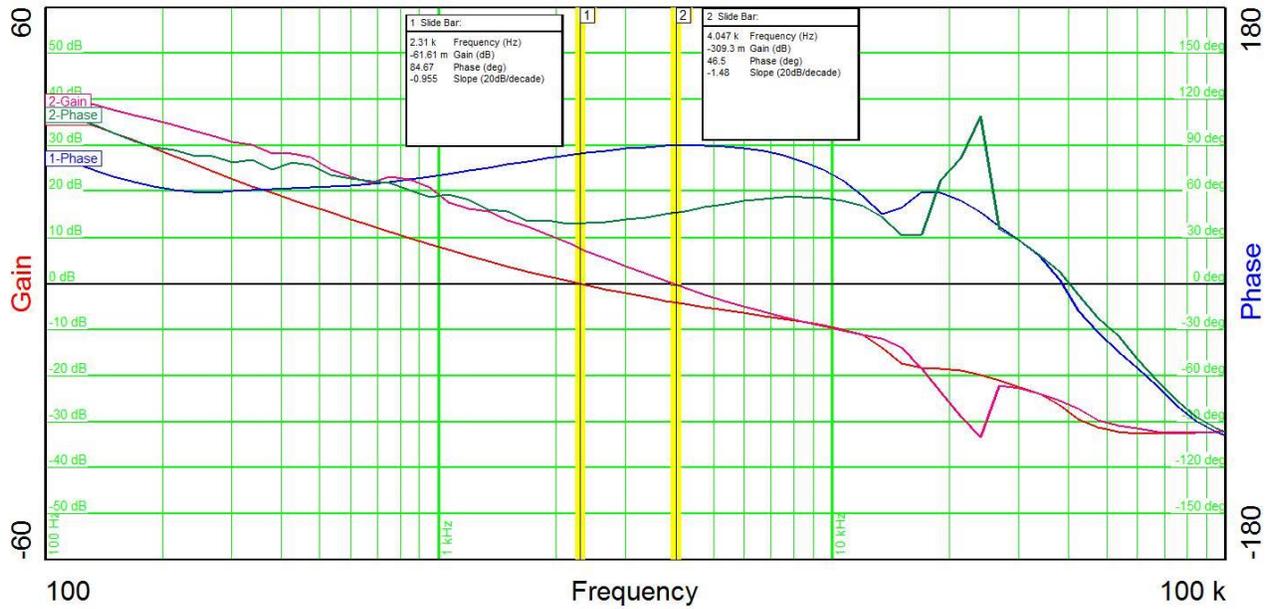

7.2 24V_{in}

Curve 1 is measured at 3.4A load.


Curve 2 is measured at no load.

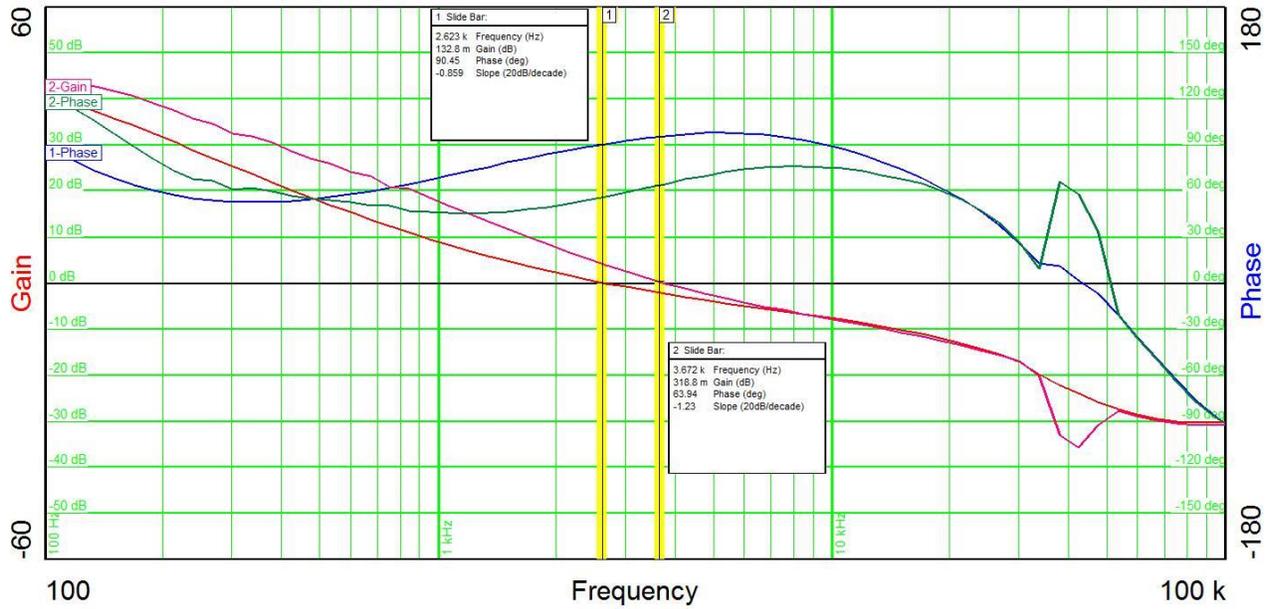

7.3 36V_{in}

Curve 1 is measured at 3.4A load.


Curve 2 is measured at no load.

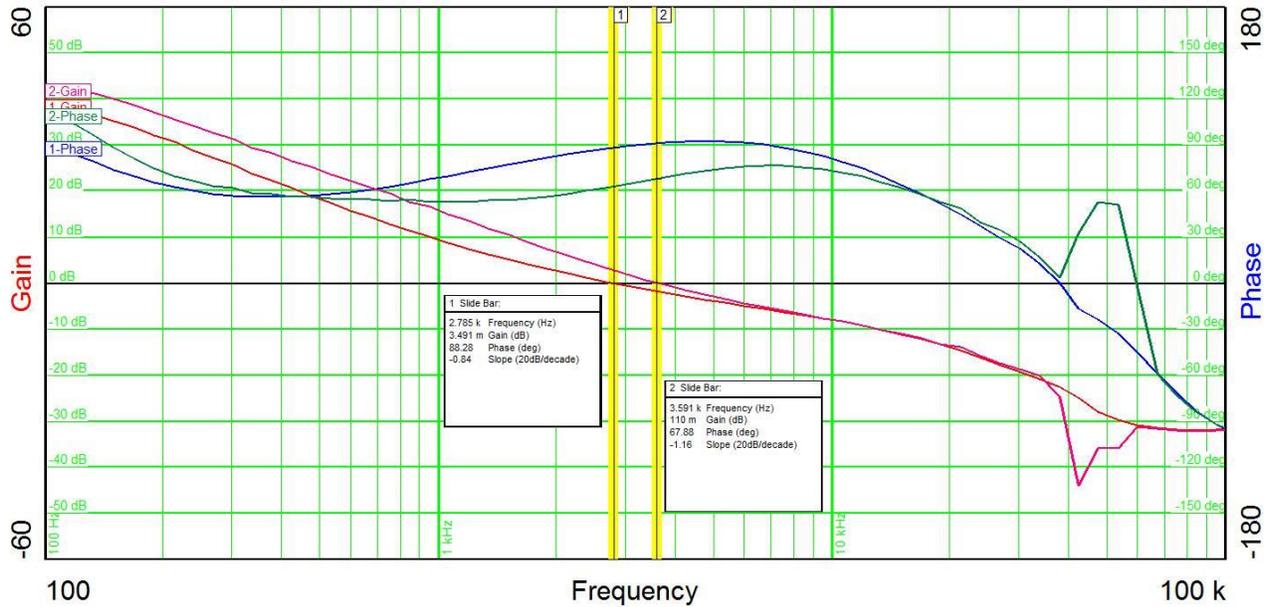

8 Dynamic Load Response

The image below shows the dynamic load response on 12V_{out} at 24V_{in}. Load step is from 0A to 3.4A.


CH3: I_{out}, CH4: V_{out}(AC)

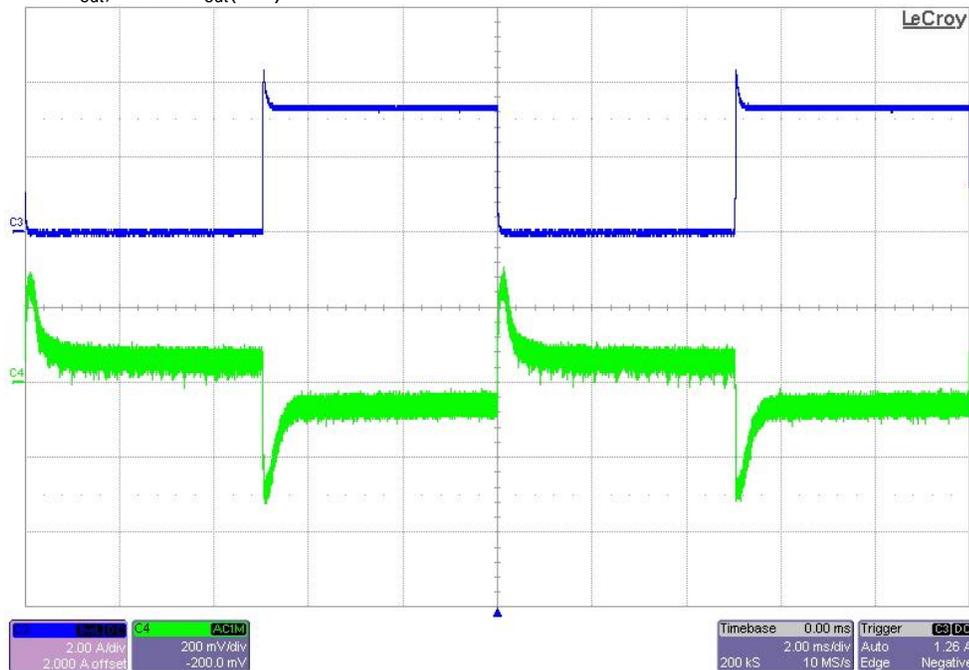

9 Over current protection

The image below shows the over current protection test on 12V_{out} at 24V_{in}. Over current protection point on the tested board is at **3.78A**.


CH3: I_{out}, CH4: V_{out}(AC)

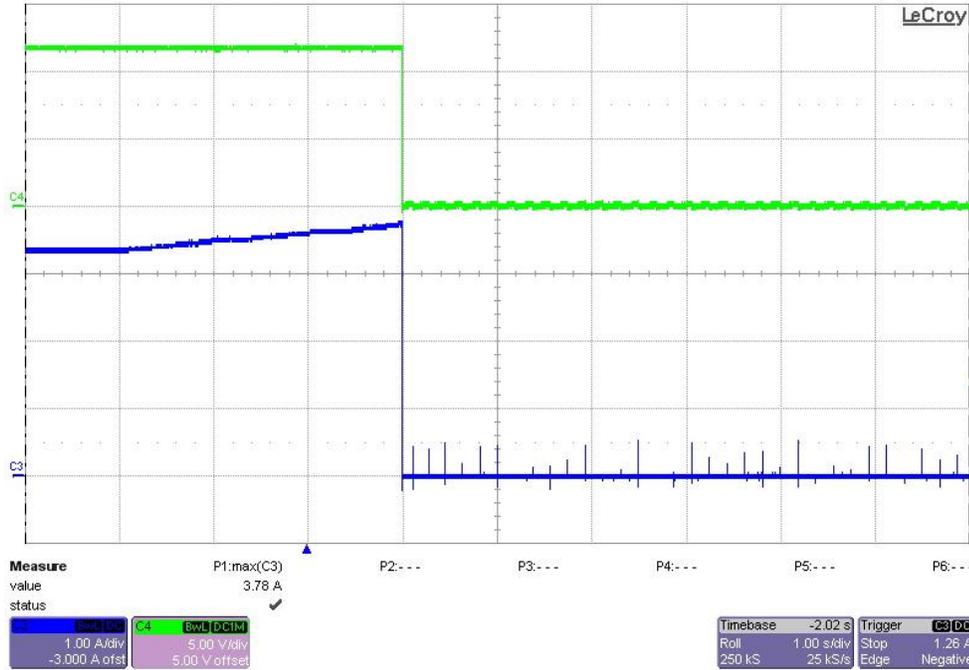

10 Over voltage protection

The image below shows the over voltage protection test on 12V_{out} /3.4A at 24V_{in}. The over voltage protection test is done by short resistor R30, and the over voltage protection point on the tested board is at **14.7V**.

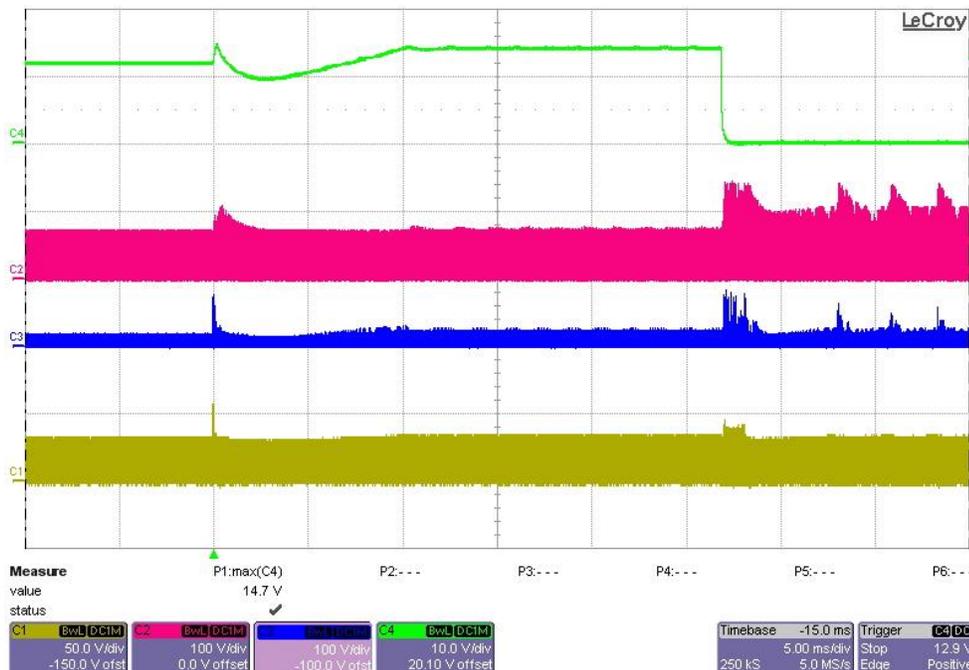
CH1: V_{DS} (Q4), CH2: V_{DS} (Q2), CH3: V_{DS} (Q6), CH4: V_{out}




11 Switching Waveforms

The images below show key switching waveforms of PMP10861RevB. The waveforms are measured with 3.4Ω resistive load. CH1: V_{DS} (Q4), CH2: V_{DS} (Q2), CH3: V_{DS} (Q6), CH4: V_{out}

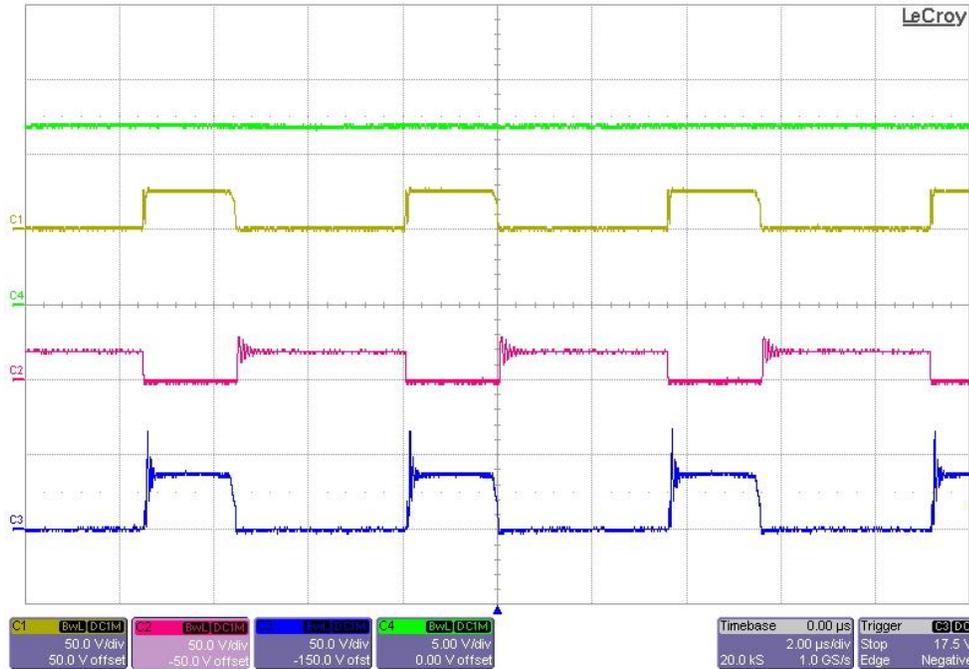
11.1 Voltage stresses on power MOSFETs V_{DS} @ $9V_{in}$ and 3.4Ω load resistor



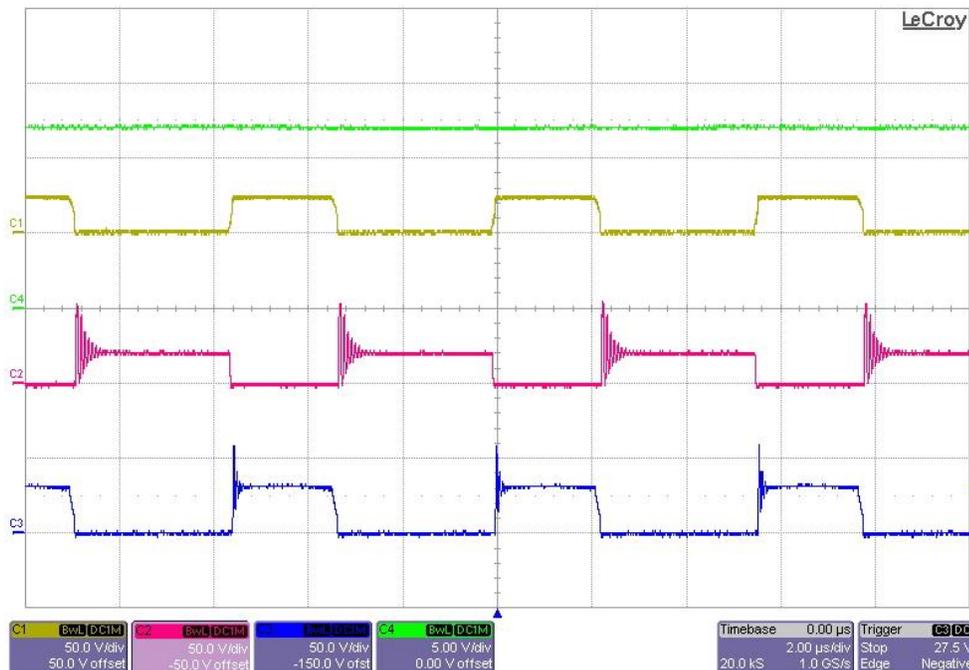
11.2 Voltage stresses on power MOSFETs V_{DS} @ $9V_{in}$ and no load



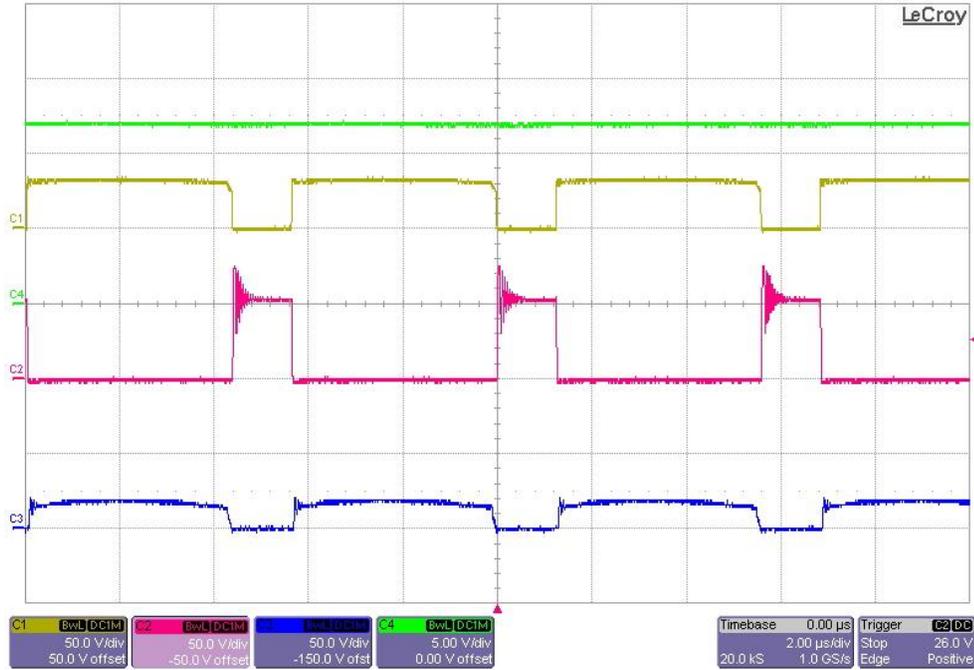
11.3 Voltage stresses on power MOSFETs V_{DS} @ $24V_{in}$ and 3.4Ω load resistor



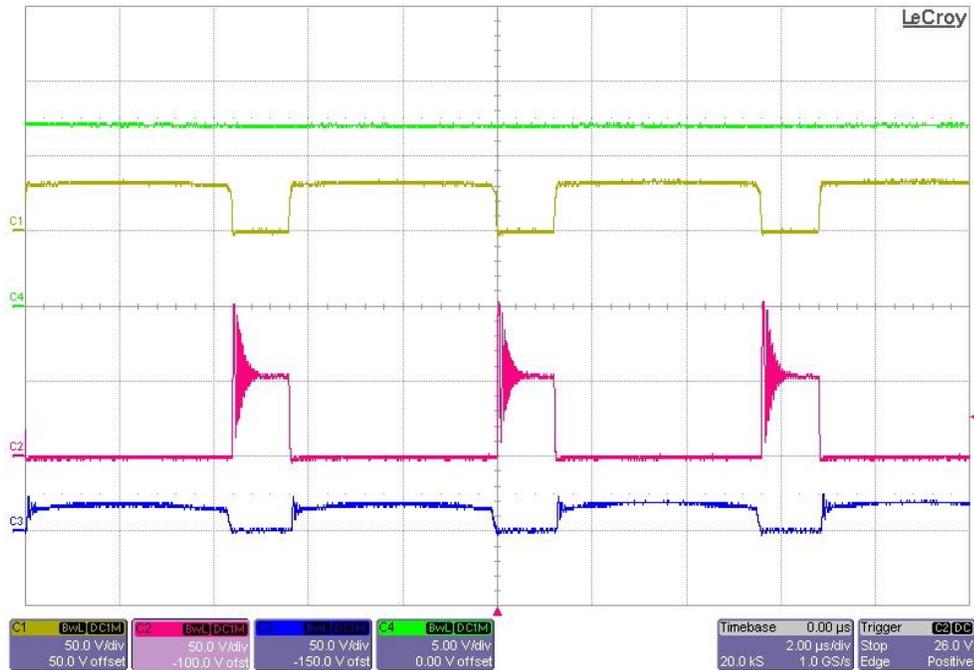
11.4 Voltage stresses on power MOSFETs V_{DS} @ $24V_{in}$ and no load



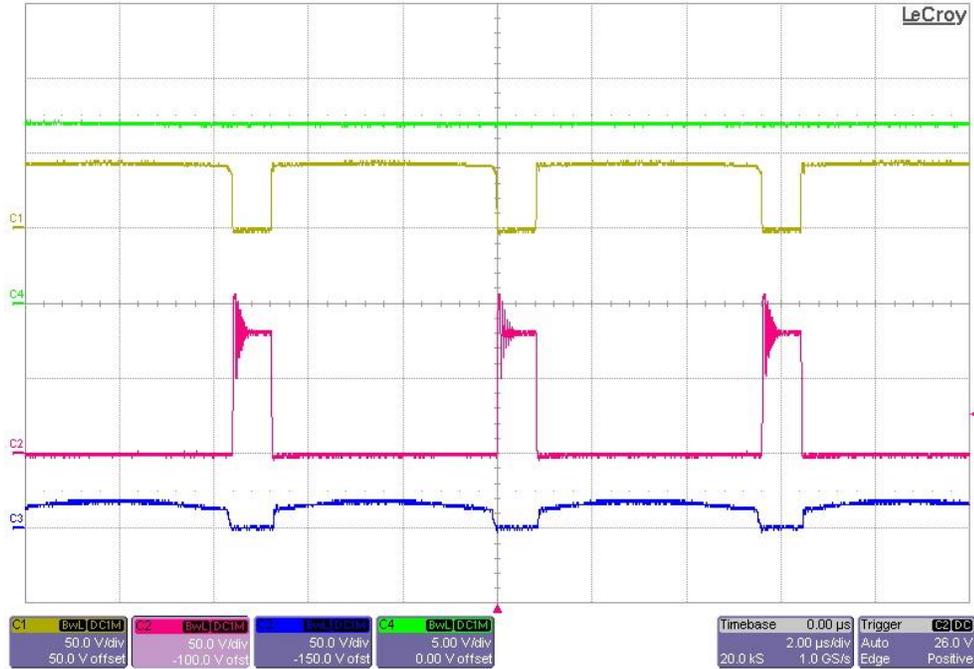11.5 Voltage stresses on power MOSFETs V_{DS} @ $36V_{in}$ and 3.4Ω load resistor



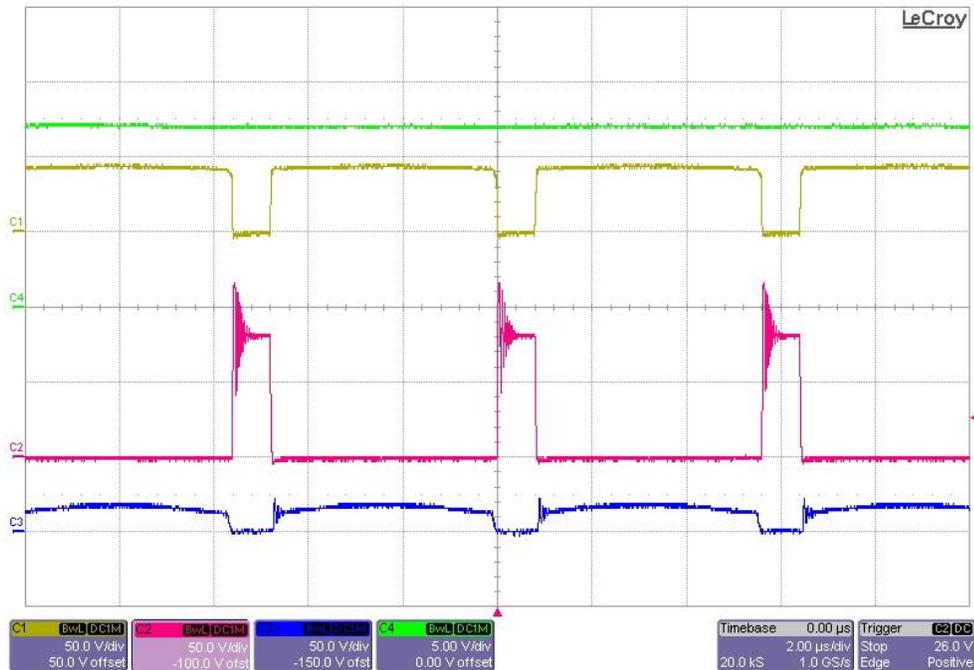11.6 Voltage stresses on power MOSFETs V_{DS} @ $36V_{in}$ and no load



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated