

AN-1376 External Serial Interface Reduces Simultaneous Switching Output Noise in FPGAs

ABSTRACT

This application report highlights how using external SerDes in conjunction with minimum current drive FPGA I/O can reduce FPGA's internal noise and reap the benefits of a serial interface across the system. This may allow designers to use low end FPGAs with external SerDes to reduce cost and still have high analog performance.

Contents

1	Introduction	2		
2 Test Setup for Simultaneous Switching Output Noise				
	2.1 Test Setup Schematic			
	2.2 Component Information	4		
3	Simultaneous Switching Output Noise	5		
4	Benefits of Using External SerDes			
	4.1 External SerDes Reliability	8		
	4.2 External SerDes With Pre-Emphasis Feature	10		
5	Conclusion	11		
6	Resources and References 12			

List of Figures

1	DS92LV16 SerDes and Cyclone FPGA Test Setup	2
2	Cyclone and DS92LV16 Connections	3
3	DS92LV16 Block Diagram	4
4	Active Output Transitions and "Quiet Output" (bottom), SS Data, 24 mA	5
5	Active Output Transitions and "Quiet Output" (bottom), SS Data, 2 mA	6
6	24 mA Drive vs 2 mA Drive for FPGA Output Clock Signal Integrity and Jitter	7
7	24 mA FPGA Output +4" Trace with PRBS Data	8
8	2 mA FPGA Output +4" Trace with PRBS Data	8
9	Eye Diagram after 1m of CAT5 Cable	9
10	DS92LV18 SerDes BER Test Setup	9
11	Eye Diagram Measured after 15m of Infiniband Cable at the Input of the DS92LV18 Receiver; f _{TCLK} = 66 MHz (1.32 Gbps); No Pre-emphasis	10
12	Eye Diagram Measured after 15m of Infiniband Cable at the Input of the DS92LV18 Receiver; f _{TCLK} = 66 MHz (1.32 Gbps); Max Pre-emphasis	11

List of Tables

1	Device Features	5

All trademarks are the property of their respective owners.

www.ti.com

2

1 Introduction

A critical issue with any FPGA (Field Programmable Gate Array) design is Simultaneous Switching Output (SSO) noise. SSO noise, also known as ground bounce, is a result of large instantaneous changes in current across the power/ground inductance of the integrated circuit. This potential problem becomes more and more serious as the number of active high-drive LVCMOS outputs on a FPGA design increases. In large FPGAs with several synchronous parallel interfaces this phenomenon can result in poor system performance or intermittent data errors.


The FPGA SSO noise is minimized by using the lowest drive current from the FPGA and reduces the parallel bus to a single differential signal. LVCMOS outputs from the FPGA are unsuited for driving over long interconnects or at high data rates. Upgrading the parallel interfaces with an external Serializer/Deserializer (SerDes) interface to the FPGA will reduce SSO noise and improve the overall system performance. The close proximity of the external SerDes to the FPGA allows the FPGA I/O to be programmed at the minimum CMOS drive level of about 2 mA. Reducing the drive level lowers the dynamic currents within the FPGA curbing the generation of SSO noise. Noise generated in the I/Os on a FPGA can corrupt the analog performance of FPGA PLLs or other system analog resources.

The Altera Cyclone or Xilinx Spartan are good examples of economical FPGAs intended for low to medium end applications. They do not contain dedicated serialization or deserialization circuitry for highspeed communications limiting the maximum data rate. This makes the Cyclone and Spartan good candidates for an external serial interface. Using a SerDes external to an FPGA allows an entire multi-byte parallel interface to be condensed to one or more high-speed signal pairs for economical transmission across system interfaces. Before and after measurements of the SSO noise on a Cyclone FPGA will help to quantify the improvements made by the change in the FPGA programmed I/O current drive.

2 Test Setup for Simultaneous Switching Output Noise

CH1 **FPGA Evaluation Board** Power Oscilloscope (5 VDC) Boot Loader and RS 232 DS92LV16 DS92LV16 Circuitry Serializer Deserializer 3.3VDC 3.3VDC LOCK w⁰ - w30 16 DIN [0:15] (even) ROUT [0:15] Power Power FPGA 80 MHz S 1 TCLK 80 MHz REFCLK RIN +/-80 MHz 100Ω EXT CLK ₩ DO +/-DG 2040 meter Z-Pack Twinax cable

 The FPGA/SerDes evaluation test setup is shown in Figure 1.






Test Setup for Simultaneous Switching Output Noise

www.ti.com

2.1 Test Setup Schematic

Figure 2 shows an example of a system implementation using the Cyclone and DS92LV16. The specific Cyclone I/Os used for the interface would depend upon the device selected, additional required functionality, and other layout constraints. For the best and most consistent AC performance, all the FPGA—SerDes interconnects should be selected from a single I/O bank.

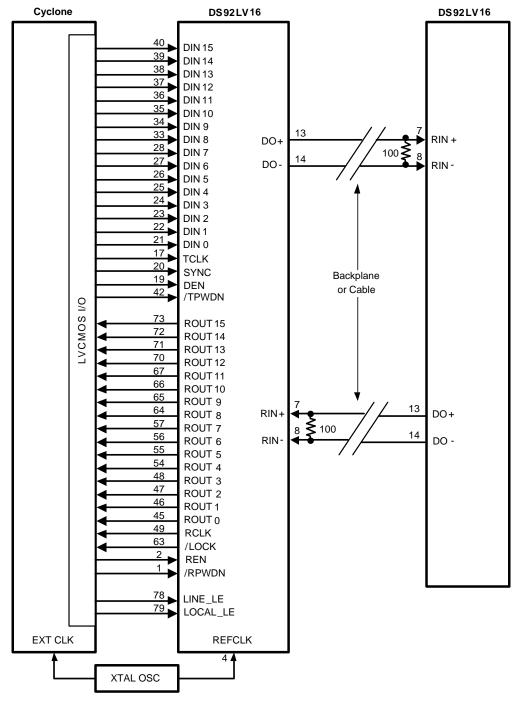





2.2 Component Information

2.2.1 DS92LV16 SerDes

Figure 3 shows the block diagram for the DS92LV16 SerDes. The serializer takes 16-bits of parallel LVCMOS data and translates it into a serial stream with embedded clock. The serial data stream is output as a Low Voltage Differential Signaling (LVDS) signal with a maximum speed of 1.44 Gbps across cables or backplanes.

The deserializer takes the differential LVDS signal and translates it back into 16-bit parallel LVCMOS data. The device also contains loop back test capability for testing line and local interfaces. The Serializer and Deserializer operate independently with separate clock, enable, and power down pins.

2.2.2 Altera Cyclone FPGA

Table 1 shows the Cyclone device family and features. After selecting an FPGA to handle the logic and processing requirements of the application, the designer may chose to add an external SerDes due to system interface requirements. The FPGA choice depends on the end application requirements; the DS92LV16 can be effectively used with any FPGA density or architecture.

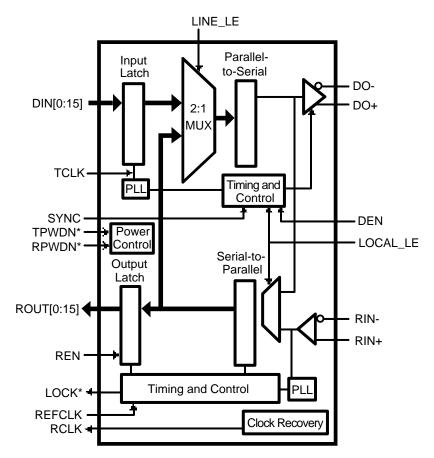


Figure 3. DS92LV16 Block Diagram

Feature	EP1C3	EP1C4	EP1C6	EP1C12	EP1C20
LEs	2,910	4,000	5,980	12,060	20,060
M4K RAM Blocks (128 × 36 bits)	13	17	20	52	64
Total RAM Bits	59,904	78,336	92,160	239,616	294,912
PLLs	1	2	2	2	2
Maximum User I/O Pins	104	301	185	249	301

Table 1. Device Features

3 Simultaneous Switching Output Noise

SSO noise, as the name implies, is the result of internal and external circuitry switching at the same time. The cumulative effect of all this switching current passing through power and ground inductance is device-generated noise. This noise is visible on non-switching outputs as internal movement in the ground or power network.

The following test was conducted with the FPGA to DS92LV16 parallel bus clocking at 80 MHz and the LVCMOS output drive current of the FPGA set to either 24 mA or 2 mA. This will allow for the observation of SSO noise and other noise related effects on the parallel bus.

- 1. Simultaneous Switching Outputs—Switched 16 FPGA outputs simultaneously while monitoring a "quiet output" for ground bounce on the FPGA evaluation board.
- 2. Clock Output Jitter—Switched 16 FPGA outputs simultaneously while monitoring a FPGA clock output for jitter.

Figure 4 shows the level of noise that can result from only 16 LVCMOS I/Os switching at the same time.

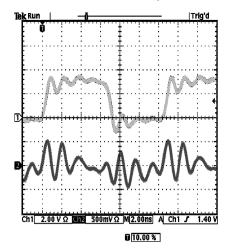


Figure 4. Active Output Transitions and "Quiet Output" (bottom), SS Data, 24 mA

The upper waveform (CH1) is the active switching transition repeated on 15 additional LVCMOS FPGA outputs driven at 24 mA. There is a visible 600 mV undershoot present just after the waveform falling edge. As expected, the bottom "quiet output" waveform (CH2) tends to follow this pattern highlighting an internal ground movement of ±500 mV around the true board ground. This internal noise in the ground and power systems can dynamically alter the supply voltage of switching logic. The dynamic shift in supply voltage will cause changes in the switching characteristics of internal signals and reduce the performance of other more sensitive analog circuitry.

In addition, the output signal also shows ringing and undershoots.



Simultaneous Switching Output Noise

www.ti.com


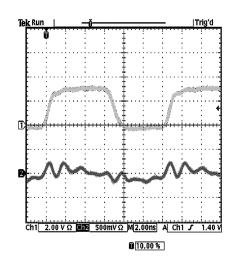


Figure 5. Active Output Transitions and "Quiet Output" (bottom), SS Data, 2 mA


Figure 5 shows the quiet and switching waveforms with the FPGA programmed for 2 mA (minimum) current drive. The upper waveform (CH1) is the active switching transition repeated on 15 additional LVCMOS FPGA outputs. Compared to the previous waveform, the 2 mA drive current results in slower transition times and greatly reduced undershoot relative to external ground. Monitoring the signal on a quiet output (CH2) shows the improvement on the internal ground as well.

The FPGA drive current reduction improves the signal integrity and lowers the jitter of output Clock signals. The noise on the clock signal is another indication of diminished FPGA PLL analog performance. In addition to the reduction in FPGA performance, analog devices located adjacent to the FPGA will also be affected by the increase in ground noise. The following series of waveforms (Figure 6) show how a reduction in drive strength can improve the signal integrity and lower the jitter seen on FPGA output signals.

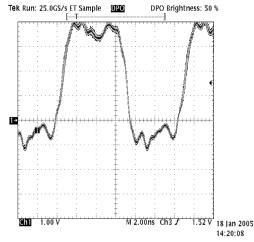



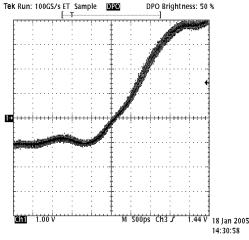With 24 mA of drive programmed into the FPGA outputs, large excursions outside the supply rails are clearly visible.




Rising Edge Magnification: This view shows greater than 200 ps of clock jitter in the FPGA output that is a result of the increased drive current.




The reduction in jitter will improve analog performance of adjacent components like the DS92LV16. Starting with a clean clock source means that significantly reduced jitter within the PLL bandwidth will allow for enhanced high-speed signal integrity.

By reducing the FPGA interconnect to short-to-point topology, the low drive (2 mA) setting can efficiently and cleanly drive the LVCMOS interconnect into the LVDS SerDes. Programming to the low drive setting reduces the noise generated by the FPGA and reduces system EMI. Figure 7 and Figure 8 clearly show undershoot and overshoot is completely eliminated and noise reduction achieved with low drive FPGA programming.

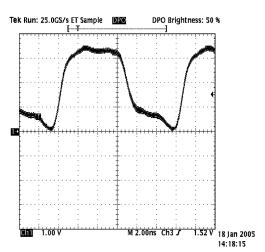

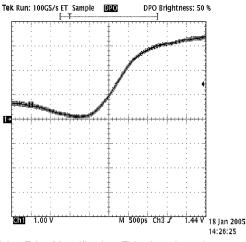Reducing the FPGA programmed drive to 2 mA results in a tightly controlled clock waveform.



Rising Edge Magnification: This view shows how a reduced 2 mA drive current maintains good signal integrity and exceptionally low (~50 ps) jitter.



www.ti.com

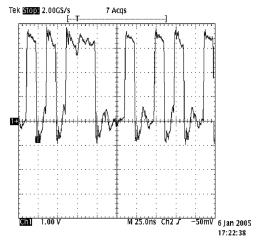


Figure 7. 24 mA FPGA Output +4" Trace with PRBS Data

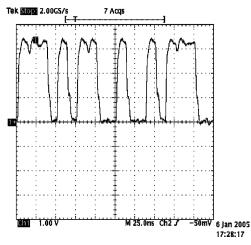


Figure 8. 2 mA FPGA Output +4" Trace with PRBS Data

4 Benefits of Using External SerDes

LVCMOS outputs from the FPGA are unsuited for driving over long interconnects or at high data rates. To address these system demands and to reduce the number of signals at backplane or cable interfaces, SerDes devices with low voltage differential signaling (LVDS) technology are often employed.

4.1 External SerDes Reliability

8

The main function of any SerDes chipset is to translate data originating from a wide parallel bus into one or more serial bit streams and to convert the data back a wide parallel bus at the receiving end. With the system improvements SerDes devices bring, one of the first questions system designers may ask is how long the interconnect between the serializer and the deserializer can be that will still ensure error-free data transfer.

To find out the answers to questions of "How far?" and "How fast?" a type of testing called BER or Bit Error Rate Testing is done on the serial interface.

Figure 9 shows the eye diagram at the DS92LV16 receiver after 1m of CAT5 cable. This diagram shows the wide open eye possible with inexpensive CAT5 cable running at a data rate of almost 1 Gbps. The maximum data rate of the DS92LV16 is approximately 1.5 Gbps.



www.ti.com

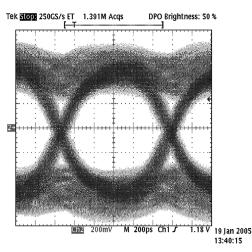


Figure 9. Eye Diagram after 1m of CAT5 Cable

A related example of this type of testing is shown below. As depicted in Figure 10, a BER transmitter provided 18-bit wide PRBS (2^{15} -1) and a BER receiver received 18-bit wide PRBS (2^{15} -1). The DS92LV18 transmitter serialized the sequence and sent it across a cable assembly; the DS92LV18 receiver then deserialized the data, and sent the 18-bit wide PRBS pattern back to the BERT for analysis. Configuring the test setup in this manner allows the maximum operating frequency to be determined for each cable length. The maximum operating frequency of this system is defined as the maximum frequency of the device transmitter clock (TCLK) at which the device receiver misinterprets zero out of 10^{12} data bits. This equates to the bit error rate of less than 1×10^{-12} . The test was conducted at room temperature and the power supply voltage for both devices was set to 3.3 volts. For a DS92LV18 SerDes the TCLK frequency equates to 1/20th of the high-speed serial data rate. For example, at the chipset maximum TCLK of 66MHz the serial data rate is running at a speed of 1.32Gbps.

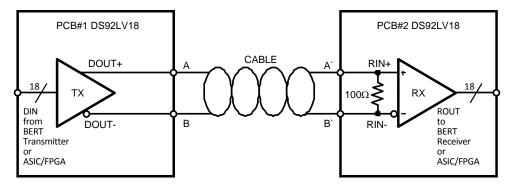


Figure 10. DS92LV18 SerDes BER Test Setup

Based on the BERT results, the DS92LV18 can be used in short to medium length cable interface applications. If employed to move data between two points across a generic category 5 cable, it can operate at its highest operating frequency (66 MHz) for cable lengths up to 10 feet. For lower operating frequencies, it can transmit error free data over cables longer than 50 feet. Shielded cables with lower nominal attenuation paired with connectors rated for gigabit operation enable you to make longer high-speed, error free connections.




Benefits of Using External SerDes

Even though the speeds have increased dramatically, the serial interface can transfer data at a rate and distance just not possible with a parallel interface. In order to accommodate Gigabytes of data 32, 64, or even 128-bit parallel bus designs have been implemented. This resulted in massive routing bottlenecks at cable assemblies, memory board, and backplane interfaces. These performance-limiting issues were addressed when the parallel interfaces were replaced with one or more high-speed serial interfaces. This architecture shift has enabled system performance, packaging, and features that could not otherwise have been achieved.

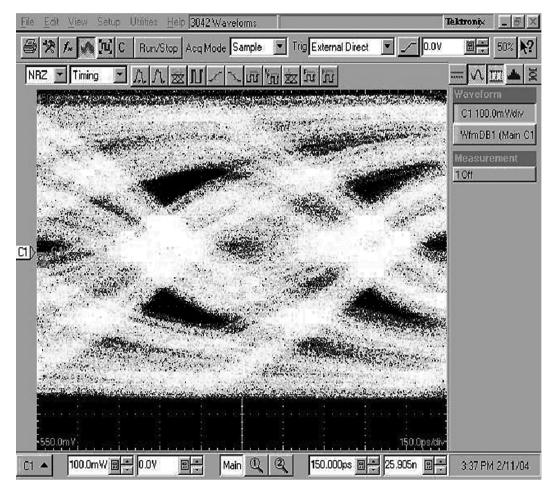
4.2 External SerDes With Pre-Emphasis Feature

Even at the lower data rates used in parallel architectures, a factor limiting transmission distance has always been the electrical losses of the transmission media. Serial architectures have progressed to address the dielectric and skin effect loss issues associated with high-speed design in several ways. In order to achieve high-speed reliable data transmission across cables up to 50 feet long something must be done to compensate for the high frequency loss in the cable. Pre-emphasis is a circuit design technique that adds high frequency energy to the transmitter output signal, negating the loss incurred during data transmission across the medium. The Texas Instruments SCAN921821, a dual 18-bit Serializer, uses 6 dB of pre-emphasis to maintain robust, error-free communication across 50 feet of cable. This added feature increases the reach of LVDS SerDes by up to 5x at >1 Gbps serial data rates.



Measured after 15m of Infiniband Cable at the Input of the DS92LV18 Receiver; f_{TCLK} = 66 MHz (1.32 Gbps); No Preemphasis

Figure 11. Eye Diagram Measured after 15m of Infiniband Cable at the Input of the DS92LV18 Receiver; f_{TCLK} = 66 MHz (1.32 Gbps); No Pre-emphasis

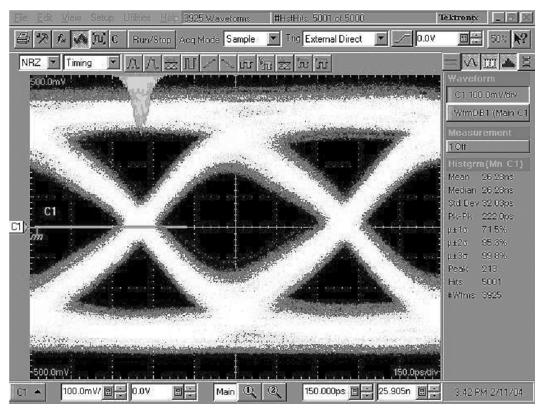

Measured after 15m of Infiniband Cable at the Input of the DS92LV18 Receiver; f_{TCLK} = 66 MHz (1.32 Gbps); Max Pre-emphasis

Figure 12. Eye Diagram Measured after 15m of Infiniband Cable at the Input of the DS92LV18 Receiver; f_{TCLK} = 66 MHz (1.32 Gbps); Max Pre-emphasis

The eye diagrams shown in Figure 11 and Figure 12 clearly show the value of pre-emphasis for driving cables up to 15 to 20 meters in length. A SCAN921821 Dual 18-bit Serializer is transmitting the data while a DS92LV18 SerDes is receiving the data.

5 Conclusion

Using a stand alone SerDes is an effective way to minimize device generated SSO noise in the FPGAs. The external SerDes device allows the used to program the FPGA with a minimum output drive. The minimum drive limits the noise generated by the FPGA due to reduced simultaneous switching currents. Reduced noise lowers the risk that adjacent analog components will become inadvertent victims of excessive digital noise.

In addition to the local noise reduction benefits shown in the application note, Using a stand alone SerDes function provides lower jitter, BER and longer drive capability resulting in better analog performance. External SerDes function may also allow lower cost solutions with performances comparable to the higher cost solutions.

Analog enhancements, such as pre-emphasis, have enabled even higher speeds and longer drive distances over lossy interconnect. This capability, achieved though low cost silicon upgrades can be used to extend the operational life and enhance the functionality of systems currently deployed in the field.

TEXAS INSTRUMENTS

www.ti.com

Resources and References

6 Resources and References

- 1. DS92LV16 16-bit SerDes Design Guide (SNLA201)
- 2. 18-bit SerDes Design Guide (DS92LV18, SCAN921821) (SNLA202)
- 3. DS92LV16 16-Bit Bus LVDS Serializer/Deserializer 25 80 MHz (SNLS138)
- 4. DS92LV18 18-Bit Bus LVDS Serializer/Deserializer 15-66 MHz (SNLS156)
- 5. Cyclone Device Handbook Volumes 1 & 2, Altera, 2003 and 2004, www.altera.com
- 6. Quartus II Handbook Volumes 1, 2 & 3, Altera, 2004, www.altera.com

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products		Applications			
Audio	www.ti.com/audio	Automotive and Transportation	www.ti.com/automotive		
Amplifiers	amplifier.ti.com	Communications and Telecom	www.ti.com/communications		
Data Converters	dataconverter.ti.com	Computers and Peripherals	www.ti.com/computers		
DLP® Products	www.dlp.com	Consumer Electronics	www.ti.com/consumer-apps		
DSP	dsp.ti.com	Energy and Lighting	www.ti.com/energy		
Clocks and Timers	www.ti.com/clocks	Industrial	www.ti.com/industrial		
Interface	interface.ti.com	Medical	www.ti.com/medical		
Logic	logic.ti.com	Security	www.ti.com/security		
Power Mgmt	power.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense		
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video		
RFID	www.ti-rfid.com				
OMAP Applications Processors	www.ti.com/omap	TI E2E Community	e2e.ti.com		
Wireless Connectivity	www.ti.com/wirelessconnectivity				

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2013, Texas Instruments Incorporated