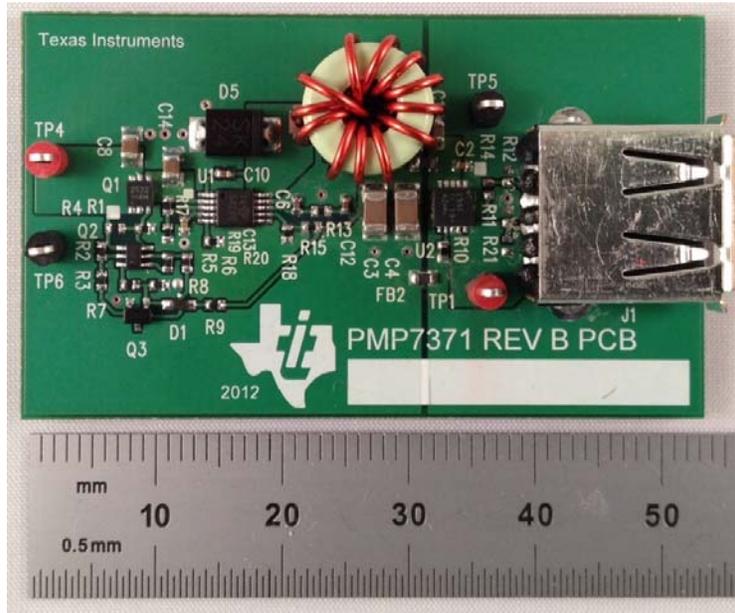



1 Photo

The image below shows a photo of the PMP7371 Rev B demo board.



2 Efficiency

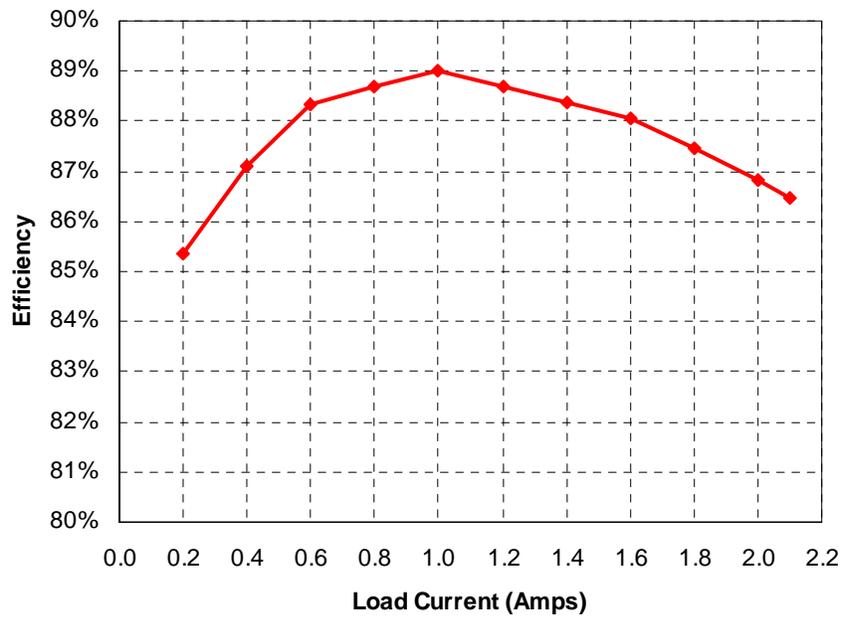The efficiency data is shown in the graph and table below.



Iout	Vout	Vin	Iin	Pout	Losses	Efficiency
0.000	4.971	12.01	0.002	0.00	0.024	0.0%
0.200	4.964	11.99	0.097	0.99	0.170	85.4%
0.400	4.956	11.98	0.190	1.98	0.294	87.1%
0.600	4.947	11.96	0.281	2.97	0.393	88.3%
0.800	4.939	12.01	0.371	3.95	0.505	88.7%
1.000	4.930	11.99	0.462	4.93	0.609	89.0%
1.200	4.922	11.98	0.556	5.91	0.754	88.7%
1.402	4.914	12.03	0.648	6.89	0.906	88.4%
1.602	4.905	12.01	0.743	7.86	1.066	88.1%
1.800	4.897	12.00	0.840	8.81	1.265	87.4%
2.000	4.889	11.98	0.940	9.78	1.483	86.8%
2.100	4.885	11.97	0.991	10.26	1.604	86.5%


3 Regulation

The output voltage measured at TP1 and TP5 for various loading conditions is shown below.

Load (A)	10Vin	12Vin	14Vin
	Vout	Vout	Vout
0.00	4.97	4.97	4.97
0.25	4.96	4.96	4.96
0.50	4.95	4.95	4.95
0.70	4.94	4.94	4.94
1.00	4.93	4.93	4.93
1.50	4.91	4.91	4.91
2.10	4.89	4.89	4.88


4 Thermal

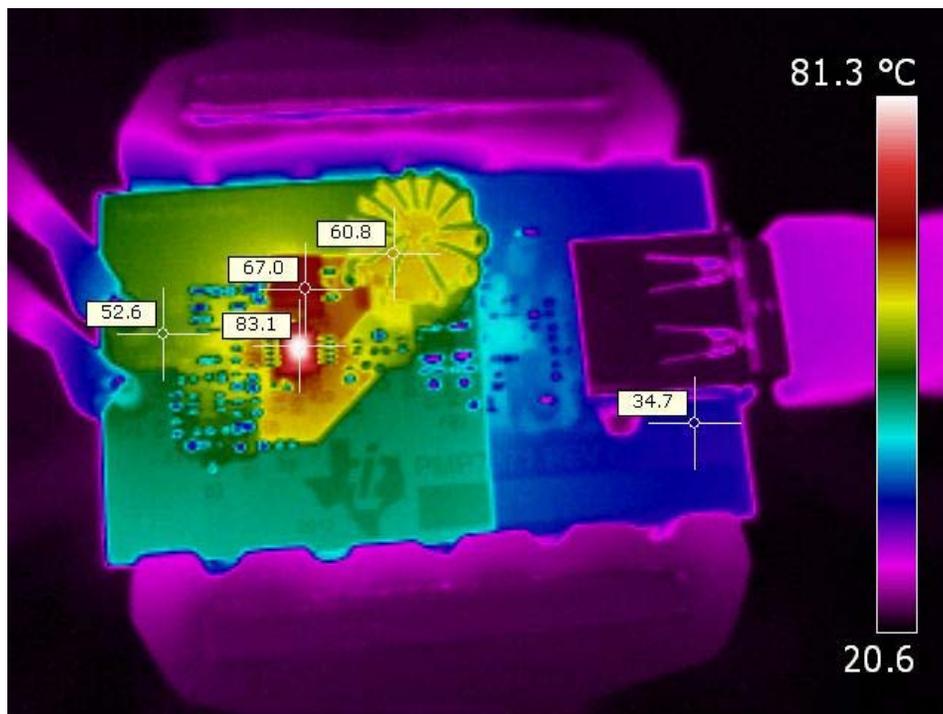The thermal image below shows the circuit board with a 12V input and 2.1A load. The ambient temperature was 25C with no air flow.




5 Startup

5.1 12V Input – No Load

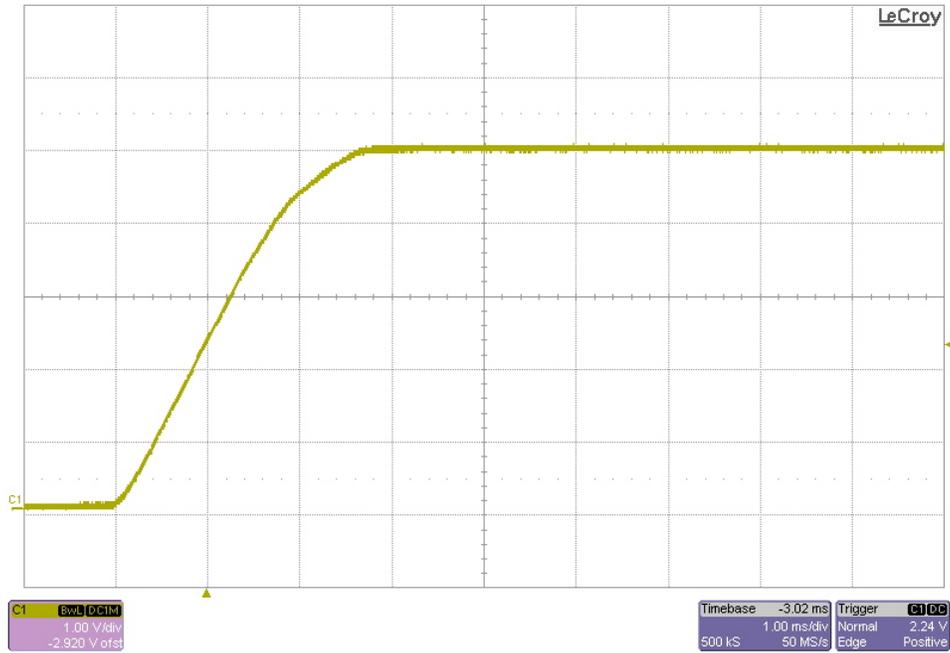


5.2 12V Input – 2Ω Load

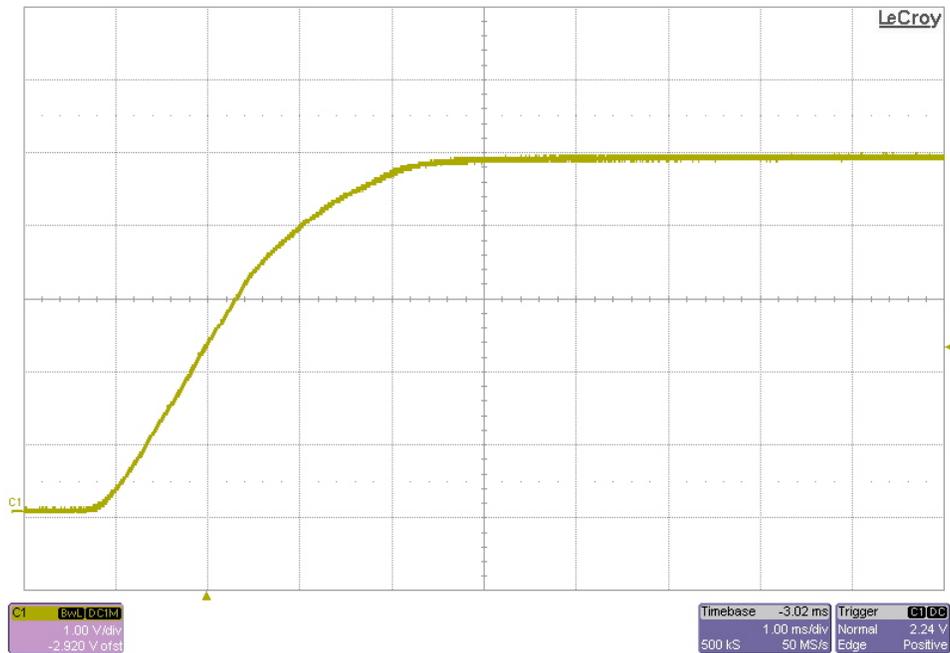


6 Output Ripple Voltage

The output ripple voltage is shown in the plots below. The input was 12V. The ripple voltage was measured on TP1.


6.1 0A Load

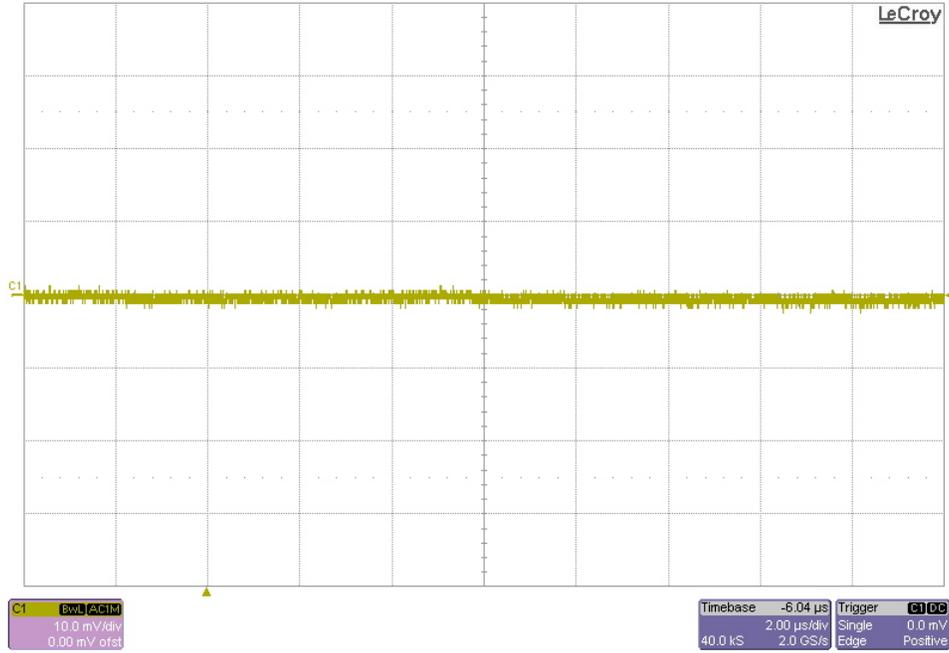


6.2 250mA Load

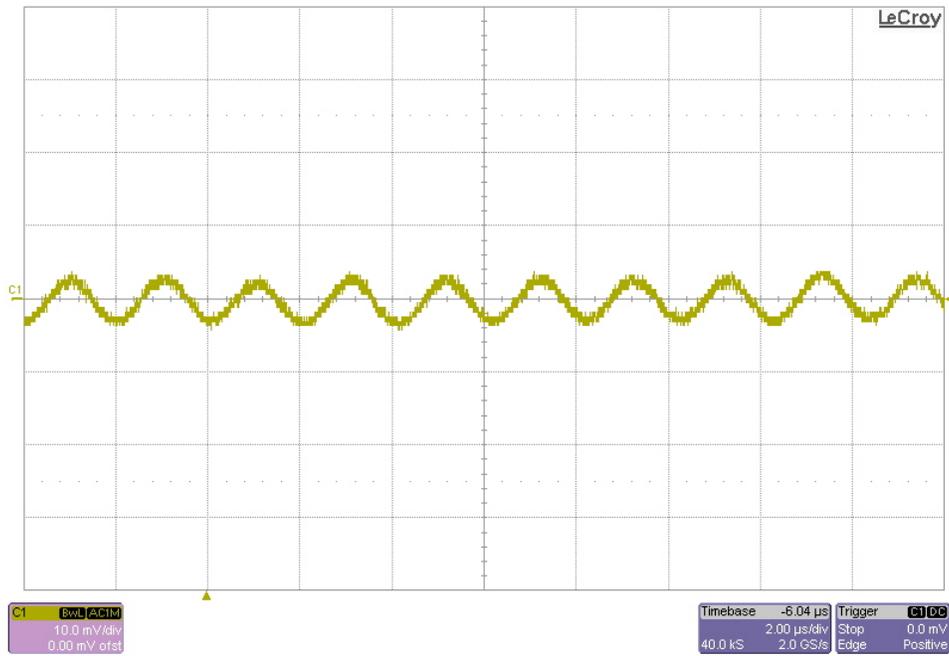


6.3 500mA Load

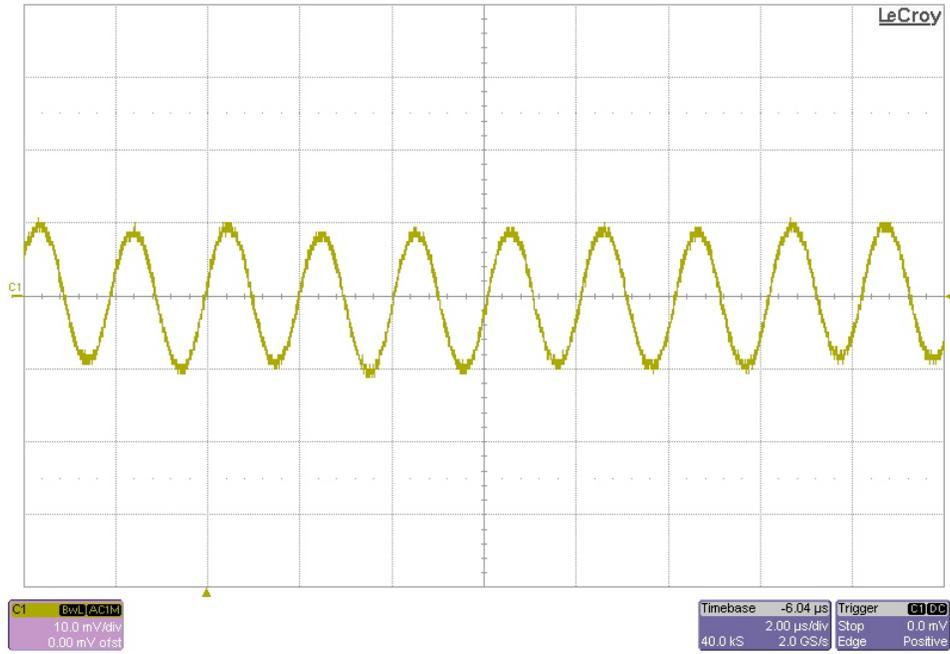


6.4 700mA Load

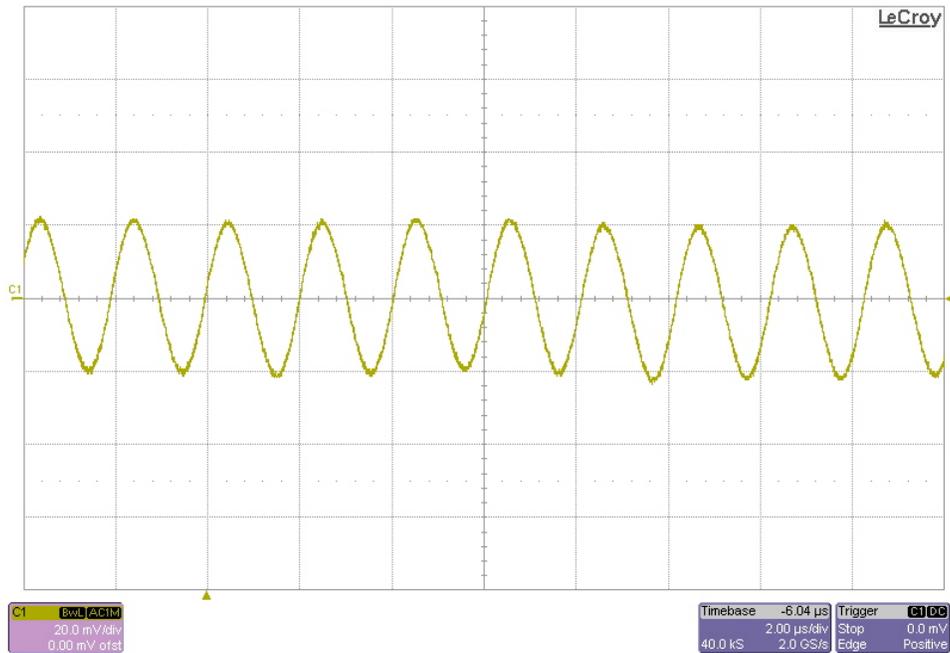


6.5 1A Load

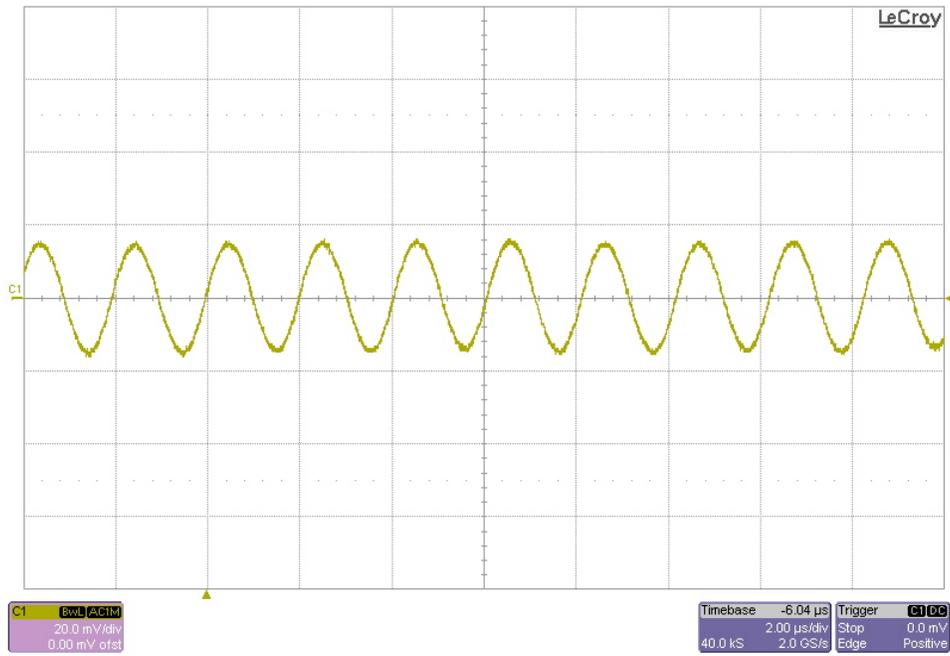

6.6 1.5A Load

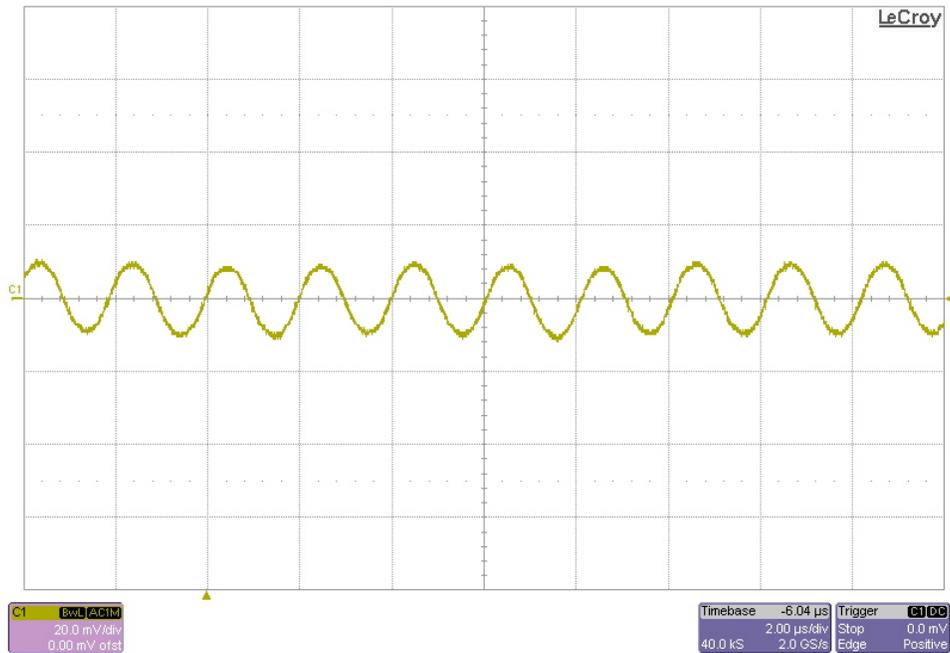


6.7 2.1A Load

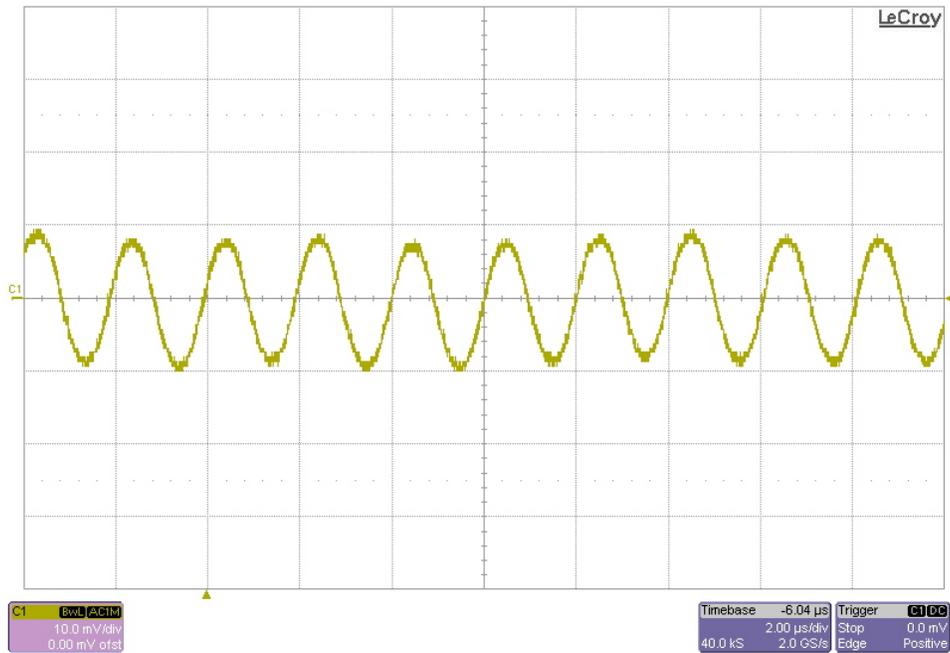

7 Frequency Response

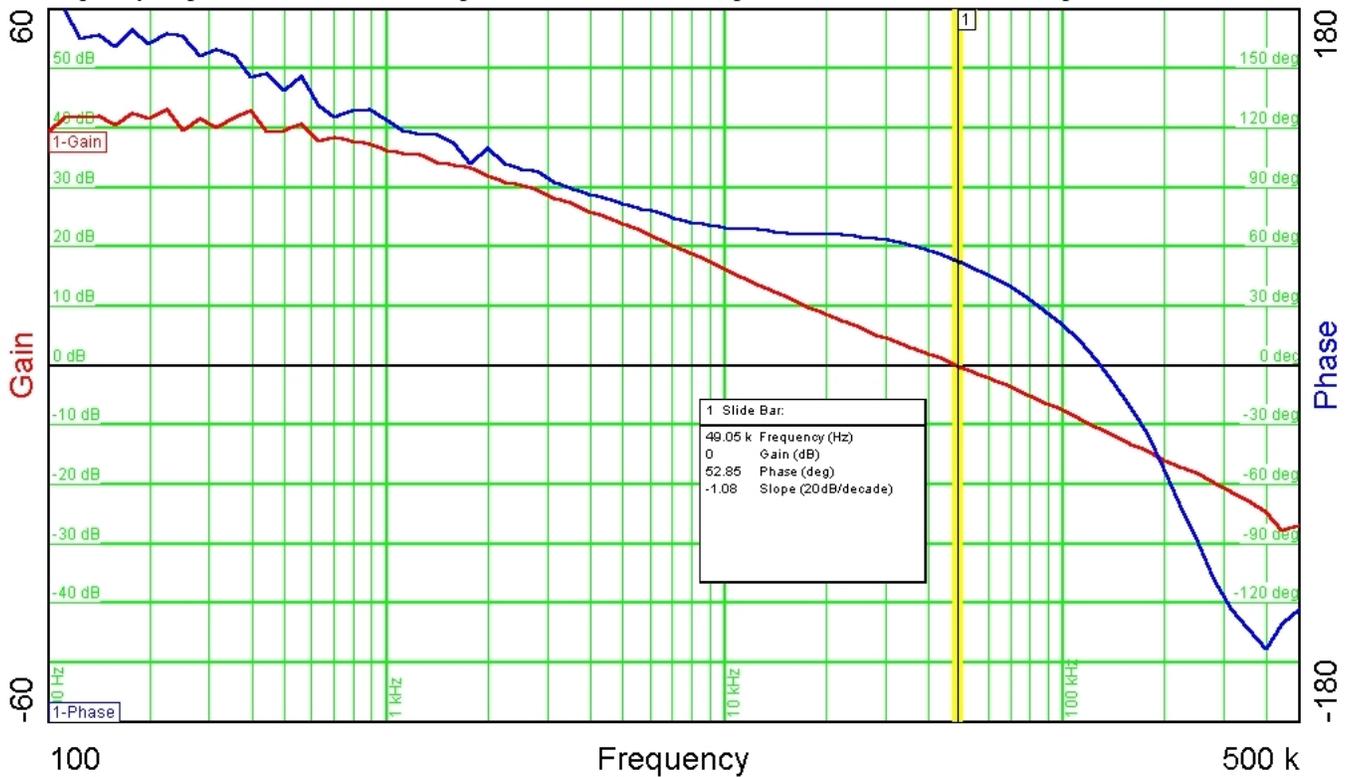
The frequency response of the feedback loop is shown below. The input was set to 12V, and the output was loaded with 2.1A.




8 Load Transients

The responses to various load steps are shown in the images below. Channel 1: Vout (ac coupled); Channel 4: Iout. The output voltage was measured on TP1.


8.1 80mA to 1A

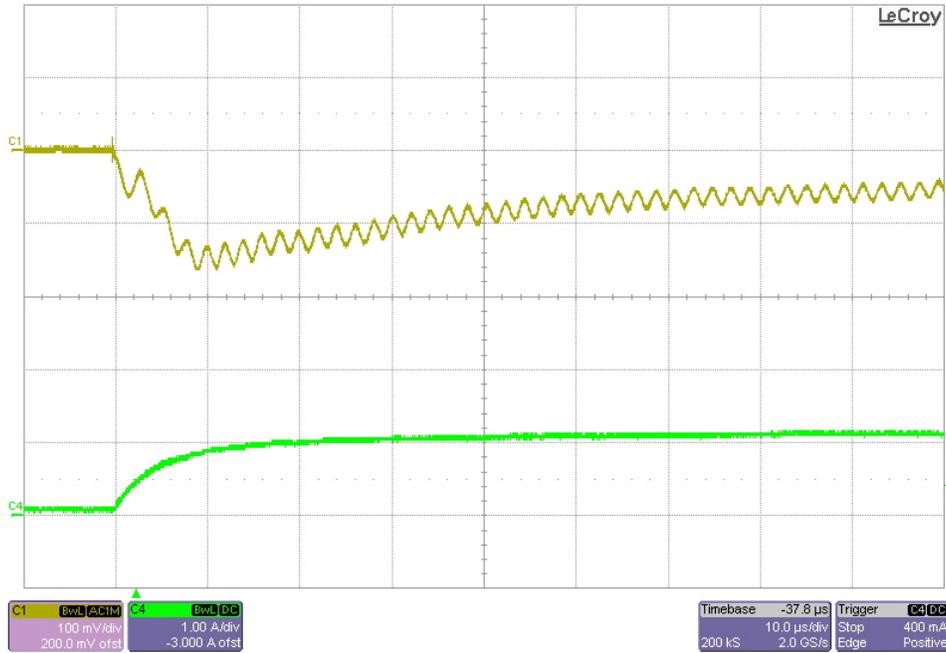


8.2 1A to 80mA

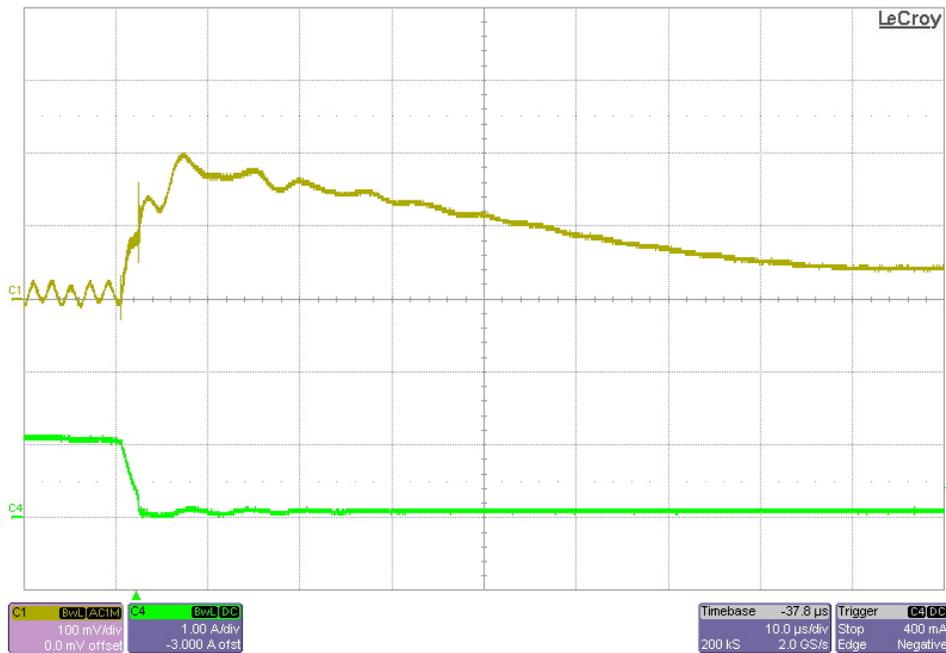


8.3 0A to 500mA

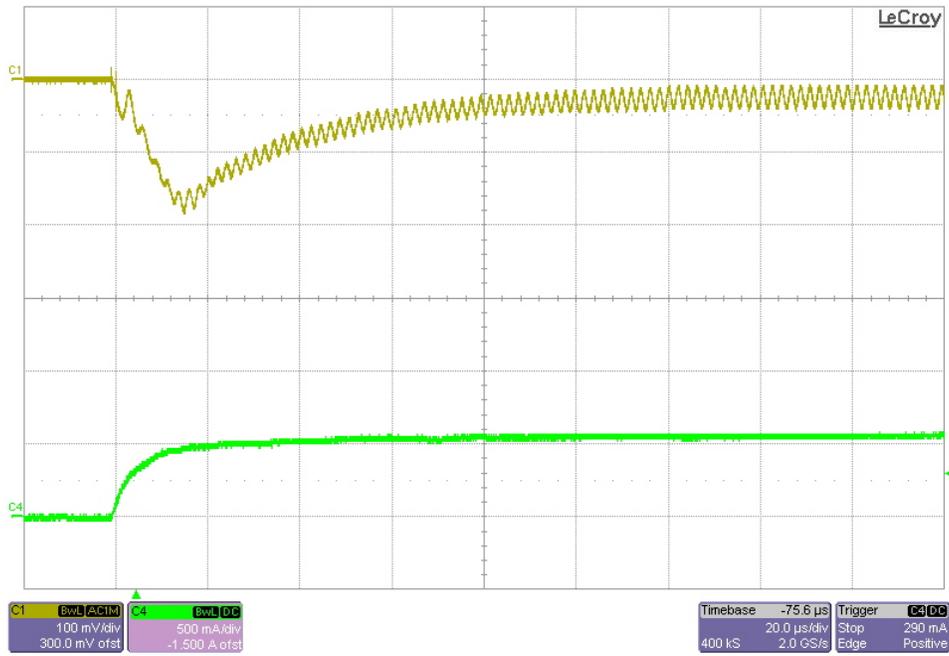


8.4 500mA to 0A

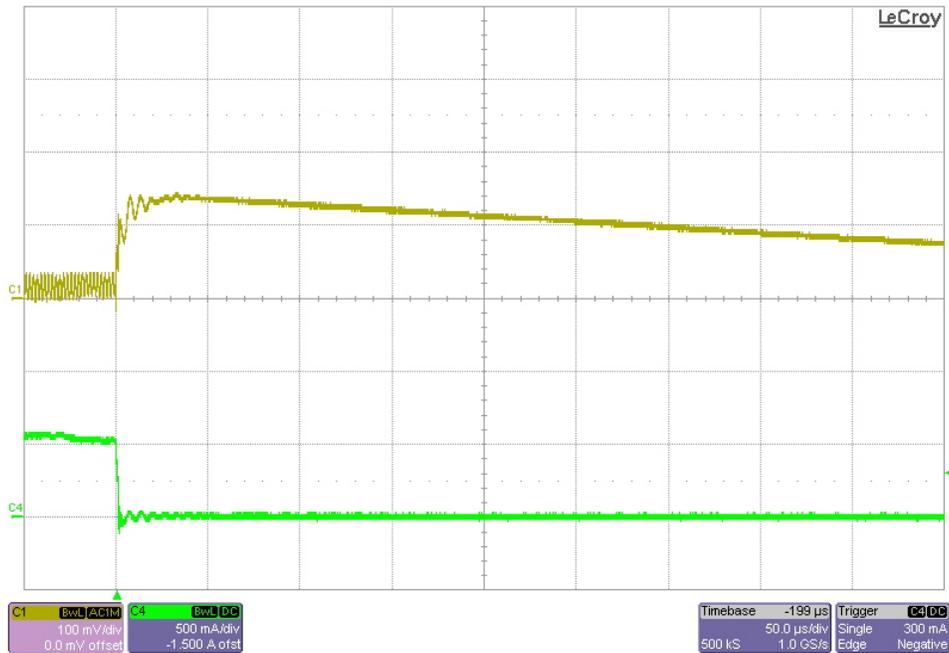


8.5 500mA to 1A

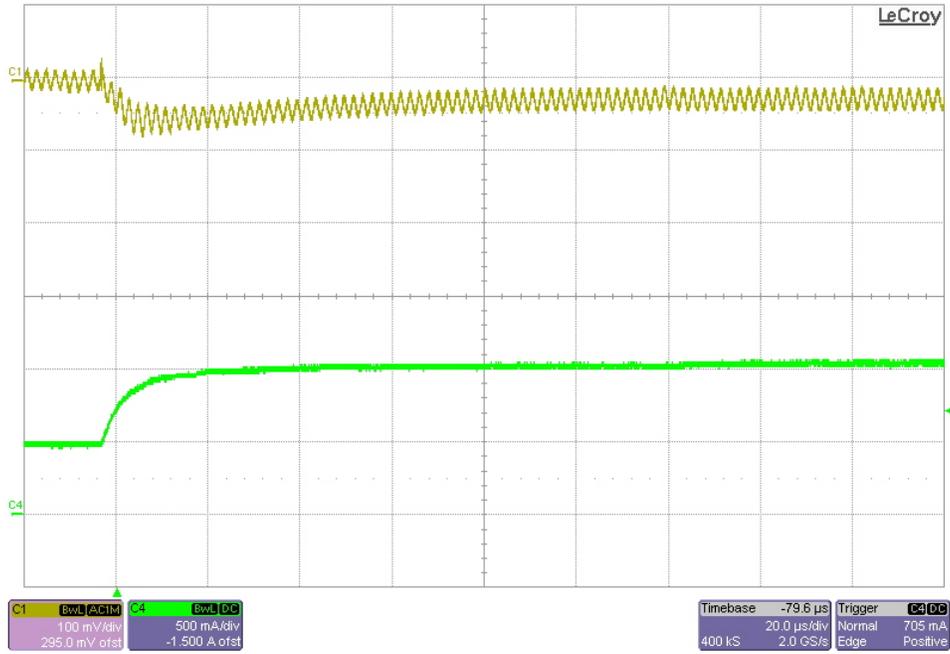


8.6 1A to 500mA

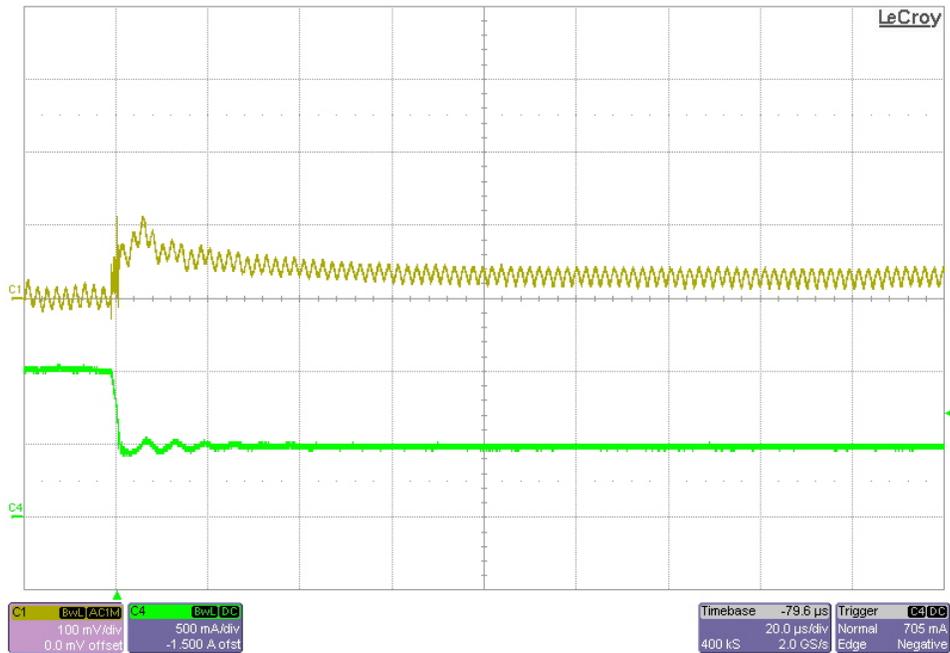


8.7 1A to 1.5A

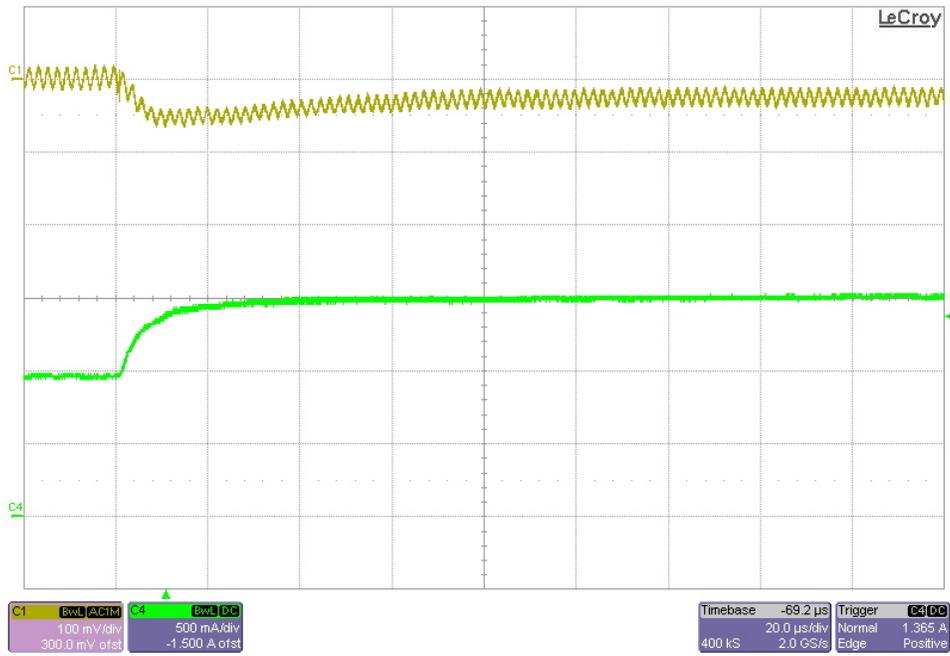


8.8 1.5A to 1A

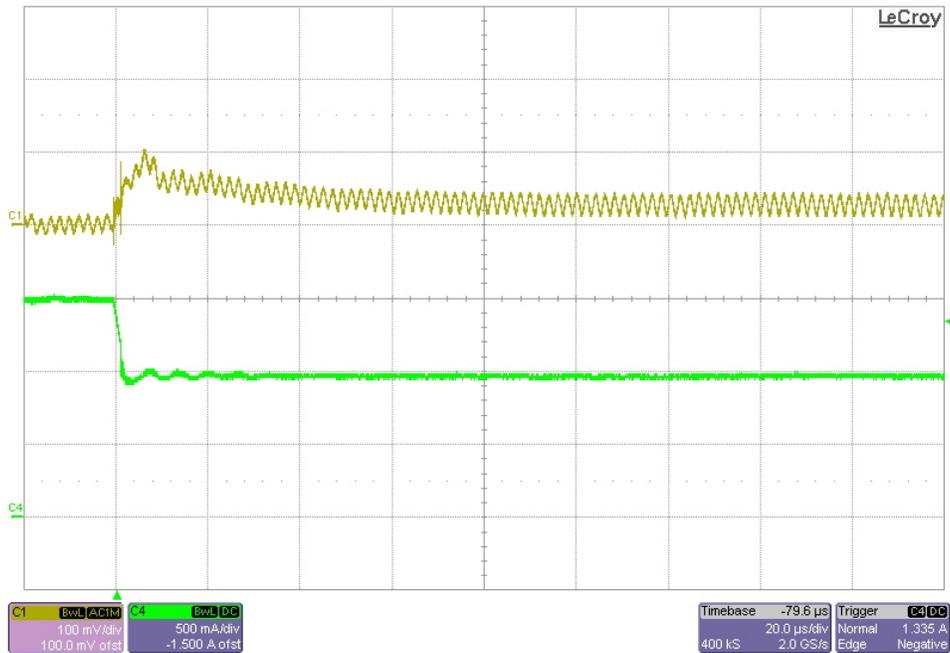

8.9 1.5A to 2.1A

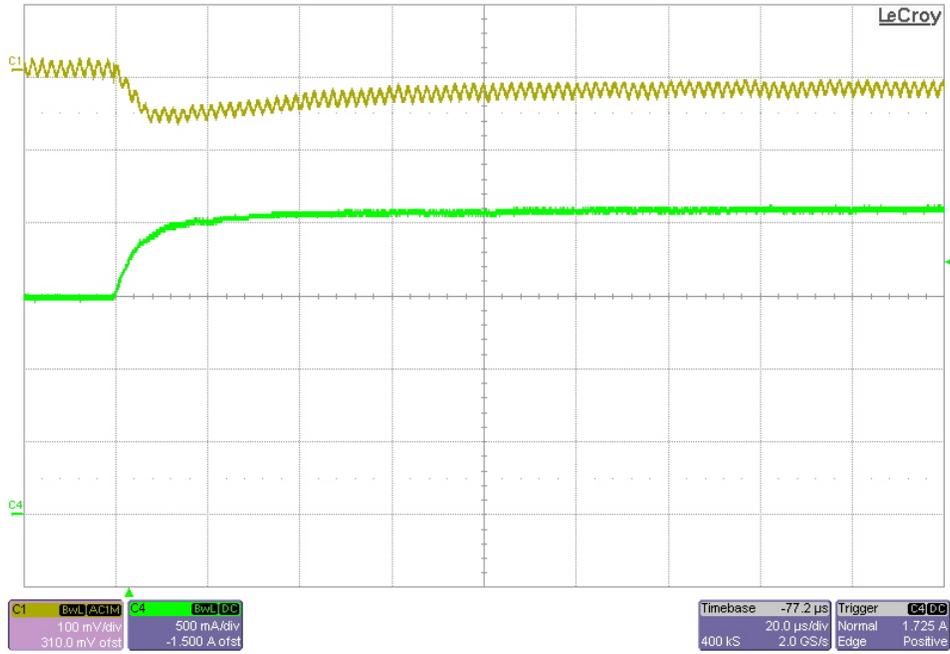


8.10 2.1A to 1.5A

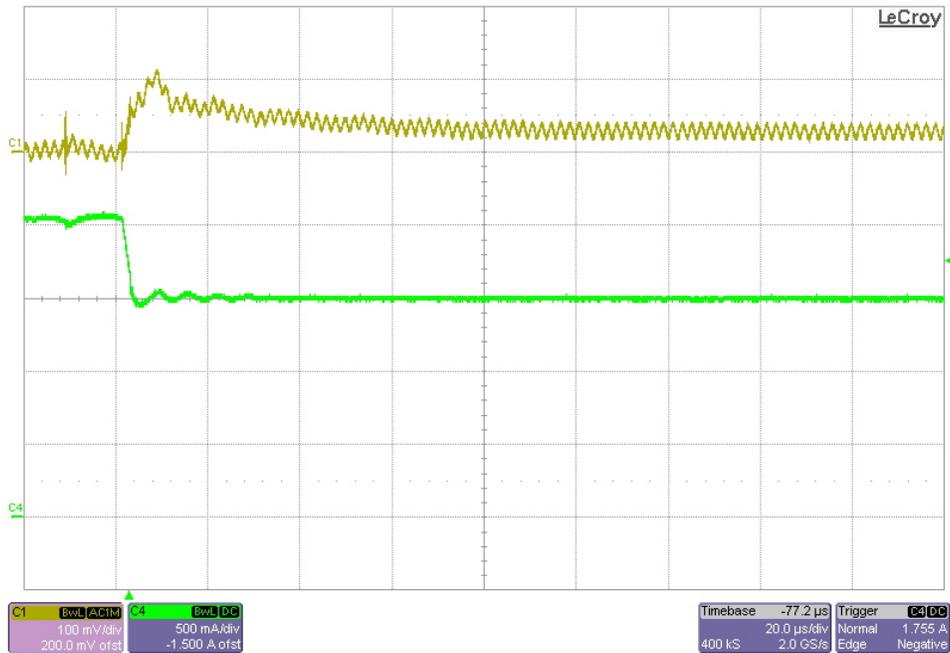


9 Short Circuit Protection

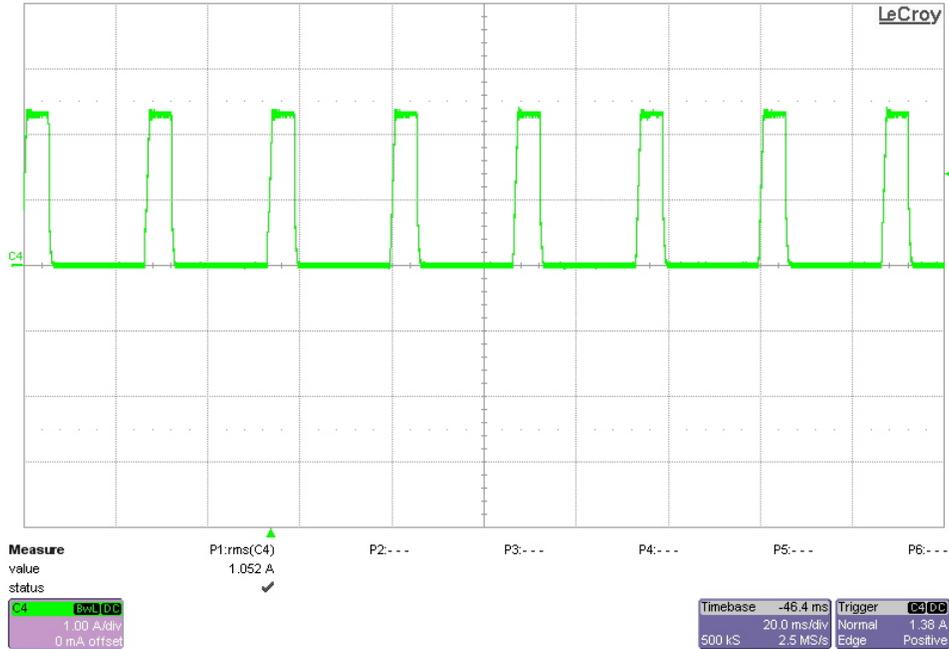The output current waveform is shown below for an over-loaded condition. The input was 12V.



10 Output Over-Voltage

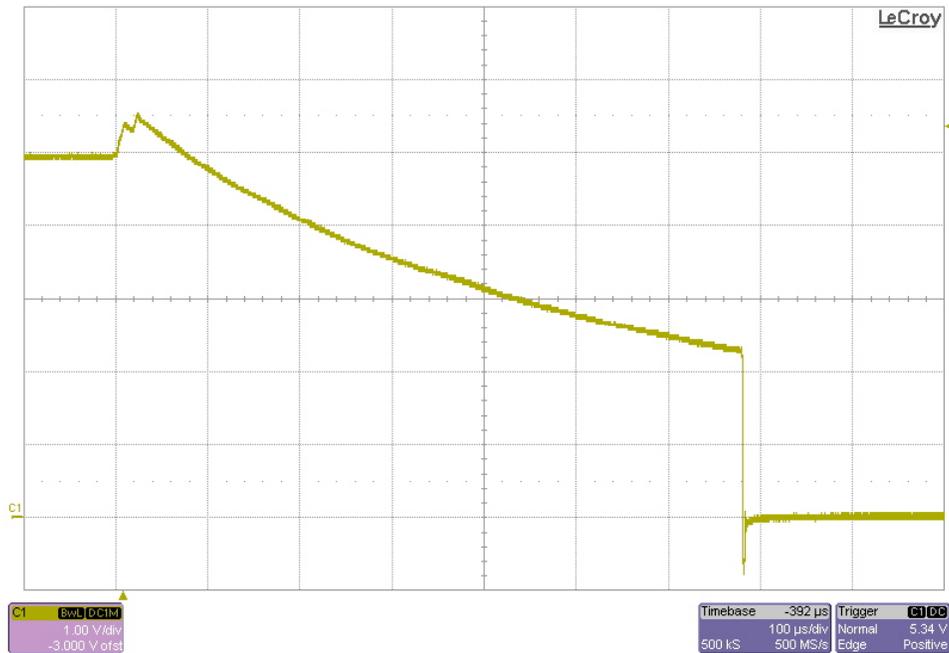
The image below shows the output voltage during an over voltage condition. The loop was broken at R15 allowing the output voltage to rise uncontrolled. The converter was latched off when the output voltage reached 5.5V. Cycling the input power allowed the converter to restart.




11 Switching Waveforms

The images below show the voltage waveform PH pin of the TPS54240. The input was 12V.

11.1 2.1A Load

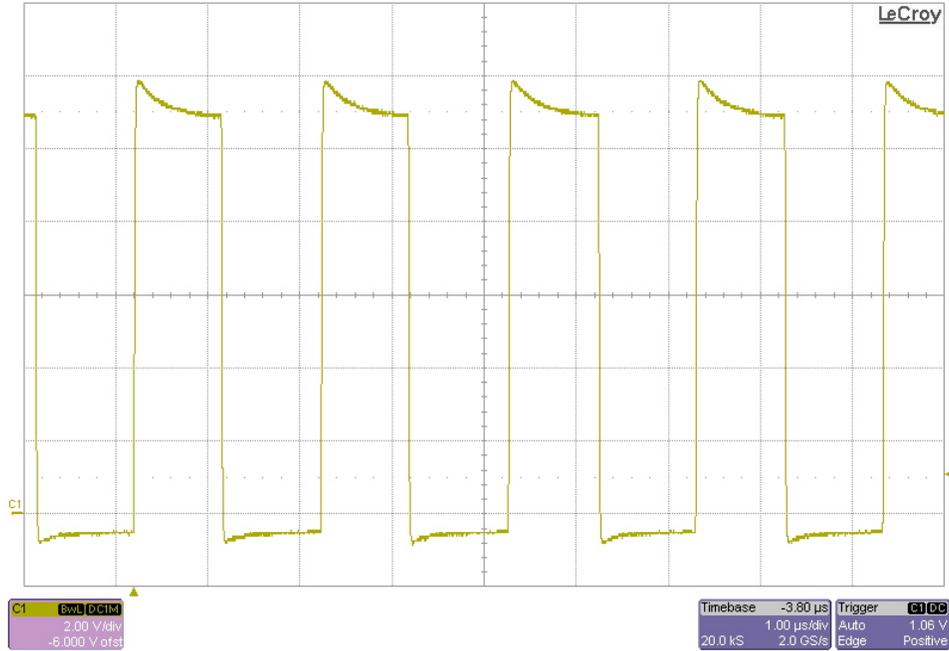

11.2 No Load

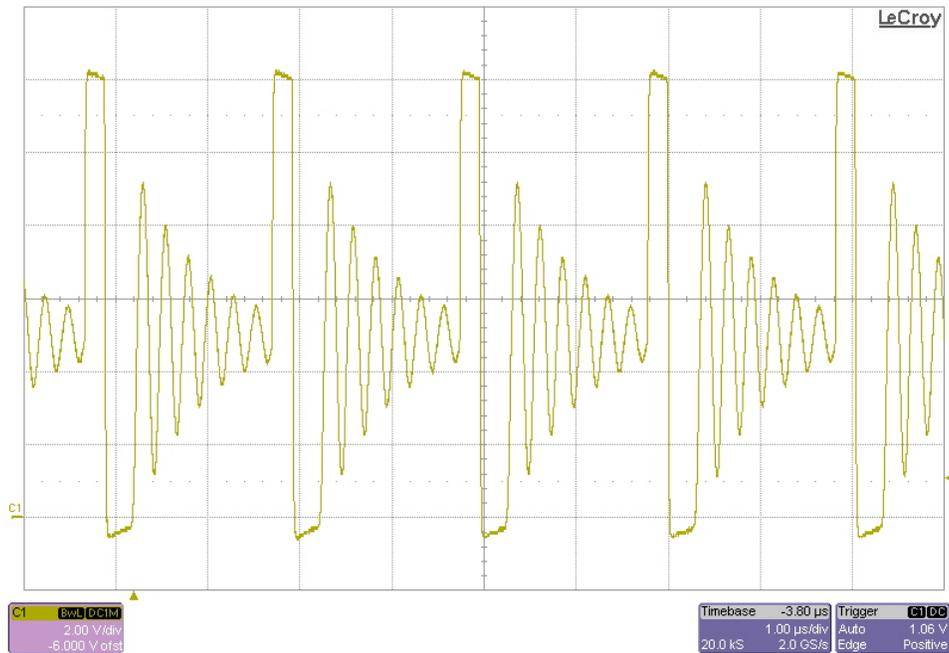

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated